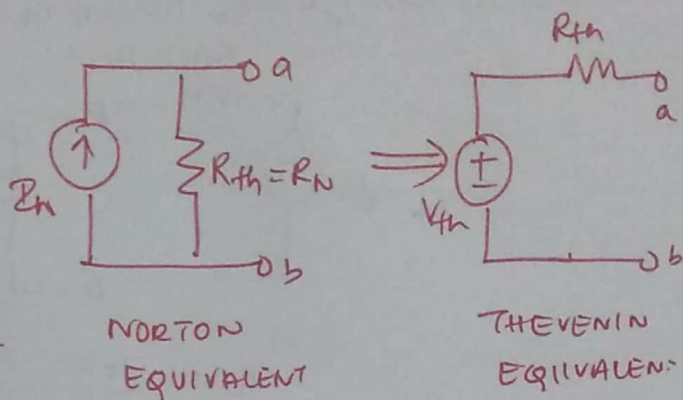


NORTON EQUIVALENT



- ① I_N = Norton Current
= Short circuit current
across the load.



Example

- ① Find the Norton Equivalent across the load

$$R_L = 5\Omega$$


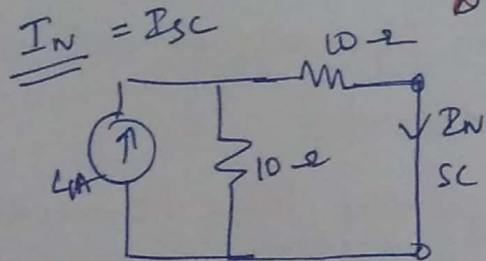
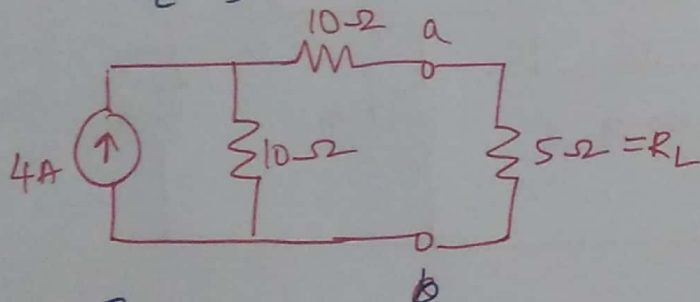


By current division.

$$I_N = 4 \times \frac{10}{10+10}$$


$$I_N = \frac{40}{20} = 2A$$

$R_N = R_{th}$ OC - current source

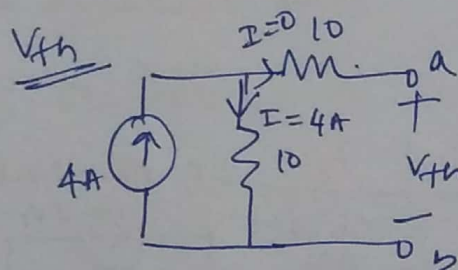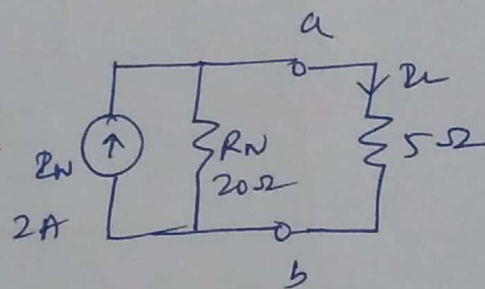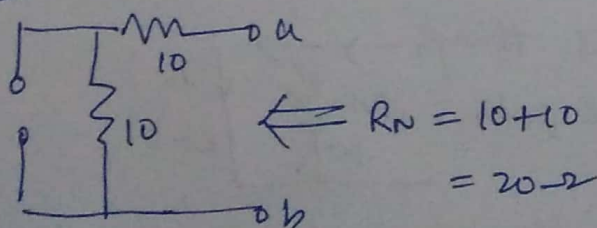

$$V_{th} = 4 \times 10 = 40V$$


THEVENIN EQUIVALENT

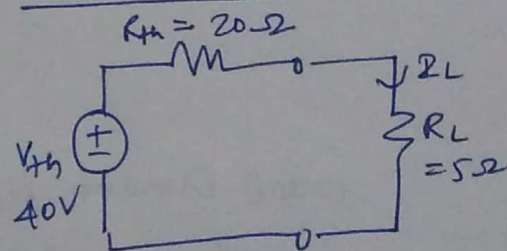

$$I_L = \frac{40}{20+5} = 1.6A$$

②

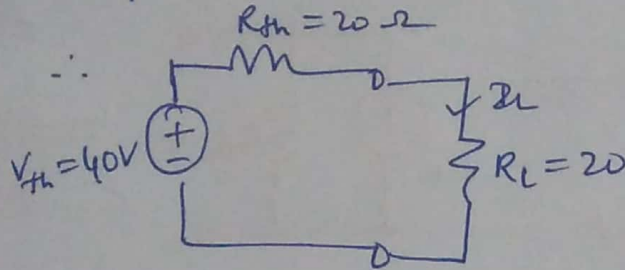maximum power transfer occurs when $R_L = R_{th} = 20\Omega$



$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$


$$= \frac{40^2}{4 \times 20}$$

$$I_L = \frac{40}{20+20} = 1A$$

$$P_{max} = I_L^2 R_L = 20W$$


$$P_{max} = 20W$$

②

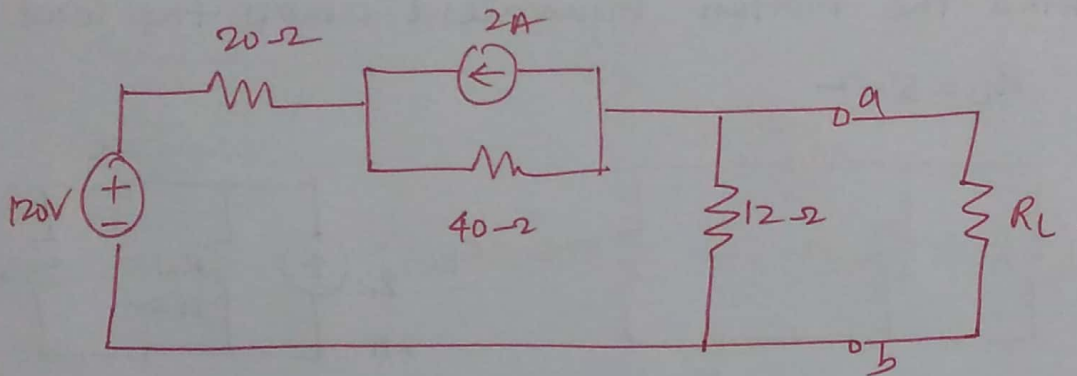

Find Thevenin & Norton Equivalents.
max power transferred?

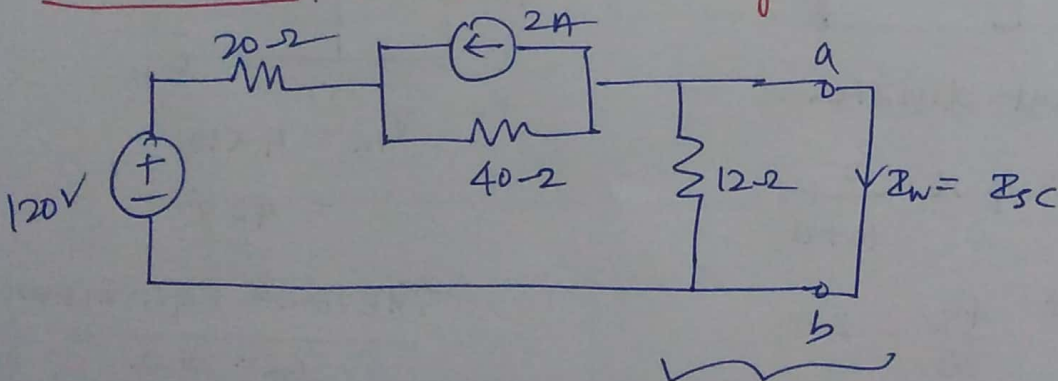To find I_{sc} : SC current through the load terminals.




Resistor in parallel to SC path
($R=0$)



entire current flows through the zero resistance path.
i.e (short circuit)

no current will flow through $R=12\Omega$, hence discarded.

(3)

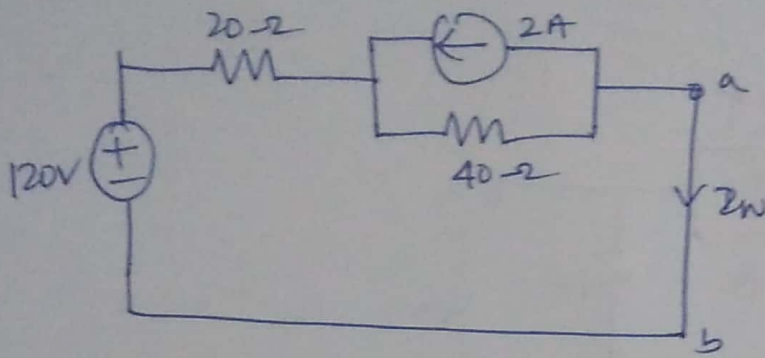

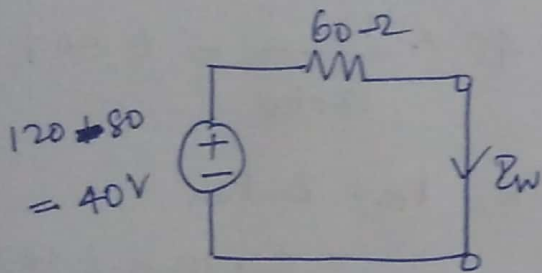
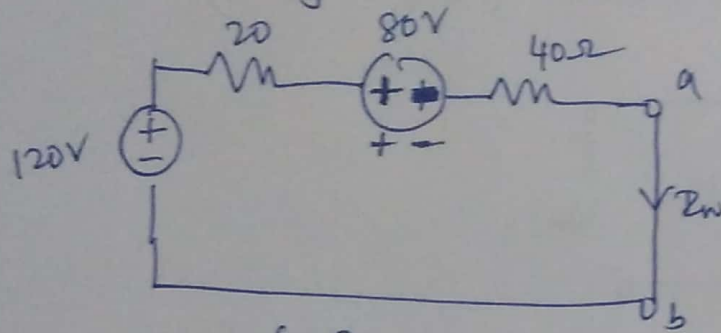
To simplify we source transformation, $V = 2 \times 40 = 80V$



$$I_{RN} = \frac{40}{60} = \frac{2}{3} A$$

To find R_{th} .

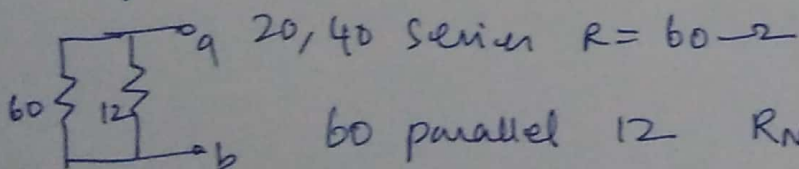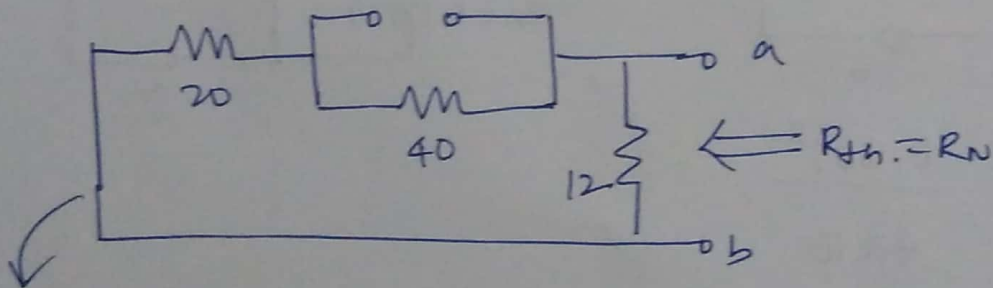
OC - current source, SC - voltage source.




$$R_N = \frac{12 \times 60}{12 + 60} = 10\Omega$$

④.

To find V_{th}

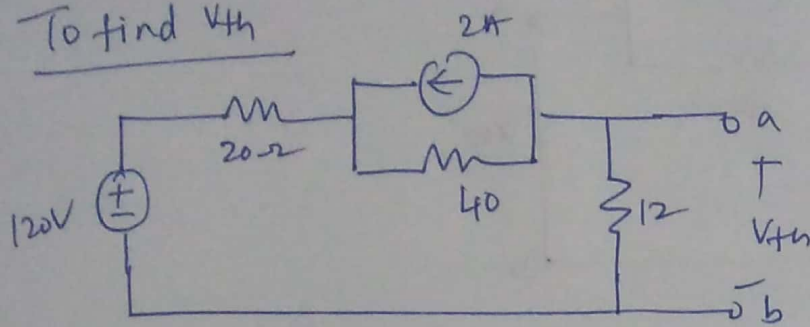


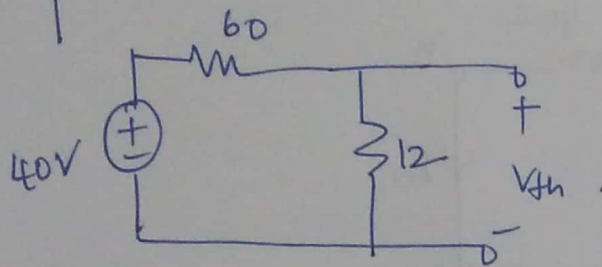
using the source transformation (see next)



By voltage division, $V_{th} = 40 \times \frac{12}{12+60} = 6.667 \text{ V}$

This can be verified using R_{th} , $V_{th} = R_{th} \cdot I_{N}$
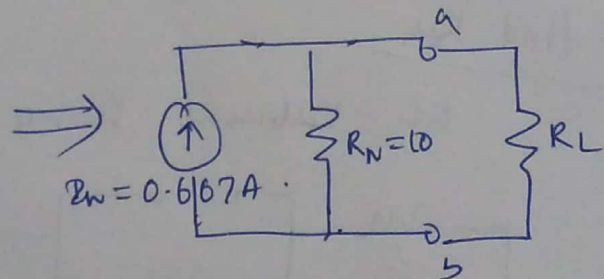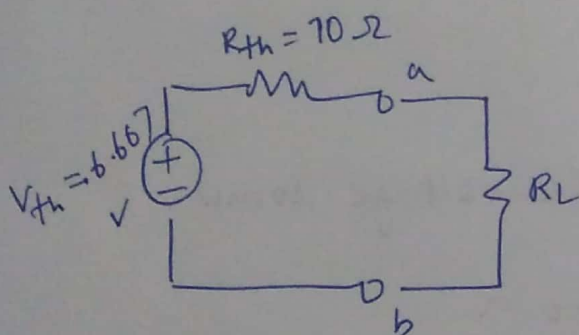
$$= \frac{2}{3} \times 10 = 6.667 \text{ V}$$



$$P_{max} = \frac{6.667^2}{4 \times 10}$$

$$= 1.1111 \text{ W}$$