

BEEE101L – Basic Electrical Engineering

Dr. R. GUNABALAN

Associate Professor

School of Electrical Engineering

Cabin No: 01, 7th floor, AB1 (nearer to Auditorium)

gunabalan.r@vit.ac.in

9894919269

Module 2 : AC Circuits

6 Hrs

Alternating voltages and currents, RMS, average, form factor, peak factor; Single phase RL, RC, RLC series and parallel circuits; Power and power factor; Balanced three phase systems


Course Outcome

- Evaluate AC circuit parameters using laws


j Operator

- $j = \sqrt{-1}$
- $j^2 = -1$
- $j^3 = -j$
- $j^4 = 1$

RL series circuit

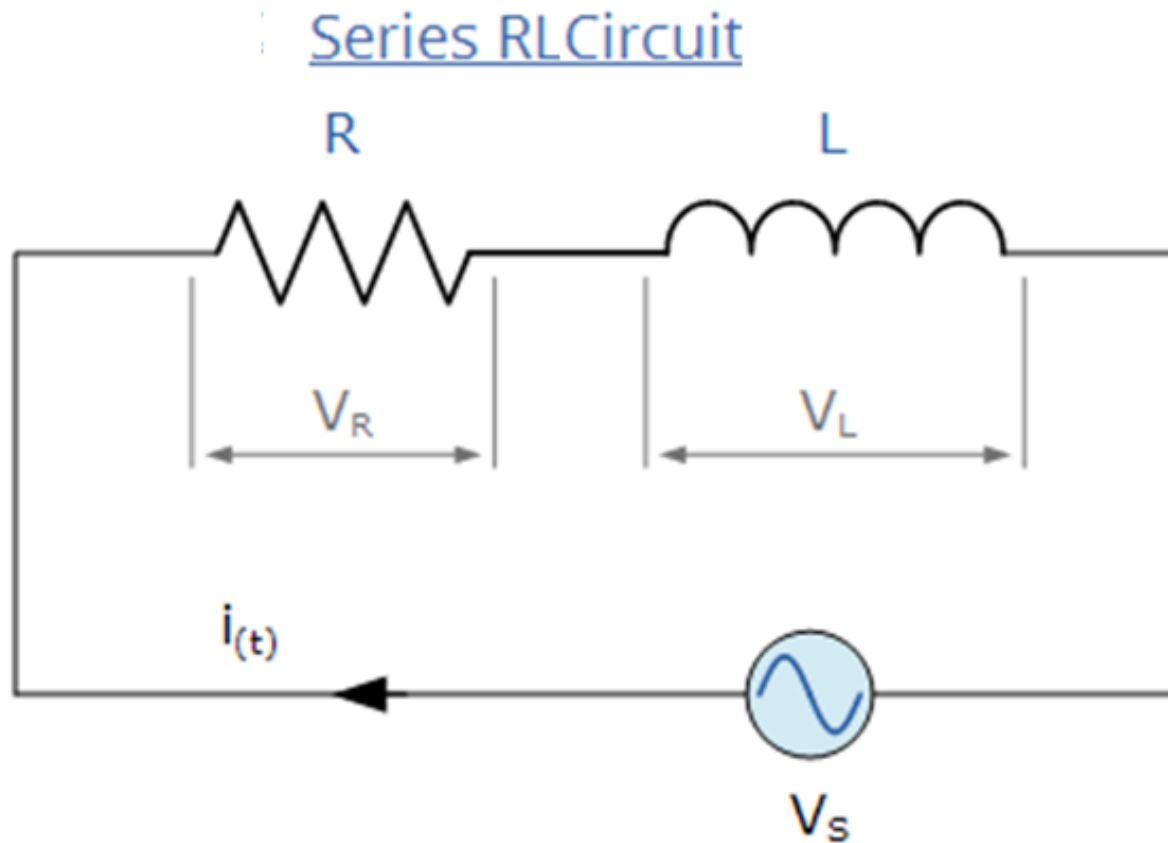


RL series circuit

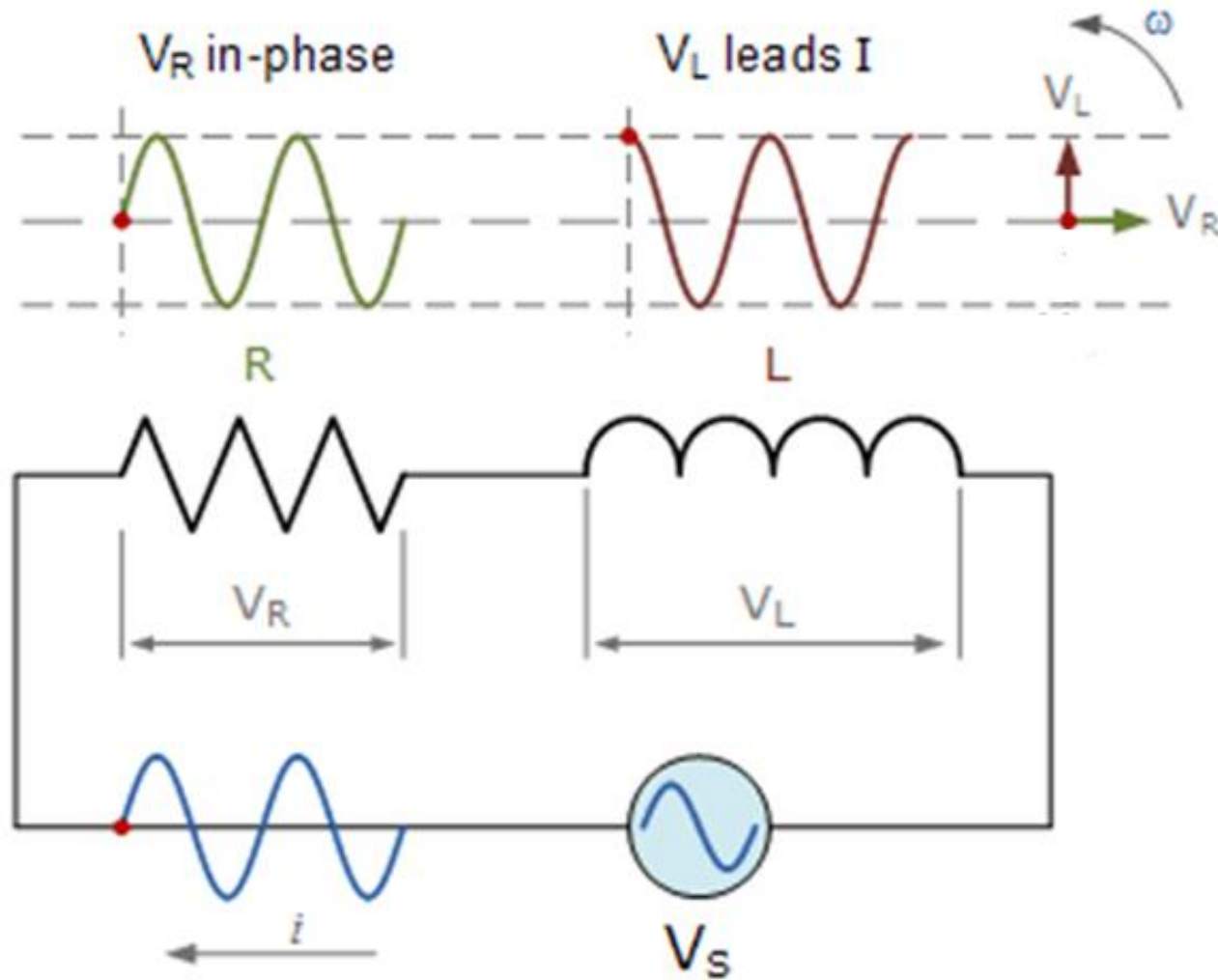


RL series circuit

Individual Voltage Vectors

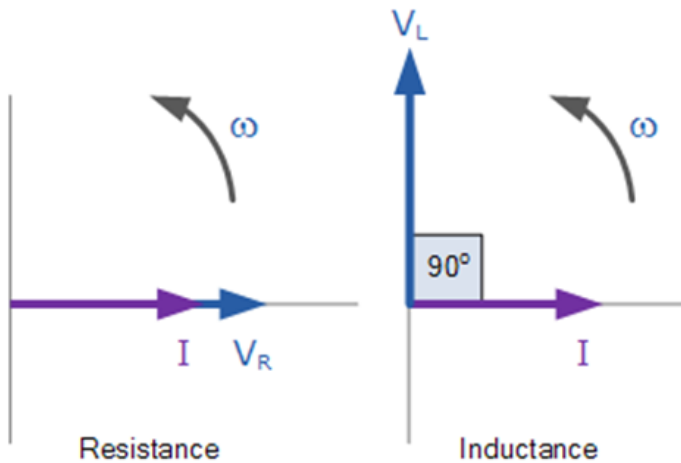

Phasor Diagram for a Series RL Circuit

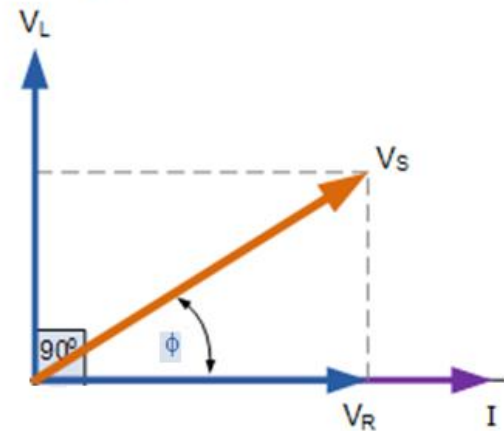

RL series circuit


$$V_R = I.R \quad V_L = jI.X_L$$

$$V_S = \sqrt{(I.R)^2 + (I.X_L)^2}$$


$$V_S = I.\sqrt{R^2 + (X_L)^2}$$

$$\therefore V_S = I \times Z \quad \text{where: } Z = \sqrt{R^2 + (X_L)^2}$$

Phasor Diagram for a Series RL Circuit

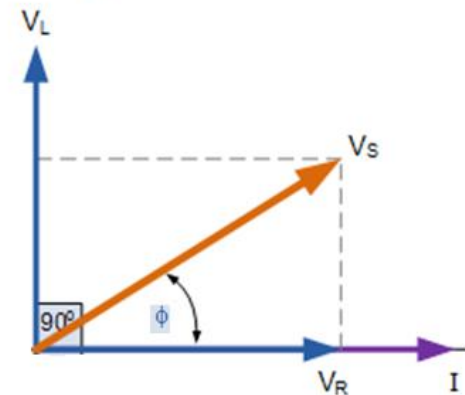

$$Z^2 = R^2 + (X_L)^2$$

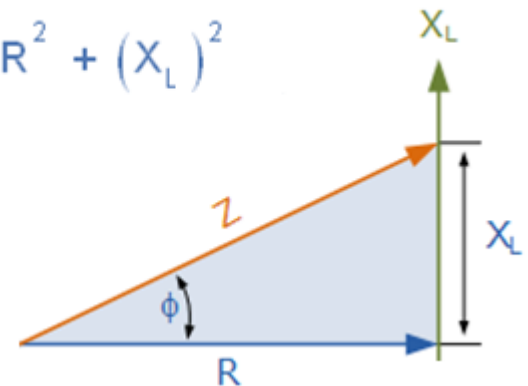


RL series circuit


- Impedance
- Phase diagram
- Impedance triangle
- Power factor
- Power

RC series circuit

Series RC Circuit


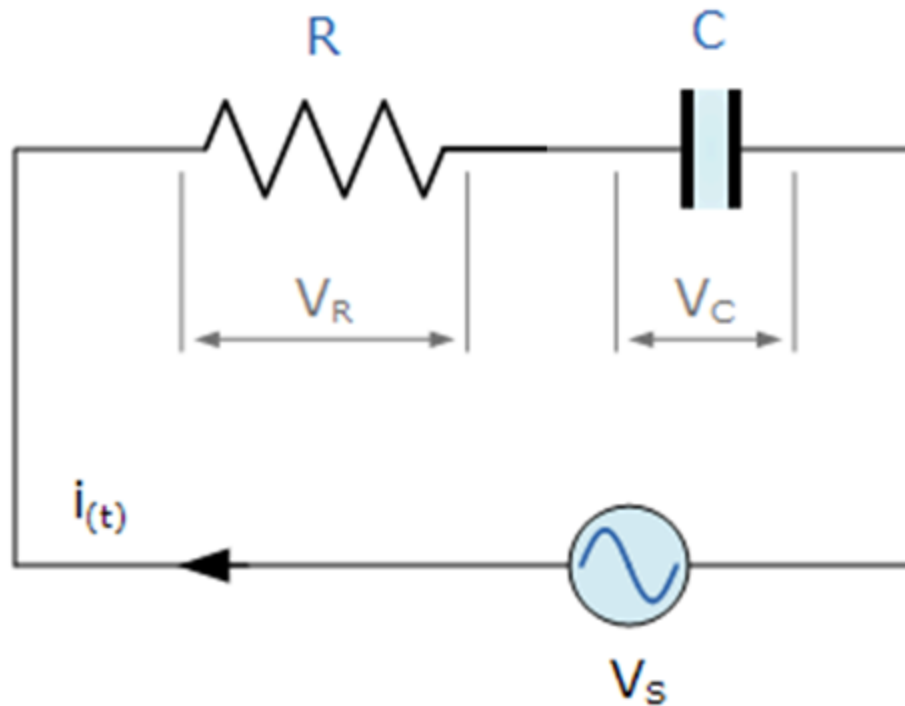


RC series circuit

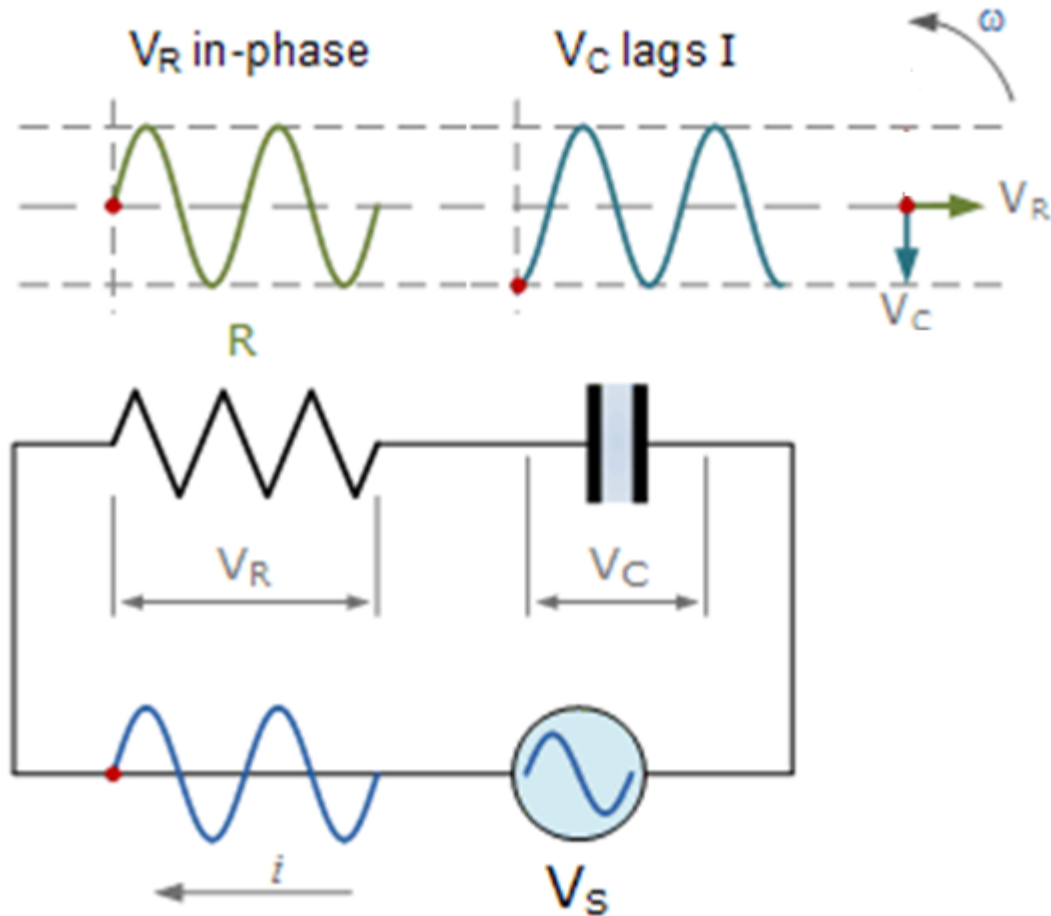

RC series circuit

Individual Voltage Vectors

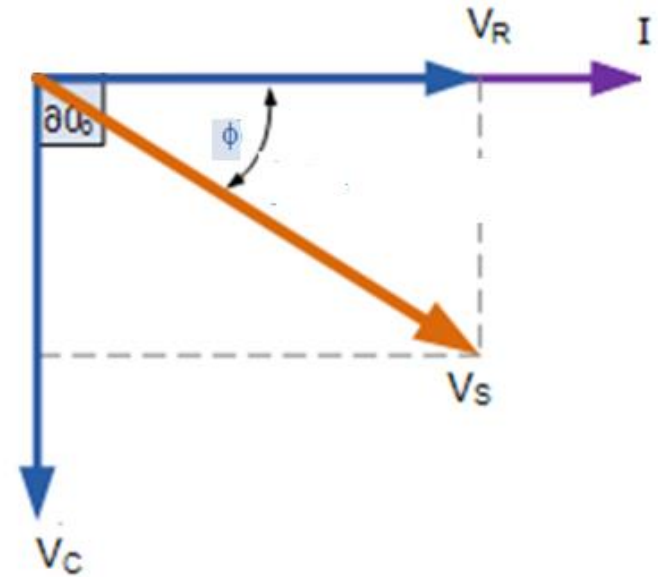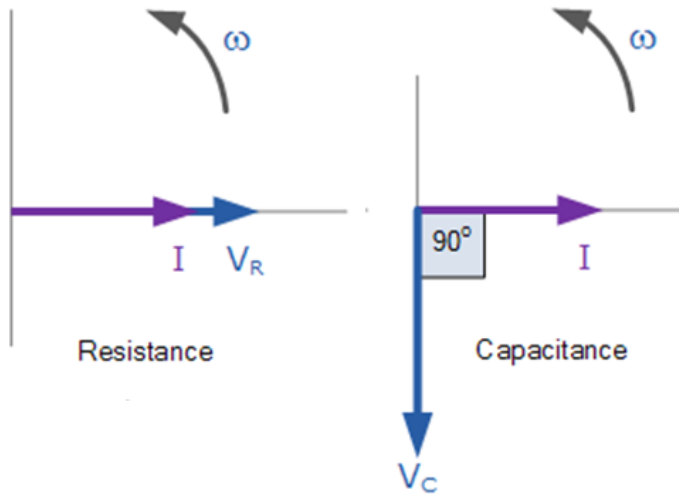


RC series circuit

$$V_R = I.R \quad V_C = -jI.X_C$$

$$V_S = \sqrt{(I.R)^2 + (I.X_C)^2}$$

$$V_S = I.\sqrt{R^2 + (X_C)^2}$$
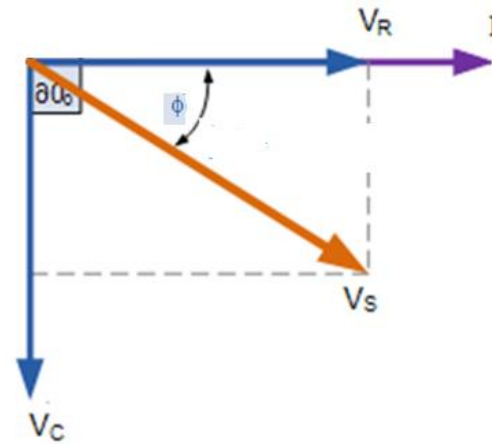
$$\therefore V_S = I \times Z \quad \text{where: } Z = \sqrt{R^2 + (X_C)^2}$$



RC series circuit

- Impedance
- Phase diagram
- Impedance triangle
- Power factor
- Power