

BEEE101L

Basic Electrical Engineering

L T P J C

2 0 0 0 2

Unit I


- **DC circuits:** Basic circuit elements and sources; Ohms law, Kirchhoff's laws; Series and parallel connection of circuit elements; Source transformation; Node voltage analysis; Mesh current analysis; Maximum power transfer theorem.

DC circuits

- A current that remains constant with time is called Direct Current (DC)
- Such current is represented by the capital I , time varying current uses the lowercase, i .
- A common source of DC is a battery.
- A current that varies sinusoidally with time is called Alternating Current (AC)
- Mains power is an example of AC



(a)

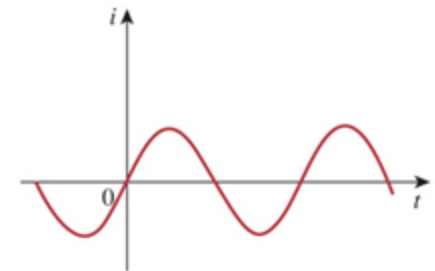

(b)

Systems of UNITS

Quantity	Basic Unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic Temperature	kelvin	K
Luminous intensity	candela	cd

The SI Prefixes

- Prefixes on SI units allow for easy relationships between large and small values


Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^2	hecto	h
10	deka	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

Charge

- **Charge** is a basic SI unit, measured in **Coulombs (C)**
- Charge of single electron is 1.602×10^{-19} C
- One Coulomb is quite large, 6.24×10^{18} electrons.
- In the lab, one typically sees (pC, nC, or μ C)
- Charge is always multiple of electron charge
- Charge cannot be created or destroyed, only transferred.

Electric Current

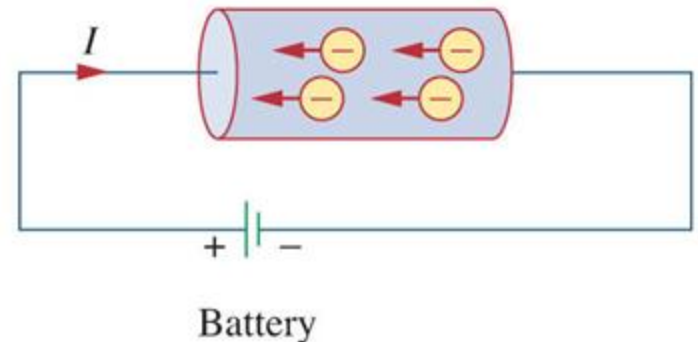- The movement of charge is called a current
- Historically the moving charges were thought to be positive
- Thus we always note the direction of the equivalent positive charges, even if the moving charges are negative.



Electric Current

- Current, i , is measured as charge moved per unit time through an element.


$$i \equiv \frac{dq}{dt}$$

- Unit is Ampere (A), is one Coulomb/second
- A positive current through a component is the same as a negative current flowing in the opposite direction.



The passive sign convention

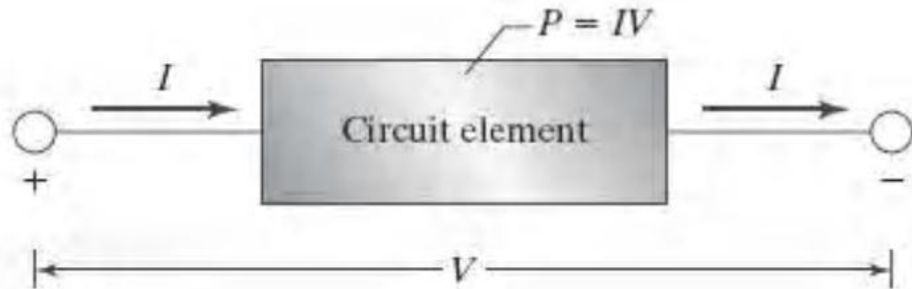- When we observe that positive current enters the positive terminal of a component, we say that the component obeys the passive sign convention (PSC).
- Therefore, when the passive sign convention is being obeyed, it indicates that a component is dissipating energy (or power) as charge is being displaced from a higher potential to a lower potential.



Voltage

- Electrons move when there is a difference in charge between two locations.
- This difference is expressed as the potential difference, or voltage (V).
- It is always expressed with reference to two locations.
- It is equal to the energy needed to move a unit charge between the locations.
- Positive charge moving from a higher potential to a lower yields energy.
- Moving from negative to positive requires energy.

Power

- Power: time rate of expending or absorbing energy
- Denoted by p
- Circuit Elements that *absorb power* have a positive value of p
- Circuit Elements that *produce power* have a negative value of p

$$p = \frac{dw}{dt}$$

$$p = \mp vi$$

$p =$ power in watts ($\text{W} = \text{J/s}$)

$w =$ energy in joules (J)

$t =$ time in seconds (s)

$v =$ voltage in volts (V)

$i =$ current in amperes (A)

Typical average monthly consumption of household appliances.

Appliance	kWh consumed	Appliance	kWh consumed
Water heater	500	Washing machine	120
Freezer	100	Stove	100
Lighting	100	Dryer	80
Dishwasher	35	Microwave oven	25
Electric iron	15	Personal computer	12
TV	10	Radio	8
Toaster	4	Clock	2

Energy

- *Law of Conservation of Energy*: the net power absorbed by a circuit is equal to 0.
- In other words, the total energy produced in a circuit is equal to the total energy absorbed
- *Energy*: capacity to do work, measured in joules (J)

$$w = \int_{t_0}^t p \, dt = \int_{t_0}^t (\pm vi) \, dt$$


If current and voltage are constant (DC),

$$w = \int_{t_0}^t p \, dt = p(t - t_0)$$


Circuit Elements

- **Ideal Independent Source:** provides an active element with specified voltage or current that is completely independent of other circuit variables
- **Ideal Independent**

Voltage Source:

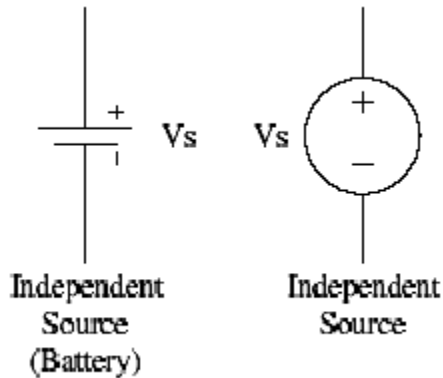

Current Source

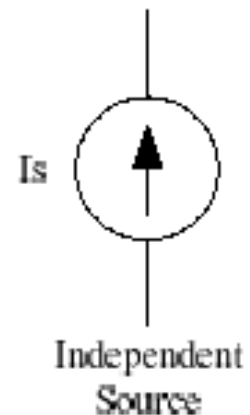

Circuit Elements


- An ideal dependent (or controlled) source is an active element in which the source quantity is controlled by another voltage or current.
- Diamond symbols
- Ideal dependent voltage source



Current source




Dependent Source example

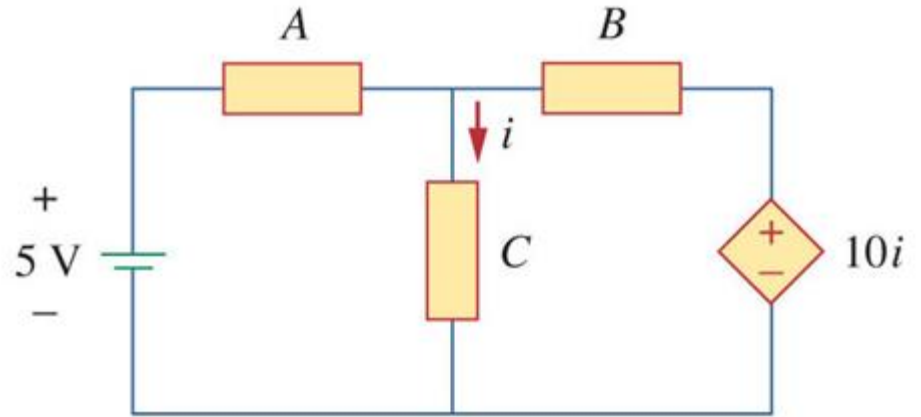

- Types:

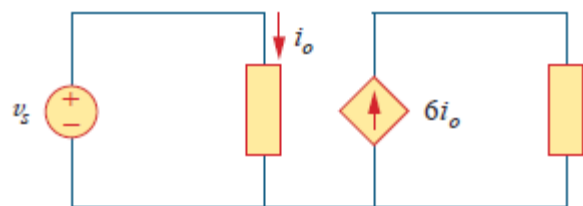
1. A Voltage Controlled Voltage Source (VCVS)
2. A Current Controlled Voltage Source (CCVS)
3. A Voltage Controlled Current Source (VCCS)
4. A Current Controlled Current Source (CCCS)




Basic circuit Elements

- Resistors
- Inductors
- Capacitors


Structure of carbon composition resistor

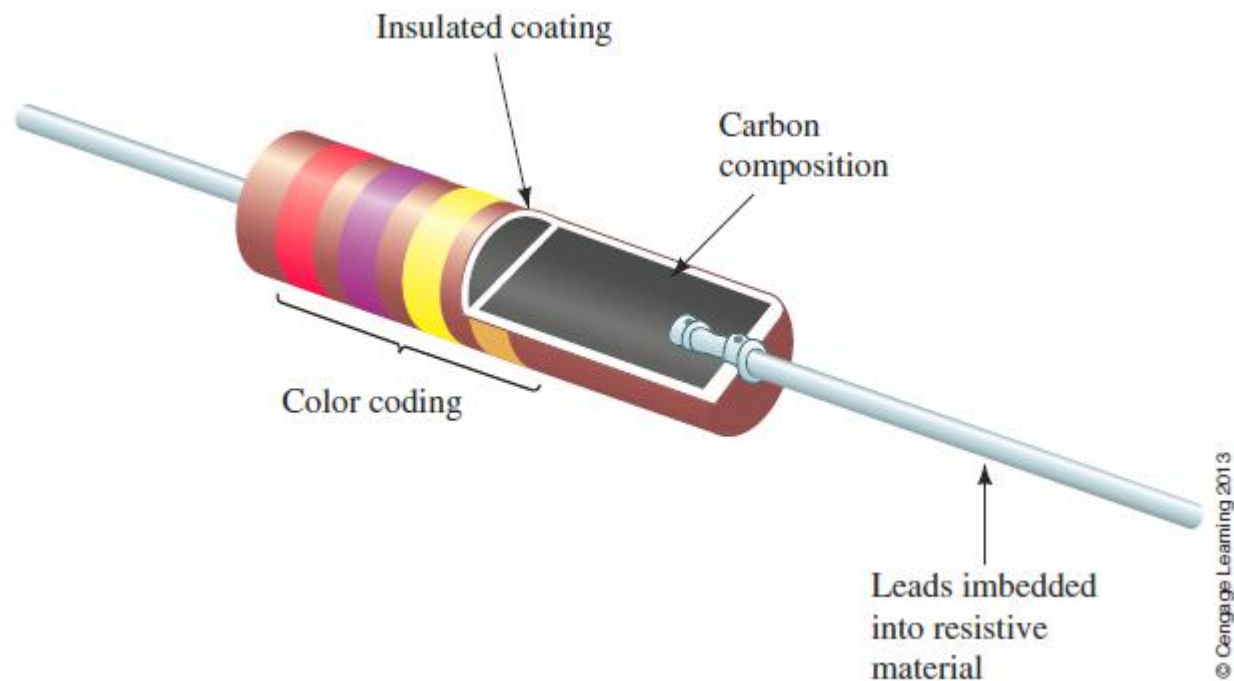

Size- 2W, 1W, 1/2W, 1/4W, 1/8W

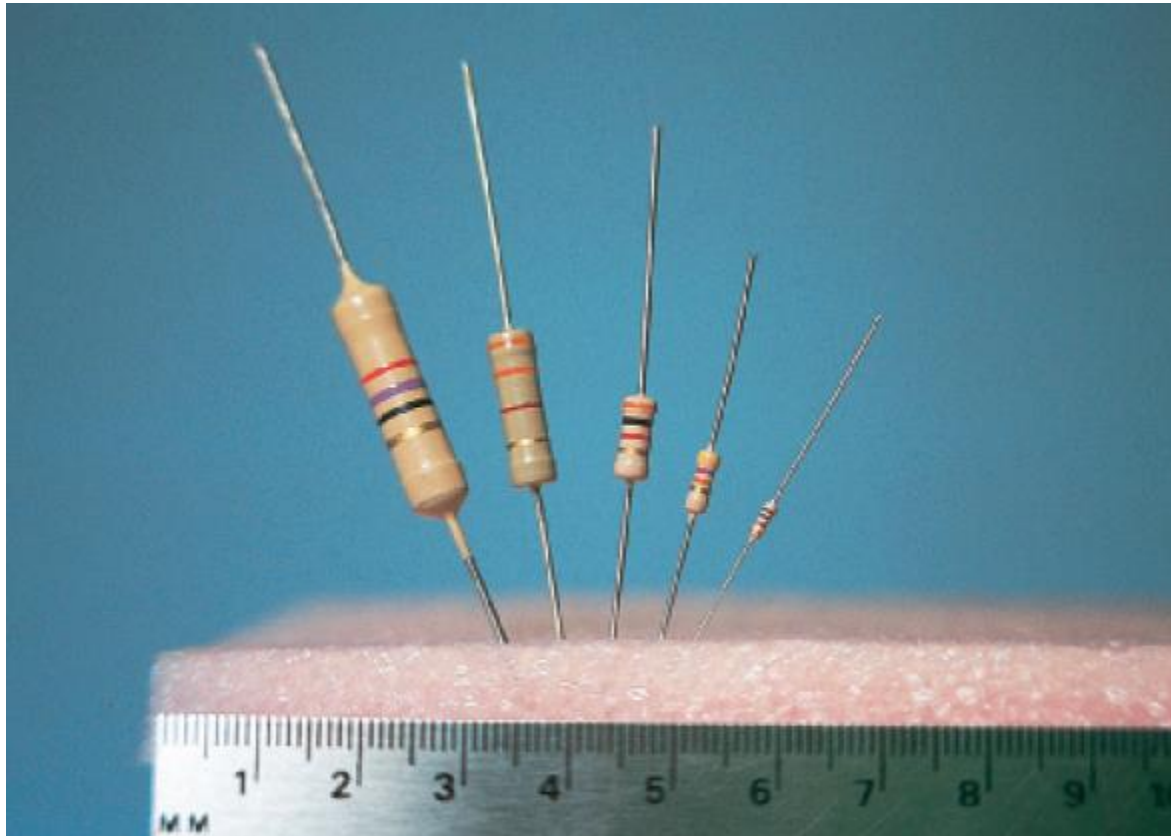


Power resistors

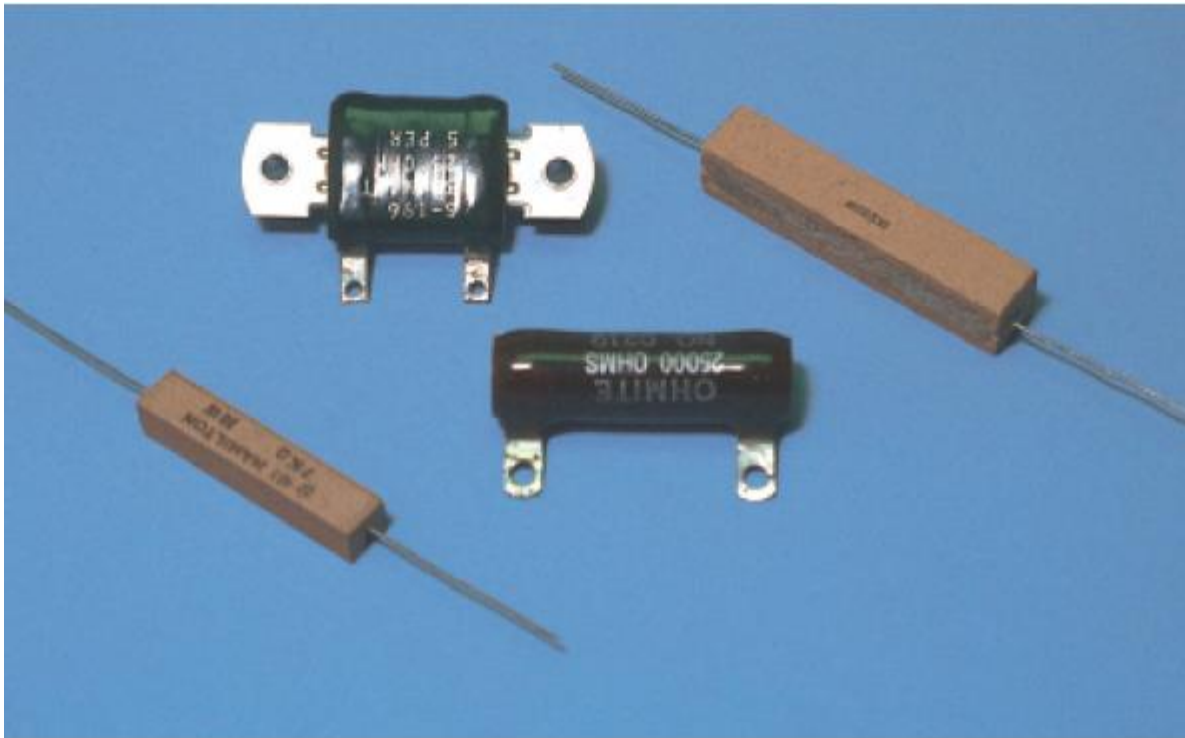

Variable resistor



(a) External view of variable resistors

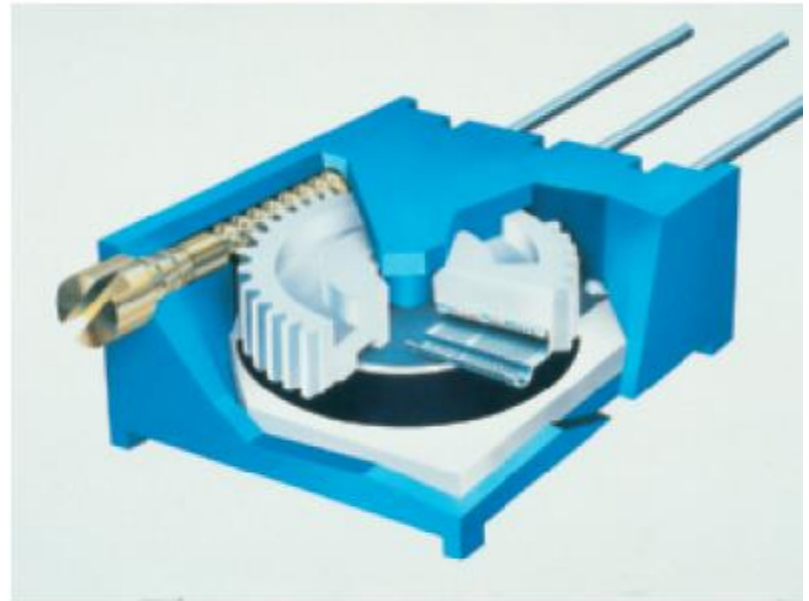


(b) Internal view of variable resistor

■ Component values

<p> </p> <p> 0 1 2 3 4 5 6 7 8 9 0 Black 1 Brown 2 Red 3 Orange 4 Yellow 5 Green 6 Blue 7 Purple 8 Grey 9 White ±1% Brown ±2% Red ±5% Gold ±10% Silver </p>	<p> </p> <p> 27K EXAMPLE 0 X1 1 1 X10 2 2 X100 3 3 X1000 4 4 X10000 5 5 X100000 6 6 X1000000 7 7 ÷10 8 8 ÷100 9 9 </p>	<p> </p> <p> 15K EXAMPLE 0 0 X1 1 1 1 X10 2 2 2 X100 3 3 3 X1000 4 4 4 X10000 5 5 5 ÷10 6 6 6 ÷100 7 7 7 8 8 8 9 9 9 </p>	<p> </p> <p> 620K EXAMPLE 0 0 X1 1 1 1 X10 2 2 2 X100 3 3 3 X1000 4 4 4 X10000 5 5 5 ÷10 6 6 6 ÷100 7 7 7 8 8 8 9 9 9 </p>
<p>Color Codes</p>	<p>4 Band Resistors</p>	<p>5 Band Resistors</p>	<p>6 Band Resistors</p>

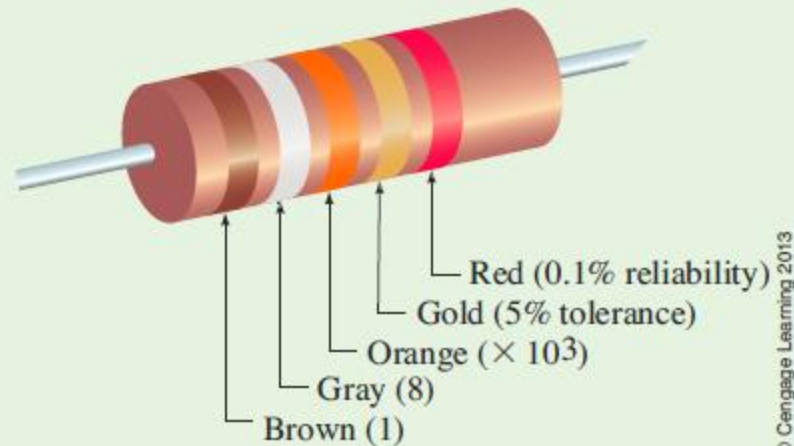Determine the resistance of a carbon film resistor having the color codes shown in Figure 3–17.




From Table, we see that the resistor will have a value determined as

$$R = 18 \times 10^3 \text{ ohm} \pm 5\%$$
$$= 18 \text{ k} \pm 0.9 \text{ k with a reliability of } 0.1\%$$



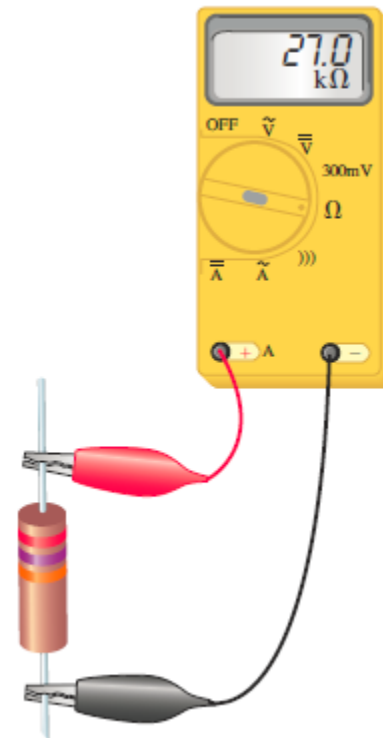Digital multimeter. To measure ohms, set the dial to Ω .





© Cengage Learning 2013

Ohmmeter used to measure an isolated component.


Capacitor / Capacitance (C - Farads)



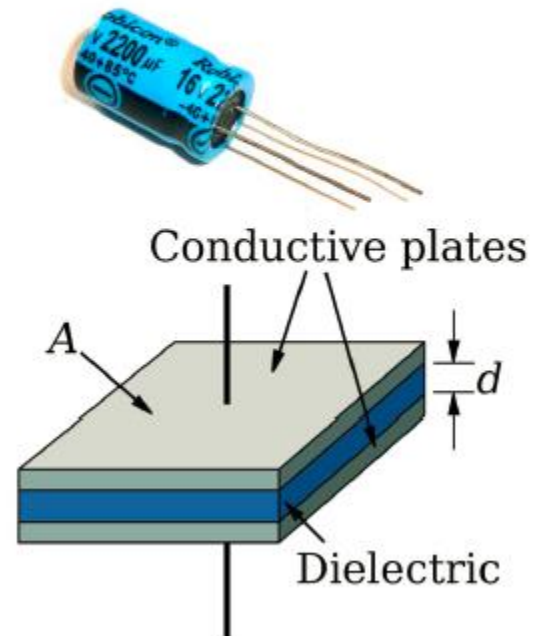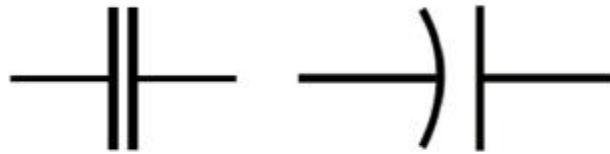





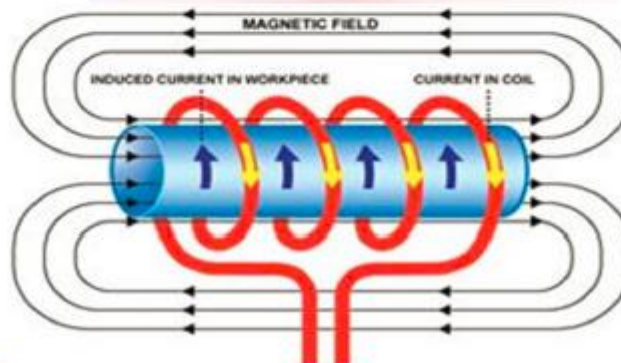




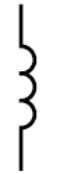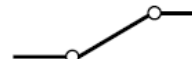
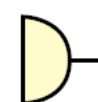
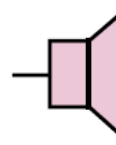

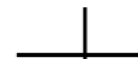
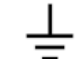
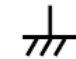


The property of being able to store electric charge












Inductor / Inductance (L - Henrys)

The property of a circuit by which a change in current induces an electromotive force by electro-magnetic induction.



 Single cell	 Multicell	 AC Voltage Source	 Current Source	 Fixed	 Variable	 Fixed	 Variable	 Air Core	 Iron Core	 Ferrite Core
Batteries				Resistors		Capacitors		Inductors		
 Lamp	 SPST  SPDT Switches		 Microphone	 Speaker	 Wires Joining	 Wires Crossing	 Earth  Chassis Grounds	  Fuses		

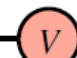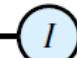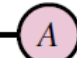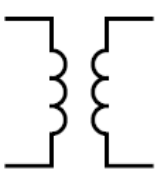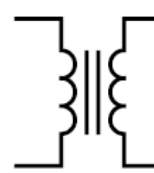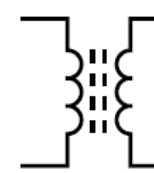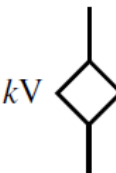
  Circuit Breakers	 Voltmeter  Ammeter  Ammeter	 Air Core	 Iron Core	 Ferrite Core	 Dependent Source
		Transformers			

Ohm's Law

- **Ohm's law** states that the voltage v across a resistor is directly proportional to the current i flowing through the resistor.
- The **resistance R** of an element denotes its ability to resist the flow of electric current; it is measured in ohms .

Resistivities of common materials.

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator


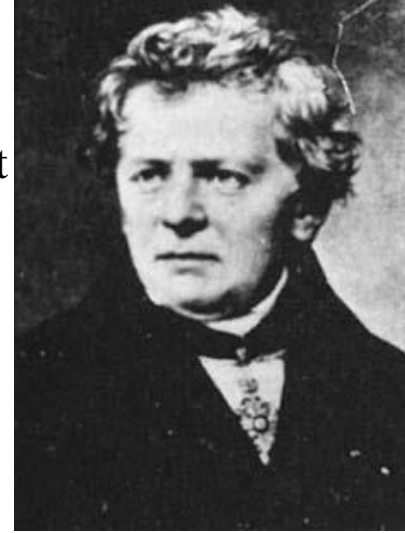


- **Georg Simon Ohm** (1787–1854), a German physicist, in 1826
- experimentally determined the most basic law relating voltage and current for a resistor. Ohm's work was initially denied by critics.
- **Andre-Marie Ampere** (1775–1836), a French mathematician and
- physicist, laid the foundation of electrodynamics. He defined the electric
- current and developed a way to measure it in the 1820s.



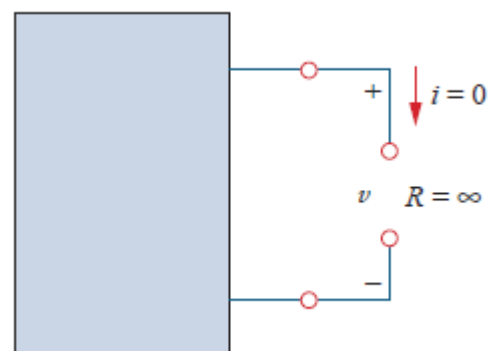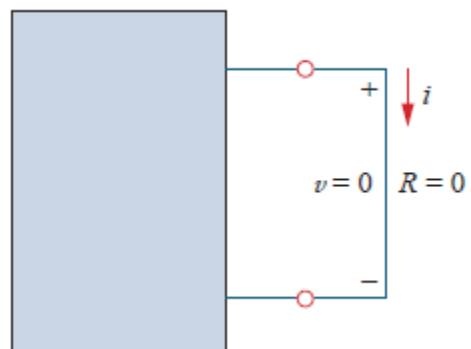- **Alessandro Antonio Volta** (1745–1827), an Italian physicist,
- invented the electric battery—which provided the first continuous flow
- of electricity—and the capacitor.






Kirchhoff's Laws

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

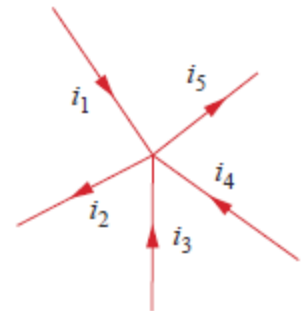- **Gustav Robert Kirchhoff** (1824–1887), a German physicist, s
- two basic laws in 1847 concerning the relationship between the c
- and voltages in an electrical network. Kirchhoff's laws, along
- with Ohm's law, form the basis of circuit theory.








Kirchhoff's Laws


- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

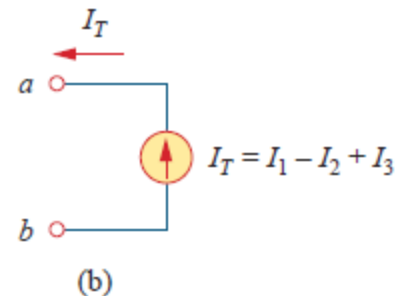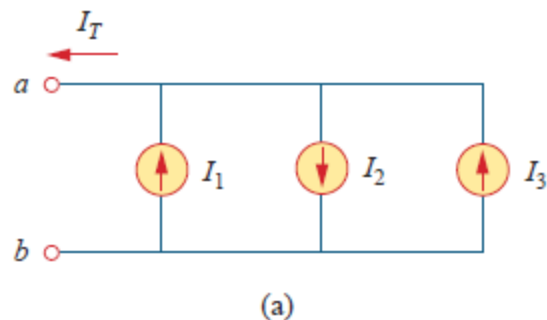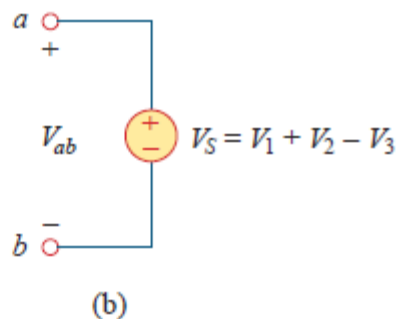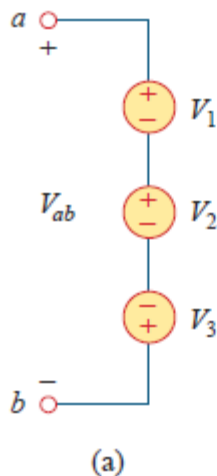
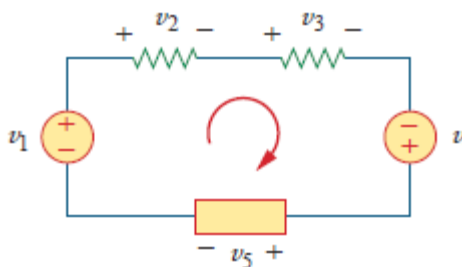
- Sum of voltage drops = Sum of voltage rises




Current division

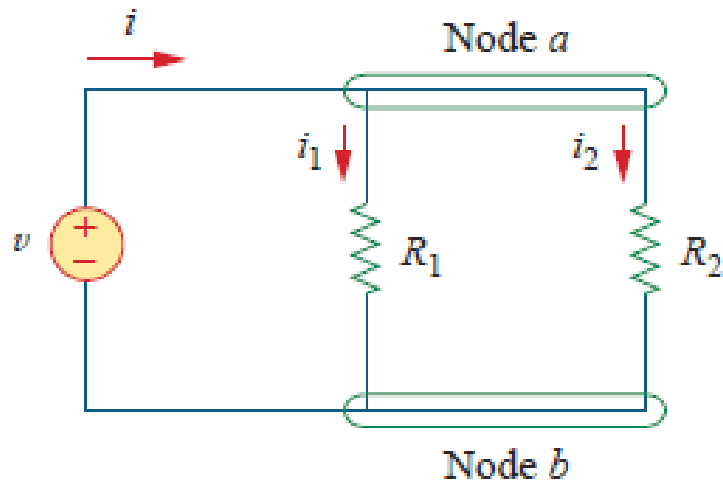
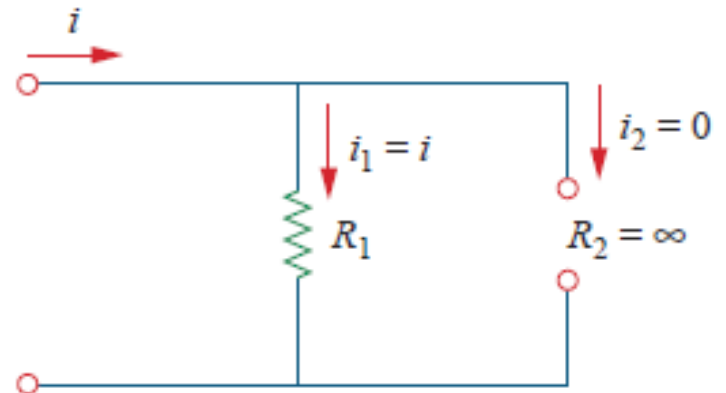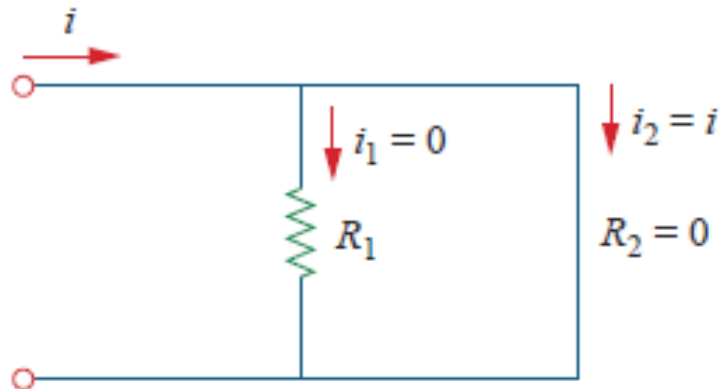
$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$







Voltage division

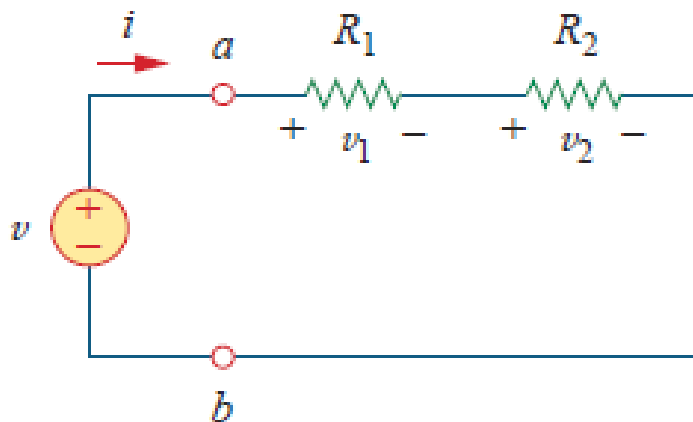


$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

Problems

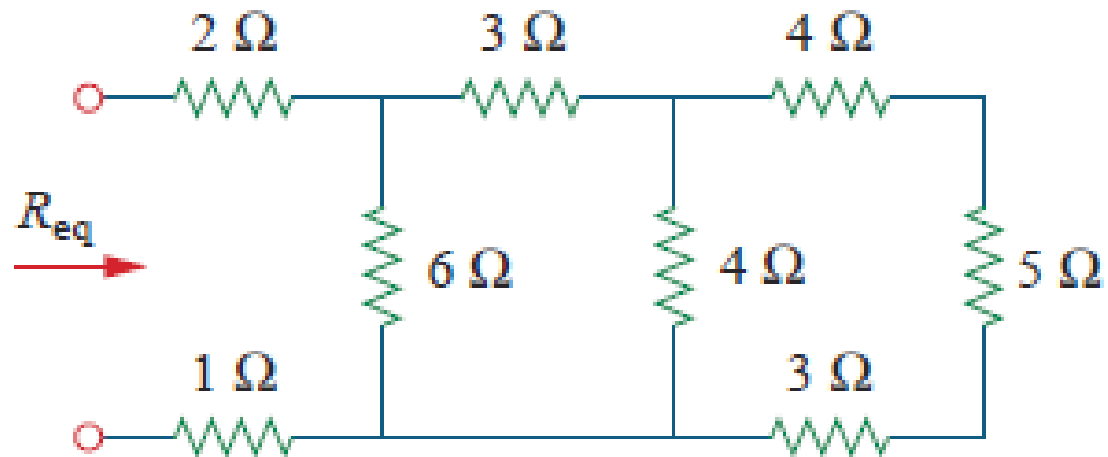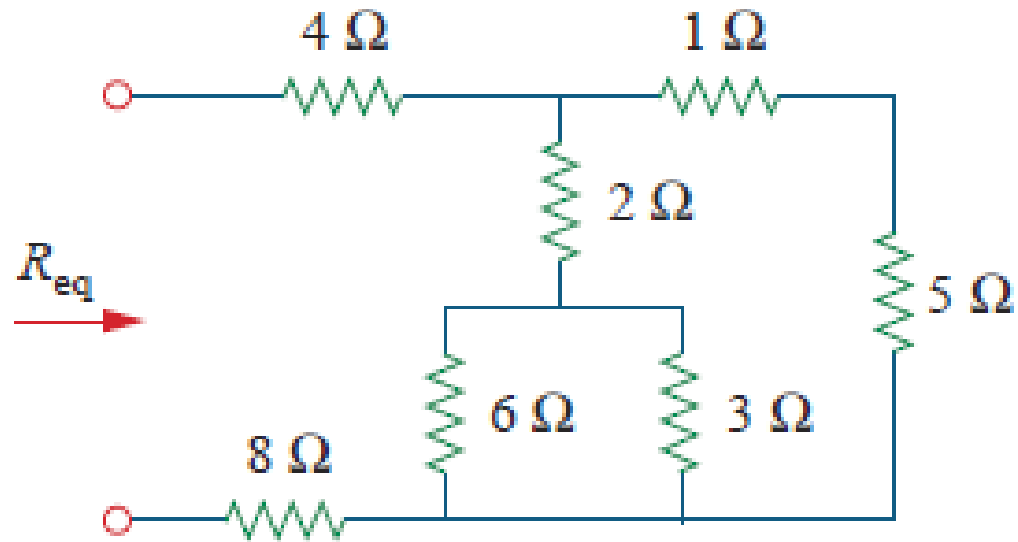


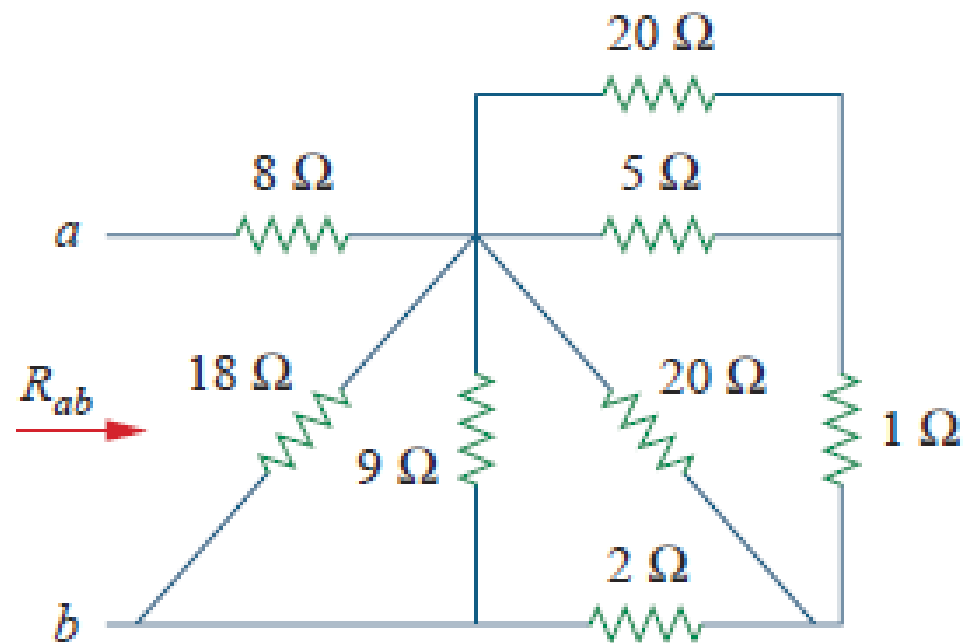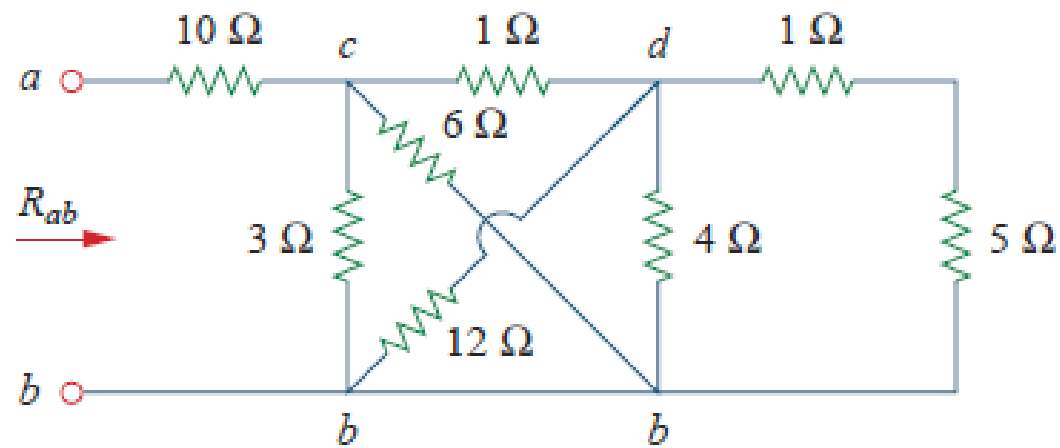


- Find the power across 3 ohm resistor

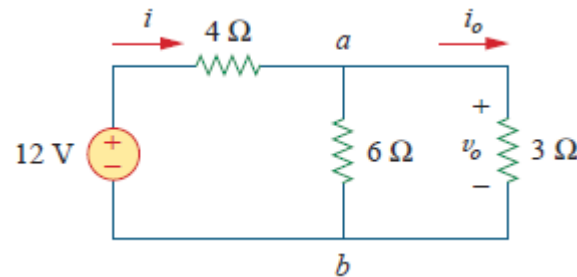

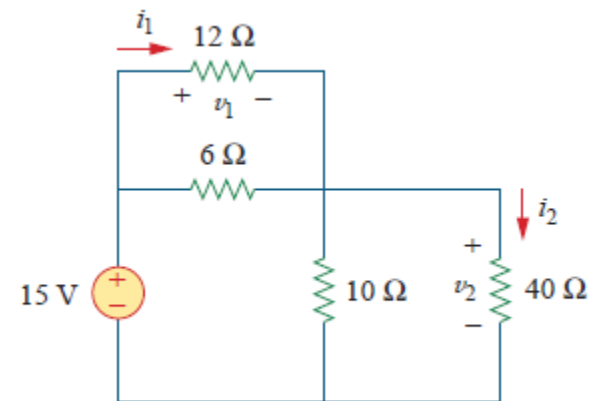- Find current, voltage and power across all the elements.




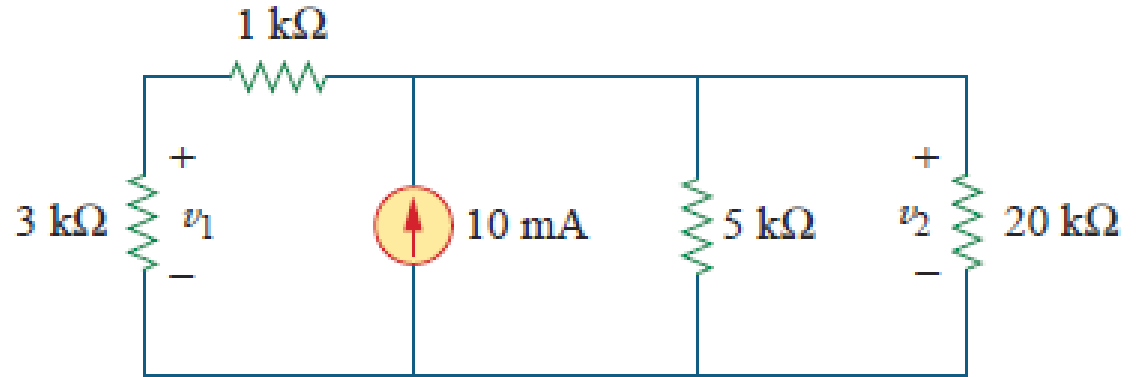- find: (a) and (b) the power dissipated in the 3-k and 20-k resistors, and (c) the power supplied by the current source.








- Find (a) the voltage v_o (b) the power supplied by the current source, (c) the power absorbed by each resistor.

•

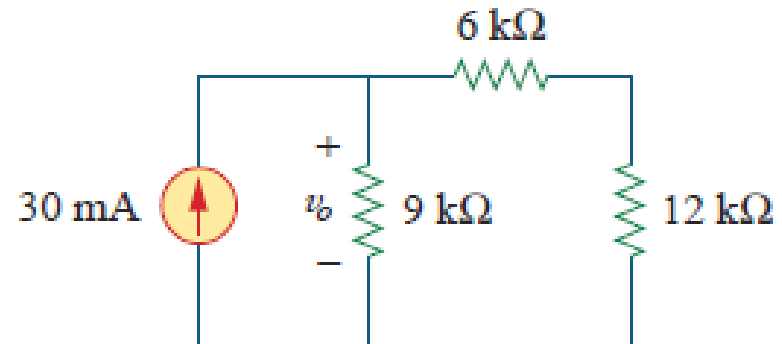

Wye-Delta Transformations

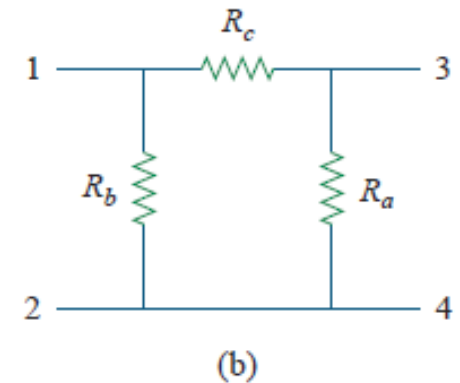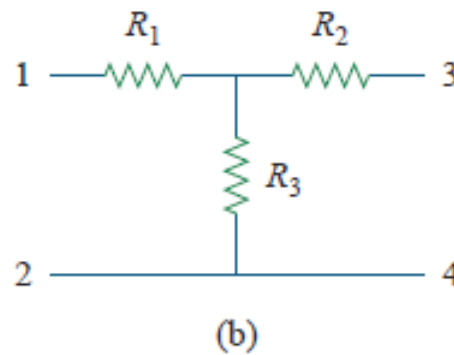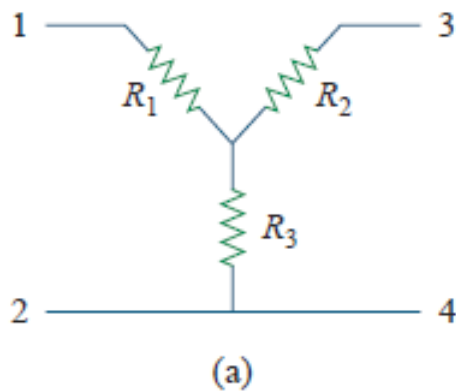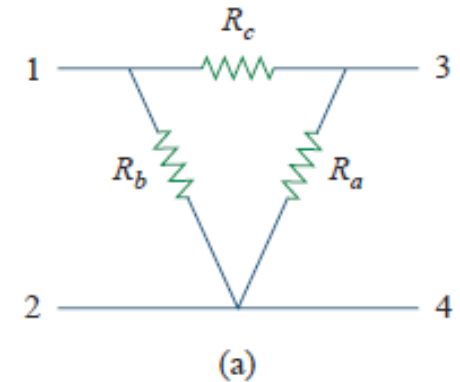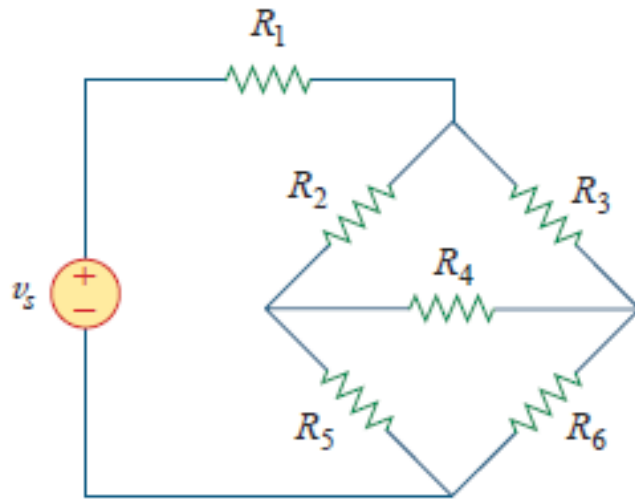

Two forms of the same network: (a) Y, (b) T.

Two forms of the same network: (a) Δ , (b) Π .

$$R_{12}(Y) = R_1 + R_3$$

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$

Setting $R_{12}(Y) = R_{12}(\Delta)$ gives

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$

Similarly,

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$


$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
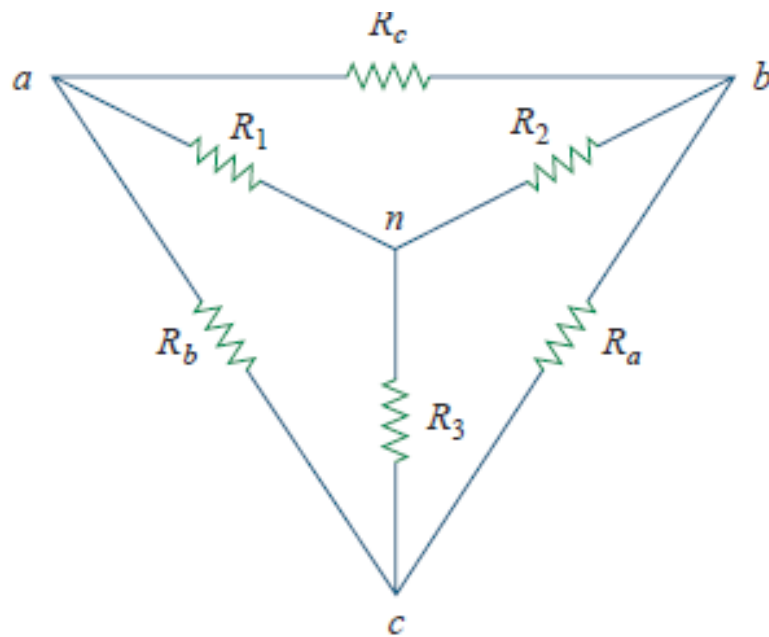
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three Δ resistors.

Wye to Delta Conversion

$$\begin{aligned} R_1 R_2 + R_2 R_3 + R_3 R_1 &= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2} \\ &= \frac{R_a R_b R_c}{R_a + R_b + R_c} \end{aligned}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

The Y and Δ networks are said to be *balanced* when



$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

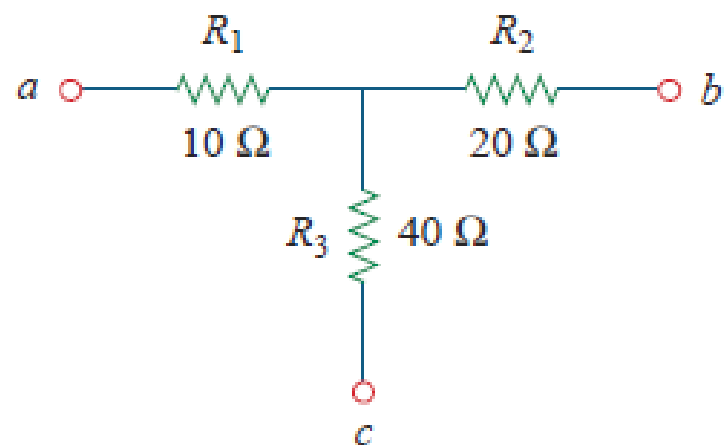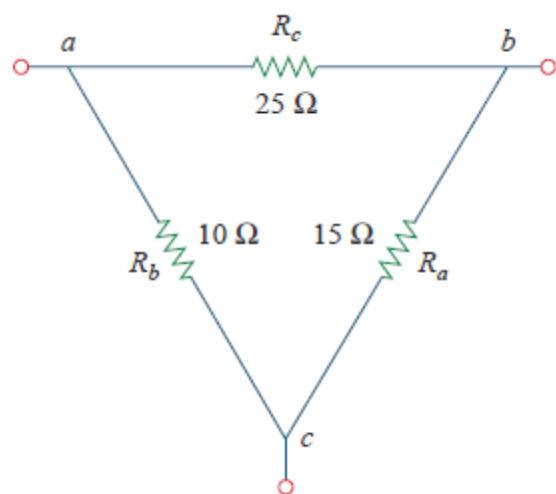
Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.




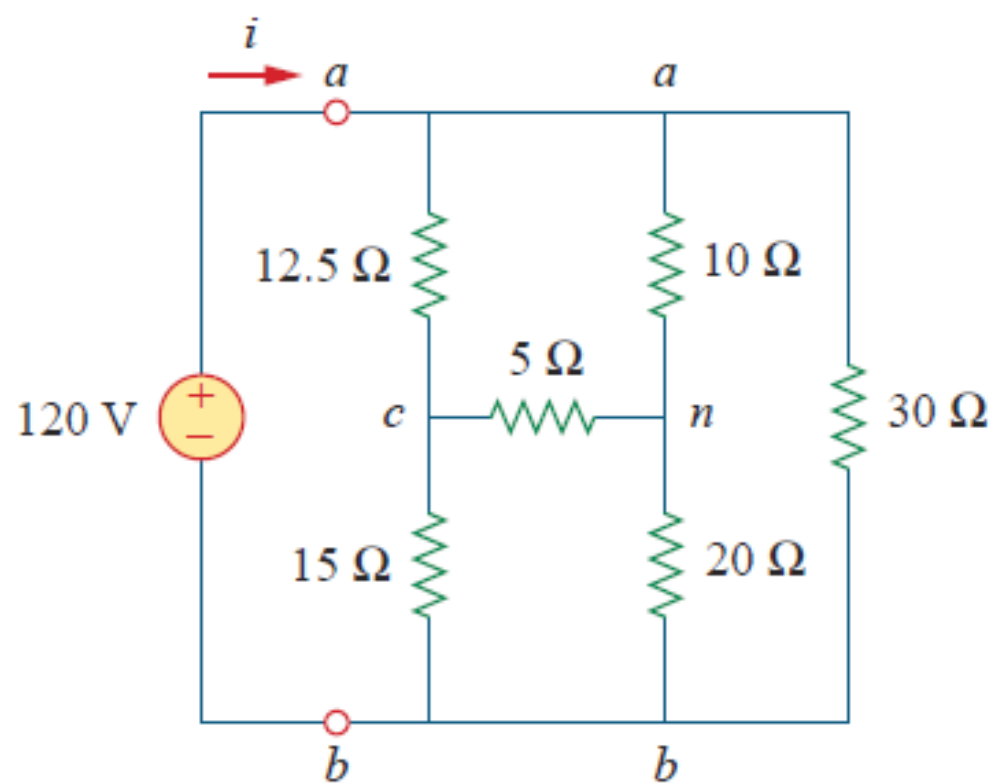


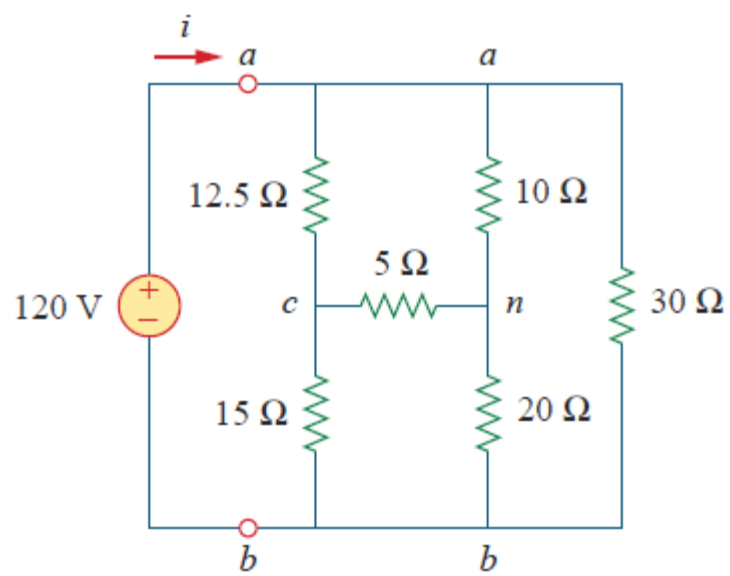


Mesh Analysis

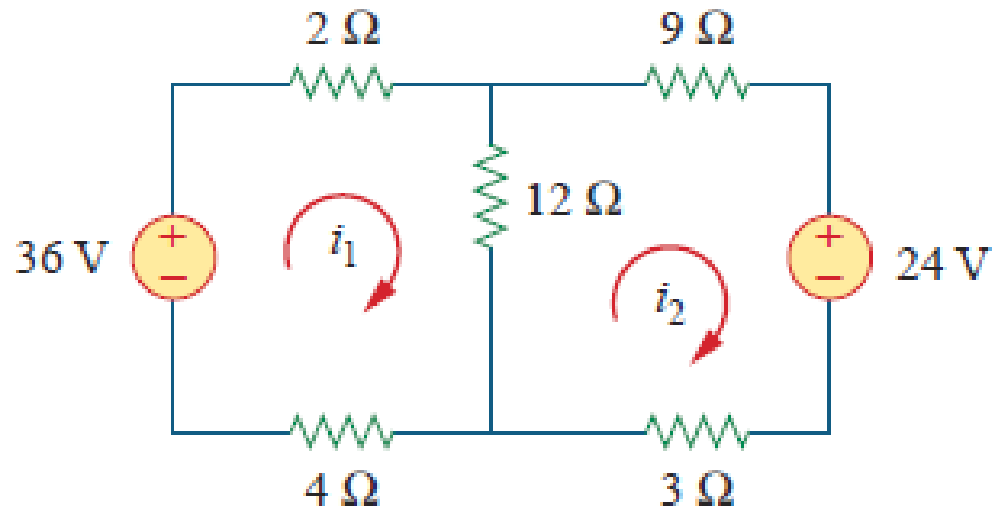


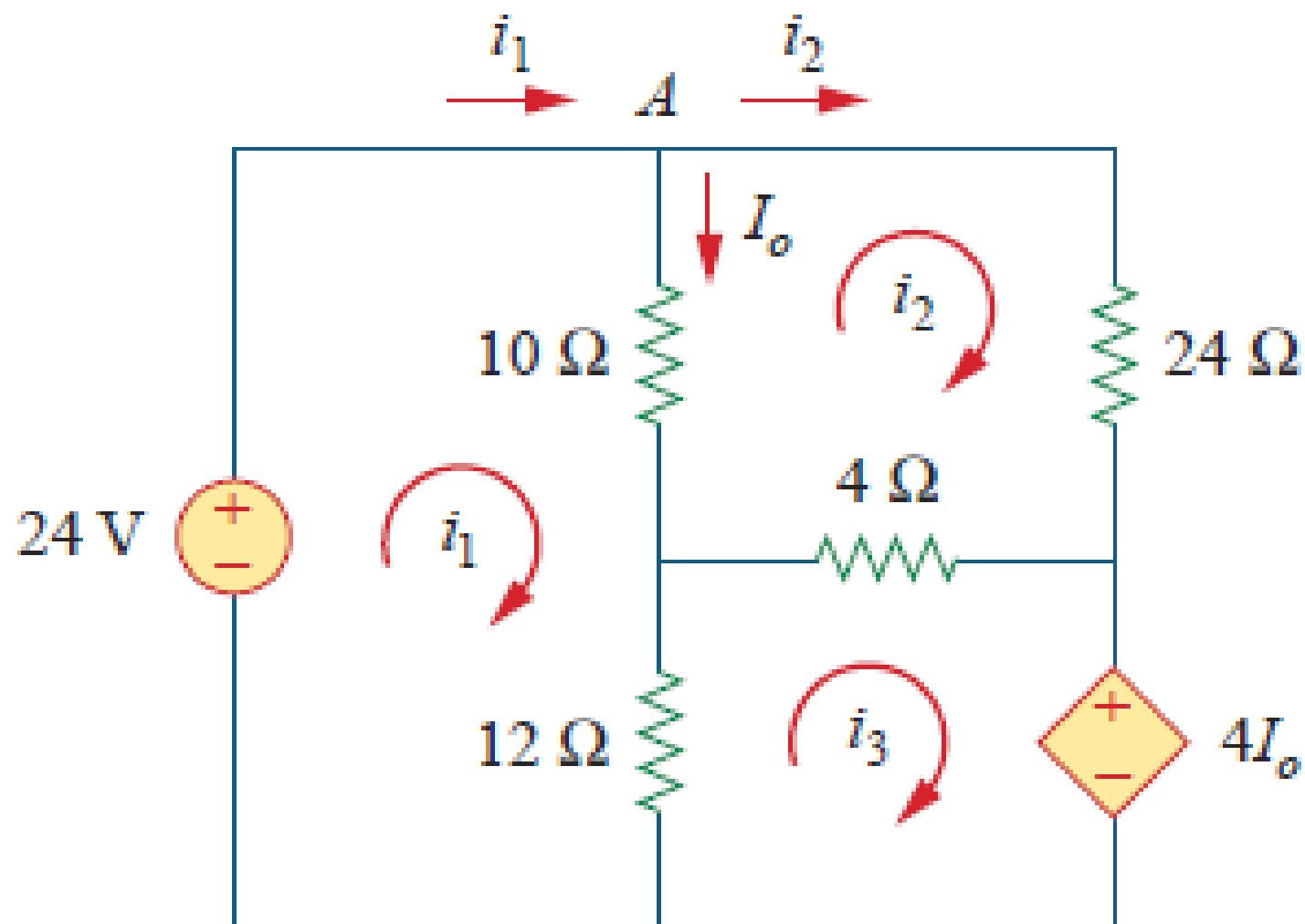


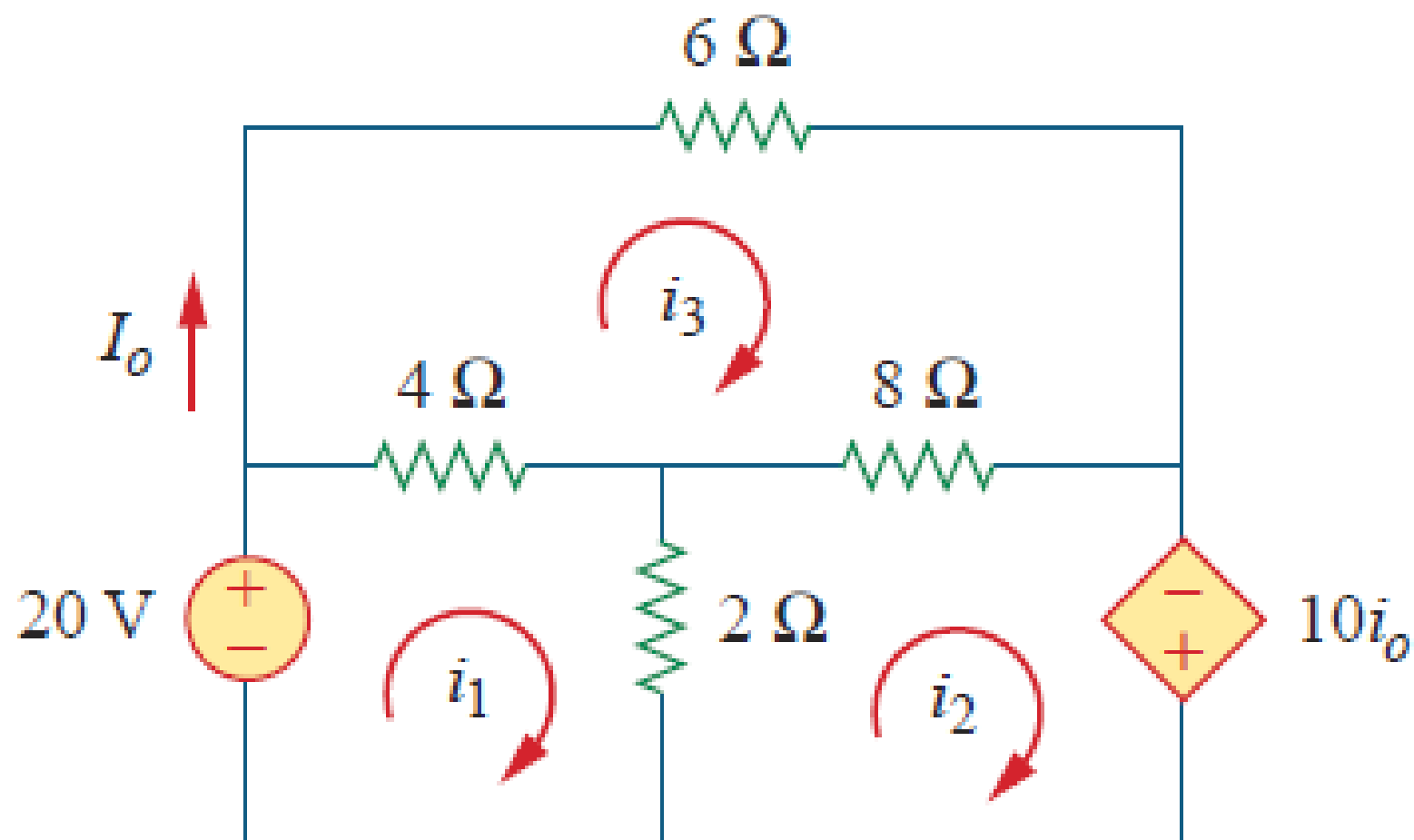

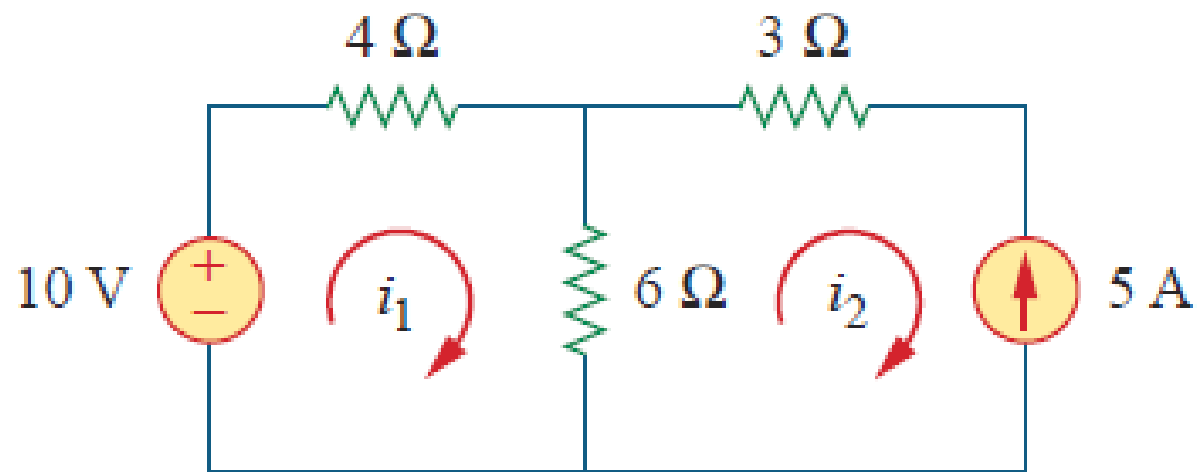

Super mesh

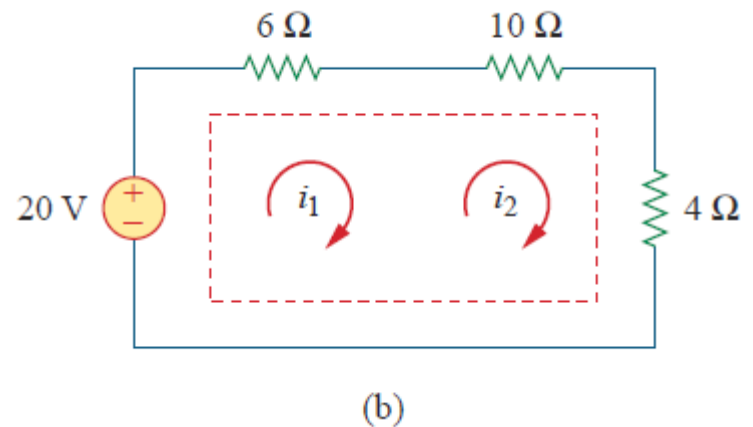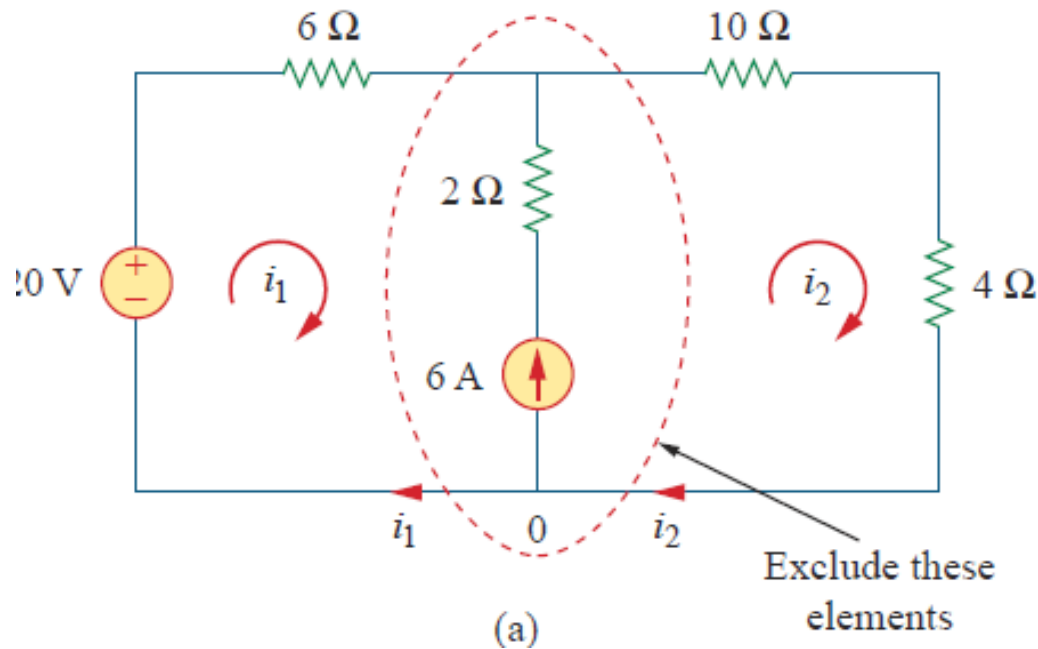A **supermesh** results when two meshes have a (dependent or independent) current source in common.



Note the following properties of a supermesh:

1. The current source in the supermesh provides the constraint equation necessary to solve for the mesh currents.
2. A supermesh has no current of its own.
3. A supermesh requires the application of both KVL and KCL.

