

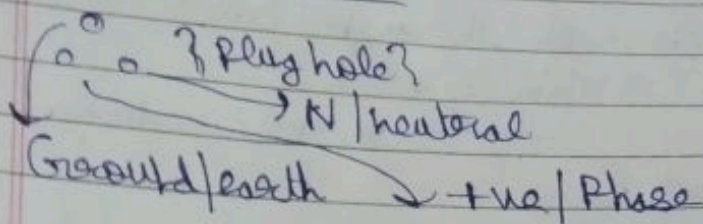


AC

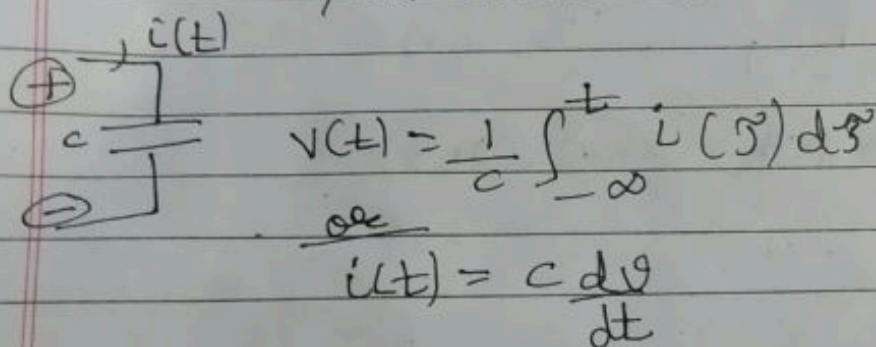


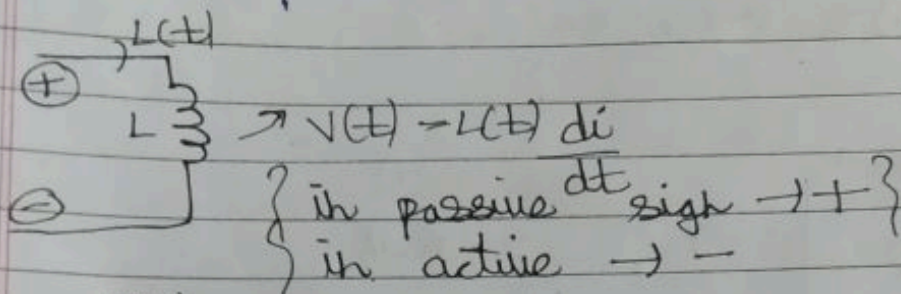Reason of earth \rightarrow for safety ~~of~~ all people and to prevent shock.




- ① if DC source added in inductor $\rightarrow \{ i(t) = SA \}$
 $V(t) = 0$.

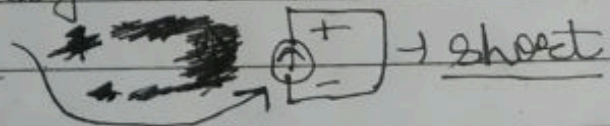so in DC at steady state inductor acts as short circuit




- ② if DC source in capacitor \rightarrow
(say $V(t) = S$)
 $i(t) = 0$.

so acts as open circuit

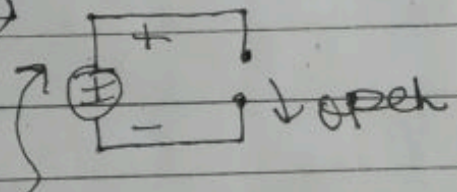

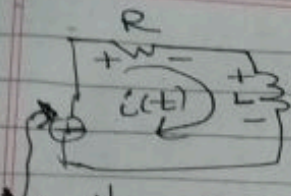
DC energy in inductor $\rightarrow \frac{1}{2} Li^2$
" " " Capacitor $\rightarrow \frac{CV^2}{2}$




$$V(t) = Ri(t) + L \frac{di(t)}{dt}$$

$$5 \cos(2\pi(50)t) = Ri(t) + L \frac{di(t)}{dt}$$


for linear system \rightarrow

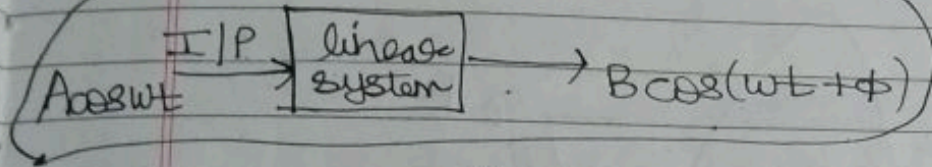

Phasors

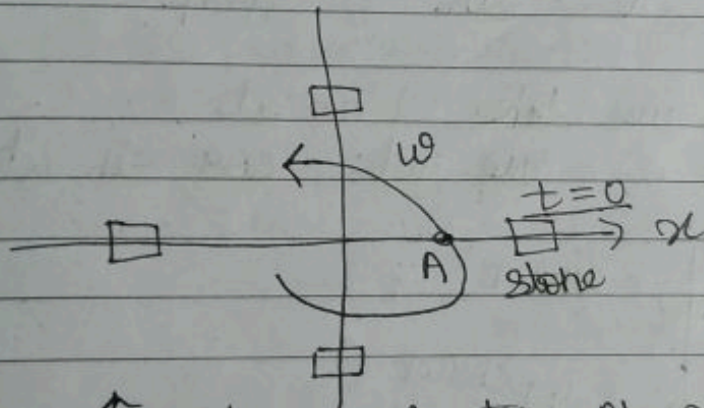



Projection of stone on x axis

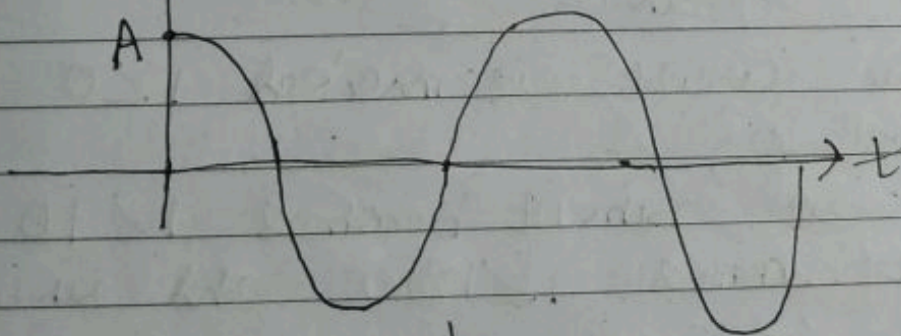


graph of $\cos \theta^h$

if we change initial posⁿ \rightarrow

} Next Page }

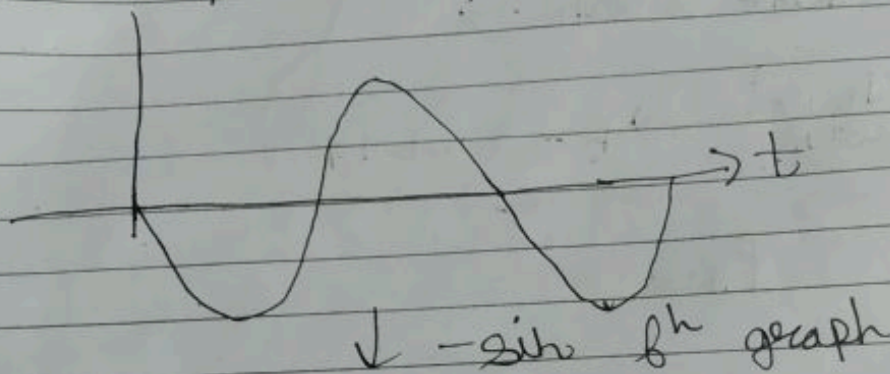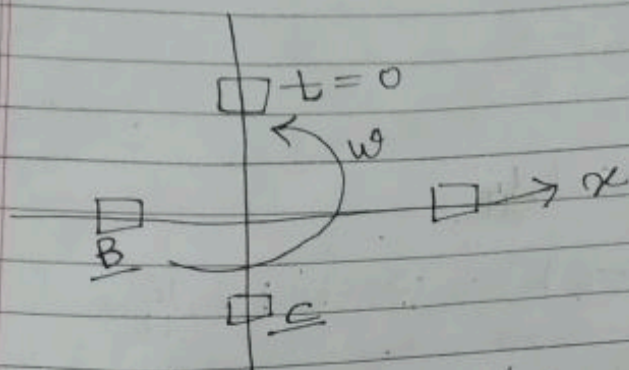


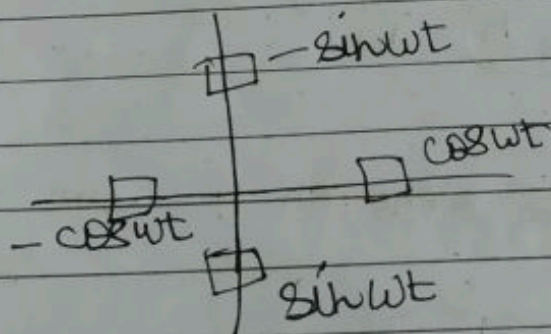Similarly if we take $t=0$ at B and C we get $-\cos$, $\sin \omega t$ s



now $\cos \omega t$ is marked $\angle 0$
{ angle 0 }

so $-\sin \omega t$ becomes $\angle 90$
 $-\cos \omega t$ becomes $\angle 180$ and $\sin \omega t$
becomes $\angle -90$

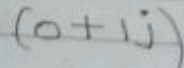
$$7=0$$


as reference had
cos.

ref phasor $\rightarrow 1 \cos \omega t$


or in time domain $\rightarrow \sqrt{2} \cos(\omega t + 135^\circ)$

↓

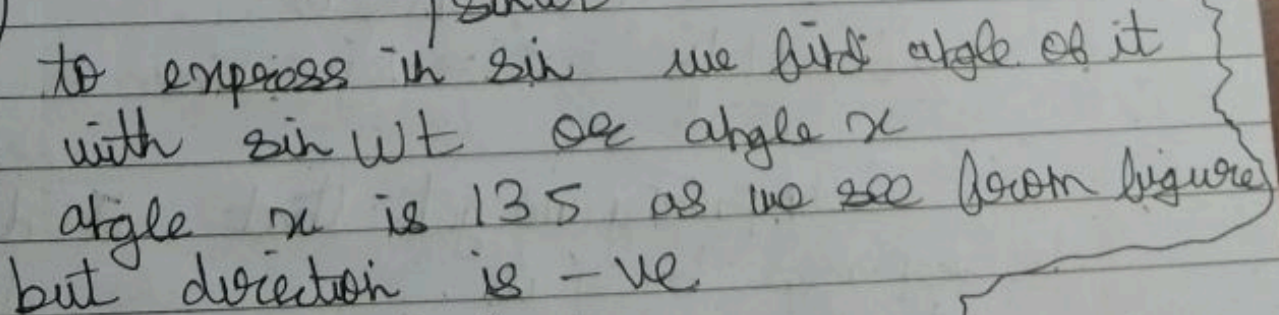

20 - 135°
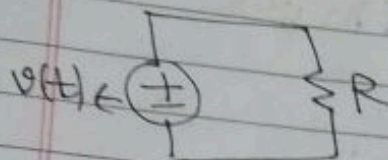
$$20 \sqrt{2} \sin(\omega t - 135^\circ)$$




$v(t) = V_m \cos(\omega t)$
given \rightarrow ref phase is $1 \cos \omega t$

so $v(t) \rightarrow \sqrt{V_m} \angle 0 = V$

now $i(t) = \frac{v(t)}{R} = \frac{V_m \cos \omega t}{R}$

so $I \rightarrow \frac{V_m \angle 0}{R}$

$V = IR$

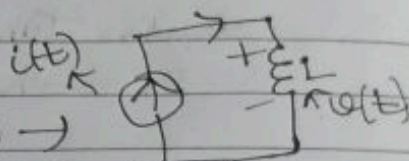

Different Circuit how \rightarrow

$i(t) = I_m \cos \omega t$, $v(t) = L \frac{di(t)}{dt}$
 $\angle I_m \angle 0$

NOTE \rightarrow Capital letters denote Phasor Domain stuff

$v(t) = L \frac{d}{dt} (I_m \cos \omega t)$

$= \omega L I_m (-\sin \omega t)$

$= \omega L I_m \cos(\omega t + 90)$

$V = \omega L I_m \angle 90$

$V = \omega L j I_m \angle 0$

$v(t) = L \frac{di}{dt}$, $V = L j \omega I_m$


comparing we get that $\frac{d}{dt}$ can be replaced by $j\omega$.
and

$V = j\omega L I$

$V = X_L I$

$X_L \rightarrow$ (in class 12)

New Circuit

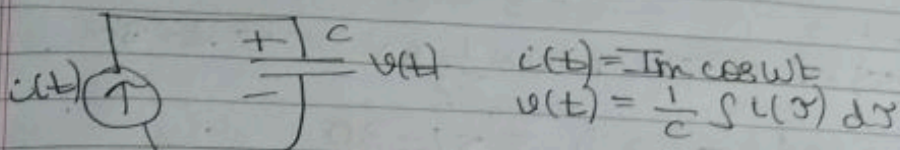

$$\text{now } v(t) = \frac{1}{C} \int I_m \cos wt \, dt$$

$$= \frac{1}{C} \frac{I_m}{\omega} \sin wt$$

$$= \frac{I_m}{\omega C} \cos(wt - 90)$$

$$V = \frac{I_m}{\omega C} \angle -90$$

$$V = \frac{I_m}{\omega C} \times 1 \angle 0 \times -j$$

$$V = \cancel{\frac{I_m}{\omega C}} + \frac{I_m}{j\omega C} \angle 0$$

$$V = \frac{I_m}{j\omega C} \angle 0$$

$$\text{as } -j = \frac{-j \times j}{j} = \frac{-j^2}{j} = \frac{1}{j}$$

$$\text{now } v(t) = \frac{1}{C} \int i(t) \, dt$$

comparing we see that \int can be replaced by $\frac{1}{j\omega}$ for capacitor $X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$

Q) find steady state response of $v(t)$

$$2 \frac{dv(t)}{dt} + 5v(t) + 10 \int v(t) \, dt = 5 \cos(5t - 30^\circ)$$

ans) as steady state \rightarrow Phasor.

$$\text{ref phasor} = 1 \cos 5t = 1 \angle 0$$

$$\frac{d}{dt} = j\omega, \quad \int = \frac{1}{j\omega}$$

$$\frac{d}{dt} = 5j, \quad \int = \frac{1}{5j}$$

so \rightarrow

$$2 \times 5j \times V + 5V + 10 \times \frac{1}{5j} \times V = 5 \angle -30$$


$$\rightarrow V(10j + 5 - 2j) = 5 \angle -30$$

$$V = \frac{5 \angle -30}{5 + 8j} \quad \left\{ \begin{array}{l} \text{we use calculator} \\ \text{here} \end{array} \right.$$

$$= 0.529 \angle -87.99$$

$$v(t) = 0.529 \cos(5t - 87.99)$$

Power


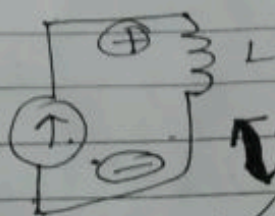


$$\begin{aligned} v(t) &= \omega L I_m \cos(\omega t + 90) \\ v &= j\omega L I_m \end{aligned}$$


\downarrow (derived earlier)

$$\begin{aligned} i(t) &= A(-\sin \omega t) \quad \left\{ A = \omega L I_m \right\} \\ i(t) &= B \cos \omega t \quad \left\{ B = I_m \right\} \end{aligned}$$
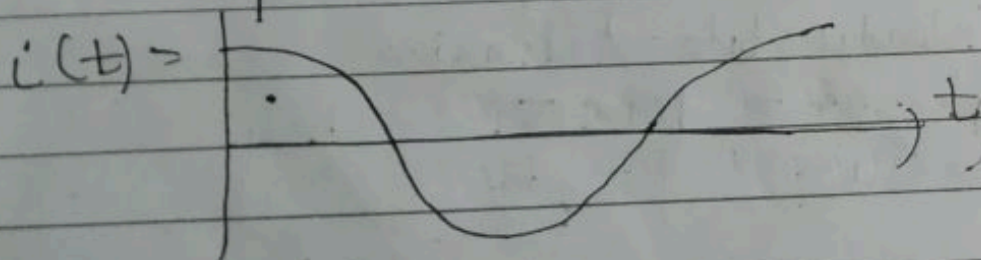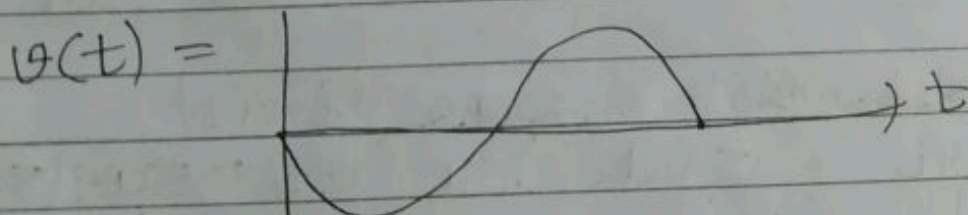
$$\begin{aligned} p(t) &= v(t) \times i(t) \\ &= AB \cos \omega t \times -\sin \omega t \end{aligned}$$



multiply graphically \rightarrow

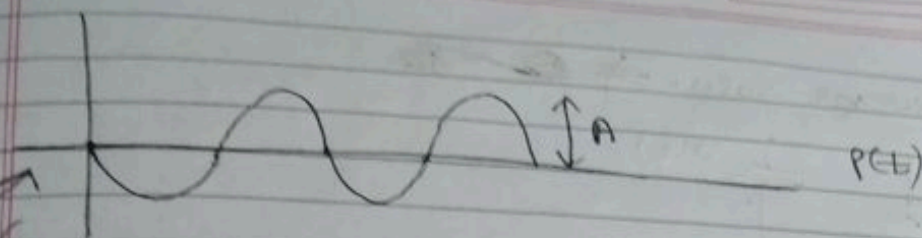


divide into quarter cycle and then multiply values $- \times - = +$, $- \times + = -$ and so on

One quarter cycle it absorbs and in next it releases

average value = Real power = 0 = P




Amplitude = A = peak power of oscillating = A

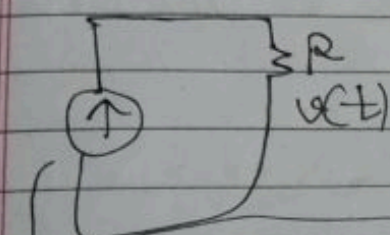+ as R in passive sign for inductor is +ve




$$i(t) = I_m \cos \omega t = B \cos \omega t$$
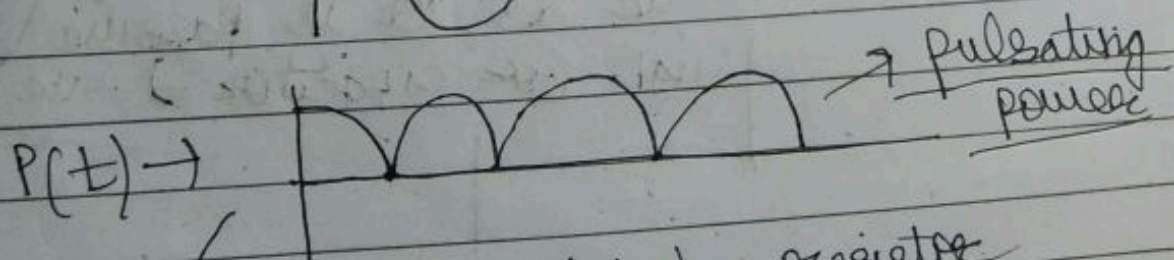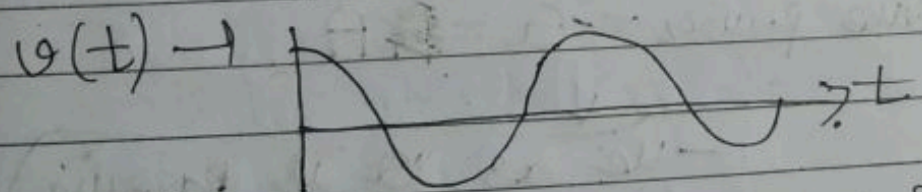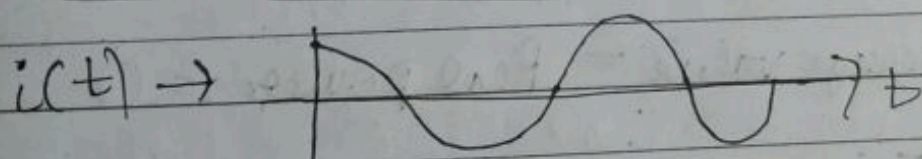
$$v(t) = I_m \times R \cos \omega t = A \cos \omega t$$



power absorbed by resistor
in DC \rightarrow Power Resistor \rightarrow const
in AC \rightarrow Power resistor \rightarrow Pulsating

Average Value $\neq 0$



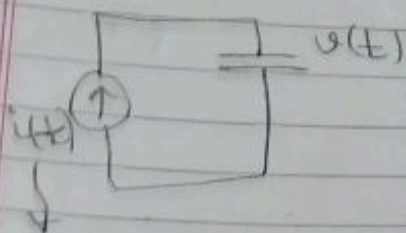


In circuit

$$v(t) = \frac{1}{C} \int i(t) dt = \frac{I_m \sin \omega t}{\omega C}$$

$$= \frac{1}{\omega C} \times I_m \angle -90$$

$$= \frac{I_m}{j\omega C}$$

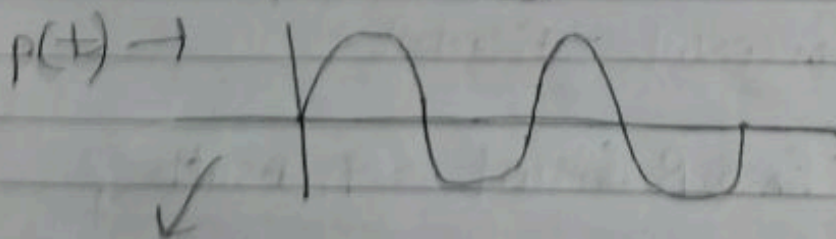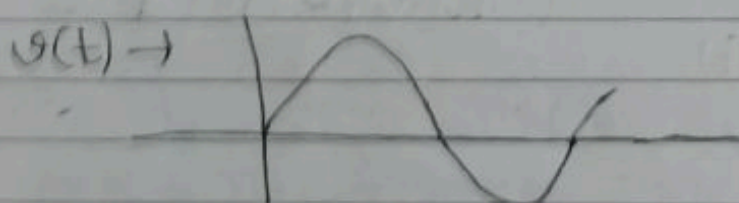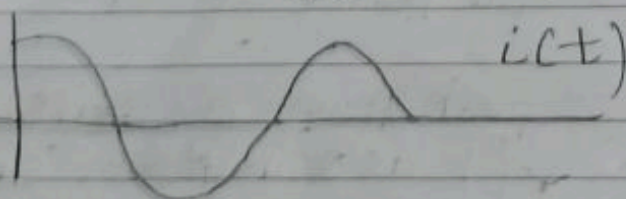


average value = Real power = 0

Reactive power = $-Q = -A$

↓
-ve as Q in passive sign for capacitor -ve

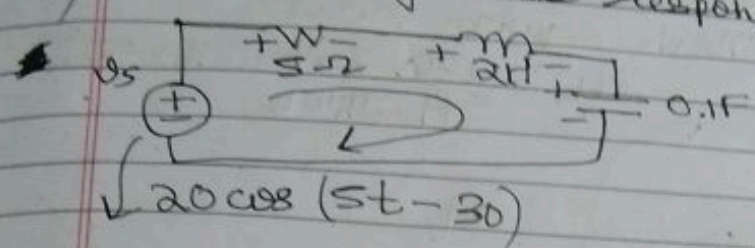a) Find steady state response \rightarrow



ans) using KVL \rightarrow

Method 1

$$v_s = v_R + v_L + v_C$$


$$20 \cos(5t - 30) = 5i(t) + 2 \frac{di(t)}{dt} + \frac{1}{0.1} \int i(t) dt$$

$$20 \angle -30 = 5i + 2j\omega \times i + \frac{i}{j\omega}$$

$$20 \angle -30 = (5 + 8j)I$$

$$I = \frac{20 \angle -30}{5 + 8j} = 2.119 \angle -87.99$$

$$= 2.119 \cos(5t - 87.99)$$

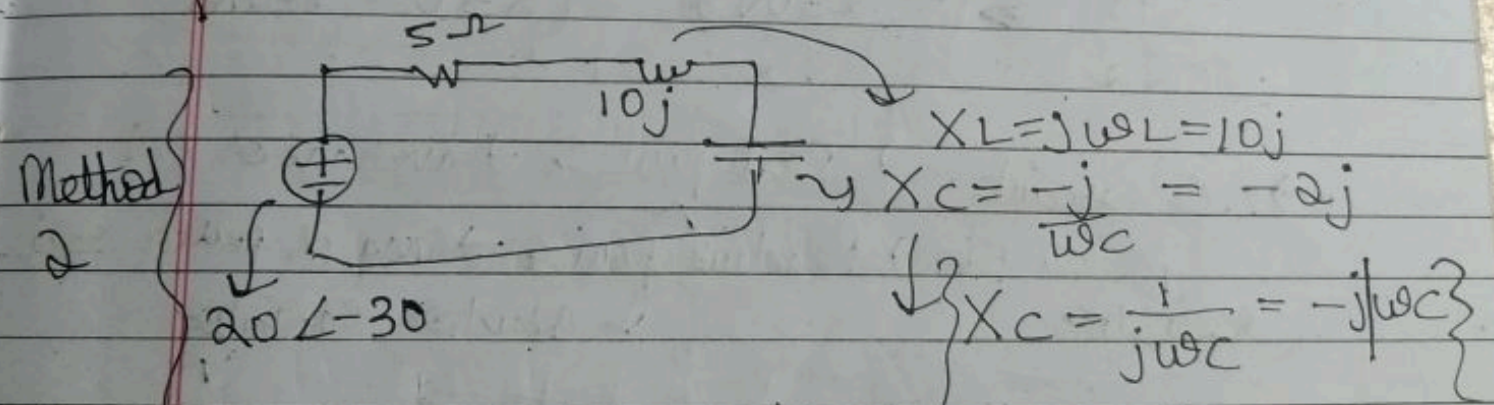

$$Z_{eq} = 5 + 10j - 2j = 5 + 8j$$


$$I = \frac{20 \angle -30}{5 + 8j} \text{ (ans)}$$

$$= 2.119 \angle -87.99$$

$$= 2.119 \cos(5t - 87.99)$$

AC Circuits

RMS \rightarrow Root Mean square value

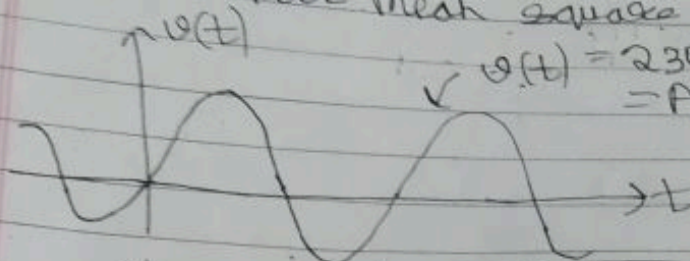

$$v(t) = 230\sqrt{2} \sin(2\pi \times 50 t) = A \sin \omega t$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T \sin^2 \omega t dt} \times A^2$$

$$= \frac{A^2}{\sqrt{T}} \int_0^T \frac{1 - \cos 2\omega t}{2} dt$$


$$= A \sqrt{\frac{1}{T} \int_0^T \frac{1}{2} dt}$$

$$= \frac{A}{\sqrt{2}} \Rightarrow = \frac{230\sqrt{2}}{\sqrt{2}} = 230 = V_{rms}$$

$P = V_{rms} I_{rms} \cos \phi$
 $Q = V_{rms} I_{rms} \sin \phi$

\rightarrow AC Circuit \rightarrow Real power \rightarrow average of $P(t)$
 \rightarrow Reactive power \rightarrow mag of power in
 resistor inductor capacitor

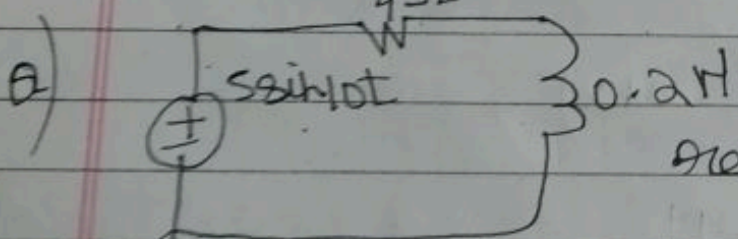Apparent $S = V_{rms} \times I_{rms} = P + jQ$
 \downarrow conjugate



reference $\rightarrow \cos 10t \rightarrow 1 < 0$

are \rightarrow

[LOKENATH]
Page No.
Date

$$\left. \begin{array}{c} 4 \angle 0 \\ 5 \angle -90 \end{array} \right\} 0.2H \text{ or } j\omega L = (2j\Omega)$$

$$Z_{eq} \rightarrow (4 + 2j) \Omega$$

$$I = \frac{5 \angle -90}{4 + 2j}$$

$$= 1.18033989 \angle -116.565052$$

$$i(t) = 1.18 \cos(10t - 116.56) A$$

Power supplied = $V_{rms} \times I_{rms}^*$ conjugate

$$= \frac{5 \angle -90}{\sqrt{2}} \times \frac{1.12 \angle -116.56}{\sqrt{2}}$$

$$= \frac{5 \angle -90}{\sqrt{2}} \times \frac{1.12}{\sqrt{2}} \angle 116.56$$

$$\left\{ (x + jy)^* = x - jy \right\}$$

conjugate

$$= \cancel{2.5} (2.5 + 1.25j) \quad \left\{ \begin{array}{l} \text{use use cartesian?} \\ \text{for this} \end{array} \right\}$$

$$= P + jQ$$

Watts

Volts ampere Reactive


or
VAR

power factor = $\cos(\text{angle between } Z \text{ angle's})$

$$\cos(\text{angle between } 4.472 \angle 26.56505)$$

$$\cos(26.56505) = 0.894$$

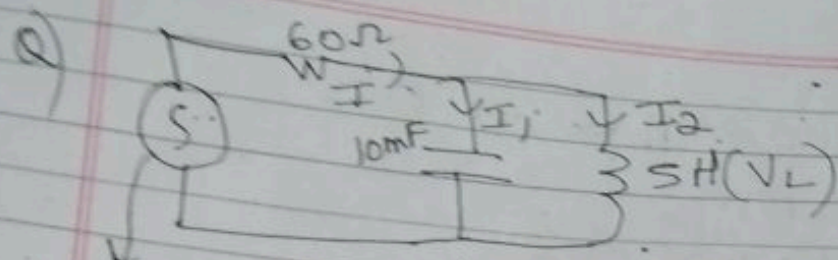or $\cos(\text{phase diff of voltage and current})$



$$20(\cos 4t - 15)$$

$$20 \angle -15^\circ \rightarrow 1 \cos 4t \rightarrow 1 \angle 0$$

ans) $10\text{mF} = \frac{1}{j\omega C} = \frac{-j}{\omega C} = -25j$

$$SH \rightarrow j\omega L = 20j$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_{cap}} + \frac{1}{Z_{ind}}$$

$$Z_{eq} = \left(\frac{1}{Z_C} + \frac{1}{Z_L} \right)^{-1}$$

$$Z_{eq} = 100j$$

$$Z_{total} = 60 + 100j$$

$$I = \frac{20 \angle -15^\circ}{60 + 100j} = 0.171 \angle -74.03^\circ$$

$$\text{Power Supp} = \frac{20 \angle -15^\circ}{\sqrt{2}} \left(\frac{0.171 \angle 74.03^\circ}{\sqrt{2}} \right)$$

$$= 0.88 \text{ W} + 1.46 \text{ VAR}$$

$$V_{across \text{ inductor}} = Z_{eq} = 100j \text{ and}$$

$$I = 0.174 \angle -74.02^\circ$$

$$V_L = 0.174 \angle -74.02^\circ \times 100j$$

$$= 17.15 \angle 15.78^\circ \text{ V}$$