

Phasor algebra

To represent R , X_L , X_C in rectangular form

$$Z_R = R + j0.$$

$$Z_L = 0 + jX_L.$$

$$Z_C = 0 - jX_C.$$

To represent R , X_L , X_C in polar form.

$$Z_R = R \angle 0^\circ.$$

$$Z_L = X_L \angle 90^\circ.$$

$$Z_C = X_C \angle -90^\circ.$$

converting rectangular to polar form.

Eg: $Z = (10 + j15) \Omega$ convert this into polar form.

soln:

1. Display 10
2. Press Shift key
3. Press R \rightarrow P
4. Display 15
5. Press = It shows 18.03 Ω

6. Press $\boxed{x \rightarrow y}$ It shows the angle 56.31° .

7. In polar form now z is written as
 $z = 18.03 \angle 56.31^\circ$.

converting polar to rectangular form.

eg: convert $10 \angle 60^\circ$ into rectangular form.

Solution:

1. Display 10

2. Press $\boxed{\text{shift}}$ key

3. Press $\boxed{P \rightarrow R}$

4. Display 60°

5. Press $\boxed{=}$ It shows 5 (active part)

6. Press $\boxed{x \rightarrow y}$ It shows 8.66 (reactive part)

7. So $z = 5 + j8.66$.

Note: The calculator must be set in 'deg' mode for conversions.

Addition and subtraction should be in Rectangular form.

Multiplication and division should be in polar form.

$$A \angle \theta + B \angle \phi = AB \angle \theta + \phi.$$

$$A \angle \theta \div B \angle \phi = \frac{A}{B} \angle \theta - \phi.$$

$$(A+jB) + (C+jD) = (A+C) + j(B+D)$$

$$(A+jB) - (C+jD) = (A-C) + j(B-D)$$

Write the result in polar form.

$$10 \angle 60^\circ + 8 \angle -45^\circ.$$

$$= 5 + j8.66 + 5.66 - j5.66$$

$$= 10.66 + j3$$

$$= 11.07 \angle 15.72^\circ.$$

1. $Z_1 = 10 + j10$ & $Z_2 = 20 - j30$, are in series. Find Z_T in polar form.

Soln:

$$\begin{aligned} Z_T &= Z_1 + Z_2 \\ &= 10 + j10 + 20 - j30 \\ &= 30 - j20 \\ &= 36.1 \angle -33.7^\circ \end{aligned}$$

2. The total impedance of a circuit in which Z_1 , Z_2 are in series is equal to $(30 + j40)\Omega$. $Z_1 = (20 + j60)\Omega$. Find Z_2 .

$$Z_T = Z_1 + Z_2$$

$$\begin{aligned} Z_2 &= Z_T - Z_1 \\ &= 30 + j40 - 20 - j60 \end{aligned}$$

$$= 10 - j20 \text{ (Rectangular form)}$$

$$= 22.36 \angle -63.43 \text{ (polar form)}$$

3. In a given circuit $I = 10 \angle 60^\circ$, $Z = 20 \angle 30^\circ$. Find V .
solution.

$$\begin{aligned} V &= I Z \\ &= 10 \angle 60^\circ \cdot 20 \angle 30^\circ \\ &= (10 \times 20) \angle 60 + 30^\circ \\ &= 200 \angle 90^\circ \end{aligned}$$

4. In a circuit $V = 200V$, $I = 10 \angle 30^\circ$. Find Z both in polar form and rectangular form.

$$\begin{aligned} I &= \frac{V}{Z} \\ &= \frac{200 \angle 0^\circ}{10 \angle 30^\circ} = 20 \angle 0 - 30^\circ = 20 \angle -30^\circ \\ &= 17.32 - j10 \end{aligned}$$