

$$\text{From } (1) \Rightarrow -2i_1 - i\left(\frac{-8}{9}\right)i = 1$$

$$-\frac{18i_1 + 56i}{9} = 1 \Rightarrow i_1 = \frac{9}{38} \text{ A}$$

$$R_{Th} = \frac{38 \Omega}{9} = 4.222 \Omega$$

$$P = V \cdot I$$

$$P = \frac{V^2}{R}$$

For max power $\Rightarrow R_{Th} = R_L$



$$P_L = \frac{V_{Th}^2}{4R_L} = \frac{(6.6)^2}{4 \times 4.222} = 2.596 \text{ W}$$

MODULE:2 : AC circuits

* Use dont connect capacitor / inductor in DC circuits,

$$V_L = -L \frac{di}{dt} ; \quad i_C = C \frac{dv}{dt}$$

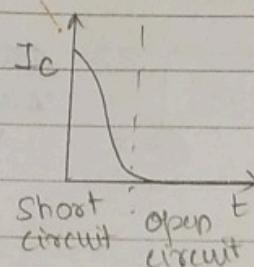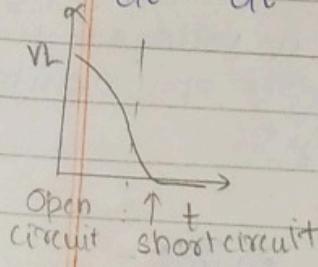$\frac{di}{dt}, \frac{dv}{dt} = 0$ in DC circuit, hence, $V_L = 0$ & $i_C = 0$




Equivalent capacitance


$$\text{Series} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} ; \quad \text{Parallel} \Rightarrow C_{eq} = C_1 + C_2$$

* AC: current & Voltage are sinusoidal

$$V_t = V_m \sin(\omega t + \phi)$$

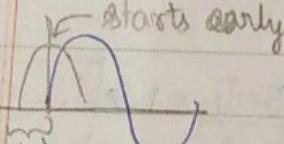

$$V_t = V_m \sin(\omega t + \phi)$$

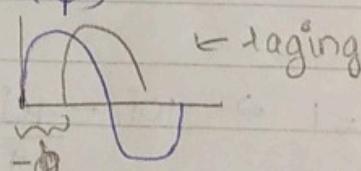

$$V_t = V_m \sin(\omega t - \phi)$$

(should see like which wave reaches peak first/ 0 first)

*


$$V_{av} = \frac{1}{\pi} \int_0^\pi V \sin \omega t dt$$

$$= -\frac{1}{\pi} [V_m \cos \omega t]_0^\pi$$

$$\boxed{V_{av} = \frac{2V_m}{\pi}}$$

*

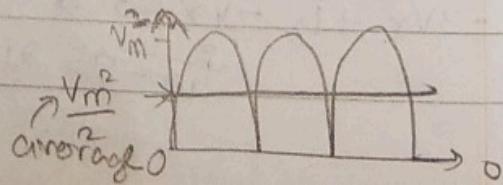
$$V_{RMS} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$



We cannot add voltage across an AC element scalarly.

hence we convert sinusoids to phasors:-


* Phasors: complex number (represented as $a+ib \Rightarrow |a| e^{i\phi}$) which represents magnitude and direction in rectangular form polar form exponential form

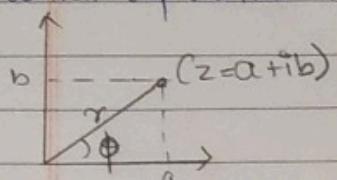

$$\phi = \tan^{-1} \left(\frac{b}{a} \right) : r = \sqrt{a^2 + b^2}$$

$$\exp: re^{i\phi} = r(\cos\phi + i\sin\phi)$$

* in phasors:

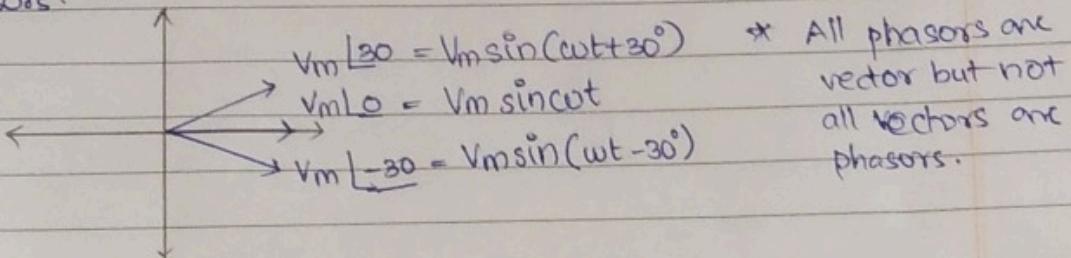

All phasors are vector but not all vectors are phasors.

Problem 1: $V_1 = 12 \sin(wt + 30^\circ)$; $V_2 = 20 \cos(wt - 30^\circ)$

$$\Rightarrow V_1 = 12 \cos(wt - 60^\circ)$$

$$V_1 = 12 \angle -60^\circ$$

$$a = 12 \cos 60^\circ = 6$$

$$b = 12 \sin 60^\circ = \frac{\sqrt{3}}{2} \times 12 = 6\sqrt{3}$$

$$V_1 = 6 + 6\sqrt{3}i$$

$$V_1 + V_2 = 23.2 - j(20.39)$$

$$r = \sqrt{a^2 + b^2} = \sqrt{(23.2)^2 + (-20.39)^2} = 30.88$$

$$\phi = \tan^{-1} \left(\frac{b}{a} \right) = -41.31^\circ$$

$$V_1 + V_2 = 30.88 \cos(-41.31^\circ)$$

* multiplication of 2 phasors $\vec{V}_1 \times \vec{V}_2 = V_1 V_2 \angle \phi_1 + \phi_2$

* division of 2 phasors, $\vec{V}_1 \div \vec{V}_2 = \frac{V_1}{V_2} \angle \phi_1 - \phi_2$

* square of phasor $\vec{V}_1 = V_1^2 \angle 2\phi_1$

* square root of phasors $\sqrt{V_1} = \sqrt{V} \angle \frac{1}{2}\phi_1$

* addition of $V_1 = a_1 + ib_1$ & $V_2 = a_2 + ib_2$

$$V = (a_1 + a_2) + i(b_1 + b_2)$$

* Subtraction of $V_1 = a_1 + ib_1$ & $V_2 = a_2 + ib_2$

$$V = (a_1 - a_2) + i(b_1 - b_2)$$

* conjugate of $V = a + ib$ is $\bar{V} = a - ib$

$$V = V_m \angle \phi$$

$$V = re^{i\phi}$$

$$is V = V_m \angle -\phi$$

$$is V = r e^{-i\phi}$$

H.W: Evaluate the complex numbers

(a) $(40 \angle 50^\circ + 20 \angle -30^\circ)^{1/2}$

$V_1 \angle \Phi_1 + V_2 \angle \Phi_2 = (a_1 + a_2) \pm (b_1 + b_2)i$

$V_1 = 40 \cos 50^\circ + 5V_2 \therefore V_2 = 20 \cos(-30^\circ)$

$\therefore V_1 = a_1 + ib_1$

$a_1 = 40 \cos 50^\circ = 25.711$

$b_1 = 40 \sin 50^\circ = 30.641$

$V_2 = a_2 + ib_2$

$a_2 = 20 \cos(-30^\circ) = 17.32$

$b_2 = 20 \sin(-30^\circ) = -10$

$\sqrt{r^2}$

$40 \angle 50^\circ + 20 \angle -30^\circ = (a_1 + a_2) \pm (b_1 + b_2)i$

$= (25.711 + 17.32) \pm (30.641 - 10)i$

$= 43.031 \pm 20.641i$

$r = \sqrt{(43.031)^2 + (20.641)^2} = \sqrt{1851.66 + 426.05}$

$\theta = 47.72$

$\phi = 25.62^\circ$

hence $(40 \angle 50^\circ + 20 \angle -30^\circ)^{1/2}$

$= \left(\frac{47.72}{2} \angle \frac{25.62^\circ}{2} \right)^{1/2}$

$= \sqrt{47.72} \angle \frac{25.62^\circ}{2}$

$= 6.907 \angle 12.81^\circ$

(b)

$\frac{10 \angle -30^\circ + (3+j4)}{(2+j4)(3-j5)}$

$\therefore 10 \angle -30^\circ \therefore a = 10 \cos(-30^\circ); b = 10 \sin(-30^\circ)$

$a = 8.660 \therefore b = -5$

$10 \angle -30^\circ = 8.660 \angle -5^\circ$

$\frac{(8\sqrt{3}-5j) + (3+4j)}{(2+j4)(3-j5)} = \frac{15\sqrt{3} + 20j - 15j - 20j^2}{(13+j)(13-j)}$

$= \frac{(5\sqrt{3}+3) - j}{(13+j)} = \frac{(5\sqrt{3}+3) - j}{(13-j)} = \frac{81 \times (5\sqrt{3}+3) - j}{(13+j)(13-j)}$

$= \frac{1}{2} \times \frac{(5\sqrt{3}+3) - j}{(13+j)} \times \frac{26+2j}{26-2j} = \frac{(5\sqrt{3}+3) - j}{(26+2j)} \times \frac{(26-2j)}{(26-2j)}$

$= \frac{1}{2} \times \frac{225 \cdot 16 - 303 \cdot 16 - 23 \cdot 32j - 26j + 2j^2}{676 - 4j^2}$

$= \frac{301 \cdot 16 - 49 \cdot 32j}{676 - 4j^2}$

680

$= 0.4428 - 0.0725j$

$$\gamma = \sqrt{(0.4428)^2 + (0.0725)^2} = \sqrt{0.196 + 0.00525} = \sqrt{0.2012}$$

$$\gamma = 0.4485$$

$$\phi = \tan^{-1} \left(\frac{-0.0725}{0.4428} \right) = -9.2985^\circ$$

hence the simplified one $0.4485 \cos(-9.2985^\circ)$

$$= 0.4485 \angle -9.2985^\circ$$

* In AC Analysis:-


1. sinusoids to Phasors

2. Technique

3. Phasors to sinusoids.

In Inductive circuit, current lags voltage


Ex 1:

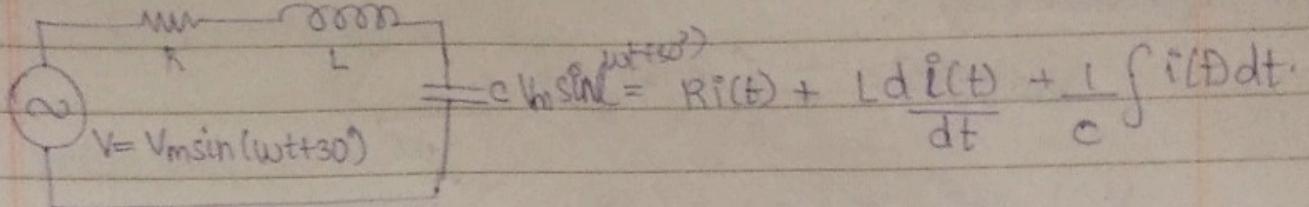

We have to convert $i(t)$ into phasors before diff/integrating

$$V_m | -60^\circ = RI + L j\omega L + \frac{1}{C} \frac{I}{j\omega}$$

cont \Rightarrow next page \Rightarrow

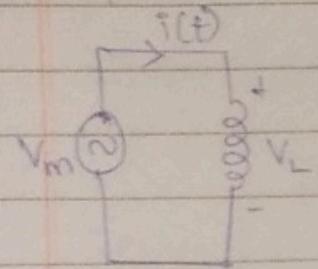* 

$$V(t) = V_m \sin \omega t = V_m | 0^\circ$$

$$V(t) = L \frac{di(t)}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

$$i(t) = \frac{1}{L} \int V_m \sin \omega t dt$$

$$i(t) = \frac{V_m}{WL} (-\cos \omega t) \Rightarrow P(t) = \frac{V_m^2}{WL} (\cos \omega t)$$

$$\sin(270^\circ + \theta) \because \sin(270^\circ + \theta) = -\cos \omega t$$

$$i(t) = \frac{V_m}{WL} \sin(270^\circ + \omega t) \quad \because \sin(360^\circ + \theta) = \sin(0^\circ - \theta)$$

$$= \frac{V_m}{WL} \sin(270^\circ + \omega t - 360^\circ) \Rightarrow i(t) = \frac{V_m}{WL} \sin(-90^\circ + \omega t)$$

$$\rightarrow i(t) = \frac{V_m}{WL} \sin(\omega t - 90^\circ) \Rightarrow i(t) = \frac{V_m}{WL} | -90^\circ$$

$$V_m = V = V_m | 0^\circ \quad ; \quad I = I_m | -90^\circ \quad \begin{matrix} \text{current lags in} \\ \text{inductive circuit.} \end{matrix}$$

$$V_m = I_m \omega L / | -90^\circ \Rightarrow V_m = I_m \omega L | 0^\circ$$

$$\Rightarrow V_m = \underbrace{I_m \omega L}_{\text{①}} | 90^\circ$$

$$I | 90^\circ = I e^{j 90^\circ} = I (\cos 90^\circ + j \sin 90^\circ) = I (0 + 1j) = j$$

$$\boxed{90^\circ = j} \quad \boxed{-90^\circ = -j}$$

hence eqn ① $\Rightarrow V = j\omega L I$

* In sinusoids

$$V = L \frac{di(t)}{dt}$$

In phasors

$$V = j\omega L I$$

Comparing these equations: $\frac{d}{dt} = j\omega$

* In sinusoids

$$i(t) = \frac{1}{L} \int v(t) \cdot dt$$

In phasors

$$I = \frac{V}{j\omega L}$$

Comparing these equations: $\int dt = \frac{1}{j\omega}$

cont. of previous page:-

$$V_m \angle -60^\circ = I \left(R + j\omega L + \frac{1}{j\omega C} \right)$$

$$V_m \angle -60^\circ = I \left[R + j \left(\omega L - \frac{1}{\omega C} \right) \right]$$

* In sinusoids

(i) $v(t) = i(t)R$

In phasors

$$V = IR$$

(ii) $v(t) = L \frac{di(t)}{dt}$

$$V = j\omega L I$$

(iii) $i(t) = \frac{1}{L} \int v(t) dt$

$$I = \frac{V}{j\omega L}$$

(iii) $V = \frac{1}{C} \int i(t) dt$

$$V = \frac{I}{j\omega C}$$

* In RLC series circuit, we have impedances,

$$jX_L = \frac{V}{I} = j\omega L$$

* In capacitive circuit: $jX_C = \frac{1}{j\omega L}$

Impedance $= Z = R + jX$ reactance

where $X = \left(\omega L - \frac{1}{\omega C} \right)$

hence eq① \Rightarrow $V = j\omega L I$

* In sinusoids

$$V = L \frac{di(t)}{dt}$$

In phasors

$$V = j\omega L I$$

Comparing these equations:

$$\frac{d}{dt} = j\omega$$

* In sinusoids

$$i(t) = \frac{1}{L} \int v(t) \cdot dt$$

in phasors


$$I = \frac{V}{j\omega L}$$

Comparing these equations:

$$\int dt = \frac{1}{j\omega}$$

3 - Phasors to sinusoids

Ex 1:

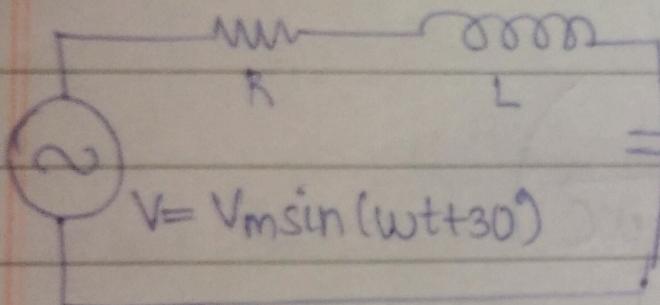

$$cV_m \sin(wt + 30^\circ) = RI(t) + L \frac{di(t)}{dt} + \frac{1}{c} \int i(t) dt.$$

We have to convert $i(t)$ into phasors before diff/integrating

$$V_m \angle -60^\circ = RI + L j\omega I + \frac{1}{C} \frac{I}{j\omega}$$

$$V_m L - 60^\circ = I \left(R + j\omega L + \frac{1}{j\omega C} \right)$$

$$V_m L - 60^\circ = I \left[R + j \left(\omega L - \frac{1}{\omega C} \right) \right]$$

* In sinusoids

$$(i) V(t) = i(t) R$$

$$(ii) V(t) = L \frac{di(t)}{dt}$$

$$\text{iii) } i(t) = \frac{1}{L} \int v(t) dt$$

$$(iii) V = \frac{1}{C} \int i(t) dt$$

In phasors

$$V = IR$$

$$V = j\omega LI$$

$$I = \frac{V}{j\omega L}$$

$$V = \frac{I}{j\omega C}$$

* In RLC series circuit, we have impedances,

$$jX_L = \frac{V}{I} = j\omega L$$

$$* \text{ In capacitive circuit : } jX_C = \frac{1}{j\omega L}$$

$$\text{Impedance} = Z = R + jX_{\text{reactance}}$$

$$\text{where } X = \left(\omega L - \frac{1}{\omega C} \right)$$

Ex 2: Using the phasor approach, determine the current $i(t)$ in a circuit described by the integrodifferential equation.

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ) \quad \text{--- (1)}$$

solution :

$$V_m = 50; \omega = 2, \phi = 75^\circ$$

Converting sinusoidal (1) to phasors

$$4I + \underline{8I} - 3\underline{j(2)}I = 50 \underline{75^\circ}$$

$$I (4 - 4j - 6j) = 50 \underline{75^\circ}$$

$$I (4 - 10j) = 50 \underline{75^\circ}$$

$$I = \underline{50 \underline{75^\circ}}$$

$$4 - 10j$$

$$\therefore \text{polar form of } 4 - 10j \Rightarrow \sqrt{4^2 + 10^2} \left[\tan^{-1}\left(\frac{-10}{4}\right) \right] = 10\cdot7 \underline{-68^\circ}$$

$$I = \underline{50 \underline{75^\circ}}$$


$$10\cdot7 \underline{-68^\circ}$$

$$I = \frac{\pm 50}{10\cdot7} \underline{75^\circ - (-68^\circ)}$$

$$I = 4\cdot67 \underline{143^\circ}$$

$$I = 4\cdot67 \cos(2t + 143^\circ)$$

Ex 3: Determine $V(t)$ and $I(t)$.

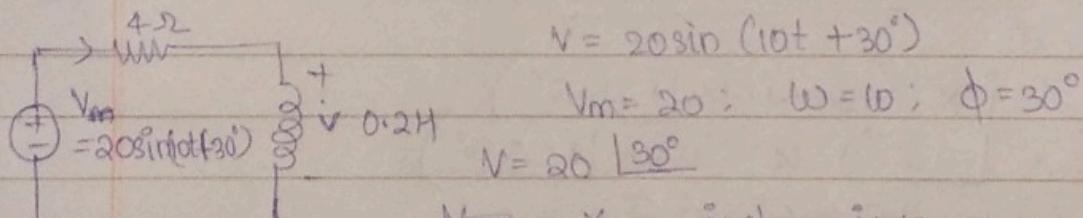

$$V = 20 \sin(10t + 30^\circ)$$

$$V_m = 20; \omega = 10; \phi = 30^\circ$$

$$V = 20 \underline{30^\circ}$$

$$X_L \cdot I = j\omega L = j \times 10 \times 0.2$$

$$X_L = 2j$$

$$4I + 2jI = 2 \underline{30^\circ}$$

$$I (4 + 2j) = 2 \underline{30^\circ} \rightarrow I = \underline{20 \underline{30^\circ}}$$

$$\begin{aligned} &4+2j \\ &\left[\tan^{-1}\left(\frac{1}{2}\right) \right] \end{aligned}$$

$$\therefore \text{Polar form of } 4+2j = \sqrt{4^2 + 2^2}$$

$$I = \underline{20 \underline{30^\circ}}$$

$$4\cdot47 \underline{26.5^\circ}$$

$$I = 4\cdot47 \underline{3.5^\circ}$$

$$I = 4\cdot47 \sin(2t + 3.5^\circ)$$

$$V = j\omega L I = V = X_L I$$

$$V = 2j I$$


$$V = 2 \angle 90^\circ \cdot 4.4 \angle 30^\circ$$

$$V = 8.94 \angle 93.5^\circ$$

$$V = 8.94 \sin(2t + 93.5^\circ)$$

$$[j = 1 \angle 90^\circ]$$

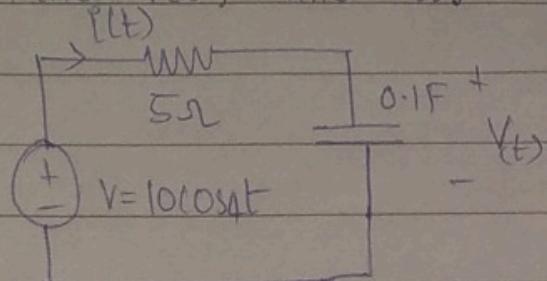H.W Find $v(t)$ and $i(t)$ in the circuit shown.



$$V = 10 \cos \omega t; \omega = 4; \phi = 0^\circ$$

$$V = 5i + iX_C$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{j(4)(0.1)} = -j \times 2.5$$

$$X_C = -2.5j$$

In phasor form.

$$10 \angle 0^\circ = 5I + I(-2.5j)$$

$$I = \frac{10 \angle 0^\circ}{5 - 2.5j}$$

$$\therefore 5 - 2.5j \text{ in polar form} = \sqrt{5^2 + (-2.5)^2} \left| \tan^{-1} \left(\frac{-1}{2} \right) \right|$$

$$= 5.59 \angle -26.5^\circ$$

$$I = \frac{10 \angle 0^\circ}{5.59 \angle -26.5^\circ} = 1.78 \angle +26.5^\circ$$

$$i(t) = 1.78 \cos(4t + 26.5^\circ)$$

$$V = X_C I$$

$$V = -2.5j \times (1.78 \angle +26.5^\circ)$$


$$= (2.5 \angle -90^\circ) \times (1.78 \angle +26.5^\circ)$$

$$V = 4.48 \angle -116.5^\circ - 63.5^\circ$$

$$V_C = 4.48 \cos(4t - 116.5^\circ)$$

$$V_C = 4.48 \cos(4t - 63.5^\circ)$$

Expt.

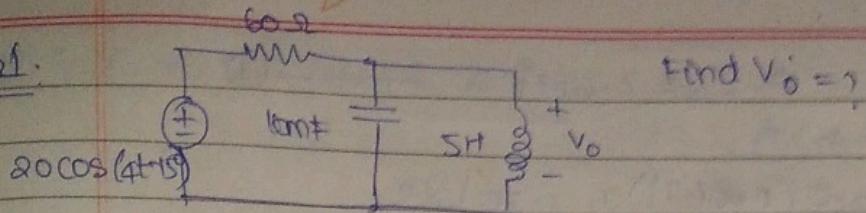


solution:-

$$\omega = 4 \therefore V = 20 | -15^\circ : X_C = \frac{1}{j\omega C} = \frac{-j}{4 \times 10^{-3}} = -25j$$

$$X_L = j\omega L = j \times 4 \times 5 = 20j$$

capacitor & inductor are in parallel \Rightarrow hence its
inductive reactance,
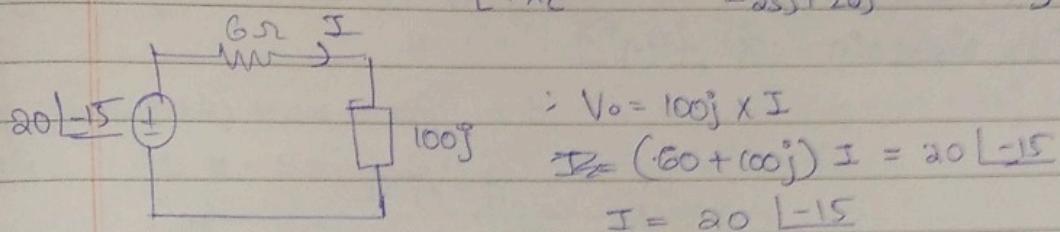
$$Z_{eq} = \frac{X_L X_C}{X_L + X_C} = \frac{-25j \cdot 20j}{-25j + 20j} = \frac{-500j^2}{+5j} = 100j$$



$$V_o = 100j \times I$$

$$I = (60 + 100j) I = 20 | -15^\circ$$

$$I = \frac{20 | -15^\circ}{60 + 100j}$$

$$\text{Polar form of } 60 + 100j = \sqrt{13600} | 59.03^\circ$$

$$= 116.61 | 59.03^\circ$$


$$I = 0.171 | -74.03^\circ$$

$$V_o = 100j \times 0.171 | -74.03^\circ$$

$$V_o = 100 | 90^\circ \times 0.171 | -74.03^\circ$$

$$V_o = 17.1 \cos(4t + 15.97^\circ)$$

Ex 2:

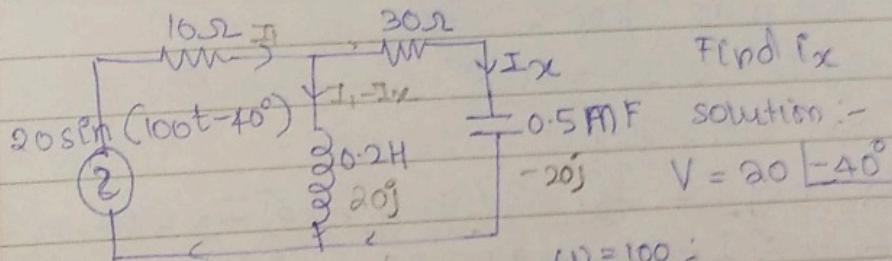

$$\omega = 100 :$$

$$X_L = j\omega L = j \times 100 \times 0.2H = 20j$$

$$X_C = \frac{1}{j\omega C} = \frac{j}{100 \times 0.5 \times 10^{-3}} = -20j$$

Find I_X

solution:-

$$V = 20 | -40^\circ$$

applying mesh analysis on loop 1:-

$$10jI_1 + 20j(I_1 - I_X) = 20 | -40^\circ \quad \text{--- (1)}$$

$$\text{in Loop 2: } 30I_X + -20jI_2 + 20j(I_X - I_1) = 0$$

$$30I_X = 20jI_1$$

$$I_x = \frac{2}{3} I_1 \Rightarrow I_x = 0.667 I_1 \quad \text{--- } ①$$

Substituting ② in ①:

$$I_1 (10 + 20j) - 20j (0.667 I_1) I_1 = 20 | -40^\circ$$

$$I_1 = \frac{20 | -40^\circ}{23.34 + 20j}$$

$$\begin{aligned} \text{Polar form of } 23.34 + 20j &= \sqrt{144.75} | 40.6^\circ \\ &= 30.72 | 40.6^\circ \end{aligned}$$


$$I_1 = \frac{20 | -40^\circ}{30.72 | 40.6^\circ} = 0.651 | -80.6^\circ$$

$$I_x = 0.667 | 90^\circ \times 0.651 | -80.6^\circ$$

$$I_x = 0.434 | 9.4^\circ$$

$$I_x = 0.434 \sin(100t + 9.4^\circ)$$

H.W

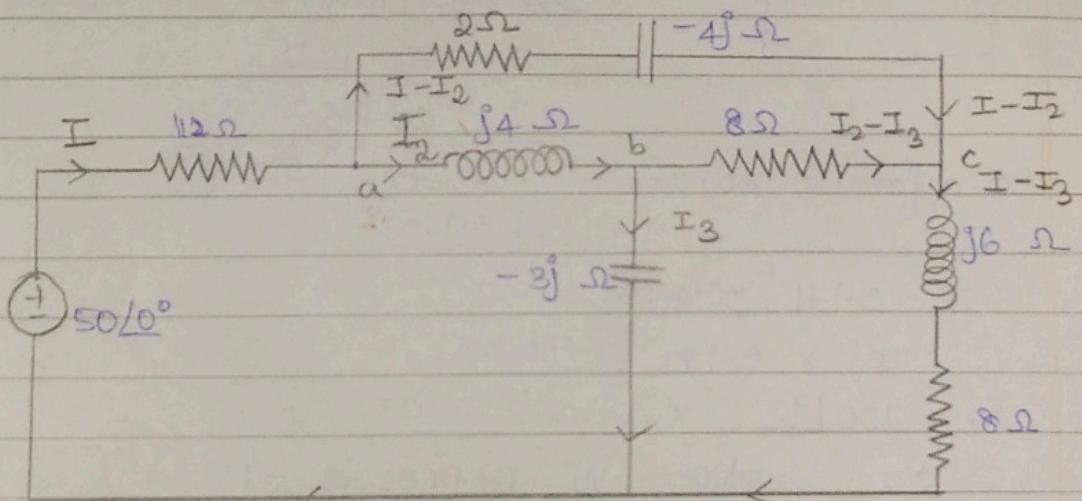

$$V_m = 50 \cos 0^\circ = 50 | 0^\circ ; I = ?$$

applying KVL along loop 1; loop

$$12I + 4j I_2 - 3j I_3 = 50 | 0^\circ \quad \text{--- } ①$$

applying KVL along loop 2:-

$$8(I_2 - I_3) + 6j(I - I_3) + 8(I - I_2) + 3jI_3 = 0$$

$$8I_2 - 8I_3 + 6jI - 6I_3 + 8I - 8I_2 + 3jI_3 = 0$$

$$(8 + 6j)I + 8I_2 + (-22 + 3j)I_3 = 0 \quad \text{--- } ②$$

applying KVL along loop 3:-

$$2(I - I_2) - 4j(I - I_2) - 8(I_2 - I_3) - 4jI_2 = 0$$

$$2I - 2I_2 - 4jI + 4I_2 - 8I_2 + 8I_3 - 4jI_2 = 0$$

$$(2 - 4j)I + (-6 - 4j)I_2 + 8I_3 = 0 \quad \text{--- } ③$$

$$I_3 = (6 + 4j)I_2 + (-2 + 4j)I \quad \text{--- } ③$$

$$\textcircled{3} \text{ in } \textcircled{1} \Rightarrow 12I + 4j I_2 - 3j I_3 = 50 | 0^\circ$$

$$12I + 4j I_2 - 3j \left[\frac{(6+4j) I_2 + (-2+4j) I}{8} \right] = 50 | 0^\circ$$

$$96I + 32j I_2 + (-18j + 12) I_2 + (6j + 12) I = 400 | 0^\circ$$

$$I_2 (48 + 14j) + I (108 + 6j) = 400 | 0^\circ \quad \textcircled{4}$$

$$\textcircled{3} \text{ in } \textcircled{2} \Rightarrow (8+6j)I + 8I_2 + \frac{(-22+3j)}{8} \left[\frac{(6+4j) I_2 + (-2+4j) I}{8} \right] = 0$$

$$= (8+6j)I + 8I_2 + \frac{-22}{8} \left[(6+4j)I_2 + (-2+4j)I \right] + \frac{3j}{8} \left[(6+4j)I_2 + (-2+4j)I \right]$$

$$= (64 + 42j)I + 64I_2 + (-132 + 88j)I_2 + (44 - 88j)I \\ + (18j - 12)I_2 + (-6j - 12)I = 0$$

$$= (64 + 42j + 44 - 88j - 6j - 12)I + I_2 (64 - 132 + 88j + 18j - 12) = 0$$

$$= (96 - 52j)I + I_2 (-80 + 106j) = 0$$

$$\Rightarrow (48 - 26j)I = (40 - 53j)I_2$$

$$\Rightarrow I_2 = \frac{40 - 53j}{48 - 26j} I$$

$$= \frac{40 - 53j}{\sqrt{48^2 + 26^2}} \left| \tan^{-1} \left(\frac{-26}{48} \right) \right| - \sqrt{2980} \left| -28.442^\circ \right.$$

$$\left. \frac{\sqrt{40^2 + 53^2}}{\sqrt{40^2 + 53^2}} \left| \tan^{-1} \left(\frac{-53}{40} \right) \right| \right. - \sqrt{4409} \left. \left| -52.955^\circ \right. \right.$$

$$I_2 = (0.822 | 24.515^\circ) I$$

$$\text{From } \textcircled{4} \Rightarrow I_2 (12 + 14j) + I (108 + 6j) = 400 | 0^\circ$$

$$I_2 \text{ Polar form of } 12 + 14j = \sqrt{12^2 + 14^2} \left| \tan^{-1} \left(\frac{14}{12} \right) \right| \\ = 18.44 | 49.39^\circ$$

$$\text{Polar form of } 108 + 6j = \sqrt{(108)^2 + 6^2} \left| \tan^{-1} \left(\frac{6}{108} \right) \right| \\ = 108.166 | 3.18^\circ$$

$$\text{From } \textcircled{4} \Rightarrow I_2 (18.44 | 49.39^\circ) + I (108.166 | 3.18^\circ) = 400 | 0^\circ$$

$$(0.822 | 24.515^\circ) (18.44 | 49.39^\circ) + I (108.166 | 3.18^\circ) = 400 | 0^\circ$$

$$15.158 | 73.90^\circ + I (108.166 | 3.18^\circ) = 400 | 0^\circ$$

$$I (108.166 | 3.18^\circ) = 400 | 0^\circ - 15.158 | 73.90^\circ$$

$$400 | 0^\circ$$

$$15.158 | 73.90^\circ \quad \textcircled{5}$$

$$a_1 = 400 \cos 0^\circ = 400$$

$$a_2 = 15.158 \cos (73.90^\circ) = 4.204$$

$$b_1 = 400 \sin 0^\circ = 0$$

$$b_2 = 15.158 \sin (73.90^\circ) = 14.565$$

$$r_1 = 400 + 0j$$


$$r_2 = 4.204 + 14.565j$$

$$r = 404.204 + 14.565j$$

$$\text{Polar form} \Rightarrow \sqrt{404.204^2 + (14.565)^2} \left| \tan^{-1} \left(\frac{14.565}{404.204} \right) \right|$$

$$\begin{aligned}
 &= \sqrt{163380.874 + 212.14} \quad | 2.064^\circ \\
 &= \sqrt{163,593.014} \quad | 2.064^\circ \\
 &= 404.47 \quad | 2.064^\circ \\
 &\text{I} = \frac{404.47}{108.166} \quad | 2.064^\circ \\
 &\text{I} = 3.74 \quad | 2.064^\circ \\
 &\text{I} = 3.74 \quad | -1.116 \Rightarrow |\text{I}| \neq 3.74 \cos \theta
 \end{aligned}$$

Instantaneous & Average Power

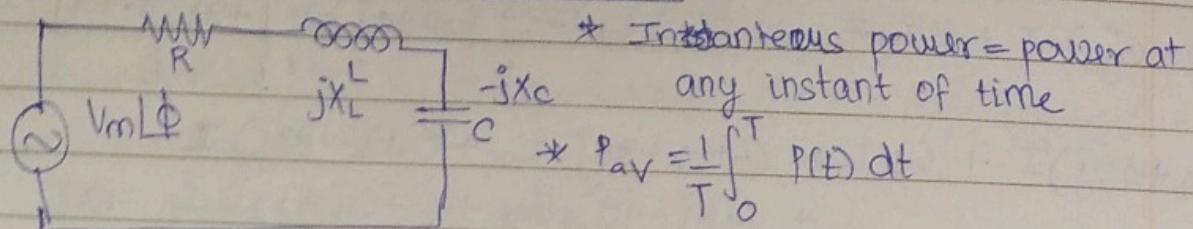

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = V(t) \cdot I(t) = V_m I_m \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$

$$[\cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]]$$

$$\begin{aligned}
 P(t) &= \frac{1}{2} V_m I_m \cos(\omega t + \theta_v - \omega t - \theta_i) + \frac{1}{2} I_m V_m \cos(\omega t + \theta_v + \theta_i) \\
 P(t) &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)
 \end{aligned}$$

integrating

↳ Instantaneous power

$$P_{av} = \frac{1}{T} \int_0^T P(t) dt$$

$$P_{av} = \frac{1}{2} I_m V_m \cos(\theta_v - \theta_i) \Rightarrow P_{av} = I_{rms} \cdot V_{rms} \cdot \cos(\theta_v - \theta_i)$$

Power factor

$$\left[I_{rms} = \frac{I_m}{\sqrt{2}}, \quad V_{rms} = \frac{V_m}{\sqrt{2}} \right]$$

* If 230V DC voltage is supplied to a load & thus it generates a power P, then 230V ~~Vrms~~ AC voltage produces exactly the same amount of power P.

* Vrms, Irms & does not depend on phase but only on peak value.

* Power factor = $\cos \phi = \cos(\theta_v - \theta_i)$
 $\phi = \theta_v - \theta_i$

(i) In resistance circuit, $P_{av} = V_{rms} I_{rms} \cos(0^\circ)$
 $\therefore \theta_V - \theta_I = 0$

$P_{av} = V_{rms} I_{rms}$ (which is of same as DC circuit)

(ii) In inductive circuit, $P_{av} = V_{rms} I_{rms} \cos(0^\circ - (-90^\circ))$
 $P_{av} = 0$

AV power consumed by an inductor is 0.

(iii) which is similar to inductor in DC circuit.

(Inductor in DC circuit will be short circuit)


(iv) In capacitive circuit, $P_{av} = V_{rms} I_{rms} \cos(0^\circ - 90^\circ)$

$$\therefore P_{av} = 0$$

which is similar to ^{capacitor} inductor in DC circuit.

(Capacitor in DC circuit will be open circuited)

* In Resistive circuit

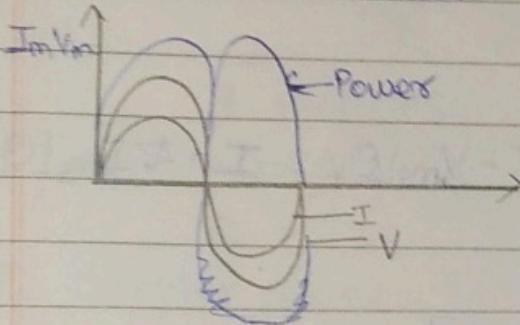


$$P = I_m V_m$$


$$P_{av} = \frac{I_m V_m}{2} = \frac{I_m}{\sqrt{2}} \cdot \frac{V_m}{\sqrt{2}}$$

$$P_{av} = I_{rms} \cdot V_{rms}$$

* In Inductive load.

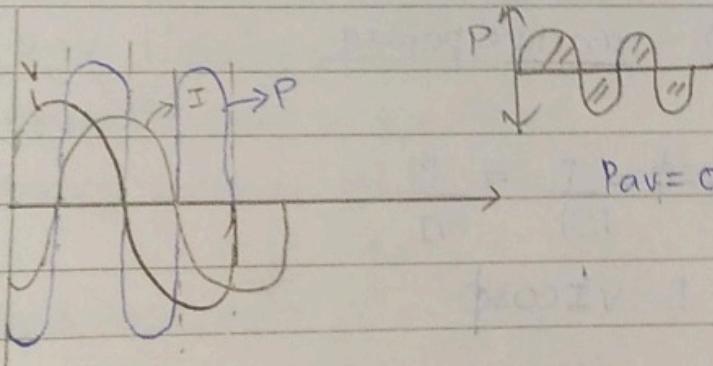

* In capacitive load:-

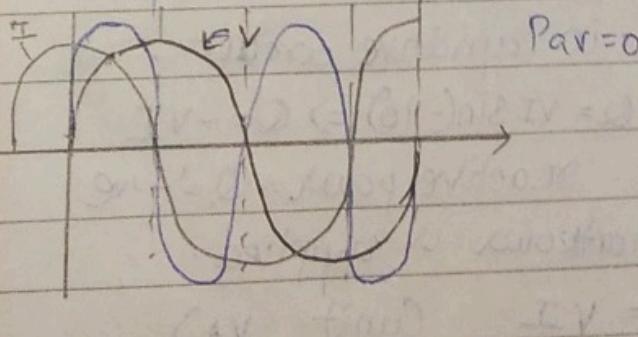

Ex 1: $V(t) = 120 \cos(377t + 45^\circ)$: $I(t) = 10 \cos(377t - 10^\circ)$
 find instantaneous power =?
 average power =?

Ans: $P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m (2vt + \theta_v + \theta_i)$
 $= \frac{1}{2} (120)(10) \cos(45^\circ - (-10^\circ)) + \frac{1}{2} (120)(10) (2(377)t + 45^\circ)$
 $P(t) = 344.1 + 600 \cos(754t + 35^\circ)$
 $P_{av} = \frac{1}{2} (120)(10) \cos(45^\circ - 40^\circ)$
 $P_{av} = 344.1$

Complex Power

$$P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P_{av} = V_m^2 |V| \cos(\theta_v - \theta_i)$$

$$P_{av} = \frac{1}{2} V_m I_m |\theta_v - \theta_i|$$

$$\text{if } V = V_m \angle \theta_v : I = I_m \angle \theta_i$$

$$P = V I^* \leftarrow I \text{ conjugate}$$

$$P = V I \angle \phi \Rightarrow S = V I e^{j\phi}$$


$$S = V I [\cos \phi + j \sin \phi]$$

$$* S = P + jQ \Rightarrow \text{complex power}$$

$$P = V I \cos \phi \Rightarrow \text{real power} \quad (\text{unit: Watt})$$

$$Q = V I \sin \phi \Rightarrow \text{reactive power} \quad (\text{unit: VAR})$$

volt amp reactive

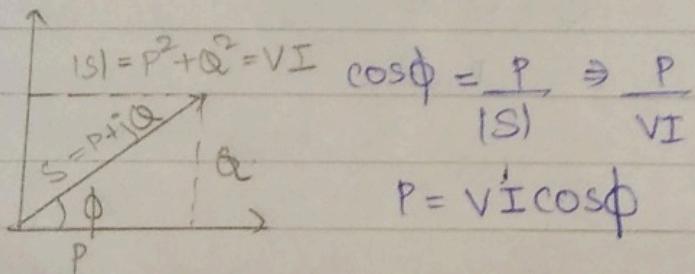

$$\phi = 90^\circ$$

in inductor circuit.

$$Q = VI \sin 90^\circ \Rightarrow Q = VI$$

real active power = $Q = +ve$

reactive power is absorbed

$$\phi = -90^\circ$$

in capacitive circuit.

$$Q = VI \sin(-90^\circ) \Rightarrow Q = -VI$$

real active power = $Q = -ve$


reactive power is supplied.

* Apparent power = $|S| = VI$ (unit: VA)
 $= \sqrt{P^2 + Q^2}$

Problem 1: The voltage across a load is $v(t) = 60 \cos(\omega t - 10^\circ)$ V & the current through the element in the direction of voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ)$ A. Find the

- complex & apparent powers.
- real & reactive powers
- Power factor & load impedance

Solution:

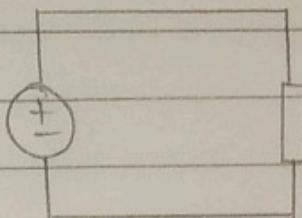

Given:-

$$v(t) = 60 \cos(\omega t - 10^\circ) = 60 \angle -10^\circ$$

$$i(t) = 1.5 \cos(\omega t + 50^\circ) = 1.5 \angle 50^\circ$$

a) complex power = $VI \cos\phi + j VI \sin\phi$

b) real power = $VI \cos\phi = V_{rms} \cdot I_{rms} \cdot \cos\phi$
 $= \frac{60}{\sqrt{2}} \cdot \frac{1.5}{\sqrt{2}} \times \cos(-10^\circ - 50^\circ)$

$$P = 22.5 \text{ W}$$

reactive power = $VI \sin\phi = \frac{60}{\sqrt{2}} \cdot \frac{1.5}{\sqrt{2}} \cdot \sin(-60^\circ)$
 $Q = -38.97 \text{ VAR}$

c) complex power = $S = P + j Q$
 $= 22.5 + j (-38.97)$
 $= 22.5 - 38.97j$

apparent power = $|S| = \sqrt{P^2 + Q^2} = \sqrt{62.5^2 + (38.97)^2}$
 $= \sqrt{506.25 + 1518.66} = \sqrt{2024.9109}$

apparent power = 44.99 W

c) Power factor = $\cos\phi = \cos(0^\circ - 60^\circ) = \cos(-10^\circ - 50^\circ)$
 $= \frac{1}{2} = 0.5$

load impedance $\frac{V}{I} = \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ} = 40 \angle -60^\circ$

$$a = 40 \cos(-60^\circ) = 20 ; b = 40 \sin(-60^\circ) = -34.641$$

$$\therefore Z = 20 + 34.641j$$