

SUPERPOSITION PRINCIPLE

①

If a circuit is linear it obeys

Superposition + homogeneity.
(additivity) (scaling)


LINEAR

Output \propto input.

In a dc circuit, $V \propto I$. Linear.

But $P = I^2 R = \frac{V^2}{R}$ (non-linear).

Example

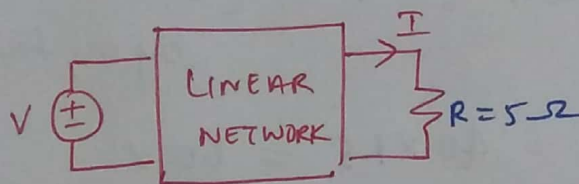

$V = \text{Input}$
 $I = \text{Output}$


If $V = 10 \text{ V}$ $I = \frac{10}{5} = 2 \text{ A}$

If $V = 1 \text{ V}$ $I = \frac{1}{5} = 0.2 \text{ A}$


If $V = 100 \text{ V}$ $I = \frac{100}{5} = 20 \text{ A}$

Scaled by
same
factor.


(HOMOGENEITY)

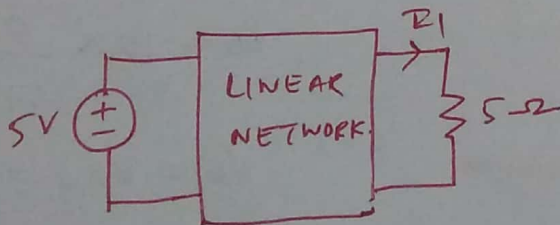

$I_1 = 1 \text{ A}$

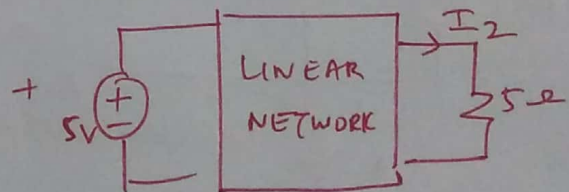

$I_2 = 1 \text{ A}$

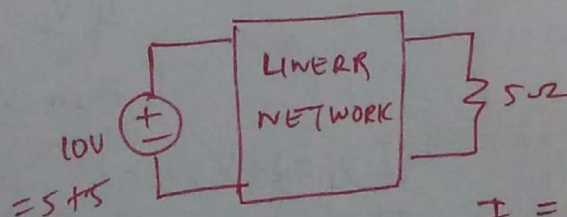


$I = 2 \text{ A} = I_1 + I_2$

(SUPERPOSITION - ADDITIVITY)

②

LINEARITY EXAMPLE

①

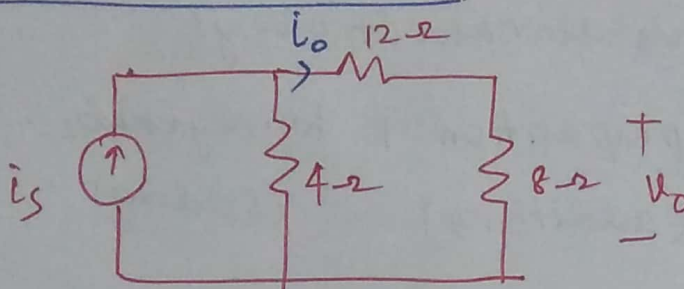

Find V_o , when

$$i_s = 30 \text{ A}$$

$$i_s = 45 \text{ A}$$

when $i_s = 30 \text{ A}$,

$$i_o = 30 \times \frac{4}{4+8+12} = 5 \text{ A}$$

$$V_o = 8 \times 5 = 40 \text{ V}$$


when $i_s = 30 \text{ A}$, $V_o = 40 \text{ V}$

$$\frac{45}{30} = 1.5$$

By linearity, when $i_s = 45 \text{ A}$ (current increased by a factor 1.5)

$$\therefore \text{voltage } V_o = 40 \times 1.5 = 60 \text{ V}$$

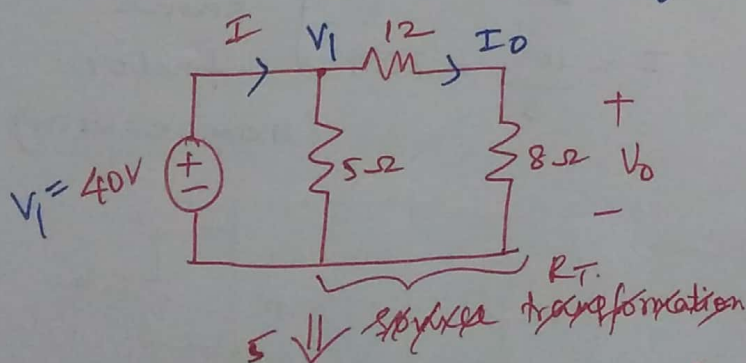
② Assume $V_o = 1 \text{ V}$, using linearity calculate the actual value of V_o in the circuit.



$$\therefore I = \frac{40}{4} = 10 \text{ A}$$

$$I_o = 10 \times \frac{5}{5+20} = 2 \text{ A}$$

$$V_o = 8 \times 2 = 16 \text{ V}$$

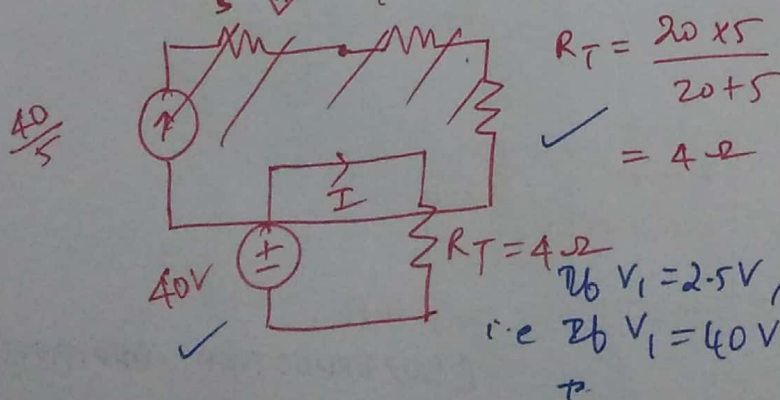

By linearity,

$$\text{If } V_o = 1 \text{ V} \rightarrow I_o = \frac{1}{8} \text{ A}$$

$$\text{then } V_1 = \frac{1}{8} \times 20 = \frac{5}{2}$$

$$V_1 = 2.5 \text{ V}$$


$$V_o = 16 \text{ V}$$

SUPERPOSITION

1. In a given circuit, consider one source at a time and solve.
 2. Net Result = Sum of individual output.
- when considering one source, turn off all other independent sources.
i.e. OC - current source; SC - voltage source.

Example


①

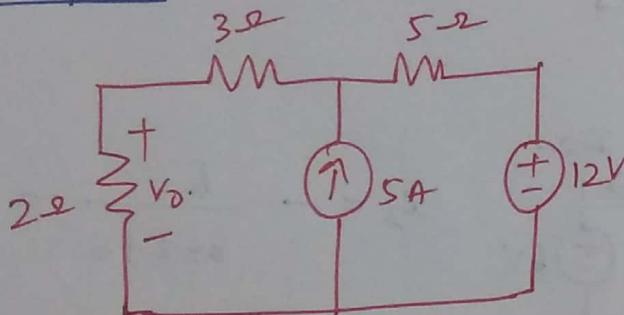

Find V_o using Superposition..

$$V_o = V_o^1 + V_o^2$$

due to two sources.

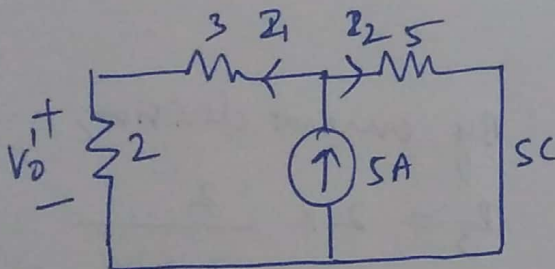


By current division,

$$I_1 = 5 \times \frac{5}{5+2+3}$$

$$I_1 = 2.5 \text{ A}$$

$$V_o^1 = 2 \times 2.5$$

$$V_o^1 = 5 \text{ V}$$

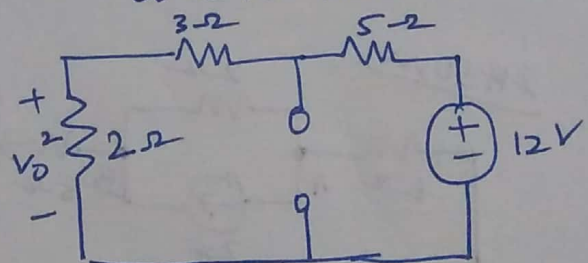

By voltage division,

$$V_o^2 = 12 \times \frac{2}{2+3+5}$$

$$V_o^2 = 2.4 \text{ V}$$


By superposition

$$V_o = 5 + 2.4 = 7.4 \text{ V}$$

$$\underline{V_o = 7.4 \text{ V}}$$


4

② Find I using Superposition.

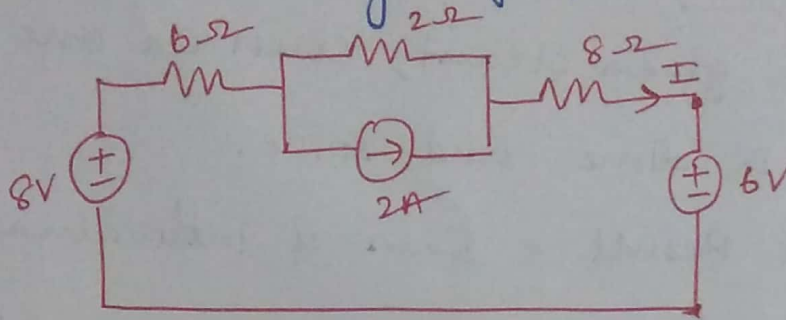


Solve considering 1 source at a time. $I = I_1 + I_2 + I_3$

8V Source.

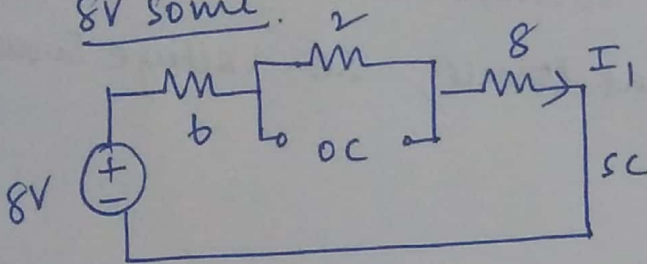


$$I_1 = \frac{8}{8+2+6} = 0.5 \text{ A}$$

6V Source

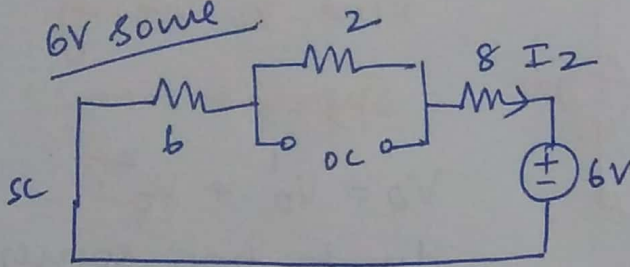

$$I_2 = -\frac{6}{8+2+6} = -0.375 \text{ A}$$

2A Source.

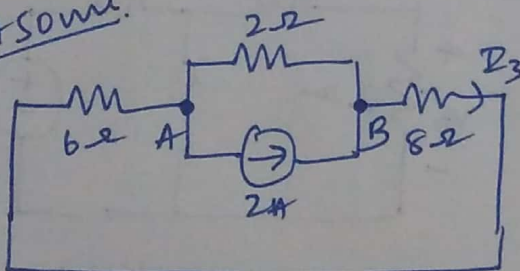


By current division,

$$I_3 = 2 \times \frac{2}{2+14}$$

$$I_3 = 0.25 \text{ A}$$

6, 8 series $\Rightarrow 14$

14 in parallel to 2

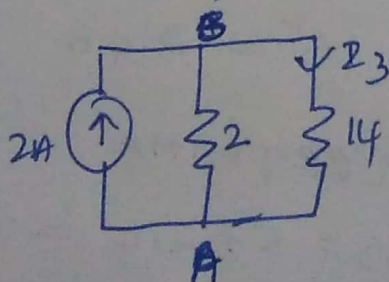

By superposition,

$$I = 0.5 - 0.375 + 0.25$$

$$I = \underline{\underline{0.375 \text{ A}}}$$