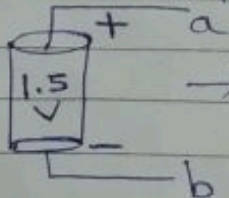


Electrical engineering

Voltage \rightarrow unit is J/C or Volt
 \downarrow also can be called potential difference

if a battery rated 1150mAh number of charges
 $\rightarrow 1150 \times 10^{-3} \frac{C}{Sec} \times 3600$

$$= 4140 C$$




$$\rightarrow V_{ba} = -1.5V, V_{ab} = 1.5V$$

$$P = VI \rightarrow \frac{J}{C} \times \frac{C}{S} = \frac{J}{S} = W$$


Power unit $\rightarrow J/S = W$

active sign convention \rightarrow

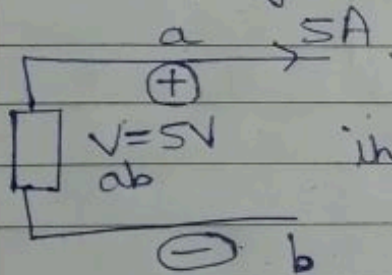


in this Power Supplied = 25W

Passive sign convention \rightarrow

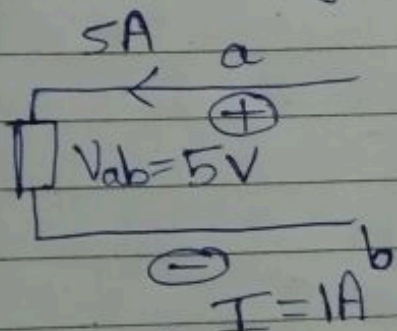

power absorbed = 25W

Q)

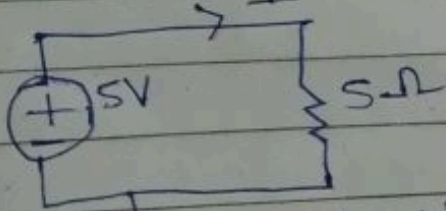


Ans)

$$I = \frac{V_a - V_b}{5\Omega} = 1A$$

for Source \rightarrow active sign convention
 so Power supplied $= 5 \times 1 = 5W$

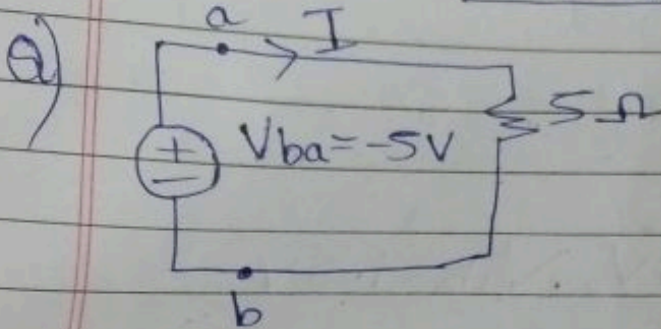for Resistor \rightarrow passive sign convention
 so Power absorbed $= 5 \times 1 = 5W$




ans) $V_{ba} = -5$

$$\text{Power absorbed} = V_{ba} \times I$$

$$= -5W.$$

Basically \rightarrow

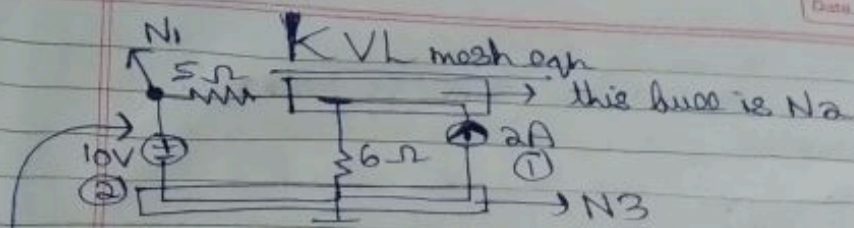if entering $+$ \rightarrow Passive
 if leaving $+$ \rightarrow active



Terms →

- ① is independent current source
- ② is independent voltage source


there are 4 branches in this 3 element → branch?
 { 1 with V source, 2 with 5Ω, 6Ω resp., 1 with current source }

Nodes → where branches join.

N₁, N₂, N₃ are nodes

Note - if no components after intersection of two branches → whole area is node.

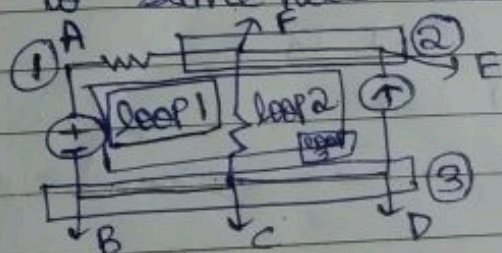loops → start from one node and come back to same node then loop formed.



AFCB → loop 1


AEDB → loop 2

FCDE → loop 3

independent loop → formula → $L = b - n + 1$
 ↓ combinations of 2 loops which covers all branches/elements → independent loop
 or

loop which contains atleast 1 branch which isn't present in any other independent loop

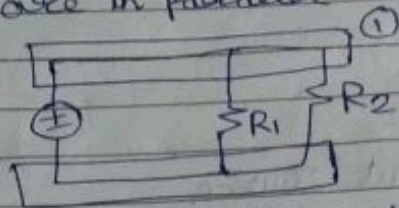
if any 2 element between same 2 nodes they are in parallel



$$R1, R2 \rightarrow ||$$

KVL mesh equation

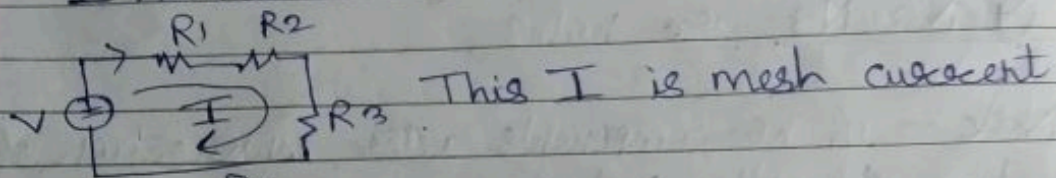
$$\sum V \text{ in circuit} = 0 \rightarrow \text{KVL}$$



Current through $R1 \rightarrow I1$

through $R2 \rightarrow I2$

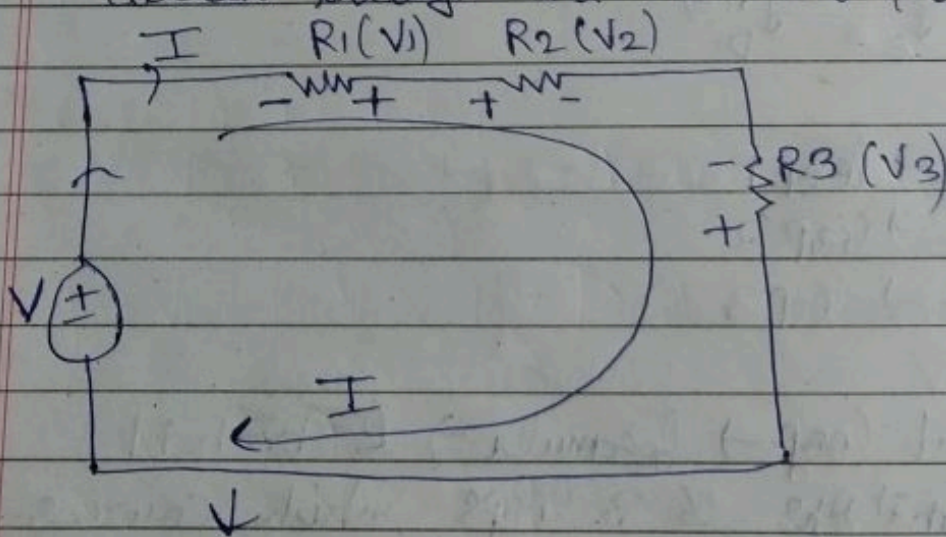current through $R2 \rightarrow I1 - I2$? Branch current




$$\sum V_{active} = \sum V_{passive}$$

$$V + V1 + V3 = V2$$

If current entering + of Resistor $\rightarrow IR$
 if current leaving + of Resistor $\rightarrow -IR$
 or
 Resistor is in active sign $\rightarrow -IR$
 Resistor is in passive sign $\rightarrow IR$

$$20V - IR_1 - IR_3 = IR_2$$

$$\text{or } V = I(R_1 + R_2 + R_3)$$

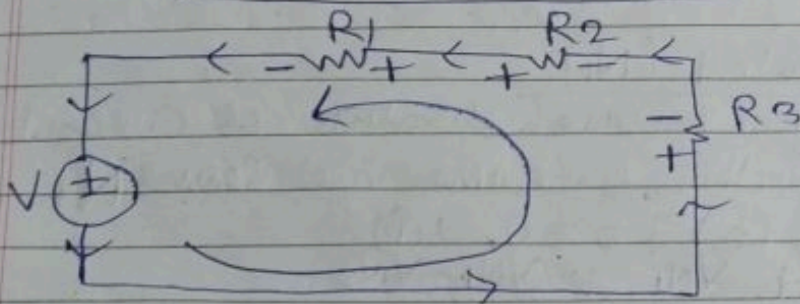


in this \rightarrow

$$\sum V_{\text{passive}} = \sum V_{\text{active}}$$

$$V_3 + V_1 + V = V_2$$

$$\text{or } V = I(R_1 + R_2 + R_3)$$

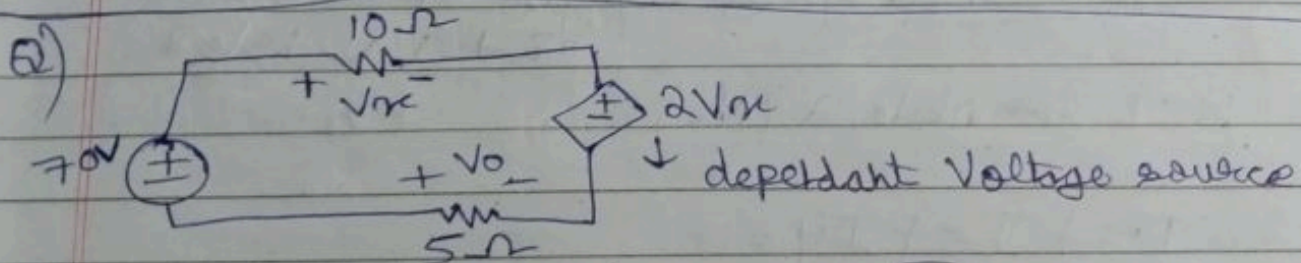

ans) assume direction as

$$\sum V_{\text{active}} = \sum V_{\text{passive}}$$

$$70 + V_0 = V_x + 2V_x$$

$$70 + V_0 = 3V_x$$

now $V_x = 10I$, $V_0 = -5I$

so


$$70 - 5I = 30I$$

$$\boxed{I = 2A}$$

$$V_0 = -10V, V_x = 20V$$

KCL / Nodal analysis
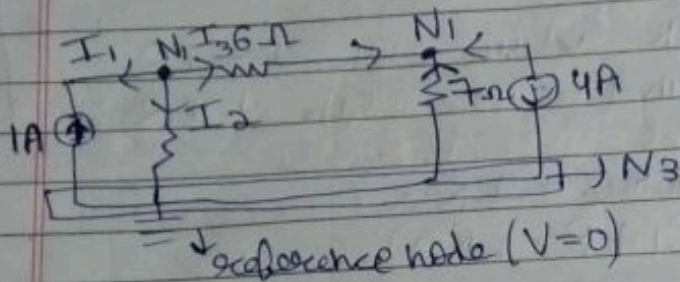
$$\sum I_{\text{entering}} = \sum I_{\text{leaving}}$$



→ KCL for node 1 (N1)

(arbitrarily assume direction of current from N1, in this I assume all leaves N1)

$$\rightarrow \text{so } I_1 + I_2 + I_3 = 0 \rightarrow \textcircled{1}$$

$$\rightarrow 0 = -1 + \frac{V_{N1}}{6} + \frac{V_{N1} - V_{N2}}{7}$$

$\left\{ \begin{array}{l} I_1 = -1A \text{ as opposing } 1A \text{ of current source} \\ V_{N1} \rightarrow V \text{ at Node 1} \\ V_{N2} \rightarrow V \text{ at Node 2} \end{array} \right\}$

$$\rightarrow \boxed{6 = 4V_1 - V_2} \rightarrow \textcircled{2} \quad \left\{ \begin{array}{l} V_1 \rightarrow V \text{ at node 1} \\ V_2 \rightarrow V \text{ at node 2} \end{array} \right\}$$

→ KCL for Node 2 (N2)


$$I_3 + I_5 + I_4 = 0$$

$$\frac{V_1 - V_2}{6} + \frac{(-V_2)}{7} - 4 = 0$$

$$\boxed{7V_1 - 13V_2 = 168} \rightarrow \textcircled{3}$$

solve $\textcircled{2}, \textcircled{3}$

$$V_1 = -2, V_2 = -14 \text{ (ans)}$$

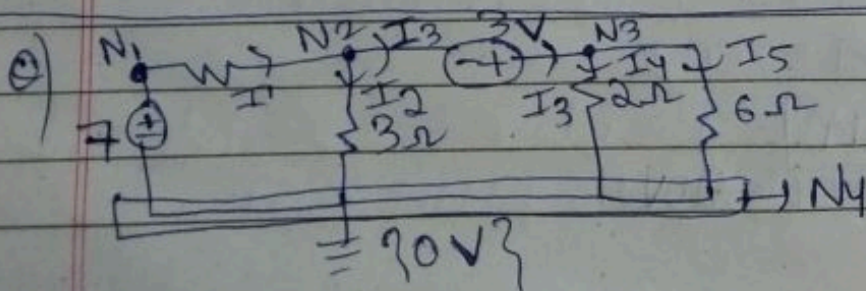

ans) $V_{N1} = V_1, V_{N2} = V_2, V_{N3} = V_3, V_{N4} = 0$ and node?

now $V_1 = 7V$ as voltage source of $7V$

now KCL for Node 2

$$I_1 = I_2 + I_3$$

$$\frac{7 - V_2}{4} = \frac{V_2}{3} + I_3 \rightarrow \text{leave } I_3 \text{ as is?}$$

KCL for Node 3

$$I_3 = I_4 + I_5$$

$$I_3 = \frac{V_3}{2} + \frac{V_3}{6} \rightarrow (2)$$

now eliminate I_3 , { (2) in (1) }

$$\frac{7 - V_2}{4} = \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6}$$

$$21 - 3V_2 = 4V_2 + 6V_3 + 2V_3$$

$$7V_2 + 8V_3 = 21 \rightarrow (3)$$

$$V_3 - V_2 = 3 \rightarrow$$

solving \rightarrow


$$V_2 = \frac{-1}{5} = -0.2V$$

$$V_3 = 2.8V$$

Voltage source + sign
whenever - Voltage source
sign = Voltage of source
or

whenever we have a voltage
source marked + and -
we understand that
potential of marked +
wrt - terminal is voltage
of source.

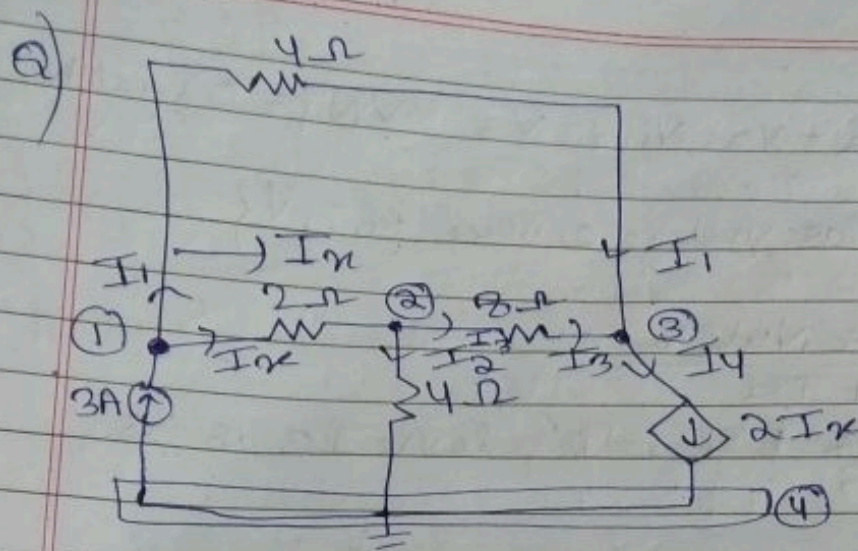~~xxxxxx~~
Note $\forall \forall \forall$ imp



ans) Node 1 →

$$3 = I_1 + I_x$$

$$3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} \quad \text{--- (1)}$$

Node 2 → $I_x = I_2 + I_3$

$$\frac{V_1 - V_2}{2} = \frac{V_2}{4} + \frac{V_2 - V_3}{8} \quad \text{--- (2)}$$


Node 3 → $I_3 + I_1 = 2I_x$

$$\frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4} = 2 \left(\frac{V_1 - V_2}{2} \right) \quad \text{--- (3)}$$

Solving →


$$\begin{aligned} V_1 &= 4.8V \\ V_2 &= 2.4V \\ V_3 &= -2.4V \end{aligned}$$

(ans)

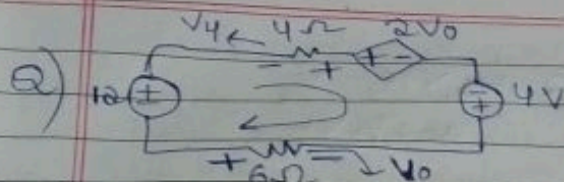

ans) $\sum V_{active} = \sum V_{passive}$
 $V_4 + 4 + V_0 + 12 = 2V_0$
 $-4I + 4 - 6I + 12 = -12I$
 $\boxed{I = -8A}$

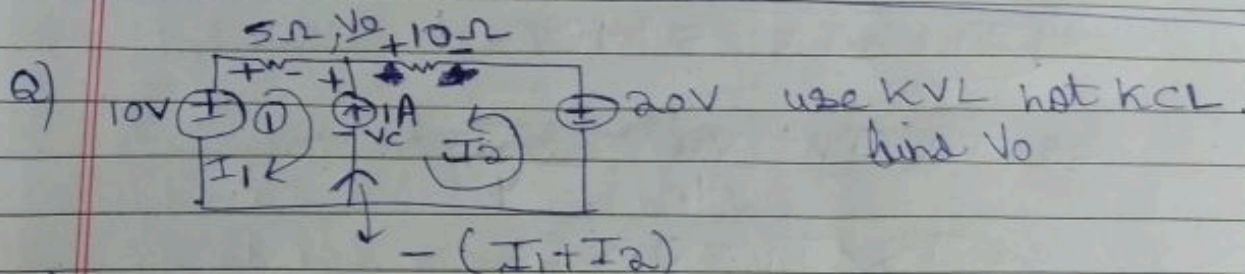$V_0 = -6I = 48V$ (ans), $V_4 = -4I = 32A$
 Power absorbed by 4V = $4 \times 8 = 32W$.



ans) loop ① $\rightarrow \sum V_{active} = \sum V_{passive}$
 $10 = V_0 + V_c$
 $10 = 5I_1 + V_c$
 $\boxed{V_c = 10 - 5I_1} \rightarrow ①$


loop ② $\rightarrow \sum V_{active} = \sum V_{passive}$
 $20 + V_{10} = V_c$
 $\boxed{20 - 10I_2 = V_c} \rightarrow ②$

$20V_0 = 5I_1$
 $= -\frac{20V}{3}$ (ans)

and $-(I_1 + I_2) = 1$
 $\boxed{I_1 + I_2 = -1} \rightarrow ③$

from ① and ②
 $10 - 5I_1 = 20 - 10I_2$
 $\rightarrow \boxed{5I_1 - 10I_2 = -10} \rightarrow ④$

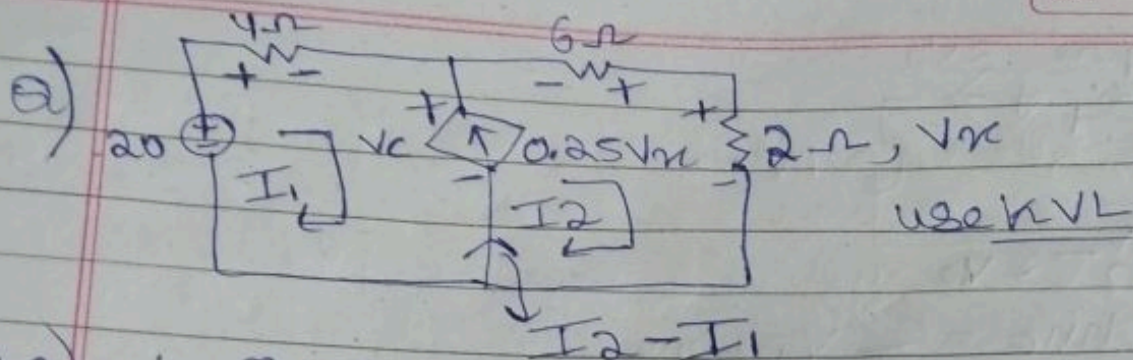so $I_2 = \frac{1}{3}A, I_1 = -\frac{4}{3}A$



ans) in ① →

$$20 = V_4 + V_c$$

$$\boxed{20 - 4I_1 = V_c} \rightarrow \text{①}$$

in ② → $V_c + V_6 = V_x$

$$\boxed{V_c = 8I_2} \rightarrow \text{②}$$

$$20 - 4I_1 = 8I_2$$

$$\rightarrow \boxed{I_1 + 2I_2 = 5} \rightarrow \text{③}$$

$$\text{so } I_2 - I_1 = \frac{V_x}{4} = \frac{2I_2}{4}$$

$$\text{so } I_2 - I_1 = 0.5I_2$$

$$\boxed{0.5I_2 = I_1}$$

$$\boxed{I_1 = 1A, I_2 = 2A} \text{ (ans)}$$


$$\text{so } V_x = 4V.$$

Superposition Theorem


Linear system \rightarrow obeys superposition and homogeneity
Homogeneity: if input is changed by a factor a , output also changes by a .

$$\left. \begin{array}{l} \text{ex} \rightarrow \text{if } V=1 \rightarrow i=1 \\ V=5 \rightarrow i=5 \end{array} \right\} \text{assuming } R=1\Omega$$

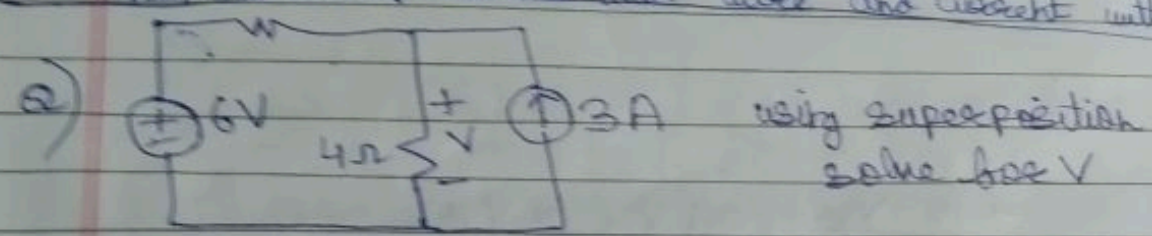Superposition \rightarrow for all linear systems, net response by 2 or more inputs is sum of responses/outputs caused by each input individually.
Replace voltage source with wire and current with open.




Ans) (i) $V=6V, I=0A$

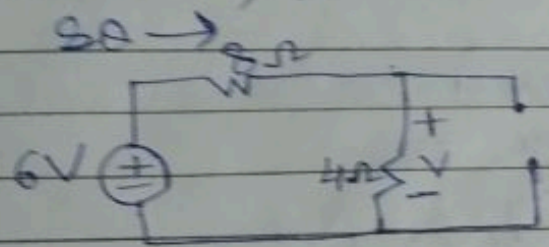

$$I = \frac{6}{12} = 0.5A$$


$$\text{so } V_1 = 0.5 \times 4 = 2V$$

(ii) $V=0V, i=3A$

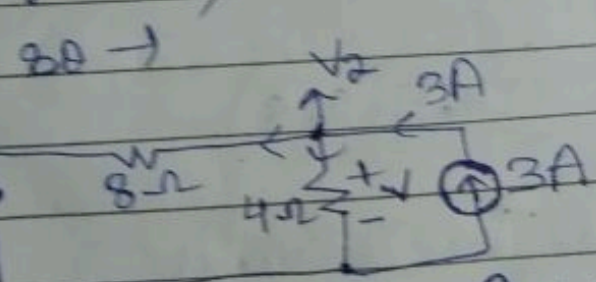


$$3 = \frac{V_2 - 0}{4} + \frac{V_2 - 0}{8} \quad \text{so } \boxed{V_2 = 8V}$$

so $V_{4\Omega} = 2V + 8V = 10V$ (ans)

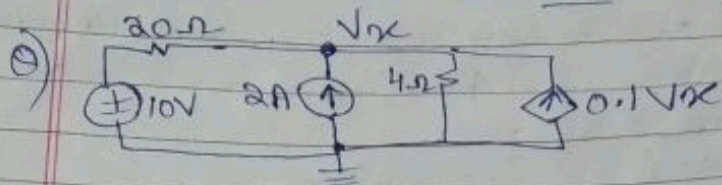

find V_x

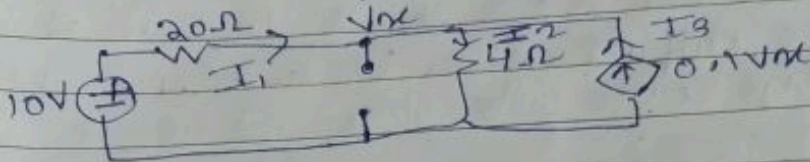ans) (i) consider only voltage source \rightarrow




Kcl at $V_x \rightarrow$

$$\rightarrow I_1 + I_3 = I_2$$

$$\rightarrow \frac{10 - V_x}{20} + 0.1 V_x = \frac{V_x}{4}$$

$$V_x = 2.5V$$

(ii) only current source \rightarrow

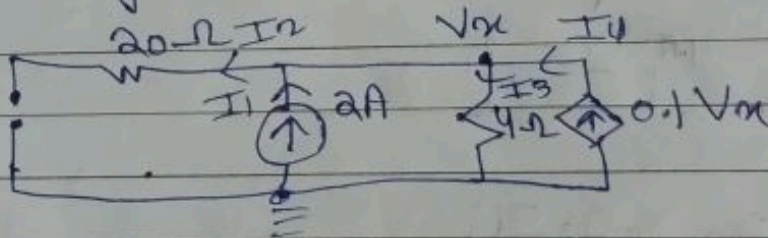


$$I_1 + I_4 = I_2 + I_3$$

$$2 + 0.1 V_x = \frac{V_x}{20} + \frac{V_x}{4}$$

$$V_x = 10V$$

so $V_x = 10 + 2.5 = 12.5$ (ans)

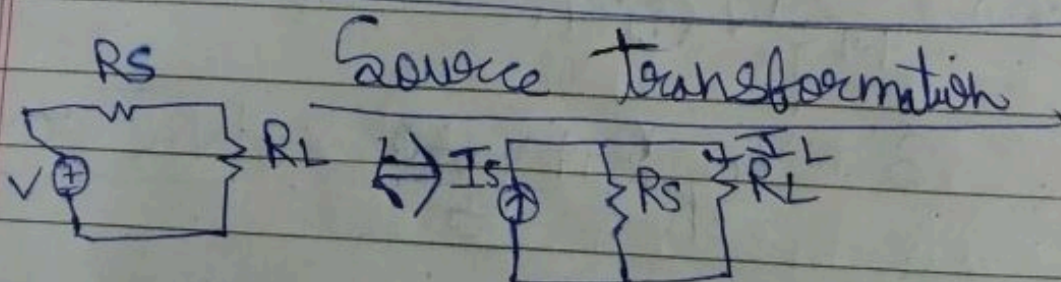

to do this $V_L \text{ voltage} = V_L \text{ current}$

so $V_L \text{ voltage} = \frac{V R_L}{R_S + R_L} \rightarrow (1)$


$I_L = \frac{I_S R_S}{R_L + R_S}$

so $V_L \text{ current} = \frac{I_S R_S \times R_L}{R_L + R_S} \rightarrow (2)$





comparing (1) and (2)

we get $V = I_S R_S$

so $I_S = \frac{V}{R_S}$

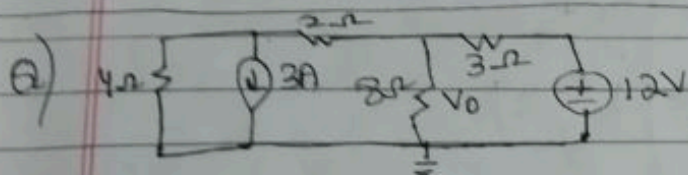

ans) find $V_0 \rightarrow$

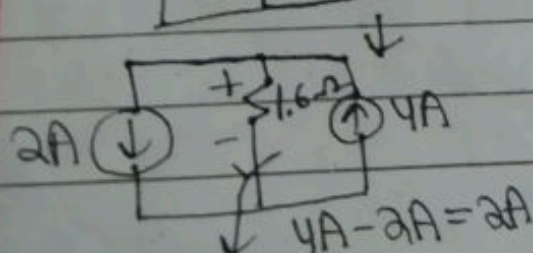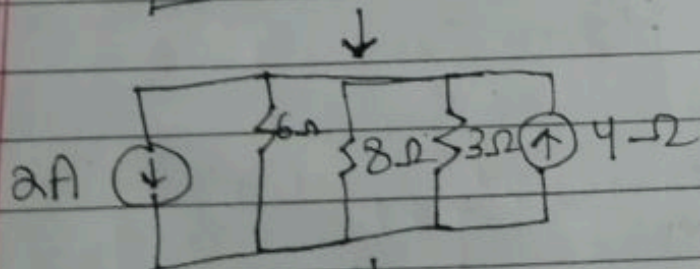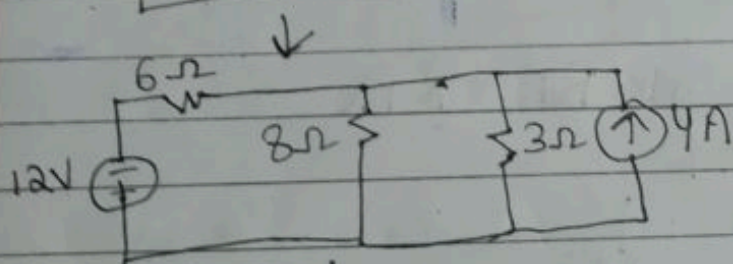
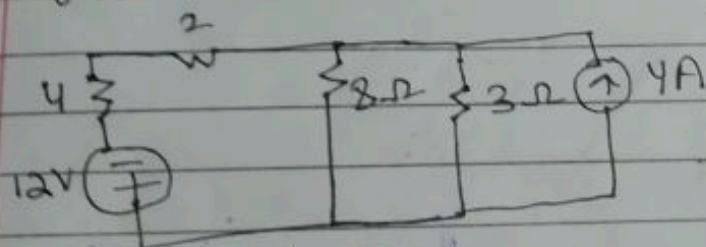


so $V_0 = 2 \times 1.6 = 3.2V \text{ (ans)}$


Max power transfer theorem




R_L	P
5Ω	$5W$
3Ω	$8.33W$
2Ω	$12.5W$
1Ω	$25W$
0.5Ω	$50W$
0.05Ω	$100W$

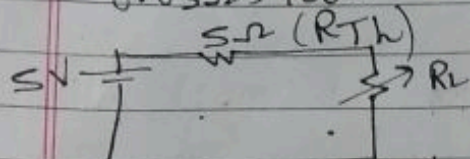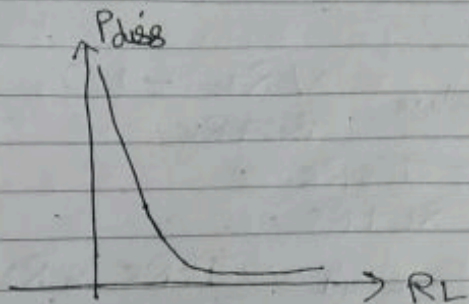

R_L	I	P_{RL}
10	0.66	1.089
6	$\frac{5}{11}$	1.215
5	$\frac{1}{2}$	1.25
2.5	$\frac{5}{4.5}$	1.089
0	1	0

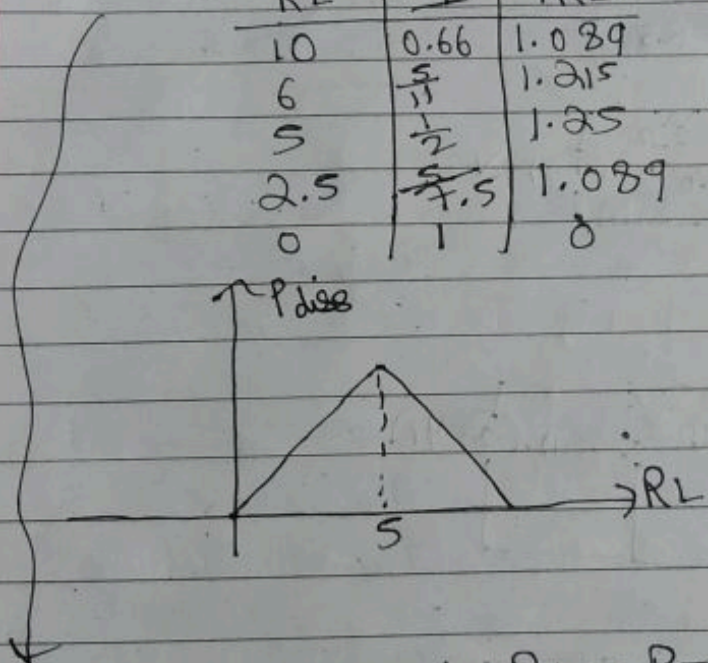


max power at $R_L = R_{TH}$

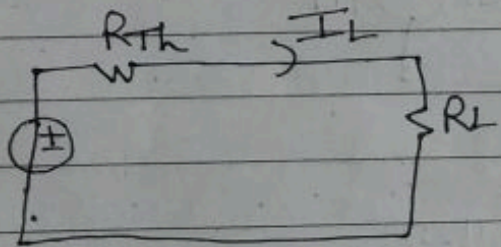

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$P_{RL} = \frac{V_{th}^2}{(R_{th} + R_L)^2} \times R_L$$

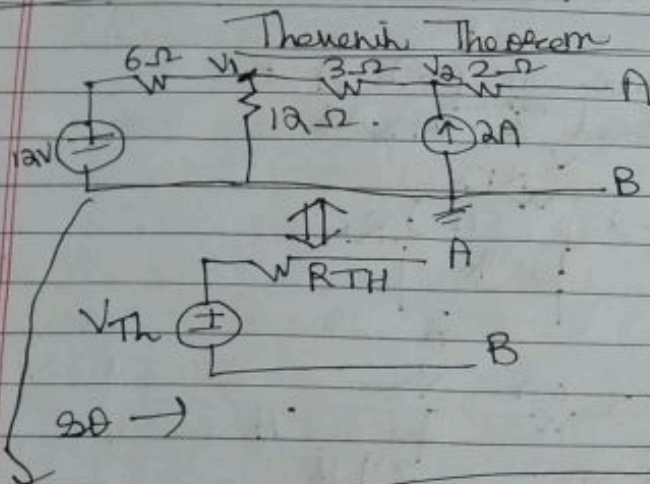how we maximize P_{RL}
and get $[R_L = R_{TH}]$ ✓✓✓✓




$$Kcl \rightarrow ① \quad \frac{12 - V_1}{6} = \frac{V_1}{12} + \frac{V_1 - V_2}{3} \quad \rightarrow ①$$

$$Kcl \rightarrow ② \quad \frac{V_1 - V_2}{3} + 2 = 0 \rightarrow V_1 - V_2 = -6 \quad \rightarrow ②$$

$$V_2 = 22V, \quad V_1 = 16$$

$$V_{AB} = V_2 = 22V$$

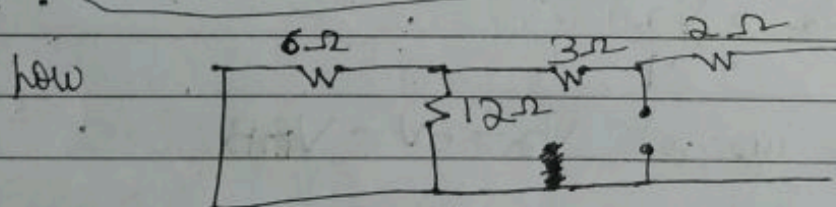


$$R_{eq} = R_{th} = 9\Omega \quad \left\{ \begin{array}{l} 6\Omega \text{ in } ||, 5\Omega \text{ series} \end{array} \right\}$$

as in R_{th} we need independent voltage source and current source to be 0 so we remove them


Basicly to find $V_{th} \rightarrow$ remove load resis-

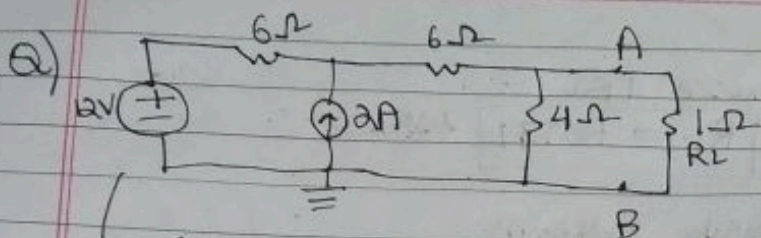tor and find open circuit ~~current~~ Voltage




find max power at port A, B
and $P_{\text{transferred}}$ when 1Ω is connected

ans)

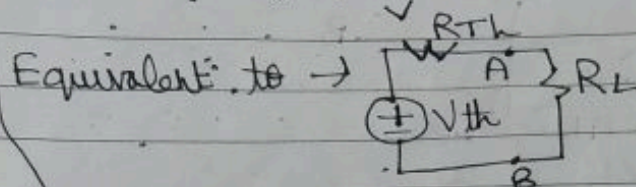

so \downarrow

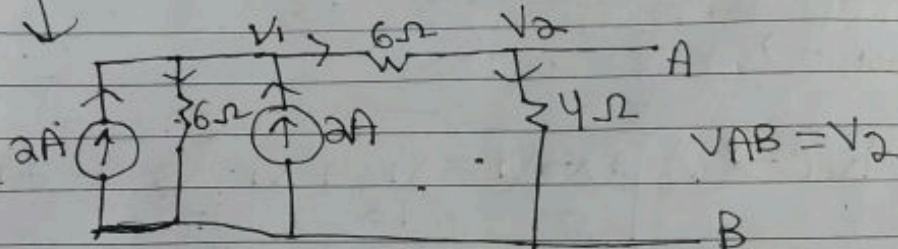

$$\textcircled{1} \rightarrow 2 + 2 = \frac{V_1}{6} + \frac{V_1 - V_2}{6}$$


$$\rightarrow 2V_1 - V_2 = 24$$

$$\textcircled{2} \rightarrow \frac{V_1 - V_2}{6} = \frac{V_2}{4}$$

solving we get $V_2 = 6V = V_{AB}$


so open circuit voltage $= 6V = V_{th}$

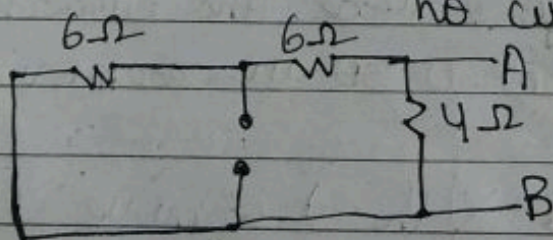now $R_{eq} = R_{th}$ } No indep voltage source
no current source



\downarrow
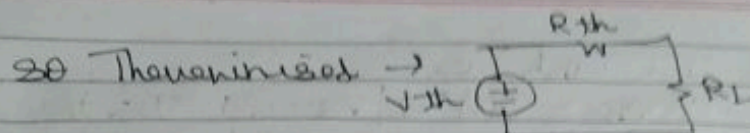
$$12\Omega \parallel 4\Omega \rightarrow 3\Omega = R_{th}$$




$$\rightarrow P_{max} = \left(\frac{6V}{6\Omega} \right)^2 \times R_L$$

for max power $R_L = R_{th}$

$$\text{so } \rightarrow \boxed{P_{max} = 3W}$$

for (b) 1-2 connected


so thevenin circuit \rightarrow

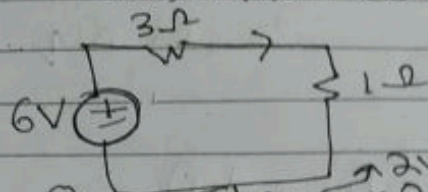

$$P_{1\Omega} = (1.5)^2 \times 1$$


$$= 2.25W \text{ (ans)}$$

a)

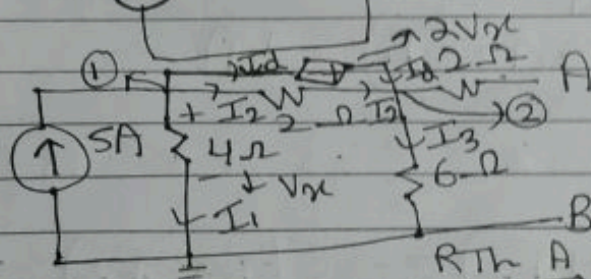

ans)

equivalent to \rightarrow

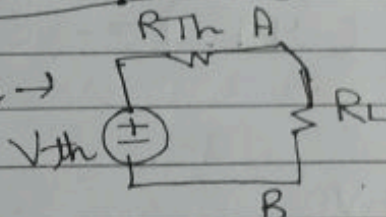

$$\downarrow V_{AB} = V_2$$

using KCL ①

$$\rightarrow 5 = \frac{V_1}{4} + \frac{V_1 - V_2}{2} + I_d$$

$$\rightarrow 20 = V_1 + 2V_1 - 2V_2 + I_d \times 4$$

$$\rightarrow \boxed{2V_1 - 2V_2 = 20 - 4I_d}$$

for ②

$$\rightarrow \frac{I_d + V_1 - V_2}{2} = \frac{V_2}{6}$$


$$\rightarrow \boxed{6I_d = -3V_1 + 4V_2}$$

eliminate I_1 and use

$$V_2 - V_1 = 2V_x = 2V_1 \rightarrow V_2 - 3V_1 = 0 \rightarrow (3)$$

we get $V_2 = V_{AB} = V_{th} = 20V$

now $R_{th} \rightarrow$

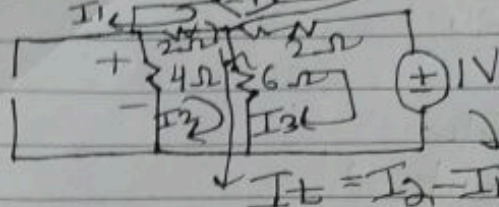

$$I_t = I_2 - I_1$$

added so we can find I and use $V = IR$ to find R_{eq} .

using KVL $\rightarrow (1)$

$$2V_x = V_2$$

$$2(-4I_2) = -2(I_2 - I_1) \rightarrow (1)$$

for loop (2)

$$V_x + V_{21} = V(6\Omega)$$

$$-2(I_2 - I_1) + (-4I_2) = -6(I_3 - I_2) \rightarrow (2)$$

for loop 3 \rightarrow

$$V_{6\Omega} = V_{22} + V$$

$$-6(I_3 - I_2) = 2I_3 + 1 \rightarrow (3)$$


$$\text{we get } I_3 = -\frac{1}{6}$$

$$\text{so } I_3 \times R_{th} = 1V$$


$$\text{so } R_{th} = 6\Omega$$

so for max power $R_L = 6\Omega$
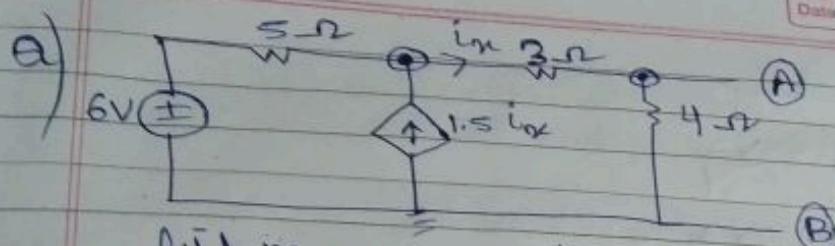
$$\text{and max power} = \left(\frac{20}{12}\right)^2 \times 6 \text{ (ans)}$$



find max power at A-B port

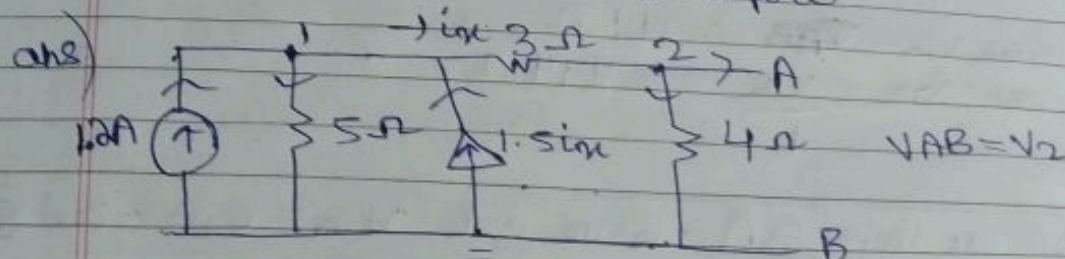

$$\text{Kcl ①} \rightarrow 1.2 + 1.5 I_x = \frac{V_1}{5} + I_x$$

$$I_x = \frac{V_1 - V_2}{3}$$

$$\text{so } 1.2 = \frac{V_1}{5} - 0.5 \left(\frac{V_1 - V_2}{3} \right) \rightarrow \text{①}$$


$$\text{Kcl ②} \rightarrow \frac{V_1 - V_2}{3} = \frac{V_2}{4}$$

$$\rightarrow 4V_1 - 7V_2 = 0 \rightarrow \text{②}$$

~~Find V_2~~

$$\boxed{V_2 = 5.33V} = V_{th}$$

For $R_{th} \rightarrow$

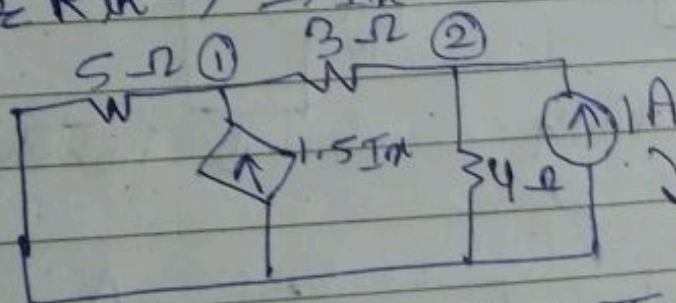

2 added to find R_{eq}

$$\text{at ① } 1.5 I_x = \frac{V_1}{5} + I_x$$

$$\rightarrow 0.5 I_x = \frac{V_1}{5} \rightarrow \boxed{\frac{V_1 - V_2}{6} = \frac{V_1}{5}} \rightarrow \text{①}$$

at (2)


$$\rightarrow ix + 1 = \frac{V_2}{4}$$

$$\rightarrow \frac{V_1 - V_2 + 1}{3} = \frac{V_2}{4}$$

now $V_2 = \cancel{0.444} \Omega$

$$\text{so } R_{th} = \frac{V_2}{1} = 0.444 \Omega$$

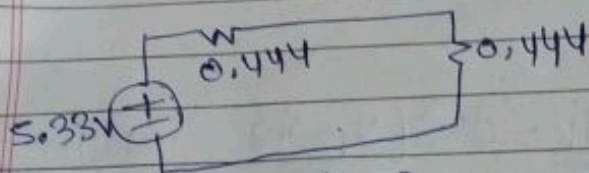
if we took 2A we we get $V_2 = 0.888 \text{ due to linearity}$




$$\downarrow P_{max} = \left(\frac{5.33}{0.888} \right)^2 \times 0.444$$

Norton equivalent

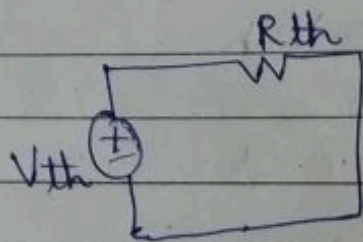
connect V_{th} to a current source, and that is Norton equivalent.



\downarrow Thevenin eq

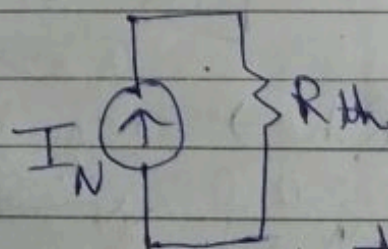

\downarrow Norton eq

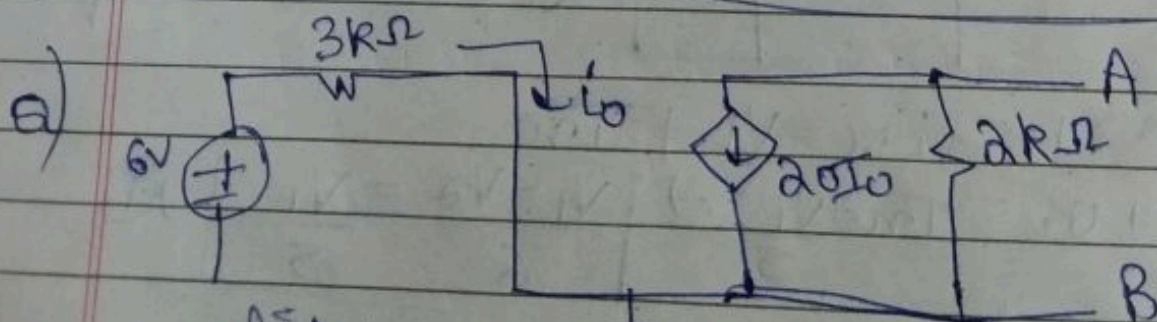

find max power =

ans) as open circuit current through $2k = 20I_0$
 so $V_{AB} = 20I_0 \times 2k \times -1$


↓ opposite direction

$$V_{AB} = -40I_0 \times 10^3$$

now in (i) $\rightarrow I_0 = \frac{6}{3k\Omega} = 2 \times 10^{-3} A$

$$\text{so } V_{AB} = -80V = V_{th}$$

$R_{th} \rightarrow$

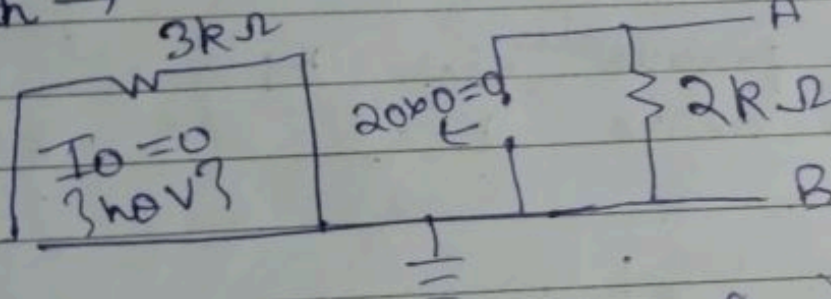

$$\text{so } R_{th} = 2k\Omega. (\text{ans})$$