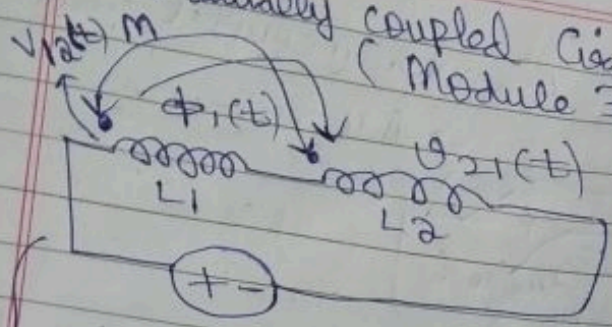




Mutually coupled Circuits (Module 3)



$V_{21} \rightarrow$ voltage in L_2 due to flux of L_1

$V_{12} \rightarrow$ voltage in L_1 due to flux of L_2

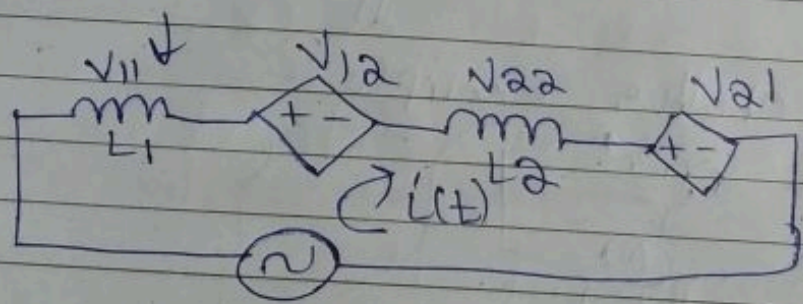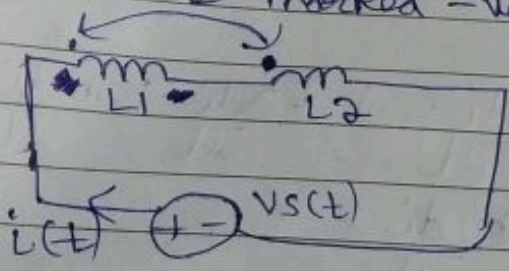When current enters the dotted terminal \rightarrow next dotted terminal will be +
 \leftarrow current leaving dotted \rightarrow next dotted will be marked -ve.





$\sum \text{active} = \sum \text{passive}$

$$V_s(t) = V_{11}(t) + V_{12}(t) + V_{22}(t) + V_{21}(t)$$

$$V_s(t) = \frac{L_1 di}{dt} + \frac{M di}{dt} + \frac{L_2 di}{dt} + \frac{M di}{dt}$$
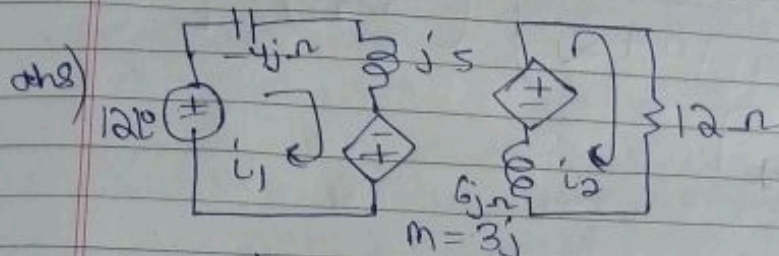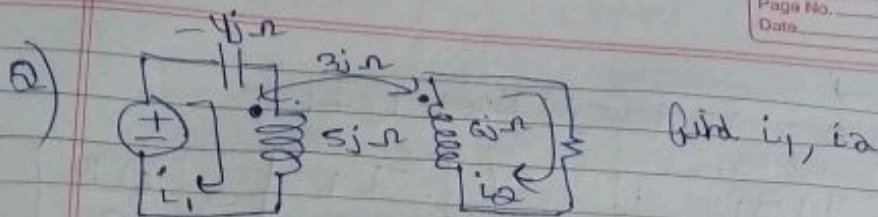
$$V_s(t) = (L_1 + L_2 + 2M) \frac{di}{dt}$$



KVL \rightarrow



Loop 1 $12 + 3j i_2 = -j4 i_1 + 5j i_1$

$12 = 1j I_1 - 3j I_2 \rightarrow (1)$

Loop 2 $3j I_1 = 6j I_2 + 12 I_2$
 $3j I_1 - (12 + 6j) I_2 = 0$
 $I_1 = \frac{(12 + 6j)}{3j} I_2 \rightarrow (2)$

Solving \rightarrow (1) method \rightarrow put (2) in (1)
 (2) method \rightarrow Cramer's rule
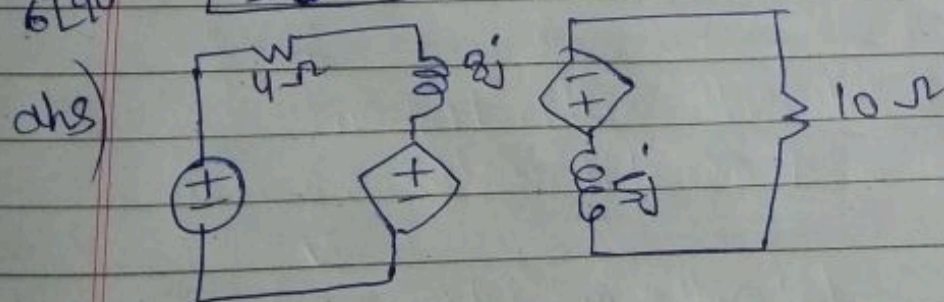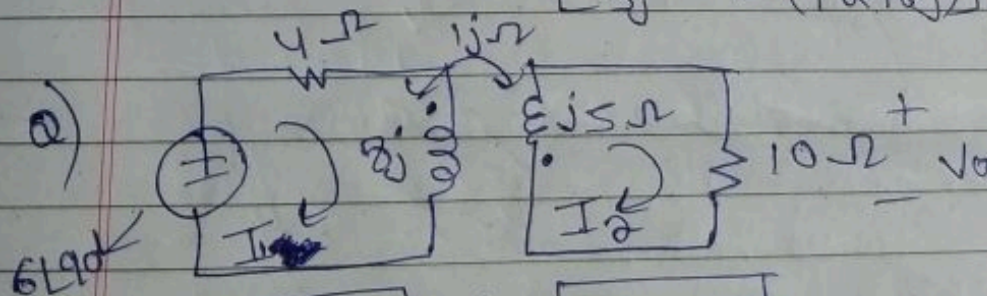
$$\begin{bmatrix} 1j & -3j \\ 3j & -(12+6j) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$



$6 = 4 I_1 + 8j I_1 + 1j I_2$
 $= (4 + 8j) I_1 + 1j I_2 \rightarrow (1)$


Ques 2 →

$$0 = 10 + (5j)I_2 + 1jI_1$$

$$\text{so } \begin{bmatrix} 4+8j & 1j \\ 1j & 10+5j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \angle 90^\circ \\ 0 \end{bmatrix}$$

$$\boxed{V_0 = 10 \angle 90^\circ}$$


CAT stuff ? for CAT 2

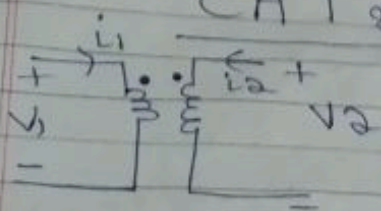

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$


? same for this?

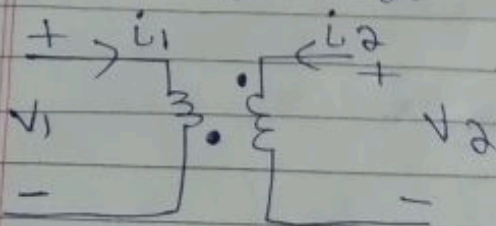

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

? same for this?

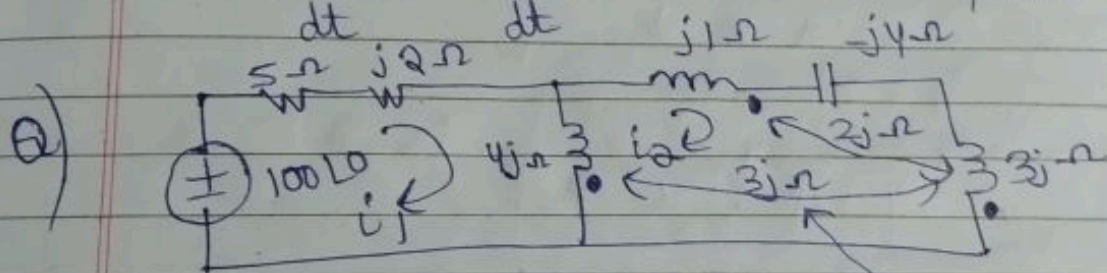

and

$$100\angle 0 = 5i_1 + j2i_1 + j4(i_1 - i_2) + 3ji_2$$

and

$$0 = ji_2 + j2i_2 - j4i_2 + j3i_2 + 2ji_2 - j3(i_2 - i_1)$$

as current enters both dots


as current enters dot

as current enters both

$$+ j4(i_2 - i_1) - j3i_2$$



$$0 = ji_2 + j2i_2 - j4i_2 + j3i_2 + j2i_2 - j3(i_2 - i_1) + j4(i_2 - i_1) - j3i_2 \rightarrow (2)$$

solve both.

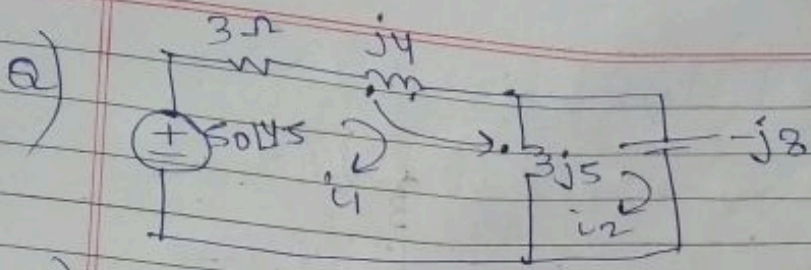

ans) $50\angle 45^\circ = 3i_1 + 4j + j5(i_1 - i_2) + j3(i_1 - i_2)$
 $+ j3i_1 \rightarrow (1)$

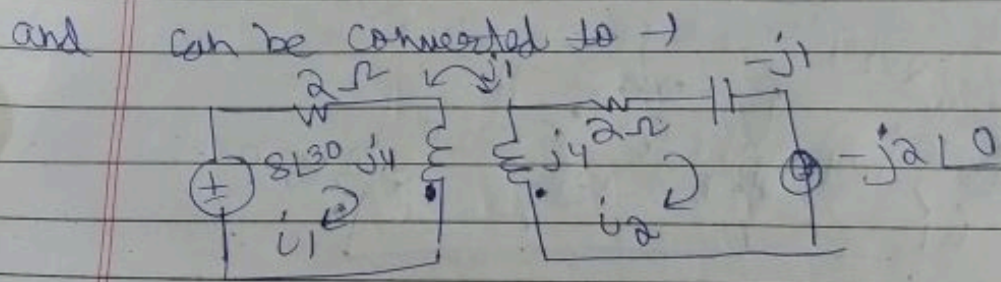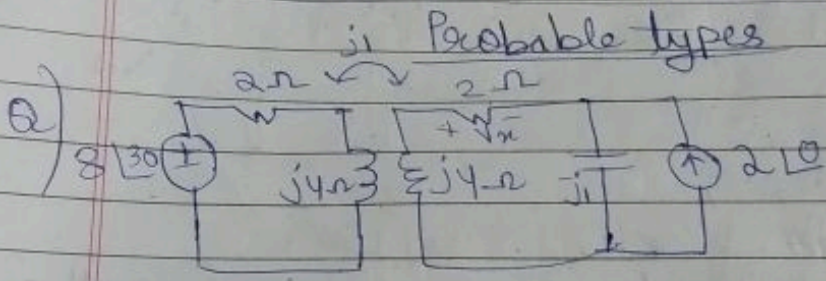$0 = -j8i_2 + j5(i_2 - i_1) - j3i_1 \rightarrow (2)$
solve both




$8L30 + 2i_1 + 4ji - j1i_2 = 0$

and

~~$j4i_2 + 2i_2 - j1i_2 - j210 - j1i_1 = 0$~~

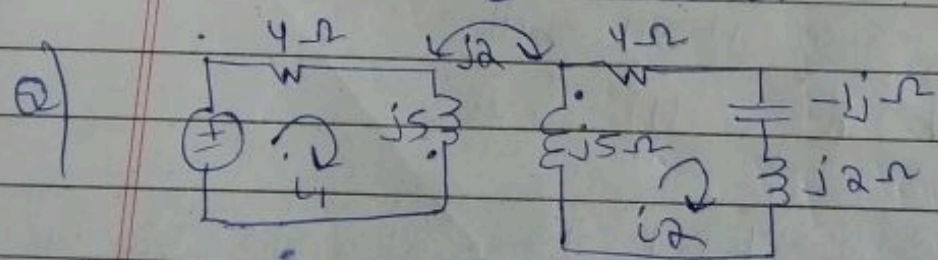$j4i_2 + 2i_2 - j1i_2 - j210 - j1i_1 = 0$
solve both.



ans) $Z_s = \frac{V_s}{I_s}$

$$Z_s = \frac{80 L_0}{I_1}$$

$$(4 + j5)i_1 + j2i_2 = 80 L_0 \rightarrow (1)$$

$$j2i_1 + (j5 + 4 - j1 + j2)i_2 = 0 \rightarrow (2)$$

$$\text{find } Z_s = \frac{80 L_0}{i_1}$$

Force fields

$\epsilon_0 \rightarrow$ unit \rightarrow Farad / metre or $\frac{Nm}{V^2}$

$\mu_0 \rightarrow$ Henry / metre or $Nm / ampere^2$


$$\phi = \int_S \vec{B} \cdot d\vec{s} \quad \left\{ \frac{J}{A} \text{ or } \frac{Nm}{A} \right\}$$

{ flux }

$$\mathcal{E}(t) = N \frac{d\phi}{dt} \quad \left\{ \text{Faraday's law} \right\}$$

$$\mathcal{E}(t) = N \frac{d\phi}{di} \times \frac{di}{dt} = L \frac{di}{dt}$$

(unit $\frac{J}{C}$)

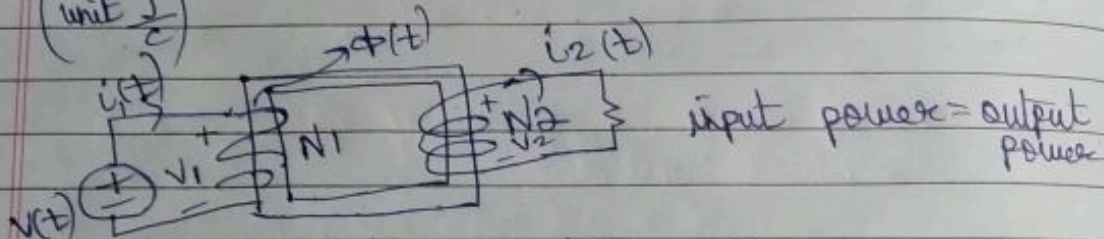

$$V_1(t) = N_1 \frac{d\phi}{dt}$$

$$V_2(t) = N_2 \frac{d\phi}{dt}$$


$N_1, N_2 \rightarrow$ no. of turns

$$\frac{V_1(t)}{V_2(t)} = \frac{N_1}{N_2} = \frac{i_2}{i_1}$$

$$P_1(t) = P_2(t)$$

$$V_1(t) i_1(t) = V_2(t) i_2(t)$$

Q)

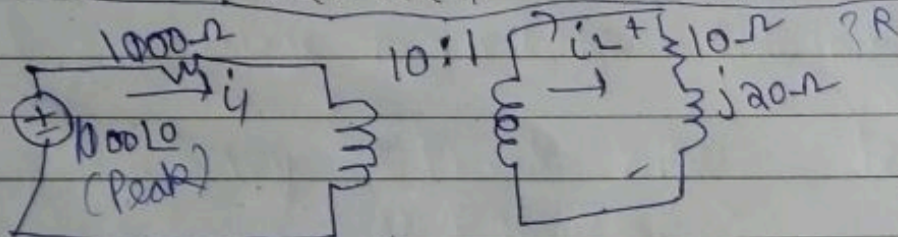

↓ step down transformer

ans) $i_1^2 R_{L_{eq}} = i_2^2 R_L$


$R_{L_{eq}} = \frac{I_2^2 R_L}{I_1^2}$

$$R_{L \text{ equivalent}} = \left(\frac{I_2}{I_1} \right)^2 R_L = \left(\frac{N_1}{N_2} \right)^2 R_L$$

$$I_1^2 X_{L \text{ eq}} = I_2^2 X_L$$

Basically we replace resistor and inductor and put equivalent of it in 1st circuit

so accordingly \rightarrow

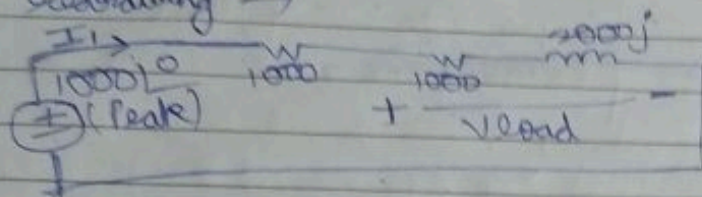


$$I_1 \text{ peak} = \frac{1000 \angle 0}{2000 + 2000j} = 0.35 \angle -45$$

$$V_{\text{load}} = 0.35 \angle -45 \quad (\Rightarrow 1000 + 2000j)$$

- Q) Speaker of 9- Ω effective R connected to \rightarrow
 case 1 \rightarrow power of 10V with internal R of 1- Ω
 case 2 \rightarrow transformer of 1:3 b/w source and load
 find P absorbed


ans) ①

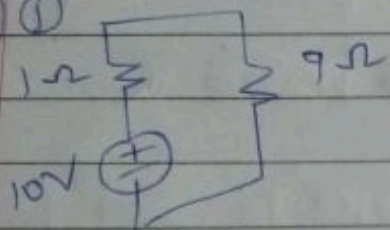


$$\rightarrow I = \frac{10V}{10\Omega} = 1A$$

$$P = i^2 R = 9W$$

②

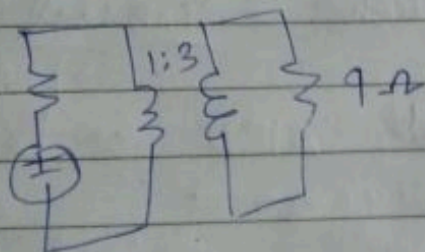

so circuit becomes

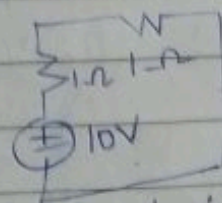

$$\downarrow i = 5A$$



$$\text{so } P = 25W$$

$$R_{L,1} = \left(\frac{N_1}{N_2} \right)^2 R_L$$


$$= \left(\frac{1}{3} \right)^2 9 = 1\Omega$$

to shift all to left side we use perov method.

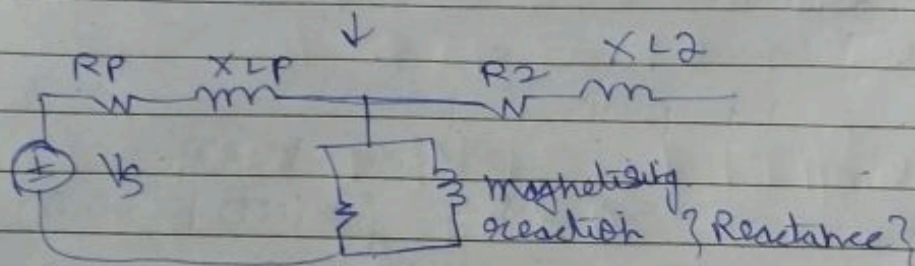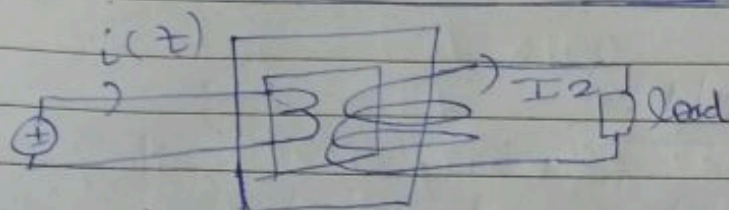to shift all to right side multiply voltage source by highest turns
R becomes 9Ω , voltage becomes $30V$
and you get same power.



↑ this is a realistic model


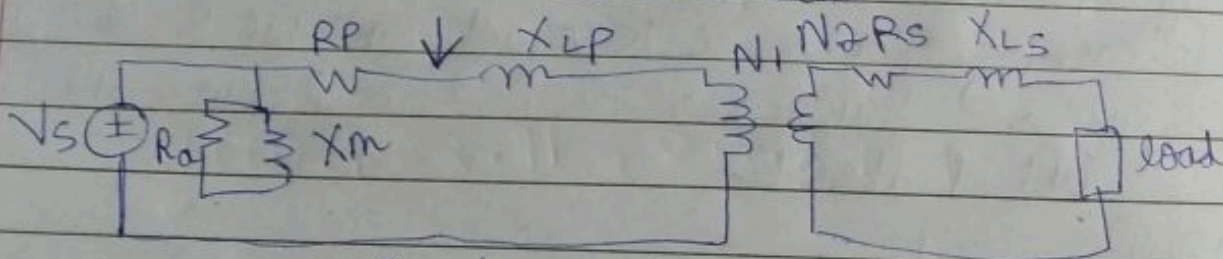


↑ takes lot of losses in account

$$\% \text{ voltage regulation} = \frac{V_{no \text{ load}} - V_{load}}{V_{load}} \times 100$$

$$\text{efficiency} = \frac{P_{Load}}{P_{in}} \times 100$$

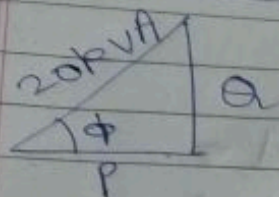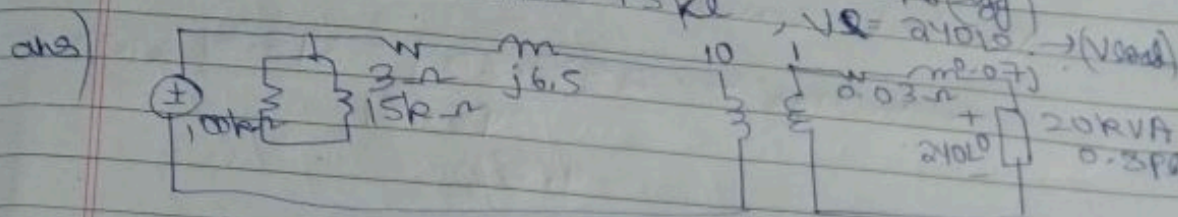a) $R_p = 3\ \Omega$, $X_{Lp} = 6.5j$, $N_1:N_2 = 10:1$, $R_s = 0.03\ \Omega$,
 $X_{Ls} = 0.07j$, $\text{load} = 20\text{KVA}$, 0.8pf (lag) ,
 $R_a = 100\text{K}\Omega$, $X_m = 15\text{K}\Omega$, $V_s = 240\angle 0^\circ \rightarrow (V_{\text{load}})$



$\cos\phi = 0.8 \text{ } \{ \text{lag} \}$
 $\phi = 36.8^\circ$

$P = S \cos\phi = 16014.627$

$Q = S \sin\phi = 11980.47$

$S = V_{\text{rms}} \times I_{\text{rms}}$

$I_{\text{rms}} = \frac{16014.627 + j11980.47}{240\angle 0}$

$I_{\text{rms}} = 83.333 \angle 36.799$

$I_{\text{rms}} = 83.33 \angle -36.799 \text{ A } \{ I_2 \}$

using mesh analysis in (2)

$V_2 = (0.03 + 0.07j) 83.28 \angle -36.82 + 240\angle 0$

$V_2 = 245.51 \angle 0.73 \text{ V}$

$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$ we find $V_1 = 2455.1 \angle 0.7$

$I_1 = 8.328 \angle -36.83 \text{ A}$

$V_s = I_1 (3 + 6.5j) + 2455.1 \angle 0.7$

$$V_s = 2508.04211.333$$

V_{load} = scaled value of V_s by turns

$$\% \text{ voltage} = \frac{2508.04 - 245.51}{245.51} \times 100 = 4.5\%$$

$$\text{efficiency} = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100$$

P_{out} = Real power of load

P_{in} = P_{out} + Losses in all resistors

P_{in} = P_{out} + ~~losses in all resistors~~ + loss in power by R

$$P_{\text{in}} = 16000 + \frac{|V_s|^2}{100 \text{ k}\Omega} + |I_1|_{\text{rms}}^2 \times 3 +$$

$$|I_2|_{\text{rms}}^2 \times 0.03$$


$$= 16000 + \frac{(2508.2)^2}{100,000} + (8.33)^2 \times 3 + \frac{(83.33)^2}{100.03}$$

$$= 16000 + 62.91 + 208.37 + 208.316$$

$$\text{so } P_{\text{in}} = 16000 + 479.58$$


$$\text{so efficiency} = \frac{16000}{16479.58} \times 100\% = 97.01\%$$

a) 1 ϕ , 10KVA, 2200V/220V 60Hz

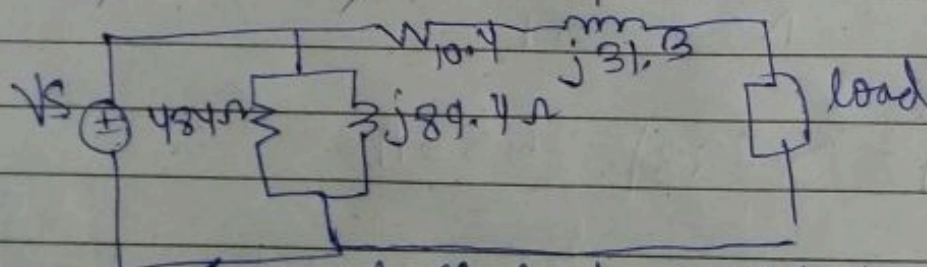

① 75% of full load, 0.6 p.f lag
find % voltage drop is 4.86

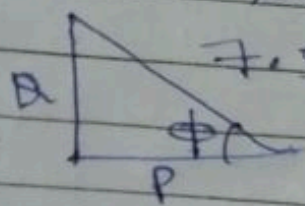ans) load $\rightarrow \frac{75 \times 10000}{100} = 7500 \text{ VA}$



$\phi = \cos^{-1} 0.6$
 $\phi = 53.13^\circ$
 so $P = 4500 \text{ W}$
 $Q = 6000 \text{ W}$

so $S = 4500 + 6000j$

so $i_{\text{rms}}^* = \frac{4500 + 6000j}{2200}$

$i_{\text{rms}}^* = 3.4090 \angle 53.136$

$i_{\text{rms}} = 3.4090 \angle -53.130$ (D)