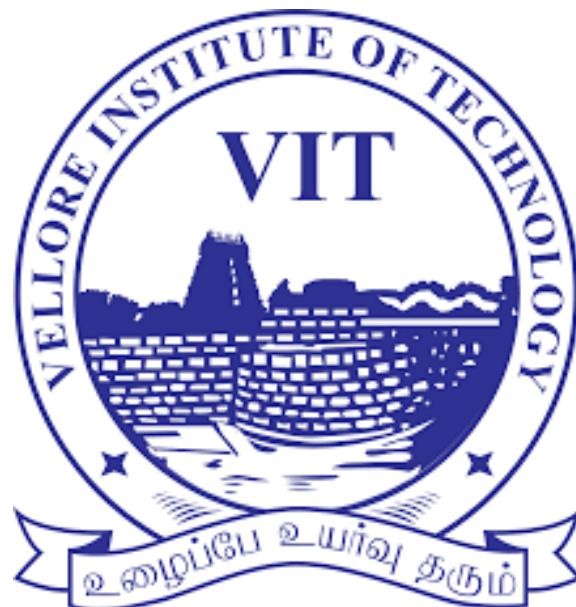


# **EEE1001**

## **Basic Electrical and Electronics Engineering**


**Dr. M.A Inayathullaah,**

**Faculty, School of Electrical Engineering,  
Vellore Institute of Technology, Chennai.**



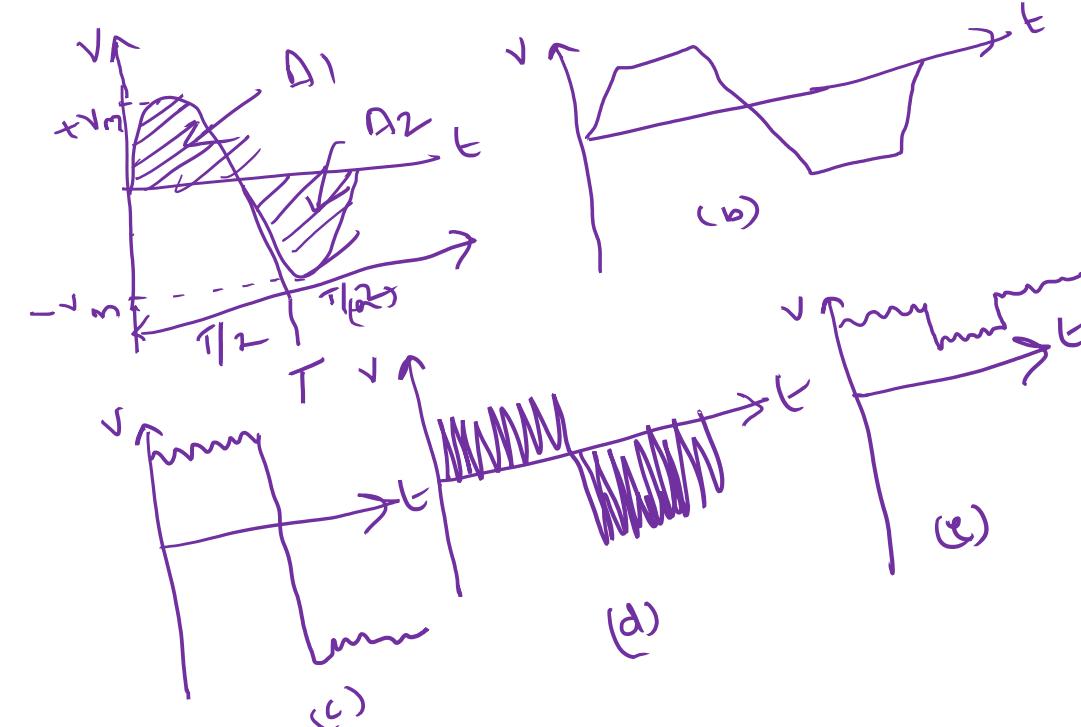
## Module -2: AC circuits

- ▶ Alternating voltages and currents,
- ▶ RMS,Average,Form factor, Peak Factor
- ▶ Single Phase RL, RC, RLC Series circuits,
- ▶ Single Phase RL, RC, RLC Parallel circuits,
- ▶ Power and Power Factor
- ▶ Balanced Three Phase Systems – Star and Delta Connection



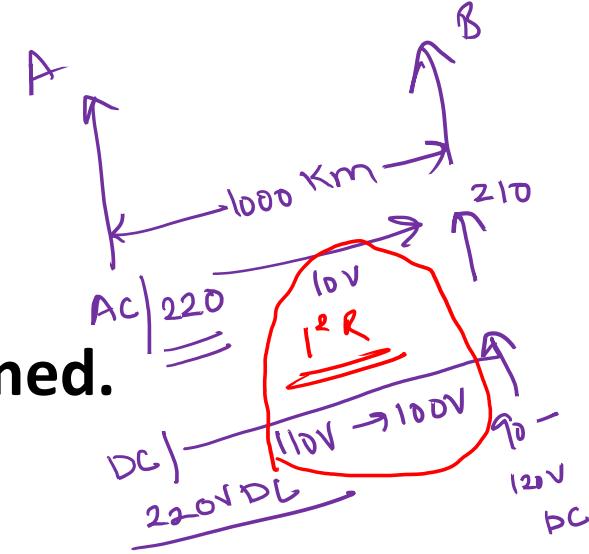
# Alternating Current


- ▶ The single greatest advantage of alternating current is that AC current can be transformed and DC current cannot be transformed.
- ▶ This allows high-voltage electrical power to be distributed with smaller wires and lower amperage.
- ▶ The electrical power is then transformed to a lower voltage where it is needed.




# Alternating Current

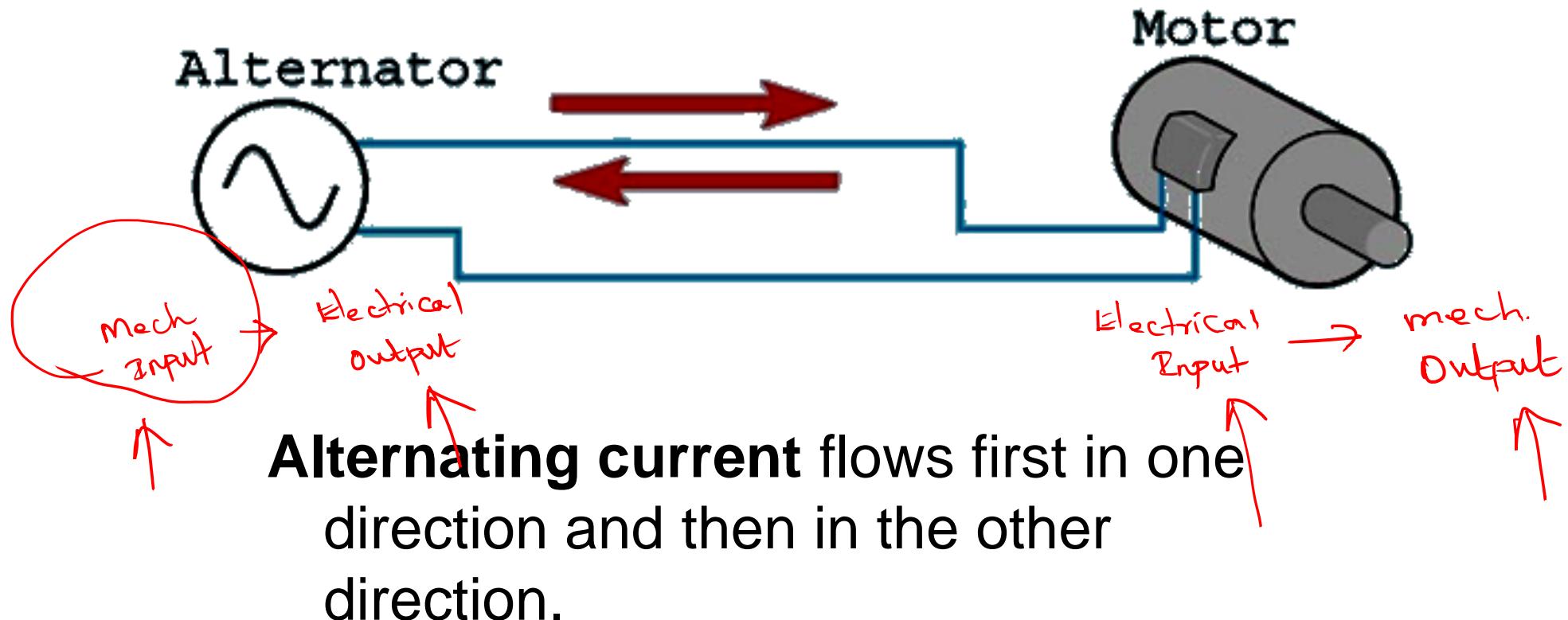

# Alternating Current

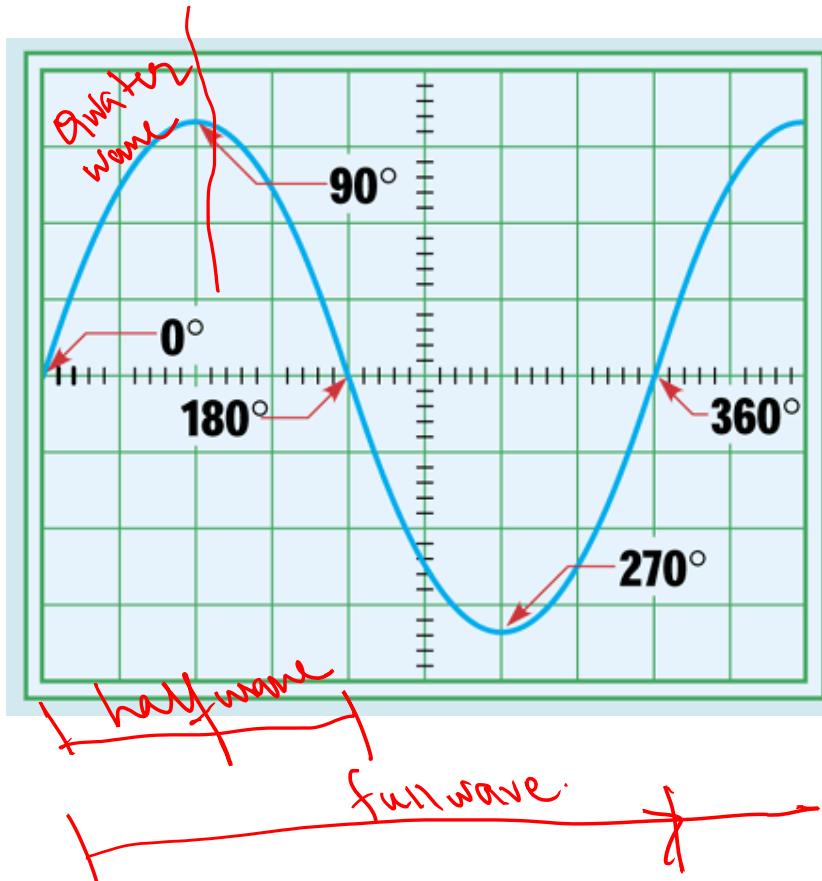

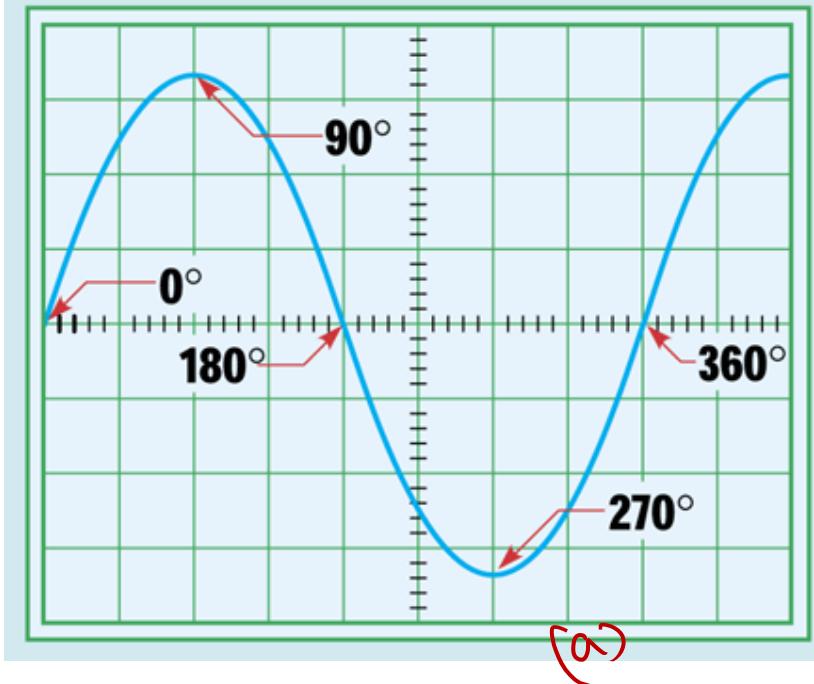- The sine wave is the most common of all the AC wave forms.
- One sine wave is 360 electrical degrees.




## Alternating Current

- The voltage at any point along the **sine wave** is equal to the maximum, or **peak**, value times the **sine of the angle of rotation**.

$$\underline{E_{\text{inst}}} = E_{\text{max}} \sin \theta \quad / \quad \underline{E_{\text{inst}}} = E_{\text{max}} \cos(90 - \theta)$$

$$\underline{\underline{E_{\text{(INST)}} = E_{\text{(MAX)}} \times \text{SINE } \theta}}$$

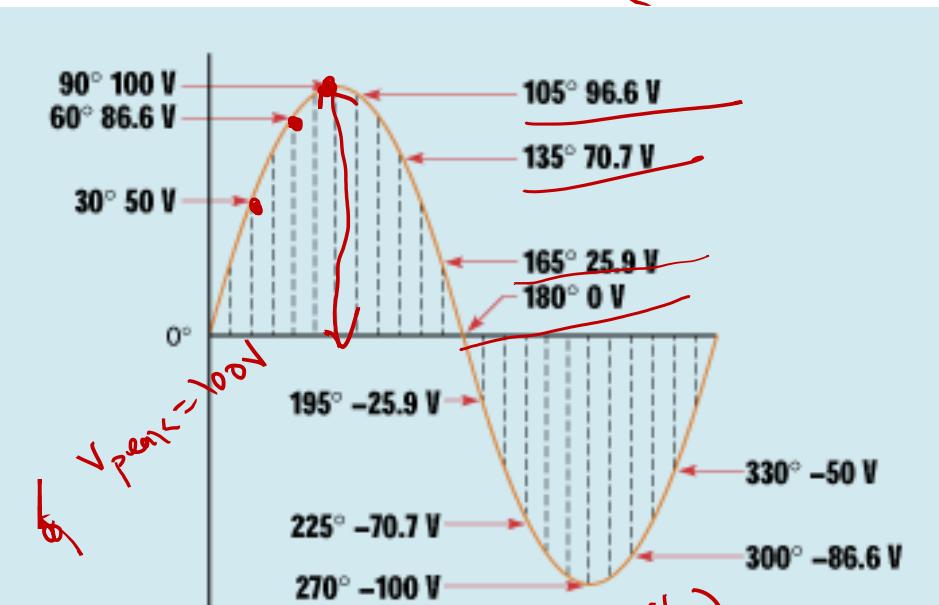
$E_{\text{(INST)}}$  = the voltage at any point on the wave form  
 $E_{\text{(MAX)}}$  = the maximum, or peak, voltage  
 $\text{SINE } \theta$  = the sine of angle theta, the angle of rotation



Instantaneous values of voltage along a sine wave.

**Instantaneous values** are the values of the alternating quantities at any instant of time. They are represented by small letters,  $i$ ,  $v$ ,  $e$

# Alternating Current

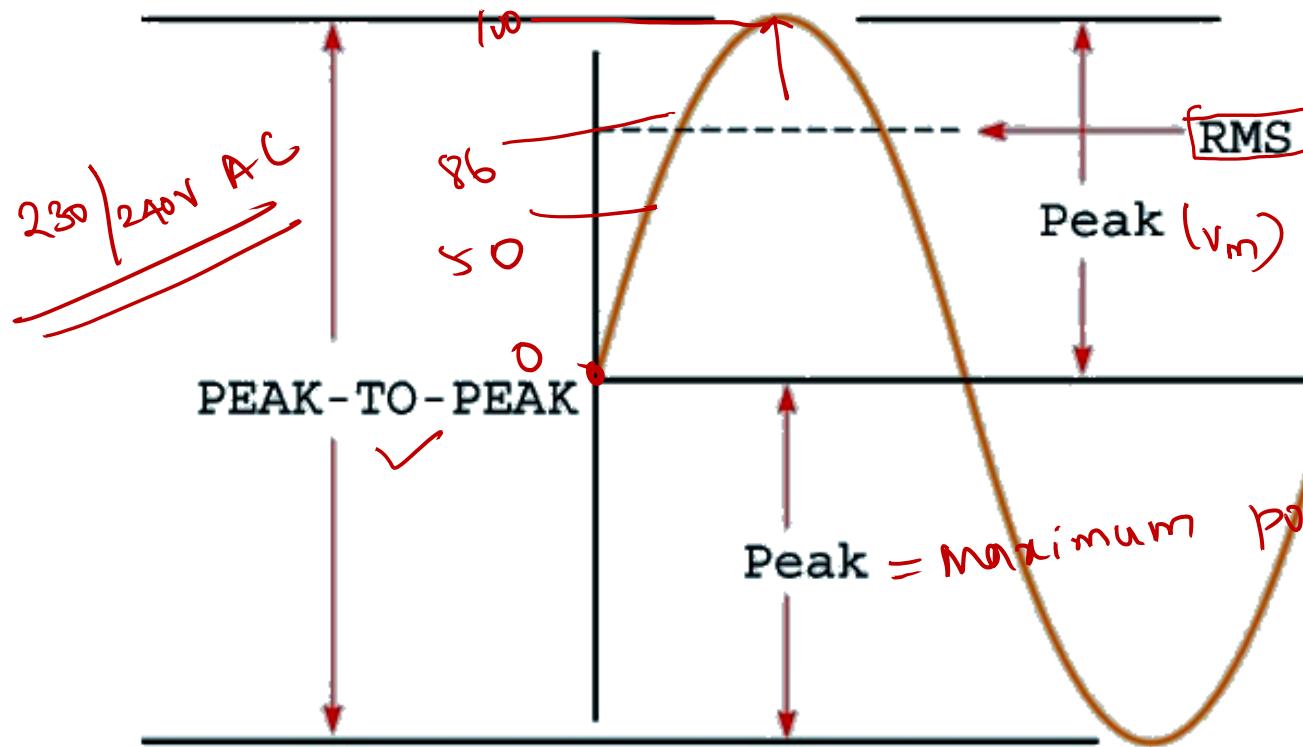


Peak, Peak-to-Peak, and RMS values along a sine wave.

$$\checkmark \quad \text{RMS} = \text{Peak} \times 0.707 \quad \checkmark$$

$$\underline{\text{Peak}} = \text{RMS} \times 1.414 \quad \checkmark = \sqrt{2}$$

# Alternating Current

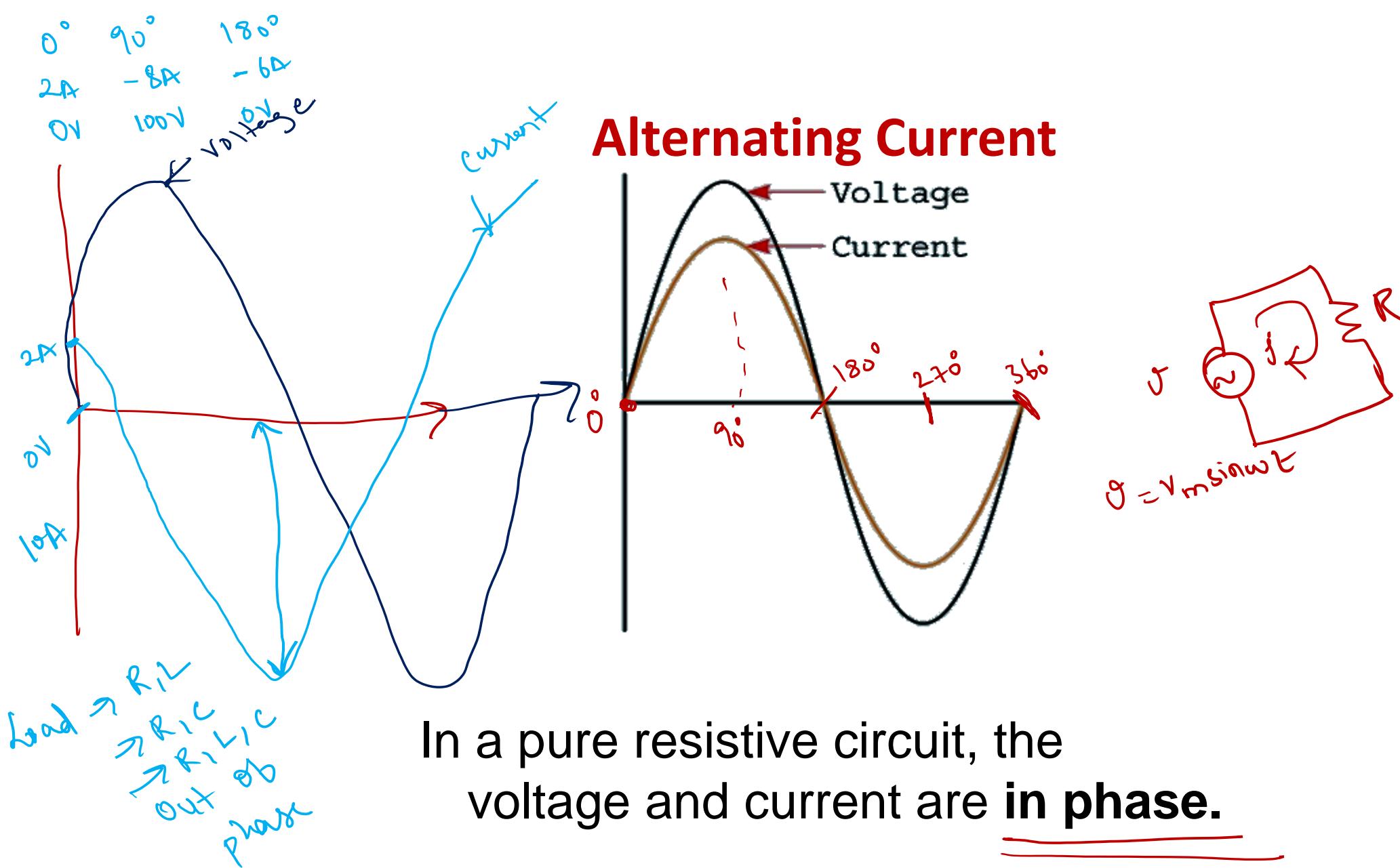

In a pure resistive circuit, the voltage and current are in phase.

# Alternating Current

1. Most of the electrical power generated in the world is alternating current.
2. Alternating current can be transformed and direct current cannot.
3. Alternating current reverses its direction of flow at periodic intervals.
4. The most common AC wave form is the sine wave.
5. There are 360 degrees in one complete sine wave.
6. Sine waves are produced by rotating machines.
7. The instantaneous voltage at any point on a sine wave is equal to the peak, or maximum, voltage times the sine of the angle of rotation.
8. The peak-to-peak voltage is the amount of voltage attained by the wave form.
9. The peak value is the maximum amount of voltage attained by the wave form.
10. The current and voltage in a pure resistive circuit are in phase with each other.

# Alternating Current

$$T = \frac{1}{f} \text{ or } f = \frac{1}{T}$$

Problem 1. Determine the periodic time for frequencies of  
(a) 50 Hz and (b) 20 kHz

(a) Periodic time  $T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s or } 20 \text{ ms}$

(b) Periodic time  $T = \frac{1}{f} = \frac{1}{20000} = 0.000\ 05 \text{ s or } 50 \mu\text{s}$

Problem 2. Determine the frequencies for periodic times of  
(a) 4 ms, (b) 4  $\mu\text{s}$

(a) Frequency  $f = \frac{1}{T} = \frac{1}{4 \times 10^{-3}} = \frac{1000}{4} = 250 \text{ Hz}$

(b) Frequency  $f = \frac{1}{T} = \frac{1}{4 \times 10^{-6}} = \frac{1\ 000\ 000}{4}$   
 $= 250\ 000 \text{ Hz or } 250 \text{ kHz or } 0.25 \text{ MHz}$

Problem 3. An alternating current completes 5 cycles in 8 ms.  
What is its frequency?

Time for 1 cycle  $= \frac{8}{5} \text{ ms} = 1.6 \text{ ms} = \text{periodic time } T$

---

Frequency  $f = \frac{1}{T} = \frac{1}{1.6 \times 10^{-3}} = \frac{1000}{1.6} = \frac{10000}{16} = 625 \text{ Hz}$

---

$$(I_{dc}^2 R) = (I_{ac}^2)$$

# Alternating Current

The average or mean value of a symmetrical alternating quantity,

(such as a sine wave), is the average value measured over a half cycle,

(since over a complete cycle the average value is zero).

$$\text{Average or mean value} = \frac{\text{area under the curve}}{\text{length of base}}$$

RMS


The effective value of an alternating current is that current which will produce the same heating effect as an equivalent direct current. The effective value is called the root mean square (rms) value and whenever an alternating quantity is given, it is assumed to be the rms value.

$$\text{Form factor} = \frac{\text{rms value}}{\text{average value}}$$

For a sine wave,  
form factor = 1.11

$$\text{Peak factor} = \frac{\text{maximum value}}{\text{rms value}}$$

For a sine wave,  
peak factor = 1.41



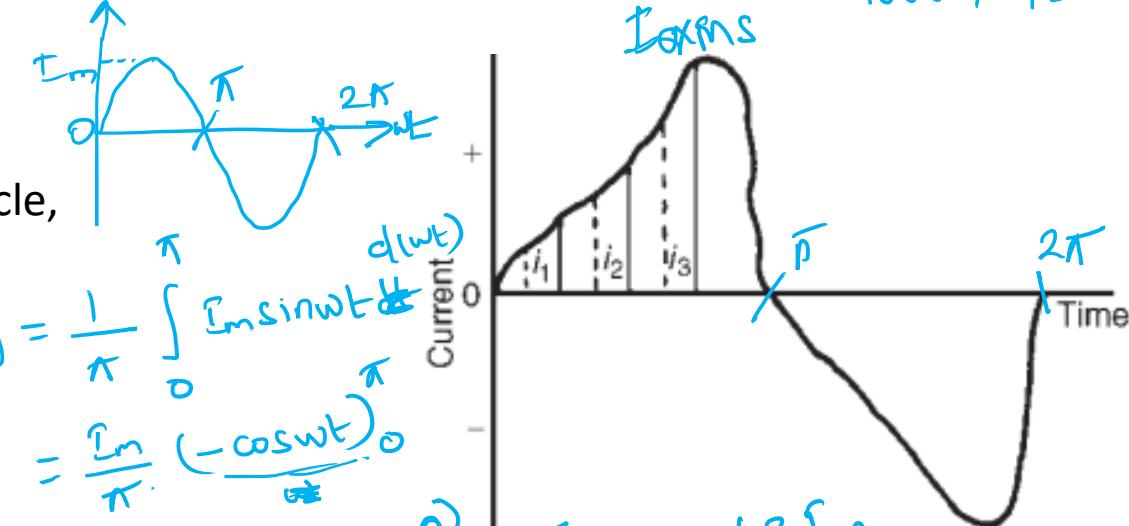


$$\begin{aligned} I_{avg} &= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, d\omega t \\ &= \frac{I_m}{\pi} \left[ -\cos \omega t \right]_0^\pi \\ &= \frac{I_m}{\pi} (\cos \pi - \cos 0) \\ &= -\frac{I_m}{\pi} (-1 - 1) = \frac{2I_m}{\pi} = 0.63 I_m \end{aligned}$$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \omega t)^2 \, d\omega t}$$

square root

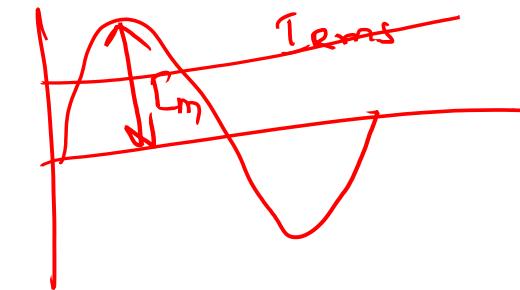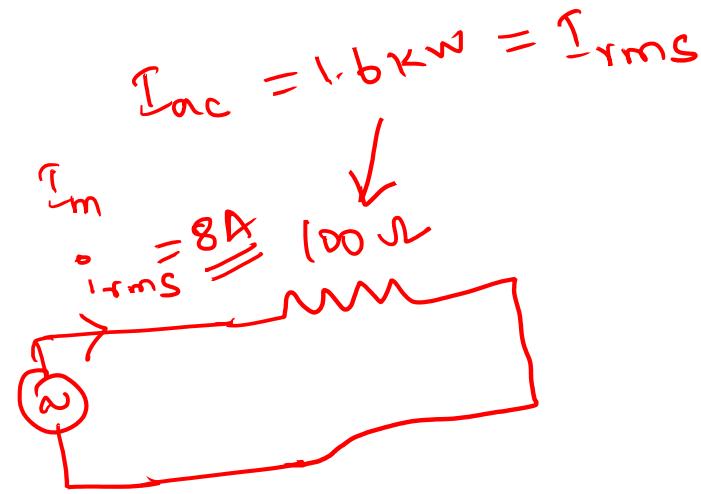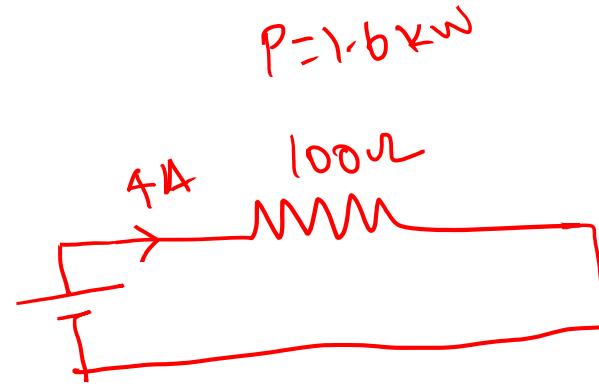where  $n$  is the number of intervals used.




$I_{rms}$

$I_{dc}$


# Alternating Current

## Purely resistive a.c. circuit

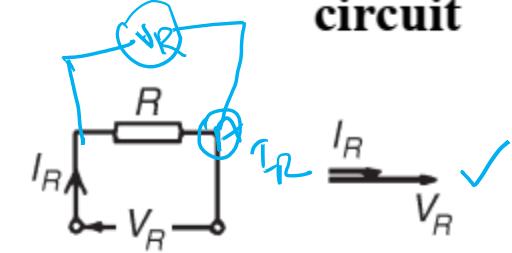


CIRCUIT  
DIAGRAM

PHASOR  
DIAGRAM

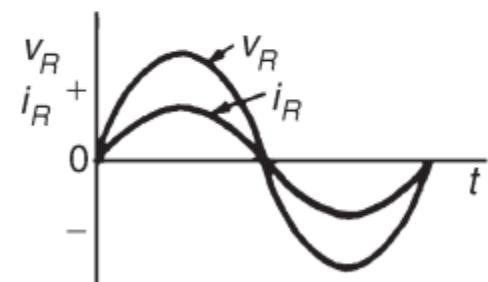


CURRENT AND VOLTAGE  
WAVEFORMS


## Purely inductive a.c. circuit

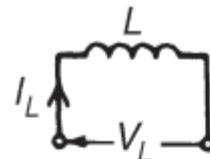

CIRCUIT  
DIAGRAM

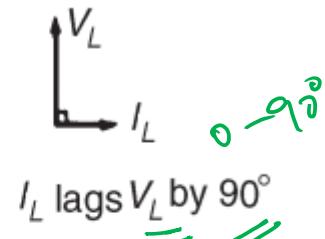


PHASOR  
DIAGRAM

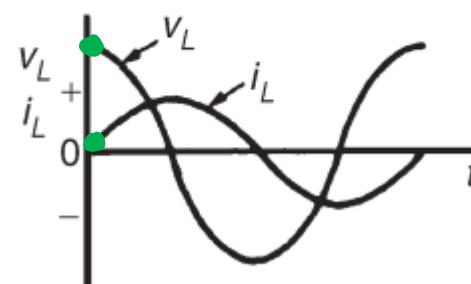


$$X_L = \frac{V_L}{I_L} = 2\pi fL \Omega$$


## Purely capacitive a.c. circuit

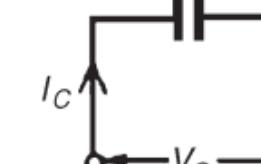

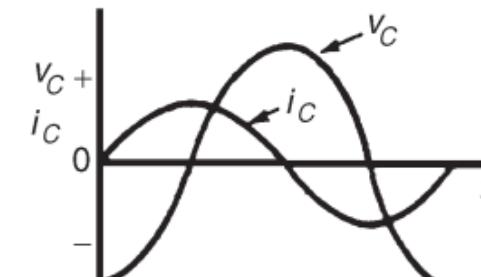$I_C$  leads  $V_C$  by  $90^\circ$  (ideal)


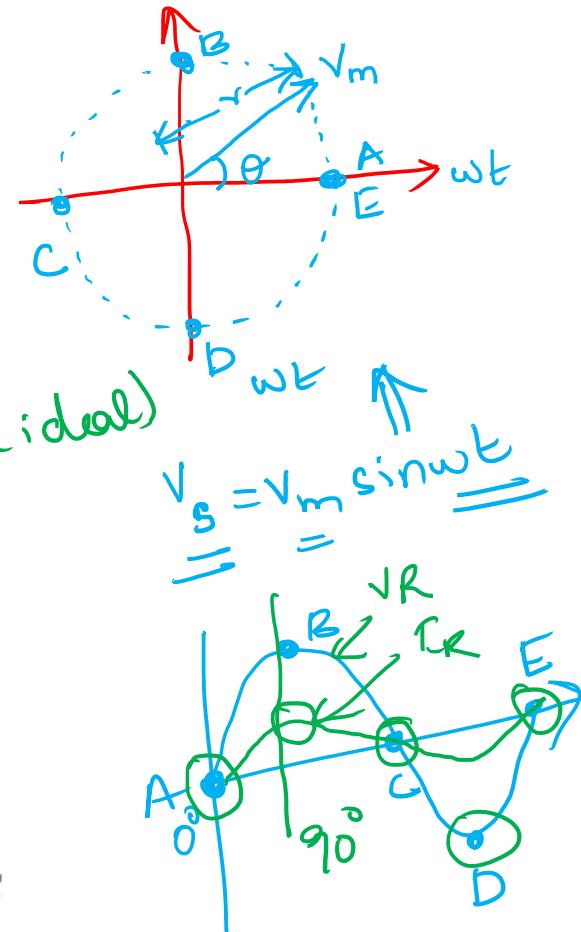
$$X_C = \frac{V_C}{I_C} = \frac{1}{2\pi fC} \Omega$$



In a purely inductive circuit the opposition to the flow of alternating current is called the **inductive reactance**,  $X_L$


In a purely capacitive circuit the opposition to the flow of alternating current is called the **capacitive reactance**,  $X_C$

# Alternating Current

$X_L$

(a) Calculate the reactance of a coil of inductance 0.32 H when it is connected to a 50 Hz supply. (b) A coil has a reactance of 124  $\Omega$  in a circuit with a supply of frequency 5 kHz. Determine the inductance of the coil.


$$L = 0.32 \text{ H}$$

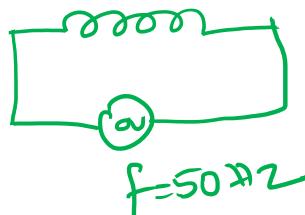

$$\text{a)} X_L = \omega L = 2\pi f L = 2\pi \times 50 \times 0.32 = 100.48 \Omega$$

$$\text{b)} L = \frac{X_L}{2\pi f} = \frac{124}{2\pi \times 5 \times 10^3} = 3.94 \text{ mH}$$

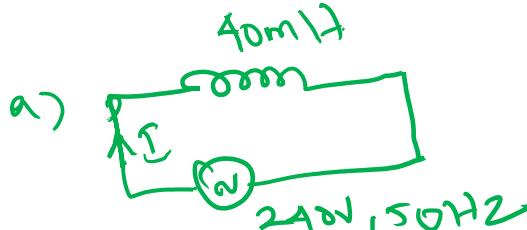A coil has an inductance of 40 mH and negligible resistance. Calculate its inductive reactance and the resulting current if connected to (a) a 240 V, 50 Hz supply, and (b) a 100 V, 1 kHz supply.



$$L = 40 \times 10^{-3} \text{ H}$$

$$X_L = 2\pi f L = 2\pi \times 50 \times 40 \times 10^{-3} =$$

$$I = \frac{V}{X_L} =$$

# Alternating Current

Determine the capacitive reactance of a capacitor of  $10 \mu\text{F}$  when connected to a circuit of frequency (a) 50 Hz (b) 20 kHz

A capacitor has a reactance of  $40 \Omega$  when operated on a 50 Hz supply. Determine the value of its capacitance.

# Alternating Current

Calculate the current taken by a  $23 \mu\text{F}$  capacitor when connected to a  $240 \text{ V}, 50 \text{ Hz}$  supply.

# Alternating Current

(a) Calculate the reactance of a coil of inductance 0.32 H when it is connected to a 50 Hz supply. (b) A coil has a reactance of 124 Ω in a circuit with a supply of frequency 5 kHz. Determine the inductance of the coil.

(a) Inductive reactance,  $X_L = 2\pi fL = 2\pi(50)(0.32) = \mathbf{100.5 \Omega}$

(b) Since  $X_L = 2\pi fL$ , inductance  $L = \frac{X_L}{2\pi f} = \frac{124}{2\pi(5000)} \text{H} = \mathbf{3.95 \text{ mH}}$

A coil has an inductance of 40 mH and negligible resistance. Calculate its inductive reactance and the resulting current if connected to (a) a 240 V, 50 Hz supply, and (b) a 100 V, 1 kHz supply.

(a) Inductive reactance,  $X_L = 2\pi fL = 2\pi(50)(40 \times 10^{-3}) = \mathbf{12.57 \Omega}$

Current,  $I = \frac{V}{X_L} = \frac{240}{12.57} = \mathbf{19.09 \text{ A}}$

(b) Inductive reactance,  $X_L = 2\pi(1000)(40 \times 10^{-3}) = \mathbf{251.3 \Omega}$

Current,  $I = \frac{V}{X_L} = \frac{100}{251.3} = \mathbf{0.398 \text{ A}}$

# Alternating Current

(a) Calculate the reactance of a coil of inductance 0.32 H when it is connected to a 50 Hz supply. (b) A coil has a reactance of 124  $\Omega$  in a circuit with a supply of frequency 5 kHz. Determine the inductance of the coil.

Required

a) Reactance ( $X_L$ )

Given

a) Self Inductance ( $L$ ) = 0.32 H  
frequency ( $f$ ) = 50 Hz

b) Reactance ( $X_L$ )  
Self inductance ( $L$ )  
b) Reactance = 124  $\Omega$   
frequency = 5 kHz

Solution

a)  $X_L = 2\pi f L = 2\pi \times 50 \times 0.32 = 100.53 \Omega$

b)  $L = \frac{X_L}{2\pi f} = \frac{124}{2\pi \times 5 \times 10^3} = 39.5 \times 10^{-4} H = 3.95 mH$

A coil has an inductance of 40 mH and negligible resistance. Calculate its inductive reactance and the resulting current if connected to (a) a 240 V, 50 Hz supply, and (b) a 100 V, 1 kHz supply.

Given

Supply Voltage ( $V$ ) = 240 V  
frequency ( $f$ ) = 50 Hz  
Inductance ( $L$ ) =  $40 \times 10^{-3}$  H.

Required data

1) Inductive Reactance ( $X_L$ )  
2) Inductive Current ( $I_L$ )

a)  $X_L = 2\pi f L = 2\pi \times 50 \times 40 \times 10^{-3} = 12.56 \Omega$

$I_L = \frac{V}{X_L} = \frac{240}{12.56} = 19.1 A$

# Alternating Current

Determine the capacitive reactance of a capacitor of  $10 \mu\text{F}$  when connected to a circuit of frequency (a) 50 Hz (b) 20 kHz

Required data

$$X_C = ?$$

Given data

$$C = 10 \mu\text{F}$$

Solution

$$X_C = \frac{1}{2\pi f C} \Rightarrow$$

a) 50 Hz

$$X_{C(50\text{Hz})} = \frac{1}{2\pi \times \underline{50} \times 10 \times \underline{10^{-6}}} = 318.5 \Omega$$

b) 20 kHz

$$X_{C(20\text{kHz})} = \frac{1}{2\pi \times \underline{20} \times 10^3 \times 10 \times \underline{10^{-6}}} = 7.96 \Omega$$



A capacitor has a reactance of  $40 \Omega$  when operated on a 50 Hz supply. Determine the value of its capacitance.

$$X_C = 40 \Omega$$

$$f_s = 50 \text{ Hz}$$

$$C = ?$$

Solution

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 40} = \underline{\underline{8 \mu\text{F}}}$$

# Alternating Current

Calculate the current taken by a  $23 \mu\text{F}$  capacitor when connected to a  $240 \text{ V}, 50 \text{ Hz}$  supply.

$$\begin{aligned}\text{Current } I &= \frac{V}{X_C} = \frac{V}{\left(\frac{1}{2\pi f C}\right)} = 2\pi f C V = 2\pi(50)(23 \times 10^{-6})(240) \\ &= \mathbf{1.73 \text{ A}}\end{aligned}$$

# Alternating Current


Determine the capacitive reactance of a capacitor of  $10 \mu\text{F}$  when connected to a circuit of frequency (a)  $50 \text{ Hz}$  (b)  $20 \text{ kHz}$

$$\begin{aligned}\text{(a)} \quad \text{Capacitive reactance } X_C &= \frac{1}{2\pi f C} = \frac{1}{2\pi(50)(10 \times 10^{-6})} \\&= \frac{10^6}{2\pi(50)(10)} \\&= 318.3 \Omega\end{aligned}$$

$$\begin{aligned}\text{(b)} \quad X_C &= \frac{1}{2\pi f C} = \frac{1}{2\pi(20 \times 10^3)(10 \times 10^{-6})} = \frac{10^6}{2\pi(20 \times 10^3)(10)} \\&= 0.796 \Omega\end{aligned}$$

A capacitor has a reactance of  $40 \Omega$  when operated on a  $50 \text{ Hz}$  supply. Determine the value of its capacitance.
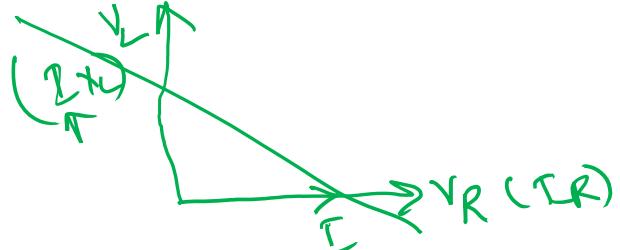
$$\begin{aligned}\text{Since } X_C &= \frac{1}{2\pi f C}, \text{ capacitance } C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(50)(40)} \text{ F} \\&= \frac{10^6}{2\pi(50)(40)} \mu\text{F} = 79.58 \mu\text{F}\end{aligned}$$



## RL Series AC Circuit

For the  $R-L$  circuit:  $V = \sqrt{(V_R^2 + V_L^2)}$  (by Pythagoras' theorem)

$$\text{and } \tan \phi = \frac{V_L}{V_R} \quad (\text{by trigonometric ratios})$$

In an a.c. circuit, the ratio  $\frac{\text{applied voltage } V}{\text{current } I}$  is called the **impedance**  $Z$ ,  
i.e.

$$Z = \frac{V}{I} \Omega$$


$$Z = \sqrt{(R^2 + X_L^2)}$$

*Reactance + Resistance*



$$\tan \phi = \frac{X_L}{R}, \sin \phi = \frac{X_L}{Z} \text{ and } \cos \phi = \frac{R}{Z}$$

heater  
Tubelight  
lamp


CIRCUIT DIAGRAM

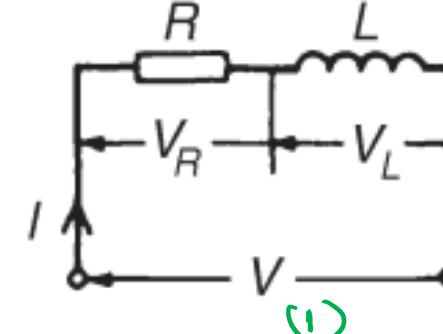


PHASOR DIAGRAM

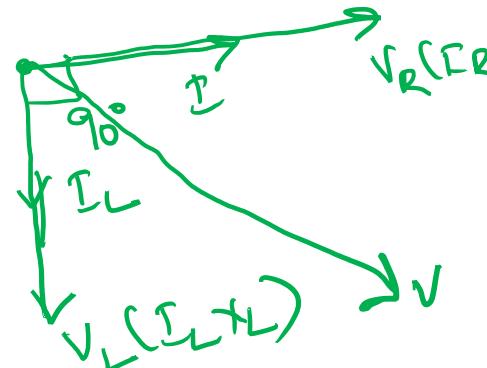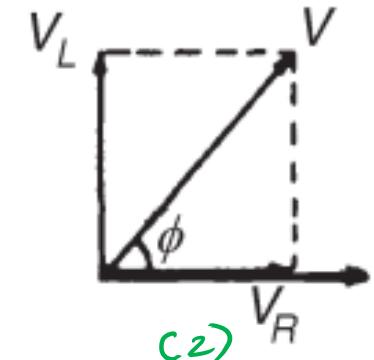

VOLTAGE TRIANGLE

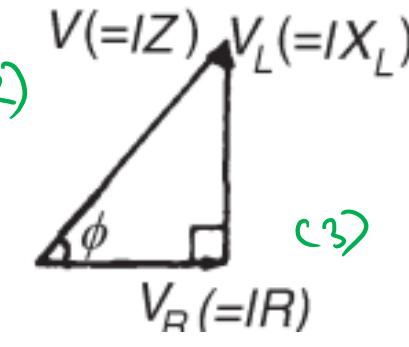

IMPEDANCE TRIANGLE

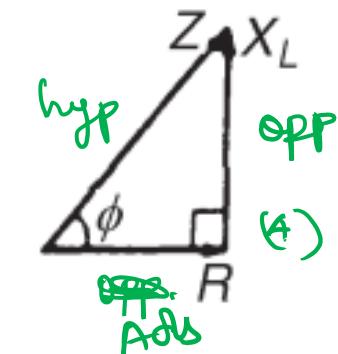


# RL Series AC Circuit

In a series R-L circuit the p.d. across the resistance R is 12 V and the p.d. across the inductance L is 5 V. Find the supply voltage and the phase angle between current and voltage.

Given data

Inductive drop ( $V_L$ ) = 5 V

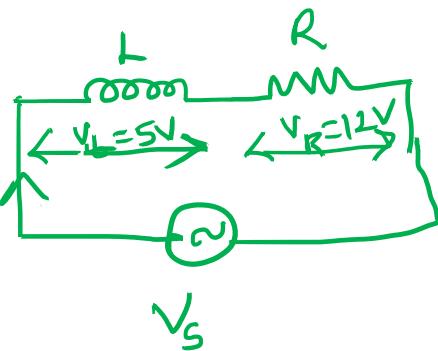

Resistance drop ( $V_R$ ) = 12 V

Required data

Phase angle ( $\phi$ )


Supply Voltage ( $V_s$ ) ✓



Solution

$$\text{WKT, } V_s = \sqrt{V_R^2 + V_L^2}$$
$$= \sqrt{12^2 + 5^2}$$
$$= \sqrt{144 + 25} = 13 V$$

$$\tan \phi = \frac{V_L}{V_R} = \frac{5}{12}$$

$$\phi = \tan^{-1} (5/12) = 22.5^\circ$$

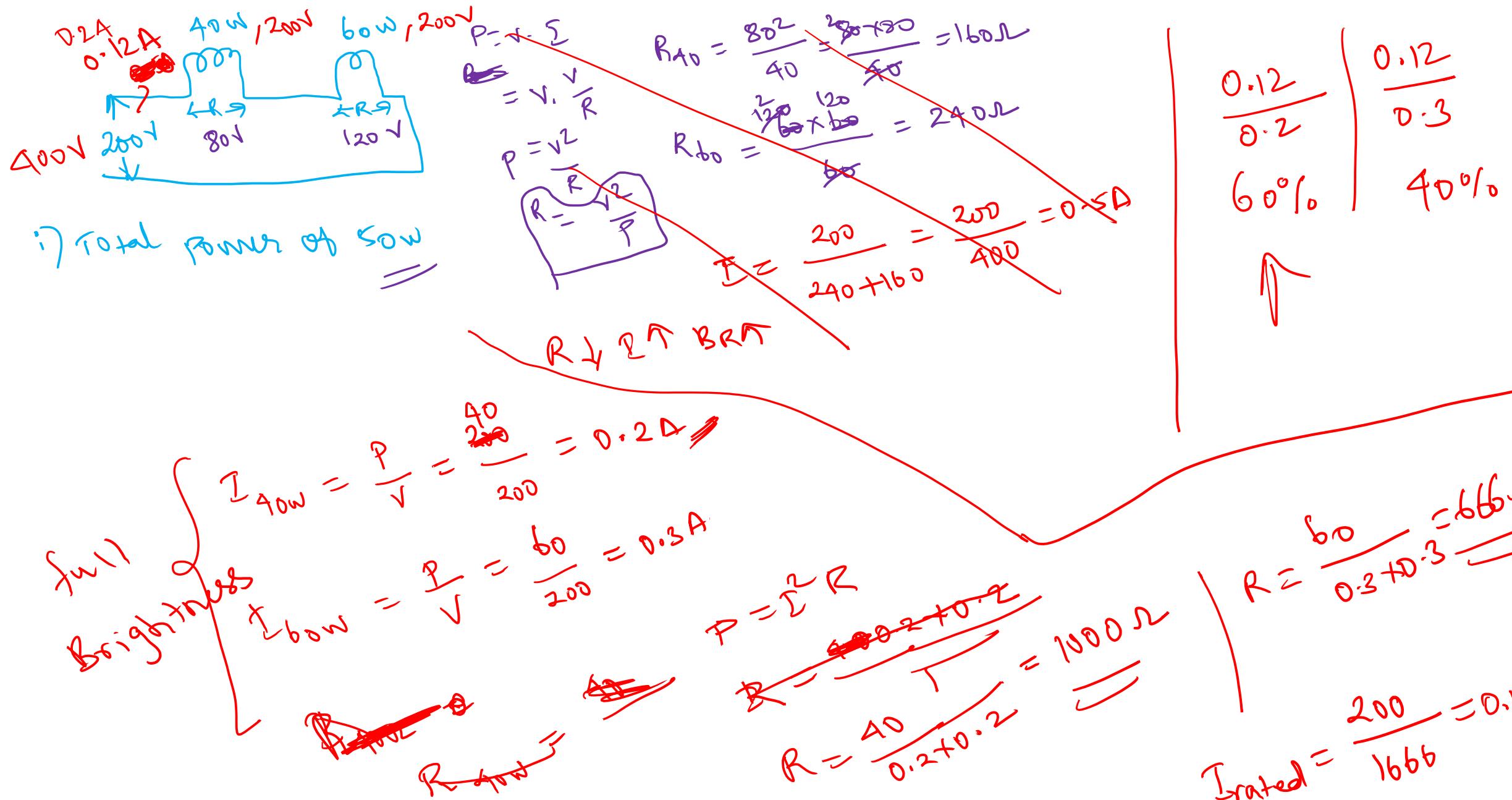

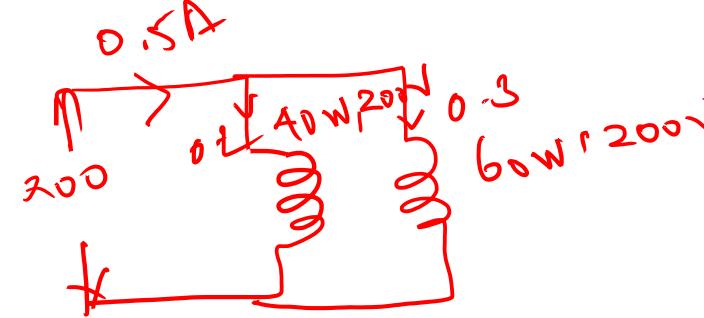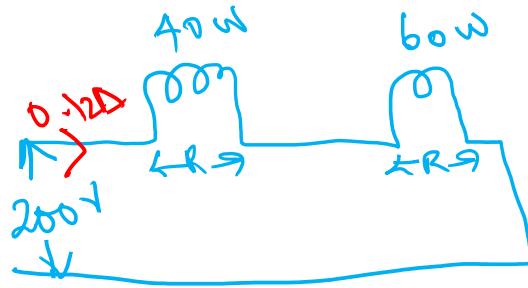

∴ Total power of 50W +  
100W +  
60W +  
40W


$$I_{40W} = \frac{P}{\sqrt{V}} = \frac{40}{\sqrt{200}} = 0.2A$$

$$I_{60W} = \frac{P}{\sqrt{V}} = \frac{60}{\sqrt{200}} = 0.3A$$

For the periodic waveforms shown in Figure determine for each: (i) frequency (ii) average value over half a cycle (iii) rms value (iv) form factor and (v) peak factor

$$a) f = \frac{1}{\text{Time period}} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz}$$

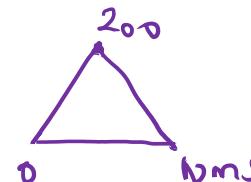
$$b) V_{\text{avg}} = \frac{1}{2} \times 10 \times 10 + 200 = 100 \text{ V}$$



$$c) \text{Rms} = \sqrt{\frac{V_1^2 + V_2^2 + V_3^2 + V_4^2}{T}}$$

$$= \sqrt{\frac{50^2 + 100^2 + 150^2 + 200^2}{4 \times 10^{-3}}}$$

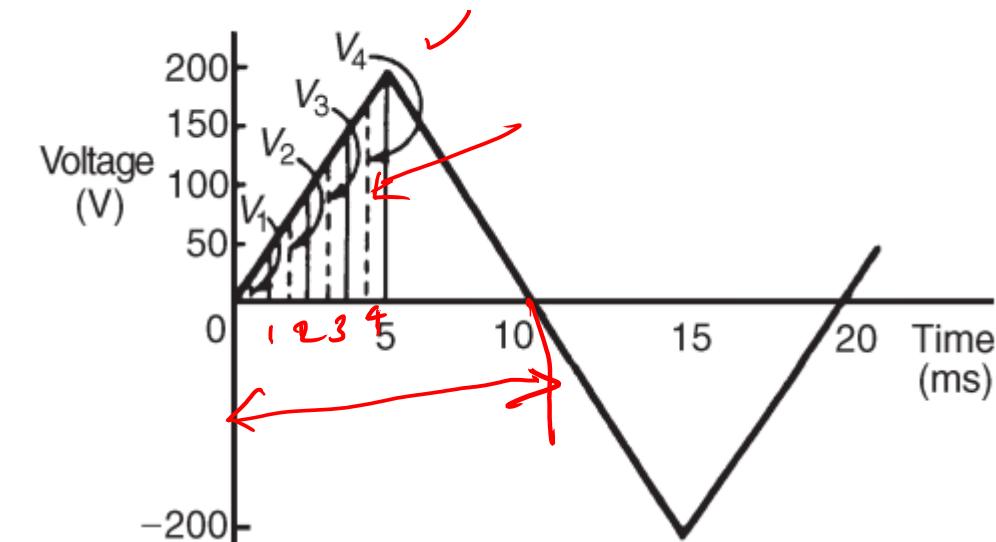
$$= \cancel{50} \times \cancel{3872.98} \times \cancel{1000} = \cancel{1330.94}$$




$$\text{FF} = \frac{\text{Rms}}{\text{Avg}} =$$

$$\text{PF} = \frac{\text{Max}}{\text{Rms}} =$$

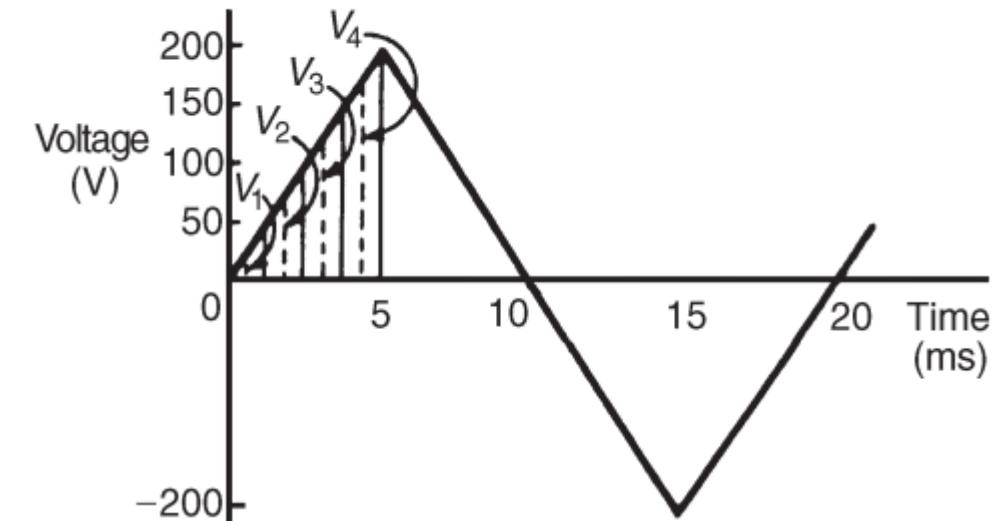**For the periodic waveforms shown in Figure determine for each: (i) frequency (ii) average value over half a cycle (iii) rms value (iv) form factor and (v) peak factor**



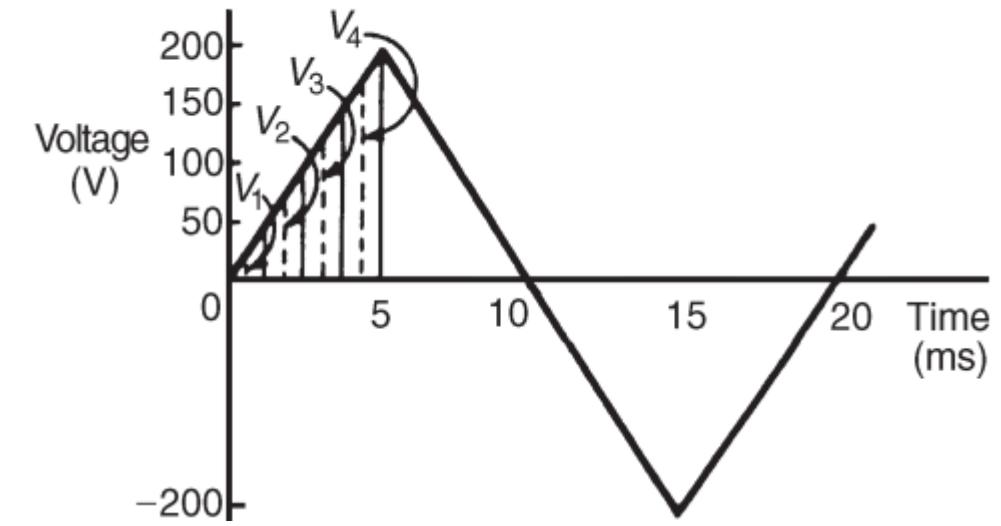**For the periodic waveforms shown in Figure determine for each: (i) frequency (ii) average value over half a cycle (iii) rms value (iv) form factor and (v) peak factor**



# RL Series AC Circuit

A coil has a resistance of  $4\Omega$  and an inductance of  $9.55 \text{ mH}$ . Calculate (a) the reactance, (b) the impedance, and (c) the current taken from a  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply. Determine also the phase angle between the supply voltage and current.

# RL Series AC Circuit

A coil has a resistance of  $4\Omega$  and an inductance of  $9.55 \text{ mH}$ . Calculate (a) the reactance, (b) the impedance, and (c) the current taken from a  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply. Determine also the phase angle between the supply voltage and current.



## RC Series AC Circuit

$$V = \sqrt{(V_R^2 + V_C^2)}$$

$$\tan \alpha = \frac{V_C}{V_R}$$

**impedance  $Z$ , i.e.  $Z = \frac{V}{I} \Omega$**        $Z = \sqrt{(R^2 + X_C^2)}$
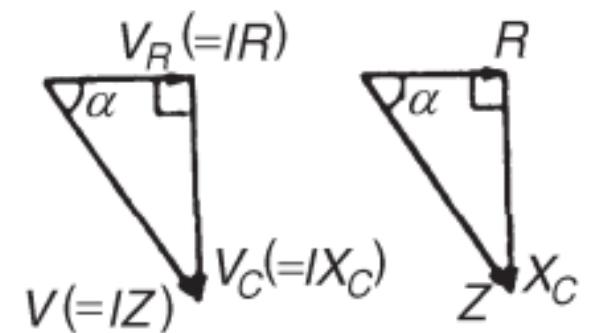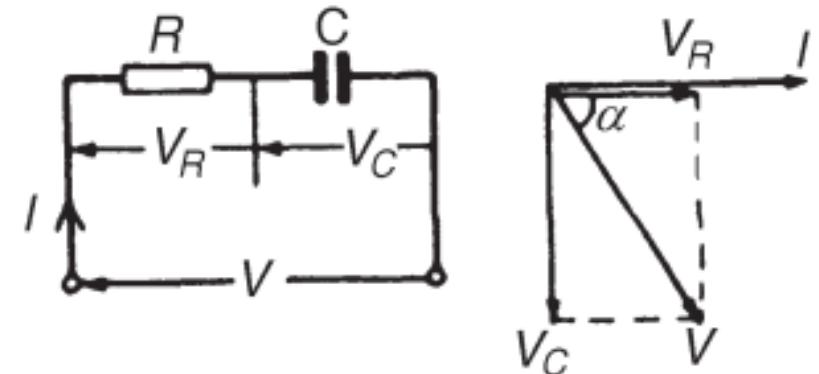
$$\tan \alpha = \frac{X_C}{R}, \sin \alpha = \frac{X_C}{Z} \text{ and } \cos \alpha = \frac{R}{Z}$$



# RC Series AC Circuit

A capacitor C is connected in series with a  $40\ \Omega$  resistor across a supply of frequency 60 Hz. A current of 3 A flows and the circuit impedance is  $50\ \Omega$ . Calculate: (a) the value of capacitance, C, (b) the supply voltage, (c) the phase angle between the supply voltage and current, (d) the p.d. across the resistor, and (e) the p.d. across the capacitor. Draw the phasor diagram.

# RC Series AC Circuit


A capacitor C is connected in series with a  $40 \Omega$  resistor across a supply of frequency 60 Hz. A current of 3 A flows and the circuit impedance is  $50 \Omega$ . Calculate: (a) the value of capacitance, C, (b) the supply voltage, (c) the phase angle between the supply voltage and current, (d) the p.d. across the resistor, and (e) the p.d. across the capacitor. Draw the phasor diagram.

# RLC Series AC Circuit


When  $X_L > X_C$

$$: Z = \sqrt{R^2 + (X_L - X_C)^2}$$
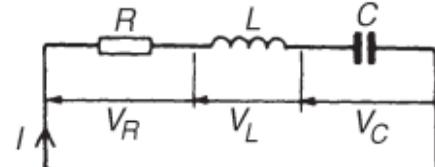
$$\text{and } \tan \phi = \frac{(X_L - X_C)}{R}$$



(a)

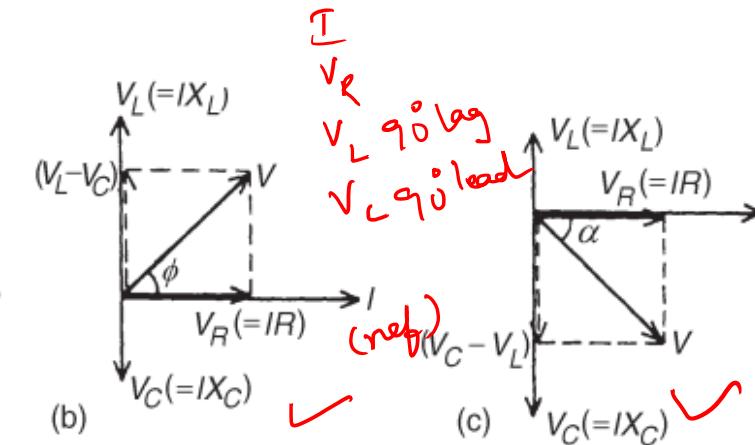

(b)


(c)

When  $X_C > X_L$


$$: Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\text{and } \tan \alpha = \frac{(X_C - X_L)}{R}$$

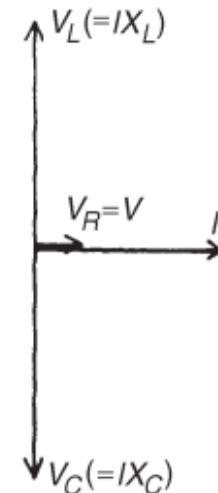When  $X_L = X_C$   
the applied voltage  $V$  and the current  $I$  are in phase. This effect is called **series resonance**




IMPEDANCE TRIANGLE

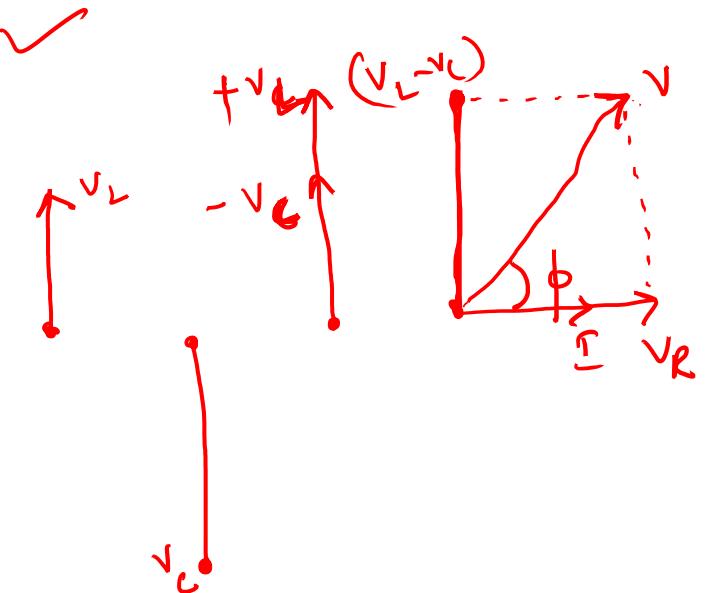
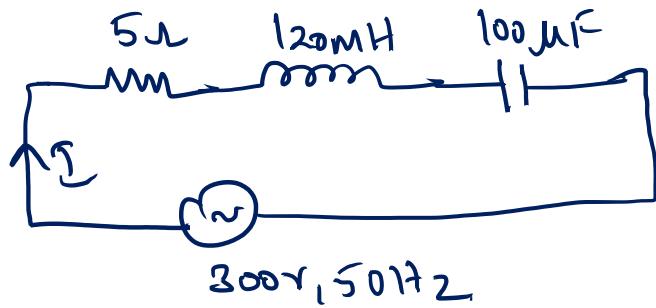
# RLC Series AC Circuit

A coil of resistance  $5 \Omega$  and inductance  $120 \text{ mH}$  in series with a  $100 \mu\text{F}$  capacitor, is connected to a  $300 \text{ V}, 50 \text{ Hz}$  supply.

Calculate (a) the current flowing, (b) the phase difference between the supply voltage and current, (c) the voltage across the coil and (d) the voltage across the capacitor.



Given data  $\underline{300 \sin 10t}$

$$\text{Resistance } (R) = 5\Omega$$

$$\text{Inductance } (L) = 120 \times 10^{-3} \text{ H}$$

$$\text{Capacitive reactance } (X_C) = 100 \times 10^{-6} \text{ F}$$

$$\text{Voltage } (V) = 300\text{V}$$

$$\text{frequency } (f) = 50 \text{ Hz}$$

Required data

Supply current ( $I$ )

Phase angle ( $\phi$ )

Inductive drop ( $V_L$ )

Capacitive drop ( $V_C$ )

Soln

\* ( $X_L$ ) Inductive reactance

$$X_L = 2\pi f L = 2 \times \frac{22}{7} \times 50 \times 120 \times 10^{-3}$$
$$= 37.68 \Omega$$

\* Capacitive reactance

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times \frac{22}{7} \times 50 \times 100 \times 10^{-6}}$$
$$= 31.38 \Omega$$

\* We infer,  $X_L > X_C$

# RLC Series AC Circuit

A coil of resistance  $5 \Omega$  and inductance  $120 \text{ mH}$  in series with a  $100 \mu\text{F}$  capacitor, is connected to a  $300 \text{ V}, 50 \text{ Hz}$  supply.

Calculate (a) the current flowing, (b) the phase difference between the supply voltage and current, (c) the voltage across the coil and (d) the voltage across the capacitor.

\* Supply current ( $I$ )

$$\begin{aligned}\text{Impedance } (Z) &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{5^2 + (37.68 - 31.38)^2} \\ &= 7.681 \Omega\end{aligned}$$

$$\text{By Ohms law, } I = \frac{V}{Z} = \frac{300}{7.681} = 39.05 \text{ A}$$

\* Phase angle ( $\phi$ )

$$\begin{aligned}\phi &= \tan^{-1} \left( \frac{X_L - X_C}{R} \right) \\ &= \tan^{-1} \left( \frac{37.68 - 31.38}{5} \right) = 49.43^\circ\end{aligned}$$

\* Inductive drop ( $V_L$ )

$$\begin{aligned}V_L &= I X_L \\ &= 39.05 \times 37.68 = 1471.4 \text{ V}\end{aligned}$$

\* Capacitive drop ( $V_C$ )

$$\begin{aligned}V_C &= I X_C \\ &= 39.05 \times 31.38 = 1225.38 \text{ V}\end{aligned}$$


\* Resistive drop ( $V_R$ )

$$V_R = 39.05 \times 5 = 195.25 \text{ V}$$

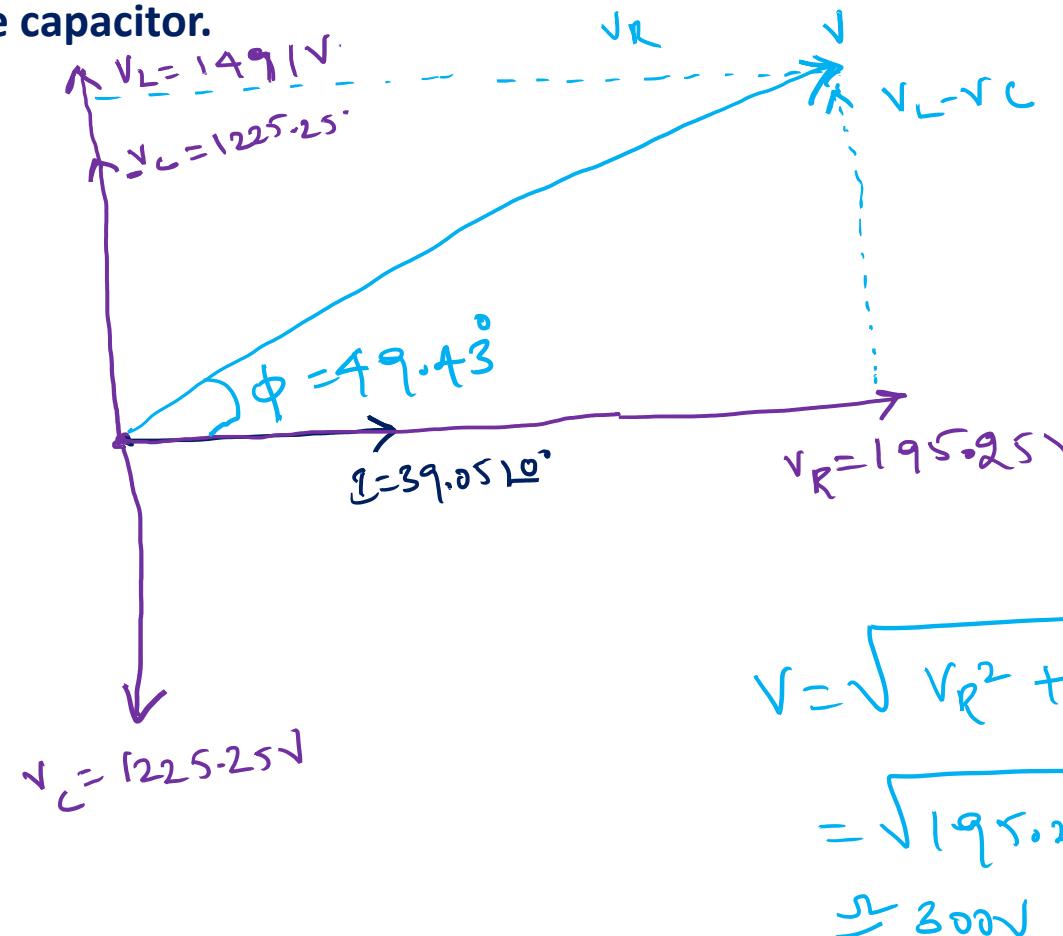
# RLC Series AC Circuit

A coil of resistance  $5 \Omega$  and inductance  $120 \text{ mH}$  in series with a  $100 \mu\text{F}$  capacitor, is connected to a  $300 \text{ V}, 50 \text{ Hz}$  supply.

Calculate (a) the current flowing, (b) the phase difference between the supply voltage and current, (c) the voltage across the coil and (d) the voltage across the capacitor.


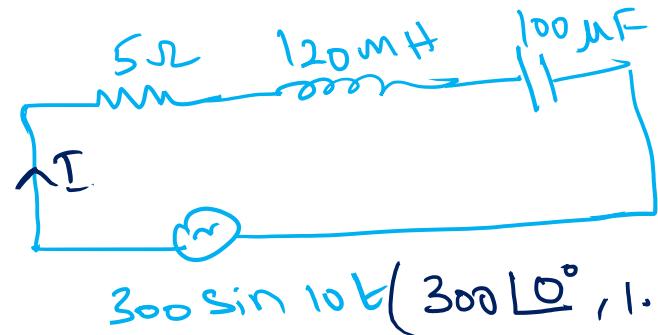
$$\begin{aligned}V &= \sqrt{V_R^2 + (V_L - V_C)^2} \\&= \sqrt{195.25^2 + (1471 - 1225)^2} \\&\approx 300 \text{ V}\end{aligned}$$



\*  $300 \sin 10t$

$$V_m \sin(\omega t + \phi)$$

$$\phi = 0^\circ$$


$$\omega = 10 = 2\pi f$$

$$f = \frac{10 \times 7}{2 \times 22} = \frac{70}{44} = 1.59 \text{ Hz}$$

$$* X_L = 120 \times 10^{-3} \times 2 \times 22 \times \frac{1}{7} \times 1.59 = 1.2 \Omega$$

$$X_C = \frac{1}{10 \times 100 \times 10^{-6}} = 100 \Omega$$


\* Circuit diagram in freq. domain

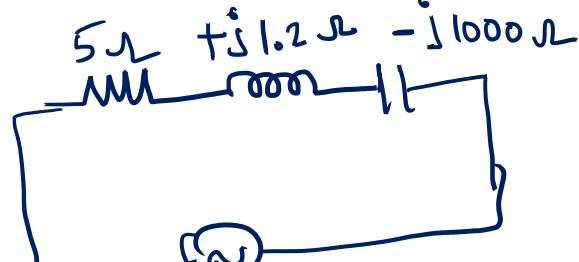

$$\begin{aligned} Z &= 5 + j1.2 - j1000 \Omega \\ &= 5 - j998.8 \angle 998.8^\circ \Omega \\ &= 998.8 \angle 270^\circ \Omega \end{aligned}$$

$$a + jb = r \angle \theta$$
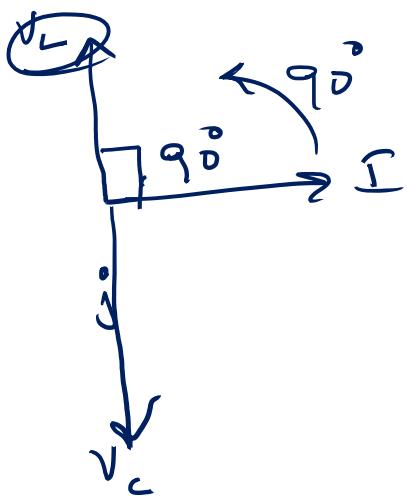
$$\begin{aligned} r &= \sqrt{a^2 + b^2} = 998 \\ \theta &= \tan^{-1}(b/a) = 270^\circ \end{aligned}$$



$$\begin{aligned} I &= \frac{V}{Z} \\ &= \frac{300 \angle 0^\circ}{998.8 \angle 270^\circ} \end{aligned}$$


$$I = 0.3 \angle -270^\circ \text{ A}$$

\* Resistive drop ( $V_R$ )

$$V_R = I R$$

$$= 0.3 \angle^{-270^\circ} \times 5 \cancel{\Omega}$$

$$= 1.5 \angle^{270^\circ} V //$$

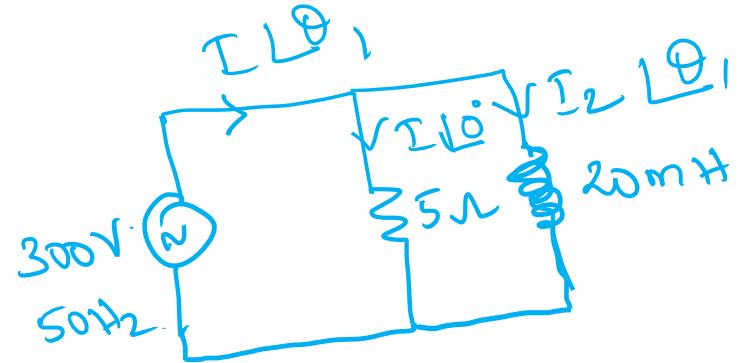

$$Z = \sqrt{\left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2 + R^2}$$

$$\frac{1}{Z} = \sqrt{\left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2 + \frac{1}{R^2}}$$


$X_L > X_C$

By Ohms law  $I = \frac{V}{R} = \frac{300}{5} = 60 \text{ A}$

\*  $I_2 = \frac{V}{X_L} = \frac{300}{2\pi \times 50 \times 10^{-3}} =$
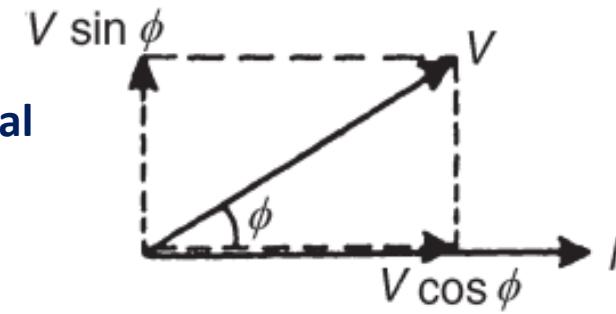
# Power Factor

The phasor diagram in which the current  $I$  lags the applied voltage  $V$  by angle  $\Phi$ . The horizontal component of  $V$  is  $V \cos \Phi$  and the vertical component of  $V$  is  $V \sin \Phi$ . If each of the voltage phasors is multiplied by  $I$ , known as the 'power triangle'.



(a) PHASOR DIAGRAM

Apparent power,  $S = VI$  volt amperes (VA)


True or active power,  $P = VI \cos \Phi$  watts (W)

Reactive power,  $Q = VI \sin \Phi$  reactive volt amperes (var)

$$\text{Power factor} = \frac{\text{True power } P}{\text{Apparent power } S}$$



For sinusoidal voltages and currents, power factor =  $\frac{P}{S} = \frac{VI \cos \phi}{VI}$ , i.e.
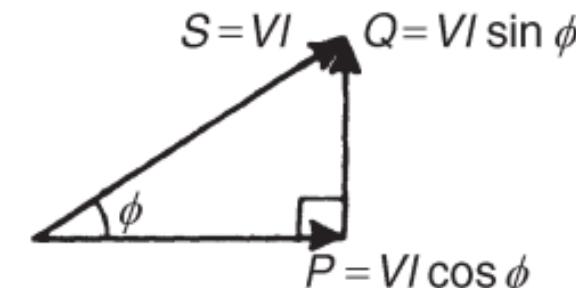
$$\text{p.f.} = \cos \phi = \frac{R}{Z}$$



(b) POWER TRIANGLE

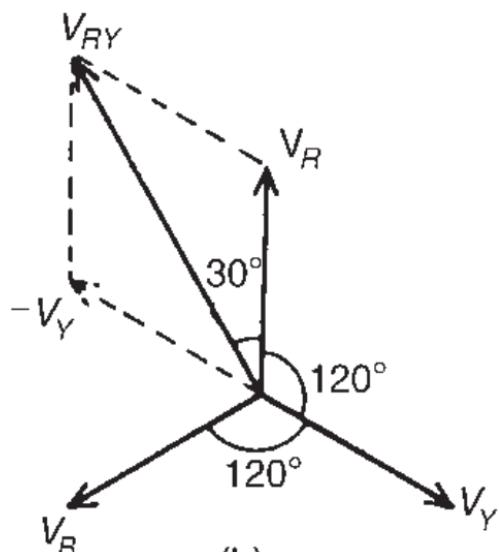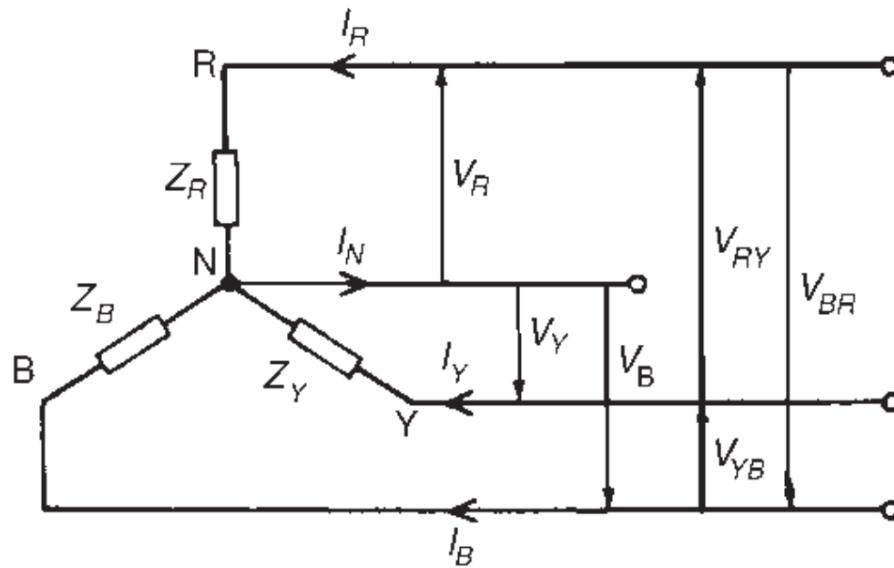
# Three Phase Systems – Star and Delta Connection



- A star-connected load is shown in Figure , where the three line conductors are each connected to a load and the outlets from the loads are joined together at N to form what is termed the neutral point or the star point.
- The voltages,  $V_R$ ,  $V_Y$  and  $V_B$  are called phase voltages or line to neutral voltages. Phase voltages are generally denoted by  $V_p$
- The voltages,  $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  are called line voltages
- The phase currents (generally denoted by  $I_p$ ) are equal to their respective line currents  $I_R$ ,  $I_Y$  and  $I_B$ , i.e. for a star connection

$$I_L = I_p$$
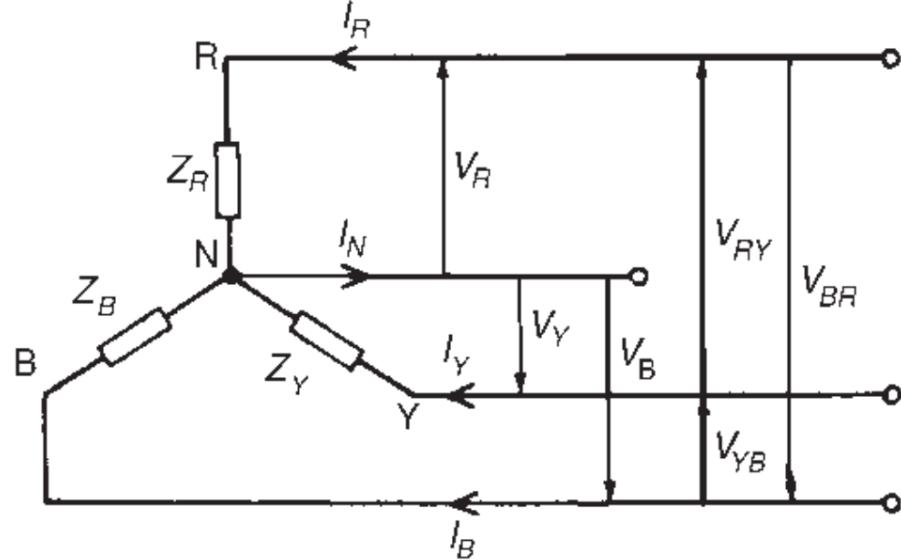
# Relation between Line and Phase Voltage in Star Connection



From the diagram, it is found that

$$V_{RY} = V_R + (-V_Y)$$

$$\text{Similarly, } V_{YB} = V_Y + (-V_B)$$

$$V_{BR} = V_B + (-V_R)$$

$$V_L = |V_{RY}| = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ}$$

$$= \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph} V_{ph} \times \frac{1}{2}}$$

$$= \sqrt{3}V_{ph}$$

$$\therefore V_L = \sqrt{3}V_{ph}$$


Thus, for the star-connected system line voltage =  $\sqrt{3} \times$  phase voltage.

Line current = Phase current



$$V_{ph} I_{ph} \cos \phi = \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

So the total power of three phase system is
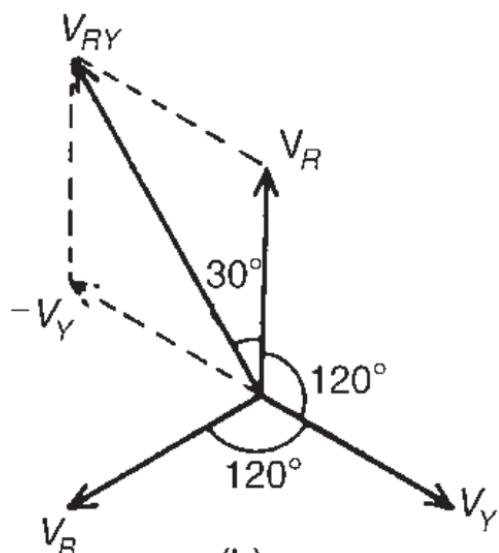
$$3 \times \frac{V_L}{\sqrt{3}} I_L \cos \phi = \sqrt{3} V_L I_L \cos \phi$$






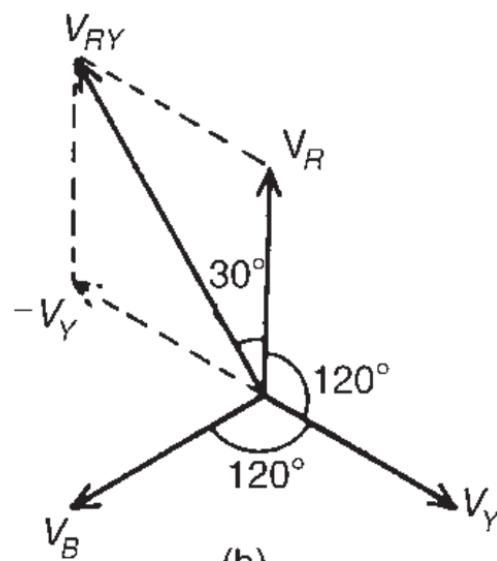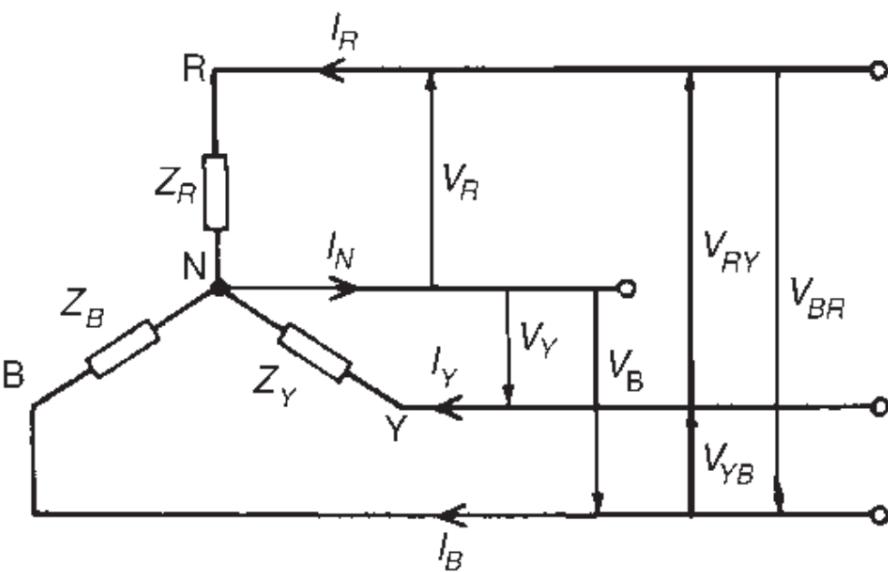
# Three Phase Systems – Star and Delta Connection



- For a balanced system:  $I_R = I_Y = I_B$ ,  $V_R = V_Y = V_B$ ,  $V_{RY} = V_{YB} = V_{BR}$ ,  $Z_R = Z_Y = Z_B$
- The current in the neutral conductor,  $I_N = 0$ , When a star connected system is balanced, then the neutral conductor is unnecessary and is often omitted.
- The line voltage,  $V_{RY}$ , shown in Figure is given by  $V_{RY} = V_R - V_Y$  ( $V_Y$  is negative since it is in the opposite direction to  $V_{RY}$ ).
- The phasor  $V_Y$  is reversed (shown by the broken line) and then added phasorially to  $V_R$  (i.e.  $V_{RY} = V_R + (-V_Y)$ ).
- By trigonometry, or by measurement,  $V_{RY} = \sqrt{3}V_R$ , i.e. for a balanced star connection.
- $V_L = \sqrt{3}V_P$
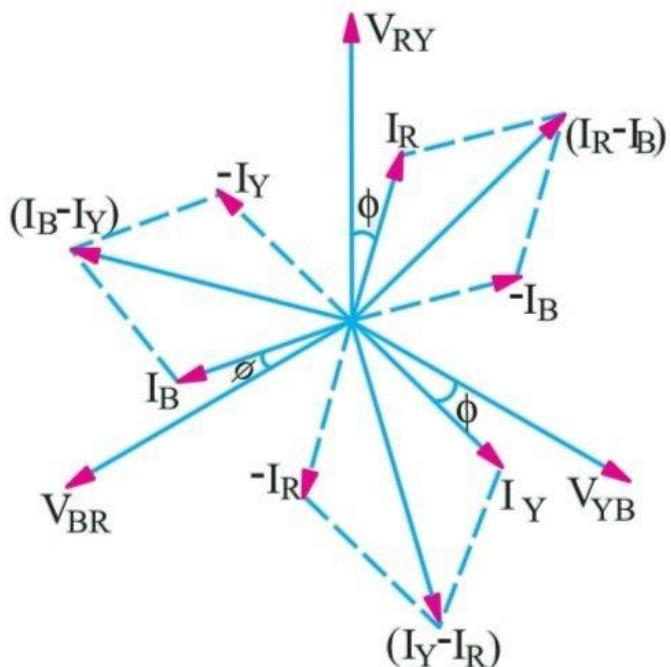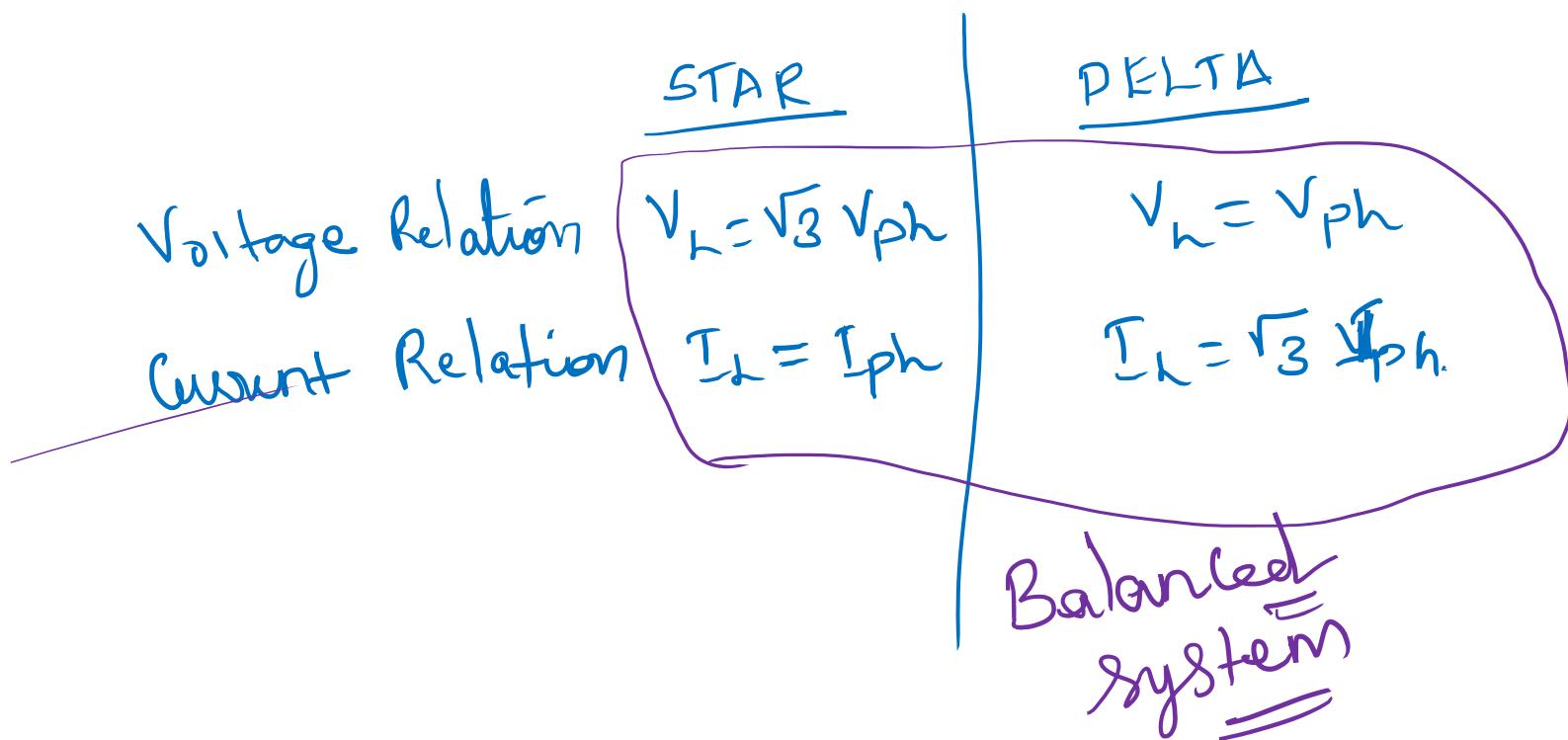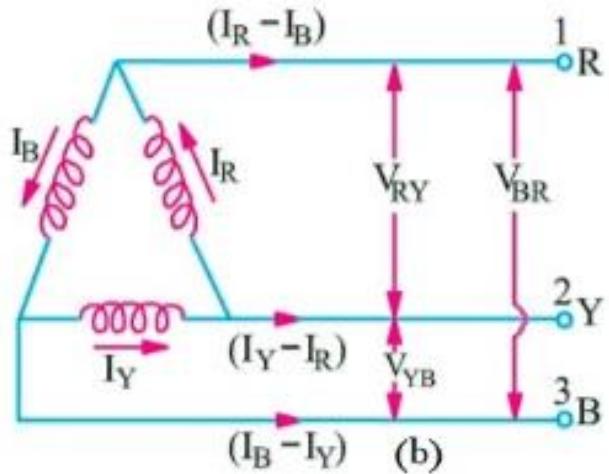
# Relation between Line and Phase Voltage in Delta Connection



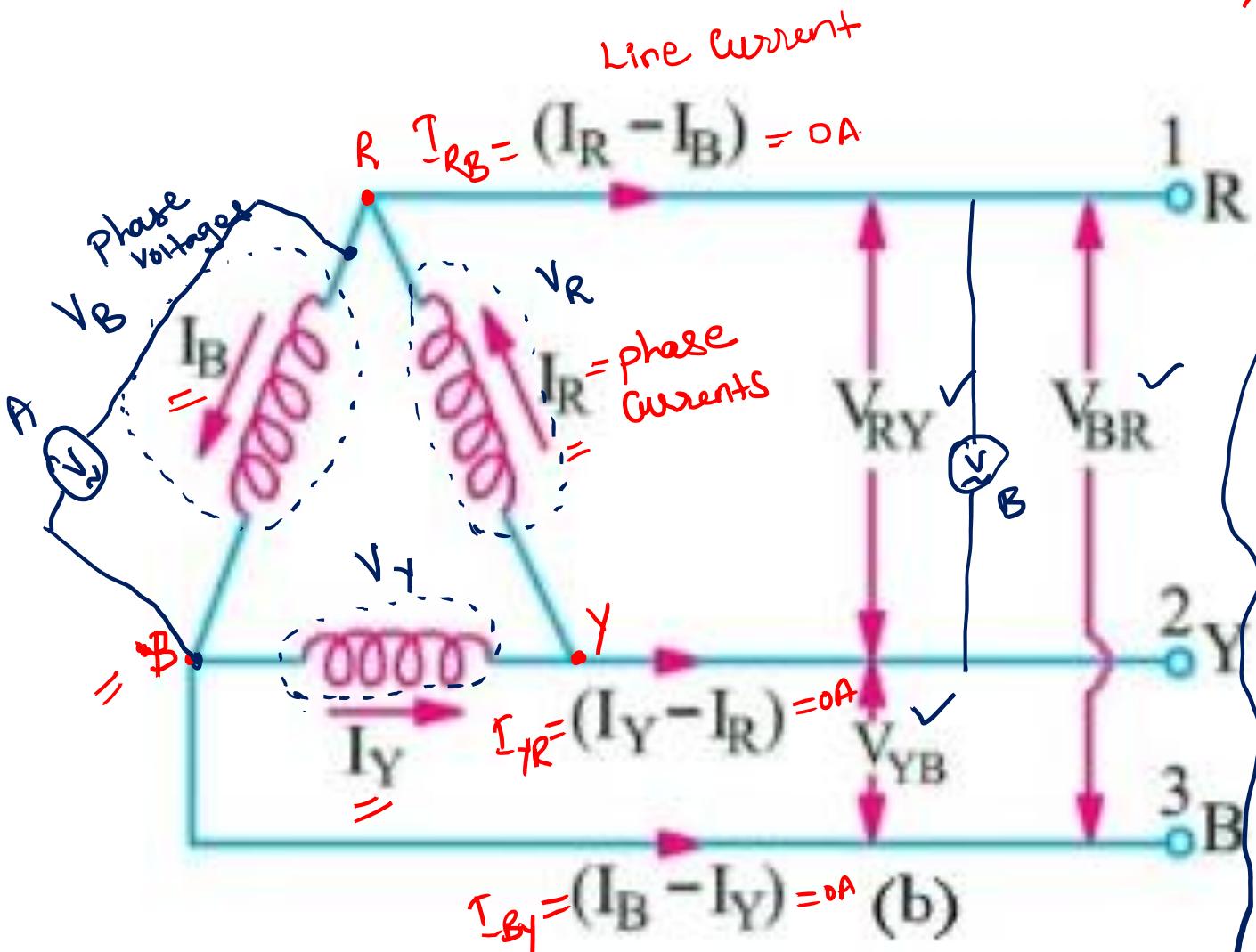


$$I_R = I_B = I_Y = 10A$$

$$V_R = V_Y = V_B = V_{ph}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

$$V_L = V_{ph}$$

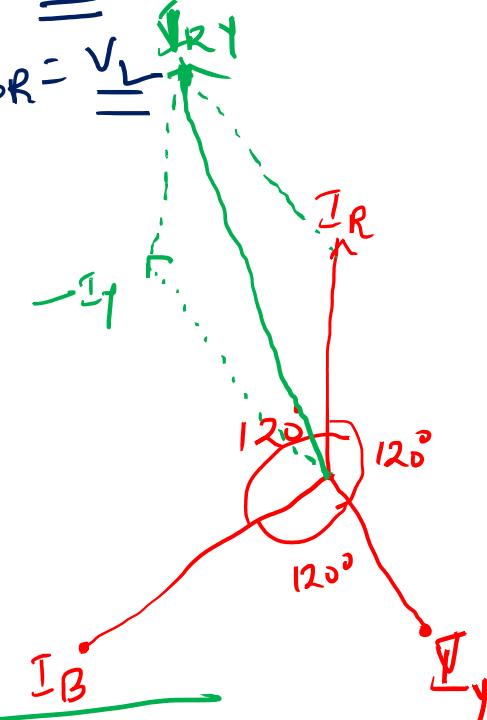

$$I_{RY} = \sqrt{I_R^2 + I_Y^2 + 2 I_R I_Y \cos 60^\circ}$$

$$= \sqrt{I_{ph}^2 + I_{ph}^2 + 2 I_{ph}^2 (1/2)}$$

$$I_L = \sqrt{3} I_{ph}$$