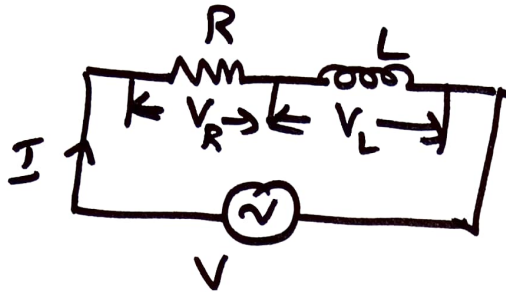


## RL Series circuit



$V = V_m \sin \omega t$  - applied voltage

$i$  = instantaneous current

$f$  = frequency.

Voltage across Resistor  $R = V_R = IR$

Voltage across inductor  $L = jIX_L = V_L$ .

$$\therefore V = V_R + V_L$$

$$= IR + jIX_L$$


$$= I(R + jX_L)$$

$$\frac{V}{I} = R + jX_L = Z$$


$$Z = R + jX_L$$

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} X_L / R$$

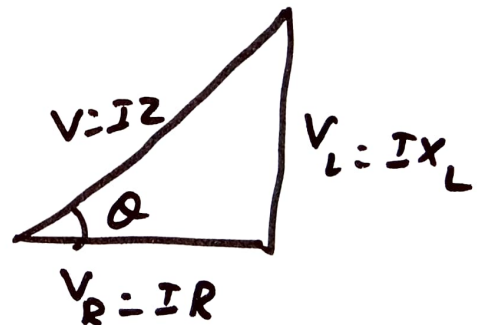

Voltage triangle

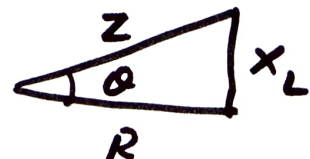

power factor :  $p.f = \cos \phi$

From the impedance triangle

$$\cos \phi = \frac{R}{Z} \quad (\text{or}) \quad \cos \left[ \tan^{-1} \left( \frac{X_L}{R} \right) \right]$$

Hence  $I$  lags the voltage.  $\therefore$  p.f is also lagging.

Active power (or) real power =  $VI \cos \phi$

$$= VI \cdot \frac{R}{Z}$$

$$= \frac{V}{Z} IR = I^2 R.$$

Reactive power =  $VI \sin \phi$

$$= VI \cdot \frac{X_L}{Z} = I^2 X_L.$$

1. A coil having a resistance of  $10\Omega$  and an inductance of  $0.01\text{ H}$  is connected across a  $220\text{V}$ ,  $50\text{Hz}$  supply. calculate (a) the current  
b) phase angle between current and voltage  
c) p.f (d) power.

Soln:.

$$V = 220V, R = 10\Omega, f = 50Hz, L = 0.01H$$

$$X_L = 2\pi fL = 3.141\Omega.$$

$$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 3.14^2} = 10.48\Omega$$


$$a) \text{ current } I = \frac{V}{Z} = \frac{220}{10.48} = 20.99A.$$

$$b) \phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{3.141}{10} = 17.43^\circ \text{ lag.}$$

$$c) P.f = \cos\phi = 0.954 \text{ lag.}$$

$$\begin{aligned} d) \text{ power} &= VI \cos\phi \\ &= 220 \times 20.99 \times 0.954 \\ &= 4406.2W. \end{aligned}$$


RL series circuit

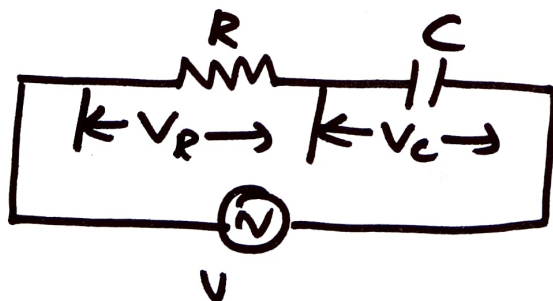

$$V = V_m \sin \omega t$$

$i$  : instantaneous current

$f$  : frequency

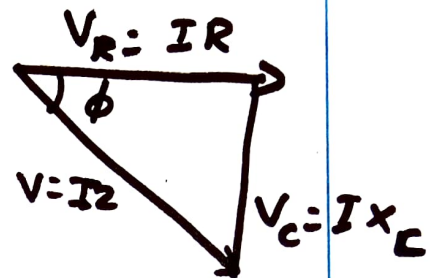

voltage across  $R$  :  $V_R = IR$  in phase with  $I$

voltage across  $C$  :  $V_C = IX_C$  lagging  $I$  by  $90^\circ$ .

$$V = V_R + V_C.$$

voltage triangle

$$V = IR - jIX_C = I(R - jX_C)$$

$$\frac{V}{I} = R - jX_C = Z$$


$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{1/\omega C}{R} = \tan^{-1} \frac{1}{\omega CR}$$

$$X_C = \frac{1}{\omega C}$$

$\phi$  : phase angle

$$Z = R - jX_C = |Z| \angle -\phi$$

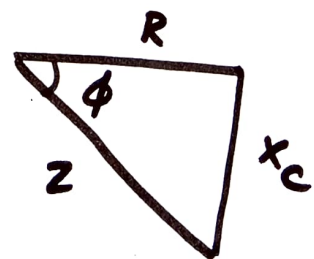

$$P.f = \cos \phi = R/Z.$$

Active power =  $VI \cos \phi$  (watts)

Reactive power =  $VI \sin \phi$  (VAR)

Find the circuit constants of a two element series circuits which consumes 700W with 0.707 leading p.f. The applied voltage is

$$V = 141.4 \sin 314t.$$

Soln:...

$$V_m = 141.4$$

$$V_{rms} = \frac{141.4}{\sqrt{2}} = 99.98 \text{ V.}$$

$$\cos \phi = 0.707 \text{ leading}$$

$$\text{power} = VI \cos \phi$$

$$700 = 99.98 \times I \times 0.707.$$

$$I = 9.9 \text{ A.}$$

$$Z = \frac{V}{I} = \frac{99.98}{9.9} = 10.09 \Omega.$$

$$\cos \phi = R/Z$$

$$R = Z \cos \phi$$

$$= 10.09 \times 0.707 = 7.13 \Omega.$$

$$\phi = \cos^{-1} 0.707 = 45^\circ$$



$$\sin \phi = \frac{X_C}{Z} \Rightarrow X_C = Z \sin \phi$$


$$\begin{aligned} X_C &= 10.09 \times \sin 45^\circ \\ &= 10.09 \times 0.707 \\ &= 7.13 \Omega. \end{aligned}$$

$$X_C = \frac{1}{2\pi fC}$$

$$C = \frac{1}{2\pi X_C} = 446.6 \mu F.$$
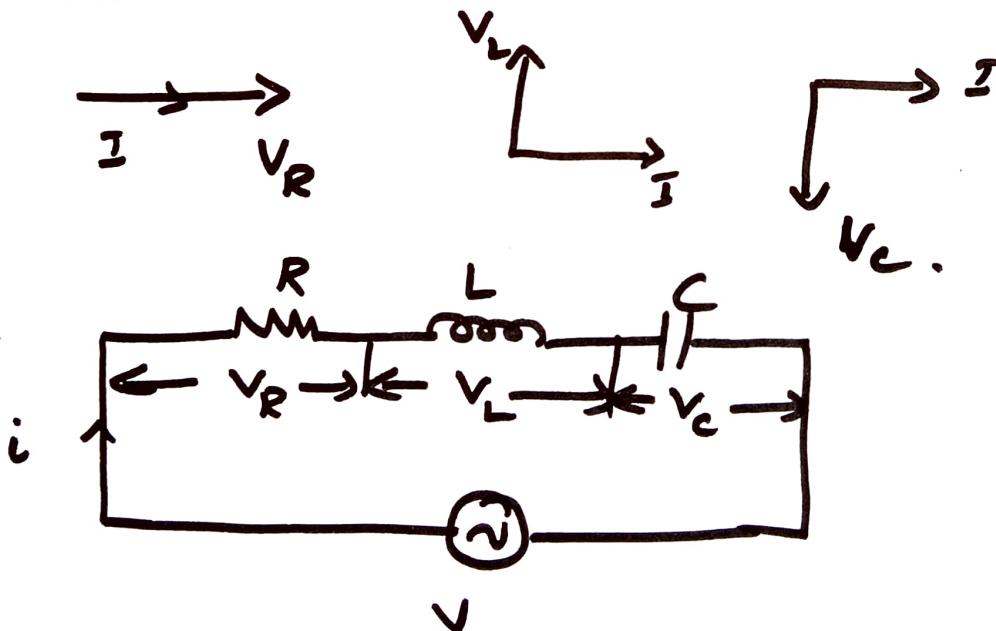
## RLC Series circuits

consider a circuit having Resistance  $R \Omega$ , inductance  $L$  Henrys and capacitance  $C$  farads all are connected in series.



$$V = V_m \sin \omega t$$

$i$  : instantaneous current

$I$  is taken as reference vector

Voltage across  $R = V_R = IR$  in phase with  $I$

Voltage across  $L = V_L = IX_L \angle 90^\circ$   $V$  leads  $I$  by  $90^\circ$ .

$$= jIX_L$$

Voltage across  $C = V_C = IX_C \angle -90^\circ$   $V$  lags  $I$  by  $90^\circ$ .

$$= -jIX_C$$

Applied voltage  $V = V_R + V_L + V_C$ .

$$= IR + jIX_L - jIX_C$$

$$= I(R + jX_L - jX_C)$$

$$\frac{V}{I} = Z = (R + jX_L - jX_C)$$

$$= R + j(X_L - X_C)$$

$$= Z \angle \phi$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$



$(X_L - X_C) \rightarrow$  net reactance.

If  $X_L > X_C$  the circuit behaves like R-C circuit.

If  $X_C > X_L$  the circuit behaves like R-L circuit.

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

case (i) If  $X_L > X_C$ .

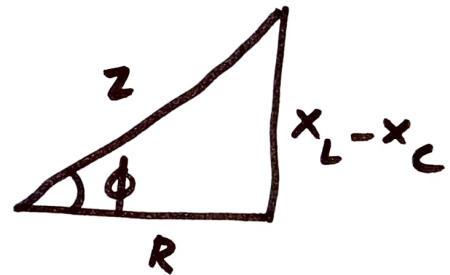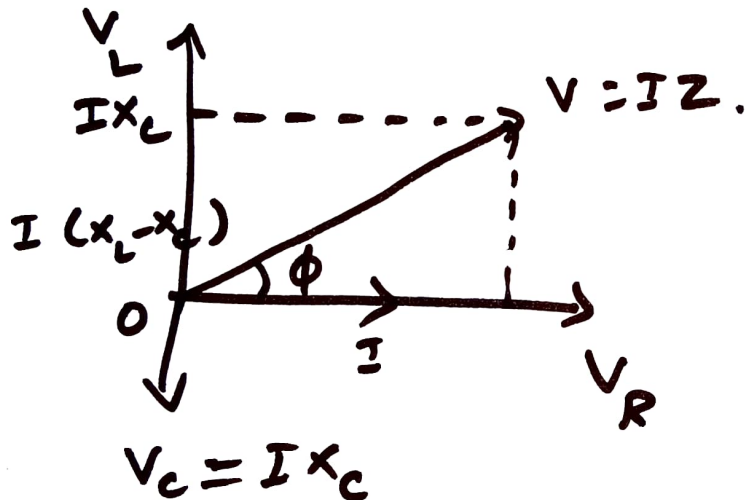

$$\tan \phi = \frac{X_L - X_C}{R}$$



$$= \frac{(\omega L - 1/\omega C)}{R}$$

$$\phi = \tan^{-1} \left( \frac{\omega L - 1/\omega C}{R} \right)$$

$$P.F. = \cos \phi = R/Z \text{ lagging (R-L)}$$



Case (ii) If  $x_c > x_L$  RC circuit-

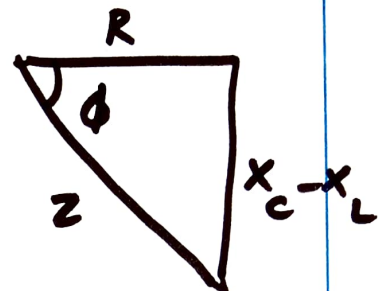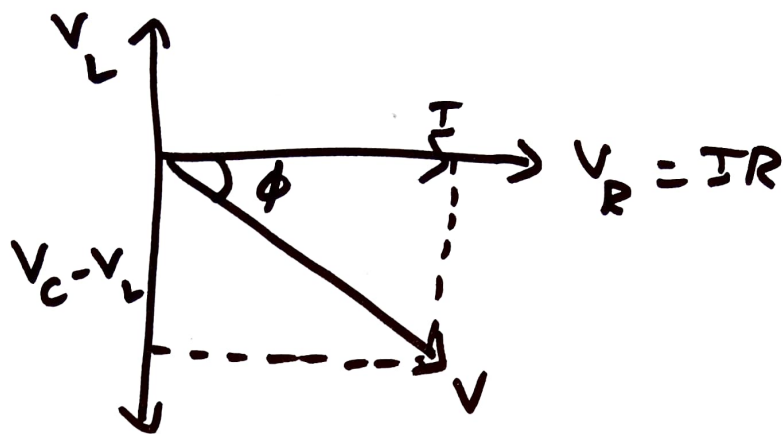

$$V_c = IX_c$$

$$\tan \phi = \frac{x_c - x_L}{R} = \frac{\frac{1}{\omega c} - \omega L}{R}$$

$$\phi = \tan^{-1} \left( \frac{\frac{1}{\omega c} - \omega L}{R} \right)$$

$$\text{P.f} = \cos \phi = R/Z, \text{ leading (RC circuit)}$$

$$\text{Actual power} = VI \cos \phi \text{ (watts)}$$

$$\text{Reactive power} = VI \sin \phi \text{ (VAR)}$$

A coil of resistance  $10\Omega$  and  $L = 0.1\text{H}$  is connected in series with a  $150\mu\text{F}$  capacitor across  $200\text{V}$ ,  $50\text{Hz}$  supply. calculate (a) inductive reactance (b) capacitive reactance (c) impedance (d) current (e) p.f (f) voltage across coil and capacitor.

Solution:

$$\text{a) } X_L = \omega L = 2\pi fL = 31.42\Omega.$$

$$\text{b) } X_C = 1/\omega C = 1/2\pi fC = 21.22\Omega.$$

$$\text{c) } Z = \sqrt{R^2 + (X_L - X_C)^2} = 14.28\Omega$$

$$\text{d) } I = \frac{V}{Z} = \frac{220}{14.28} = 14\text{A}.$$

$$\text{e) } \text{p.f} = \cos\phi = R/Z = 0.7.$$

$$\text{f) Voltage across coil} = I \times \text{impedance of the coil}$$

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{10^2 + 31.42^2} = 32.97\Omega. \end{aligned}$$

$$V_{\text{coil}} = 461.62\text{V}.$$

$$V_C = IX_C = 297.08\text{V}.$$