

AC CIRCUITS

①

LECTURE # 12, 13


SINUSOIDS & PHASORS

$$\text{Sinusoid } v(t) = V_m \sin \omega t$$

V_m = amplitude

ω = angular frequency (rad/s)

ωt = argument of the sinusoid.

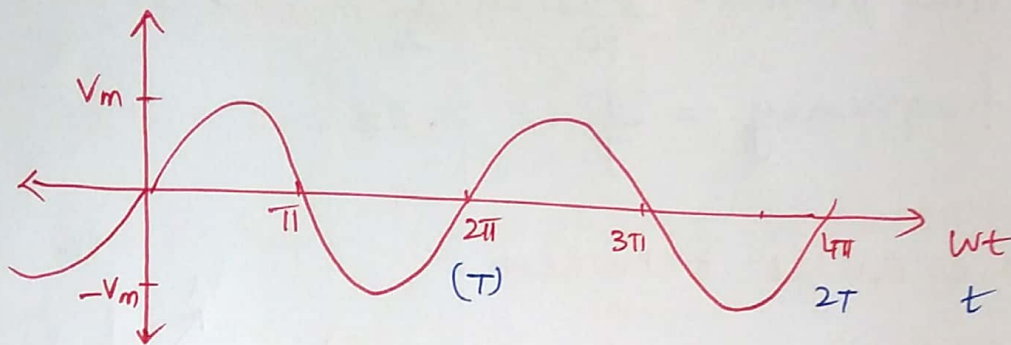

$$T = \frac{2\pi}{\omega} = \text{time period of sinusoid.}$$

Sinusoid is periodic : $v(t) = v(t+T)$


Time period $T \rightarrow$ number of secs/cycle.

$$f = \frac{1}{T} = \text{frequency} \rightarrow \text{cycles/sec.}$$

$$\omega = 2\pi f \text{ (rad/s)} \quad \downarrow \text{Hertz.}$$

If we have two sinusoids.
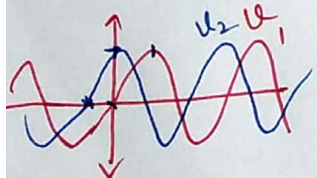
$$v_1(t) = V_m \sin \omega t \quad v_2(t) = V_m \sin(\omega t + \phi)$$



then ϕ = phase angle between v_1 & v_2

v_1 lags v_2 by ϕ (or) v_2 leads v_1 by ϕ .

(2)

example

① $v(t) = 12 \cos(4\pi t - 75^\circ)$

Amplitude $V_m = 12$

phase $\phi = -75^\circ$

angular frequency $\omega = 4\pi = 12.57 \text{ rad/s}$


$$\text{Time period} = \frac{2\pi}{\omega} = \frac{1}{2} = 0.5 \text{ s.}$$

$$\text{frequency} = \frac{1}{T} = 2 \text{ Hz.}$$

② phase angle between.

$$i_1(t) = -4 \sin(377t + 55^\circ)$$

$$i_2(t) = 5 \cos(377t - 65^\circ)$$

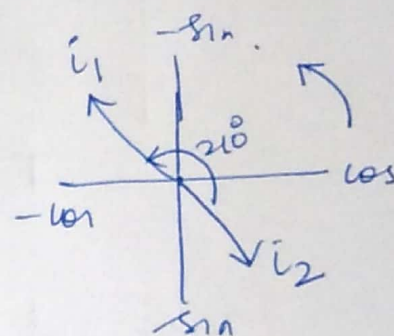

$$i_1(t) = 4 \cos(377t + 55 + 90^\circ)$$

$$= 4 \cos(377t + 145^\circ)$$

$$i_2(t) = 5 \cos(377t - 65^\circ)$$

$\phi = 210^\circ$ i_1 leads i_2 by 210° .

PHASOR

- complex $z = x + jy$

$$z = r \angle \phi$$

$$z = r e^{j\phi}$$


$$u(t) = V_m \cos(\omega t + \phi)$$

$$= \operatorname{Re} \{ V_m e^{j(\omega t + \phi)} \}$$

$$= \operatorname{Real} \{ \underline{V}_m e^{j\omega t} \cdot e^{j\phi} \}$$

$$u(t) = \operatorname{Re} \{ V e^{j\omega t} \}$$
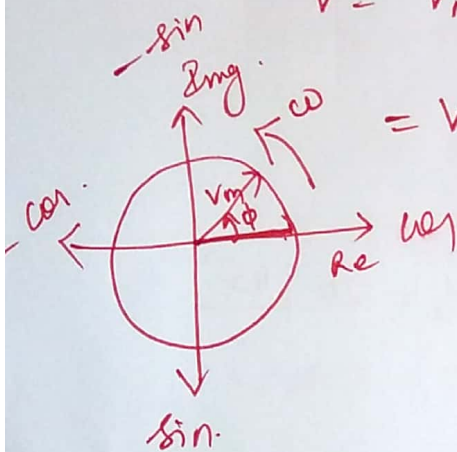
$$V = V_m e^{j\phi} \rightarrow \text{phasor representing the sinusoid.}$$



$$= V_m \angle \phi$$

projection Real axis $\cos \omega t$

$$u(t) = 7 \cos(2t + 40^\circ) \Rightarrow V = 7 \angle 40^\circ \quad \omega = 2 \text{ rad/s.}$$

$$i(t) = -4 \sin(10t + 10^\circ) \Rightarrow \underline{I} =$$

$$= 4 \cos(10t + 10 + 90^\circ)$$

$$= 4 \cos(10t + 100^\circ) \Rightarrow \underline{I} = 4 \angle 100^\circ \quad \omega = 2 \text{ rad/s.}$$

PRACTICE

$$V = -25 \angle 40^\circ$$

$$I = j(12 - j5)$$

$$I_{eff}$$

sum of two phasors

$$u_1 = -10 \sin(\omega t - 30^\circ)$$

$$u_2 = 20 \cos(\omega t + 45^\circ)$$

$$u = u_1 + u_2 = ?$$

④

Sum of phasors


$$u_1(t) = -10 \cos(\omega t - 30^\circ)$$

$$u_2(t) = 20 \cos(\omega t + 45^\circ)$$

Find $u = u_1 + u_2$.

To add this in time domain, we need to use $\cos(A+B)$ identity and simplify.

Hence change to phasor domain and solve.

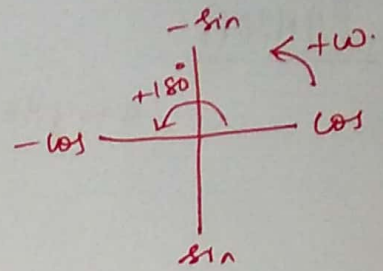

$$V_1(t) = +10 \cos(\omega t - 30^\circ + 180^\circ)$$

$$= 10 \cos(\omega t + 150^\circ)$$

$$\therefore V_1 = 10 \angle 150^\circ$$

$$u_2(t) = 20 \cos(\omega t + 45^\circ) \therefore V_2 = 20 \angle 45^\circ$$

$$V = V_1 + V_2$$

$$V = 10 \angle 150^\circ + 20 \angle 45^\circ$$

$$V = 19.91 \angle 74^\circ \cdot V$$

PRACTICE

$$u_1(t) = -10 \sin(\omega t - 20^\circ)$$


$$u_2(t) = \sin(\omega t + 10^\circ)$$

Find $u_1(t) + u_2(t)$.



Angle between phasors

$$u_1(t) = -10 \sin(\omega t - 30^\circ) = 10 \cos(\omega t + 60^\circ)$$
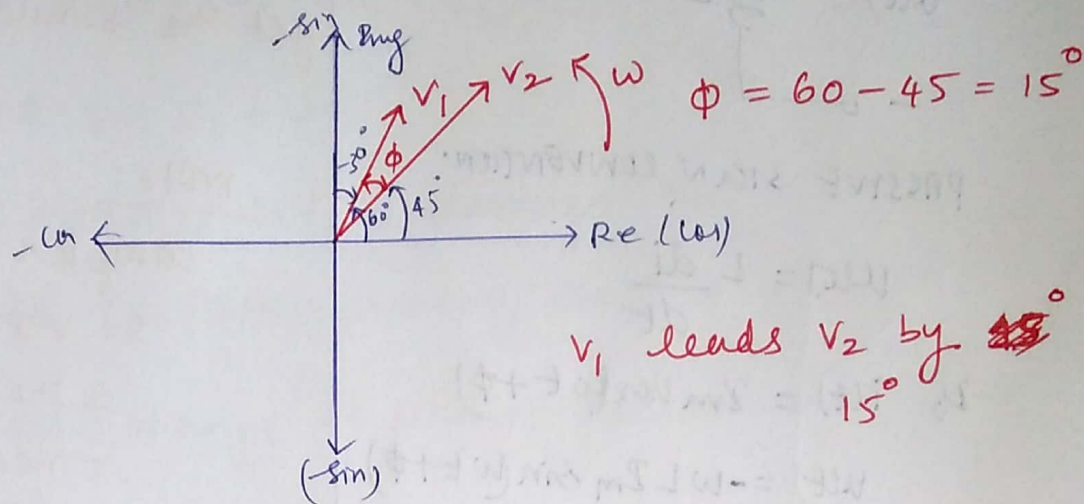
$$u_2(t) = 20 \cos(\omega t + 45^\circ)$$



PHASOR RELATIONSHIPS OR R, L, C

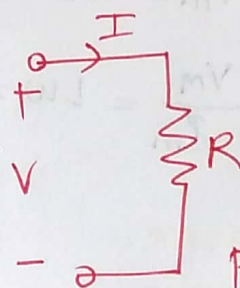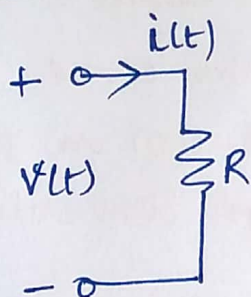

phasor equivalent of R.

$$u(t) = i(t) \cdot R$$

$$\text{If } i(t) = I_m \cos(\omega t + \phi)$$


$$u(t) = R I_m \cos(\omega t + \phi)$$

V_m

As phasors,

$$I = I_m \angle \phi$$


$$V = V_m \angle \phi$$

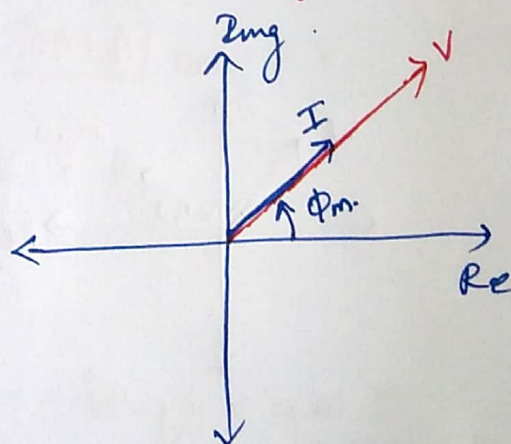

V, I in phase for a resistor.

6

Inductor (L).

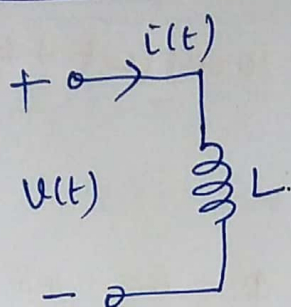

PASSIVE SIGN CONVENTION.

$$v(t) = L \frac{di}{dt}$$

$$\text{Let } i(t) = I_m \cos(\omega t + \phi)$$

$$v(t) = -\omega L I_m \sin(\omega t + \phi)$$

$$= V_m \cos(\omega t + \phi + 90^\circ)$$


$$\text{Where } V_m = \omega L I_m.$$

$$\text{Inductive reactance } \Leftarrow \frac{V_m}{I_m} = \omega L = |X_L|$$

In phasor form.

$$I = I_m \angle \phi$$

$$V = V_m \angle \phi + 90^\circ$$

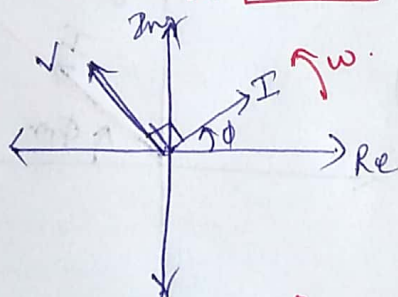

I lags V by 90° .

Complex power

$$S = V I^* = V_m I_m \angle \phi + 90 - \phi$$

$$S = P + jQ = V_m I_m \angle 90^\circ$$

$$S = P + jQ = 0 + j V_m I_m$$

To do:

Try and repeat the same for inductor in active sign convention and get the similar conclusions.

Note:

Complex power.

$$S = V I^* \text{ (defined)}$$

$$= P + jQ$$

= real power + reactive power.

$$P = 0 \text{ (no real power)}$$

$$Q = V_m I_m \text{ (+ve)}$$

In this case of Inductor in passive sign convention.

$$\Rightarrow \omega L I_m \angle \phi \angle 90^\circ$$

$$\therefore V = j\omega L I \quad v(t) = L \frac{di}{dt}$$

$$\frac{V}{I} = j\omega L$$


We see that

$$\frac{d}{dt} \rightarrow j\omega$$

In phasor domain

$$L \rightarrow j\omega L$$

Capacitor (C)

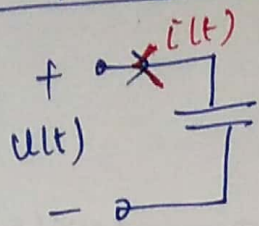

active sign convention

$$i(t) = -C \frac{du}{dt}$$

$$\text{let } u(t) = V_m \cos(\omega t + \phi)$$

$$\begin{aligned} i(t) &= +C\omega V_m \sin(\omega t + \phi) \\ &= C\omega V_m \cos(\omega t + \phi - 90^\circ) \end{aligned}$$

In phasor form,

$$V = V_m \angle \phi$$

$$\begin{aligned} I &= C\omega V_m \angle \phi - 90^\circ = -jC\omega V \\ &= Z_m \angle \phi - 90^\circ \Rightarrow X_C = \frac{1}{j\omega C} \end{aligned}$$

X_C = capacitive reactance.

Complex power

$$S = VI^* = V_m \angle \phi \cdot Z_m \angle 90 - \phi$$

$$S = P + jQ = V_m Z_m \angle 90^\circ$$

$$P + jQ = 0 + jV_m Z_m$$

$P = 0$ (real power is zero)

$Q = V_m Z_m$ (reactive power).

Hence,

$$\int \rightarrow \frac{1}{j\omega} \text{ in phasor domain}$$

$$C \rightarrow \frac{1}{j\omega C}$$

Todo:

Repeat for capacitor in passive sign convention. ⑦


note:

$$i(t) = -C \frac{du}{dt}$$

$$I = \frac{C V}{(1/j\omega)}$$

$$(\text{or}) u(t) = \frac{1}{C} \int i(t) dt$$

$$V = \frac{1}{C} \frac{I}{j\omega}$$

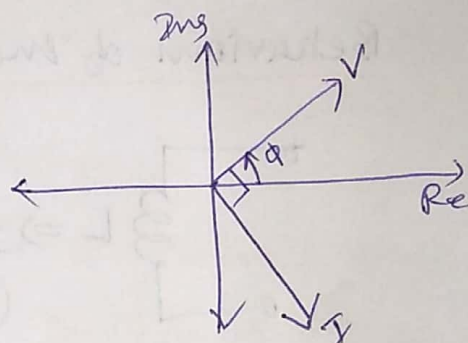

I lags V by 90° .

8

Impedance and Admittance.

In phasor domain,


$$V = RI \Rightarrow Z = R \quad \text{Impedance (Z)}$$

$$V = j\omega L I \Rightarrow Z = j\omega L \quad \text{Admittance}$$

$$V = \frac{1}{j\omega C} I \Rightarrow Z = \frac{1}{j\omega C} \quad Y = \frac{1}{Z}$$

Impedance $Z = R + jX$. (Resistance + reactance)

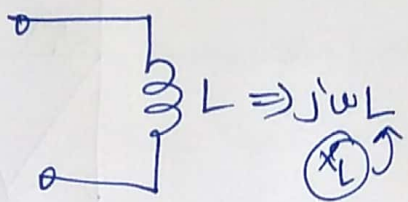Behaviour of Inductor and Capacitor at diff frequency




As $\omega \rightarrow 0$ $X_L \rightarrow 0$ (dc)

Inductor \rightarrow SC

As $\omega \rightarrow \infty$ $X_L \rightarrow \infty$ (high freq ac)

Inductor \rightarrow OC

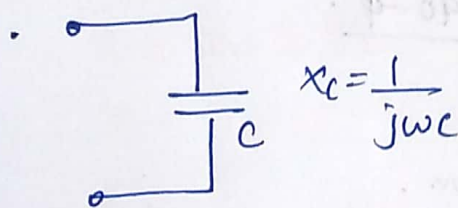

As $\omega \rightarrow 0$, $X_C \rightarrow \infty$ (dc)

Capacitor \rightarrow open circuited (OC)

As $\omega \rightarrow \infty$, $X_C \rightarrow 0$ (ac)

Capacitor \rightarrow short circuited (SC)

note:

Capacitor in open circuit to dc. Hence it acts as a filter, allowing dc (low freq) to pass through and block high frequency ac signals (act as a SC $V=0$).

Application of Phasors

(1) Solving an integro-differential equation.

In phasor domain

$$\frac{d}{dt} \rightarrow j\omega \quad \int \rightarrow \frac{1}{j\omega}$$

Consider,

$$2 \frac{du}{dt} + 5u(t) + 10 \int u(t) dt = 50 \cos(5t - 30^\circ)$$

Transform to phasor domain, $\omega = 5 \text{ rad/s}$.

$$2 j\omega V + 5V + 10 \frac{V}{j\omega} = 50 \angle -30^\circ$$

$$V \left[5 + j10 + \frac{10}{5j} \right] = 50 \angle -30^\circ$$

$$V [5 + j10 - j2] = 50 \angle -30^\circ$$

$$V = \frac{50 \angle -30^\circ}{5 + j8}$$

$$V = 0.1855 - 5.2967j$$

$$V = 5.299 \angle -87.99^\circ$$

$$V \approx 5.3 \angle -88^\circ$$

$$\therefore u(t) = 5.3 \cos(5t - 88^\circ)$$

PRACTICE (9.25) sadiku.

$$(a) 2 \frac{di}{dt} + 3i(t) = 4 \cos(2t - 45^\circ)$$


$$(b) 10 \int i(t) dt + \frac{di}{dt} + 6i(t) = 5 \cos(5t + 22^\circ) \text{ A}$$

(10)

(2) solving circuit with ac source in phasor domain.

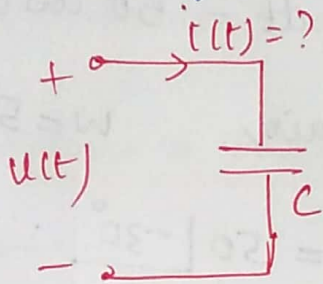example

24 $v = 10 \cos(100t + 30^\circ)$ is applied to a $50 \mu\text{F}$ capacitor, calculate the current through the capacitor.



$$v(t) = 10 \angle 30^\circ$$

$$\omega = 100 \text{ rad/s}$$

$$C = 50 \mu\text{F}$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times 100 \times 50 \times 10^{-6}}$$

$$V = IZ = IX_C$$

$$I = \frac{V}{Z}$$
$$= \frac{10 \angle 30^\circ}{200 \angle -90^\circ}$$

$$X_C = -j200 \Omega$$
$$= 200 \angle -90^\circ$$

$$I = 0.05 \angle 120^\circ$$

$$\therefore i(t) = 0.05 \cos(100t + 120^\circ) \text{ A}$$

PRACTICE

The voltage $v(t) = -12 \cos(60t + 45^\circ)$ is applied to a 0.1 H inductor. Find the steady state current through the inductor.