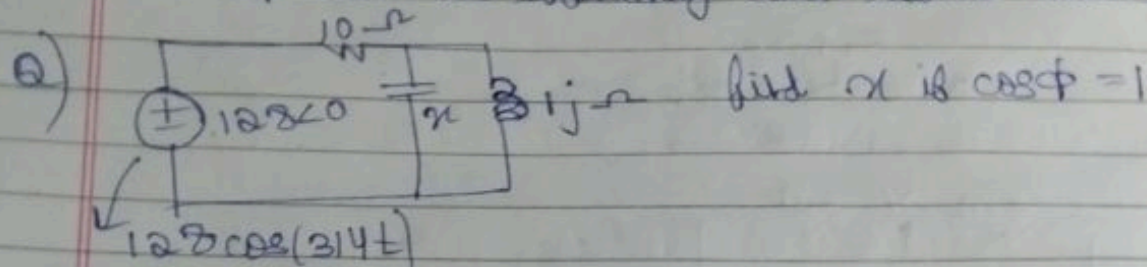



AC (continued)

Power factor correction - technique
 → where capacitor is used to reduce reactive power component of an AC circuit in order to improve its efficiency and reduce current



$$I = \frac{128 \angle 0}{10 + j} = 12.6 \angle -5.7^\circ \text{ A}$$
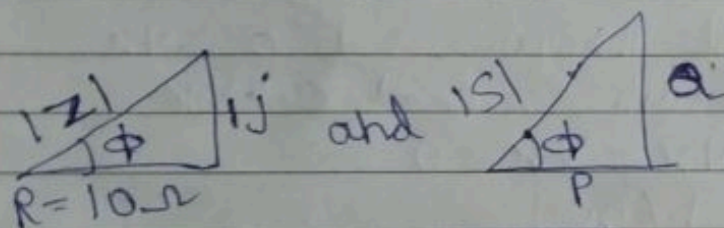
$$S = P_{\text{supp}} = \frac{128 \angle 0}{\sqrt{2}} \times \frac{12.6 \angle -5.7}{\sqrt{2}} \\ = 802.49 + j 80.09 \text{ } \{P + Qi\}$$



(b) $\cos \phi = 1 \rightarrow \boxed{\phi = 0}$

$$\text{Power capacitor} = I_{\text{rms}}^2 \times X_c = \frac{V_{\text{rms}}^2}{X_c} = S_c$$

~~For~~ $\phi = 0 \rightarrow S_c = 0$


$$80.09 = \left(\frac{128}{\sqrt{2}} \right)^2$$

$$\frac{1}{\omega C}$$

314 μF given?

so $\boxed{C = 31.1 \mu\text{F}}$ (ans)

so $\boxed{X_c = 101.03}$

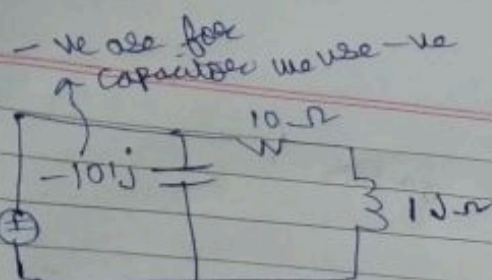


$$20 \angle 0^\circ \rightarrow 10.01 + 0j$$

$$20 \angle 0^\circ = 12.8 \angle 0^\circ$$

$$S_{\text{new}} = \frac{128 \angle 0^\circ}{\sqrt{2}} \times \frac{12.8 \angle 0^\circ}{\sqrt{2}} = 819.2 + 0j$$

Q)

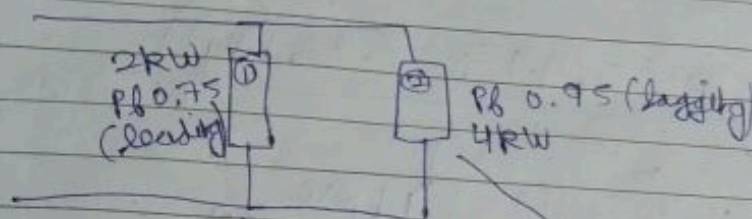

ans)

ϕ_1 $Q = ?$

$P = 2000W$
 $\cos \phi_1 = 0.75 \text{ (leading)}$
 $\phi_1 = 41.41^\circ$
 $Q_1 = 2000 \tan 41.41^\circ$
 $= -1763.85 \text{ VAR}$

ϕ_2 $Q = ?$

$+1314.3 \text{ VAR}$

$\cos \phi_2 = 0.95$
 $\phi_2 = 18.19^\circ \text{ (lag)}$
 $\tan \phi_2 = \frac{Q_2}{4000}$
 $Q_2 = 1314.3 \text{ VAR}$

how lagging power factor means its a inductor
 and leading power factor means its a capacitor

V V V imp


for inductor $\rightarrow Q$ is +ve
 for capacitor $\rightarrow Q$ is -ve

$$20 \ S = (2000 + 4000) + j(1314.3 - 1763.85)$$

$$= 6000 - 449.5j$$

\downarrow \downarrow
 W VAR

for total power factor \rightarrow

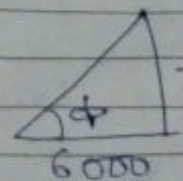


$$\tan \phi = \frac{-449.5}{6000}$$

$$\phi = 4.283^\circ \text{ (leading) (as } \phi \rightarrow -ve \text{)}$$

{ we can ignore sign }


$$\cos \phi = 0.997 \text{ (leading)}$$

a)

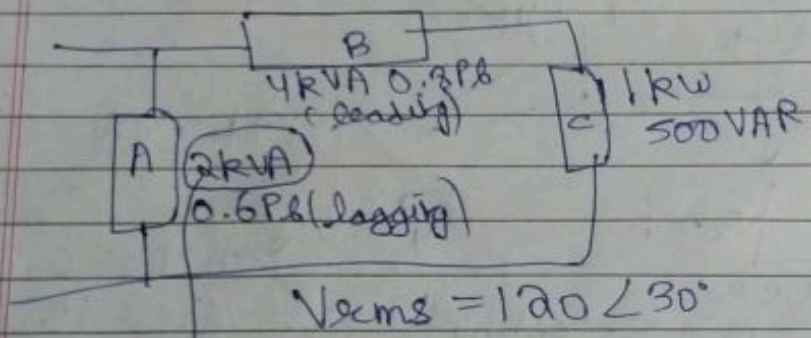


indicates hypotenuse $|S|$ of ϕ triangle

ans)

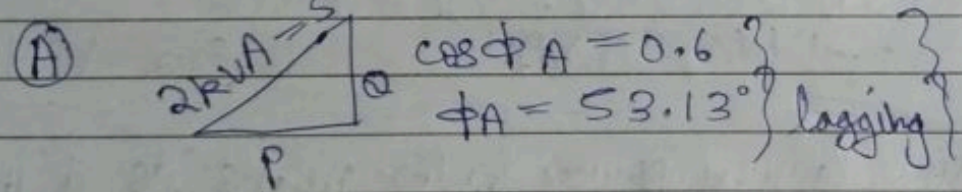

$$P = S \cos \phi_A, \quad Q = S \sin \phi_A$$
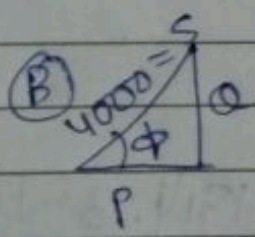
$$P = 1200 \text{ W} \quad Q = +1600 \text{ VAR} \quad \left. \begin{array}{l} +ve \text{ as} \\ \text{lagging} \end{array} \right\}$$



$$\cos \phi = 0.8 \quad \left. \begin{array}{l} \text{leading} \\ \phi = 36.86^\circ \end{array} \right\}$$

$$P = 4000 \cos \phi, \quad Q = 4000 \sin \phi$$

$$P = 3200 \text{ W} \quad Q = -2400 \text{ VAR}$$





{ -ve as leading }

$P = 1 \text{ kW}$
 $Q = 500 \text{ VAR} \leftarrow \text{C}$

$$S_{\text{tot}} = (3200 + 1000 + 1200) + j(500 + 1600 - 2400) \\ = 5400 - 300j$$

$$I_{\text{rms}} = \frac{5400 - 300j}{120 \angle 30} = 45.06 \angle -33.18^\circ \text{ A}$$
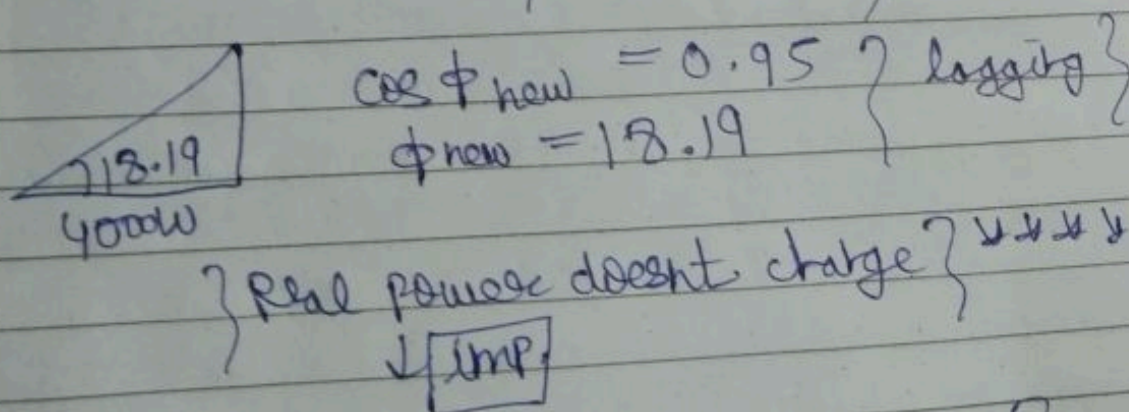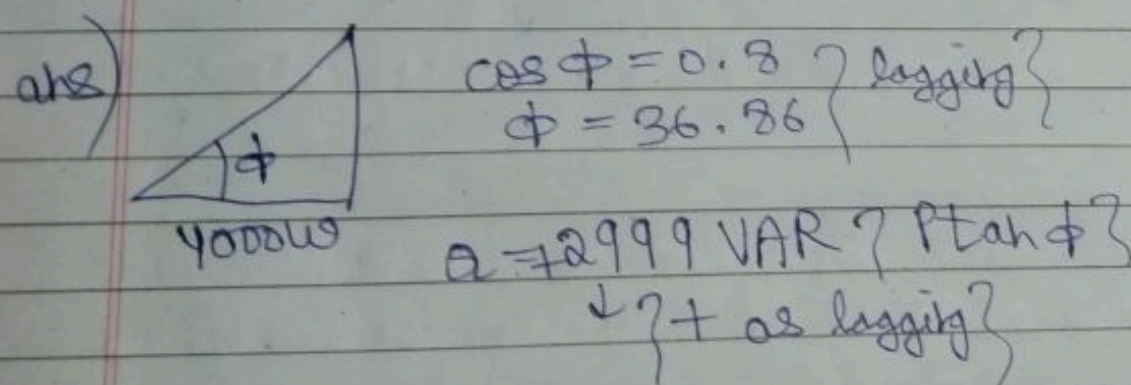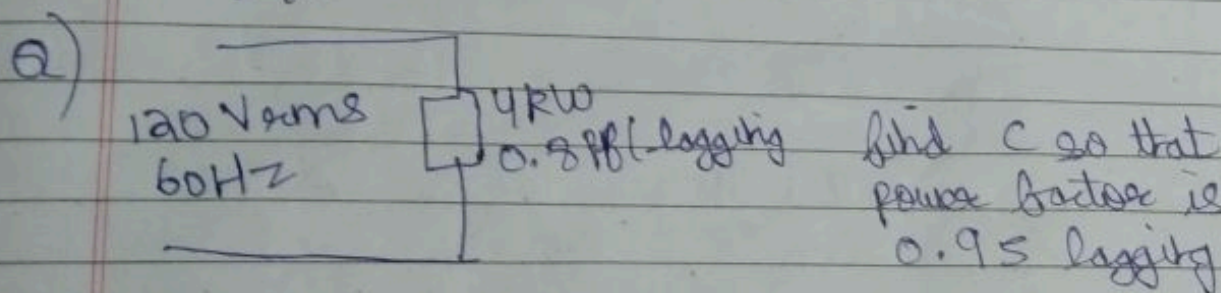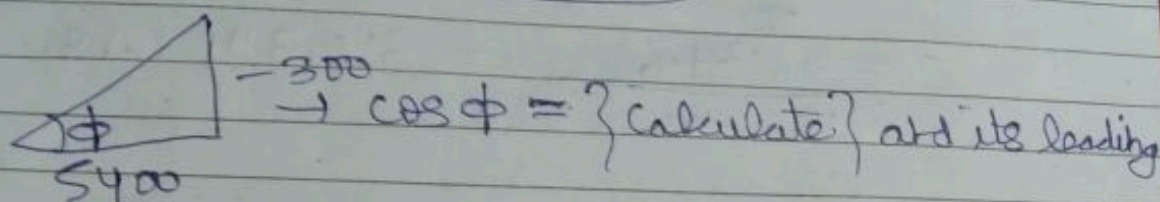
$$I_{\text{rms}} = 45.06 \angle 33.18^\circ \text{ A}$$



$$Q_{\text{new}} = +1314.3 \{ + \text{ as lagging} \}$$

$$Q_c = 2999 - 1314.3$$
$$= +1684.6 \text{ VAR}$$

$$I_{\text{rms}}^2 X_c = \frac{V_{\text{rms}}^2}{X_c}$$



$$\frac{V_{\text{rms}}^2}{\frac{1}{\omega C}} = 1684.6$$



$$C = \frac{1684.6}{120^2 \times 2\pi \times 60} = 310.3 \mu\text{F (ans)}$$

Three phase Systems

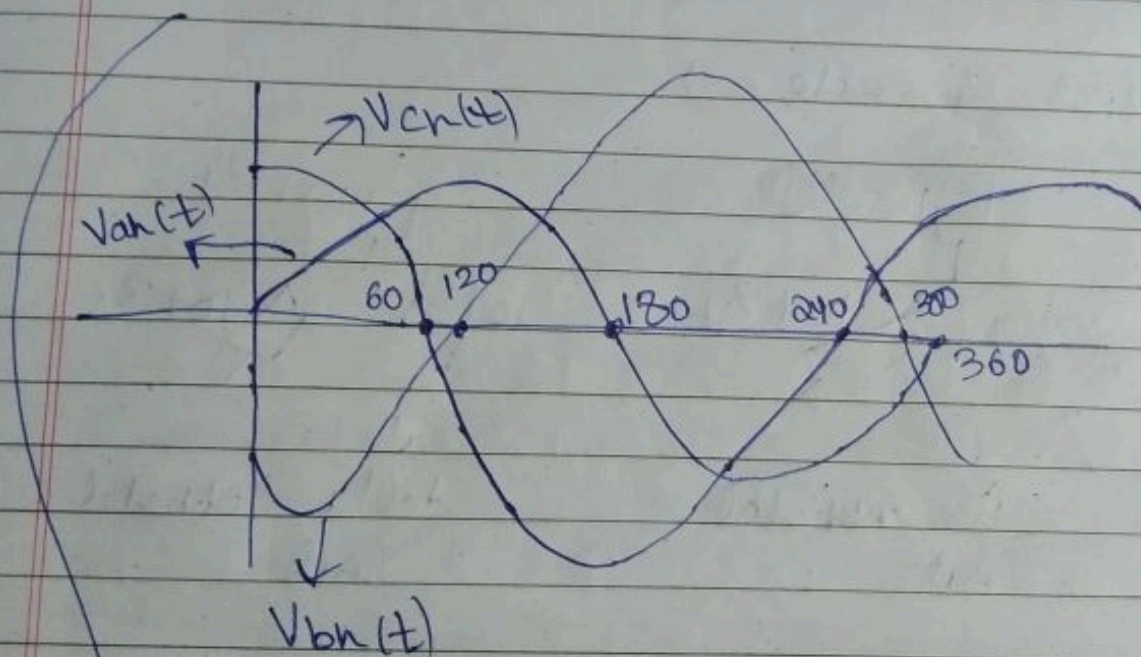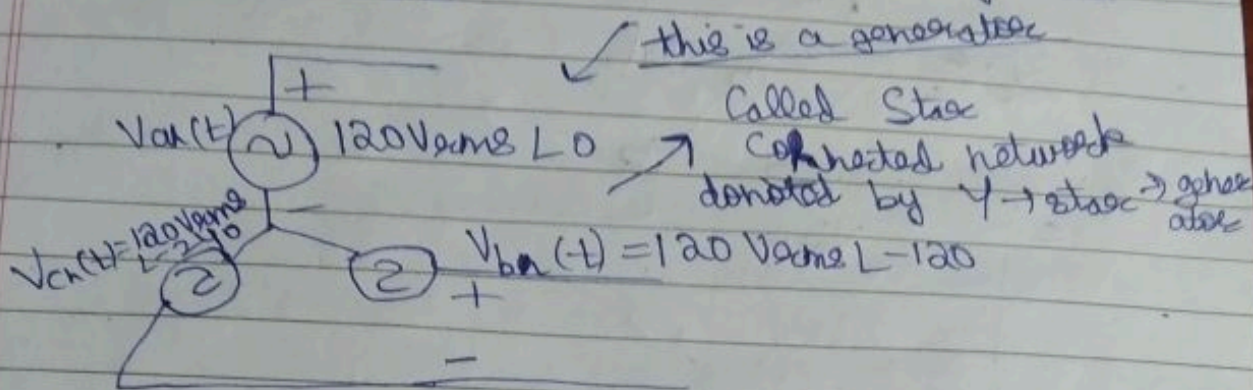drawback of single phase \rightarrow ① cant connect lots of loads to it ② power is oscillatory and varies w.r.t time




reference $\rightarrow \cos(2\pi \times 50 t)$

$$V_{an}(t) = 120\sqrt{2} \cos(2\pi \times 50 t)$$



$$V_{bn}(t) = 120\sqrt{2} \cos(2\pi \times 50 t - 120)$$

$$V_{cn}(t) = 120\sqrt{2} \cos(2\pi \times 50 t - 240)$$

Delta connected network

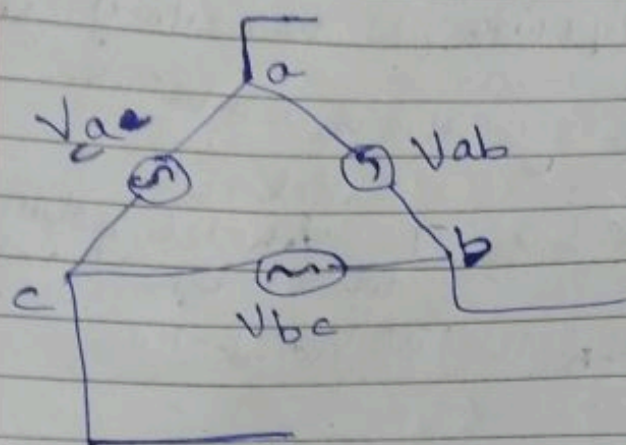

types of loads \rightarrow

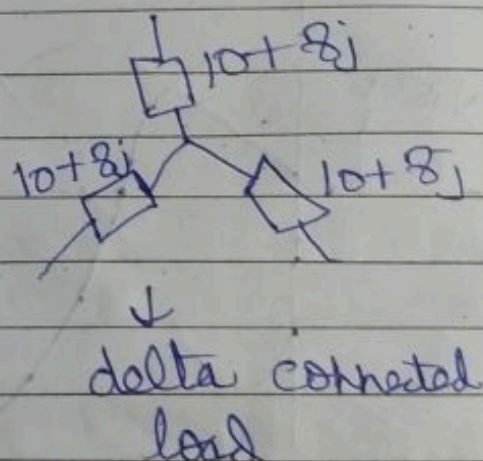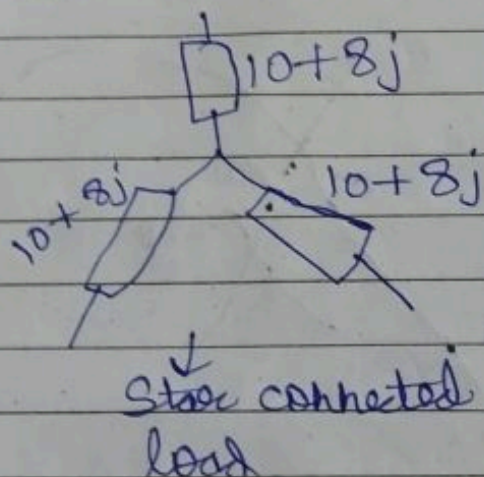


If balanced system \rightarrow all loads are of same value and voltage source phase differs by 120°


only balanced system is in syllabus for us.

Star network can have delta and star load. Same with delta network

voltage in 1 phase

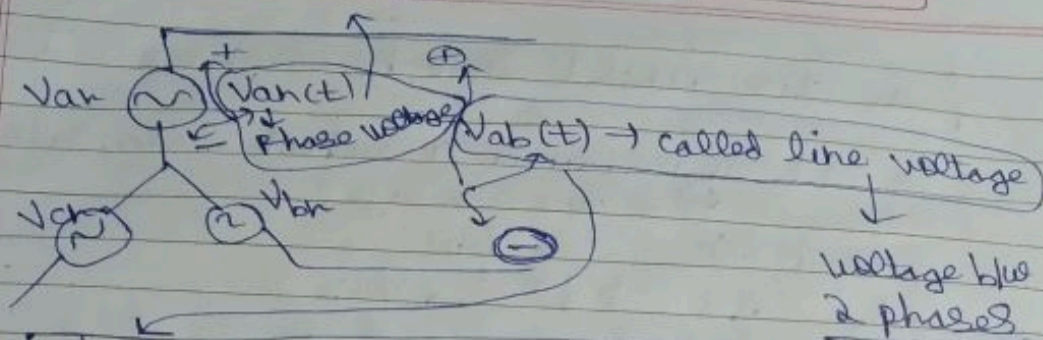

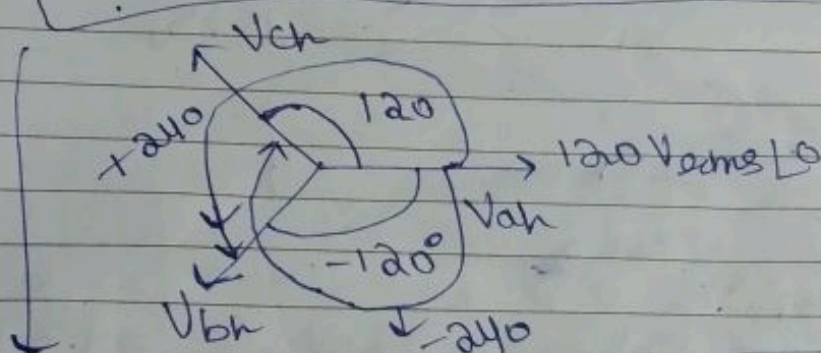
$$\begin{aligned} V_{ab}(t) &= V_{an}(t) - V_{bn}(t) \\ V_{ab} &= V_{an} - V_{bn} \\ &= 120 \text{ Vrms} \angle 0 - 120 \text{ Vrms} \angle -120 \\ &= 120\sqrt{3} \angle 30 \end{aligned}$$



similarly



$$\begin{aligned} V_{bc} &= 120 \angle -120 - 120 \angle -240 \\ &= 120\sqrt{3} \angle -90 \\ V_{ca} &= 120 \angle -240 - 120 \angle 0 \\ &= 120\sqrt{3} \angle 150 \end{aligned}$$

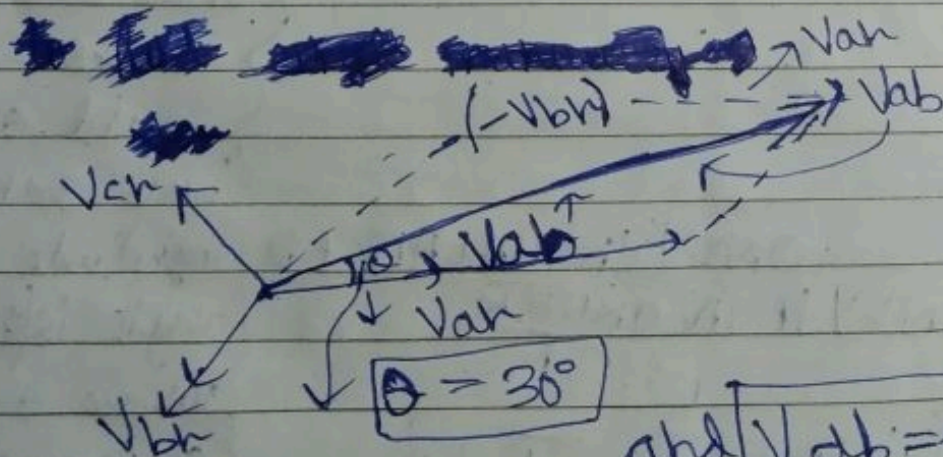We can say \rightarrow line voltage is scaled by $\sqrt{3}$ of phase voltage and some angle.



and $V_{ab} = V_{rms} \times \sqrt{3}$

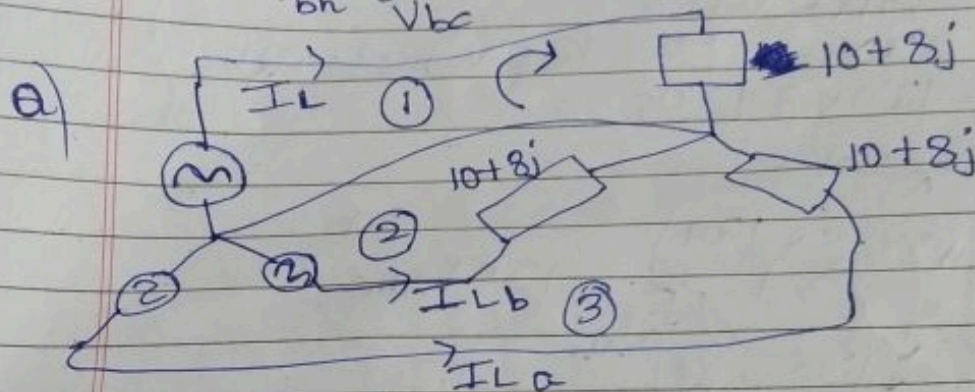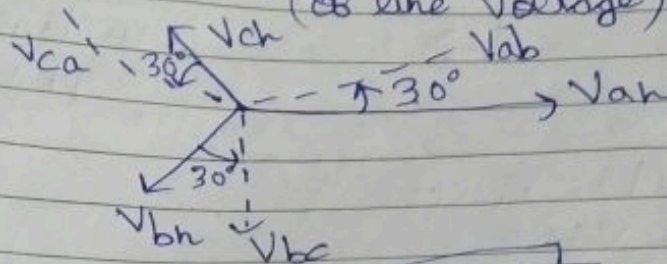In star connected network $I_{\text{phase}} = I_{\text{line}}$
 to find angle manually without calculator
 (of line voltage)



Ans) in loop ①

$$I_L = I_{\text{phase}} = \frac{120V_{\text{rms}} \angle 0}{10 + 8j} = 9.37 \angle -38.6$$

in loop ②

$$I_{Lb} = \frac{120V_{\text{rms}} \angle -120}{10 + 8j} = 9.37 \angle -158.6$$

$$I_{La} = \frac{120 \angle -240}{10 + 8j} = 9.37 \angle -278.6$$


ONLY IN BALANCED
 AND ONLY IF IN ORDER

meaning I_a, I_b, I_c


if you find
 one current
 others can be
 found as they
 have same
 magnitude and
 angle is $(\theta - 120)$
 where θ is angle
 of previous current

Extra Note
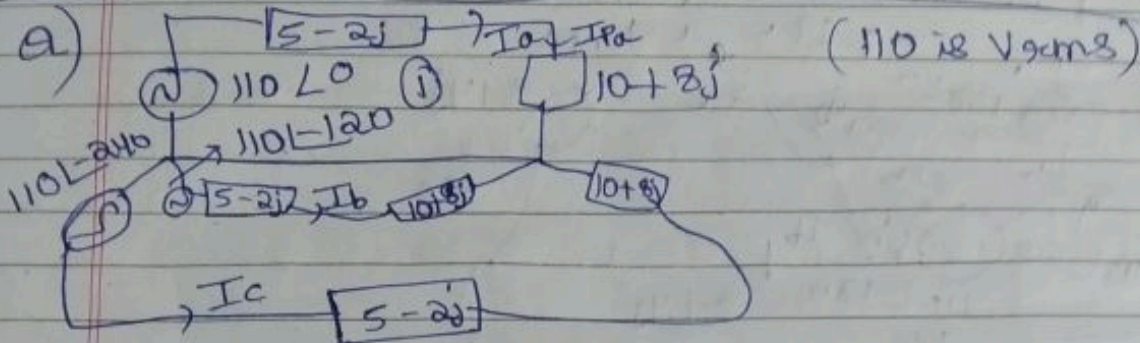
$$\begin{aligned} & \begin{array}{c} \nearrow xL0 \\ xL-240 \quad \searrow xL-120 \end{array} \rightarrow \text{resultant} = xL0 + xL-120 + xL-240 \\ & = 0 \text{ (always).} \end{aligned}$$


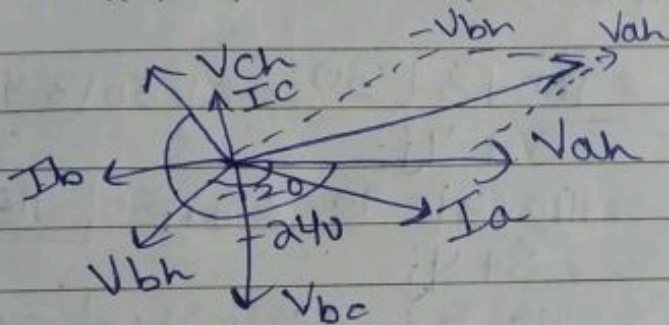
$$\begin{aligned} V_{an}(t) &= 110\sqrt{2} \cos(\omega t - 0) \\ V_{bn}(t) &= 110\sqrt{2} \cos(\omega t - 120) \\ V_{cn}(t) &= 110\sqrt{2} \cos(\omega t - 240) \end{aligned}$$



$$\begin{aligned} V_{ab \text{ rms}} &= V_{an \text{ rms}} - V_{bn \text{ rms}} = 110\sqrt{3} \angle 30^\circ \\ V_{bc \text{ rms}} &= V_{bn \text{ rms}} - V_{cn \text{ rms}} = 110\sqrt{3} \angle -90^\circ \\ V_{ca \text{ rms}} &= V_{cn \text{ rms}} - V_{an \text{ rms}} = 110\sqrt{3} \angle -210^\circ \end{aligned}$$

I_a in loop ① \rightarrow

$$I_{a \text{ rms}} = \frac{110 \angle 0}{15 + 6j} = 6.80 \angle -21.80$$

$$I_{b \text{ rms}} = \frac{110 \angle -120}{15 + 6j} = 6.80 \angle -141.80$$


$$I_{c \text{ rms}} = \frac{110 \angle -240}{15 + 6j} = 6.80 \angle -261.80$$

$$I_{line} = I_{phase}$$

$$I_{pa} = 6.8 \angle -21.80$$

$$I_{pb} = 6.8 \angle -141.80$$

$$I_{pc} = 6.8 \angle -261.80$$

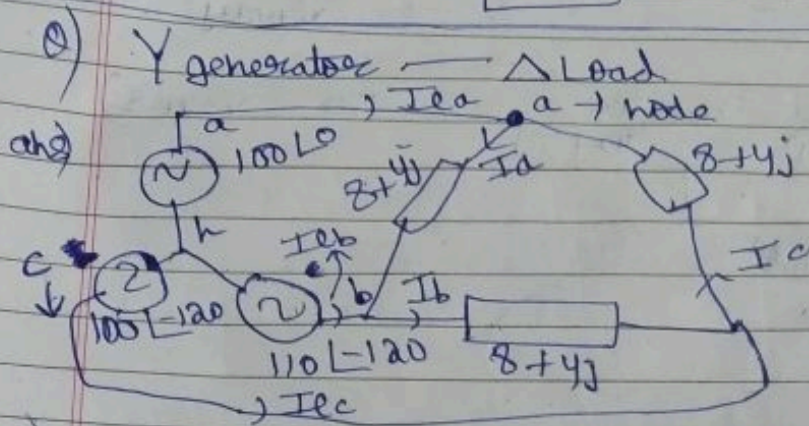

ans)

$$V_{ab} = 100\sqrt{3} \angle 30^\circ$$

$$V_{bc} = 100\sqrt{3} \angle -90^\circ$$

$$V_{ca} = 100\sqrt{3} \angle -210^\circ$$

$$I_a = \frac{V_{ab}}{Z} = \frac{100\sqrt{3} \angle 30^\circ}{8+j4} = 21.30 \angle 3.43$$

$$I_b = \frac{V_{bc}}{Z} = \frac{110\sqrt{3} \angle -90^\circ}{8+j4} = 21.30 \angle -116.57$$

$$I_c = \frac{V_{ca}}{Z} = \frac{110\sqrt{3} \angle -210^\circ}{8+j4} = 21.30 \angle -236.57$$



Same -120°
trend follows
here


at node a

use KCL $\rightarrow I_{La} + I_c = I_a$

$$I_{La} = I_a - I_c$$


$$I_{La} = 36.89 \angle -26.53$$

$$= 21.30\sqrt{3} \angle -26.53$$

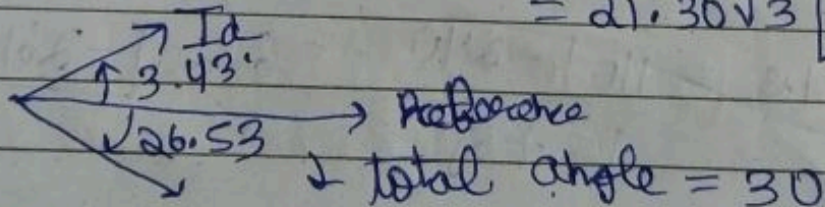


similarly $I_{Lb} = I_b - I_a = 36.89 \angle -146.53$
 $I_{Lc} = I_c - I_b = 36.89 \angle -266.53$

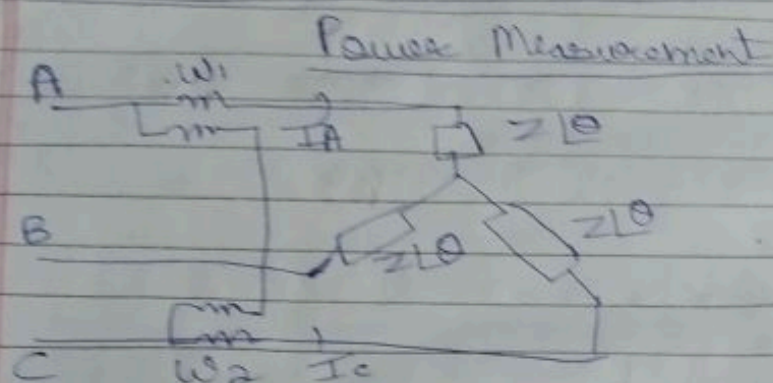So in delta
 $V_{line} = V_{phase}$
 $I_L = I_p \sqrt{3} \angle -30$
 in star
 $I_L = I_{ph}$
 $V_L = V_{ph} \sqrt{3} \angle 30$



$\uparrow V_{AB}, I_A$ $W_1, W_2 \rightarrow$ Wattmeters.

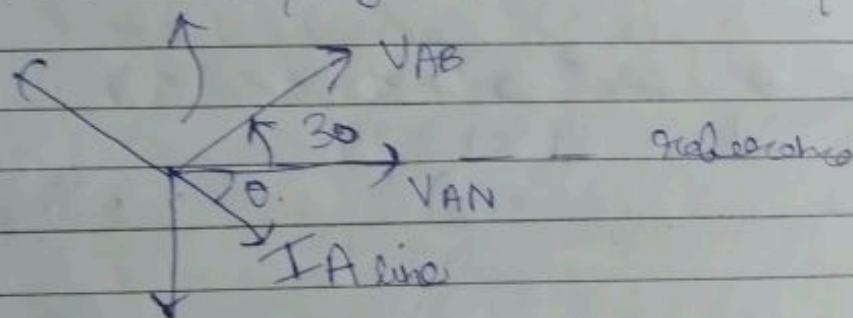
W_1 reading $\rightarrow P_1 = V I \cos \phi$
 $= V_{line} \times I_{line} \cos \phi$
 $\phi = 30 + \theta$ { angle b/w V_L and I_L }



So $P_1 = V_L I_L \cos(30 + \theta)$

$\uparrow V_{CB}, I_c$

W_2 reading \rightarrow

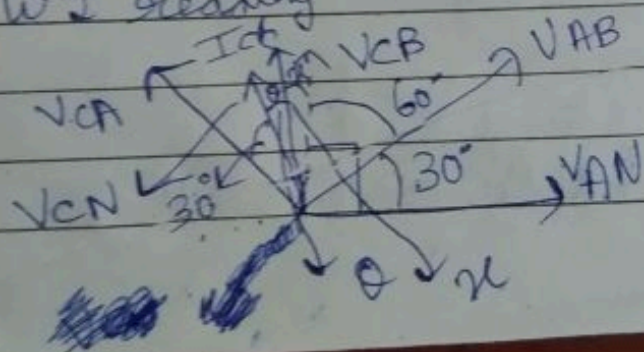

So $\alpha = 30 - \theta$

$$20 \quad P_1 + P_2 = \sqrt{3} V_L I_L [\cos(30+\theta) + \cos(30-\theta)]$$

$$P_{3\text{phase}} = \sqrt{3} V_L I_L \cos \theta$$

~~Star~~ $\rightarrow V_{ph} = \frac{V_{line}}{\sqrt{3}}, I_{ph} = I_L$

$$P_{3\text{phase}} = \sqrt{3} V_L I_L \cos \theta$$

$\Delta \rightarrow V_{ph} = V_L, I_{ph} = \frac{I_L}{\sqrt{3}}$

$$P_{3\text{phase}} = \sqrt{3} V_L I_L \cos \theta$$

$$P_{3\text{phase}} = 3 V_{ph} I_{ph} \cos \theta$$

total reactive power $\rightarrow Q_{3\text{phase}} = \sqrt{3} V_L I_L \sin \theta$

$$20 \quad \left[\theta = \tan^{-1} \frac{Q}{P} = \tan^{-1} \left(\frac{\sqrt{3}(P_2 - P_1)}{P_2 + P_1} \right) \right]$$

$$Q_{3\text{phase}} = (P_2 - P_1) \times \sqrt{3} = \sqrt{3} V_L I_L \sin \theta$$

Q) $\lambda - \lambda, V_L = 197 \text{ V}$ (Vrms)
 $Z = 51 \angle 22^\circ$ per phase

ans)

$$P_1 = V_L I_L \cos(\theta + 30^\circ)$$

$$|I_L| = \frac{V_{ph}}{Z} = \frac{197}{\frac{51}{\sqrt{3}}} = 2.23 \text{ A}$$

$$P_1 = 197 \times 2.23 \times \cos(22 + 30)$$

$$P_1 = 270 \text{ W}$$

$$P_2 = 197 \times 2.23 \cos(8)$$

$$= 435 \text{ W}$$

$$20 \quad P_{3\text{phase}} = 705 \text{ W}$$

$$Q_{3\text{phase}} = \sqrt{3}(P_2 - P_1) = 285 \text{ VAR}$$

$$\phi = \tan^{-1} \left(\frac{285}{705} \right) = 22^\circ$$

$$\text{so } \cos \phi = 0.927$$

or ϕ = angle of
of impedance
so $\phi = 22^\circ$
 $\cos 22 = 0.927$

Q) $V_L = 208V$
 $P_1 = -560W$ $f = 50Hz$
 $P_2 = 800W$

ans) $P_{3\text{phase}} = 240W$
 $Q_{3\text{phase}} = \sqrt{3} (P_2 - P_1) = 23.56VAR$
 $\phi = \tan^{-1} \frac{Q}{P} = 84^\circ = 0.96 - 0.28j$

$$\cos \phi = 0.1014$$

$$P_{3\text{phase}} = 240 = 3 (P_{1\text{phase}}) = 80W \times 3$$

$$\text{so } P_{1\text{phase}} = 80$$


$$80 = V_{ph} I_{ph} \cos \phi = 80$$

$$|I_{ph}| = \frac{80}{120 \times 0.1014}$$

$$|I_{ph}| = 6.57A$$

$$I_{ph} = 6.57 \angle 0^\circ - 0^\circ$$

$$= 6.57 \angle -84^\circ$$

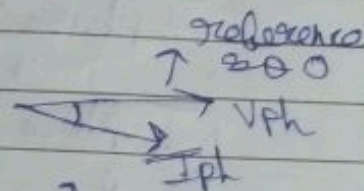

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{120}{6.57 \angle -84^\circ} = 18.2 \angle 84^\circ$$

(ans)

$$Z_{ph} = 1.9 + j18.1$$


↓ Inductive load

$$\text{so } R + jX_L$$

$$R = 1.9, X_L = 18.1$$

$$\omega L = 18.1 \rightarrow L = \frac{18.1}{100\pi (2\pi \times 50)} \quad (\text{ans})$$

Classification

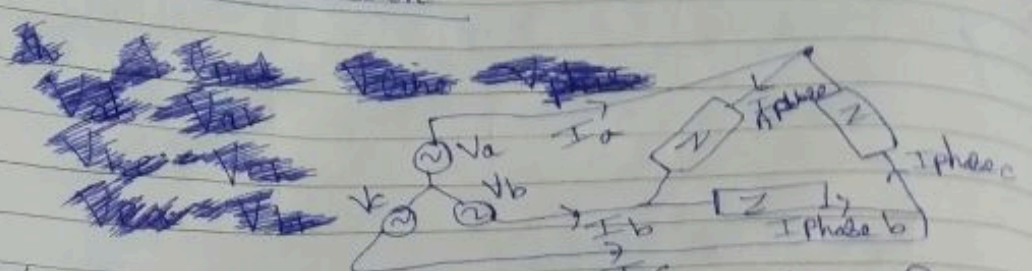


① Y-Δ circuit { Y source, Δ load }

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \times \sqrt{3} \angle 30^\circ = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} \quad \begin{bmatrix} I_{\text{phase a}} \\ I_{\text{phase b}} \\ I_{\text{phase c}} \end{bmatrix}$$

{ Phase voltages } { line voltages } = $\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} \times \frac{1}{\sqrt{3}}$

$$\begin{bmatrix} I_{\text{phase a}} \\ I_{\text{phase b}} \\ I_{\text{phase c}} \end{bmatrix} \times \sqrt{3} \angle -30^\circ = \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

{ Phase current } { line current }

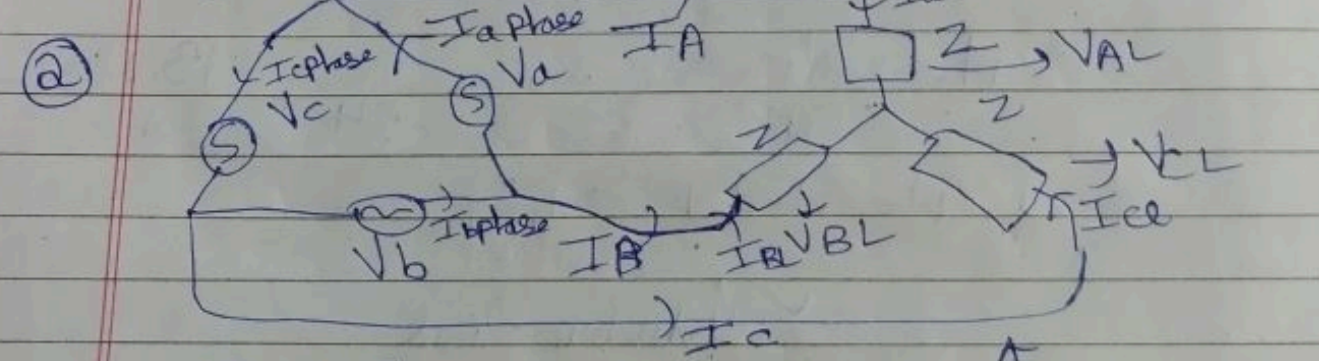

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} \quad \boxed{\text{Delta-Star}}$$

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} \times \frac{1}{\sqrt{3} \angle 30^\circ} = \begin{bmatrix} V_{al} \\ V_{bl} \\ V_{cl} \end{bmatrix}$$

$$\begin{bmatrix} I_{as} \\ I_{bs} \\ I_{cs} \end{bmatrix} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \times \frac{1}{\sqrt{3} \angle -30^\circ}$$


\downarrow phase current \downarrow line current

$\begin{cases} I_{as} = I_{\text{phase a}} \\ I_{bs} = I_{\text{phase b}} \\ I_{cs} = I_{\text{phase c}} \end{cases}$

$$\begin{bmatrix} I_{al} \\ I_{bl} \\ I_{cl} \end{bmatrix} = \begin{bmatrix} V_{al} \\ V_{bl} \\ V_{cl} \end{bmatrix} \times \frac{1}{Z} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

\downarrow line current

③ Stage Stage Circuit

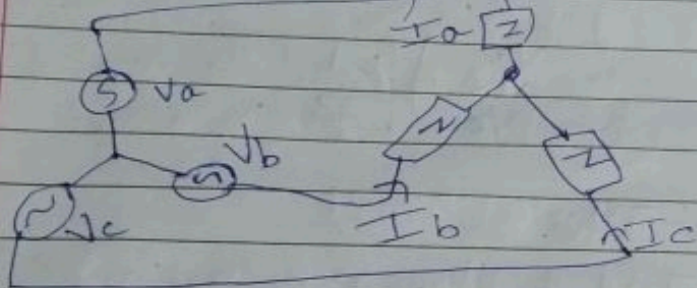

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \times \sqrt{3} \angle 30^\circ = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}$$

\downarrow phase voltage \downarrow line voltage

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \times \frac{1}{Z}$$

\downarrow phase current


Phase current = line current

$$\begin{matrix} I_{La} & I_{Lb} & I_{Lc} \\ \downarrow & \downarrow & \downarrow \\ I_a & I_b & I_c \end{matrix} \quad \left. \vphantom{\begin{matrix} I_{La} \\ I_{Lb} \\ I_{Lc} \end{matrix}} \right\} \text{equal}$$

Phase voltage $\times \sqrt{3} \angle 30^\circ = \text{line voltage}$

④

Delta - Delta Circuit

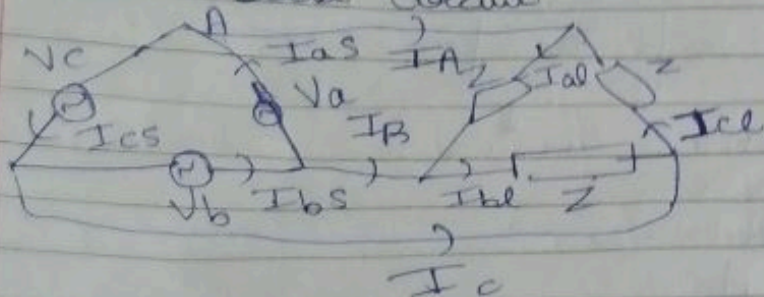

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}$$

\downarrow Phase voltage \downarrow line voltage

$$\begin{bmatrix} I_{al} \\ I_{bl} \\ I_{cl} \end{bmatrix} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \times \frac{1}{Z}$$

$$I_a = I_{al} - I_{cl}$$

$$I_b = I_{bl} - I_{al}$$

$$I_c = I_{cl} - I_{bl}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} I_{al} \\ I_{bl} \\ I_{cl} \end{bmatrix} \times \sqrt{3} \angle -30^\circ$$

\downarrow
line current


$$\begin{bmatrix} I_{as} \\ I_{bs} \\ I_{cs} \end{bmatrix} = \begin{bmatrix} I_{al} \\ I_{bl} \\ I_{cl} \end{bmatrix}$$

\downarrow
Phase current

so $\boxed{\text{phase current} \times \sqrt{3} \angle -30^\circ = \text{line current}}$

$\boxed{\text{phase voltage} = \text{line voltage}}$

Class stuff contd.

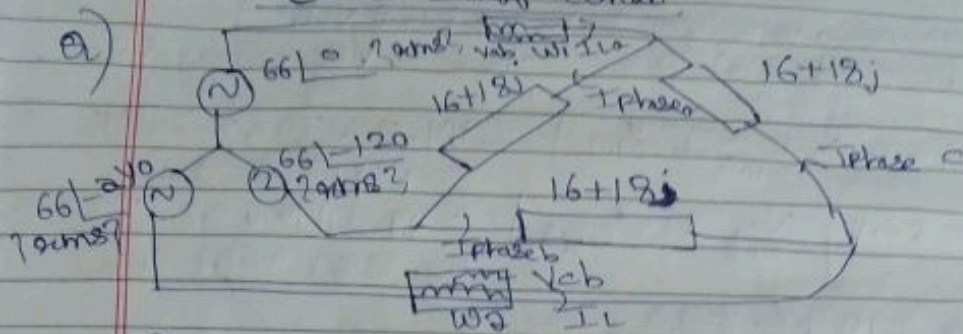

Power

$$S_{3\text{ phase}} = 3 V_{\text{phase}} I_{\text{phase}}$$

Base Y $\rightarrow \sqrt{3} V_L I_L$

Base $\Delta \rightarrow \sqrt{3} V_L I_L$

\rightarrow conjugate

$$W_1 \rightarrow V_{ab} I_{La}$$

$$W_2 \rightarrow V_{cb} I_{Lc}$$

$$W_2 = \text{Real} [V_{ca} I_{Lc}]$$

$$W_1 = \text{Real} [V_{ab} I_{La}]$$

$$P_{3\text{ phase}} = W_1 + W_2, Q_{3\text{ phase}} = \sqrt{3} (W_2 - W_1)$$

$$V_{ab} = 66\sqrt{3} \angle 30^\circ = 114.32 \angle 30^\circ$$

$$V_{bc} = 114.32 \angle -90^\circ$$

$$V_{ca} = 114.32 \angle -210^\circ$$

$$I_{\text{phase a}} = \frac{V_{ab}}{Z} = \frac{114.32 \angle 30^\circ}{16 + 18j} = 4.47 \angle -18.36^\circ$$

$$I_{\text{phase b}} = 4.47 \angle -138.36^\circ$$

$$I_{\text{phase c}} = 4.47 \angle -258.36^\circ$$

$$I_{La} + I_{Lc} = I_{\text{phase a}}$$

$$I_{La} = I_{\text{phase a}} - I_{\text{phase c}} = 8.20 \angle -48.36^\circ$$

$$I_{Lb} = 8.20 \angle -168.36^\circ \text{ A}$$

$$I_{Lc} = 8.20 \angle -288.36^\circ \text{ A}$$

$\omega_2 \rightarrow$ voltage is V_{bc} but we know $V_{cb} \rightarrow$
 $V_{bc} = 114.32 \angle 90^\circ$ } angle of V_{bc} reversed?


$$\omega_1 = \text{Real} \left[\frac{V_{ab}}{90^\circ} I_{a \text{ rms}}^* \right] = 114.32 \angle 30^\circ \times 8.20 \angle 48.36^\circ$$

$$\omega_2 = \text{Real} \left[\frac{V_{ca}}{90^\circ} I_{c \text{ rms}}^* \right] = 114.32 \angle 90^\circ \times 8.20 \angle 288.36^\circ$$

$$P_{3\text{ phase}} = 1078.83 \text{ W}$$

$$Q_{3\text{ phase}} = 1213.4 \text{ VAR}$$

Checking power triangle \rightarrow

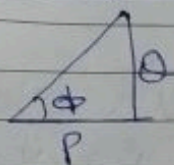

$$\tan \phi = \frac{Q}{P}$$

$$\phi = 48.36^\circ$$

$$\cos \phi = 0.67$$



} lagging as inductive

$$16 + 18j = 24.08 \angle 48.36^\circ$$

which matches phase angle we got.

Mutually coupled

Circuits

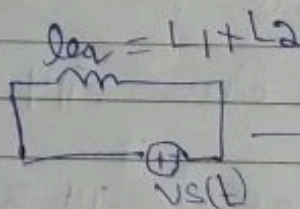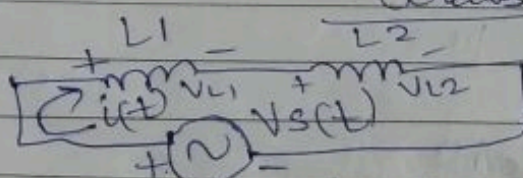

$$V_S(t) = V_{L1} + V_{L2} \quad \text{active = passive}$$


$$V_{L1}(t) = L_1 \frac{di}{dt}, \quad V_{L2} = L_2 \frac{di}{dt}$$

$$V_S(t) = (L_1 + L_2) \frac{di}{dt}$$



$$V_{L1}(t) = L_1 \frac{di}{dt} = N \frac{d\phi}{di} \frac{di}{dt}$$
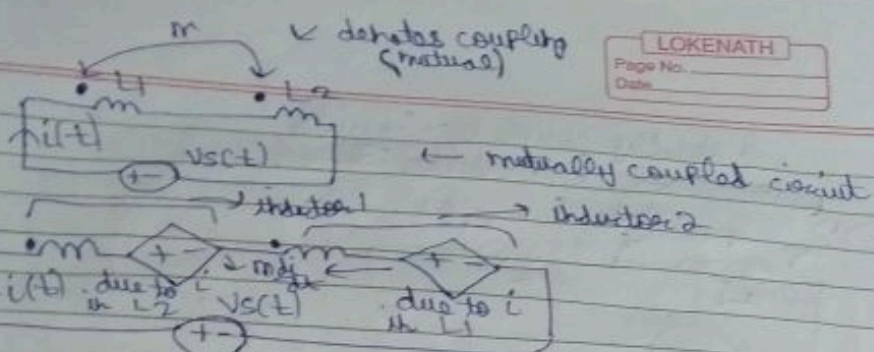
$$\text{so } V(t) = N \frac{d\phi}{di} \frac{di}{dt}$$




in mutually coupled \rightarrow when current passes through one inductor voltage is produced in other inductor

dot convention \rightarrow when current enters dotted terminal other (next) is positive

$$V(t) = L_1 \frac{di}{dt} + m \frac{di}{dt} + L_2 \frac{di}{dt} + m \frac{di}{dt}$$

$$= (L_1 + L_2 + 2m) \frac{di}{dt}$$

dot other example

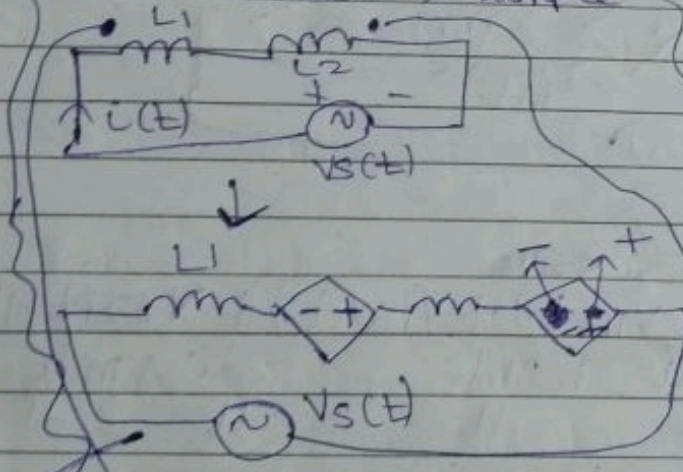

current enters this dot so other dot is +

current leaves this dot so other dot is -

in this

$$V_s(t) = (L_1 + L_2 - 2m) \frac{di}{dt}$$