

## Module 2 : AC Circuits

6 Hrs

Alternating voltages and currents, RMS, average, form factor, peak factor; Single phase RL, RC, RLC series and parallel circuits; Power and power factor; **Balanced three phase systems**



### Course Outcome

- Evaluate AC circuit parameters using laws




# Poly-phase system




- Single phase - two wire system
- Poly phase - same frequency but different phases
- Two phase – same frequency and the phase angle difference between the phases are  $90^\circ$
- Three phase -same frequency and the phase angle difference between the phases are  $120^\circ$

# Different supply systems

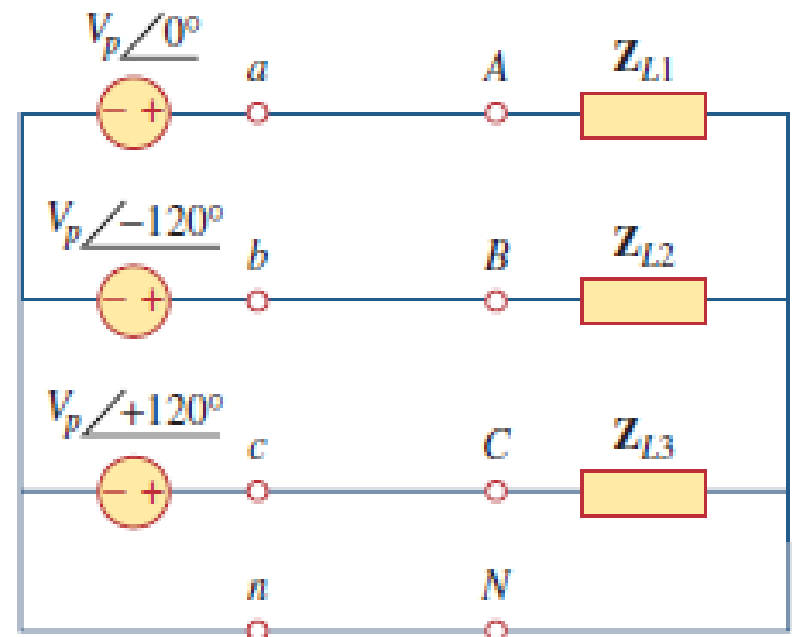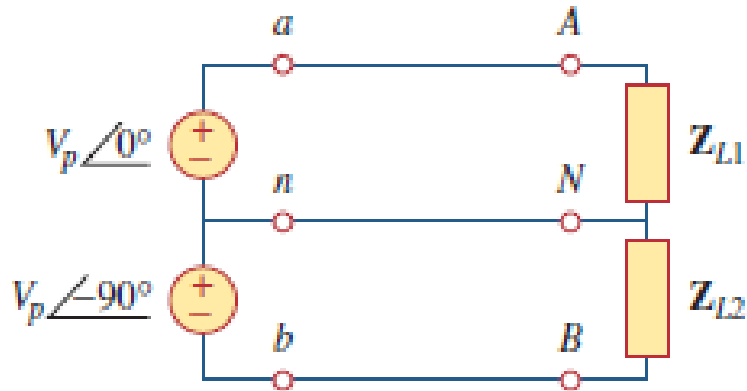

# Different supply systems

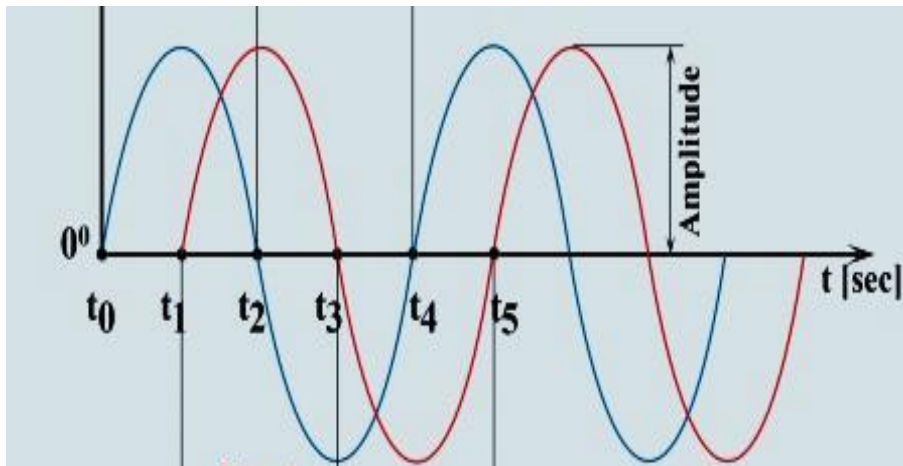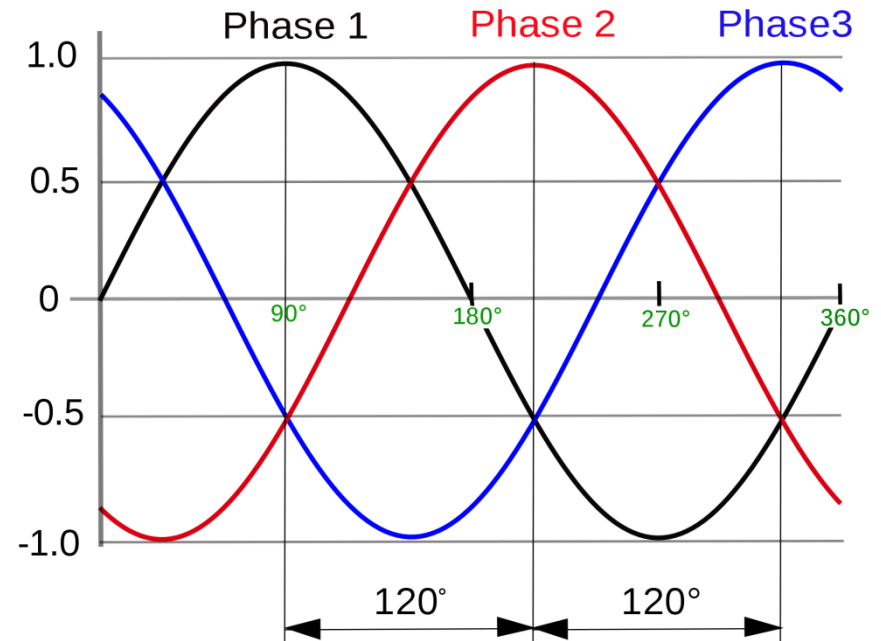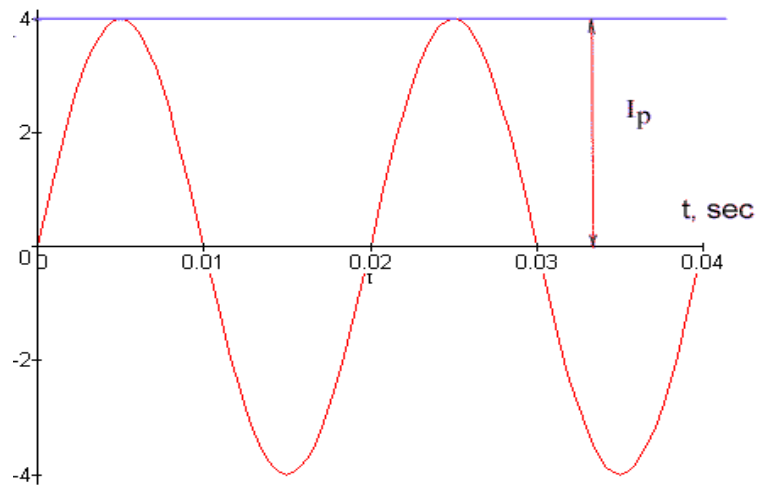

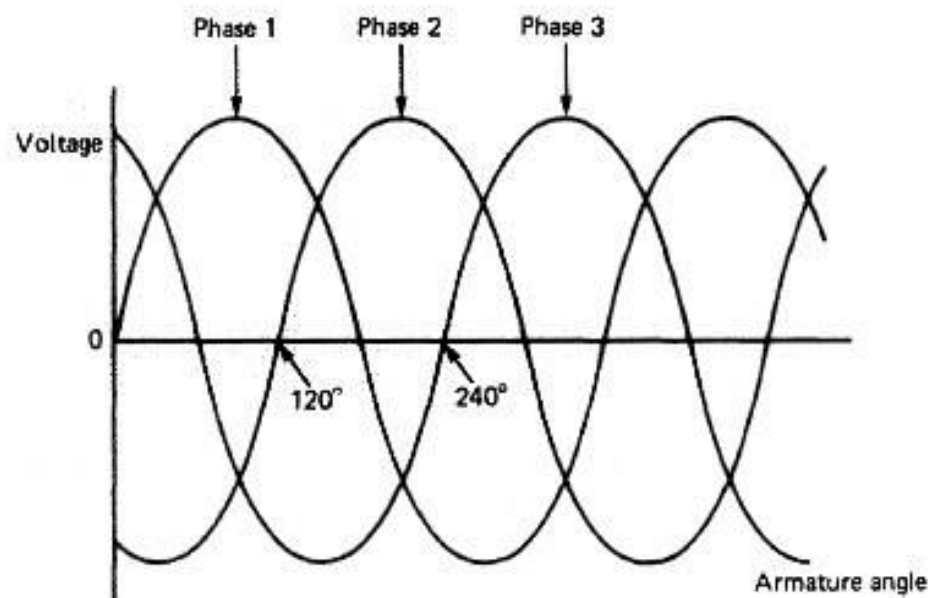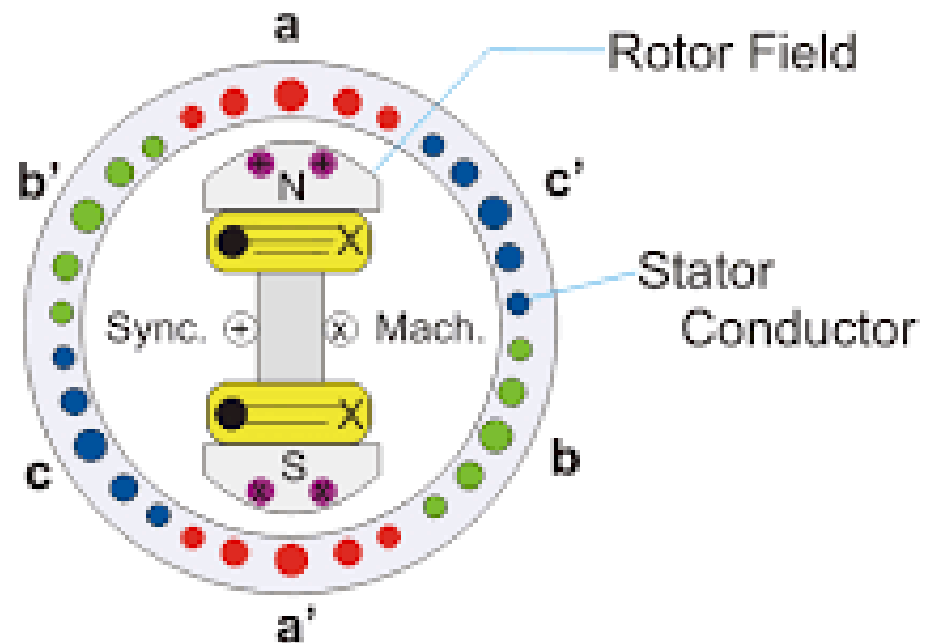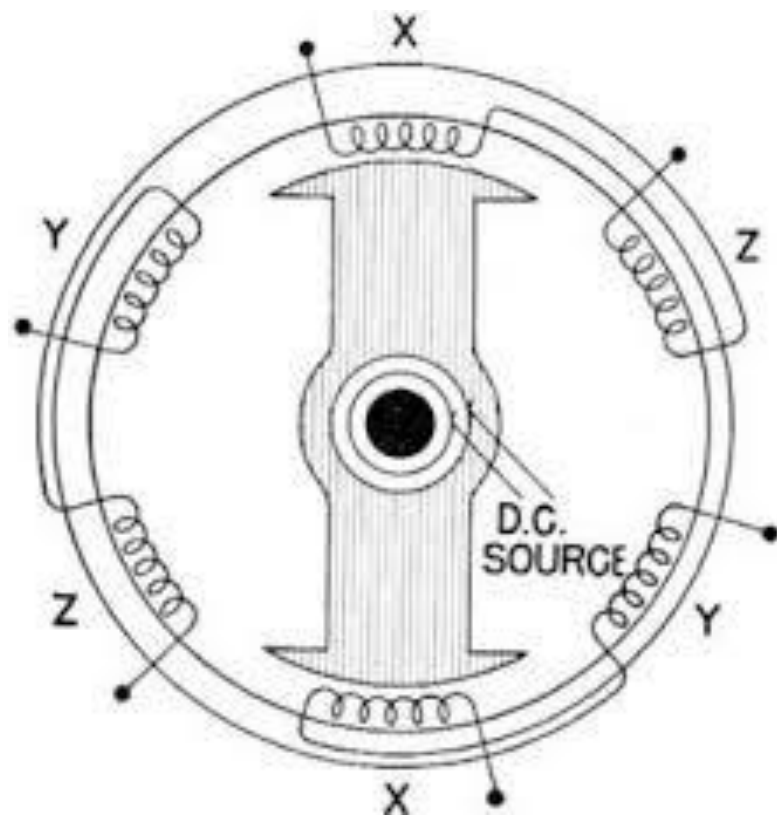

# Three Phase Systems

## Advantages of three phase system

- Three phase power distribution requires lesser amount of copper or aluminium for transferring the same amount of power.
- 3 phase alternator or electrical machines occupy less space and less cost compared to single phase machine having same rating.
- Three phase system gives steady output.
- 3 phase motors will have uniform torque whereas single phase motors will have pulsating torque.


# Three phase connections

## Star (wye) connection (Y)


- Three similar ends of the three phase coils are joined together to form a common point called star point or neutral point.
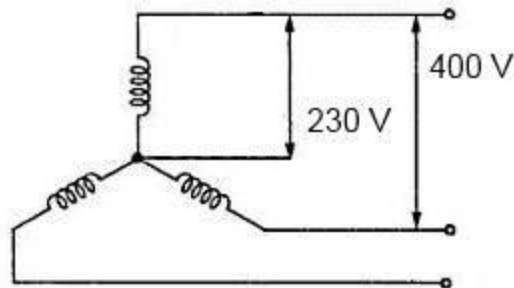
## Delta (mesh) connection ( $\Delta$ )

- Dissimilar ends of the three phase coils are connected together to form a mesh. Wires are drawn from each junction for connecting load.




Star Connection

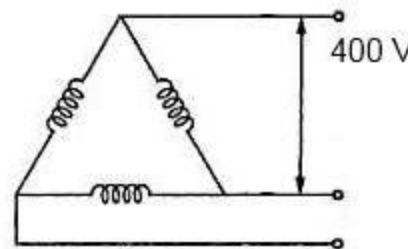

Delta Connection

# Three phase voltage sources

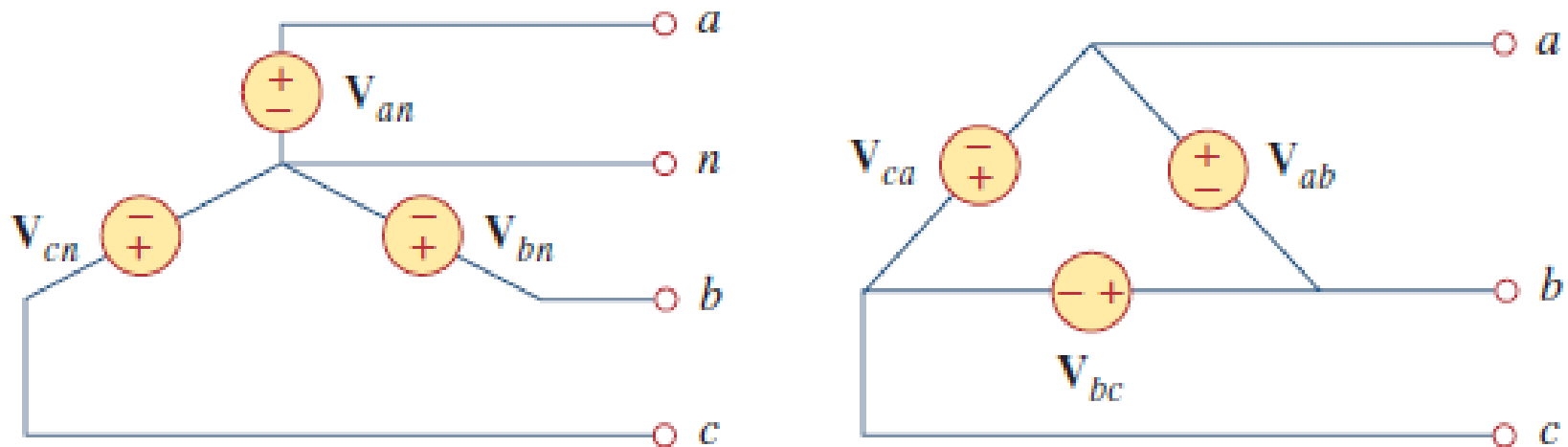


## Balanced system

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$



# Positive phase sequence

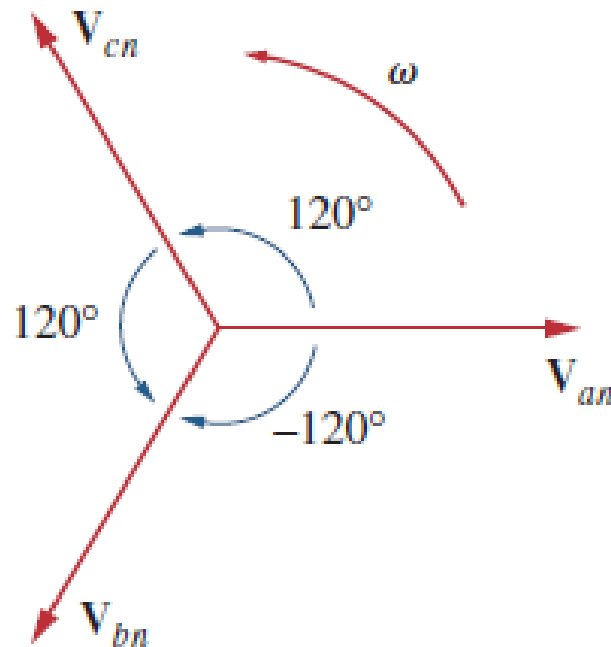


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

# Negative phase sequence


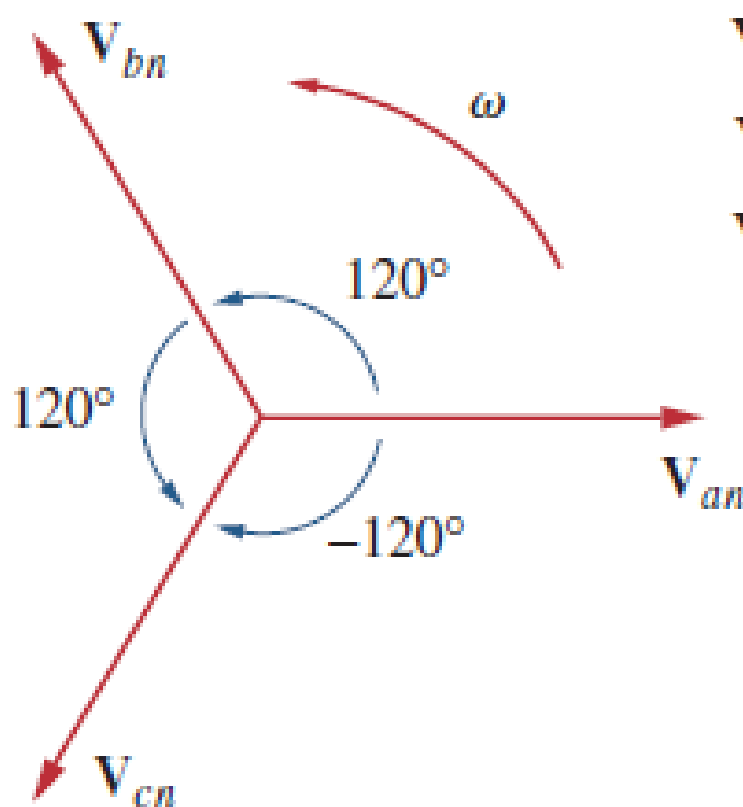


$$V_{an} = V_P \angle 0^\circ$$

$$V_{cn} = V_P \angle -120^\circ$$

$$V_{bn} = V_P \angle -240^\circ = V_P \angle +120^\circ$$

# Three phase load configurations

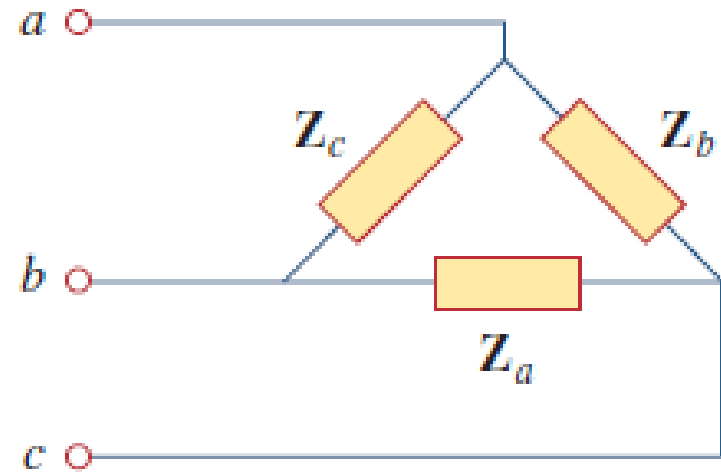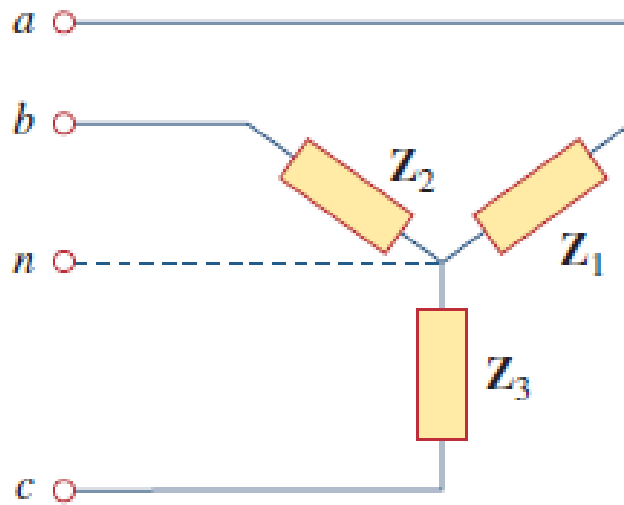

For a balanced star connected load

$$Z_1 = Z_2 = Z_3 = Z_Y$$

For a balanced delta connected load

$$Z_a = Z_b = Z_c = Z_{\Delta}$$

# Identify the type of 3-phase connection





# Identify the type of 3-phase connection



# Balanced three phase systems
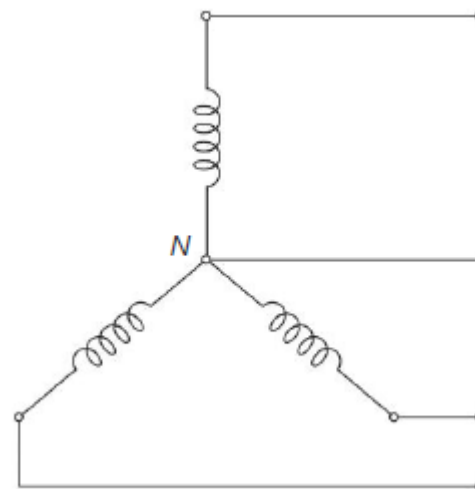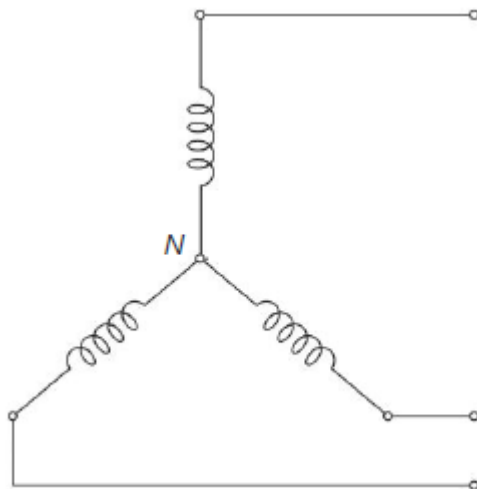
## Star (wye) connection (Y)

- Three wire system
- Four wire system
- The phase angle difference between each phase is  $120^\circ$
- All the three phase voltages have the same amplitude, same period and frequency.



# Voltage and current relationship

$E_R, E_Y, E_B$  : Phase voltages of  $R, Y$  and  $B$  phases

$I_R, I_Y, I_B$  : Phase currents

$V_{RY}, V_{YB}, V_{BR}$  : Line voltages

$I_{L1}, I_{L2}, I_{L3}$  : Line currents


In a balanced system,

$$E_R = E_Y = E_B = E_P$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

$$I_R = I_Y = I_B = I_P$$

$$I_{L1} = I_{L2} = I_{L3} = I_L$$

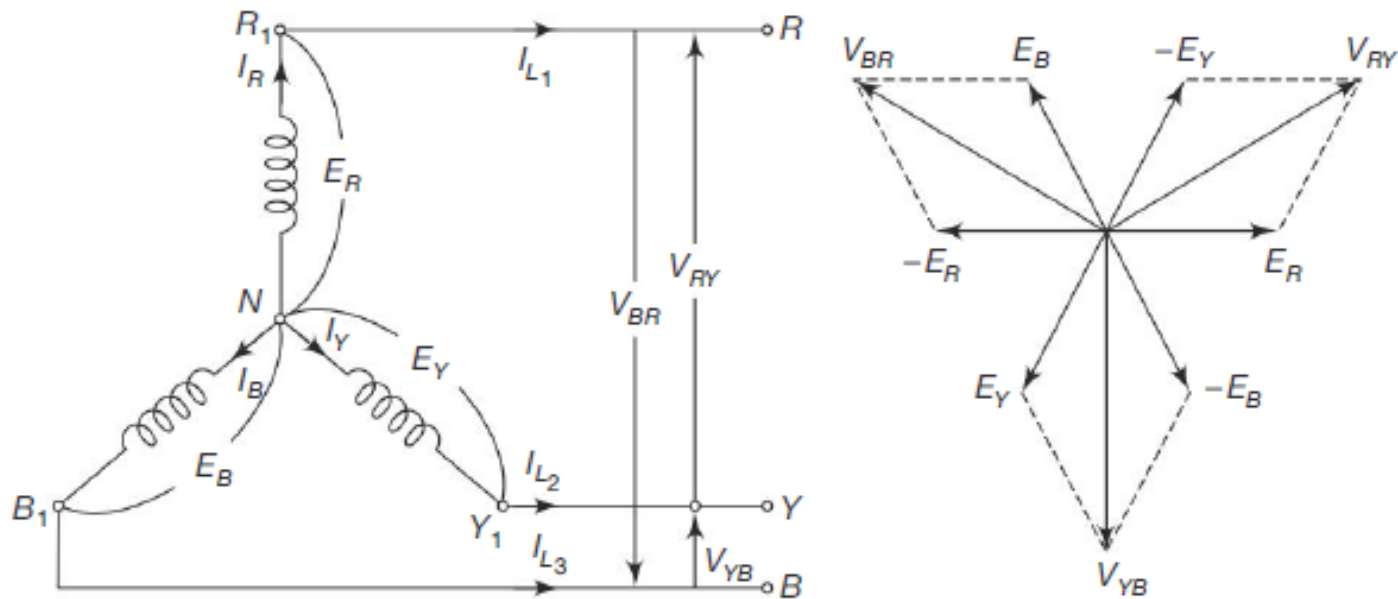

**Current Relationship** Applying Kirchhoff's current law at nodes  $R_1, Y_1, B_1$  we get  $I_R = I_{L1}$ ;  $I_Y = I_{L2}$ ;  $I_B = I_{L3}$ .

This means that in a balanced star connected system, phase current equals the line current

$$I_P = I_L.$$

**Voltage Relationship** Let us apply Kirchhoff's voltage law to the loop consisting of voltages  $E_R, V_{RY}$  and  $E_Y$ . We have

$$\bar{E}_R - \bar{E}_Y = \bar{V}_{RY}$$

Using law of parallelogram,

$$\begin{aligned} |\bar{V}_{RY}| = V_{RY} &= \sqrt{E_R^2 + E_Y^2 + 2 E_R E_Y \cos 60^\circ} \\ &= \sqrt{E_P^2 + E_P^2 + 2 E_P E_P (\%0)} = E_P \sqrt{3} \end{aligned}$$

Similarly,

$$\bar{E}_Y - \bar{E}_B = \bar{V}_{YB} \quad \text{and} \quad \bar{E}_B - \bar{E}_R = \bar{V}_{BR}$$

$$\therefore \quad \bar{V}_{YB} = E_P \sqrt{3} \quad \text{and} \quad \bar{V}_{BR} = E_P \sqrt{3}$$

Thus,

$$V_L = \sqrt{3} E_P$$

Line voltage =  $\sqrt{3}$  phase voltage



**Power Relationship** Let  $\cos \phi$  be the power factor of the system.

$$\text{Power consumed in one phase} = E_P I_P \cos \phi$$

$$\begin{aligned}\text{Power consumed in three phases} &= 3E_P I_P \cos \phi \\ &= 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi \\ &= \sqrt{3} V_L I_L \cos \phi \text{ watts}\end{aligned}$$

$$\text{Reactive power in one phase} = E_P I_P \sin \phi$$

$$\begin{aligned}\text{Total reactive power} &= 3E_P I_P \sin \phi \\ &= \sqrt{3} V_L I_L \sin \phi \text{ VAR}\end{aligned}$$


$$\text{Apparent power per phase} = 3 E_P I_P$$


$$\text{Total apparent power} = 3E_P I_P = \sqrt{3} V_L I_L \text{ volt amp}$$

# Balanced three phase systems
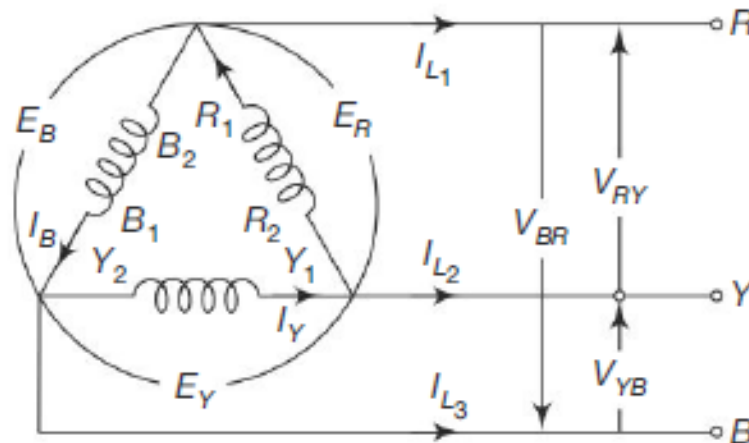
## Delta (mesh) connection ( $\Delta$ )


- Three wire system
- The phase angle difference between each phase is  $120^\circ$
- All the three phase voltages have the same amplitude, same period and frequency.



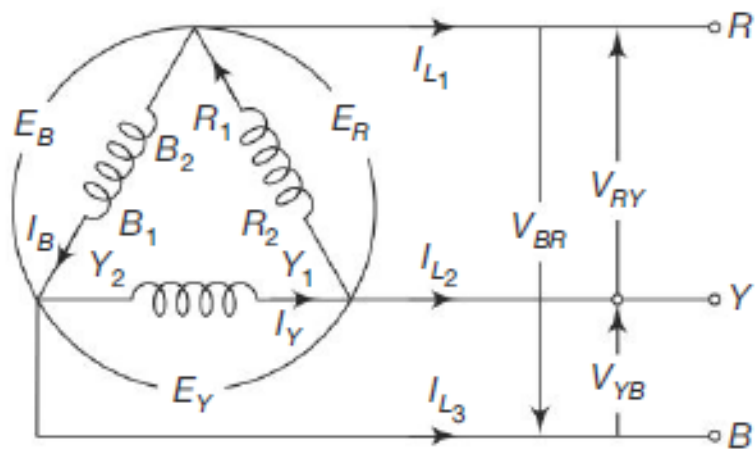

$$\begin{aligned}
 E_R &= E_Y = E_B = E_P, \\
 I_R &= I_Y = I_B = I_P, \\
 V_{RY} &= V_{YB} = V_{BR} = V_L, \\
 I_{L1} &= I_{L2} = I_{L3} = I_L,
 \end{aligned}$$

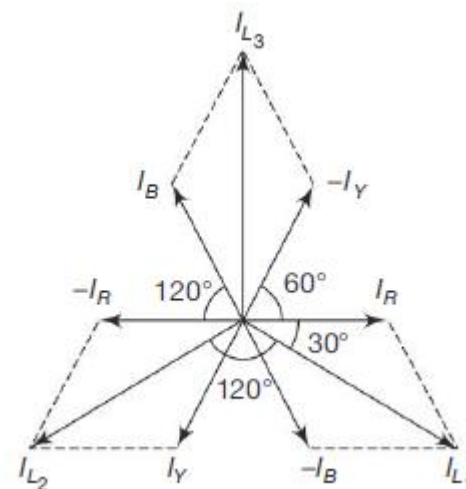phase voltage  
 phase current  
 line voltage  
 line current



**Voltage Relationship** Applying Kirchhoff's voltage law to the loop consisting of  $E_R$  and  $V_{RY}$ , we have  $E_R = V_{RY}$ .

Similarly,  $E_Y = V_{YB}$  and  $E_B = V_{BR}$ ,

Thus  $E_P = V_L$ .

Phase Voltage = Line Voltage

**Current Relationship** Applying Kirchhoff's current law at the junction of  $R_1$  and  $B_2$ , we have  $\bar{I}_R - \bar{I}_B = \bar{I}_L$ .

Referring to the phasor diagram and applying the law of parallelogram, we have

$$\begin{aligned} I_L I &= \sqrt{I_R^2 + I_B^2 + 2I_R I_B \cos 60^\circ} \\ &= \sqrt{I_P^2 + I_P^2 + 2I_P I_P (\%0)} \\ &= I_P \sqrt{3} \end{aligned}$$

Similarly, we have

$$\bar{I}_Y - \bar{I}_R = \bar{I}_L \quad \text{and} \quad \bar{I}_B - \bar{I}_Y = \bar{I}_L$$

Hence,  $I_L = I_P \sqrt{3}$  and  $I_P = I_L / \sqrt{3}$

Thus, line current =  $\sqrt{3}$  phase current

$$I_L = \sqrt{3} I_P$$

**Power Relationship** Let  $\cos \phi$  be the power factor of the system.

$$\text{Power per phase} = E_P I_P \cos \phi$$

$$\begin{aligned}\text{Total power for all the three phases} &= 3 E_P I_P \cos \phi \\ &= 3 V_L \frac{I_L}{\sqrt{3}} \cos \phi \\ &= \sqrt{3} V_L I_L \cos \phi \text{ watts}\end{aligned}$$

$$\text{Reactive power in one phase} = E_P I_P \sin \phi$$

$$\begin{aligned}\text{Total reactive power} &= 3 E_P I_P \sin \phi \\ &= \sqrt{3} V_L I_L \sin \phi \text{ VAR}\end{aligned}$$

$$\text{Apparent power per phase} = E_P I_P$$

$$\text{Total apparent power} = 3 E_P I_P = \sqrt{3} V_L I_L \text{ volt amp}$$