
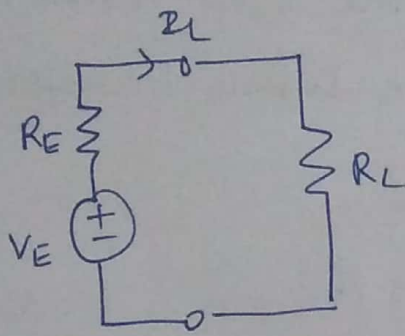


SOURCE TRANSFORMATION

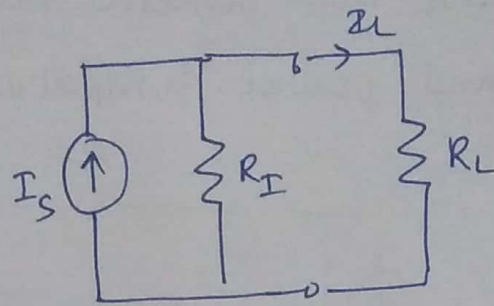

$$I_L = \frac{V_E}{R_E + R_L}$$




$$I_L = I_S \cdot \frac{R_I}{R_I + R_L}$$

For the above two circuits to be the same, I_L should be equal.

$$\therefore \frac{V_E}{R_E + R_L} = \frac{I_S R_L}{R_I + R_L}$$


This shows, $V_E = I_S R_L$
 $R_E = R_I$ } For the equivalence.

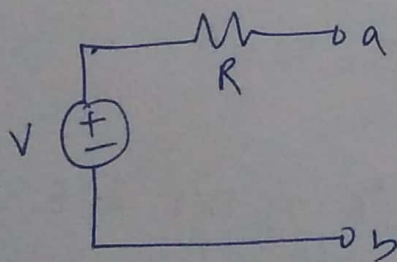Hence we use this to do some transformation
 - to simplify circuits.




$$V = IR$$

Voltage source in
series with R

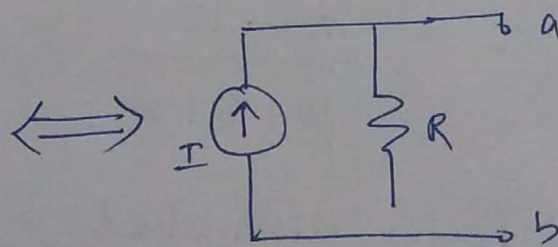



$$I = \frac{V}{R}$$

Current source in
parallel with R.

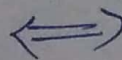

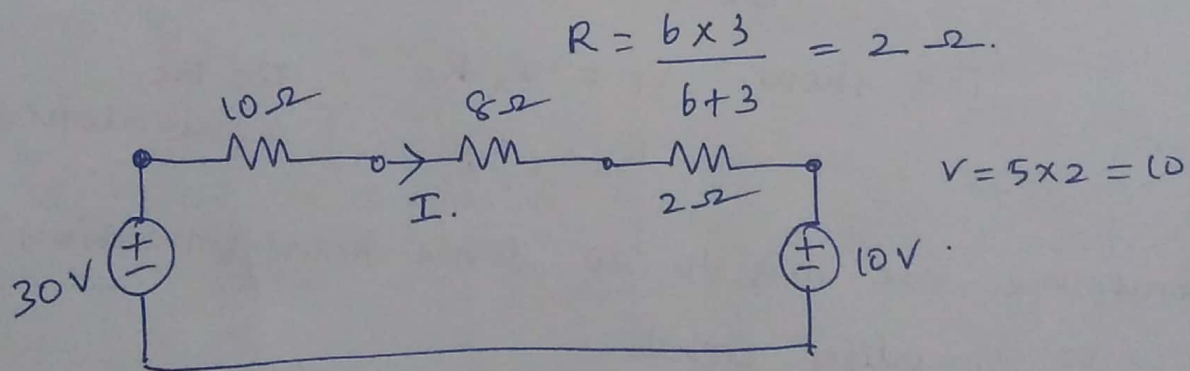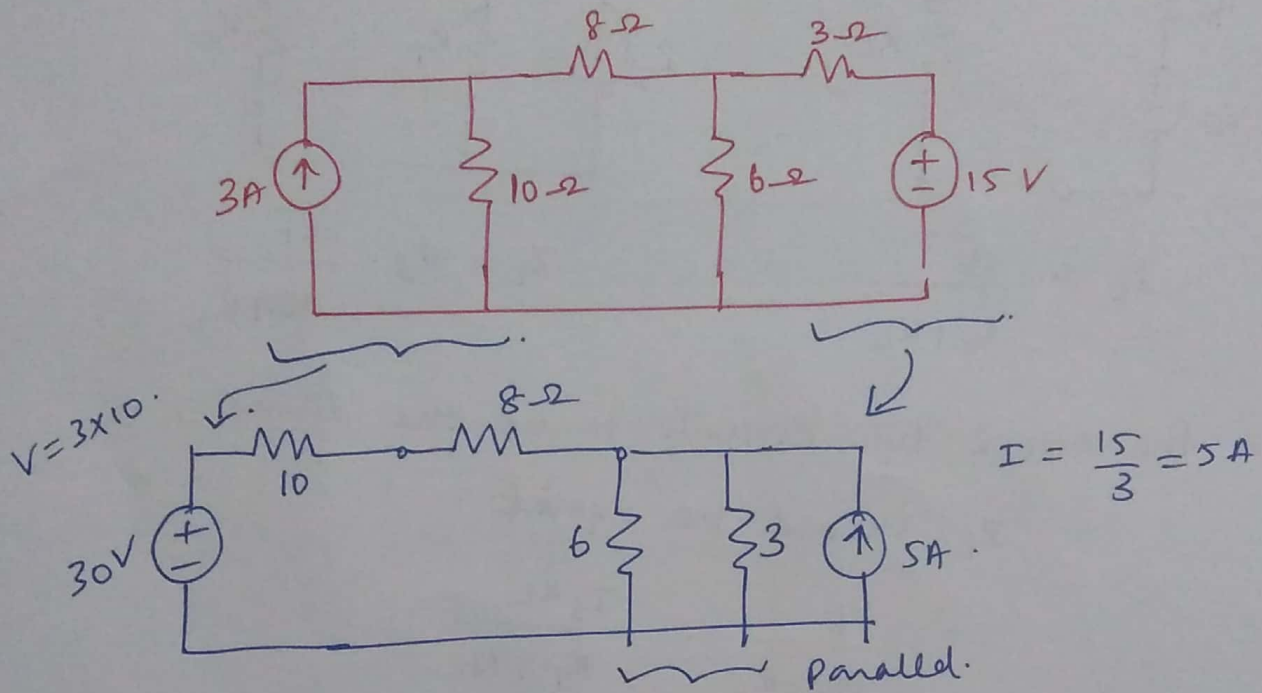Example :


- ① Find the current through the $8\text{-}\Omega$ resistor and power dissipated, use source transformation.



$$I = \frac{30 - 10}{10 + 8 + 2} = \frac{20}{20} = 1\text{A}$$

$$\text{Power dissipated} = I^2 R = 1^2 \times 8 = 8\text{W}$$


PRACTICE

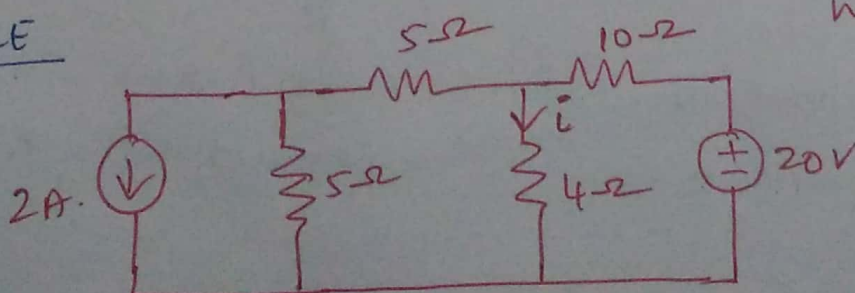

using source transformation
find i .


Ans
 $i = 0.555\text{A}$

③ Using source transformation find V_x .

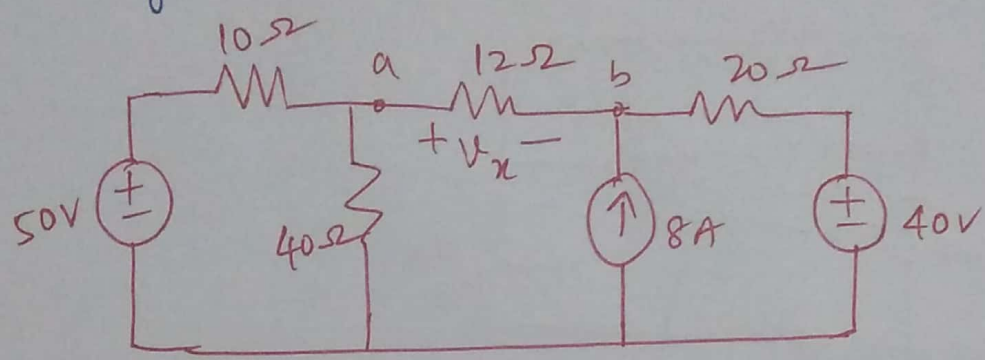


$I = \frac{50}{10} \text{ A}$

$I = \frac{40}{20}$

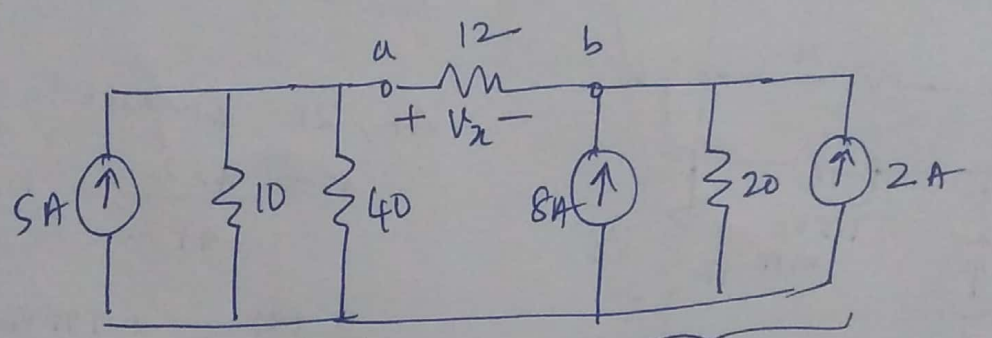


$\frac{10 \times 40}{10 + 40} = 8\Omega$

$I = 8 + 2 = 10 \text{ A}$

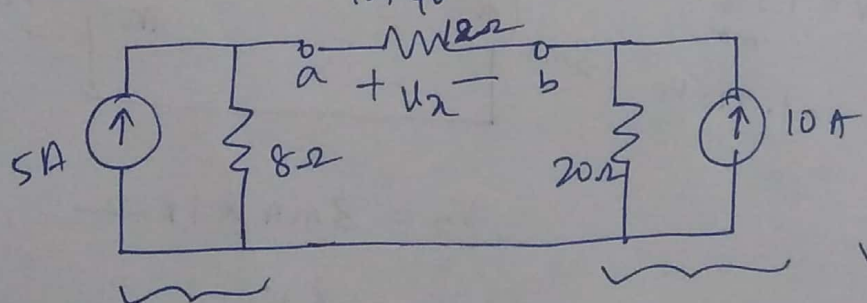

$V = I \times R = 10 \times 20$

$V = 5 \times 8$

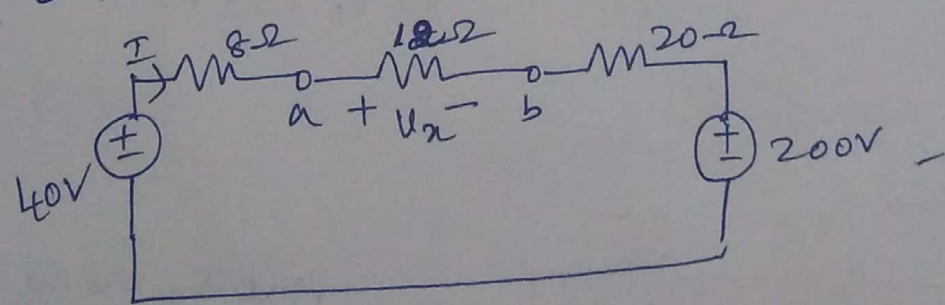

$V_x = I \times 12$

$I = \frac{40 - 200}{8 + 12 + 20} = -4 \text{ A}$


~~$V_x = -32 \text{ V}$~~

$= -4 \text{ A}$

$V_x = -4 \times 12$

$V_x = -48 \text{ V}$


② Find V_0 using source transformation

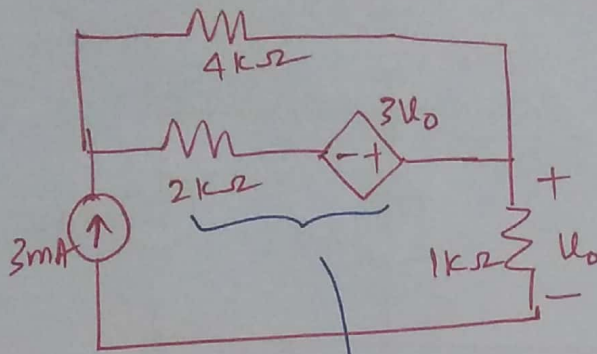


$$I = \frac{3V_0}{2k\Omega} = 1.5V_0 \text{ mA}$$

4k, 2k parallel.
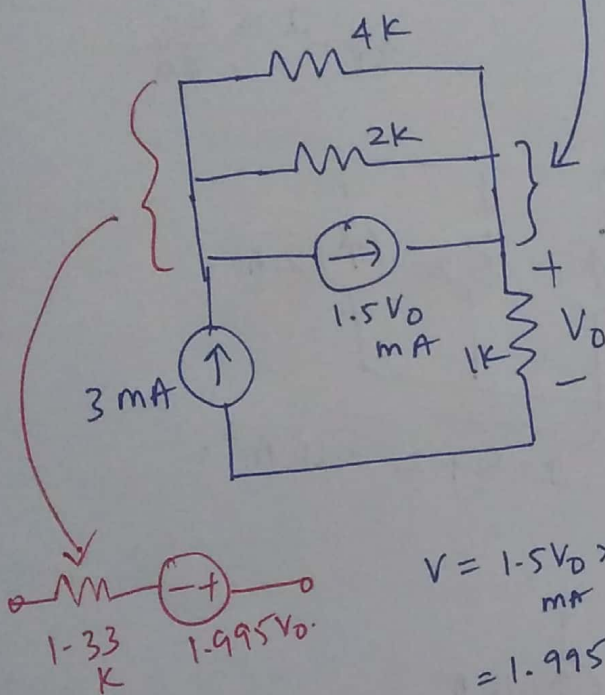
$$R = \frac{4 \times 2}{4 + 2} = 1.33k\Omega$$



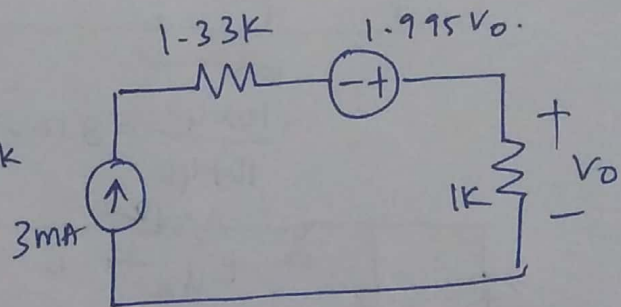
$$V = 1.5V_0 \times 1.33k\Omega = 1.995V_0$$



$$V_0 = 3\text{mA} \times 1k\Omega$$

$$V_0 = 3\text{V}$$

PRACTICE:

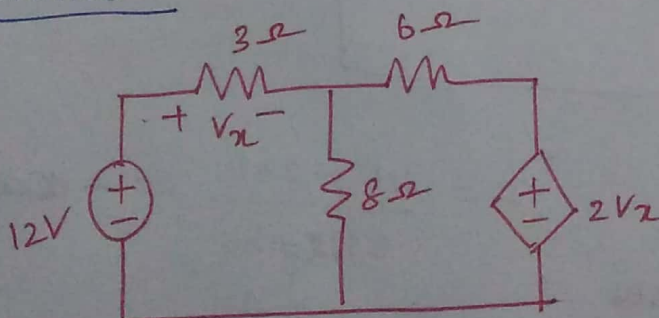

Find V_2 using source transformation.

Ans: 3.652 V