

# **BEEE101L – Basic Electrical Engineering**

**Dr. R. GUNABALAN**

Associate Professor

School of Electrical Engineering

Cabin No: 01, 7<sup>th</sup> floor, AB1 (nearer to Auditorium)

gunabalan.r@vit.ac.in

9894919269

## Module 2 : AC Circuits

6 Hrs


Alternating voltages and currents, RMS, average, form factor, peak factor; Single phase RL, RC, RLC series and parallel circuits; Power and power factor; Balanced three phase systems


### Course Outcome

- Evaluate AC circuit parameters using laws


# RLC series circuit

## Series RLC Circuit

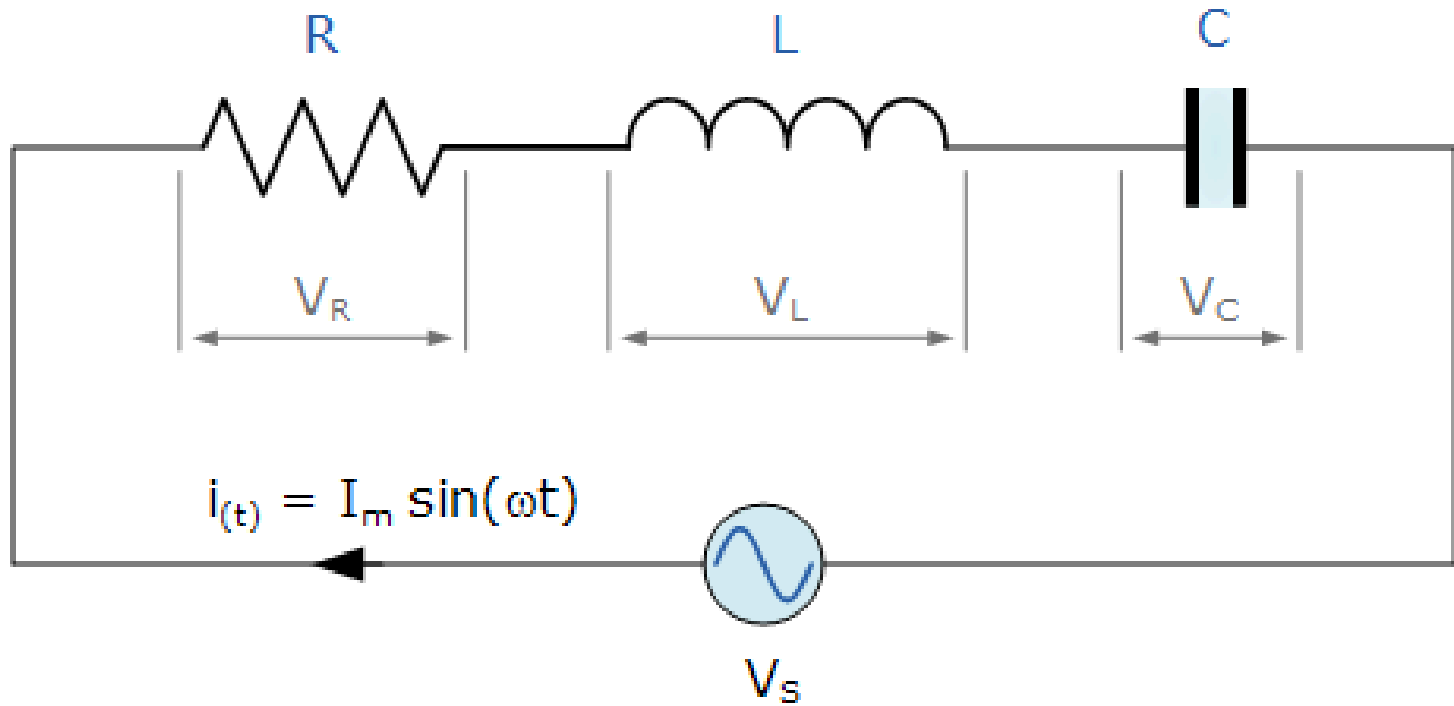

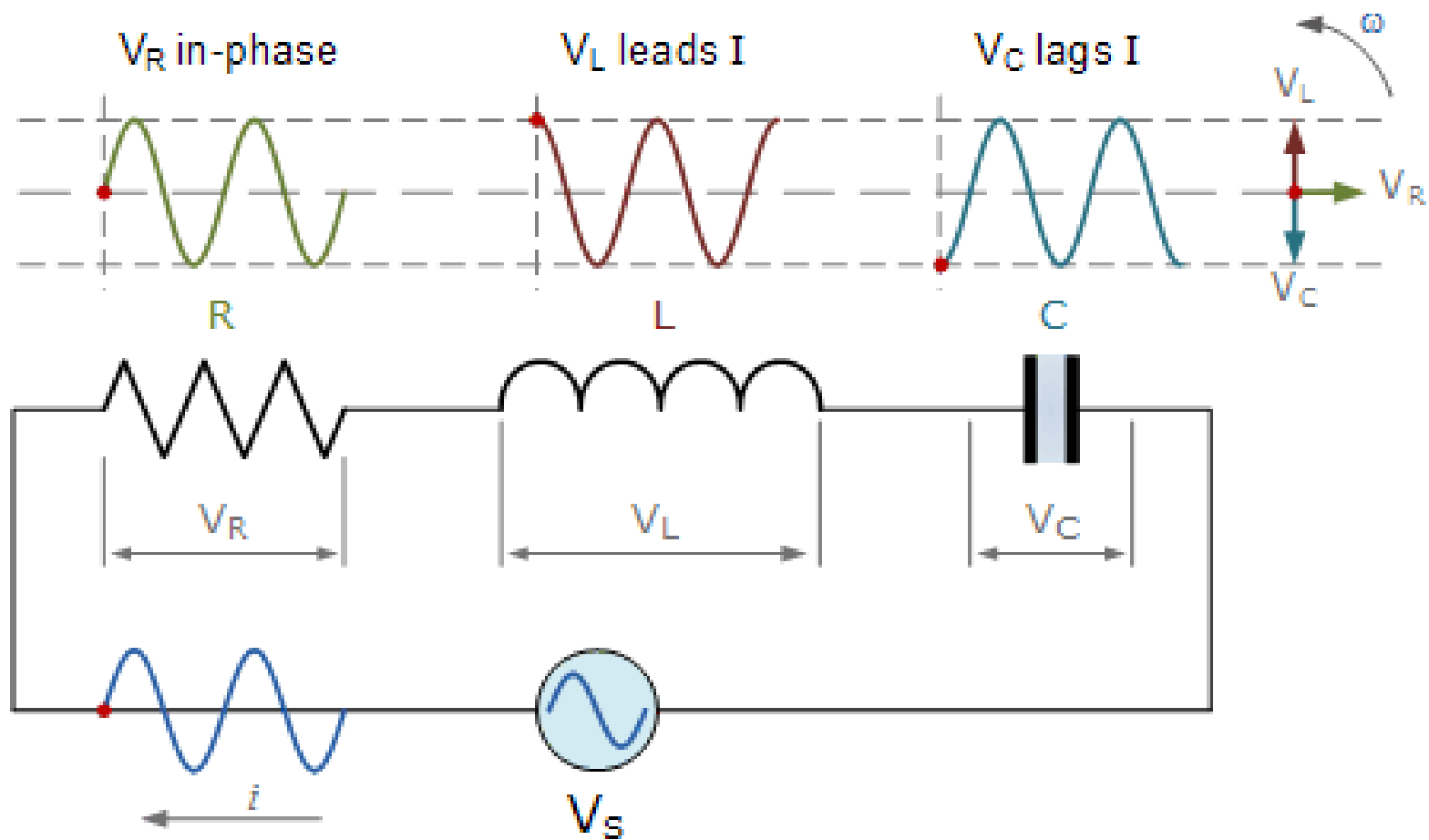


## Individual Voltage Vectors

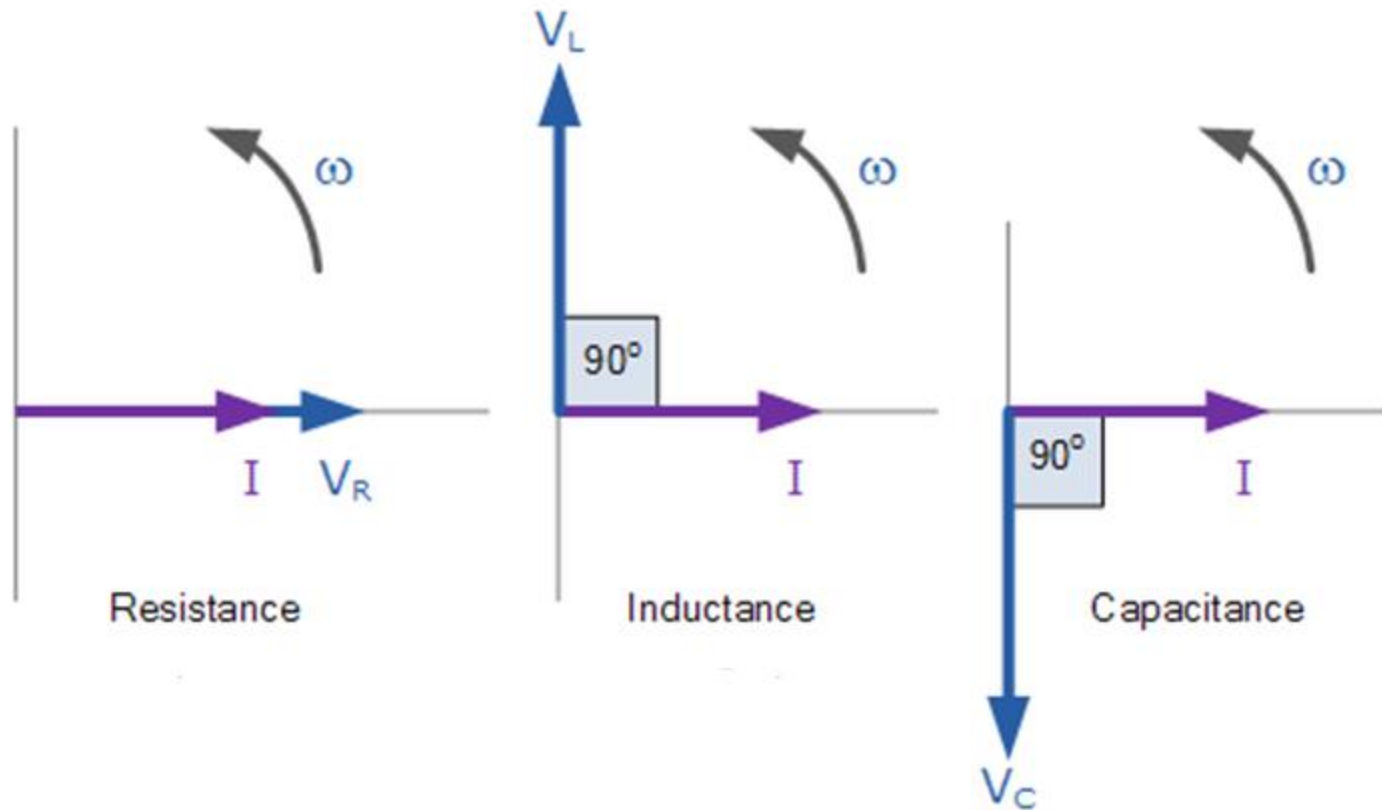

## Case (i) $V_L > V_C$
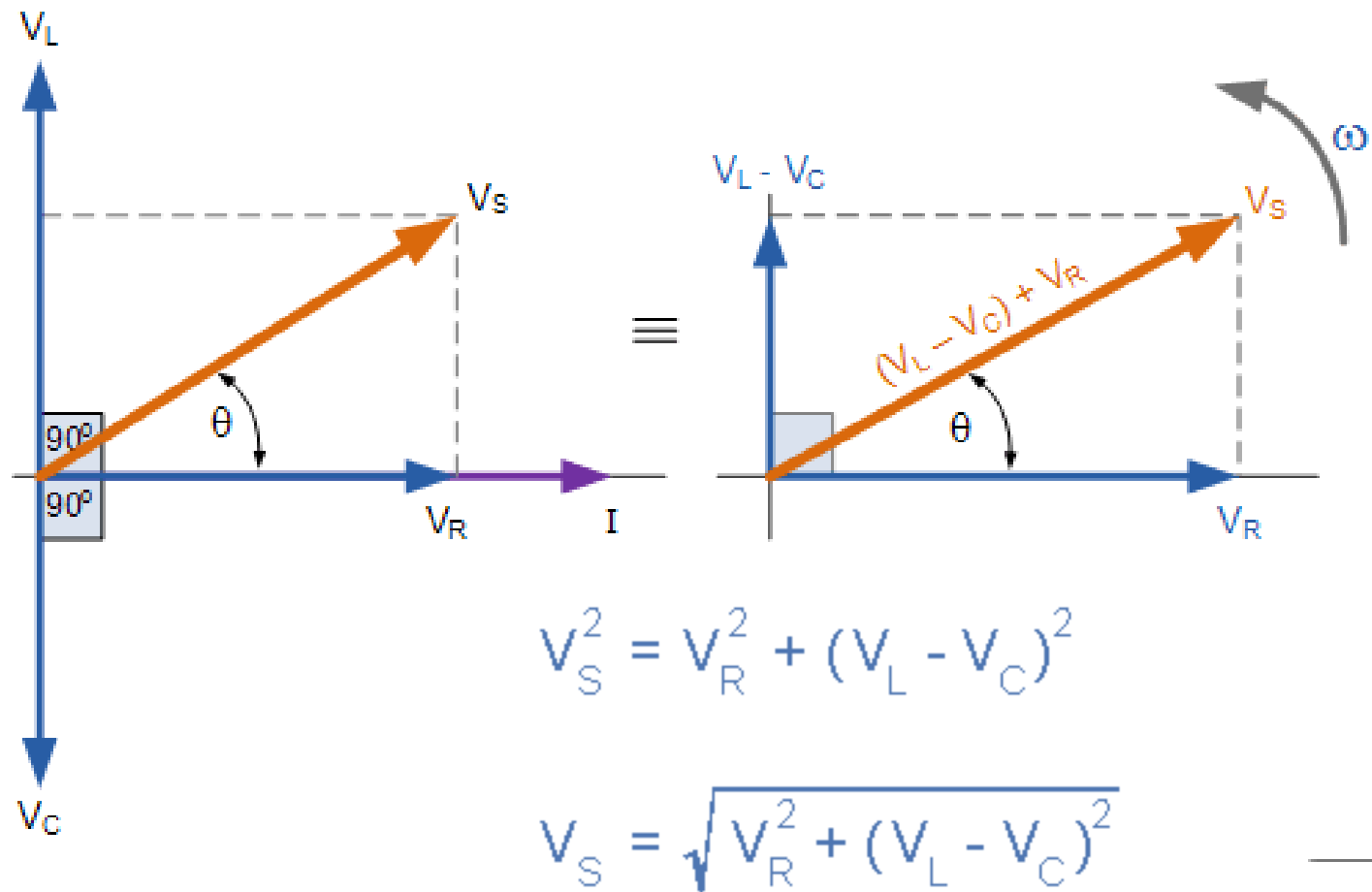
### Phasor Diagram for a Series RLC Circuit




$$V_R = I.R \quad V_L = jI.X_L \quad V_C = -jI.X_C$$

$$V_S = \sqrt{(I.R)^2 + (I.X_L - I.X_C)^2}$$


$$V_S = I.\sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore V_S = I \times Z \quad \text{where: } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z^2 = R^2 + (X_L - X_C)^2$$

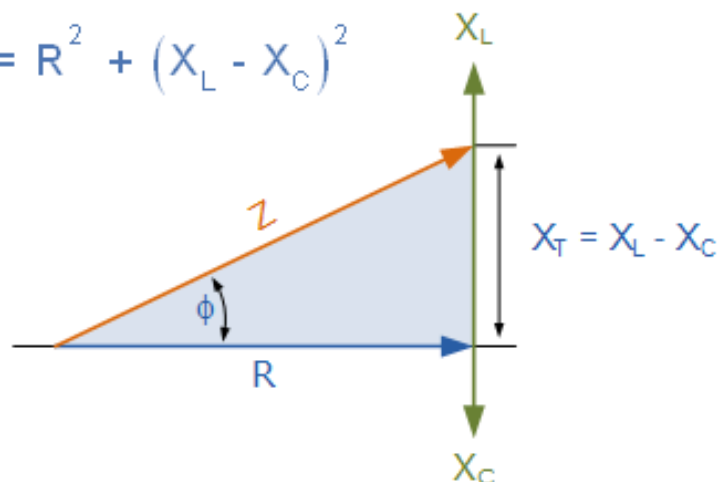

## Case (ii) $V_C > V_L$

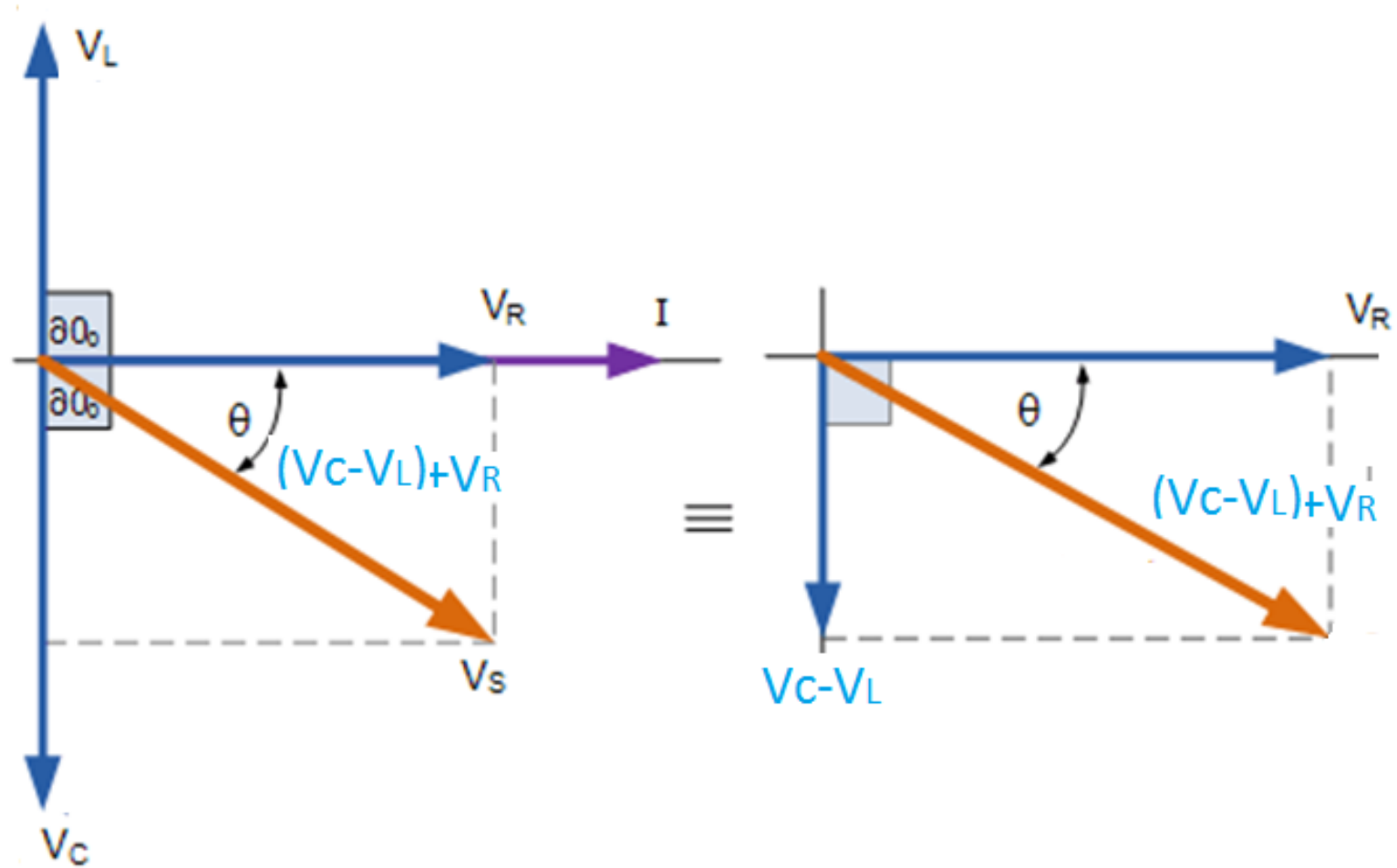



$$V_R = I.R \quad V_L = jI.X_L \quad V_C = -jI.X_C$$

$$V_S = \sqrt{(I.R)^2 + (I.X_C - I.X_L)^2}$$

$$V_S = I.\sqrt{R^2 + (X_C - X_L)^2}$$

$$\therefore V_S = I \times Z \quad \text{where: } Z = \sqrt{R^2 + (X_C - X_L)^2}$$

# Problems

An inductive coil takes 10 A and dissipates 1000 W when connected to a supply at 250 V, 25 Hz. Calculate the effective resistance, reactance, impedance and the power factor

$$Z = \frac{V}{I} = \frac{250}{25} = 10 \Omega$$

$$P = 1000 \text{ W (given)}$$

$$S = VI = 250 \times 10 = 2500 \text{ W}$$

Refer class notes

# Problems

When a voltage of 100 V at 50 Hz is applied to a choking coil A, the current taken is 8 A and the power is 120 W. When applied to a coil B, the current is 10 A and the power is 500 W. What current and power will be taken when 100 V is applied to the two coils connected in series.

Refer class notes

# Problems

A resistance of  $100\ \Omega$  is connected in series with a  $50\ \mu\text{F}$  capacitor across  $200\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate

- (i) impedance, current, power factor and phase angle
- (ii) draw the phasor diagram

Refer class notes

# Problems

Find the circuit constants of a two element series circuit which consumes 700 W with 0.707 leading power factor. The applied voltage is  $v=141.4 \sin 314t$

Refer class notes