 



# Outline

- ❑ Introduction to Logic
- ❑ Logic Gates
  - OR
  - AND
  - NOT
  - EX-OR/XOR
  - NOR
  - NAND
- ❑ Universal Gates
- ❑ Solved Examples and Exercises

# APPLICATIONS OF LOGIC GATES



Microprocessors

 


Random Access  
Memory (RAM)



Flash Memories



 Digital Data  
Transmission  
and Internet



# INTRODUCTION TO LOGIC

- **Digital logic** circuits use predefined **voltage levels** to represent the binary states e.g. '1' is represented by **high**, say 5 V and '0' is represented by **low**, say 0 V.
- As long as the variation in the voltage levels is not sufficient to change the binary state, the transmitted information is preserved (more **immune to noise** than analog representation).
- A **logic circuit** is one that behaves like a voltage-controlled **switch**, i.e. a two-position device with **ON** and **OFF** states
- This is termed a **binary device**, in which the **ON** state is represented by '1' and the **OFF** state by '0'

# BOOLEAN LOGIC

- Named after English mathematician George Boole (1815 – 1864)
- Boolean algebra uses symbols to represent a logical expression that has one of **two possible values: True/False (1/0; ON/OFF; High/Low)**
- The main purpose of these logical expressions is to describe the **relationship** between a logic circuit's **output (the decision)** and its **inputs (the circumstances)**, both of which are **binary values**.
- Boolean **constants** and **variables** are allowed to have only two possible values, **0 or 1**
- A Boolean **variable** is a quantity that may, **at different times**, be equal to **either 0 or 1**

# BOOLEAN LOGIC

- Boolean **0 and 1** do not represent actual numbers but instead represent the **state of a voltage variable**, or what is called its “**logic level**”
- A voltage in a digital circuit is said to be at the logic **0 level** or the logic **1 level**, depending on its actual numerical value (e.g. **low** or **high**)
- The **inputs** are considered **logic variables** whose logic **levels** at any time **determine** the **output levels**
- We use **letter symbols** to represent **logic variables**. For example, the letter A might represent a certain digital circuit input or output, and at any time either  $A = 0$  or  $A = 1$

# LOGIC GATES

- Logic gates are the most basic logic circuits
- These are the **fundamental building blocks** from which all other logic circuits and digital systems are constructed
- In Boolean algebra there are **only three basic operations: OR, AND, and NOT**, called logic operations
- Logic **gates** can be **constructed** from **diodes, transistors**, and resistors connected so that the circuit output is the result of a basic logic operation (OR, AND, NOT) performed on the inputs.



# Logic Gates

## Classification of Gates

### Basic Gates

1. OR Gate
2. AND Gate
3. NOT (Invertor) Gate

### Universal Gates

1. NAND Gate
2. NOR Gate

### Special Purpose

1. EX-OR Gate
2. EX-NOR Gate

# Boolean Algebra and Logic Gates

- Boolean Algebra and Logic Gates is an algebra developed by George Boole to argue the truth and falsity of statements
- Boolean Algebra and Logic Gates now serves as the mathematical basis for designing and building electronic circuits for computing devices
- Boolean Algebra and Logic Gates: The fundamental building blocks are logic gate circuits




# “OR” LOGIC GATE

- Two logic inputs, A and B, are combined using the OR operation (denoted by ‘+’ symbol) to produce the output x (x, A, B are bits).
- A **truth table** is a means for describing how a logic circuit’s **output depends** on the logic levels present at the circuit’s **inputs**

OR

A	B	$x = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table

 

OR Gate  
Circuit Symbol

# “OR” LOGIC GATE

- Example: **The bus will go to A or B.** The success (truth) of the bus going to one or other can be represented by  $x$ ; thus ‘ $x$ ’ occurs when the bus goes to **either A or B or both** (it might travel through A to get to B or vice versa)
- The Boolean expression for the OR operation is  $x = A + B$
- The **positive (+) sign** is **not** the **additive** function, but means OR in logic


$$x = A \text{ OR } B$$

		OR	
A	B		$x = A + B$
0	0		0
0	1		1
1	0		1
1	1		1

# “OR” LOGIC GATE


- In an electrical circuit, **OR** operation is equivalent to **two switches in parallel**
- The lamp F lights ( $F = 1$ ) when either switch or both switches are closed (closed switch is represented by logic level 1)

i.e.  $F = A + B$

 
 
# “OR” LOGIC GATE

- If no (zero) voltage (logic level 0) is applied to both inputs then the output voltage  $V_o$  is also zero (logic level 0) (both diodes are reverse biased i.e. open circuit)
- If, however, a positive voltage of, say, 5 V (logic level 1) is applied to either one or both inputs then at least one diode turns on (forward biased), and the output voltage is also  $\sim 5$  V




Diode-based OR-gate circuit
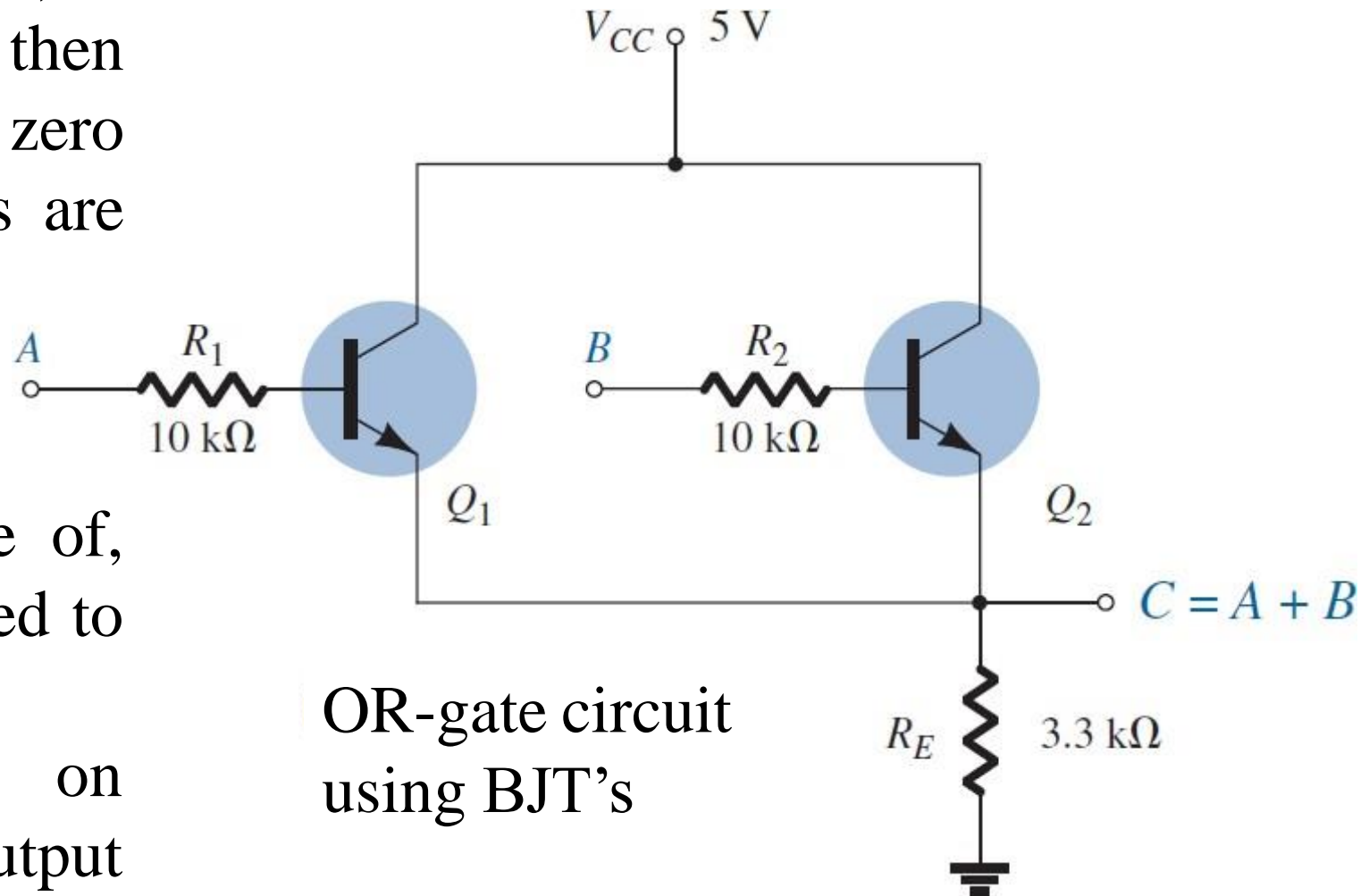
# “OR” LOGIC GATE


If no (zero) voltage (logic level 0) is applied to both inputs  $A$  and  $B$  then the output voltage  $V_o$  is also zero (logic level 0) (both transistors are in cutoff i.e. open circuit)

If, however, a positive voltage of, say, 5 V (logic level 1) is applied to either one or both inputs then at least one transistor turns on (saturation mode), and the output voltage  $C$  is also  $\sim 5$  V (logic level 1)


 
# “OR” LOGIC GATE

For three inputs, the OR-gate circuit symbol, and corresponding truth table is given below. The Boolean expression is  $x = A + B + C$



A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


# “AND” LOGIC GATE

- Two logic inputs, A and B, are combined using the AND operation (denoted by ‘.’ symbol) to produce the output x (x, A, B are bits)
- The table shows that x is a logic 1 only when both A and B are at logic 1

## AND

A	B	$x = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

 

Circuit Symbol



# “AND” LOGIC GATE

- Example: **The bus goes to A and B.** The success (truth) of the bus going to both places can be represented by x; thus ‘x’ occurs **only when** the bus goes to **both A and B**
- The Boolean expression for the AND operation is  **$F = A \cdot B$**
- The **period (.) sign** is **not** the **multiplicative** function, but means AND in logic


$$F = A \text{ AND } B$$

AND			
A	B		$x = A \cdot B$
0	0		0
0	1		0
1	0		0
1	1		1

# “AND” LOGIC GATE

- In an electric circuit, **AND** operation is equivalent to **two switches in series**
- The lamp **F lights** (i.e.  $F = 1$ ) only when **both switches are closed** (closed switch is represented by logic level 1)


i.e.  $F = A \cdot B$

 


# “AND” LOGIC GATE

- If zero voltage (logic level 0) is applied to either A or B or both, then that respective diode(s) is forward-biased (i.e. short-circuit), resulting in the output voltage becoming zero (logic level 0).
- If 10 V (logic level 1) is applied to both A and B then the both diodes are reverse-biased (i.e. open-circuit) and the output voltage rises to the 10 V (logic level 1) supply.

Diode-based  
AND-gate circuit

 

# “AND” LOGIC GATE

 


If no (zero) voltage (logic level 0) is applied to either input  $A$  or  $B$  or both, then the output voltage  $V_o$  is also zero (logic level 0) (at least one transistor is in cutoff i.e. open circuit so no current flows)

If, however, a positive voltage of, say, 5 V (logic level 1) is applied to both inputs then both transistors turn on (saturation mode), and the output voltage  $C$  is also  $\sim 5\text{ V}$  (logic level 1)

# “AND” LOGIC GATE

For three inputs, the AND-gate circuit symbol and the truth table is given below. The Boolean expression is  $x = A \cdot B \cdot C$

A	B	C	$x = ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 


# “NOT” LOGIC GATE

- The **NOT** operation is unlike the OR and AND operations because it is performed on a **single input** variable
- If the variable A is subjected to the NOT operation (also called inversion or complementation), the result x is expressed as  $x = \bar{A}$  or  $x = A'$

Truth Table


NOT

A	$x = \bar{A}$
0	1
1	0

 
 
# “EX-OR/XOR” LOGIC GATE

- Two logic inputs, **A** and **B**, are combined using the Exclusive-OR (EX-OR or simply XOR) operation (denoted by symbol  $\oplus$ ) to produce the output **F**
- The truth table shows that **F** is a logic 1 only when **A** and **B** are different



Circuit Symbol

Truth  
Table

<b>A</b>	<b>B</b>	<b>F</b>
0	0	0
0	1	1
1	0	1
1	1	0



# “EX-OR/XOR” LOGIC GATE

- Example: **The bus goes to either A or B but not to both.** The success (truth) of the bus going to one or other can be represented by F; thus ‘F’ occurs when the bus goes **only to A (and not B) or only to B (and notA)**
- The Boolean expression for the EX-OR operation is


$$F = A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$$

(in terms of the fundamental gates  
OR, AND, NOT)

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

 
# “EX-OR/XOR” LOGIC GATE

- The **XOR** operator is typically represented in an electric circuit by the **two-way switching** associated with a stair light
- The lamp **F** lights (i.e.  $F = 1$ ) **only** when **one of the switches is ON (1)** **AND the other is OFF (0)** i.e.  $F = A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$



 
# “NOR” LOGIC GATE

- NOR gate operates like an OR-gate followed by an Inverter (NOT gate)
- The NOR-gate output ( $x = \overline{A + B}$ ) is the exact inverse of the OR-gate output



Equivalent Circuit

 


Truth Table

		OR		NOR	
A	B		$A + B$		$\overline{A + B}$
0	0		0		1
0	1		1		0
1	0		1		0
1	1		1		0

 
# “NAND” LOGIC GATE

- NAND-gate operates like an AND-gate followed by an Inverter (NOT gate)
- The NAND-gate output ( $x = \overline{A \cdot B}$ ) is the exact inverse of the AND-gate



Circuit Symbol Denotes inversion

Equivalent Circuit

 

Truth Table

		AND		NAND	
		$AB$		$\overline{AB}$	
A	B				
0	0	0		1	
0	1	0		1	
1	0	0		1	
1	1	1		0	


# OPERATOR PRECEDENCE

- If an **expression contains both AND and OR operations**, the **AND operations are performed first**, unless there are parentheses in the expression, in which case the **operation inside the parentheses is to be performed first**
- Example:  $F = A . B + C$   
First AND operation is performed between A and B  
The result of above operation is then ORed with C

# UNIVERSAL GATES: NAND/NOR

- All Boolean expressions consist of various combinations of the basic operations of OR, AND, and NOT (or INVERT).
- Any expression can be implemented using combinations of OR gates, AND gates, and INVERTERS (NOT gates).
- NAND and NOR gates, in the proper combination, can be used to perform each of the Boolean operations OR, AND, and INVERT (NOT)
- Thus, it is **possible to implement any logic expression** using **NAND** or **only NOR gates** and no other type of gate
- Thus, **NAND and NOR** gates are called “**universal gates**”
- Easier/simpler to standardize by using a single type of gate. However, the number of gates that need to be used increases.


# NOT OPERATION USING NAND GATE

 



 
# AND OPERATION USING NAND GATES

Two NAND gates are required to perform the operation of one AND gate



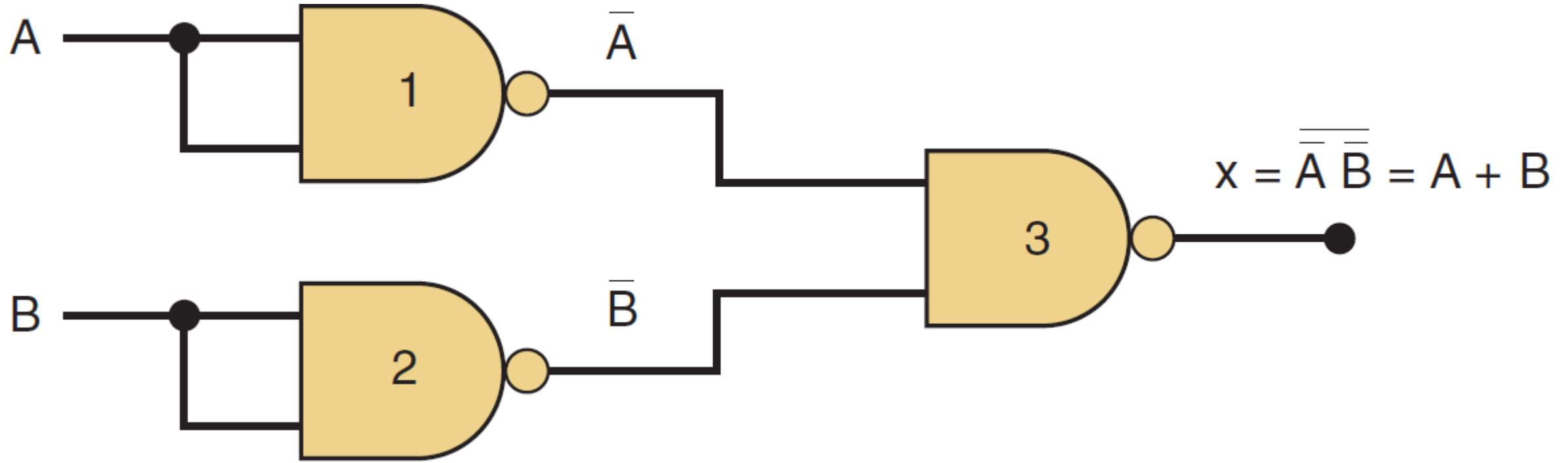
# OR OPERATION USING NAND GATES

Three NAND gates are required to perform the operation of one OR gate




# NOT OPERATION USING NOR GATE

 

 
# AND OPERATION USING NOR GATES

Three NOR gates are required to perform the operation of one AND gate


 
# OR OPERATION USING NOR GATES

Two NOR gates are required to perform the operation of one OR gate



# IC Technology-Terms

## **Datasheet**

A printed specification giving details of the pin configuration, electrical properties, and mechanical profile of an electronic device.

## **Design Specifications**


A detailed description, especially one providing information needed to make, build, or produce something.

## **Libraries**


a collections of descriptions of commonly used hardware circuits that can be used as modules in a design file

# Logic Gates IC

Device	Type	Description
4011B	CMOS	Quad 2-input NAND gate
4093B	CMOS	Quad 2-input Schmitt NAND gate
74LS00	LS TTL	Quad 2-input NAND gate
74HC00	CMOS	Quad 2-input NAND gate
74LS132	LS TTL	Quad 2-input Schmitt NAND gate
74HC132	CMOS	Quad 2-input Schmitt NAND gate
74LS10	LS TTL	Triple 3-input NAND gate
4023B	CMOS	Triple 3-input NAND gate
74LS20	LSTTL	Dual 4-input NAND gate
4012B	CMOS	Dual 4-input NAND gate
74LS30	LS TTL	8-input NAND gate
4068B	CMOS	8-input NAND gate
74HC133	CMOS	13-input NAND gate

 

 
Functional diagram of the  
74LS00 or 74HC00 quad two-input NAND  
gate IC.




Basic method of disabling unwanted TTL NAND gate inputs



# TinkerCAD-Explore NAND gate (Hardware)

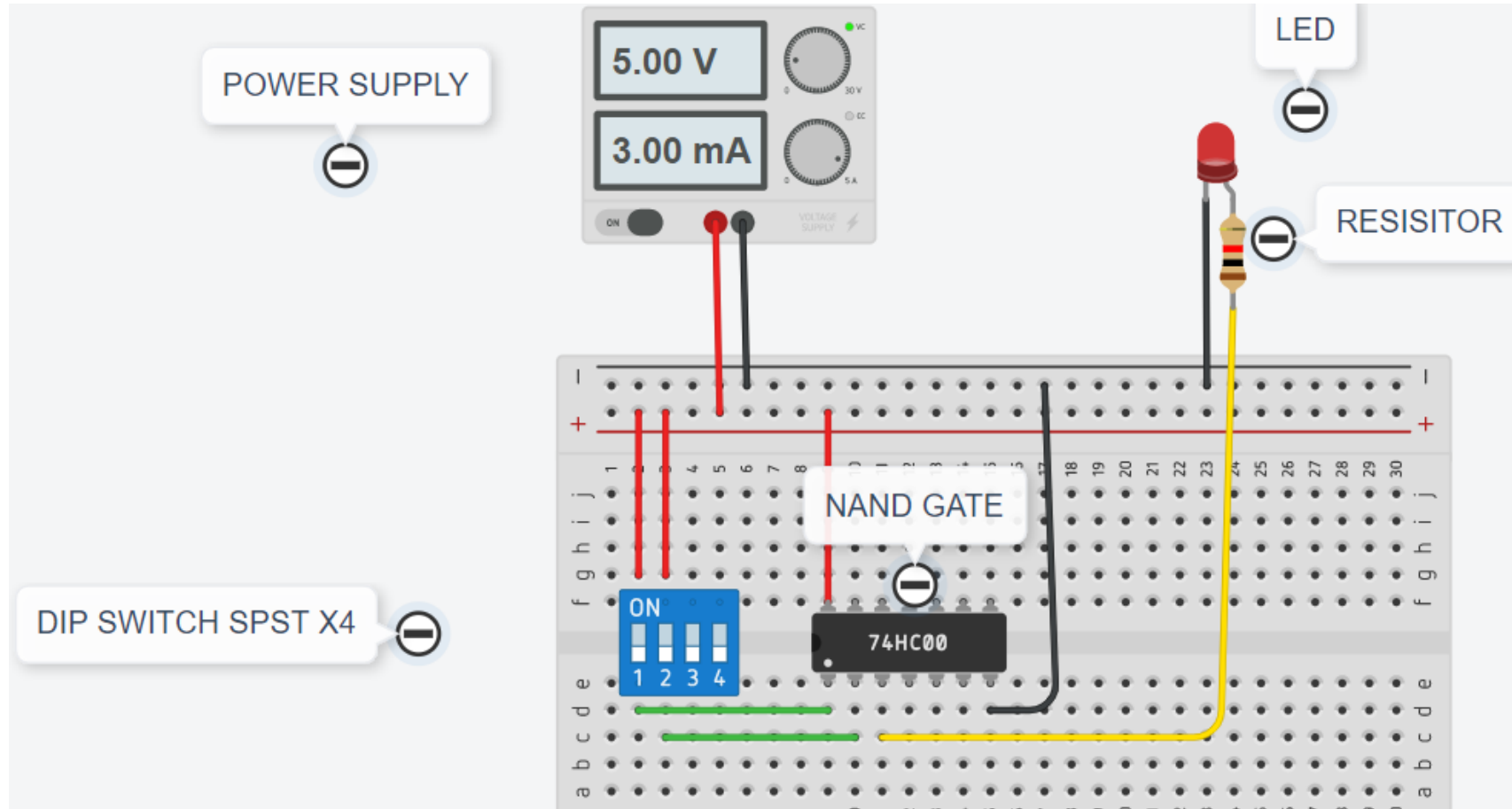
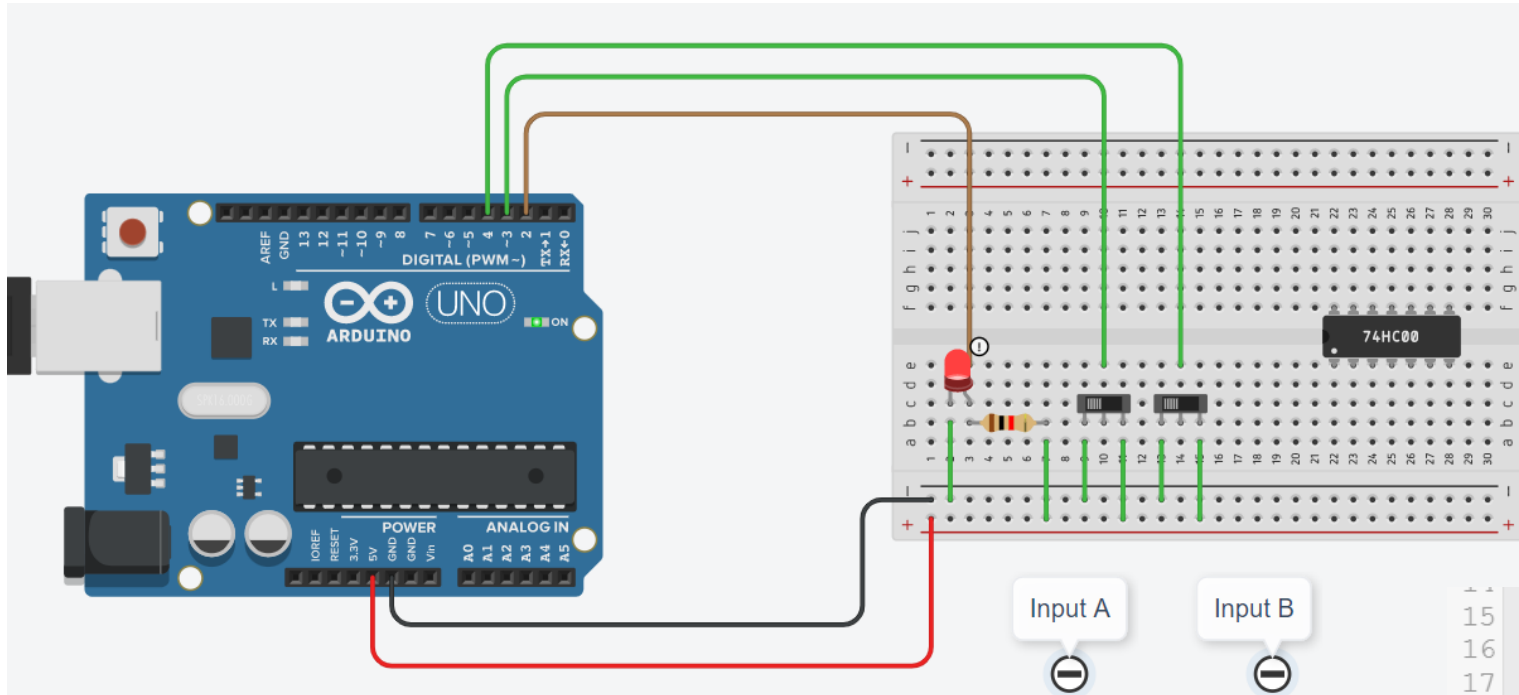
# TinkerCAD-Explore NOR gate (Hardware + Software library)



```
1 // C++ code
2 //
3 void setup()
4 {
5     int LED=2;
6     int switch_1=3;
7     int switch_2=4;
8     pinMode(LED_BUILTIN, OUTPUT);
9     pinMode(LED, OUTPUT);
10    pinMode(switch_1, INPUT);
11    pinMode(switch_2, INPUT);
12
13 }
```

```
15 void loop()
16 {
17     int LED=2;
18     int switch_1=3;
19     int switch_2=4;
20
21
22     if (!digitalRead(switch_1) & !digitalRead(switch_2)){
23         digitalWrite(LED, HIGH);
24     }
25     else {
26         digitalWrite(LED, LOW);
27     }
28
29 }
```

## SOLVED EXAMPLES

**1. Write the Boolean expression for a 3-input NAND gate.**

Sol. The output  $Y$  of the NAND gate with inputs  $A$ ,  $B$ , and  $C$  is  $Y = \overline{A.B.C}$

**2. Which logic gate generates a HIGH output when an odd number of inputs are HIGH?**

Sol. Exclusive-OR gate (EX-OR/XOR Gate)

## SOLVED EXAMPLES

3. For the given input signals A, B, C, sketch the output for an OR gate.



The output  $X = A + B + C$  is high when any of the inputs is high.

## SOLVED EXAMPLES

**4. How many different sets of input conditions will produce a HIGH output from a five-input OR gate?**

Sol. The total number of sets of input conditions are  $2^5 = 32$ . The output is low only when all the inputs are low. This happens in only one case. Therefore, 31 different sets of input conditions will produce a HIGH output.

**5. Write the Boolean expression for a 4-input XOR gate.**

Sol. The output  $Y$  of the XOR gate with inputs  $A$ ,  $B$ ,  $C$  and  $D$  is


$$Y = A \oplus B \oplus C \oplus D$$

## SOLVED EXAMPLES

**6. For the given expression, draw the corresponding logic circuit, using AND, OR and NOT gates.**

$$x = \overline{A.B(C + D)}$$

Sol.

 


## SOLVED EXAMPLES

**7. For the given expression, draw the corresponding logic circuit, using AND, OR and NOT gates.**


$$z = \overline{A + B + \overline{CDE} + \overline{BCD}}$$

Sol.

 

## SOLVED EXAMPLES

 **8. Apply the input waveforms A, B and C given below to a NOR gate, and draw the output waveform.**



Sol. The output waveform





# EXERCISES

- 1. Draw a logic circuit, incorporating any gates of your choice, which will produce an output 1 when its two inputs are different. Also draw the same logic circuit incorporating only NOR gates.**

# EXERCISES

  
1. Draw a logic circuit, incorporating any gates of your choice, which will produce an output 1 when its two inputs are different. Also draw the same logic circuit incorporating only NOR gates.

Ans. The required function is  $F = A \oplus B = (A \cdot \bar{B}) + (\bar{A} \cdot B)$


 
## EXERCISES

Circuit for  $F = A \oplus B = (A \cdot B) + (\overline{A} \cdot \overline{B})$  using only NOR gates  
(gates with single input imply that both inputs are same)



## EXERCISES

**2. Draw the circuit diagram to implement the expression below**


$$x = (A + B)(\overline{B} + C)$$

## EXERCISES

2. Draw the circuit diagram to implement the expression below


$$x = (A + B)(\bar{B} + C)$$

Ans.

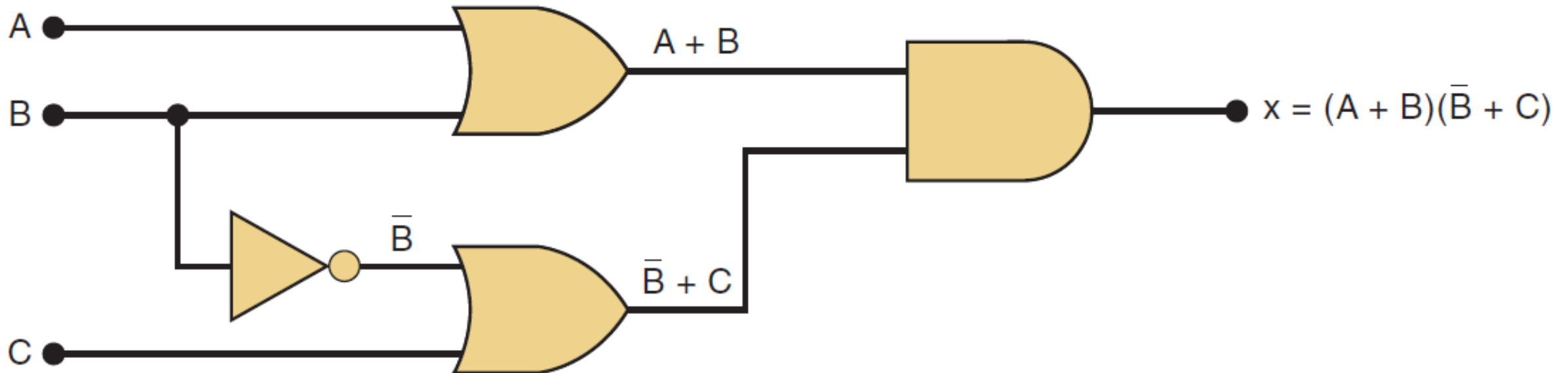


## EXERCISES

 3. Determine the output waveform for an OR gate output with inputs A and B varying according to the timing diagrams shown below




# EXERCISES

Ans.

 

# EXERCISES

 
4. Determine the output waveform for an AND gate with inputs A and B varying according to the timing diagrams shown below





# EXERCISES

Ans.

 



## EXERCISES

**5. Determine the output waveform for an AND gate with inputs A and B varying according to the timing diagrams shown below**



Ans. The output



## EXERCISES

6. Draw the circuit diagram to implement the expression


$$x = AC + B\overline{C} + \overline{A}BC$$

## EXERCISES

6. Draw the circuit diagram to implement the expression

$$x = AC + B\bar{C} + \bar{A}BC$$

Ans.

 

## EXERCISES

- 7. Draw the circuit diagram to implement the expression below, using gates with no more than three inputs**


$$x = \overline{A}BC(\overline{A+D})$$

## EXERCISES

7. Draw the circuit diagram to implement the expression below, using gates with no more than three inputs


$$x = \bar{A}BC(\overline{A + D})$$

Ans.

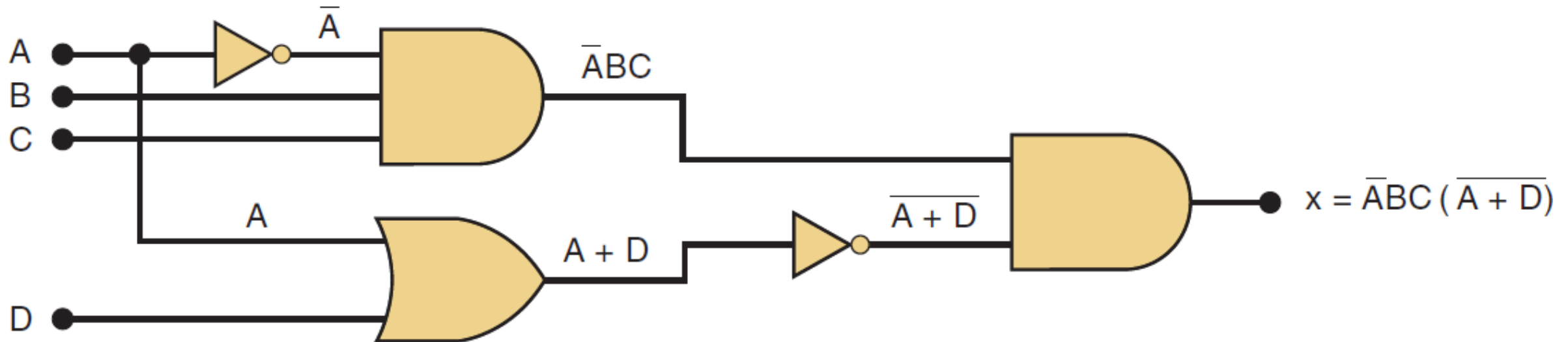

# EXERCISES

 
8. Determine the waveform at the output of a NOR gate for the input waveforms shown below





# EXERCISES


Ans.

 

$\overline{A+B}$


# EXERCISES

 9. Determine the waveform at the output of a NAND gate for the input waveforms shown below



# EXERCISES

Ans.

 

## EXERCISES

**10. Implement the logic circuit for the expression below using only NOR and NAND gates**

$$x = \overline{AB.(C + D)}$$

## EXERCISES

10. Implement the logic circuit for the expression below using only NOR and NAND gates

$$x = \overline{AB.(C + D)}$$

Ans.

