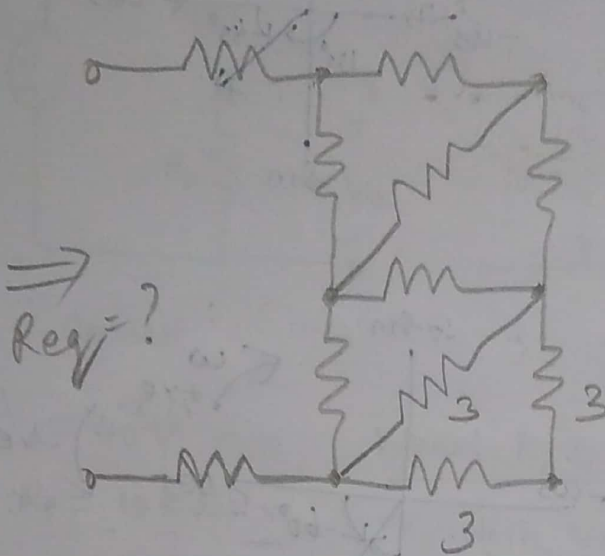


Module 1 - Solutions

(1) $R = 3\Omega$ for all resistors.



Two resistors
in parallel
of equal value
 $R_{eq} = \frac{(R)(R)}{R+R}$
 $= R/2$


$3, 3$ series $\Rightarrow 6\Omega$

$6, 3$ parallel $\Rightarrow \frac{6 \times 3}{6+3} = 2\Omega$

It can be further reduced using
star-delta transformation only.

(ignore this problem)

(2) equivalent resistance

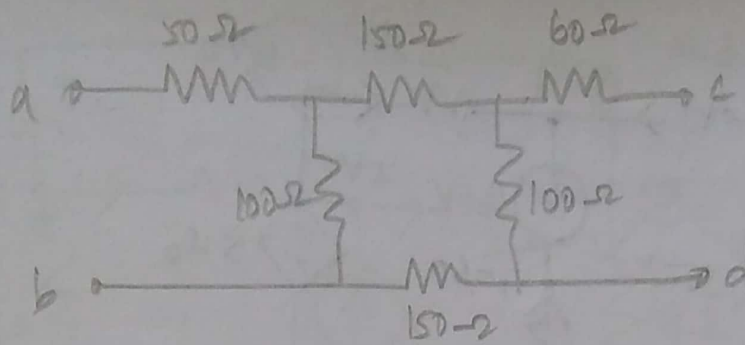

Rab

Since c-d is open, $I = 0$ through 60Ω resistor.

$150\Omega, 100\Omega, 150\Omega$ series $R = 400\Omega$

$400\Omega, 100\Omega$ parallel $R = \frac{400 \times 100}{400 + 100} = 80\Omega$

$50\Omega, 80\Omega$ series $= 130\Omega$

$R_{ab} = 130\Omega$

Rcd


Since a-b is open, $I = 0$ through 50Ω resistor.

$150, 100, 150\Omega$ series $R = 400\Omega$

$400\Omega, 100\Omega$ parallel $R = 80\Omega$

$80\Omega, 60\Omega$ series $R = 140\Omega$

③ Nodal analysis

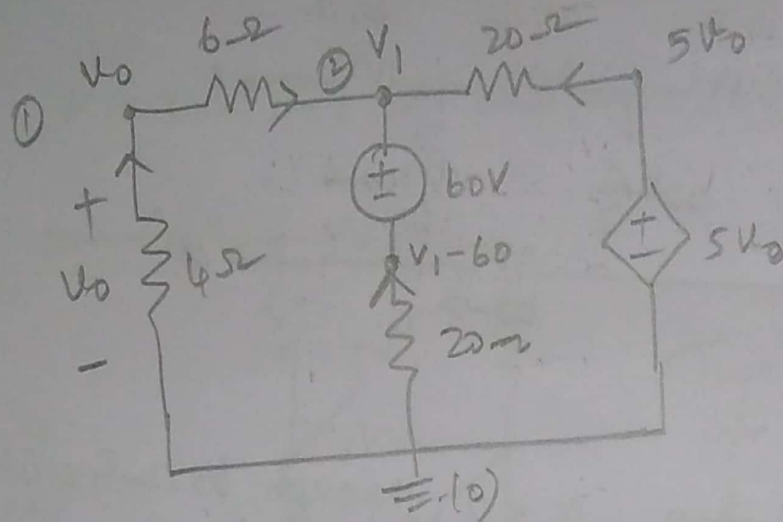

At node ①,

$$\frac{0 - V_0}{4} = \frac{V_0 - V_1}{6}$$

$$V_0 \left[\frac{1}{4} + \frac{1}{6} \right] - \frac{1}{6} V_1 = 0$$

$$0.416 V_0 - 0.166 V_1 = 0$$

At node 2

$$\frac{V_0 - V_1}{6} + \frac{0 - (V_1 - 60)}{20} + \frac{5V_0 - V_1}{20} = 0$$

$$V_0 \left[\frac{1}{6} + \frac{1}{4} \right] - V_1 \left[\frac{1}{6} + \frac{1}{20} + \frac{1}{20} \right] = -3$$


$$0.416 V_0 - 0.266 V_1 = -3$$

Solving two equations

$$V_0 = 11.97 \text{ V} \approx 12 \text{ V}$$

$$V_1 = 30 \text{ V}$$

④ Nodal Analysis.

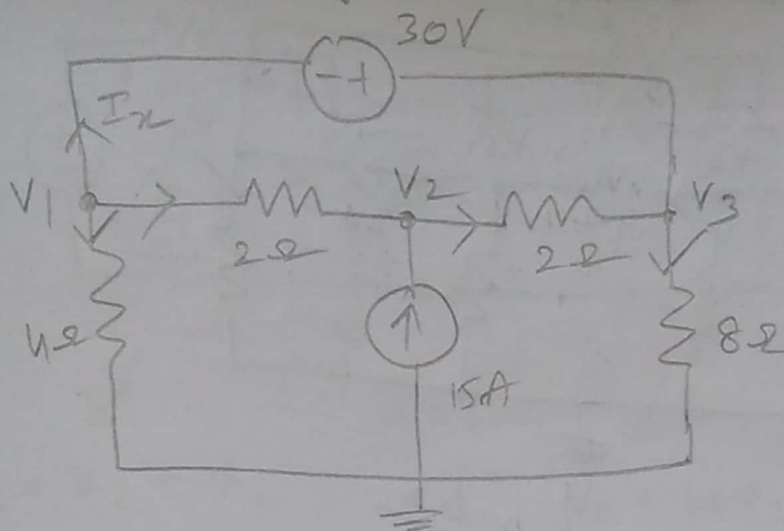

At node 1,

$$\frac{V_1 - 0}{4} + \frac{V_1 - V_2}{2} + I_x = 0$$

sub I_x in node ① eqn.

At node 3,

$$I_x + \frac{V_2 - V_3}{2} = \frac{V_3}{8}$$

$$I_x = V_3 \left[\frac{1}{8} + \frac{1}{2} \right] - \frac{1}{2} V_2$$

$$\frac{V_1}{4} + \frac{V_1}{2} - \frac{V_2}{2} - \frac{1}{2} V_2 + V_3 \left(\frac{1}{8} + \frac{1}{2} \right) = 0$$

$$0.75V_1 - V_2 + 0.625V_3 = 0 \longrightarrow \textcircled{1}$$

Between V_1 and V_3 there is a voltage source (super node)

$$\therefore V_3 - V_1 = 30 \longrightarrow \textcircled{2}$$

At node 2,


$$\frac{V_1 - V_2}{2} + 15 = \frac{V_2 - V_3}{2}$$

$$0.5V_1 - V_2 + 0.5V_3 = -15 \longrightarrow \textcircled{3}$$

Solving eqns ①, ② & ③, we get (calculator)

$$V_1 = 30 \quad V_2 = 60 \text{ V} \quad V_3 = 60 \text{ V}$$

⑤ nodal analysis

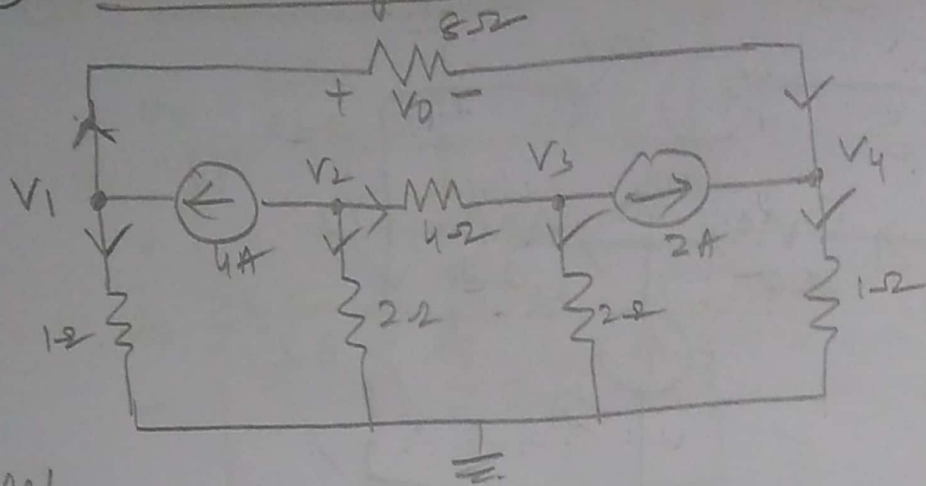

node 1

$$4 = \frac{V_1}{1} + \frac{V_1 - V_4}{8}$$

$$\textcircled{1} \leftarrow 1.125V_1 - 0.125V_4 = 4$$

node 3

$$\frac{V_2 - V_3}{4} = \frac{V_3}{2} + 2$$

$$\textcircled{3} \leftarrow 0.25V_2 - 0.75V_3 = 2$$

node 2

$$4 + \frac{V_2}{2} + \frac{V_2 - V_3}{4} = 0$$

$$0.75V_2 - 0.25V_3 = -4 \rightarrow \textcircled{2}$$

node 4

$$\frac{V_1 - V_4}{8} + 2 = \frac{V_4}{1}$$

$$0.125V_1 - 1.125V_4 = -2 \rightarrow \textcircled{4}$$

Solving ① and ④

we get,

$$V_1 = 3.8 \text{ V}$$

$$V_4 = 2.2 \text{ V}$$


Solving ② and ③

we get,

$$V_2 = -7 \text{ V}$$

$$V_3 = -5 \text{ V}$$

⑥

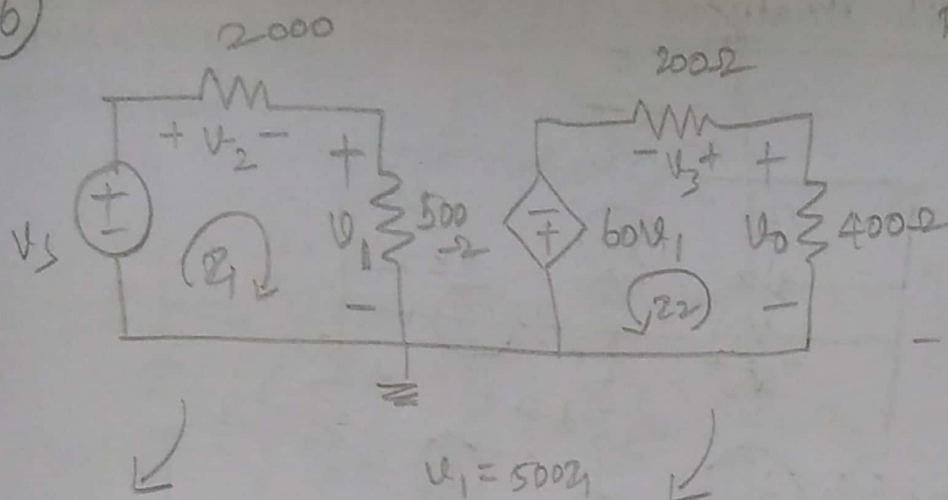

Find $\frac{V_0}{V_s}$

$$-400I_2 = V_0$$

$$I_2 = \frac{-V_0}{400}$$

$$V_1 = 500I_1$$

$$V_s = V_2 + V_1$$

$$V_s = 2000I_1 + 500I_1$$

$$V_s = 2500I_1 \rightarrow \textcircled{1}$$

$$V_0 + 60V_1 = V_3$$

$$V_0 = 200I_2 - 60(500I_1)$$

$$V_0 = 200I_2 - 30000I_1$$

$$V_0 = 200\left(\frac{-V_0}{400}\right) - 30000I_1$$

$$V_0 + \frac{V_0}{2} = 30000I_1$$

$$\frac{3V_0}{2} = 30000I_1$$

$$V_0 = 20000I_1 \rightarrow \textcircled{2}$$

From ①, ②


$$\frac{V_0}{V_s} = \frac{20000I_1}{2500I_1}$$

$$\frac{V_0}{V_s} = 8$$

$$V_0 = 8V_s$$

⑦ Mesh Analysis

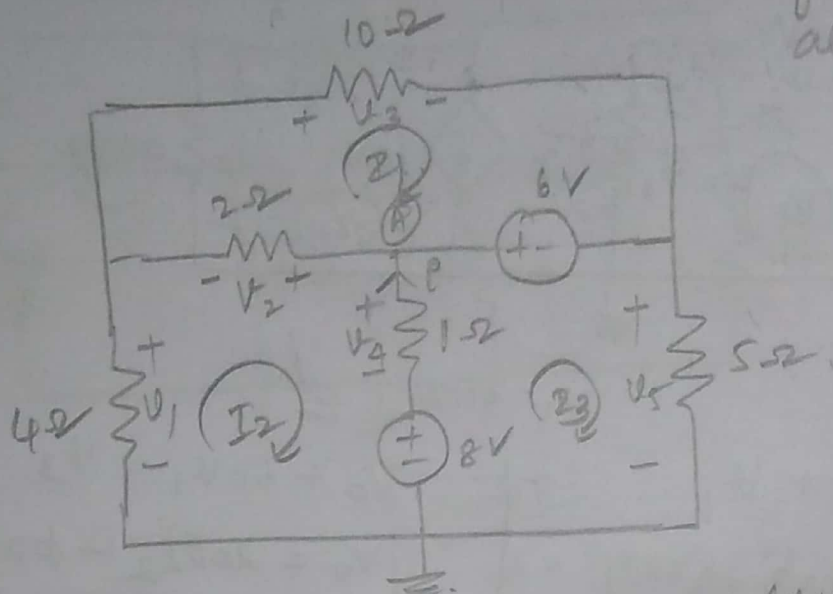Mark polarity of voltages across all element



mesh 2 $\sum \text{Active } V = \sum \text{Passive } V$

$V = IR$ (Active)
 $V = -IR$ (Passive)

$$V_1 + V_2 = V_4 + 8$$

$$-4I_2 - 2(I_2 - I_1) = 1(I_2 - I_3) + 8$$

$$-4I_2 - 2I_2 + 2I_1 - I_2 + I_3 = 8$$

$$2I_1 - 7I_2 + I_3 = 8 \longrightarrow \textcircled{1}$$

mesh 1

$$6 = V_2 + V_3 \Rightarrow 6 = 2(I_1 - I_2) + 10(I_1)$$

$$12I_1 - 2I_2 = 6 \longrightarrow \textcircled{2}$$

mesh 3

$$8 + V_4 = 6 + V_5$$

$$8 - 1(I_3 - I_2) = 6 + 5(I_3)$$

$$8 - 6 = 5I_3 + I_3 - I_2$$

$$2 = 6I_3 - I_2 \longrightarrow \textcircled{3}$$

At node A

$$I_2 + I = I_3$$


$$I = I_3 - I_2$$

$$\boxed{I = 1.1879}$$

solving eqns ①, ②, ③ we get

$$I_1 = 0.329 \quad I_2 = -1.0256, \quad I_3 = 0.1623$$

8

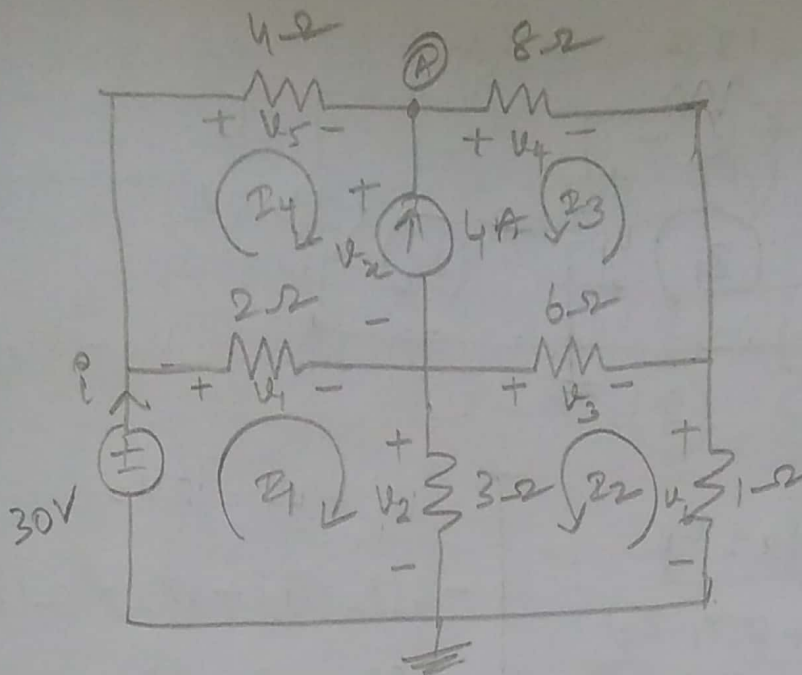

mesh 1

$$30 = V_1 + V_2$$

$$30 = 2(I_1 - I_4) + 3(I_1 + I_2)$$

$$= 2I_1 - 2I_4 + 3I_1 + 3I_2$$

$$5I_1 + 3I_2 - 2I_4 = 30 \rightarrow (1)$$

mesh 2

$$V_6 + V_3 = V_2$$

$$-10I_2 - 6(I_2 - I_3) = 3(I_2 + I_1)$$

$$-I_2 - 6I_2 + 6I_3 = 3I_2 + 3I_1$$

$$3I_1 + 10I_2 - 6I_3 = 0 \rightarrow (2)$$

mesh 3 & mesh 4 (super mesh)

mesh 4

$$V_1 = V_5 + V_x$$

$$-2(I_4 - I_1) = 4I_4 + V_x$$

Sub V_x ,

$$-2I_4 + 2I_1 - 4I_4 + 14I_3 - 6I_2 = 0$$

$$2I_1 - 6I_2 + 14I_3 - 6I_4 = 0 \rightarrow (3)$$

mesh 3

$$V_4 = V_x + V_3$$

$$-8I_3 = V_x + 6(I_3 - I_2)$$



$$V_x = -14I_3 + 6I_2$$

At node (A) $I_3 + I_4 = -4 \rightarrow (4)$

(No need to solve further)

⑩ Superposition, find $i = i_1 + i_2 + i_3$

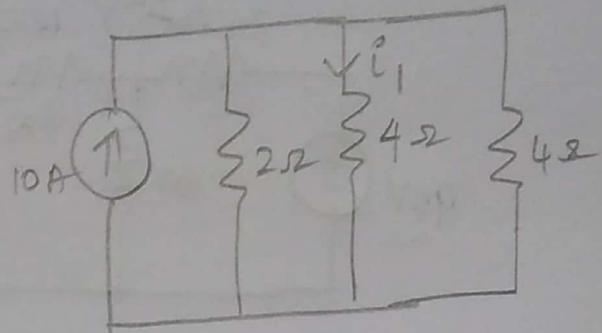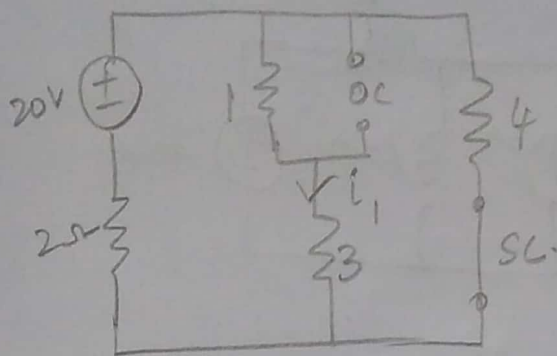
(1) Considering 20V voltage source. (i_1)



Source transformation. $I = \frac{20}{2} = 10A$


$$\frac{2 \times 4}{2+4} = 1.333$$

$$i_1 = 10 \times \frac{1.333}{5.333}$$

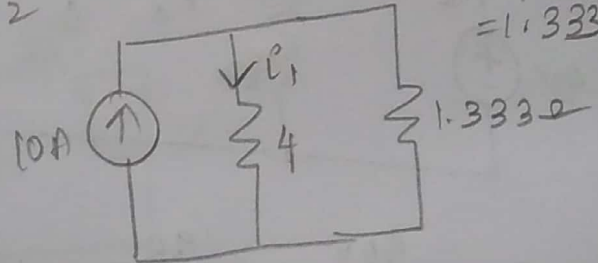

$$i_1 = 2.4995A \approx 2.5A$$

(2) With 16V voltage source (i_2)

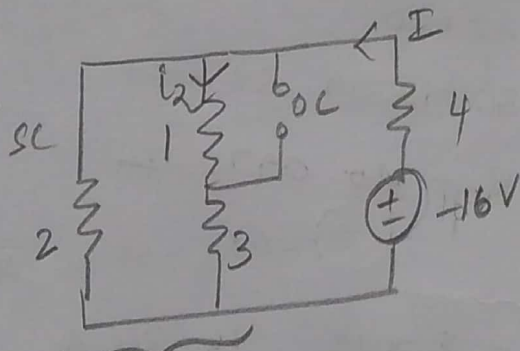


$$R_T = \frac{2 \times 4}{2+4} = 1.333 + 4 = 5.333\Omega \quad I = \frac{-16}{5.333} = -3A$$

By current division $i_2 = -3 \times \frac{2}{2+4}$

$$i_2 = -1A$$

9

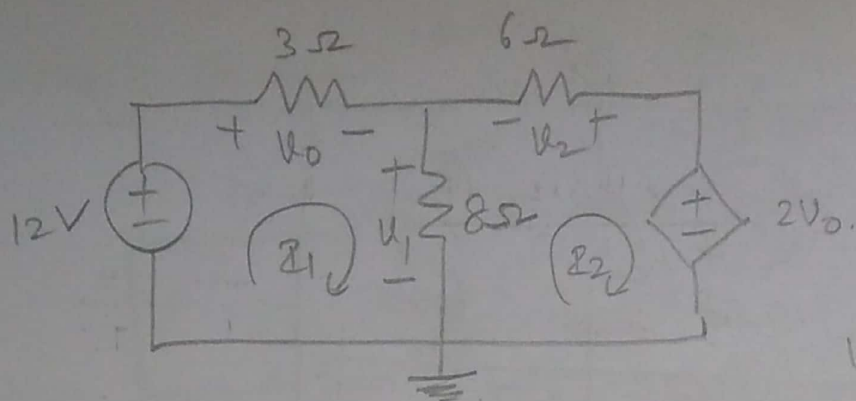

$$U_0 = 3i_1$$

mesh 1

$$12 = U_0 + U_1$$

$$12 = 3i_1 + 8(i_1 - i_2)$$

$$12 = 11i_1 - 8i_2 \rightarrow \textcircled{1}$$

$$11(7i_2) - 8i_2 = 12$$

$$77i_2 - 8i_2 = 12$$

$$69i_2 = 12$$

$$i_2 = 0.1739 \text{ A}$$

$$i_1 = 1.21739 \text{ A}$$

$$U_1 + U_2 = 2V_0$$

$$-8(i_2 - i_1) - 6i_2 = 2(3i_1)$$


$$-8i_2 + 8i_1 - 6i_2 - 6i_1 = 0$$

$$2i_1 - 14i_2 = 0$$

$$i_1 - 7i_2 = 0$$

$$i_1 = 7i_2$$


10. considering 2A current source.

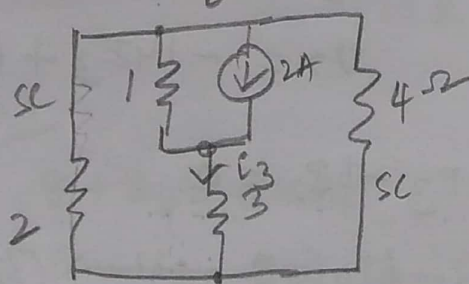

$$i_3 = 0.375 \text{ A}$$

$$\therefore i = 2.5 - 1 + 0.375$$

$$i = 1.875 \text{ A} \checkmark$$


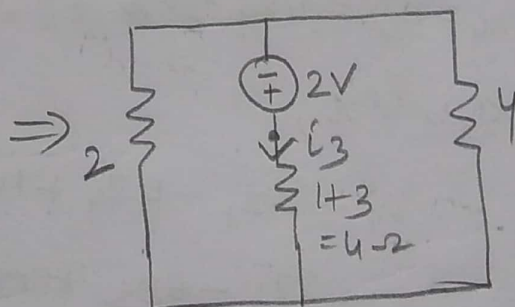


$$R_T = \frac{2 \times 4}{2 + 4} = 1.333 + 4 = 5.333 \Omega$$

$$i = \frac{2}{5.333} = 0.375 \text{ A}$$


11

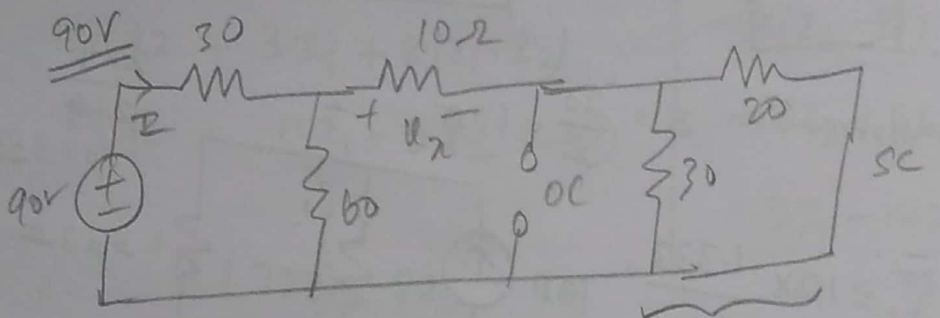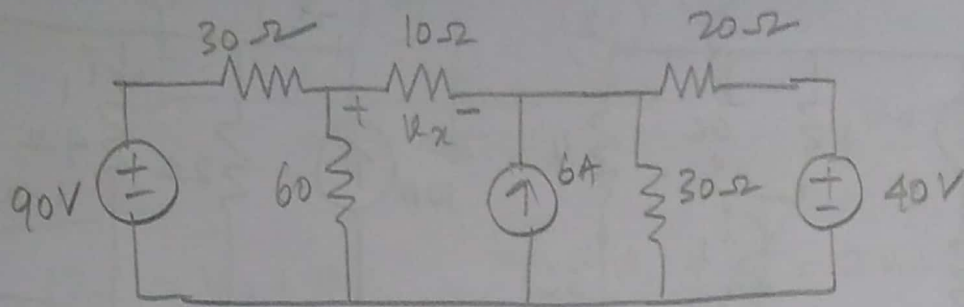Find V_x in the circuit using superposition principle.



$$I = \frac{90V}{R_T} = \frac{90}{46}$$

$$I = 1.9565 A$$

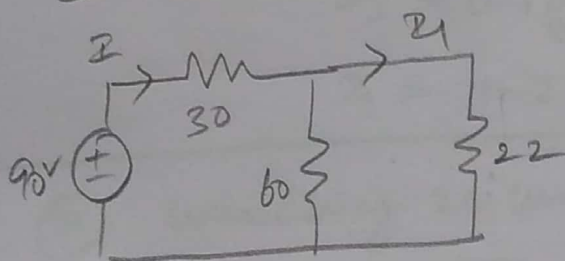

$$I_1 = 1.9565 \times \frac{60}{60+22}$$

$$I_1 = 1.4316 A$$

$$\frac{20 \times 30}{20+30} = 12 \Omega$$

$$12, 10 \Omega \text{ series } R = 22 \Omega$$


$$22, 60 \text{ parallel}$$

$$\frac{22 \times 60}{22+60} = 16.0975 \Omega$$

$$30, 16.09 \text{ series}$$

$$R_T = 46.0975 \Omega$$
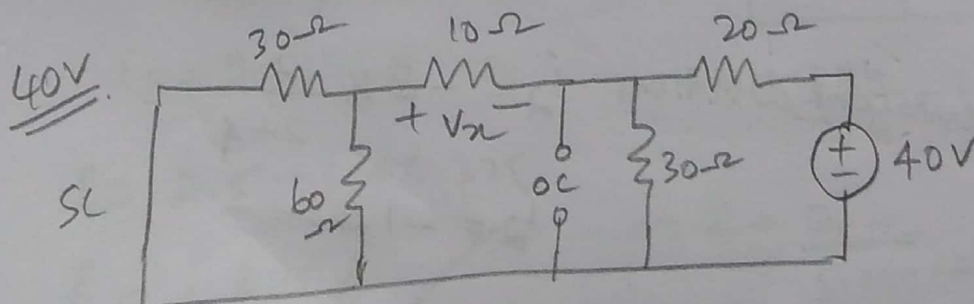
$$\therefore V_x = I_1 \times 10 = 14.316 A$$




30, 60 parallel $R = 20\Omega$

20, 10 series $R = 30\Omega$

30, 30 parallel $R = 15\Omega$



20, 15 series $R_T = 35\Omega$

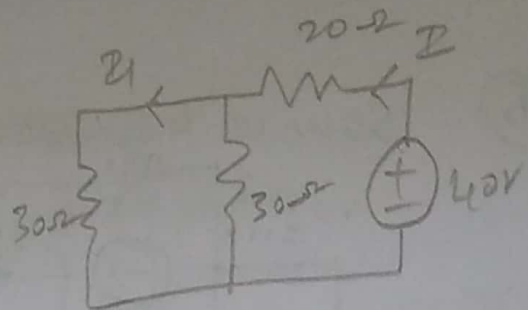

$$I = \frac{40}{35} = 1.1428$$

$$I_1 = \frac{1.1428}{2} = 0.5714 \text{ A}$$
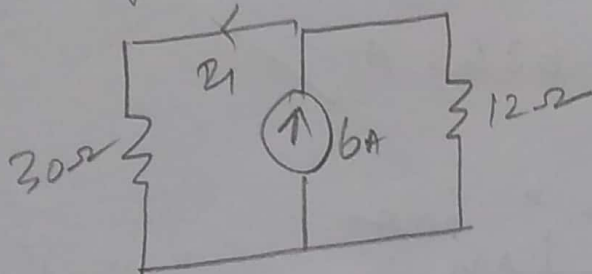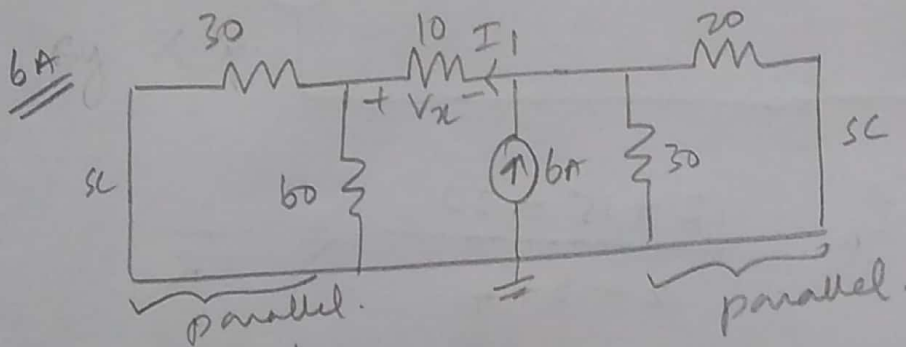
$$V_n = -10 \times 0.5714 = -5.714 \text{ V}$$



$$I_1 = 6 \times \frac{12}{30+12}$$

$$I_1 = 1.714 \text{ A}$$

$$V_n = -10 \times I_1$$

$$V_n = -17.143 \text{ V}$$


By superposition.

$$V_n = 14.316 - 5.714 - 17.143$$


$$V_n = -8.541 \text{ V}$$

12

Source transformation $i_0 = ?$

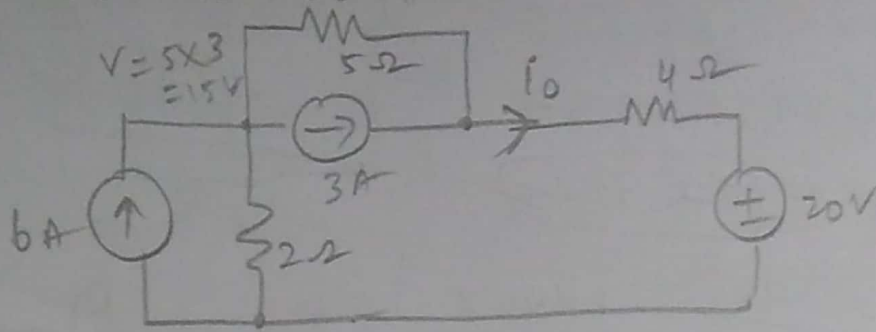


$$V = 6 \times 2 = 12$$

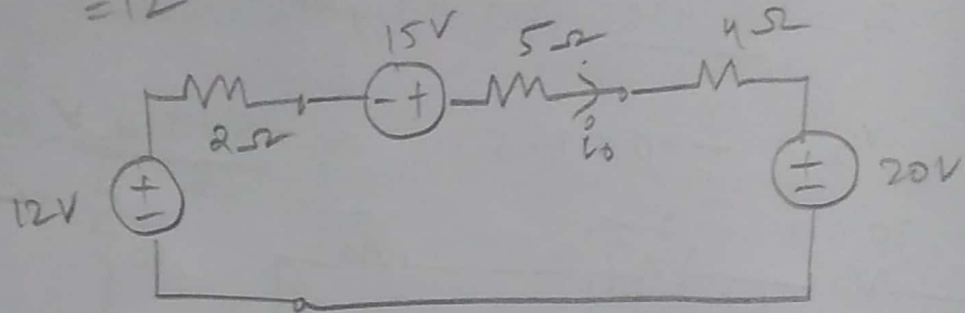

$$i_0 = \frac{12 + 15 - 20}{2 + 5 + 4} \leftarrow \frac{V}{R}$$


$$i_0 = 0.6363 \text{ A} \checkmark$$


13

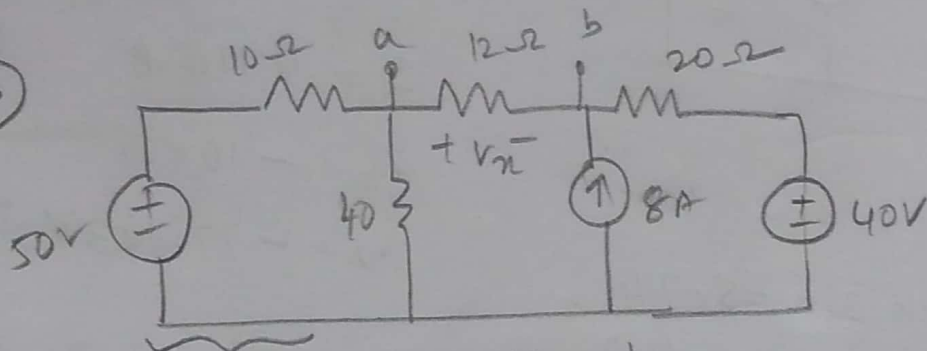


Find v_x
Source transformation

$$Z = \frac{V}{R}$$

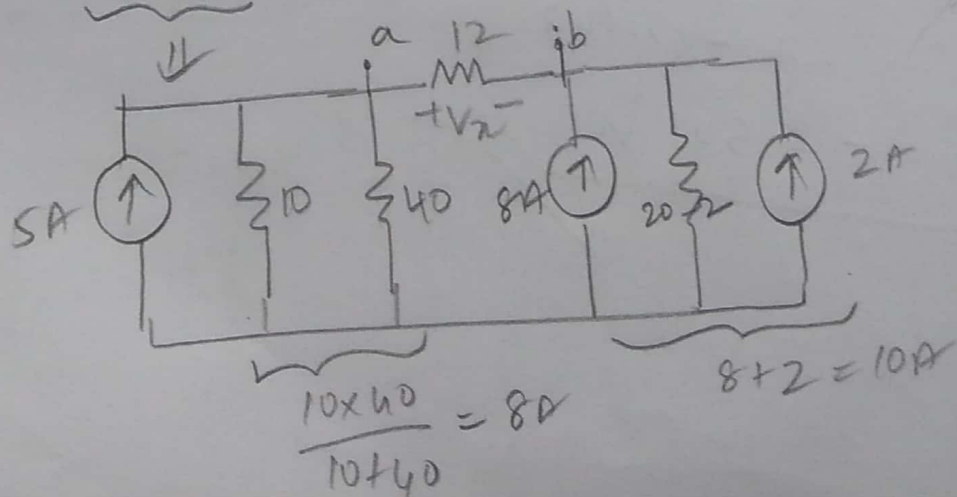

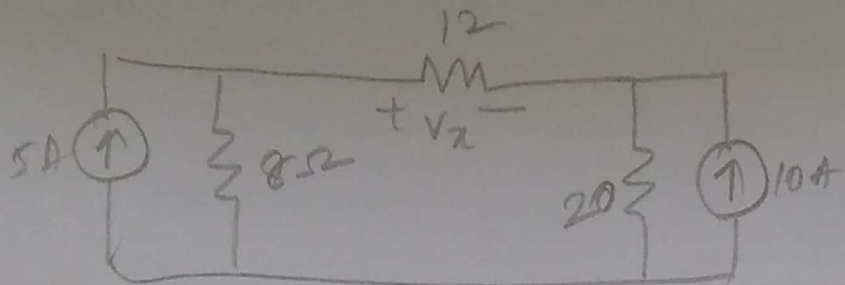

$$V = 10 \times 2 = 20V$$

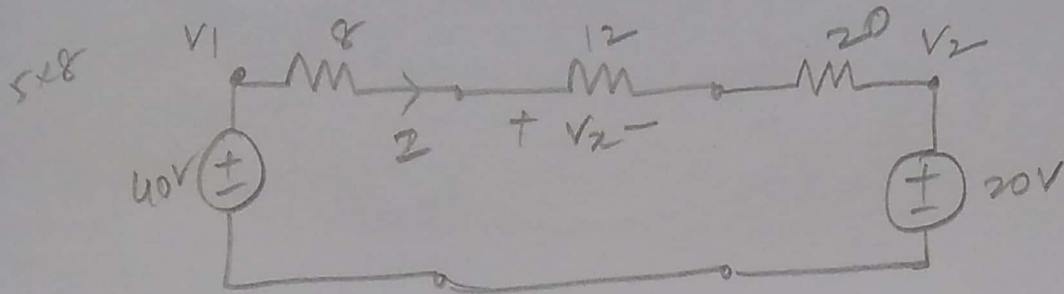


$$I = \frac{40 - 20}{20 + 8 + 12} = \frac{20}{40} A = 0.5A$$


$$V_n = 12 \times \frac{20}{40} = 6V$$

Ans
-48V

(14) Thevenin voltage

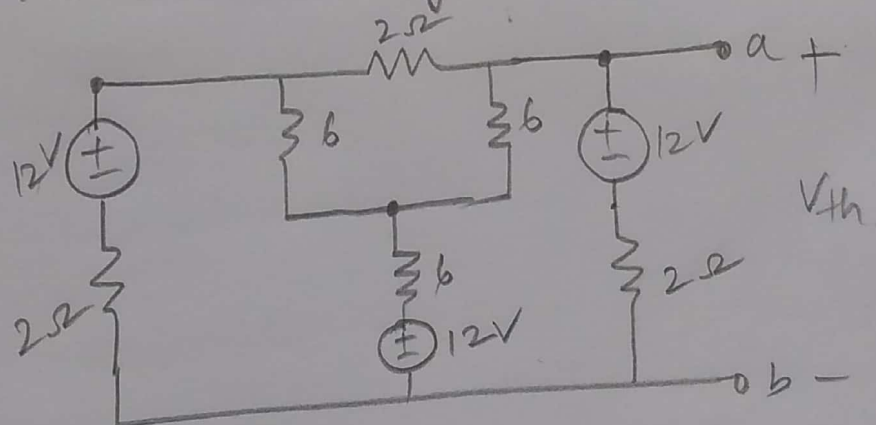

Using superposition

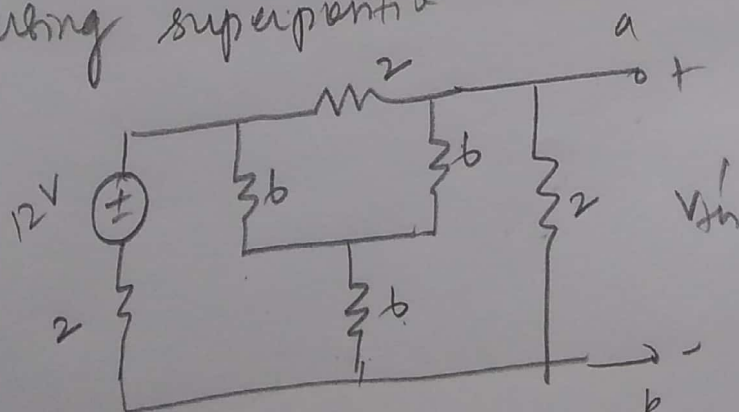

(need star delta transformation)

Ans
1.452
9.6V
8A