
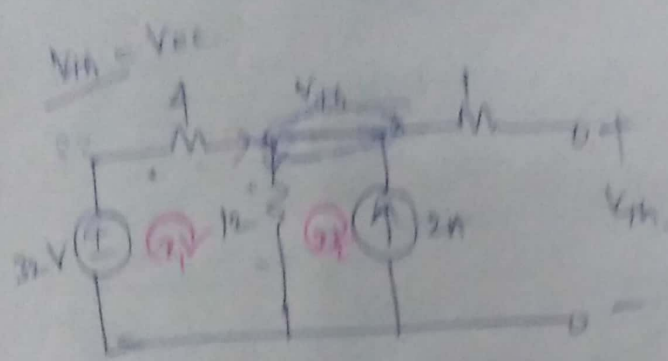


(4V)

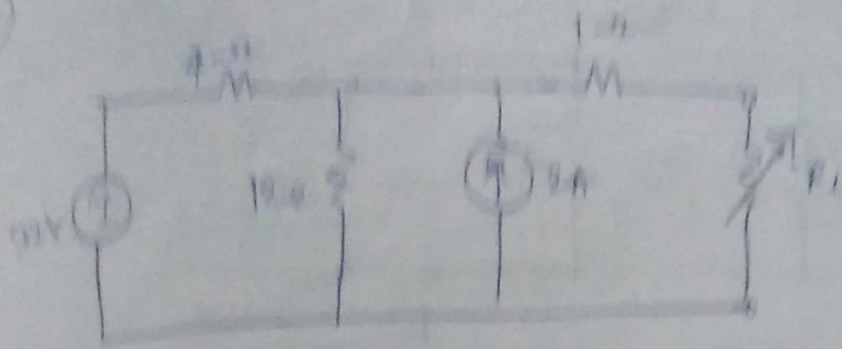

$$4I_1 + 12(I_1 - I_2) = 32$$

$$I_2 = -2$$

$$4I_1 + 12I_1 + 24 = 32$$

$$16I_1 = 8$$

$$I_1 = \frac{8}{16} = 0.5 \text{ A}$$

Using nodal analysis

$$V_{th} = 12(I_1 - I_2)$$


$$= 12 \times (0.5 + 2)$$

$$V_{th} = 30 \text{ V}$$

$$\frac{32 - V_{th}}{4} + 2 = \frac{V_{th}}{12}$$


Solving $V_{th} = 30 \text{ V}$

R_{th}

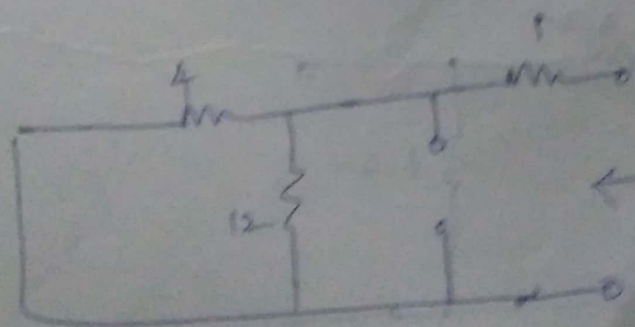

$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2}$$
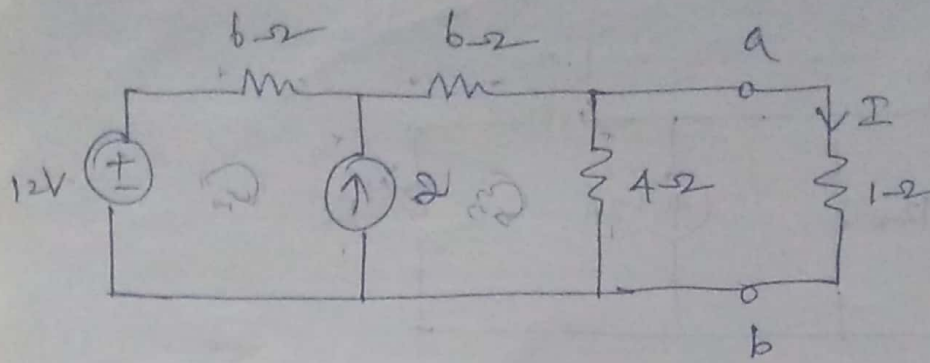
$$R_{th} = 1 \parallel 12(4) = 4 \Omega$$





$$V_{th} = 6V$$

$$R_{th} = 3\Omega$$

$$I = 1.5A$$

Norton's equivalent


(4.11)

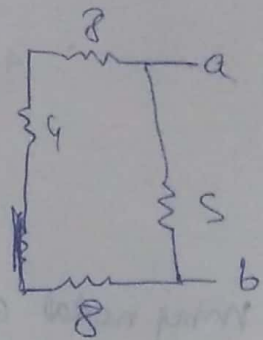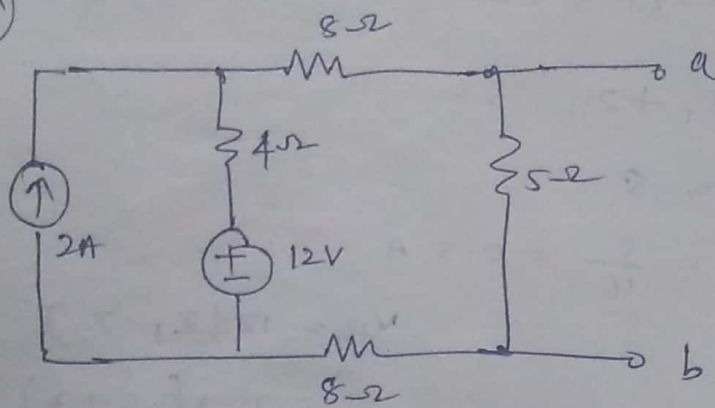

$$R_N = 4\Omega$$



$$I_N = 1A$$

$$V_{th} = 4V$$

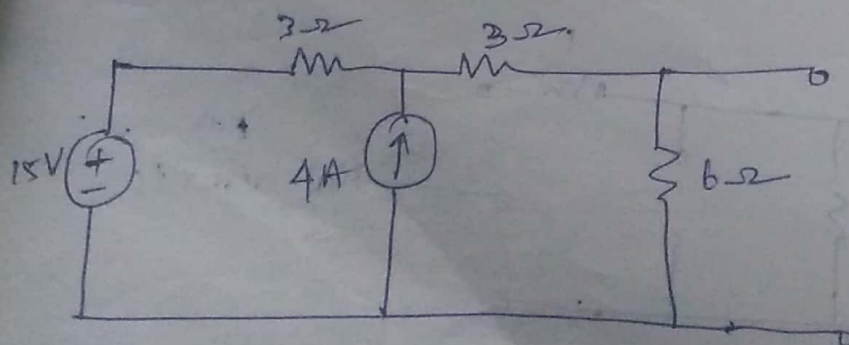

$$R_N = 3\Omega \quad I_N = 4.5A$$

Newton's Equivalent

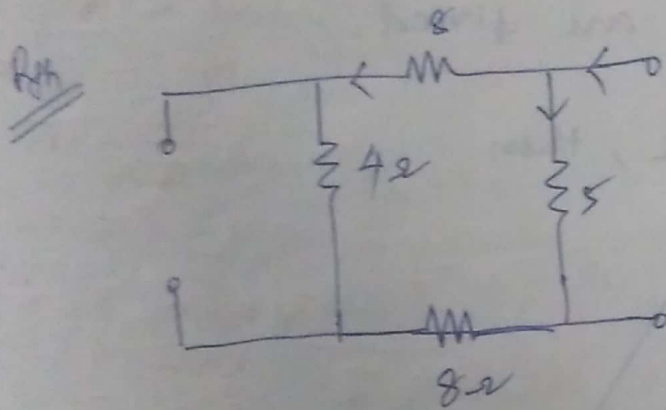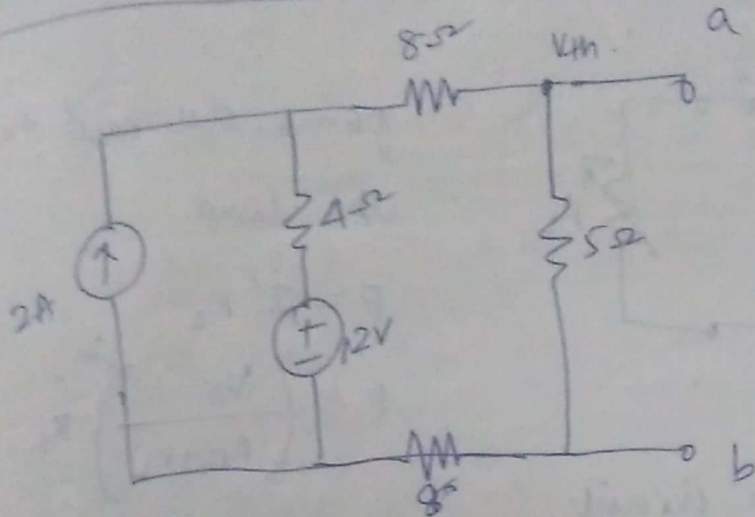


$$R_{th} = 20 \parallel 5$$

$$= \frac{20 \times 5}{20 + 5}$$

$$= \frac{100}{25} = 4 \Omega$$

$$= \underline{\underline{30 \Omega}}$$

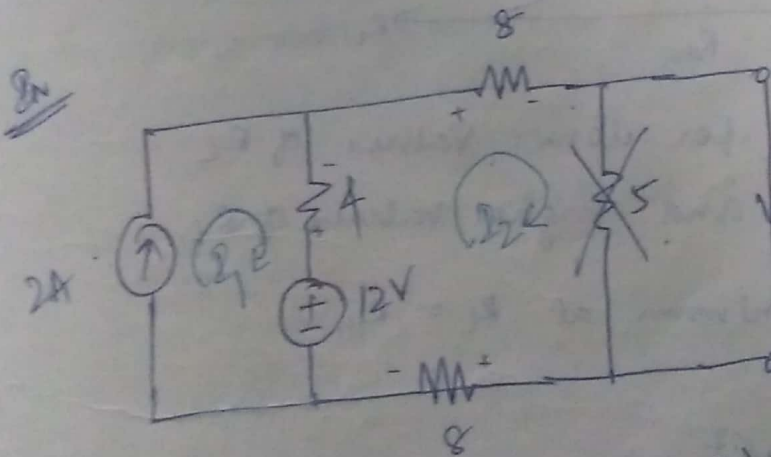

$$R_{sc} = 2 \Omega$$

$$I_1 = 2A$$

$$I_N = 1A$$

$$V_{th} =$$


$$4(I_2 - I_1) + 8I_2 + 8I_2 = 12$$

$$4, 20I_2 - 4I_1 = 12$$

$$20I_2 = 12 + 8 = 20$$

$$I_2 = 1A$$

Maximum power Transfer

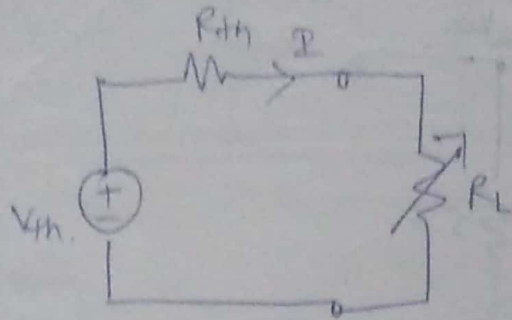

power delivered to the load


$$P = I^2 R_L$$

$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

For a given circuit,

V_{th} , R_{th} are fixed.

If we vary R_L , then

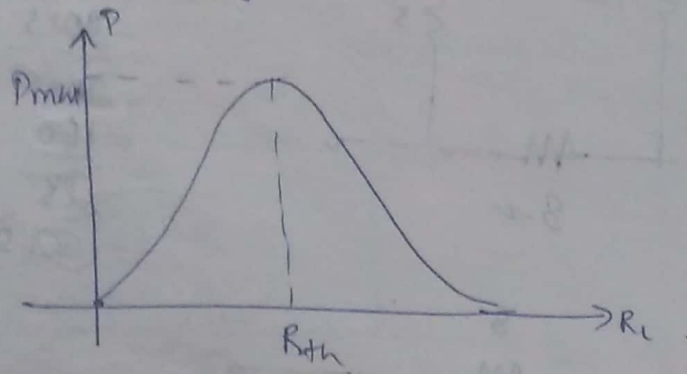

Let $V_{th} = 15V$

$R_{th} = 5\Omega$ $R_L = 10\Omega$

$$I = \frac{V_{th}}{R_{th} + R_L} = 1A$$

$$P_L = I^2 R_L = 5W$$

If $R_L = 0$ $P = 0$

$R_L = 2$ $P = 2$

$R_L = 5$ $P =$

P = low for lower values of R_L

and higher values of R_L

= maximum at $R_L = R_{th}$.

$$\frac{dP}{dR_L} = 0$$

$$\frac{d}{dR_L} \left[\frac{V_{th}^2 R_L}{(R_{th} + R_L)^2} \right] = 0$$

$$V_{th}^2 \left[\frac{(R_{th} + R_L)^2 (1) - R_L 2(R_{th} + R_L)}{(R_{th} + R_L)^4} \right] = 0$$

$$\frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4} = 0$$

$$\frac{(R_{th} + R_L)(R_{th} + R_L - 2R_L)}{(R_{th} + R_L)^4} = 0$$

$$\frac{(R_{th} + R_L)(R_{th} - R_L)}{(R_{th} + R_L)^4} = 0$$

$$R_{th} - R_L = 0$$

$$\frac{R_{th} - R_L}{(R_{th} + R_L)^3} = 0$$

$$R_{th} - R_L = 0$$

$$R_{th} = R_L$$

∴ max power transfer occurs when $R_{th} = R_L$


Source Impedance = load resistance

max power at that point is

$$P_{max} = \frac{V_{th}^2}{(R_{th} + R_{th})^2} R_{th}$$



$$= \frac{V_{th}^2}{4R_{th}^2} \times R_{th}$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

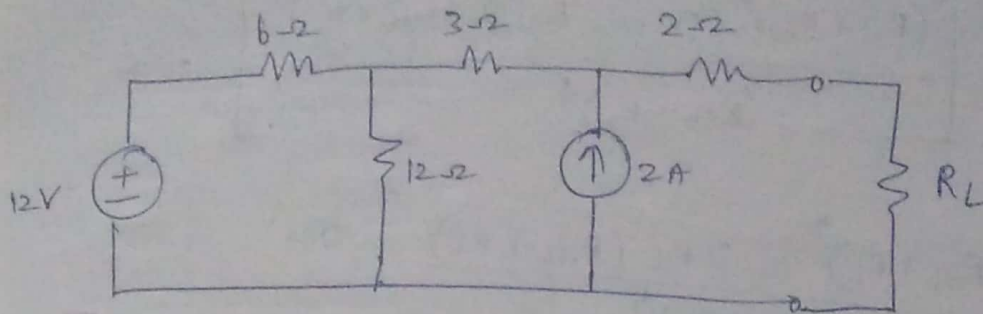

$$\underline{R_{th}} = \frac{V_{oc}}{I_{sc}}$$

$$\underline{V_{oc} = V_{th}}$$

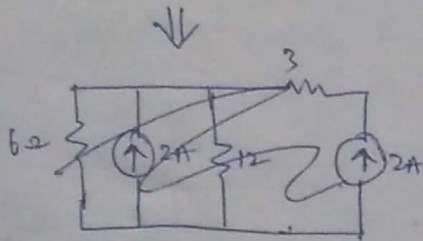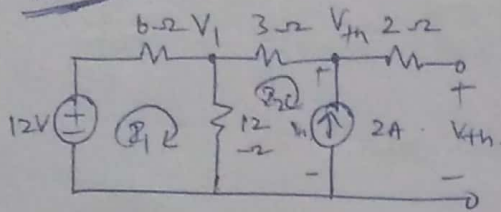

$$I_2 = -2A$$

$$12 = 6I_1 + 12(I_1 - I_2)$$

$$12 = 6I_1 + 12I_1 + 24$$

$$18I_1 = -12$$

$$I_1 = -\frac{2}{3}$$

$$V_1 = 12(I_1 - I_2)$$

$$= 12\left(-\frac{2}{3} + 2\right)$$


$$= 12\left(\frac{6-2}{3}\right)$$

$$= 4 \times 12 \times \frac{4}{3}$$

$$V_1 = 16$$

$$V_3 = I_2 \times 3 = -2 \times 3 = -6$$

$$V_{th} = V_3 = V$$

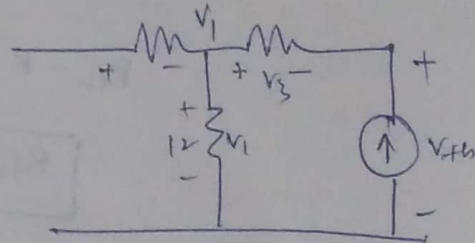


$$-V_1 + V_3 + V_{th} = 0$$

$$V_{th} = V_1 - V_3$$

$$= 16 - (-6)$$



$$\underline{V_{th} = 22}$$

$$\therefore R_{th} = R_L =$$

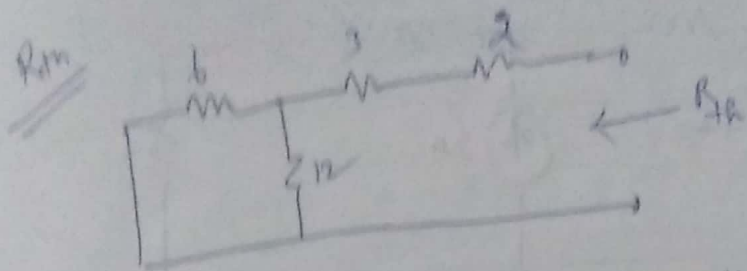

$$R_{th} = (6 \parallel 12) + 6 = \frac{6 \times 12}{6 + 12} + 6 = \frac{8 \times 12}{18} + 6 = \frac{16}{3} + 6 = 9.2$$

$R_{th} = 9.2$

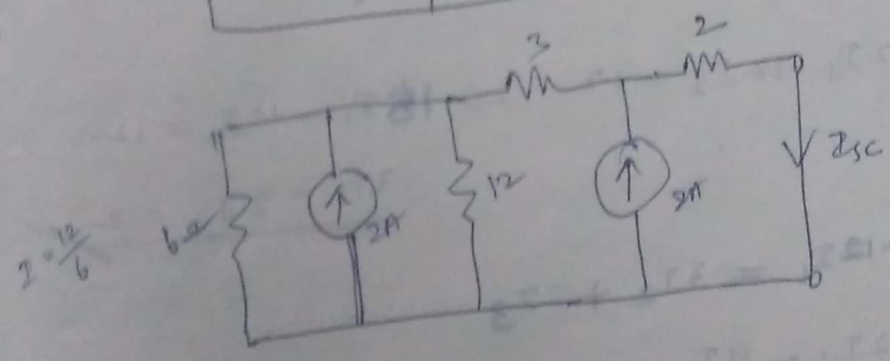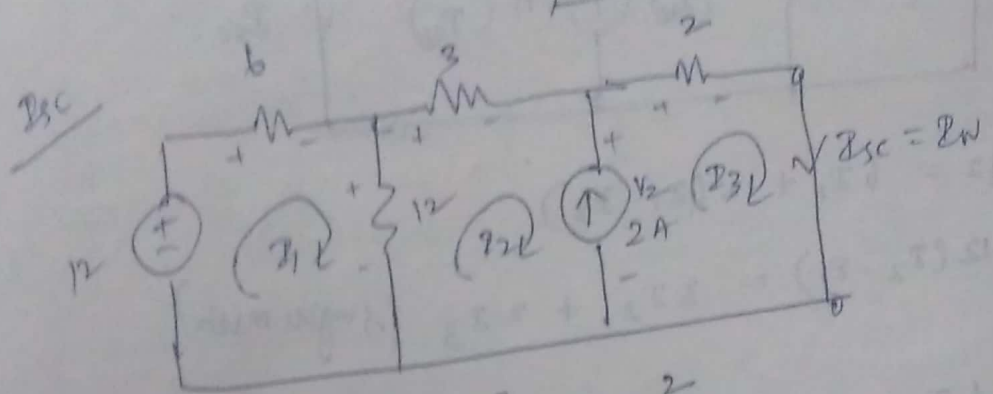

$I = \frac{12}{6}$

$$-12 + 6I_1 + 12(I_1 - I_2) = 0$$

$$18I_1 - 12I_2 = 12$$

$$3I_1 - 2I_2 = 2 \quad \text{--- (1)}$$

$$-12(I_2 - I_1) + 3I_2 + V_2 = 0$$

$$-V_2 + 2I_3 = 0$$

$$V_2 = 2I_3$$

$$-12(I_2 - I_1) + 3I_2 + 2I_3 = 0$$

$$-12I_2 + 12I_1 + 3I_2 + 4 + 2I_2 = 0$$

$$+12I_1 - 7I_2 = -4$$

$$-12I_1 - 5I_2 = 0$$

$$12I_1 - 8I_2 = 8$$

$$-12I_1 - 5I_2 = 0$$

$$-13I_2 = 8$$

$$I_2 = -\frac{8}{13}$$

$$I_3 = 2 + I_2$$



$$= 2 - \frac{8}{13}$$

$$= \frac{26 - 8}{13}$$

$$= \frac{18}{13}$$

$$I_3 - I_2 = 2A$$

$$I_3 = 2 + I_2$$

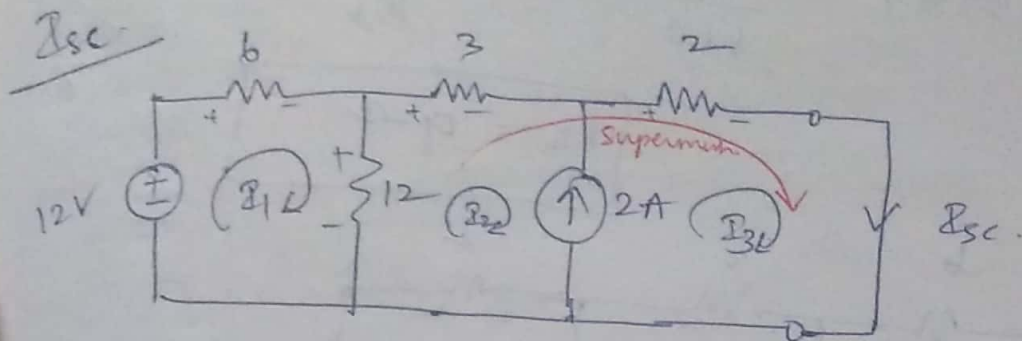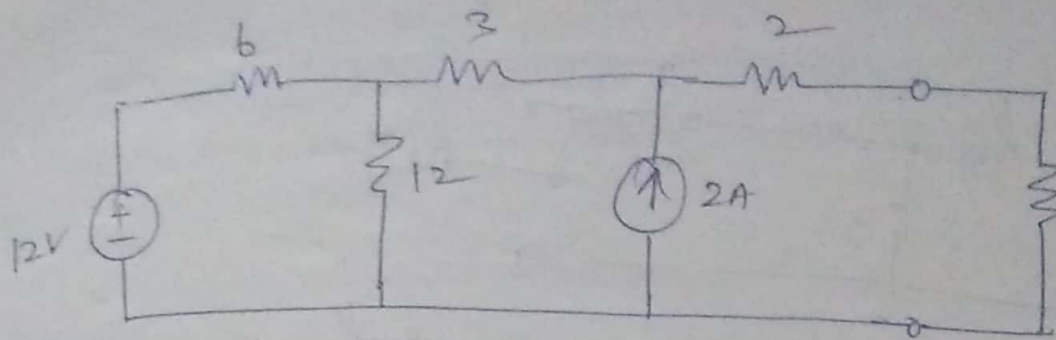

$$12 = 6I_1 + 12(I_1 - I_2)$$

$$12(I_2 - I_1) = 3I_2 + 2I_3 \quad (\text{super mesh})$$

$$\textcircled{1} \quad 6I_1 + 12I_1 - 12I_2 = 12 \Rightarrow 18I_1 - 12I_2 = 12$$

$$3I_1 - 2I_2 = 2$$

$$\textcircled{2} \quad 12I_2 - 12I_1 = 3I_2 + 2I_3$$

$$+12I_1 - 9I_2 + 2I_3 = 0$$

$$\textcircled{3} \quad I_3 - I_2 = 2 \Rightarrow I_3 = 2 + I_2$$

$$\textcircled{2} \Rightarrow 12I_1 - 9I_2 + 2(2 + I_2) = 0$$

$$12I_1 - 9I_2 + 4 + 2I_2 = 0$$

$$12I_1 - 7I_2 = -4$$

$$\therefore I_3 = -10$$

$$12I_1 - 8I_2 = 8$$

$$12I_1 - 7I_2 = -4$$


$$-I_2 = 12$$

$$I_2 = -12$$

When $V_L = \frac{V_S}{2}$

$$R_S = R_L$$

Internal resistance can be found.

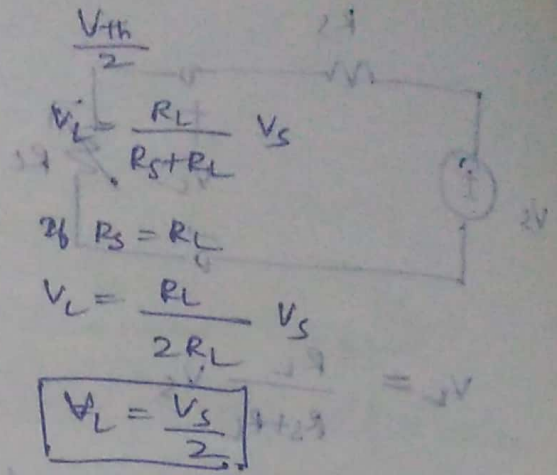

Problems

4.16 The terminal voltage of a voltage source is 12V when connected to a 2-W load. When the load is disconnected, the terminal voltage rises to 12.4V.

(a) calculate the source voltage V_S

and internal resistance R_S

(b) Determine the voltage when an 8- Ω load is connected to the source.

Soln


$$V_{OC} = 12.4 \text{ V} = V_{th} = V_S$$

When loaded (2W) $V_L = 12 \text{ V}$

$$P_L = 2 \text{ W}$$

$$P_L = \frac{V_L^2}{R_L}$$

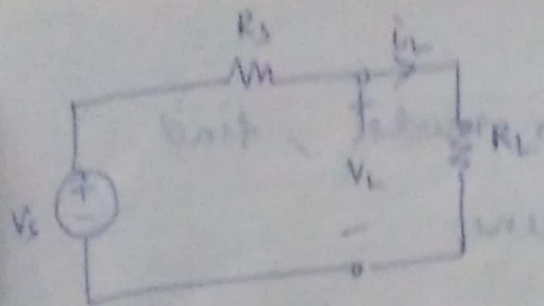
$$\therefore R_L = \frac{12^2}{2} = 72 \Omega$$



$$I_L = \frac{V_L}{R_L} = \frac{12}{6} = 2 \text{ A}$$

$$V_s = V_L = R_s I_L$$
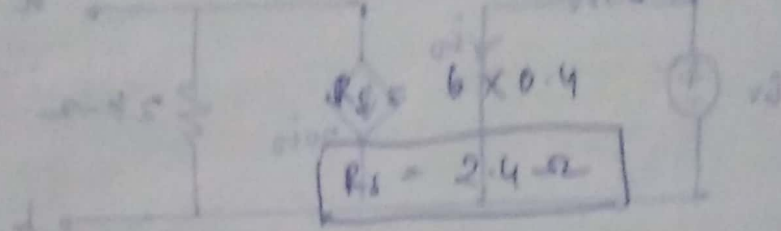
$$12.4 - 12 = R_s \left(\frac{1}{6} \right)$$



(b) When $R_L = 8 \Omega$

$$V_L = \frac{R_L}{R_s + R_L} V_s$$

$$V_L = \frac{8}{8 + 2.4} \times 12.4$$

$$V_L = 9.538 \text{ V}$$

4.16 The measured DC voltage across a certain amplifier is 9V. The voltage drops to 8V when a 20Ω loadspeaker is connected to the amplifier. Calculate the voltage when a 10Ω loadspeaker is instead.

$$V_{th} = V_{oc} = V_s = 9 \text{ V} \quad \text{When } R_L = 20 \Omega$$

$$V_L = \frac{R_L}{R_s + R_L} V_s \Rightarrow \frac{20}{20 + R_s} (9) = 8$$

\therefore When $R_L = 10 \Omega$

$$V_L = \frac{10}{25 + 10} \times 9$$

$$V_L = 7.2 \text{ V}$$

$$180 = 160 + 8 R_s$$

$$8 R_s = 20$$

$$R_s = \frac{20}{8} = 2.5$$

$$R_s = 2.5 \Omega$$