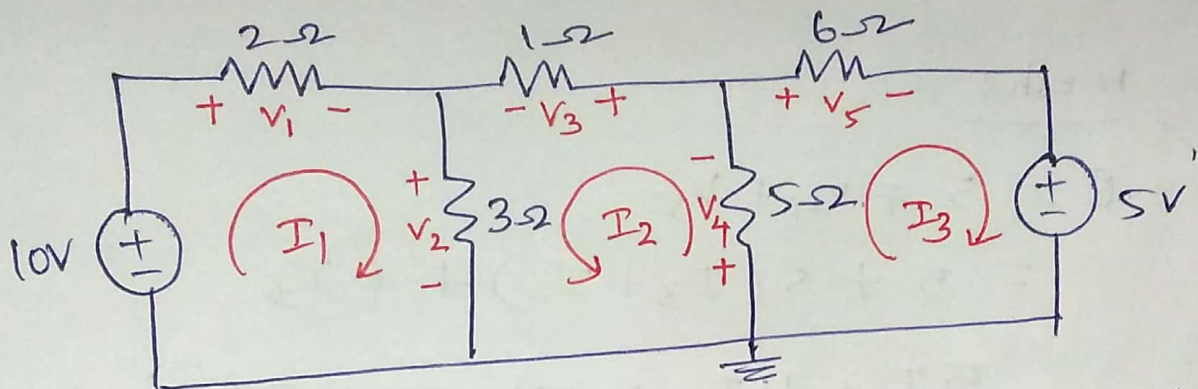


MESH ANALYSIS

- Identify mesh currents and solve using KVL & OHMS LAW.
- I is variable to be found.



Nodes = 5 Branches = 7 loops = $b - n + 1 = 3$.

Assign polarity for voltage across all branches and name them.

mesh 1

ACTIVE $V =$ PASSIVE V

$$10 = V_1 + V_2$$

$$10 = 2I_1 + 3(I_1 + I_2)$$

$$10 = 5I_1 + 3I_2 \longrightarrow \textcircled{1}$$

$\xrightarrow{+} \text{---} V_1 \text{---} \leftarrow$ (V = IR.)
PASSIVE

$\xleftarrow{-} \text{---} V_1 \text{---} \rightarrow$ (V = -IR) ACTIVE.

②

mesh 2

$$0 = V_3 + V_2 + V_4.$$

$$0 = I_2(1) + 3(I_2 + I_1) + 5(I_2 + I_3)$$

$$0 = I_2 + 3I_2 + 3I_1 + 5I_2 + 5I_3.$$

$$3I_1 + 9I_2 + 5I_3 = 0 \longrightarrow \textcircled{2}.$$

mesh 3

$$0 = 5 + V_4 + V_5$$

$$= 5 + 5(I_3 + I_2) + 6I_3$$

$$5I_2 + 11I_3 = -5 \longrightarrow \textcircled{3}$$

Solution.

$$\begin{bmatrix} 5 & 3 & 0 \\ 3 & 9 & 5 \\ 0 & 5 & 11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -5 \end{bmatrix}$$

$$\cancel{I_1 = 2.76} \quad \cancel{I_2 = -1.27} \quad \cancel{I_3 = 0.124}$$

$$V_2 = 3(I_2 + I_1)$$

$$V_2 = \cancel{4.1147} \cdot \underline{5.091}$$


$$V_4 = + 5(I_2 + I_3)$$

$$V_4 = \cancel{2.114788} \cdot \underline{2.601} \\ = 4.335$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2.453 \\ -0.756 \\ -0.111 \end{bmatrix}$$

③

②

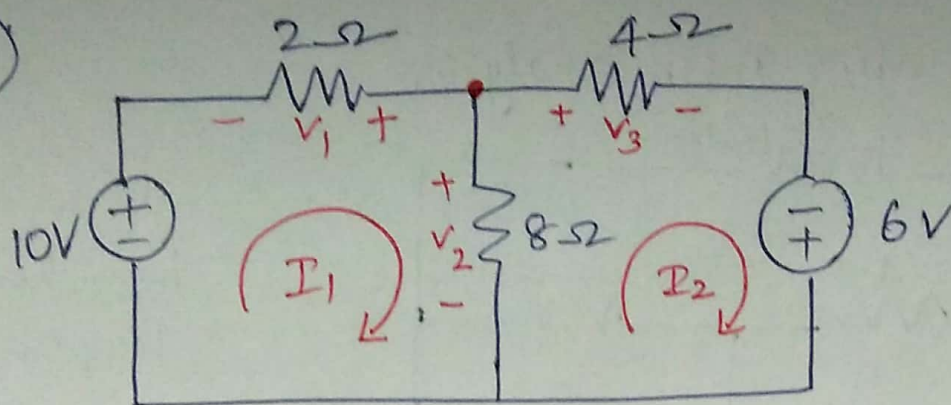

$$\text{nodes} = 4 \quad \text{branches} = 5 \quad \text{loops} = 5 - 4 + 1 = 2$$

mesh 1

Active = Passive.

$$10 + V_1 = V_2$$

$$10 - 2I_1 = 8(I_1 - I_2)$$

$$10 = 10I_1 - 8I_2 \rightarrow \textcircled{1}$$

mesh 2

Active V = Passive V

$$V_2 + 6 = V_3$$

$$-8(I_2 - I_1) + 6 = 4I_2$$

$$8I_1 - 12I_2 = -6$$

$$4I_1 - 6I_2 = -3 \rightarrow \textcircled{2}$$

Solving $\textcircled{1}$, $\textcircled{2}$ we get,

$$\begin{array}{r} 40I_1 - 38I_2 = 40 \\ 40I_1 - 60I_2 = -30 \\ \hline \end{array}$$

$$28I_2 = 70$$

$$I_2 = 2.5 \text{ A}$$

$$\text{then } I_1 = \frac{10 + 8I_2}{10}$$


$$I_1 = 3 \text{ A}$$

$$V_2 = 8(I_1 - I_2)$$

$$V_2 = 4 \text{ V}$$

Other voltages and branch currents can be found using I_1 & I_2 .

③ Find I_0 using mesh analysis.

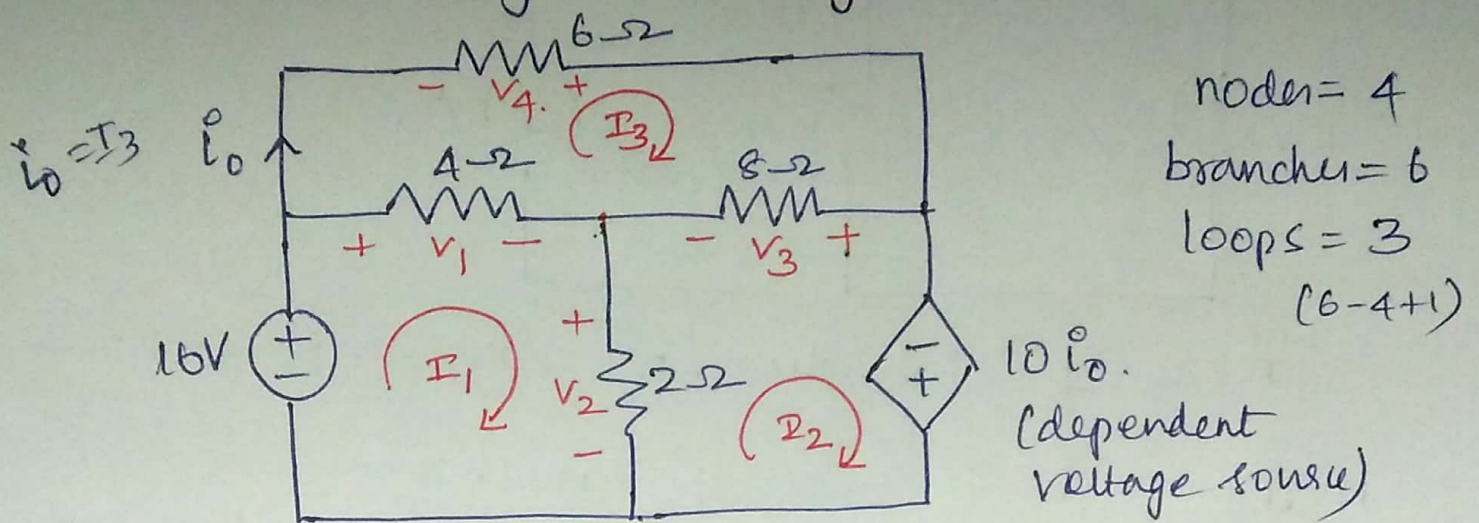

mesh 1 Active voltage = Passive voltage.

$$16 = V_1 + V_2$$

$$\begin{aligned} 16 &= 4(I_1 - I_3) + 2(I_1 - I_2) \\ &= 4I_1 - 4I_3 + 2I_1 - 2I_2 \\ 16 &= 6I_1 - 2I_2 - 4I_3 \end{aligned}$$

mesh 2

$$V_2 + V_3 + 10I_0 = 0$$

$$-2(I_2 - I_1) + 8(I_2 - I_3) + 10I_3 = 0$$

$$2I_1 - 10I_2 + 18I_3 = 0$$

mesh 3

$$V_1 + V_4 = V_3$$

$$\begin{aligned} -4(I_3 - I_1) + 6(I_3) &= 8(I_3 - I_2) \\ -4I_3 + 4I_1 - 6I_3 - 8I_3 + 8I_2 &= 0 \\ 4I_1 + 8I_2 - 18I_3 &= 0 \end{aligned}$$

Solving the equations.

$$\begin{bmatrix} 6 & -2 & -4 \\ 2 & -10 & 18 \\ 4 & 8 & -18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 16 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -2.57 \\ -7.71 \\ -4 \end{bmatrix}$$

$$I_0 = \underline{\underline{-4A}}$$