

BEEE101L – Basic Electrical Engineering

Maximum Power Transfer Theorem



VIT[®]

Vellore Institute of Technology

(Deemed to be University under section 3 of UGC Act, 1956)




Objective

- To introduce Thevenin's theorem.
- To apply Thevenin's theorem to solve electric circuits and formulate condition for maximum power transfer.


Thevenin's Theorem:

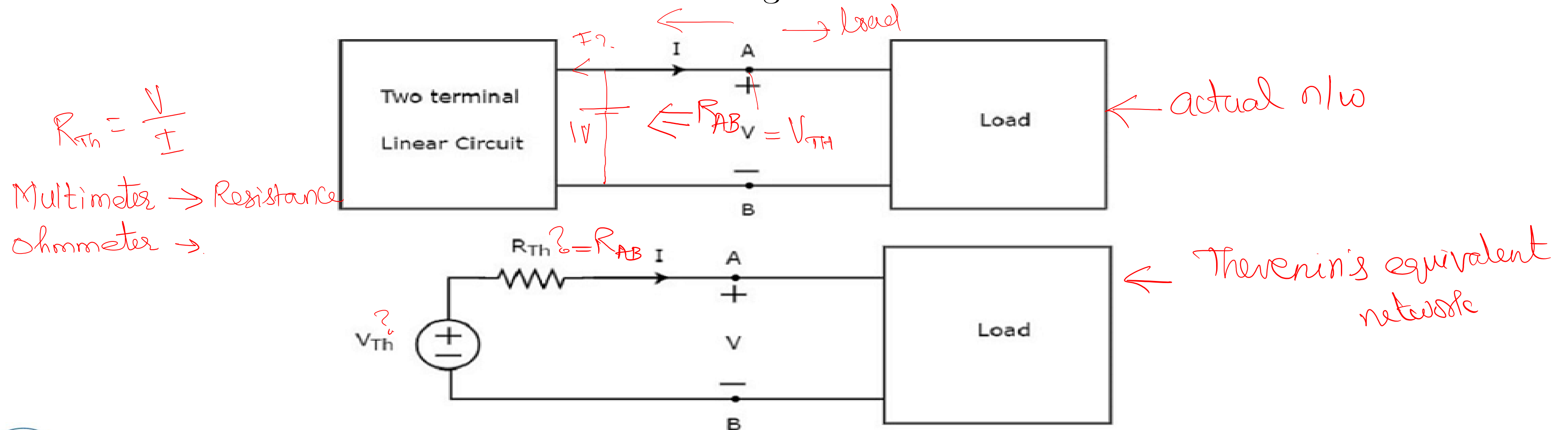- Any linear active network consisting of independent or dependent voltage and current source and the network elements can be replaced by an equivalent circuit having a voltage source in series with a resistance.
 - Where the voltage source being the open-circuited voltage across the open-circuited load terminals and the resistance being the internal resistance of the source.



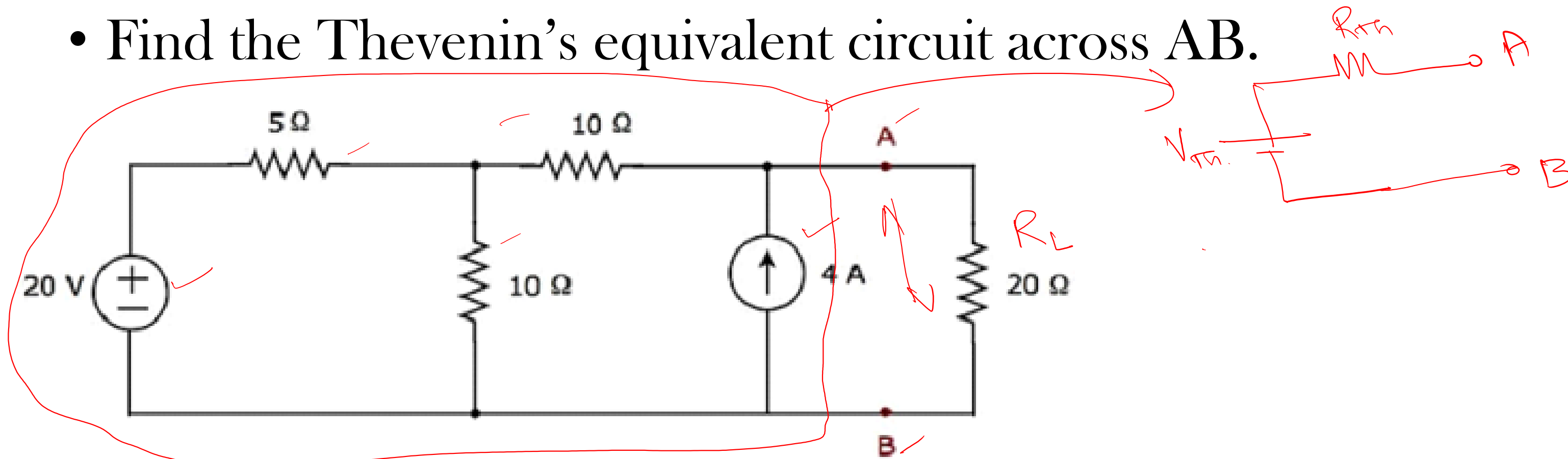Example:


- Find the Thevenin's equivalent circuit across AB.




- The solution has 3 steps:
 - To find Thevenin equivalent resistance (R_{TH}).
 - To find open circuit voltage across terminals AB.
 - Draw the equivalent circuit

Simplifying the circuit to find R_{TH} :

① Disconnect the load resistance R_L :

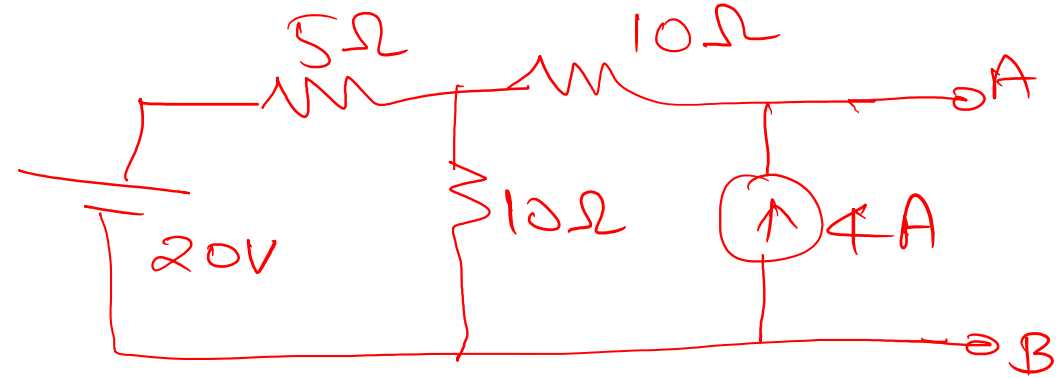

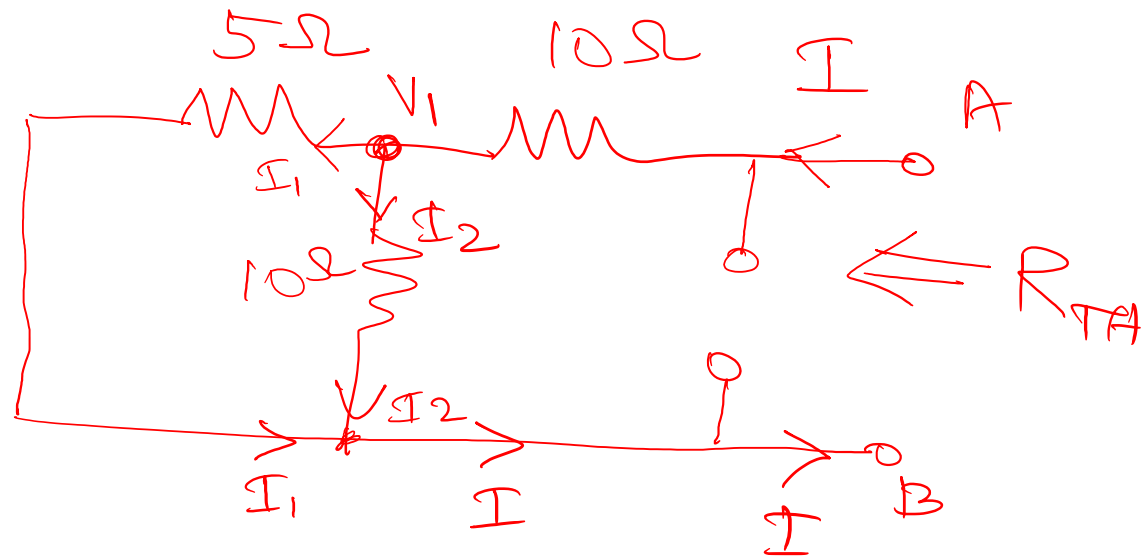② Short circuit the voltage source and open circuit the current source and find the equivalent resistance.




$$\begin{aligned} R_{TH} &= 10 + (10 \parallel 5) \\ &= 10 + \frac{10 \times 5}{10 + 5} \\ &= 10 + \frac{50}{15} \end{aligned}$$

$$\boxed{R_{TH} = 13.33 \Omega}$$

Simplifying the circuit to find R_{TH} :

To find V_{TH} :

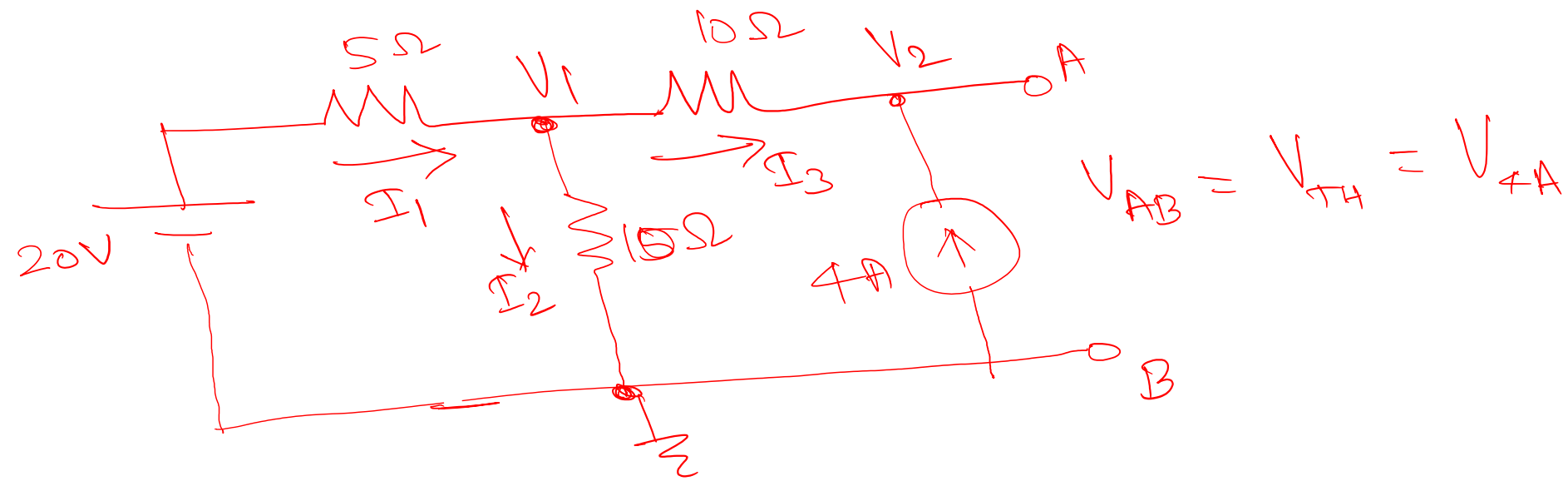

Applying KCL at node 1, we have

$$I_1 = I_2 + I_3$$

$$\frac{20 - V_1}{5} = \frac{V_1}{10} + \frac{V_1 - V_{TH}}{10}$$

$$4 = \left[\frac{1}{5} + \frac{1}{10} + \frac{1}{10} \right] V_1 - \frac{1}{10} V_{TH} \quad \text{--- (1)}$$

$$4 = \frac{4}{10} V_1 - \frac{1}{10} V_{TH} \quad \text{--- (1)}$$

Applying KCL at node 2,

$$I_3 + 4 = 0$$

$$\frac{V_1 - V_{TH}}{10} + 4 = 0$$

$$\frac{V_1}{10} + 4 = \frac{V_{TH}}{10}$$

$$\therefore V_{TH} = V_1 + 40 \quad \text{--- (2)}$$

Sub (2) in (1) and solve for V_1


$$4 = \frac{4}{10} V_1 - \frac{1}{10} V_1 - \frac{40 \cdot 4}{10}$$

$$8 = \frac{3}{10} V_1 \quad \therefore V_1 = \frac{80}{3} = 26.67V$$

$$\therefore V_{TH} = V_1 + 40 = 66.67V$$

To find V_{TH} :

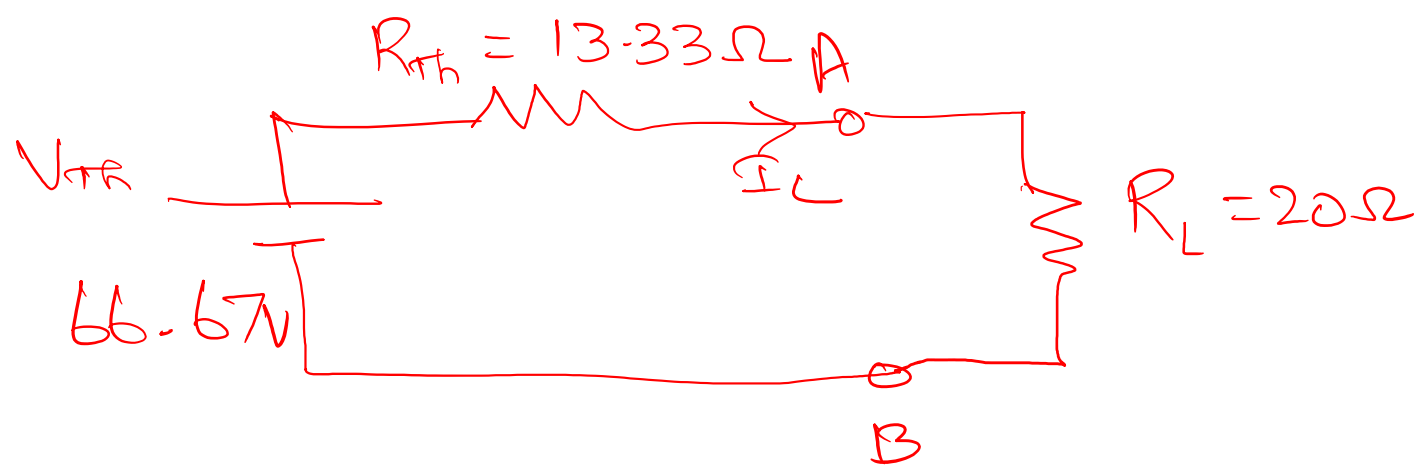To find the load current with Thevenin's equivalent circuit,




$$\text{Load current } I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$= \frac{66.67}{13.33 + 20}$$

$$= \frac{66.67}{33.33}$$

$$I_L \cong 2 \text{ A}$$

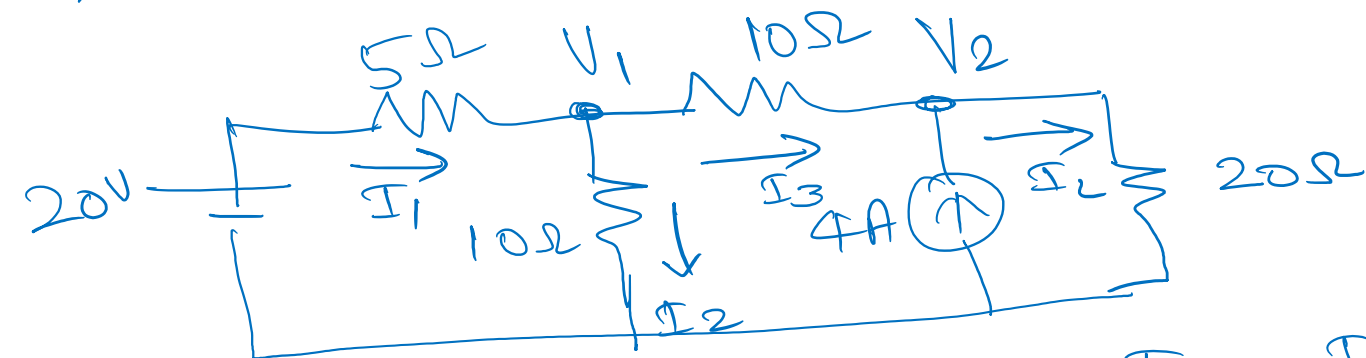To verify Thevenin's theorem, Let us compute the load current in actual circuit.



Applying KCC @ node 1, $I_1 = I_2 + I_3$

$$4 = \frac{4}{10} V_1 - \frac{1}{10} V_2 \quad \text{--- (1)}$$

Applying KCL @ node 2, $I_3 + 4 = I_L$

$$\frac{V_1 - V_2}{10} + 4 = \frac{V_2}{20}$$

$$4 = -\frac{1}{10} V_1 + \left(\frac{1}{10} + \frac{1}{20}\right) V_2$$

$$4 = -0.1 V_1 + 0.15 V_2 \quad \text{--- (2)}$$

Simplified Circuit

The load current $I_L = \frac{V_2}{20}$

To find V_2 , write equations ① & ② in matrix form

$$0.4V_1 - 0.1V_2 = 4 \quad \text{--- ①}$$

$$-0.1V_1 + 0.15V_2 = 4 \quad \text{②}$$

$$\begin{bmatrix} 0.4 & -0.1 \\ -0.1 & 0.15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 4 \end{bmatrix}$$

$$V_2 = \frac{\Delta_2}{\Delta} \quad \text{where} \quad \Delta = \begin{vmatrix} 0.4 & -0.1 \\ -0.1 & 0.15 \end{vmatrix} \quad \& \quad \Delta_2 = \begin{vmatrix} 0.4 & 4 \\ -0.1 & 4 \end{vmatrix}$$

$$\therefore V_2 = \frac{2}{0.05} = 40$$

$$\therefore \text{The load current } I_L = \frac{V_2}{20} = \frac{40}{20} = 2A$$

Maximum Power Transfer Theorem:

The power delivered to the load $P_L = I_L^2 R_L$ ✓

By Thevenin's theorem, $I_L = \frac{V_{th}}{R_{th} + R_L}$ ✓

$$\therefore P_L = \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2} \quad \text{--- (3)}$$

The power delivered to the load will be maximum if $\frac{dP_L}{dR_L} = 0$

$$\Rightarrow P_{Lmax} \text{ @ } R_L = R_{th}$$

$$P_{Lmax} = \frac{V_{th}^2 R_{th}}{(R_{th} + R_{th})^2} = \frac{V_{th}^2}{4 R_{th}}$$

To verify max-power transfer theorem,


$R_L (\Omega)$	$I_L (A)$	$P_L (W)$
10	2.85	82
12	2.63	83
13.33	2.5	83.31
15	2.35	82.83
20	2	80

R_{th} →

Applied for implementing
MPPT techniques in
Renewable energy sources
Max. Power Point Tracking


Maximum Power Transfer Theorem:

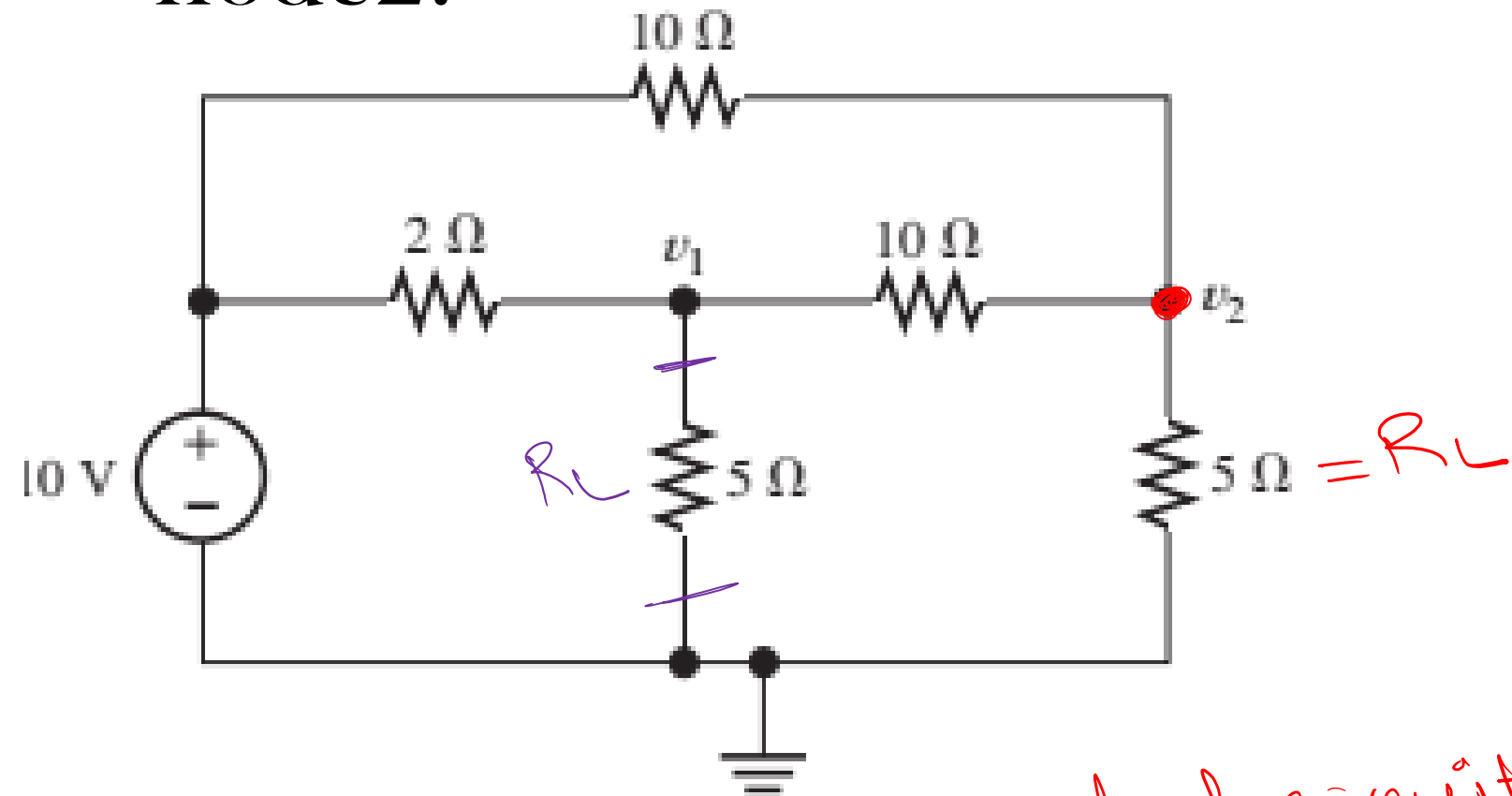Prove the power delivered by the 10V source is maximum for $R_L = R_{th}$ at node2.




1) To find Thevenin's equivalent circuit
 ↳ a) To find R_{th}
 ↳ b) To find V_{th}
 2) Apply Max. power transfer

1a) To find R_{th} :

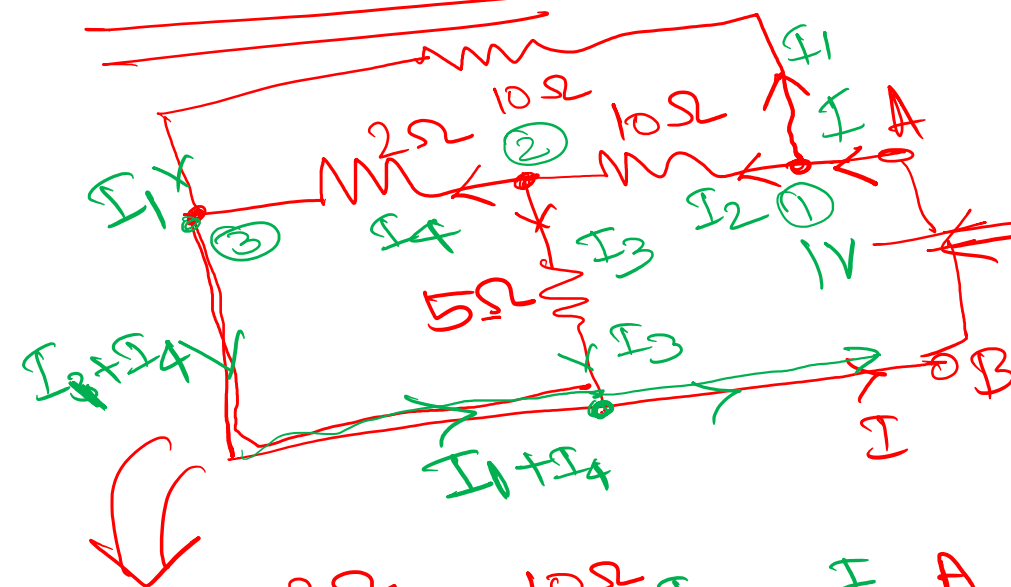

R_{AB}

$$I_1 + I_3 + I_4 = I_1 + I_2 = I$$

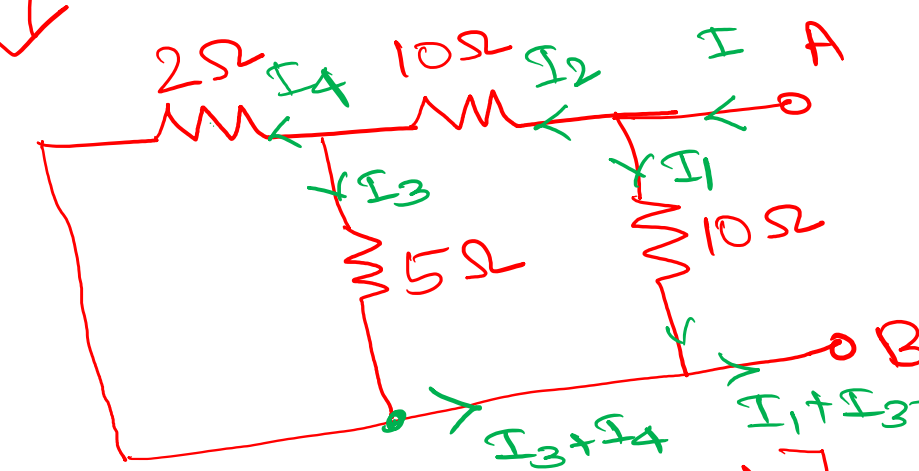

$$I_1 + I_3 + I_4 = I_2 + I_1 = I$$

$$R_{th} = 10 \parallel [10 + (5 \parallel 2)]$$

$$= 10 \parallel [10 + \frac{10}{7}] = 10 \parallel 11.43$$


$$R_{th} = 5.33 \Omega$$

$$= \frac{114.3}{21.43} = 5.33 \Omega$$

$$\frac{10}{7} = 1.4$$



Maximum Power Transfer Theorem:

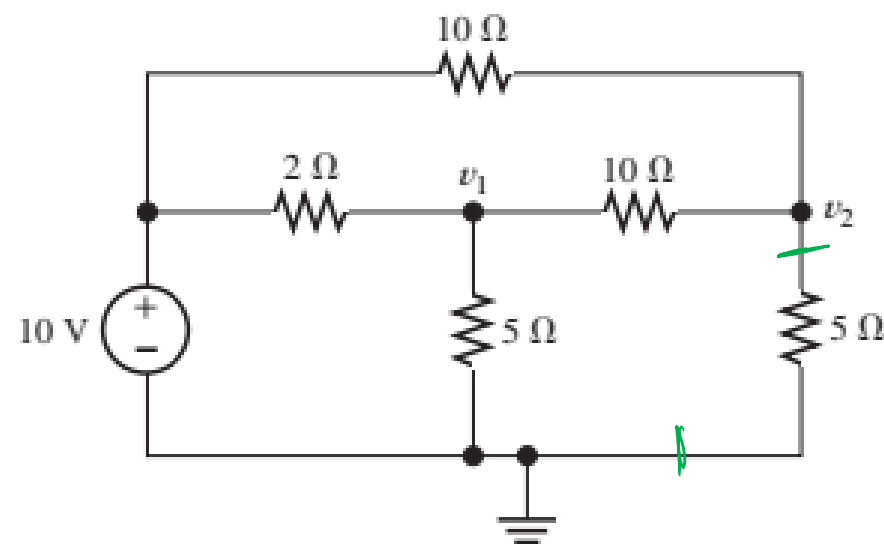

From the circuit

$$V_{AB} = 10I_1 + 5I$$

Now, $I = \frac{10}{R_{eq}}$

$$\begin{aligned} R_{eq} &= (20 \parallel 2) + 5 \\ &= \frac{40}{22} + 5 \\ &= 1.82 + 5 \\ &= 6.82 \Omega \end{aligned}$$

$$I = \frac{10}{6.82}$$

$$I = 1.47 \text{ A}$$



By current division Rule,

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$

$$= \frac{2}{20 + 2} \times 1.47$$

$$I_1 = 0.13 \text{ A}$$

To find V_{Th} :

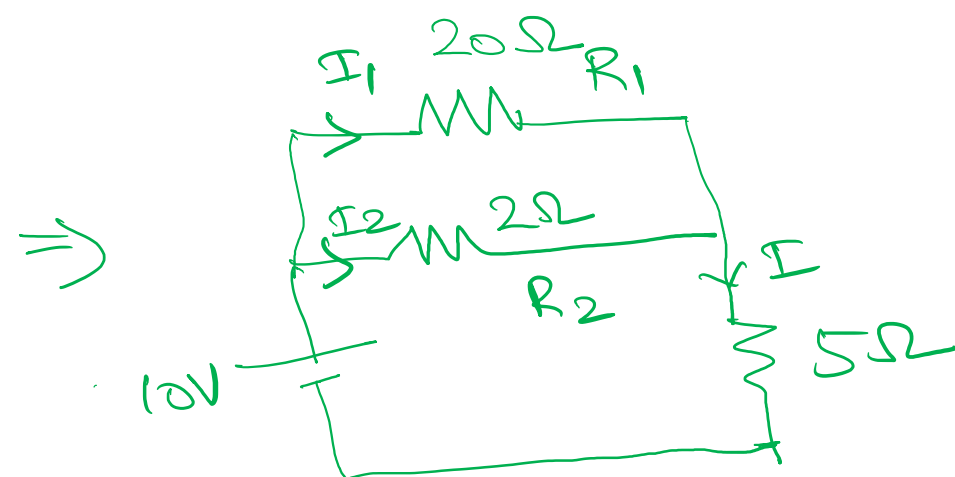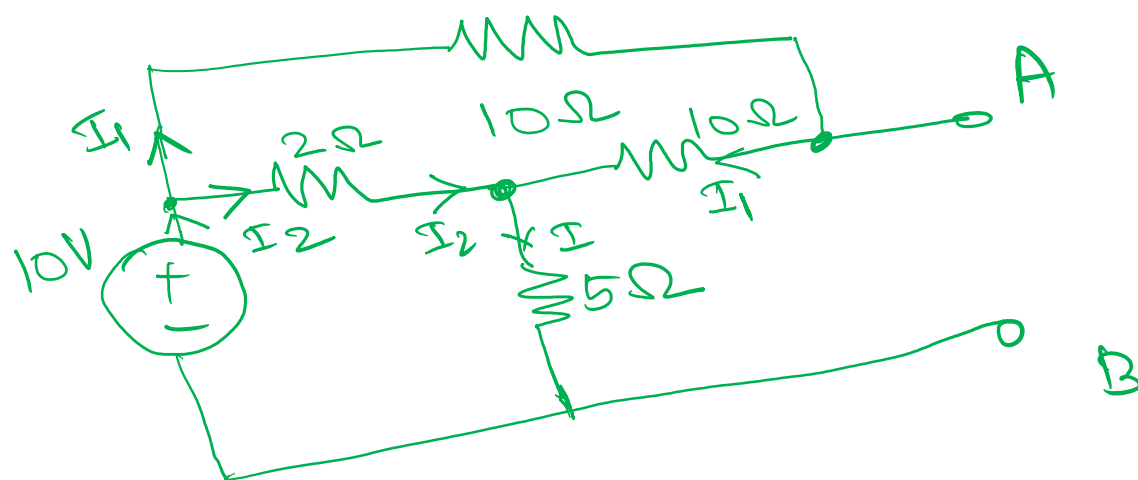


∴ The Thevenin's voltage is given

by

$$\begin{aligned} V_{Th} = V_{AB} &= 10I_1 + 5I \\ &= (10 \times 0.13) + (5 \times 1.47) \\ &= 1.3 + 7.35 \end{aligned}$$

$$V_{Th} = 8.65 \text{ V}$$

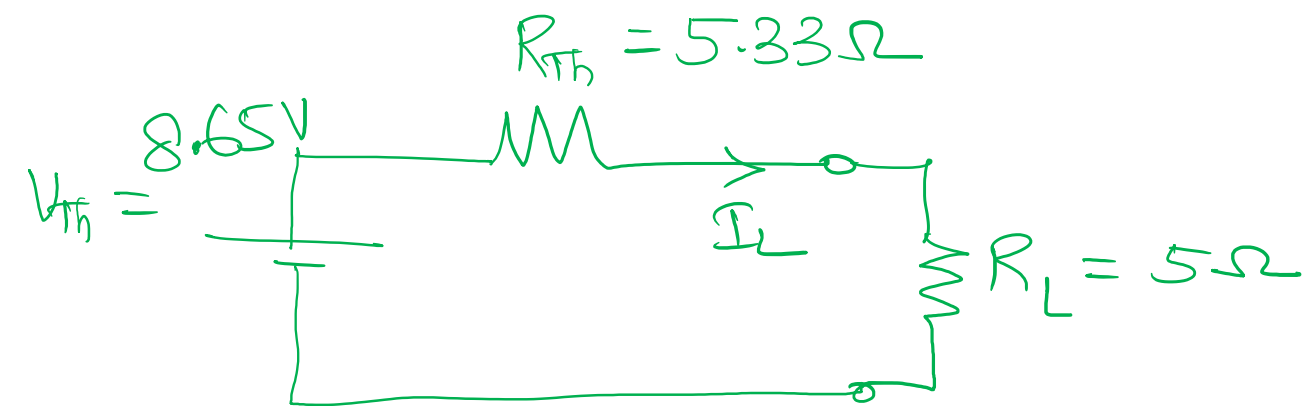To find the load current and power delivered to the load using Thevenin's equivalent circuit,



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$= \frac{8.65}{5.33 + 5}$$

$$= 0.837 \text{ A}$$

The power delivered to the load is

$$P_L = I_L^2 R_L = (0.837)^2 \times 5 = \underline{\underline{3.50 \text{ W}}}$$

To verify maximum power transfer theorem, Let us consider the following:


$R_L (\Omega)$	$I_L (\text{A})$	$P_L (\text{W})$
4	0.927	3.44
5	0.837	3.50
5.33	0.811	3.51
6	0.763	3.49

5.33 0.811 3.51 $R_L = R_{th}$.

From the above table, the power delivered by 10V source at node 2 is maximum for $R_L = R_{th}$ of the given network.

Maximum Power Transfer Theorem:

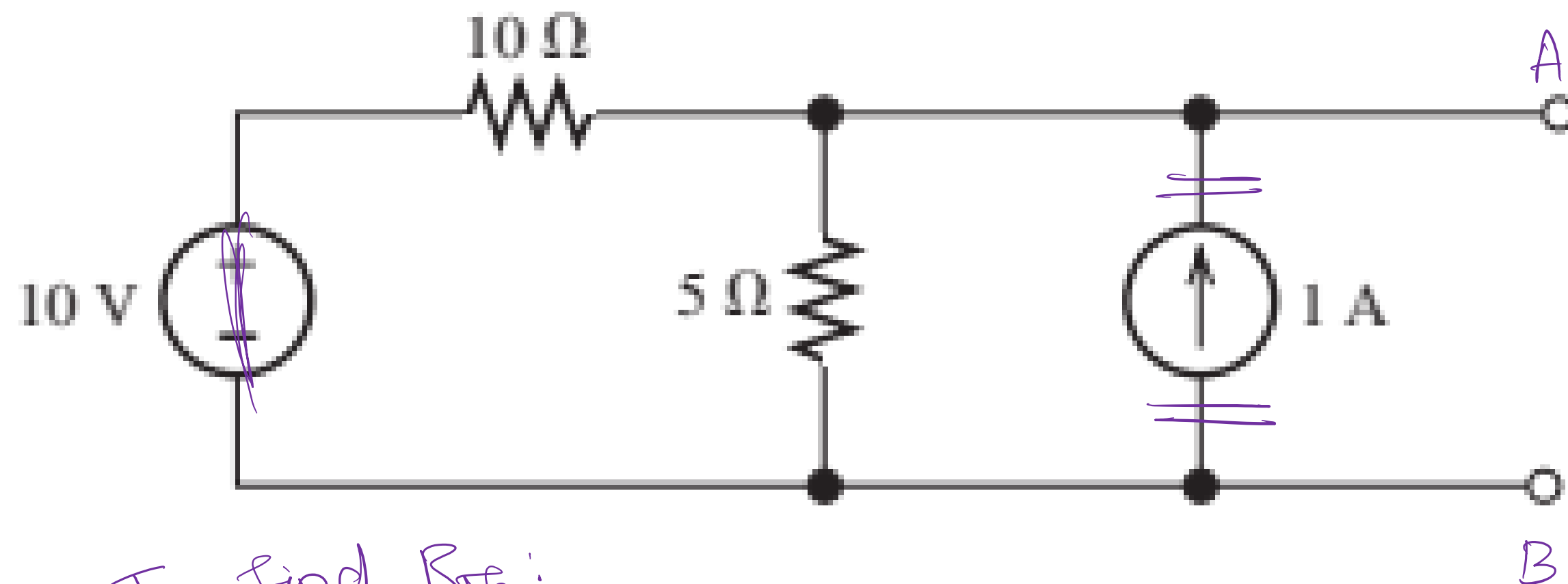Find the maximum power delivered by the 10V source in the circuit.




$$R_{Th} = ?$$

$$V_{Th} = ?$$

$$P_{max} = ?$$


To find R_{Th} :

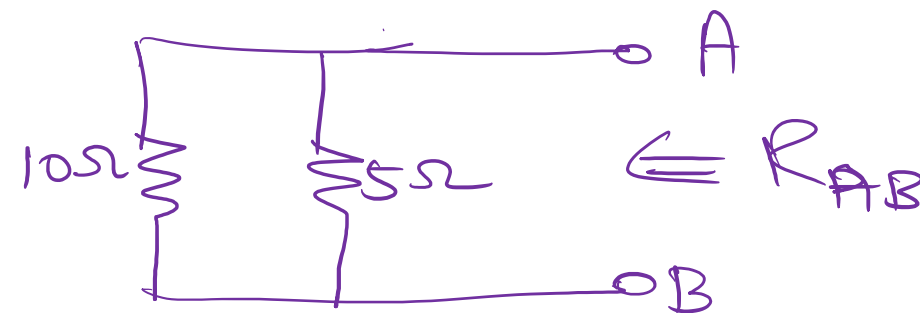

$$R_{Th} = 10 \parallel 5 = \frac{50}{15} = 3.33\Omega$$

$$R_{Th} = 3.33\Omega$$

Maximum Power Transfer Theorem:

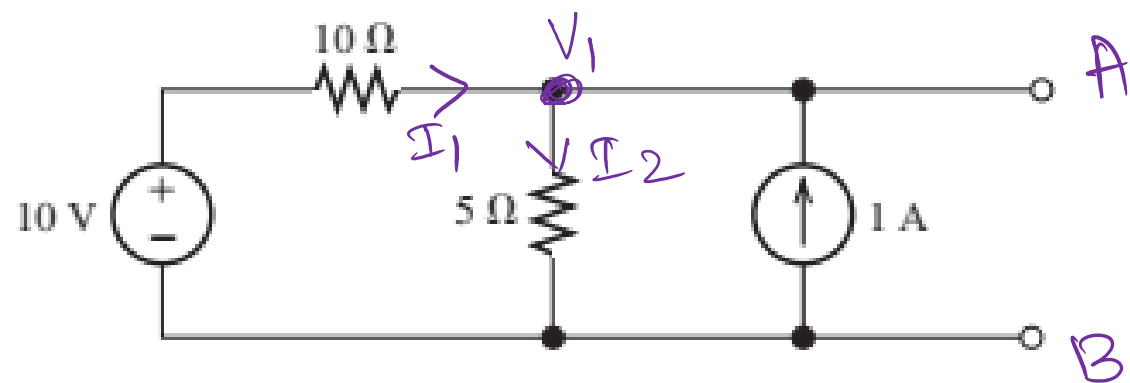

To find V_{Th} :

Apply KCL at node V_1 ,


$$I_1 + 1 = I_2$$

$$\frac{10 - V_1}{10} + 1 = \frac{V_1}{5}$$

$$1 + 1 = 0.2V_1 + 0.1V_1$$

$$V_1 = \frac{2}{0.3} = 6.67 \text{ V}$$

$$\therefore V_{Th} = 6.67 \text{ V}$$

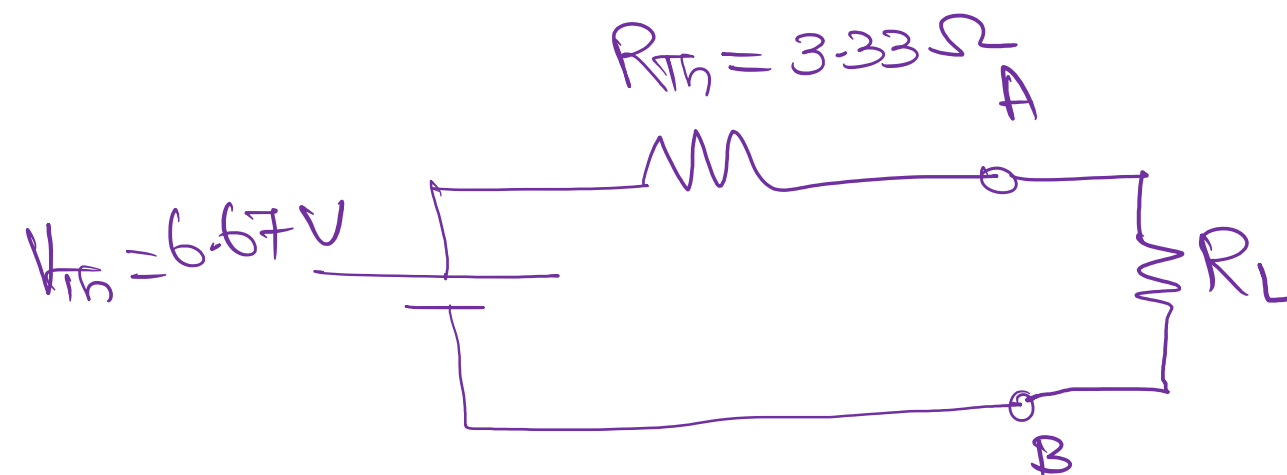

For the source to deliver maximum power, $R_L = R_{Th}$

$$\therefore P_{Lmax} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{6.67^2}{4 \times 3.33}$$

$$P_{Lmax} = 3.34 \text{ W}$$