



**Final Assessment Test (FAT) - JUNE/JULY 2023**

|              |                                              |             |                         |
|--------------|----------------------------------------------|-------------|-------------------------|
| Programme    | B.Tech.                                      | Semester    | Winter Semester 2022-23 |
| Course Title | BASIC ELECTRICAL AND ELECTRONICS ENGINEERING | Course Code | BEEE102L                |
| Faculty Name | Prof. Jamuna K                               | Slot        | B1+TB1                  |
|              |                                              | Class Nbr   | CH2022232300587         |
| Time         | 3 Hours                                      | Max. Marks  | 100                     |

**Section-A (6 X 10 Marks)**

**Answer All questions**

01. Find the maximum power that can be delivered to the resistor  $R$  in the circuit shown in Figure 1. [10]

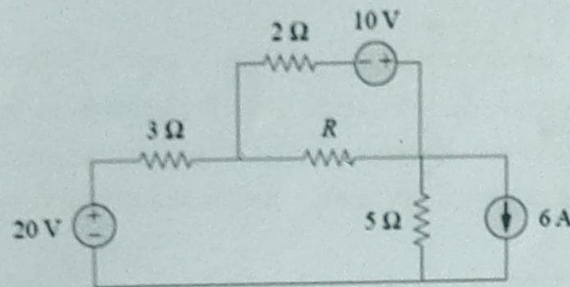


Figure 1

02. Find the node voltages  $V_a$ ,  $V_b$  and  $V_c$  for the circuit shown in Figure 2. [10]

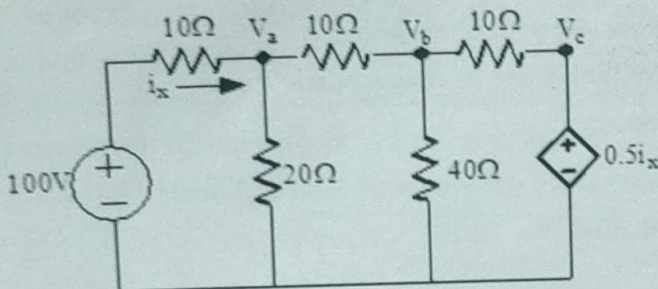


Figure 2

03. An electromagnet in the form of ID is shown in figure 3 and the iron square section 4cm wide. A flux of 1.1mwb is required in the air gap. Neglecting leakage and fringing, calculate the number of ampere turns required. Take the relative permeability of 2000 at this flux density. [10]

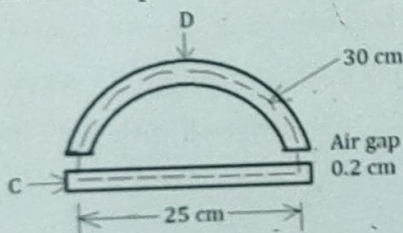


Figure 3

04. A 250V shunt motor runs at 1000 rpm at no-load and takes 8A. The total armature and shunt field resistances are  $0.2\Omega$  and  $250\Omega$  respectively. Calculate the speed when loaded and taking 50A, assume that the flux to be constant. [10]



05. Explain the operating principle of the stepper motor. Also discuss the various modes in the stepper motor.

06. Implement the Boolean function using 2 X 1 MUX.

[10]

$$F = \sum m(1, 3, 4, 6, 7, 9, 10, 12, 13, 14)$$

### Section-B (2 X 15 Marks)

Answer All questions

07. Three identical coils having a resistance of 10 ohms and inductance of 42mH are forms as (a) a star (b) a delta. These coils are connected to a voltage source of 415V with phase angle of  $0^\circ$  (rms), 50Hz, 3 phase supply. Determine the total power dissipated in each case.

[15]

08. The mutual inductance between two coils is  $M=0.2H$  for the circuit shown in Figure 4 and the source voltage is  $v_s(t) = 12\cos 10t$  V. Find the current  $i_1$  and  $i_2$ .

[15]

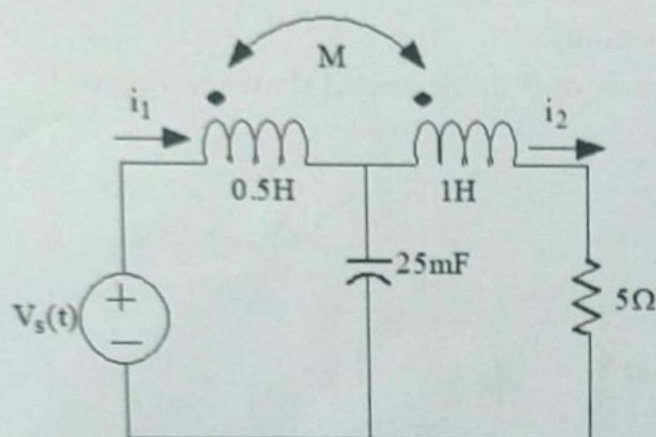


Figure 4

### Section-C (2 X 5 Marks)

Answer All questions

09. Discuss the working of a full-wave rectifier without and with filter circuit.

[5]

10. Explain the operation of the enhancement type MOSFET and its characteristic curves.

[5]

