

BEEE101L – Basic Electrical Engineering

Dr. R. GUNABALAN

Associate Professor

School of Electrical Engineering

Cabin No: 01, 7th floor, AB1 (nearer to Auditorium)

gunabalan.r@vit.ac.in

9894919269

Module 2 : AC Circuits

6 Hrs


Alternating voltages and currents, RMS, average, form factor, peak factor; Single phase RL, RC, RLC series and parallel circuits; Power and power factor; Balanced three phase systems

Course Outcome

- Evaluate AC circuit parameters


Terminology

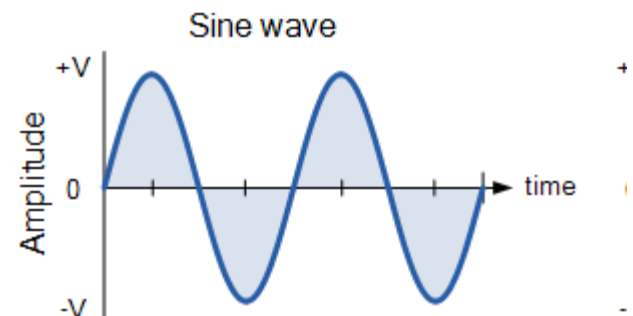- **Waveform** – It is a graph in which the instantaneous value of any quantity is plotted against time
- **Alternating waveform** – This is a wave which reverses its direction at regular recurring intervals
- **Periodic waveform** – It repeats itself after definite time intervals




Terminology

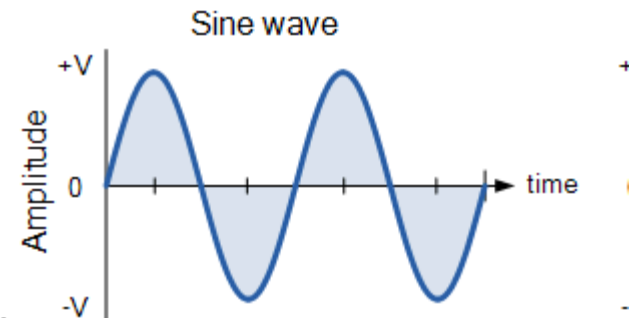- **Sinusoidal waveform** – It is an alternating waveform in which sine law is followed
- **Non-sinusoidal waveform** – It is an alternating waveform in which sine law is not followed
- **Cycle**– One complete set of positive and negative halves constitute a cycle
- **Frequency** – The number of cycles per second of an alternating quantity





Terminology

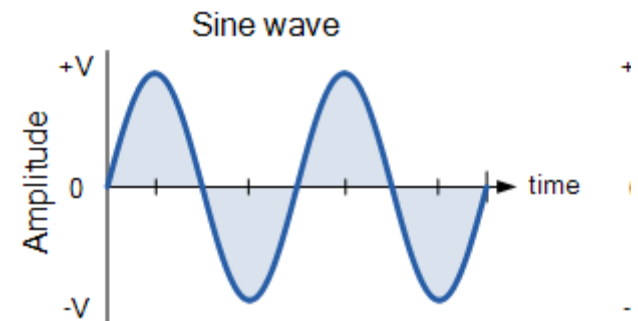- **Period**– Time taken to complete one cycle
- **Amplitude** – The maximum positive and negative value of an alternating quantity
- **Instantaneous values** - The values of the alternating quantities at any instant of time




Terminology

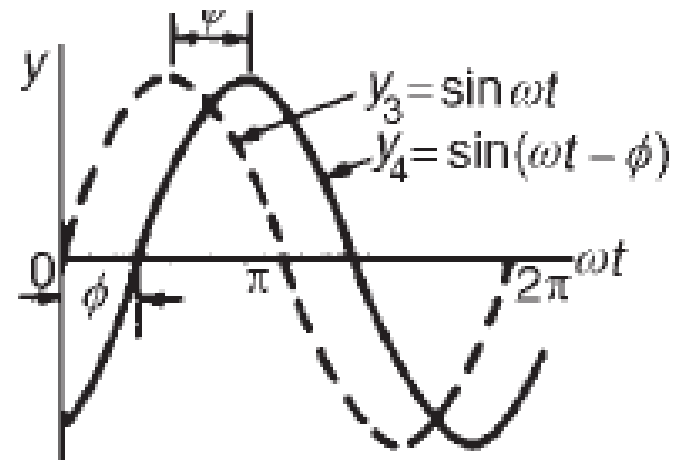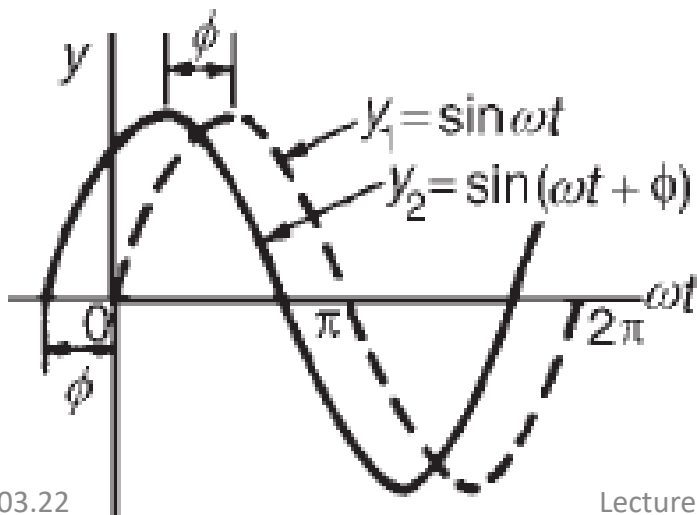- **Phase** – The time that has elapsed since the quantity has last passed through zero point of reference and passed positively
- **Phase difference** – It is used to compare the phase of two waveforms




- **RMS value** – The steady state value of (DC) current which when flows in a given circuit for a given time produces the same heat as would be produced by the alternating current flowing in the same circuit for the same time.

RMS Voltage Equivalent

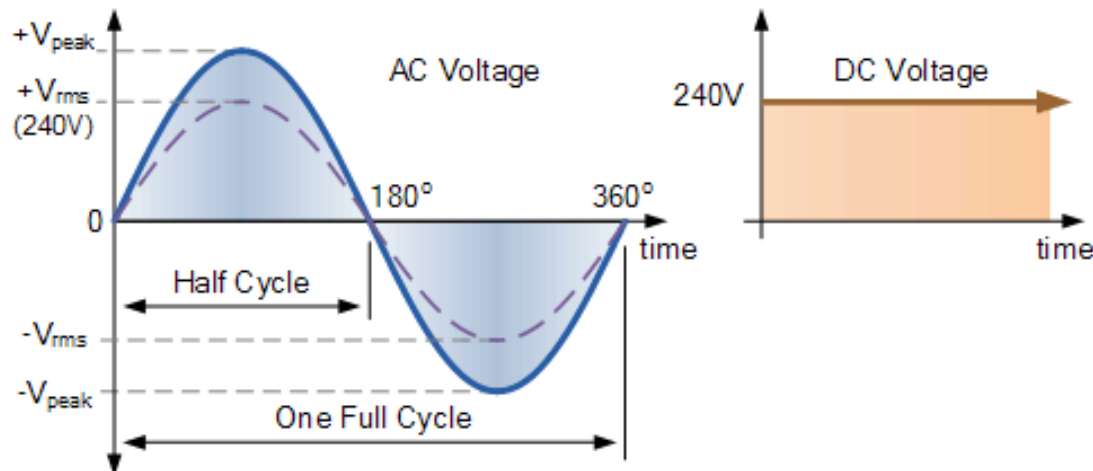

Graphical Method

Graphical Method

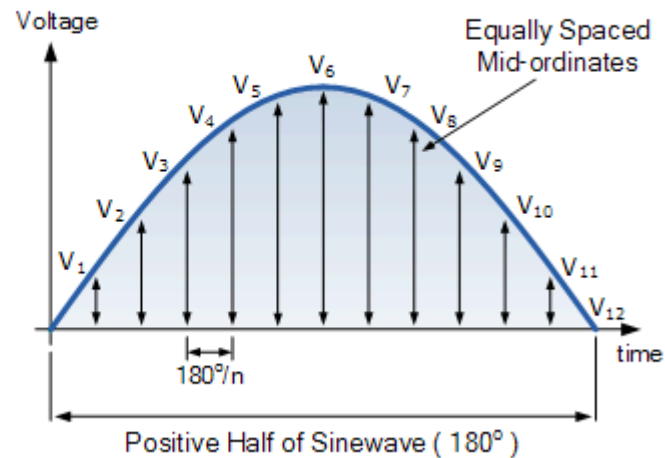


$$V_{\text{RMS}} = \sqrt{\frac{\text{sum of mid-ordinate (voltages)}^2}{\text{number of mid-ordinates}}}$$

$$V_{\text{RMS}} = \sqrt{\frac{V_1^2 + V_2^2 + V_3^2 + V_4^2 + \dots + V_{11}^2 + V_{12}^2}{12}}$$

- **Average value** – Steady current which transfers across the circuit the same charge as would be transferred by the ac across the same circuit in the same time.

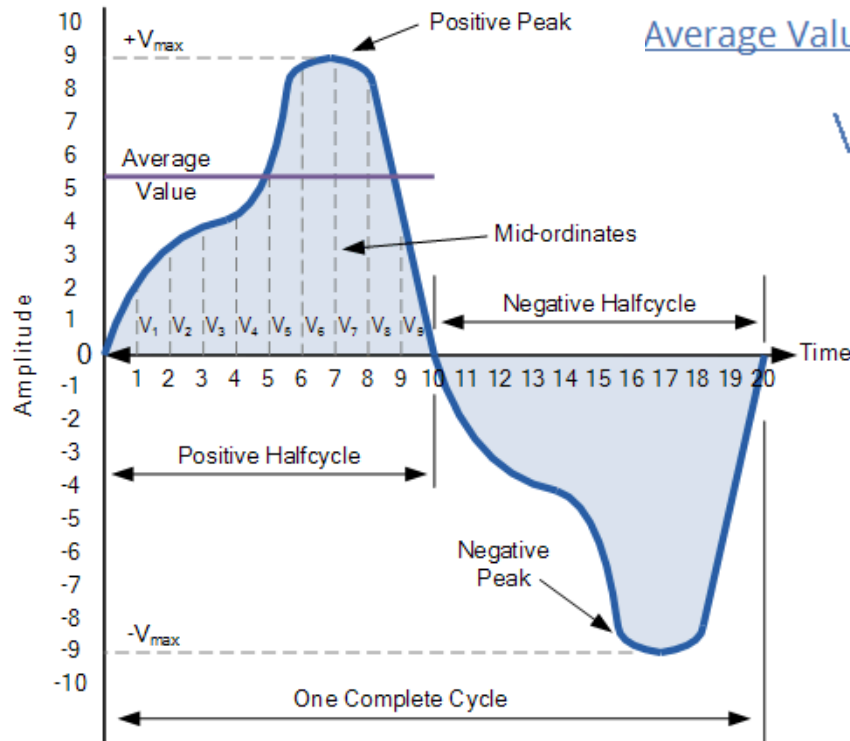Average Value of a Non-sinusoidal Waveform



Average Value of an AC Waveform

$$V_{\text{average}} = \frac{V_1 + V_2 + V_3 + V_4 + \dots + V_n}{n}$$

Find the average and RMS value of a sinusoidal wave (Analytical method)






- $I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$
- $I_{av} = \frac{2I_m}{\pi} = 0.637 I_m$

Find the average and RMS value of a sinusoidal wave (Analytical method)


- **Form factor (FF)** – the ratio of RMS value to the average value
- **Peak factor** – the ratio of peak value to RMS value
- $I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$
- $I_{av} = \frac{2I_m}{\pi} = 0.637 I_m$

Phasor representation

- A rotating vector is known as phasor

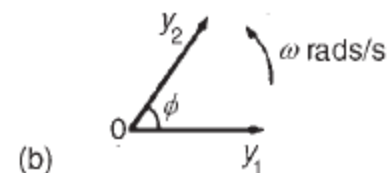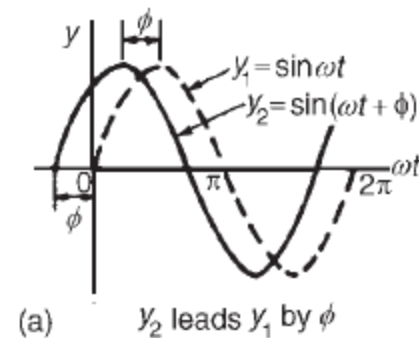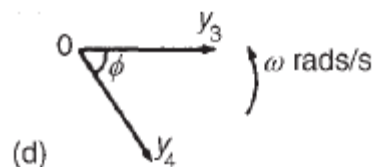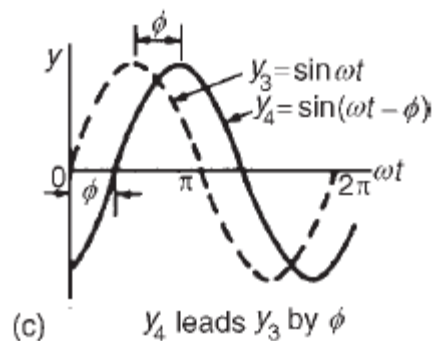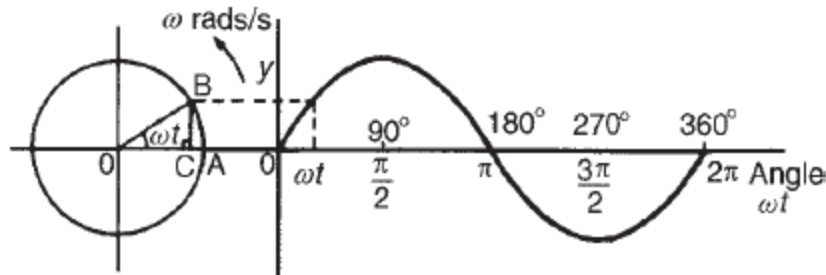

Pure resistive circuit

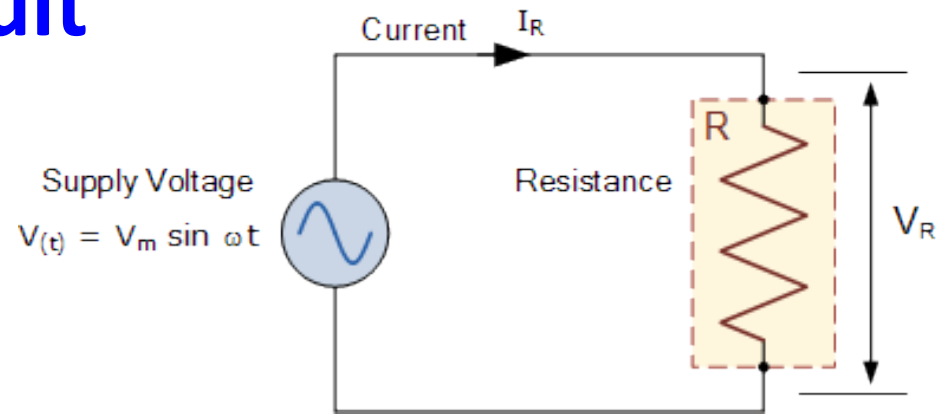

The instantaneous voltage across the resistor, V_R is equal to the supply voltage

$$V_R = V_{\max} \sin \omega t$$

The instantaneous current flowing in the resistor is

$$I_R = \frac{V_R}{R} = \frac{V_{\max}}{R} \sin \omega t = I_{\max} \sin \omega t$$


- The voltage across a resistor is given as $V_R = I.R$
- The instantaneous voltage across the resistor

$$V_R = I_{\max} R \sin \omega t$$

- For resistors in AC circuits the phase angle ϕ between the voltage and the current is zero
- The power factor of the circuit is given as $\cos 0^\circ = 1.0$.
- **Note: Power factor is defined as the cosine of the phase angle between voltage and current**

- In AC circuits, the ratio of voltage to current depends upon the frequency and phase difference or phase angle (ϕ) of the supply. So the term **Impedance**, symbol **Z** is generally used

AC impedance $Z = R$

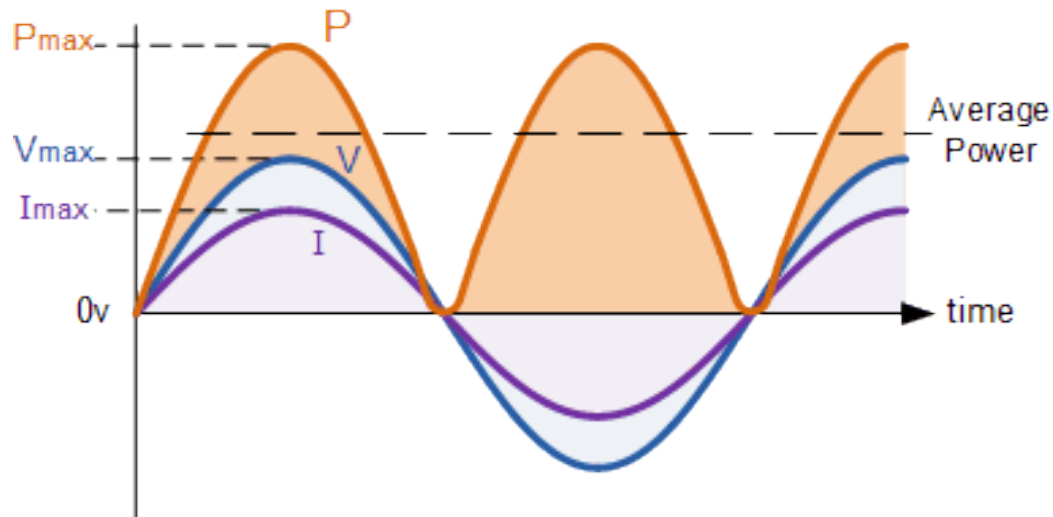

Average power

- The power in the circuit at any instant in time can be found by multiplying the voltage and current at that instant.
- $P_{av} = V_{rms} I_{rms}$

Power factor

- Cosine of the phase angle between voltage and current
- Power factor = $\cos 0 = 1$ (unity)

Pure Inductive Circuit

- Impedance $Z = X_L$
- Waveforms
- Phasor representation
- Average power
- Power factor

Pure Inductive Circuit

Pure Capacitive Circuit

- Impedance $Z = X_C$
- Waveforms
- Phasor representation
- Average power
- Power factor

Note: Derive all above parameters