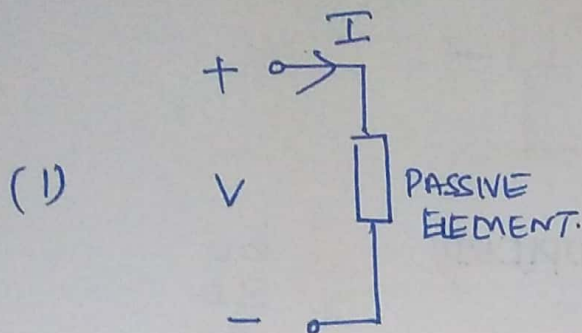


SIGN CONVENTIONS




PASSIVE SIGN CONVENTION.

$$V = IR.$$

$$P = VI \text{ ALWAYS (+ve) ABSORBED}$$

CURRENT ENTERS THE POSITIVE TERMINAL

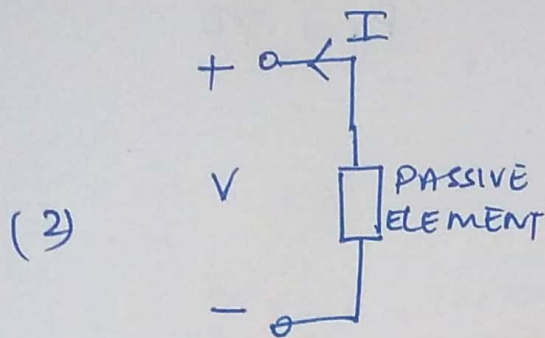


ACTIVE SIGN CONVENTION

$$V = -IR.$$

$$P = VI \text{ ALWAYS (+ve) SUPPLIED.}$$

CURRENT LEAVES THE POSITIVE TERMINAL

POWER IN A CIRCUIT.

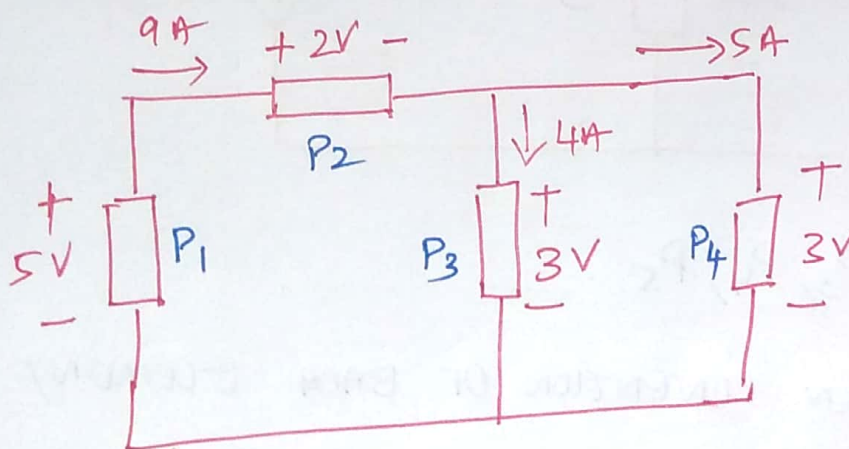

$$P_1 = 45 \text{ W SUPPLIED}$$


$$P_2 = 18 \text{ W ABSORBED}$$

$$P_3 = 12 \text{ W ABSORBED}$$

$$P_4 = 15 \text{ W ABSORBED}$$

$$\sum \text{POWER SUPPLIED} = \sum \text{POWER ABSORBED}$$

(2)

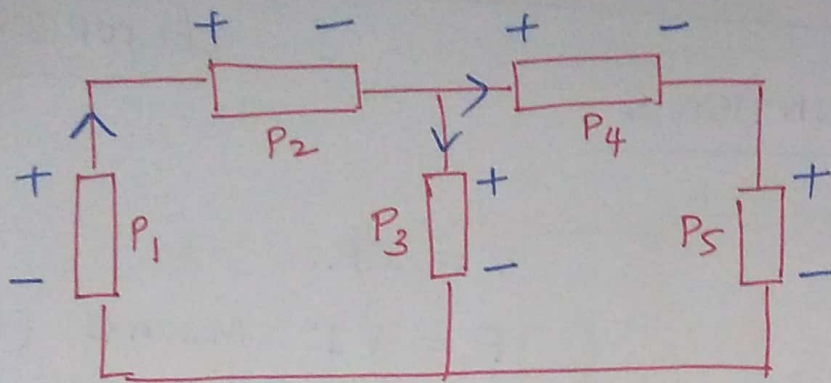

If $P_1 = -205 \text{ W}$ (SUPPLIED)

$$P_2 = 60 \text{ W}$$

$$P_5 = 30 \text{ W}$$

$$P_4 = 45 \text{ W}$$


$$P_3 = ? = 70 \text{ W}$$

ABSORBED

$$\begin{array}{r} 60 \\ + 30 \\ \hline 45 \\ \hline 135 \end{array}$$

$$P_3 = 70$$

DO IT YOURSELF

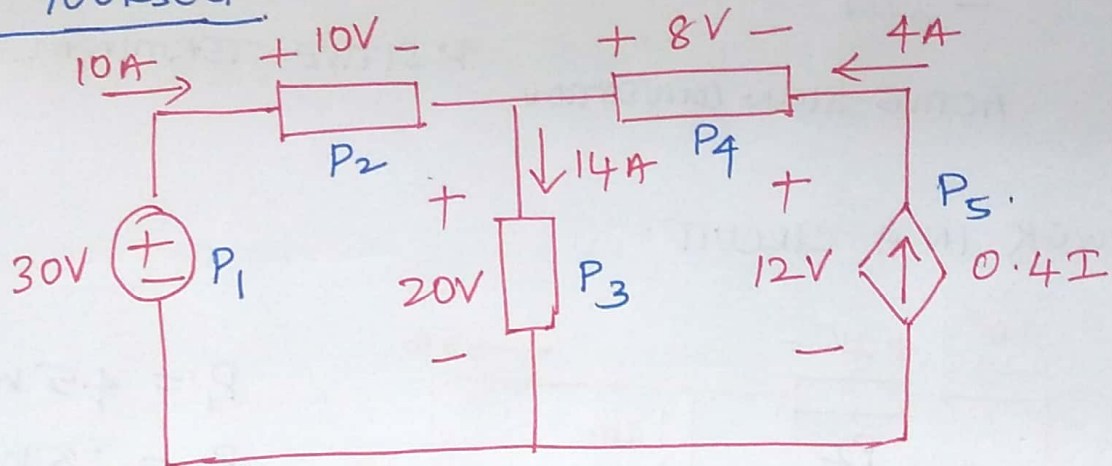


Find P_1, P_2, P_3, P_4, P_5 .

SPECIFY SIGN CONVENTION OF EACH ELEMENT

AND SAY IF POWER SUPPLIED / ABSORBED

ELEMENT	SIGN CONV.	POWER SUPPLIED	POWER ABSORBED

IDENTIFY THE NODES, BRANCHES, LOOPS.

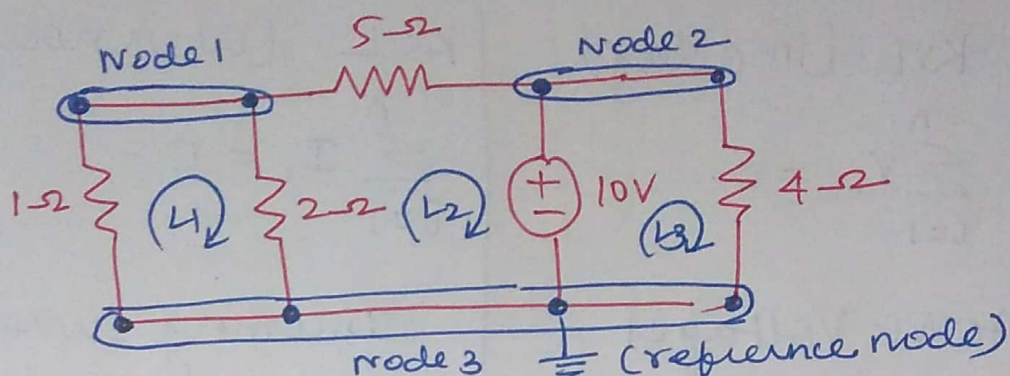

$$\text{Nodes} = 3$$

$$\text{Branches} = 5$$

$$\text{Loops} = 3$$

$$b = l + n - 1$$

$$l = b - n + 1$$

$$= 5 - 3 + 1$$


$$l = 3 \text{ (independent loops)}$$

SERIES : NONE

PARALLEL : $1\Omega, 2\Omega$

$4\Omega, 10V \text{ source}$

DO IT YOURSELF

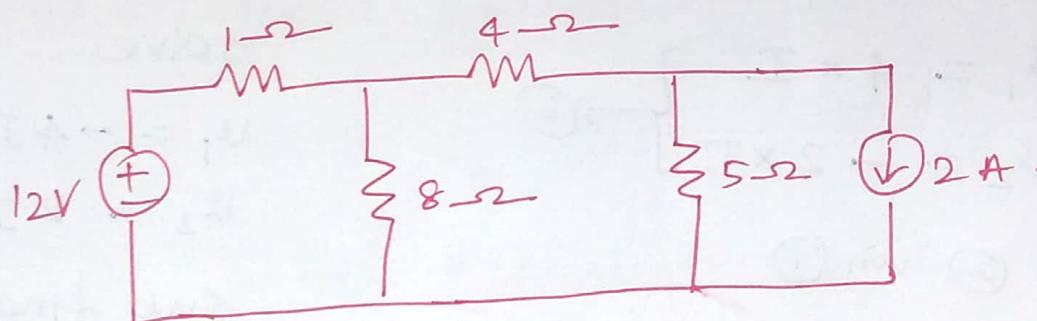

Determine the number of nodes, branches, independent loops, branches in series and branches in parallel.

4

KIRCHOFF'S LAWS:

KVL (in a loop)

$$\sum_{i=1}^n V_i = 0.$$

Active Voltages

= Passive Voltages


KCL (at a node)

$$\sum_{i=1}^n I_i = 0.$$

Incoming currents

= outgoing currents.

Example

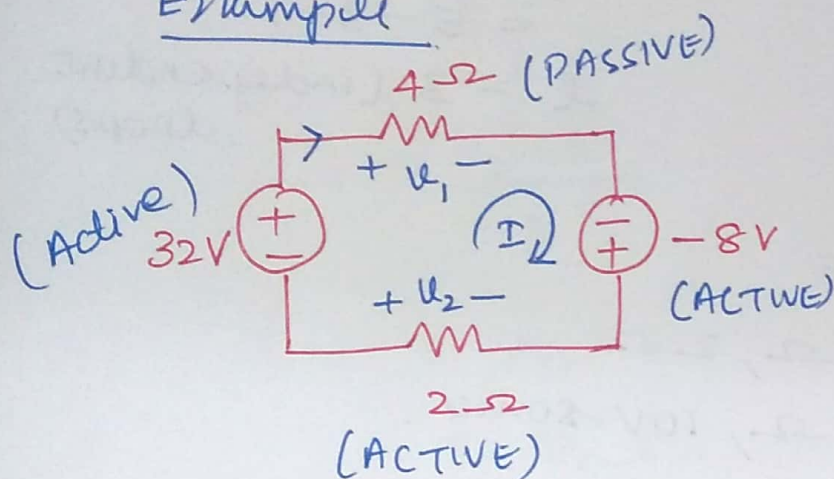

$$\therefore 32 + V_2 - 8 = V_1 \rightarrow \textcircled{1}$$

$$\left. \begin{aligned} V_1 &= 4 \times I \\ V_2 &= -2 \times I \end{aligned} \right\} \rightarrow \textcircled{2}$$


Sub ② in ①

$$24 = V_1 - V_2 = 4I + 2I.$$

$$\therefore I = \frac{24}{6} = 4A$$

$$V_1 = 16V$$

$$V_2 = -8V.$$

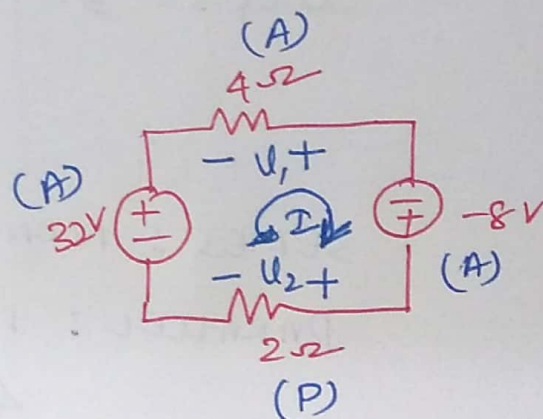

$$\therefore 32 + V_1 - 8 = V_2$$

$$32 + V_1 - 8 = V_2$$

solve

$$V_1 = -4I$$

$$V_2 = 2I.$$


sub find.

$$V_1$$

$$V_2$$

$$I.$$

Same solution.

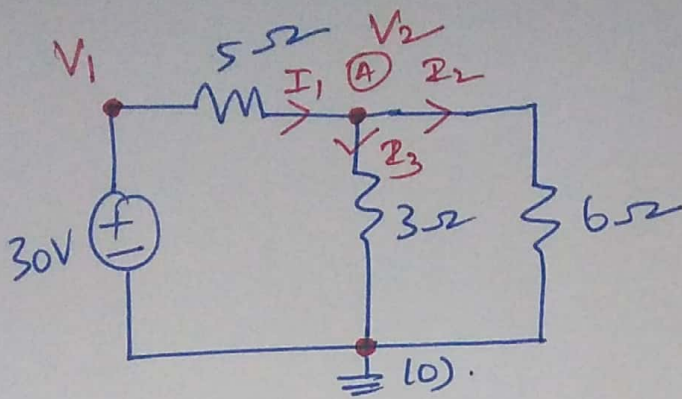

At node A, $I_1 = I_2 + I_3$ (KCL)

$$I_1 = \frac{V_1 - V_2}{5}$$

$$I_2 = \frac{V_2 - 0}{6}$$

$$I_3 = \frac{V_2 - 0}{3}$$

Find $V_1, V_2,$


I_1, I_2, I_3 .

Note: Node 1 voltage $V_1 = 30V$ (known).

Find V_2 and

Branch currents I_1, I_2, I_3 .

For both cases.

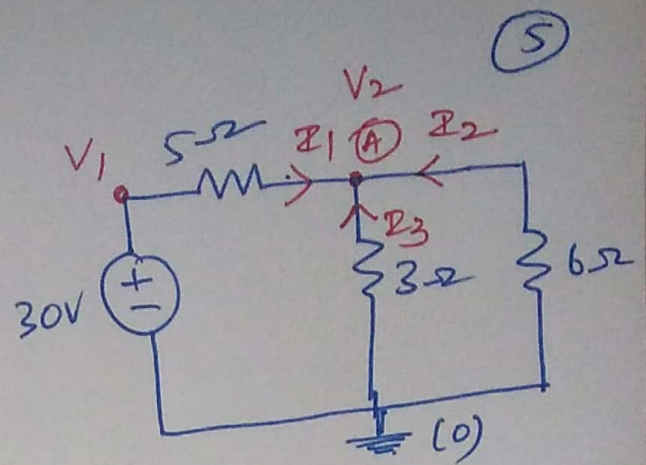

At node A,

$$I_1 + I_2 + I_3 = 0.$$

$$I_1 = \frac{V_1 - V_2}{5}$$

$$I_2 = \frac{0 - V_2}{6}$$

$$I_3 = \frac{0 - V_2}{3}$$