

Inductance, Coupling

classmate

Date
Page

Self:

$$V \text{ (or) } \mathcal{E} \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

$L \rightarrow$ self inductance

$$V \propto \frac{d\phi}{dt}$$

$$V = N \frac{d\phi}{dt}$$


$N \rightarrow$ no. of turns in the coil

$$L \frac{di}{dt} = N \frac{d\phi}{dt}$$

$$L = N \frac{d\phi}{di}$$

$$L = \frac{N\phi}{i} \rightarrow \text{when permeability is constant}$$

Mutual:

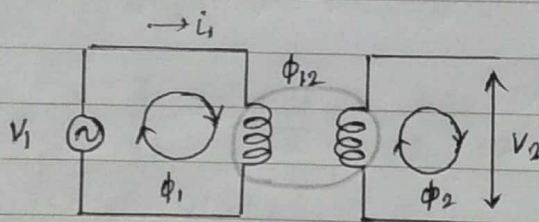

$$V_2 = N_2 \frac{d\phi_{12}}{dt}$$

$$M = N_2 \frac{d\phi_{12}}{di_1}$$

coefficient of coupling

$$K = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

ϕ_{12} is produced by i_1 and V_2

$$V_2 = M \frac{di_1}{dt}$$

$$M = N_2 \frac{d\phi_{12}}{di_1} = N_2 \frac{\phi_{12}}{i_1} \quad (\text{or}) \quad N_1 \frac{\phi_{21}}{i_2}$$

multiplying these 2

$$M^2 = \frac{N_1 N_2 \phi_{12} \phi_{21}}{i_1 i_2}$$

$$= \frac{N_1 N_2 K \phi_1 K \phi_2}{i_1 i_2}$$



$$= \frac{N_1 N_2 K^2 \phi_1 \phi_2}{i_1 i_2}$$

$$M^2 = L_1 L_2 K^2$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$


$$L_1 = \frac{N_1 \phi_1}{i_1}$$

$$L_2 = \frac{N_2 \phi_2}{i_2}$$

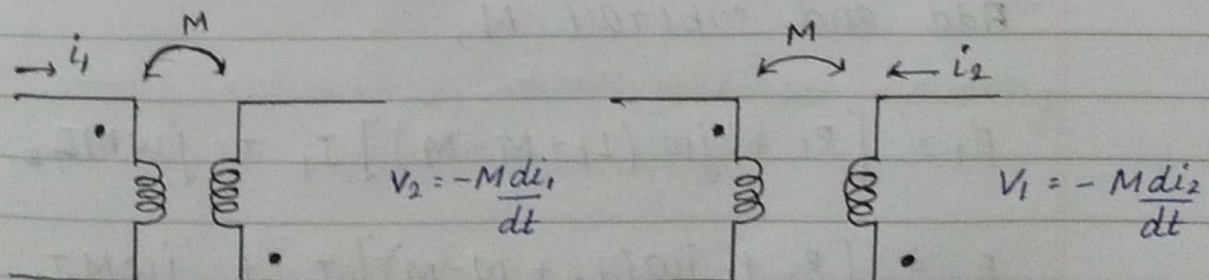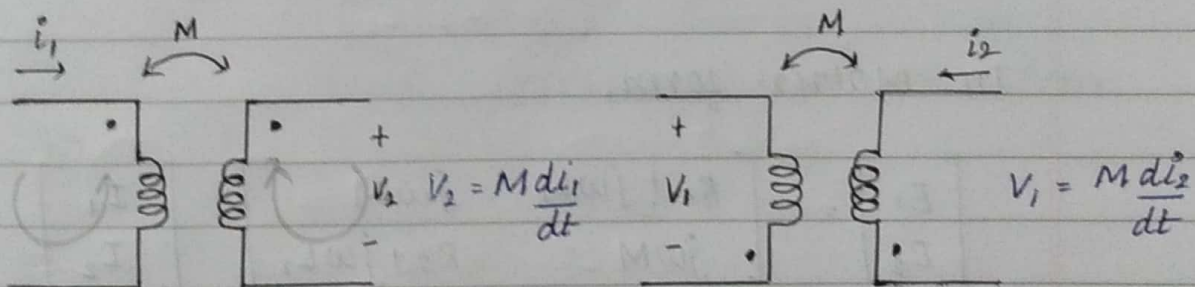

when dots are in alternative side, sign is -ve.

coupling:

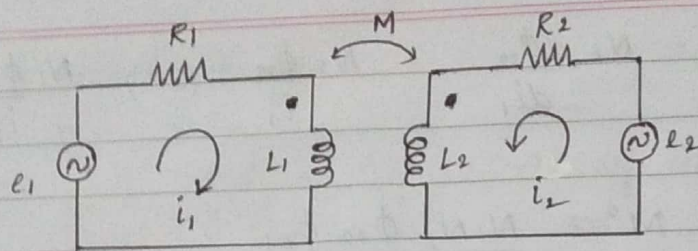

Applying KVL,

$$e_1 = R_1 i_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

as dots are same side

$$e_2 = R_2 i_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

In terms of sinusoidal steady state condition,

$$E_1 = (R_1 + j\omega L_1) I_1 + j\omega M I_2$$

$$E_2 = (R_2 + j\omega L_2) I_2 + j\omega M I_1$$

In Matrix form,


$$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} R_1 + j\omega L_1 & j\omega M \\ j\omega M & R_2 + j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Add and subtract M,


$$E_1 = [R_1 + j\omega (L_1 + M - M)] I_1 + j\omega M I_2$$

$$E_2 = [R_2 + j\omega (L_2 + M - M)] I_2 + j\omega M I_1$$

Now we draw circuit for above 2 eqns.

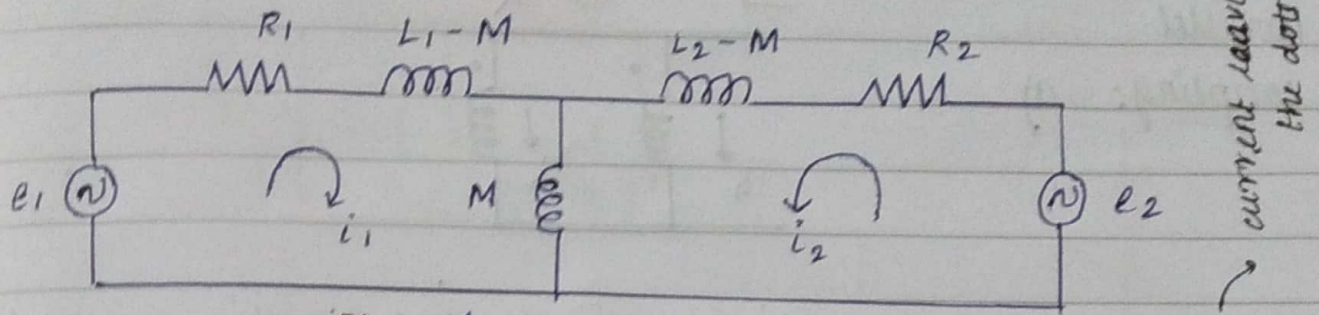

series coupling:

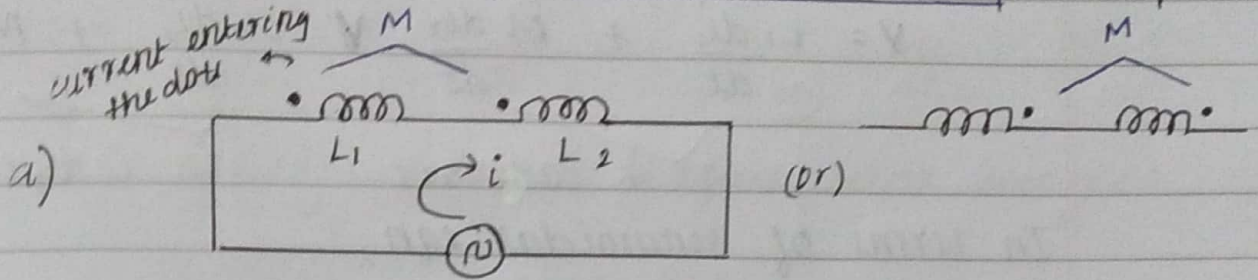


$$V(t) = L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt}$$

for first inductor

for second inductor

$$V = (L_1 + L_2 + 2M) \frac{di}{dt}$$

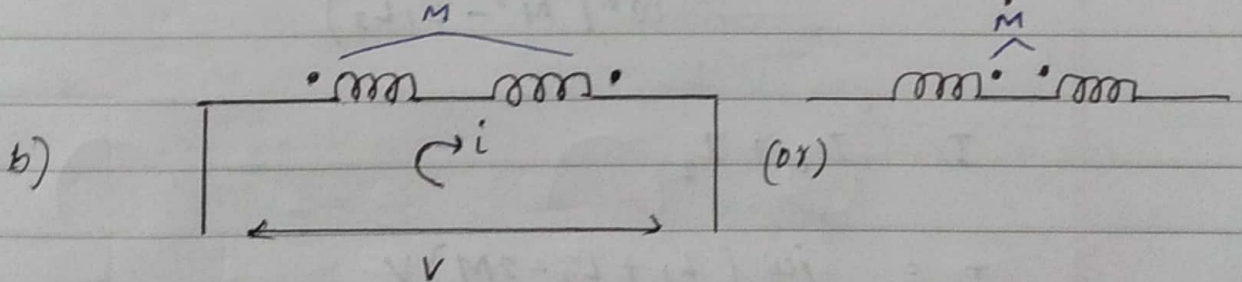
$$\therefore L_a = L_1 + L_2 + 2M \rightarrow \text{series aiding}$$



$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} - M \frac{di}{dt} - M \frac{di}{dt}$$

$$\therefore L_a = L_1 + L_2 - 2M \rightarrow \text{series opposing}$$

parallel coupling: a)

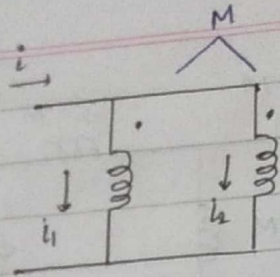

$$V = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

In terms of sinusoidal eqn,

$$V = j\omega L_1 I_1 + j\omega M I_2$$

$$V = j\omega L_2 I_2 + j\omega M I_1$$

Now solving both eqns, we get

$$I_1 = \frac{j\omega (L_2 - M) V}{\omega^2 (M^2 - L_1 L_2)}$$

$$I_2 = \frac{j\omega (L_1 - M) V}{\omega^2 (M^2 - L_1 L_2)}$$

$$I = I_1 + I_2$$


$$I = \frac{j\omega (L_1 + L_2 - 2M) V}{\omega^2 (M^2 - L_1 L_2)}$$

$$\frac{V}{I} = \frac{\omega^2 (M^2 - L_1 L_2)}{j\omega (L_1 + L_2 - 2M)} = \frac{-\omega^2 (L_1 L_2 - M^2)}{j\omega (L_1 + L_2 - 2M)}$$

$$= \frac{j\omega (L_1 \cdot L_2 - M^2)}{L_1 + L_2 - 2M}$$

$$\frac{V}{I} = j\omega L_a$$
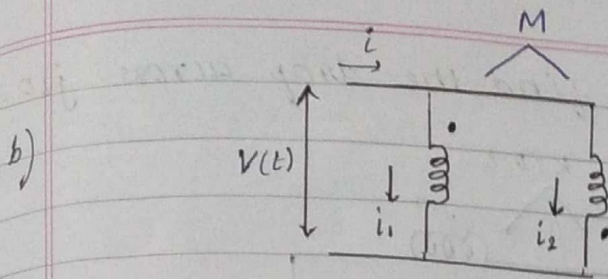
$$\therefore L_a = \frac{L_1 \cdot L_2 - M^2}{L_1 + L_2 - 2M}$$



$$V = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

on solving like the before sum we get,

$$L_b = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

1. 2 coupled coils $L_1 = 0.04 \text{ H}$, $L_2 = 0.02 \text{ H}$ and $K = 0.5$ are connected in four different ways.

- series aiding
- series opposing
- parallel aiding
- parallel opposing

$$K = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow M = K \sqrt{L_1 L_2}$$

$$= 0.5 \sqrt{(0.04)(0.02)}$$

$$= 0.014$$

a) $L_a = L_1 + L_2 + 2M$

$$= 0.04 + 0.02 + 2(0.014)$$

$$= 0.088 \text{ H}$$

b) $L_b = L_1 + L_2 - 2M$


$$= 0.06 - 2(0.014)$$

$$= 0.032$$

c) $L_a = \frac{(0.06)(0.02) - (0.014)^2}{0.06 + 0.02 - 2(0.014)} = 0.01 \text{ H}$

d) $L_b = \frac{(0.06)(0.02) - (0.014)^2}{0.06 + 0.02 + 2(0.014)} = 0.018 \text{ H}$

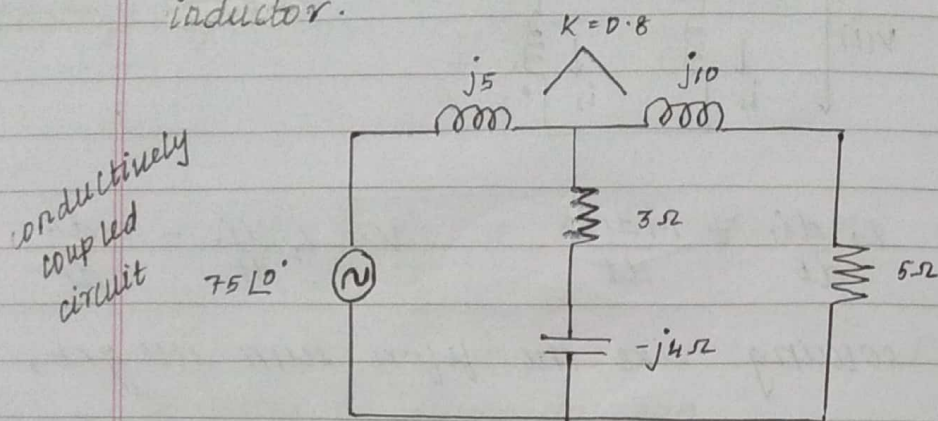2. For a given fig. find the drop across $j10\Omega$ inductor.




conductively coupled circuit to mutually coupled circuit,

$$M = K \sqrt{L_1 L_2}$$

$$= 0.8 \sqrt{5 \times 10}$$

$$M = 5.66 \Omega$$

converting the circuit,

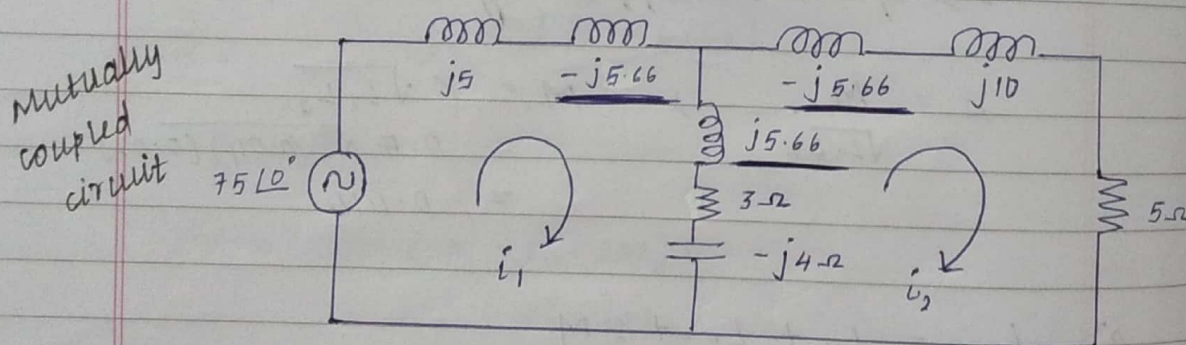

Loop 1: $75 \angle 0^\circ = j5 I_1 - j5.66 I_1 + j5.66 I_1 - j5.66 I_2 + 3(I_1 - I_2) - j4(I_1 - I_2)$

Loop 2: $0 = -j4(I_2 - I_1) + 3(I_2 - I_1) + j5.66(I_2 - I_1) - j(5.66 I_2) + j10 I_2 + 5 I_2$


on solving we get,

$$I_2 = 12.93 \angle 24.7^\circ$$

$$V_{j10\Omega} = 10 \angle 90^\circ \times 12.93 \angle 24.7^\circ$$

$$= 129.3 \angle 65.3^\circ \text{ V}$$

3. calculate the mesh currents.

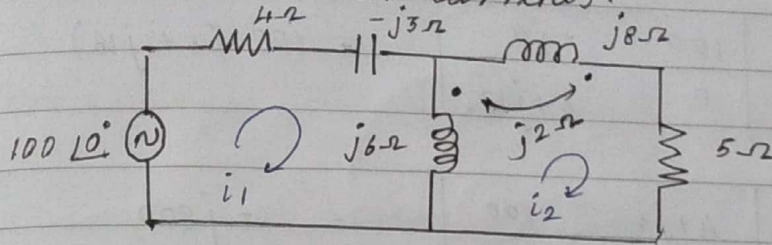

additional
due to mutual
coupling

In Loop 1: $100 \angle 0^\circ = 4 I_1 - j3 I_1 + j6 (I_1 - I_2) - \underline{j2 I_2}$

$$100 \angle 0^\circ = (4 + j3) I_1 - j8 I_2$$

how here -ve sign?

current i_1 is entering at point near $j6\Omega$ and leaving at point near $j8\Omega$. so they are opposite. so -ve.

In Loop 2: $0 = -j2 I_1 - j6 I_1 + (j6 + j8 + 2 \times j2) I_2 + 5 I_2$
 $(L_1 + L_2 + 2M)$

$$0 = -j8 I_1 + (5 + j18) I_2$$

+ve sign becoz i_2 is making at both points in loop 2.

Solving these 2 eqns,

$$\begin{vmatrix} 100 \angle 0^\circ \\ 0 \end{vmatrix} = \begin{vmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{vmatrix}$$

$$\Delta_1 = \begin{vmatrix} 100 \angle 0^\circ & -j8 \\ 0 & 5 + j18 \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} 4 + j3 & 100 \angle 0^\circ \\ -j8 & 0 \end{vmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = (4+j3)(5+j8) - (j^2)(8^2)$$

$$= 20 + j15 + j20 - 54 + 64$$

$$= 30 + j87$$

$$j^2 = -1$$

$$\Delta_1 = \begin{vmatrix} 100 & -j8 \\ 0 & 5+j18 \end{vmatrix} = 100(5+j18)$$


$$\Delta_2 = \begin{vmatrix} 4+j3 & 100 \\ -j8 & 0 \end{vmatrix} = +j800$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{500 + j1800}{30 + j87} = 20.3 \angle 3.5^\circ$$


convert into polar and do ÷

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{0 + j800}{30 + j87} = 8.7 \angle 119.03^\circ$$

DA-II
4.

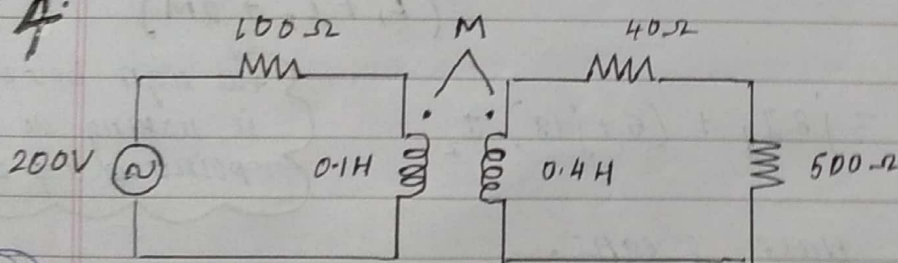

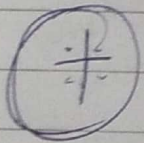$f = 159.2 \text{ Hz}$
 $k = 0.1$, Find
 loop currents
 and load
 current



First convert everything in ohm,


Given $L_1 = 0.1 \text{ H}$ $L_2 = 0.4 \text{ H}$

$$X_1 = 2\pi f L_1 = 2 \times 3.14 \times 159.2 \times 0.1 = 100 \Omega$$


$$X_2 = 2\pi f L_2 = 2 \times 3.14 \times 159.2 \times 0.4 = 400 \Omega$$

$$M = k \sqrt{L_1 L_2} = 0.1 \sqrt{0.1 \times 0.4} = 0.02 \text{ H}$$
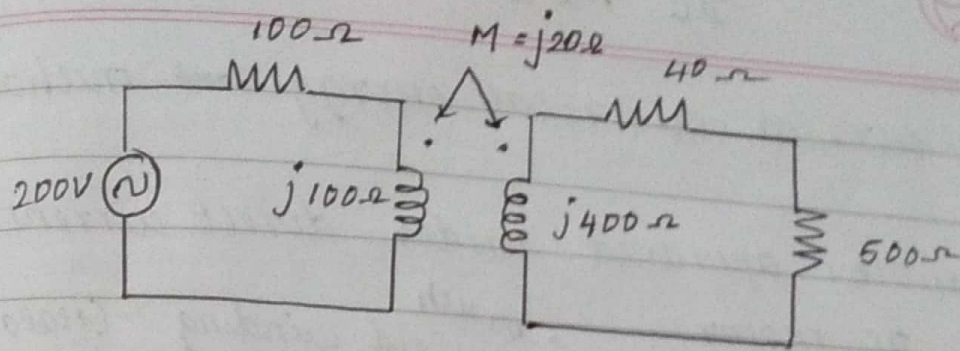
$$X_M = 2\pi f M = 2 \times 3.14 \times 159.2 \times 0.02 = 20 \Omega$$



converting into electrically equivalent circuit,

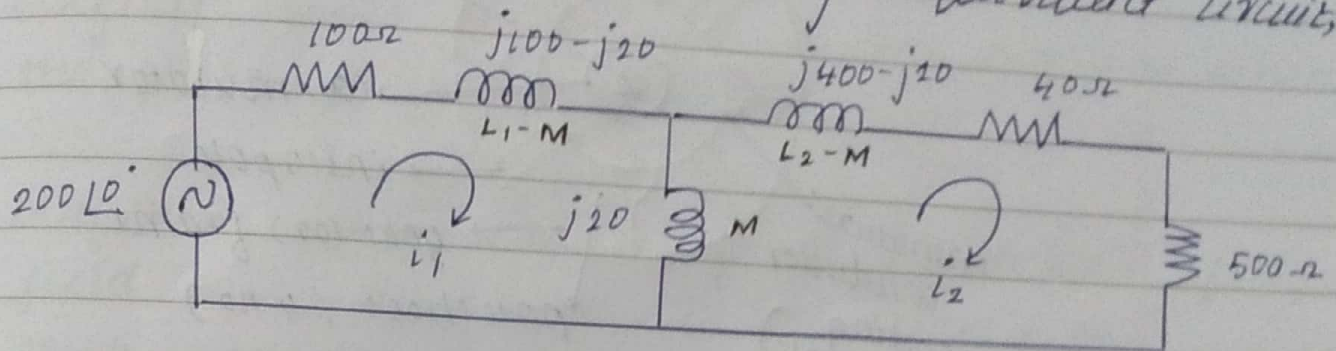

Loop 1: $200 \angle 0^\circ = 100 I_1 + j80 I_1 + j20 I_1 - j20 I_2$
 $200 = (100 + j100) I_1 - j20 I_2$

Loop 2: $0 = 500 I_2 + j20 I_2 - j20 I_1 + j380 I_2 + 40 I_2$
 $0 = (540 + j400) I_2 - j20 I_1$

on solving we get, $I_1 = 1.41 \angle -44.7^\circ, I_2 = 0.042 \angle 1.7^\circ$

$I_1 = 44.8 - j88.2$ $I_2 = 8.7 + j90$

current through load,

$$I_{RL} = 500 \times I_2$$

$$= 500 (8.7 + j90)$$

$$I_{RL} = 4350 + j45000$$