



Continuous Assessment Test - I - November - 2022

Programme	: B.Tech(EEE/ECE/ECM/Civil)	Semester	: Fall 2022-23
Course	: BEEE102L/IEEE102L - Basic Electrical & Electronics Engineering	Slot	: E1 + TE1
Faculty	: Sasipriya P (CH2022231700037)	Faculty	: Inayathullaah M A (CH2022231700039)
Faculty	: Meera P S (CH2022231700041)	Faculty	: Mohd Aneesh (CH2022231700047)
Faculty	: Chendur R (CH2022231700049)	Faculty	: Mohd Imran (CH2022231700051)
Faculty	: Srimathi R (CH2022231700187 / CH2022231700743)	Class Nbr	: Rani S (CH2022231701005)
Time	: $1\frac{1}{2}$ hours	Max. Marks	: 50

Answer all the Questions

1. Find v_x in the circuit shown in Fig. 1.

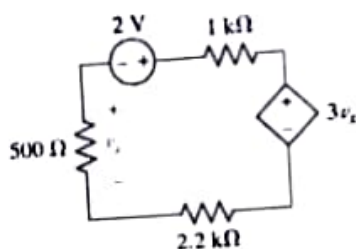


Fig. 1

2. Find the current i through the 4Ω resistance in the circuit shown in Fig. 2 using nodal analysis.

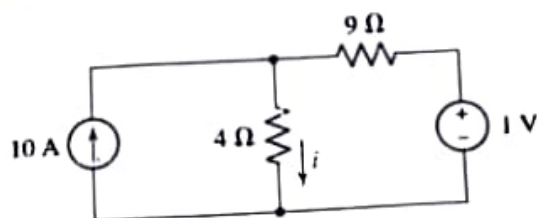


Fig. 2

3. Find the equivalent resistance and the current supplied by the voltage source in the circuit shown in Fig. 3.

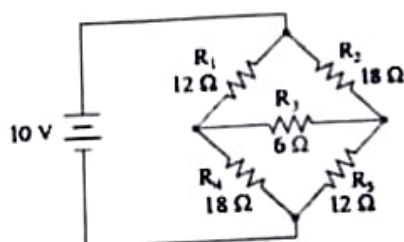


Fig. 3

Using superposition theorem, find the voltage v in the circuit shown in Fig. 4. (10)

(5)

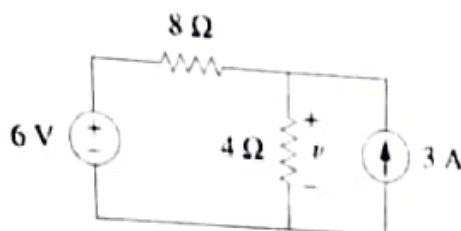


Fig. 4

5. Find the Thevenin Equivalent across the terminal $a-b$ for the circuit shown in Fig. 5. What value of load resistor connected across terminals $a-b$ will absorb maximum power from the circuit? Calculate the maximum power absorbed by the load resistor? (10)

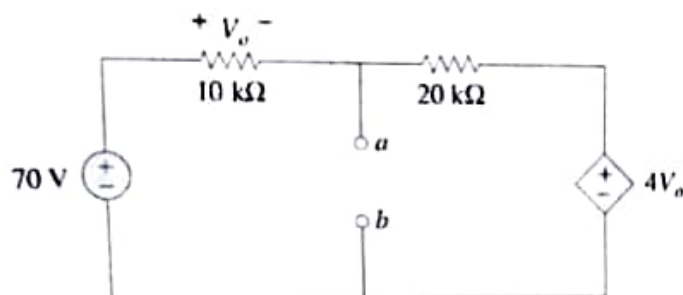


Fig. 5

6. Compute the current $i(t)$, apparent power (VA) supplied by the source and power factor of the source for the circuit shown in Fig. 6. $v_s(t) = 10 \sin(100\pi t + 45^\circ)V$. (Take $1 \angle 0^\circ = 1 \angle 0$ as reference) (10)
- Load 1 : $P = 100kW$, power factor = 0.6 (Leading)
- Load 2 : $Q = 100kVAR$, power factor = 0.8 (Lagging)

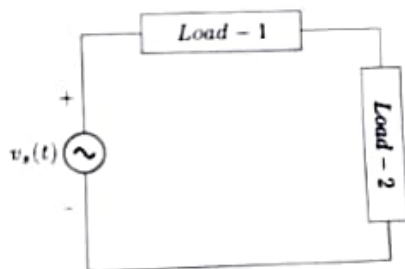


Fig. 6

7. In the series RC circuit excited by the alternating voltage source $v(t) = 10 \cos(100t)$ with $R = 10\Omega$ and $C = 0.002F$ compute the following. (10)

- RMS value of the voltage $v(t)$
- Impedance of the circuit
- the steady state current ($i(t)$) supplied by the source
- Compute the power supplied (with Units) by the source ($S = P + jQ$).
- RMS value of the voltage, if $v(t) = 10 \cos(100t + 30)$

↔ ↔ ↔