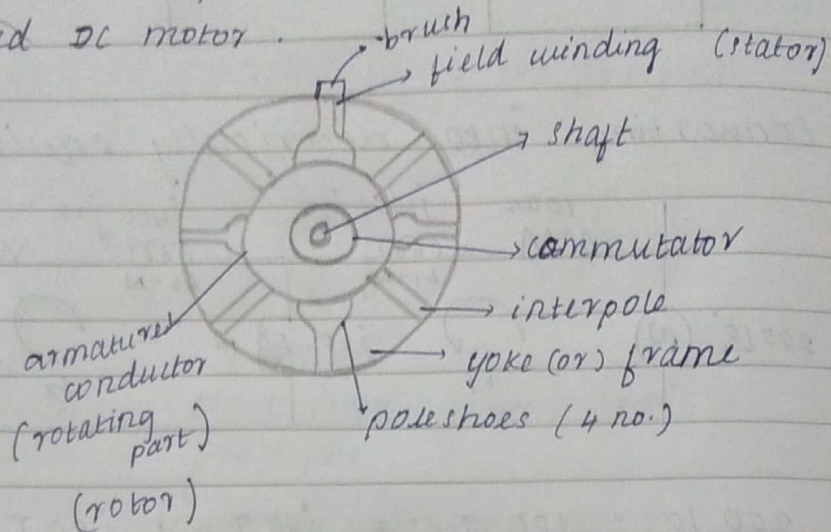


DC Motor

conversion: direct current electrical energy  $\rightarrow$  mechanical en.

→ Any motor operated under direct current is called DC motor.



Armature conductor: cylinder of electrical laminations that are insulated from one another.


commutator: commutator of DC motor is a cylindrical structure made of copper segment staked together but insulated from each other by mica.

→ primary function is to supply current to armature pointing.

Brushes: → Made with graphite (or) carbon structure  
→ conduct electric current from electric circuit to rotating commutator.

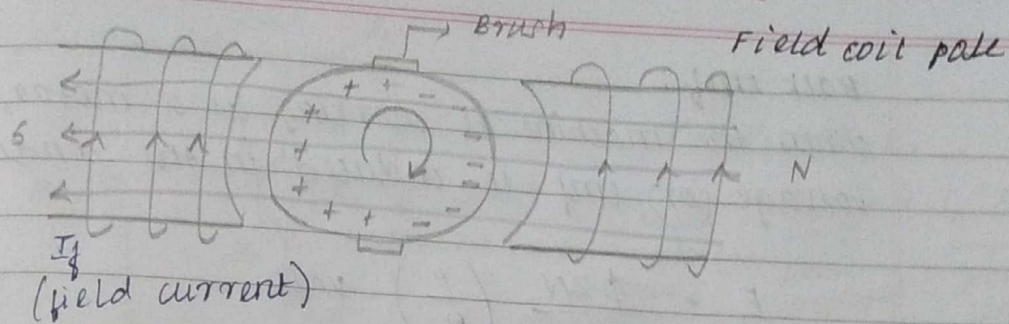commutator + brush : both together transmits the power from static electrical circuit to mechanically rotating motor region.





- Magnetic field is induced in the air gap when the field coil is energised.
  - Magnetic field enters from North pole of field coil and leaves the DC motor at south pole of field coil.
  - Conductors at interpole are subjected to force of same intensity but in opposite direction. These two opposing forces create a torque that causes motor armature to rotate.
- a current carrying conductor
- principle: → When kept in magnetic field it experiences a force which produces a torque.
- (or)
- When  $\vec{E}$  and  $\vec{M}$  fields interact, the mechanical force arises.

- Magnitude of force experienced by conductor is given by,

$$F = B l I \text{ (N)}$$

$\downarrow$                        $\downarrow$                        $\downarrow$   
 magnetic field      length      current  
 density              of  
 conductor

- Direction of motion is given by Fleming's left hand rule.
  - Fore finger - Direction of field
  - Middle - Direction of current
  - Thumb - Direction of motion.



### Back emf:

When the machine is working as a motor, the voltage (or) emf is induced in the conductor.

$$E_b = \frac{\phi Z N}{60} \left( \frac{P}{A} \right) \text{ volts}$$

$\phi$  - flux per pole


$Z$  - total no. of conductors

$N$  - speed of rotation (rpm)

$P$  - no. of poles

$A$  - no. of parallel paths.

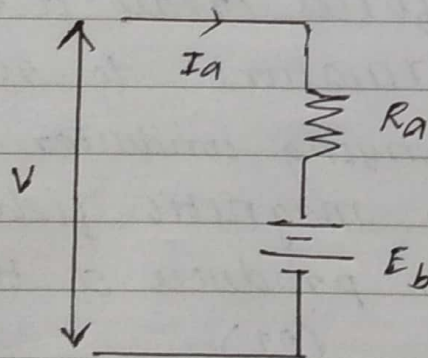Windings  $\begin{cases} A = P \rightarrow \text{Lap winding} \\ A = 2 \rightarrow \text{Wave winding} \end{cases}$




$$V = E_b + I_a R_a \Rightarrow I_a = \frac{V - E_b}{R_a}$$

Labels for the equation above:

- $V$ : applied voltage
- $E_b$ : back emf
- $I_a$ : armature current
- $R_a$ : armature resistance

$$\text{net voltage} = V - E_b$$

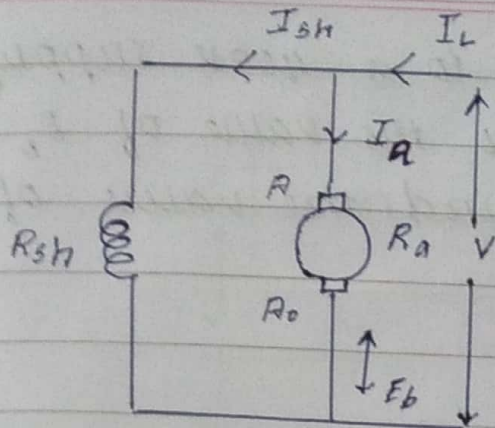

$$V = E_b + I_a R_a$$

$$VI_a = E_b I_a + I_a^2 R_a$$

electric power supply to armature
power developed in motor
power lost in armature

power developed in motor depends only on armature current as  $V$  and  $R_a$  are constant

$$P_m = E_b I_a$$

$$P_m = VI_a - I_a^2 R_a$$

$$\frac{dP_m}{dI_a} = V - 2I_a R_a$$

For max. mechanical power  $\frac{dP_m}{dI_a} = 0$

$$(ii) \quad V - 2I_a R_a = 0$$

$$I_a R_a = \frac{V}{2}$$

W.K.T  $V = E_b + I_a R_a$

$$V = E_b + \frac{V}{2}$$

$$E_b = \frac{V}{2}$$

(ie) power developed in armature is max. when  $E_b = \frac{V}{2}$



1. A DC motor connected to a 460V supply has  $R_a = 0.15 \Omega$  a) calculate the value of  $E_b$  when  $I_a = 120 \text{ A}$  b) Find the value of  $I_a$  when  $E_b = 447 \text{ V}$ .

a)  $V = E_b + I_a R_a$   
 $460 = E_b + 120 (0.15)$   
 $E_b = 442 \text{ V}$

b)  $V = E_b + I_a R_a$   
 $460 = 447 + I_a (0.15)$   
 $\frac{13}{0.15} = I_a$

$I_a = 86 \text{ amp.}$


2. A DC motor takes  $I_a = 150 \text{ A}$  at 440V. If the armature circuit has  $R_a = 0.15 \Omega$ , Find  $E_b$ .

$V = I_a R_a + E_b$   
 $E_b = V - I_a R_a$   
 $= 440 - (150)(0.15)$   
 $E_b = 417.5$

### Types of DC Motor

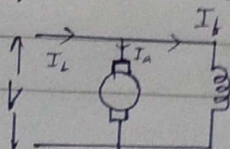- 1) Self excited motor
  - 2) Separately excited motor
- 3 types of self excited
- a) DC shunt motor
  - b) DC series motor
  - c) DC compound motor


DC shunt: Field winding connected in parallel to armature.



$I_a = I_L - I_f$

$V = E_b + I_a R_a$

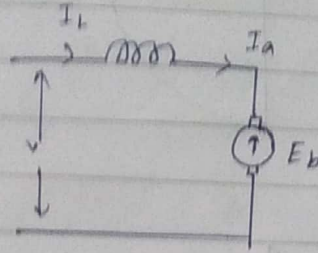DC series: Field winding connected in series to armature




$$I_a = I_L = I_f$$


$$V = E_b + I_a R_a + I_a R_{se}$$

$$V = E_b + I_a (R_a + R_{se}) \text{ series field resistance}$$

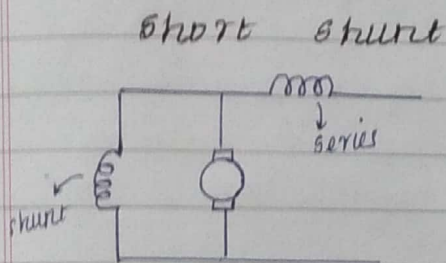compound: (shunt + series) → long shunt / short shunt depending on connections.



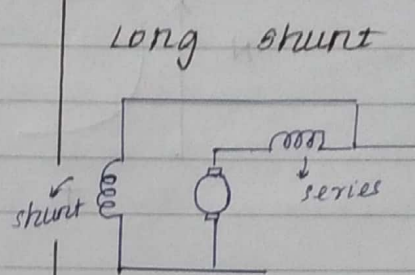Series field winding is connected in series with the parallel combination of armature and shunt field.



Series field winding is connected in series with the armature.

Characteristics of DC motor: (based on speed and torque)

$$T_a \propto I_a$$

(torque)      (current)

$$N \propto E_b / \phi$$

(speed)

- Torque armature current characteristics
- speed armature current characteristics
- speed torque armature current characteristics

Now draw all the above three characteristics graph for separately excited motor.



variable speed motor


series motor charac.:

1.

$$T \propto \phi I_a$$

$$\phi \propto I_a$$

$$\therefore T \propto I_a^2$$

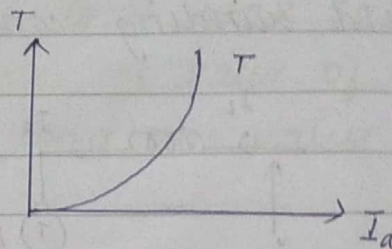


2.


$$N \propto E_b / \phi$$

$$\phi \propto I_a$$

$$N \propto \frac{1}{I_a}$$



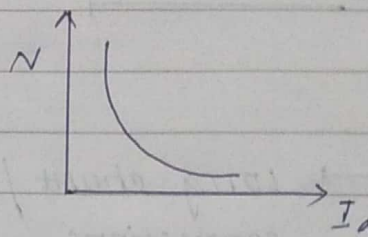


3.



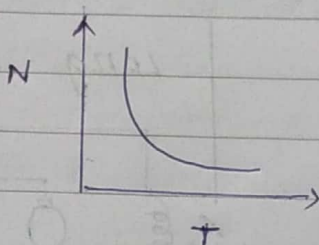


shunt motor characteristics:
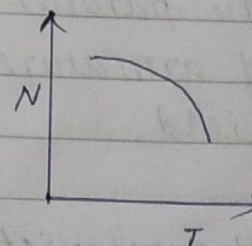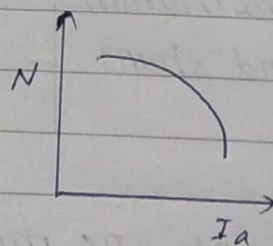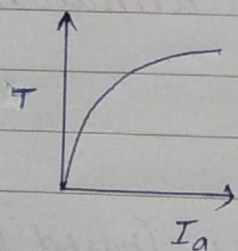
$$T \propto I_a \quad [\phi - \text{constant}]$$



compound motor characteristics:

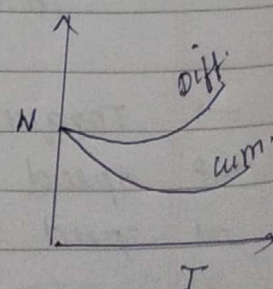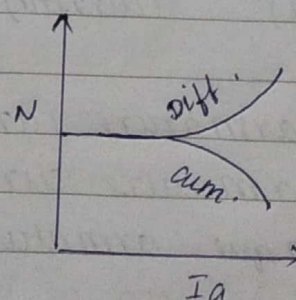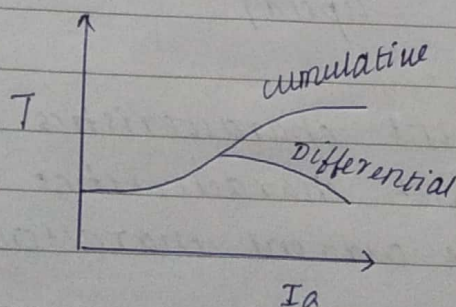


## Unbalanced Delta

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

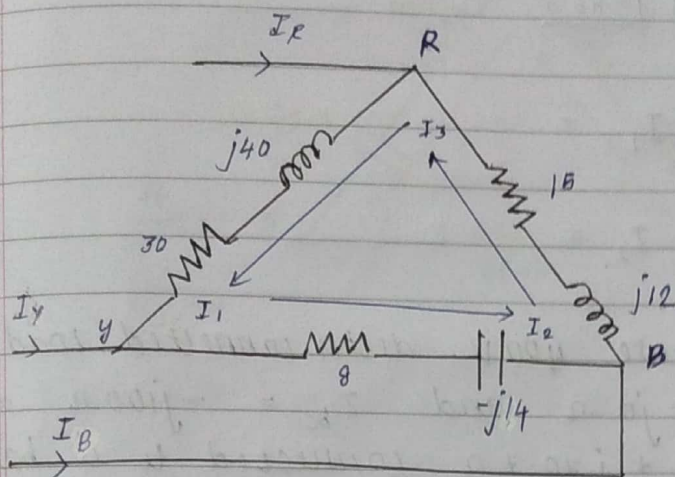1. The unbalanced delta load of Fig is supplied by balanced voltages of 200V in the positive sequence. Find line currents. Take  $V_{ab}$  as reference.



$I_1, I_2, I_3$  - phase current

$I_R, I_Y, I_B$  - line current

Given line voltage  $E_L = 200V$

$$E_{RY} = 200 \angle 0^\circ$$

$$E_{BR} = 200 \angle -240^\circ \text{ (or)} \\ 200 \angle 120^\circ$$

$$E_{YB} = 200 \angle -120^\circ$$

First we find phase currents,

$$I_1 = \frac{E_{RY}}{30 + j40} = \frac{200 \angle 0^\circ}{30 + j40} = 4 \angle -53.13^\circ \\ = (2.4 - j3.2) \text{ A}$$

↓  
value b/w branch  
R and Y

$$I_2 = \frac{E_{YB}}{8 - j14} = \frac{200 \angle -120^\circ}{8 - j14} = (6.2 - j10.74) \text{ A}$$

$$I_3 = \frac{E_{BR}}{15 + j12} = \frac{200 \angle -240^\circ}{15 + j12} = (1.6 + j10.3) \text{ A}$$



now we find line current

$$I_R = I_1 - I_3 \quad (I_3 \text{ is entering and } I_1 \text{ is leaving the point R})$$
$$= 13.53 \angle -86.5^\circ$$

$$I_Y = I_2 - I_1 =$$

$$I_B = I_3 - I_2 =$$