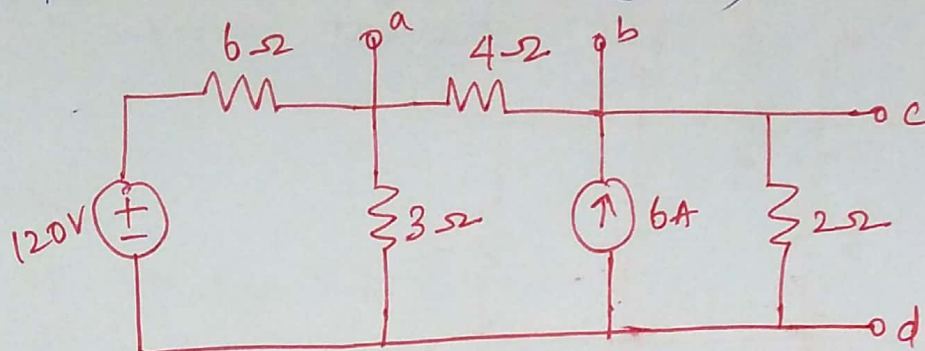



THEVENIN & NORTON EXAMPLES

- (1) Find the Thevenin & Norton Equivalents from the terminals (a-b) and (c-d)



from terminals (a-b)

Find V_{th} .

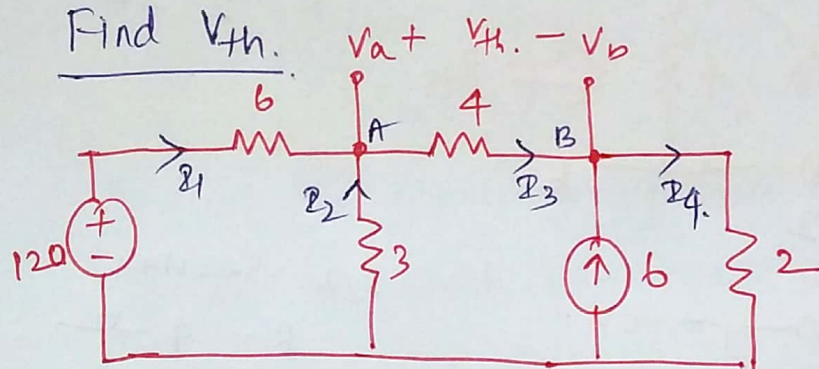

$$V_{th} = V_a - V_b$$

using nodal analysis find V_a , V_b , V_{th} .

At node (A), $I_1 + I_2 = I_3$

$$\frac{120 - V_a}{6} + \frac{0 - V_a}{3} = \frac{V_a - V_b}{4}$$

$\times 12$

$$240 - 2V_a - 4V_a = 3V_a - 3V_b$$

$$9V_a - 3V_b = 240$$

$$3V_a - V_b = 80 \rightarrow \textcircled{1}$$

At node (B),

$$6 + I_3 = I_4 \quad \times 4$$

$$6 + \frac{V_a - V_b}{4} = \frac{V_b}{2}$$

$$24 + \frac{3}{4}V_a - \frac{1}{4}V_b = 2V_b$$

$$-V_a + 3V_b = 24 \rightarrow \textcircled{2}$$



solving $\textcircled{1}$, $\textcircled{2}$, we get $V_a = 33$ $V_b = 19V$

$$V_{th} = V_a - V_b$$


$$\therefore \boxed{V_{th} = 14V}$$

②

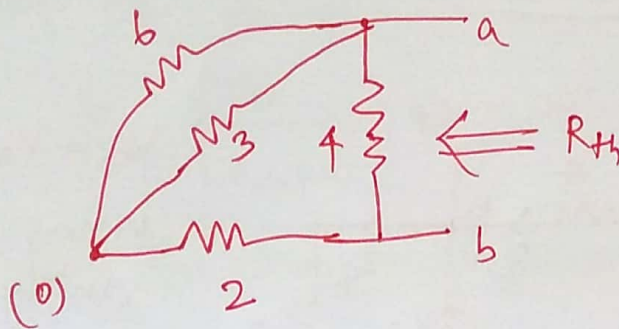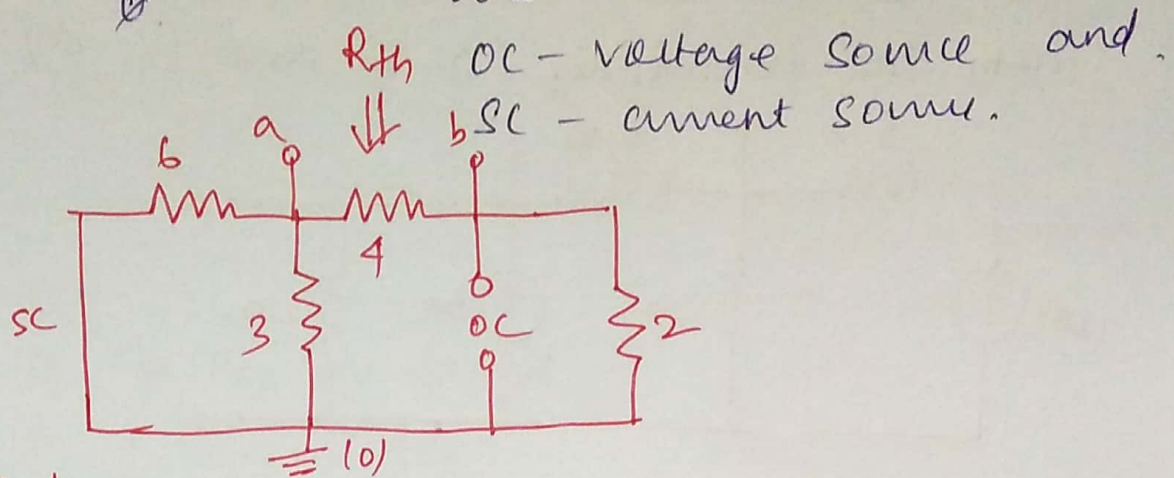To find R_{th} . (Turn off independent voltage and current sources).




b, 3 parallel.
 $R = 2 \Omega$

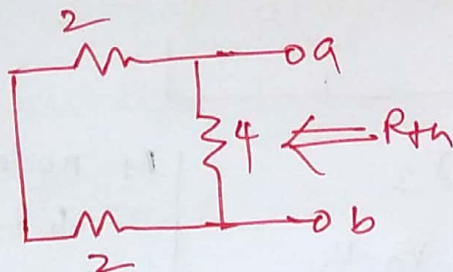


2, 2 series
 $R = 4 \Omega$
4, 4 parallel.
 $R_{th} = 2 \Omega$

THEVENIN EQUIVALENT.

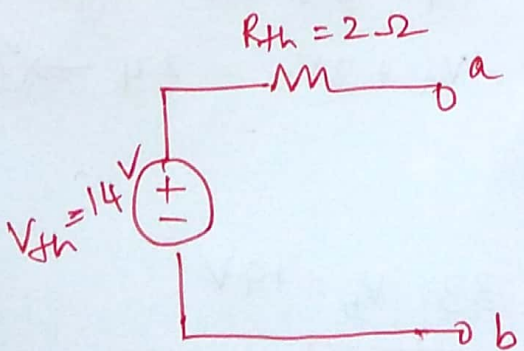


NORTON EQUIVALENT.

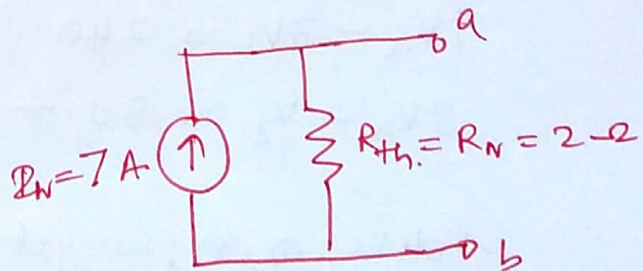

$$I_N = \frac{V_{th}}{R_{th}} \quad R_{th} = R_N$$

MAXIMUM POWER TRANSFER.

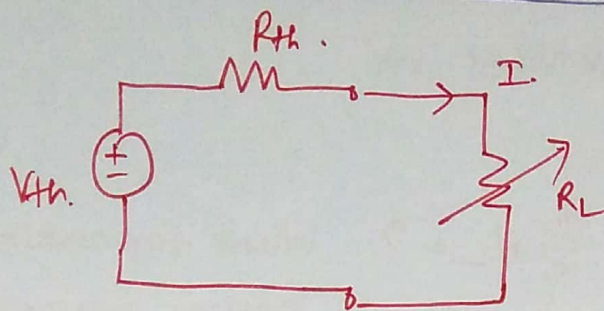


How?

If V_{th} , R_{th} are fixed
 $R_L \rightarrow$ variable load.

power $P = I^2 R_L$

$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

Power delivered to the load R_L

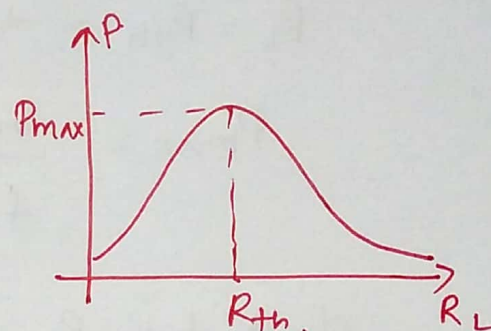

To find the maximum power and the value of R_L at which maximum power can be,
 , differentiate P with respect to R_L ,

$$\frac{dP}{dR_L} = 0.$$

$$R_{th} + R_L - 2R_L = R_{th} - R_L.$$


$$R_L = R_{th}.$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}.$$

①

For the circuit solved,

Thevenin equivalent is

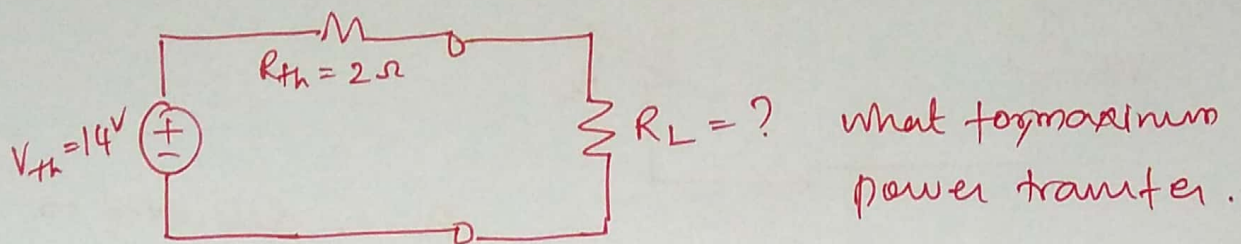


$$R_L = R_{th} = 2\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{14^2}{4 \times 2} = \underline{\underline{24.5 W}}$$

check for $R_L = 1\Omega$.

$$\text{Power delivered} = I^2 R_L$$

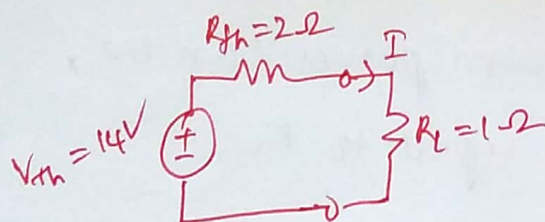


$$= \left(\frac{V_{th}}{R_L + R_{th}} \right)^2 R_L$$

$$= \frac{14^2}{(1+2)^2} \times 1$$

$$P_{1\Omega} = \underline{\underline{21.77 W}}$$

check for $R_L = 3\Omega$

$$\text{power delivered} = I^2 R_L$$

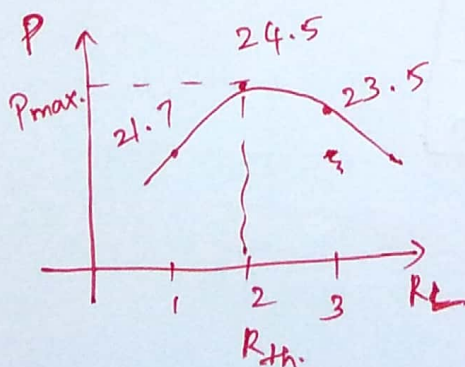

$$= \frac{V_{th}^2}{(3+2)^2} \times 3$$

$$= \underline{\underline{23.52 W}}$$