



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRICAL ENGINEERING

BEEE101L

Basic Electrical Engineering



Three phase systems

By,

Meera P. S.

Assistant Professor, SELECT


THE THREE-PHASE GENERATOR

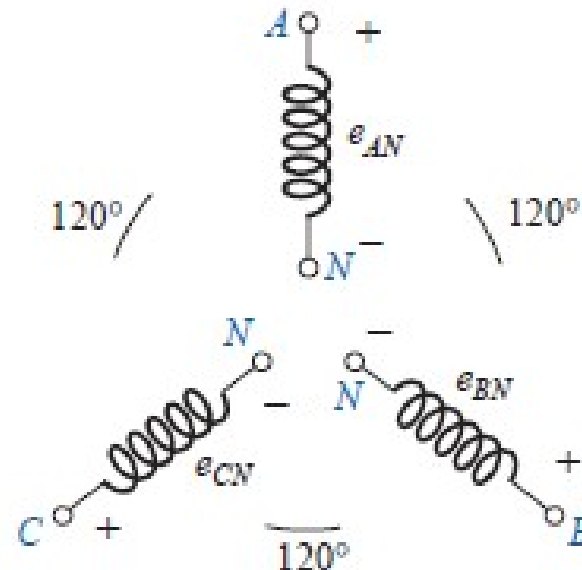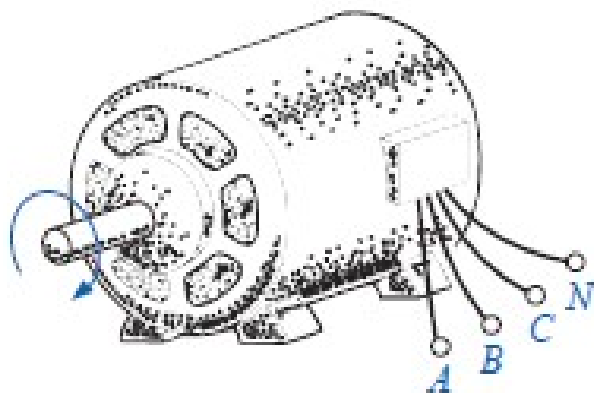

In particular, note that

at any instant of time, the algebraic sum of the three phase voltages of a three-phase generator is zero.



Three phase voltage

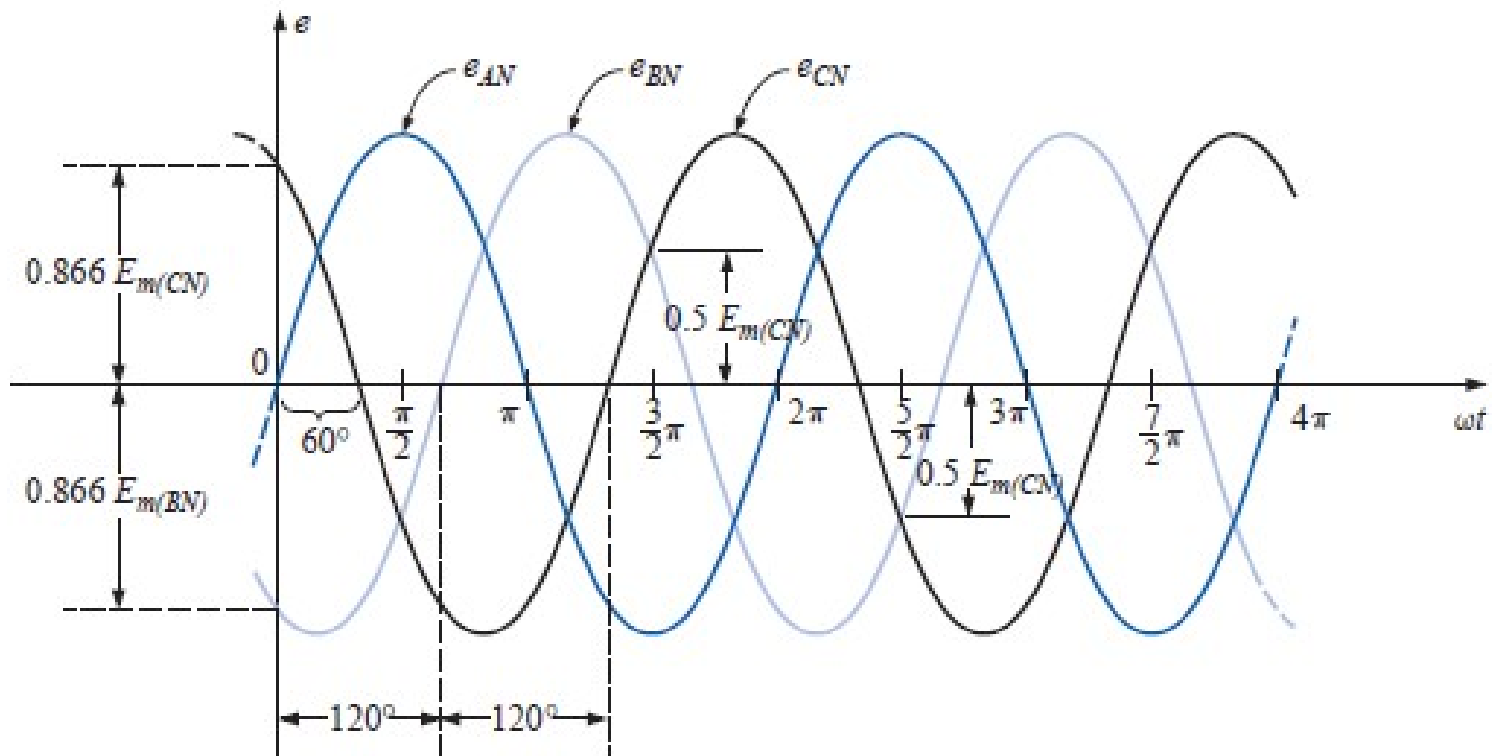

$$e_{AN} = E_{m(AN)} \sin \omega t$$


$$e_{BN} = E_{m(BN)} \sin(\omega t - 120^\circ)$$
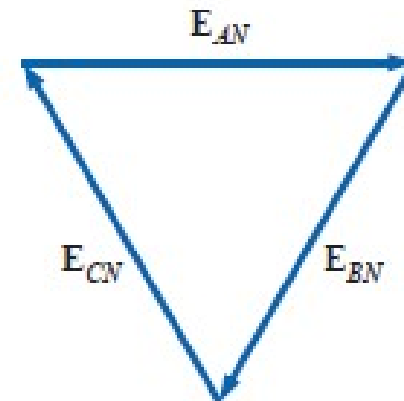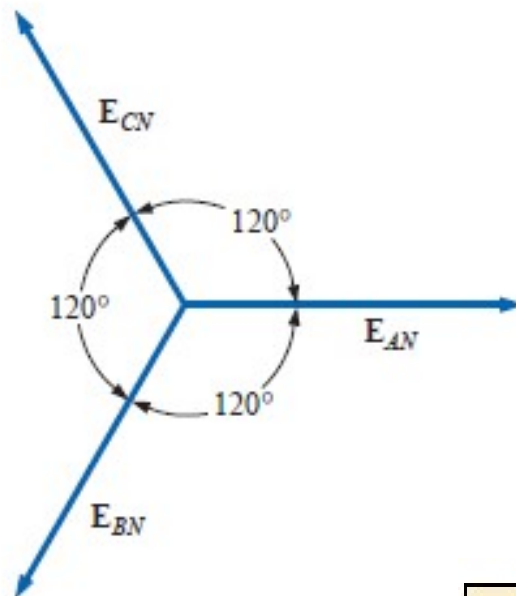
$$e_{CN} = E_{m(CN)} \sin(\omega t - 240^\circ) = E_{m(CN)} \sin(\omega t + 120^\circ)$$



$$E_{AN} + E_{BN} + E_{CN} = 0$$

THE Y-CONNECTED GENERATOR

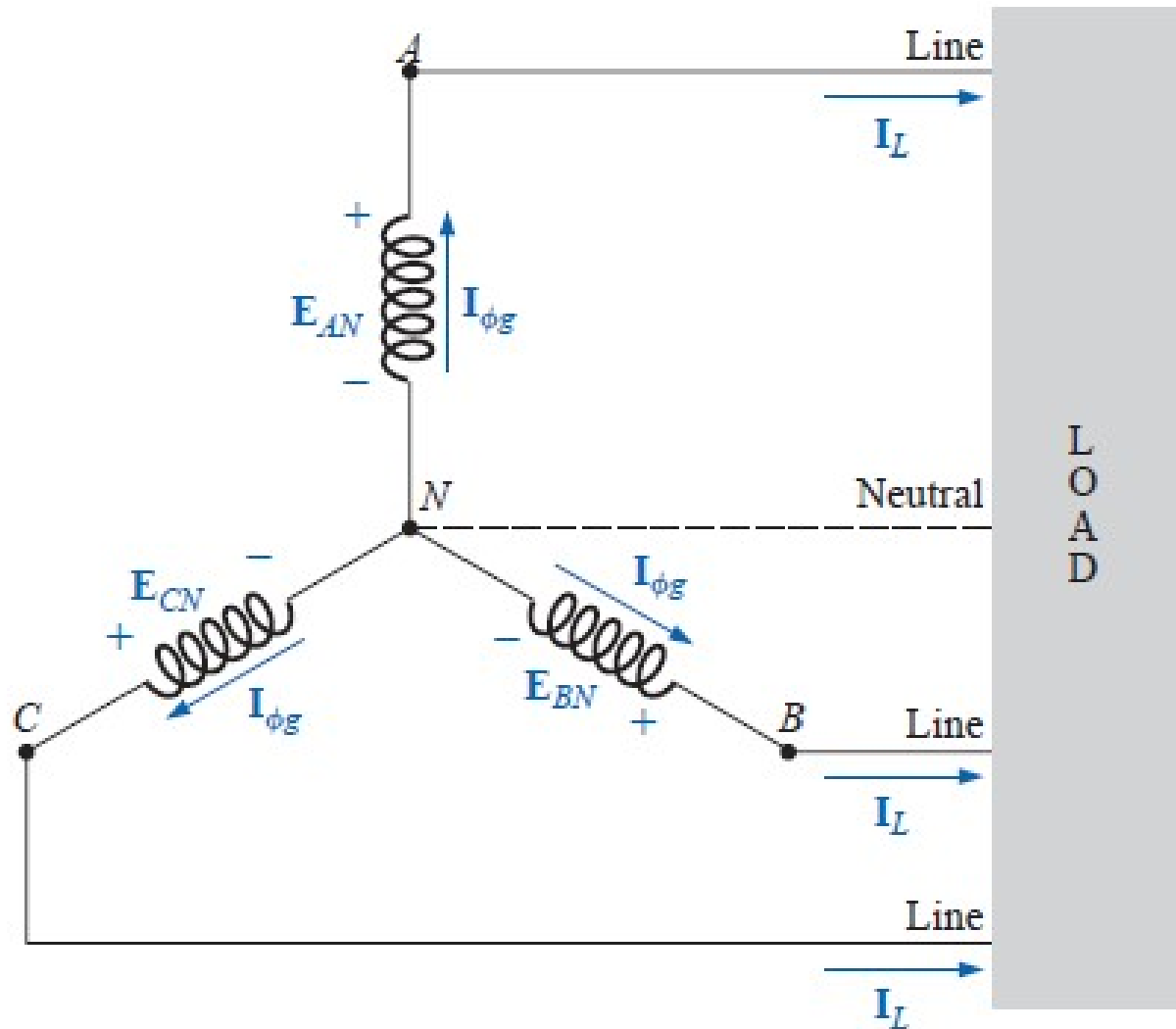


Y-CONNECTION

- The line current equals the phase current for each phase.


$$I_L = I_{\phi}$$

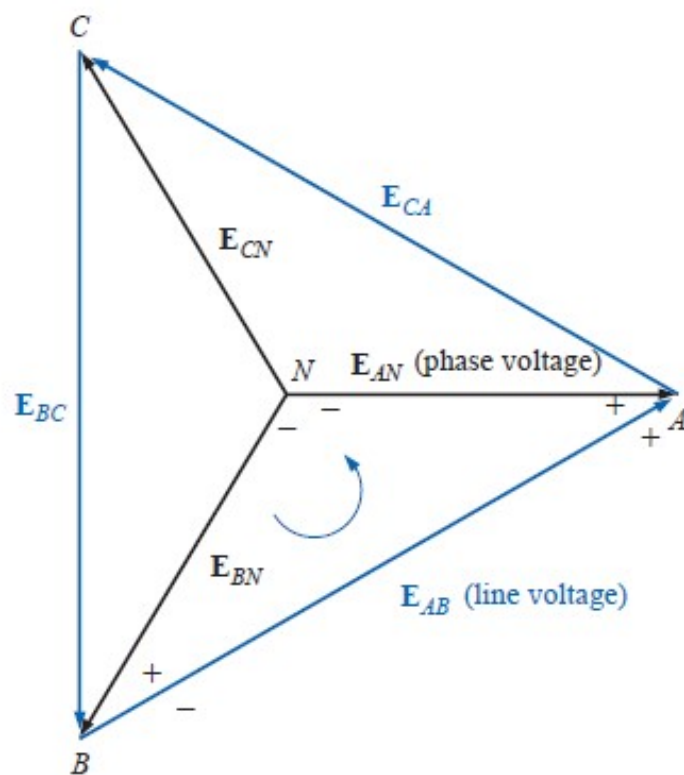- The voltage from one line to another is called a line voltage.



$$E_{AB} - E_{AN} + E_{BN} = 0$$
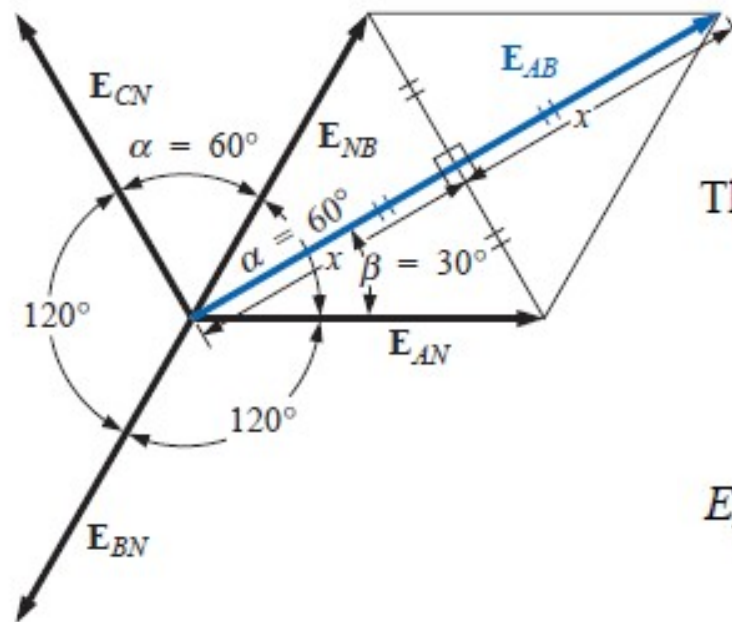
$$E_{AB} = E_{AN} - E_{BN} = E_{AN} + E_{NB}$$



The length x is

$$x = E_{AN} \cos 30^\circ = \frac{\sqrt{3}}{2} E_{AN}$$

$$E_{AB} = 2x = (2) \frac{\sqrt{3}}{2} E_{AN} = \sqrt{3} E_{AN}$$

Noting from the phasor diagram that θ of $E_{AB} = \beta = 30^\circ$, the result is

$$E_{AB} = E_{AB} \angle 30^\circ = \sqrt{3} E_{AN} \angle 30^\circ$$

and

$$E_{CA} = \sqrt{3} E_{CN} \angle 150^\circ$$

$$E_{BC} = \sqrt{3} E_{BN} \angle 270^\circ$$

$$E_L = \sqrt{3} E_\phi$$


In sinusoidal notation,

$$e_{AB} = \sqrt{2}E_{AB} \sin(\omega t + 30^\circ)$$


$$e_{CA} = \sqrt{2}E_{CA} \sin(\omega t + 150^\circ)$$

and
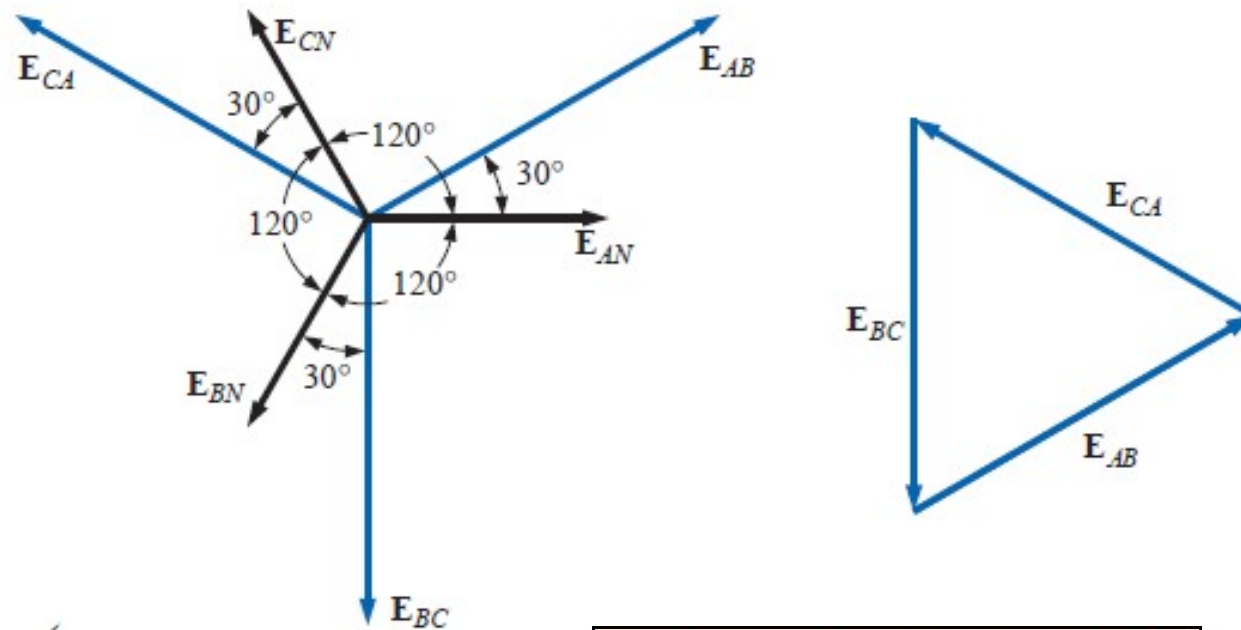
$$e_{BC} = \sqrt{2}E_{BC} \sin(\omega t + 270^\circ)$$




$$E_{AB} + E_{CA} + E_{BC} = 0$$

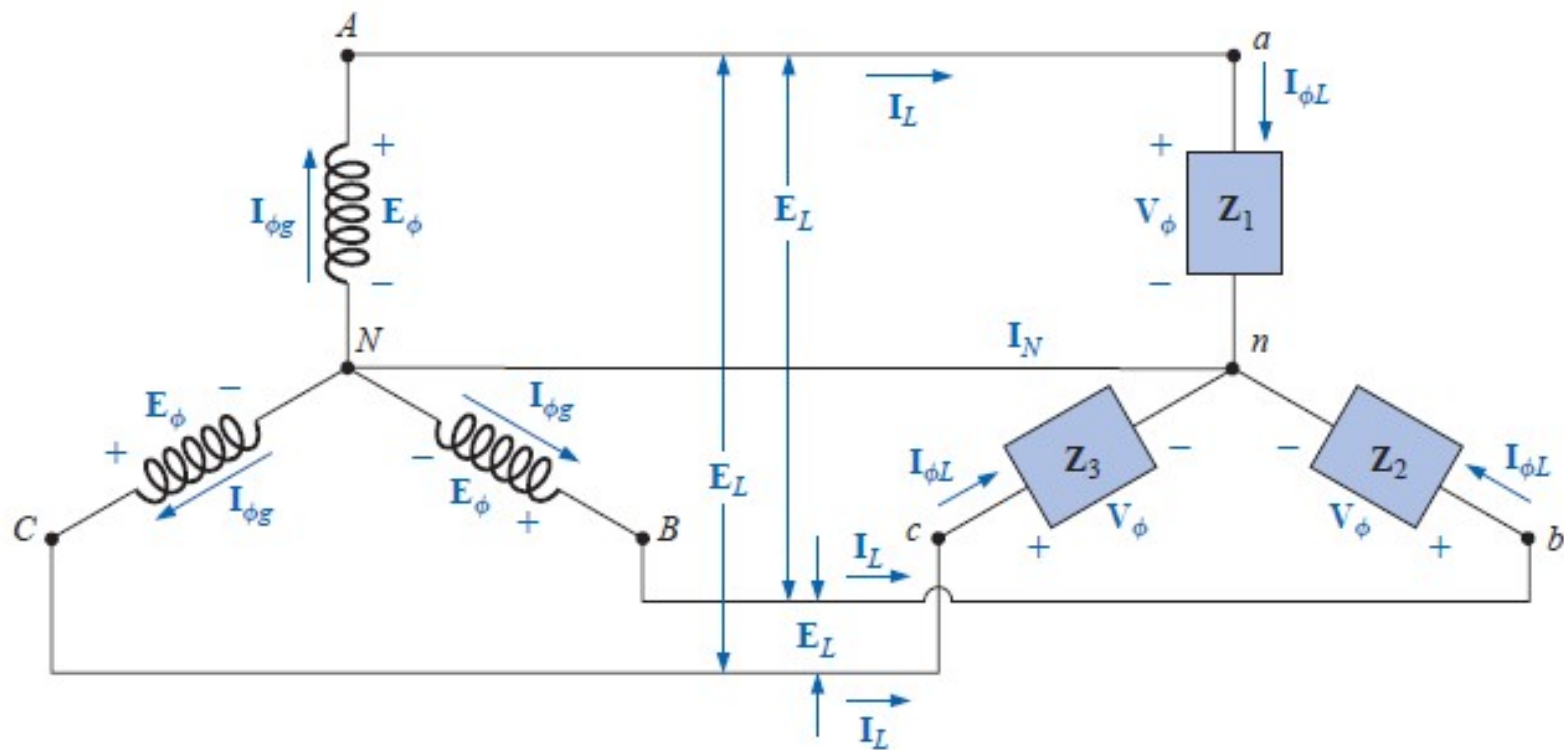

Y-connected generator with a Y-connected load.


DELTA CONNECTION

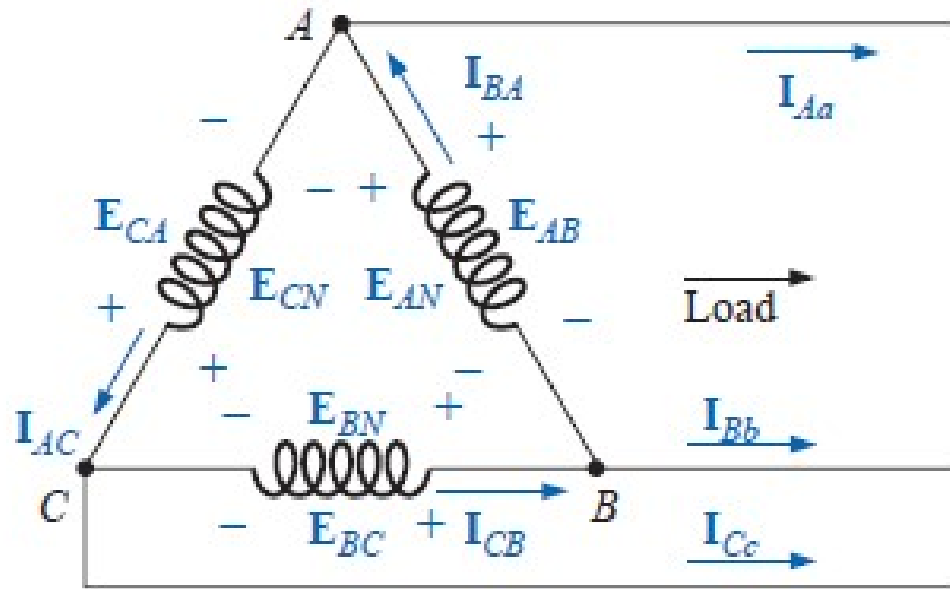

The phase and line voltages are equivalent

$$E_L = E_{\phi g}$$

DELTA CONNECTION

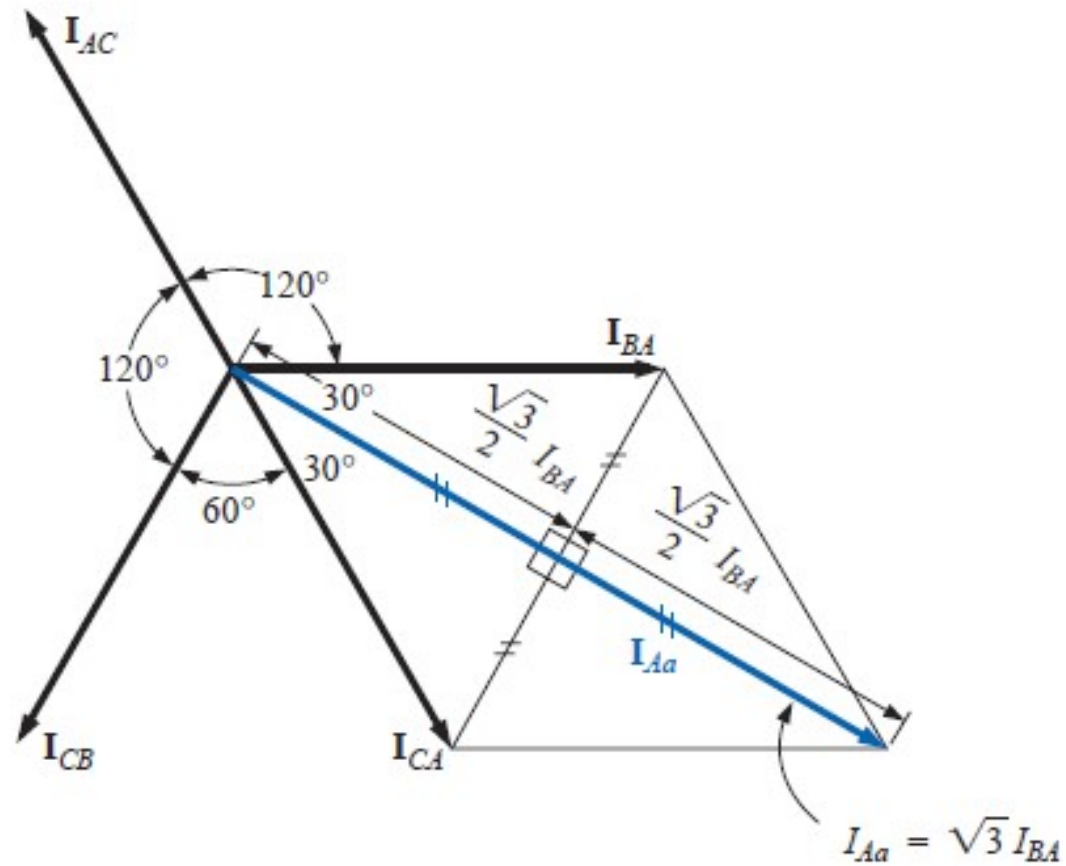

$$I_L = \sqrt{3} I_{\phi g}$$

Problem 1. Three loads, each of resistance $30\ \Omega$, are connected in star to a $415\ \text{V}$, 3-phase supply. Determine (a) the system phase voltage, (b) the phase current and (c) the line current.

For a star connection, $V_L = \sqrt{3}V_p$

Hence phase voltage, $V_p = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.6\ \text{V}$ or $240\ \text{V}$

Phase current, $I_p = \frac{V_p}{R_p} = \frac{240}{30} = 8\ \text{A}$

For a star connection, $I_p = I_L$

Hence the line current, $I_L = 8\ \text{A}$

Problem 2. A star-connected load consists of three identical coils each of resistance $30\ \Omega$ and inductance 127.3 mH . If the line current is 5.08 A , calculate the line voltage if the supply frequency is 50 Hz

Inductive reactance $X_L = 2\pi fL = 2\pi(50)(127.3 \times 10^{-3}) = 40\ \Omega$


Impedance of each phase $Z_p = \sqrt{R^2 + X_L^2} = \sqrt{30^2 + 40^2} = 50\ \Omega$

For a star connection $I_L = I_p = \frac{V_p}{Z_p}$

Hence phase voltage $V_p = I_p Z_p = (5.08)(50) = 254\text{ V}$

Line voltage $V_L = \sqrt{3}V_p = \sqrt{3}(254) = 440\text{ V}$

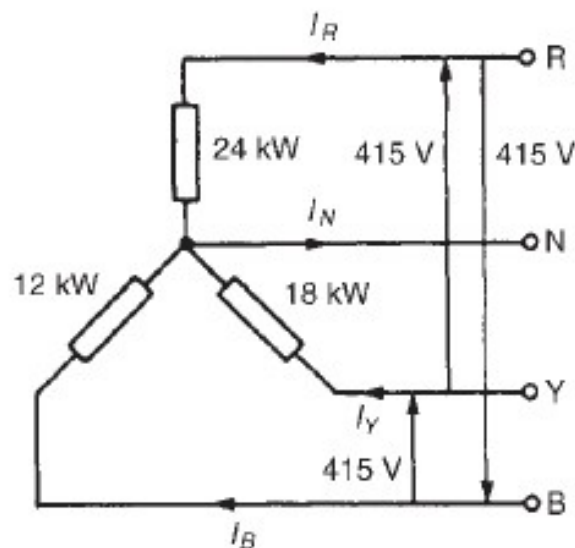Problem . A 415 V, 3-phase, 4 wire, star-connected system supplies three resistive loads as shown in Figure 19.7. Determine (a) the current in each line and (b) the current in the neutral conductor.



For a star-connected system $V_L = \sqrt{3}V_p$

Hence
$$V_p = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 240 \text{ V}$$

Since current $I = \frac{\text{Power } P}{\text{Voltage } V}$ for a resistive load

then
$$I_R = \frac{P_R}{V_R} = \frac{24\,000}{240} = 100 \text{ A}$$

$$I_Y = \frac{P_Y}{V_Y} = \frac{18\,000}{240} = 75 \text{ A}$$

$$I_B = \frac{P_B}{V_B} = \frac{12\,000}{240} = 50 \text{ A}$$

Alternatively, by calculation, considering I_R at 90° , I_B at 210° and I_Y at 330° :

$$\begin{aligned}\text{Total horizontal component} &= 100 \cos 90^\circ + 75 \cos 330^\circ + 50 \cos 210^\circ \\ &= 21.65\end{aligned}$$

$$\begin{aligned}\text{Total vertical component} &= 100 \sin 90^\circ + 75 \sin 330^\circ + 50 \sin 210^\circ \\ &= 37.50\end{aligned}$$

$$\text{Hence magnitude of } I_N = \sqrt{(21.65^2 + 37.50^2)} = 43.3 \text{ A}$$

Problem . Three identical coils each of resistance $30\ \Omega$ and inductance 127.3 mH are connected in delta to a 440 V , 50 Hz , 3-phase supply. Determine (a) the phase current, and (b) the line current.

Phase impedance, $Z_p = 50\ \Omega$

Phase current,
$$I_p = \frac{V_p}{Z_p} = \frac{V_L}{Z_p} = \frac{440}{50} = 8.8\text{ A}$$

For a delta connection, $I_L = \sqrt{3}I_p = \sqrt{3}(8.8) = 15.24\text{ A}$

Problem . Three coils each having resistance $3\ \Omega$ and inductive reactance $4\ \Omega$ are connected (i) in star and (ii) in delta to a 415 V, 3-phase supply. Calculate for each connection (a) the line and phase voltages and (b) the phase and line currents.

For a star connection: $I_L = I_p$ and $V_L = \sqrt{3}V_p$

A 415 V, 3-phase supply means that the

line voltage, $V_L = 415\ \text{V}$

$$\text{Phase voltage, } V_p = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 240\ \text{V}$$

$$\begin{aligned}\text{Impedance per phase, } Z_p &= \sqrt{(R^2 + X_L^2)} = \sqrt{(3^2 + 4^2)} \\ &= 5\ \Omega\end{aligned}$$

$$\text{Phase current, } I_p = \frac{V_p}{Z_p} = \frac{240}{5} = \mathbf{48 \text{ A}}$$

$$\text{Line current, } I_L = I_p = \mathbf{48 \text{ A}}$$

$$\text{For a delta connection: } V_L = V_p \text{ and } I_L = \sqrt{3}I_p$$

$$\text{Line voltage, } V_L = \mathbf{415 \text{ V}}$$

$$\text{Phase voltage, } V_p = V_L = \mathbf{415 \text{ V}}$$

$$\text{Phase current, } I_p = \frac{V_p}{Z_p} = \frac{415}{5} = \mathbf{83 \text{ A}}$$

$$\text{Line current, } I_L = \sqrt{3}I_p = \sqrt{3}(83) = \mathbf{144 \text{ A}}$$