

# BEEE101L – Basic Electrical Engineering

## Node Analysis – Simple Problems

---



**VIT<sup>®</sup>**

**Vellore Institute of Technology**

(Deemed to be University under section 3 of UGC Act, 1956)



# Objective

- To introduce the beginners to node voltage analysis.
- To apply nodal analysis to solve electric circuits.

# Node Analysis

- Kirchhoff's current law is the key to apply node analysis.
- KCL: *Algebraic sum of currents at any node in a circuit is zero.*
- Sign conventions are important while writing KCL equations.
- Identify the nodes and reference node in the circuit.
- At any node, assume the incoming branch currents are negative and outgoing branch currents are positive.
- Write KCL for each node and express the currents as function of node voltages and the resistances ( $I=V/R$  form).
- Solve the simultaneous equations to find node voltages.

# Node Analysis – Inspection Method

- Assume current flow in **all** nodes in **to the node**.
- Form a square matrix, whose size is equal to no. of nodes in the circuit.
- The diagonal elements is the sum of **inverse of all resistances** in the loop.
- The off-diagonal elements are the sum inverse of resistances common to the neighboring node.
- If no common resistances are present, then corresponding element is zero.

$$G_{11} = \frac{1}{R_{11}}$$


$$G_{12} = \frac{1}{R_{12}}$$

$$\begin{bmatrix} G_{11} & -G_{12} & -G_{13} \\ -G_{21} & G_{22} & -G_{23} \\ -G_{31} & -G_{31} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{aligned} V &= IR \\ I &= \frac{V}{R} = VG \\ G &= \frac{1}{R} \end{aligned}$$

- $I_1, I_2, \dots$  are the branch currents and  $V_1, V_2, \dots$  are the node voltages

# Writing Node Equations

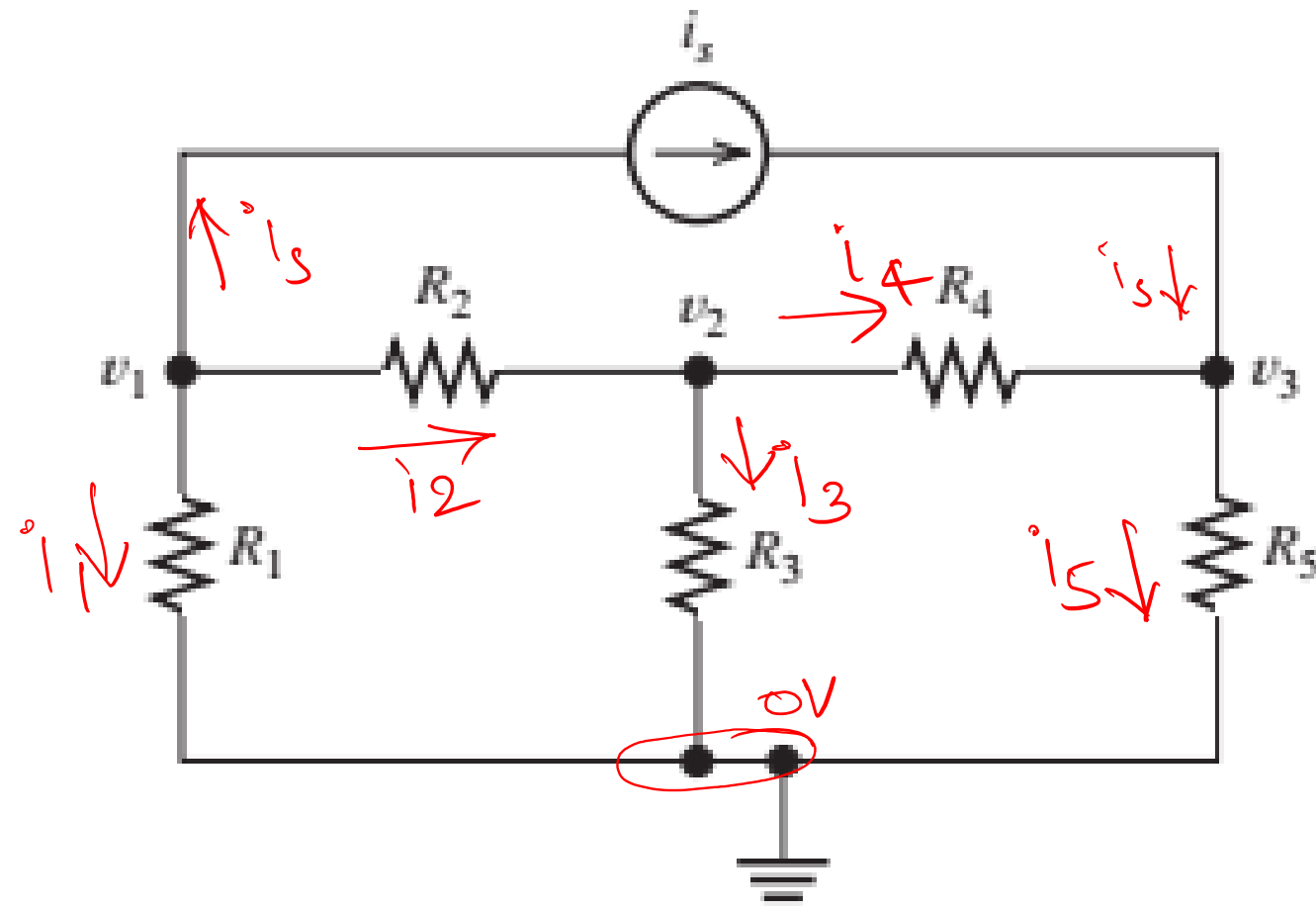

No. of nodes = 3

No. of KCL eqn = 3.

① Assume the current direction

Applying KCL to node 1

$$i_1 + i_2 + i_s = 0$$

$$\frac{v_1 - 0}{R_1} + \frac{v_1 - v_2}{R_2} + i_s = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_1 - \frac{v_2}{R_2} = -i_s \quad \text{--- (1)}$$

Apply KCL at node 2:

$$-i_2 + i_3 + i_4 = 0$$


$$-\left(\frac{v_1 - v_2}{R_2}\right) + \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4} = 0$$

$$-\frac{v_1}{R_2} + v_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_2}\right) - \frac{v_3}{R_4} = 0 \quad \text{--- (2)}$$

Applying KCL at node 3:

$$i_s + i_4 = i_5$$

# Writing Node Equations

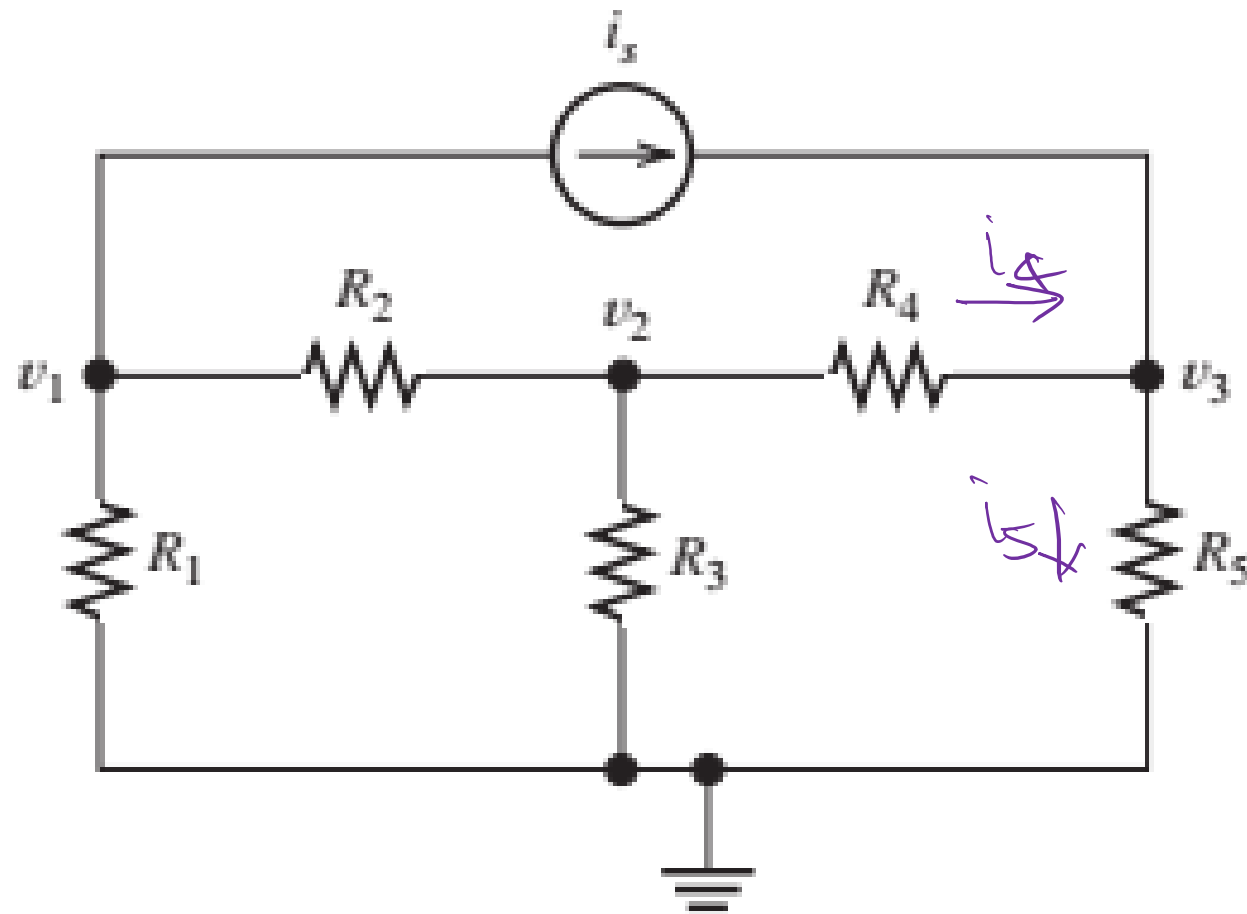

$$\textcircled{1} \Rightarrow \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_1 - \frac{1}{R_2} v_2 = -i_s$$

$$\textcircled{2} \Rightarrow -\frac{1}{R_2} v_1 + \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_2 - \frac{1}{R_4} v_3 = 0$$

$$\textcircled{3} \Rightarrow -\frac{1}{R_4} v_2 + \left( \frac{1}{R_4} + \frac{1}{R_5} \right) v_3 = i_s$$

$$i_s + i_4 = i_5$$


$$i_s = i_5 - i_4$$

$$= \frac{v_3}{R_5} - \left( \frac{v_2 - v_3}{R_4} \right)$$

$$i_s = -\frac{v_2}{R_4} + v_3 \left( \frac{1}{R_4} + \frac{1}{R_5} \right) \textcircled{3}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -i_s \\ 0 \\ i_s \end{bmatrix}$$

# Writing Node Equations

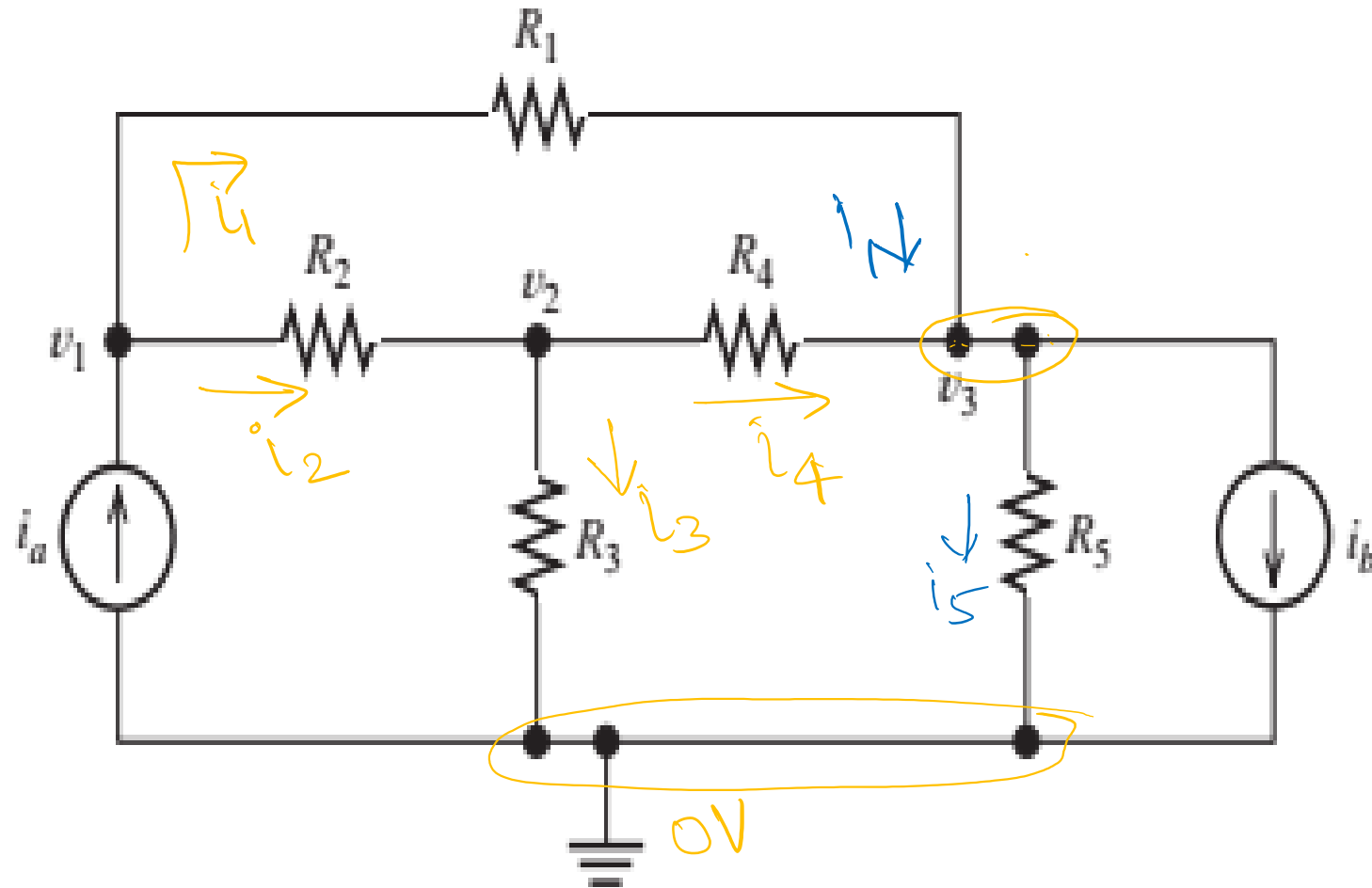

No. of nodes: 3

No. of KCL equations: 3

Applying KCL at node  $v_1$ :

$$i_a = i_1 + i_2$$

$$i_a = \frac{v_1 - v_3}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$i_a = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_1 - \frac{1}{R_2} v_2 - \frac{1}{R_1} v_3 \quad \text{--- (1)}$$

Apply KCL at node 2:

$$i_2 = i_3 + i_4$$

$$\frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4}$$

$$0 = -\frac{1}{R_2} v_1 + \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_2 - \frac{1}{R_4} v_3 \quad \text{--- (2)}$$

Apply KCL at node 3:

$$i_1 + i_4 = i_5 + i_b$$

$$-i_b = \frac{v_3}{R_5} - \left( \frac{v_2 - v_3}{R_4} \right) - \left( \frac{v_1 - v_3}{R_1} \right)$$


$$-i_b = i_5 - i_4 - i_1$$

$$-i_b = -\frac{1}{R_1} v_1 - \frac{1}{R_4} v_2 + \left( \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_5} \right) v_3 \quad \text{--- (3)}$$


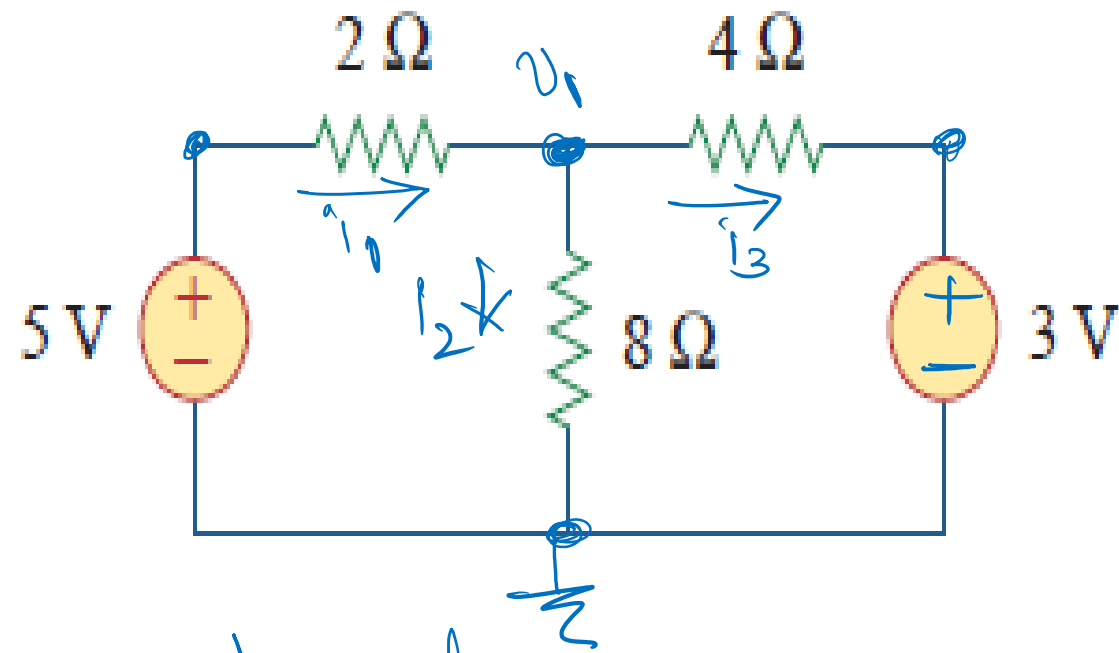
# Example 1:

- Solve for current through  $8\Omega$  resistor using KCL



KCL at node  $v_1$

$$i_1 = i_2 + i_3$$

$$\frac{5 - v_1}{2} = \frac{v_1}{8} + \frac{v_1 - 3}{4}$$

$$\frac{5}{2} + \frac{3}{4} = \frac{v_1}{2} + \frac{v_1}{8} + \frac{v_1}{4}$$

$$2.5 + 0.75 = v_1 \left[ \frac{4 + 1 + 2}{8} \right]$$

$$\frac{13}{4} = \frac{7v_1}{8}$$

$$v_1 = 3.71 \text{ V}$$

$$i_1 = \frac{5 - 3.71}{2} = 0.645 \text{ A}$$

$$i_2 = \frac{v_1}{8} = \frac{3.71}{8} = 0.463 \text{ A}$$

$$i_3 = \frac{3.71 - 3}{4} = 0.177 \text{ A}$$


To check:

$$\begin{array}{rcl} 0.463 & \leftarrow i_2 & \\ 0.177 & \leftarrow i_3 & \\ \hline 0.640 & \leftarrow i_1 & \end{array}$$



# Example 1:

KVL problem

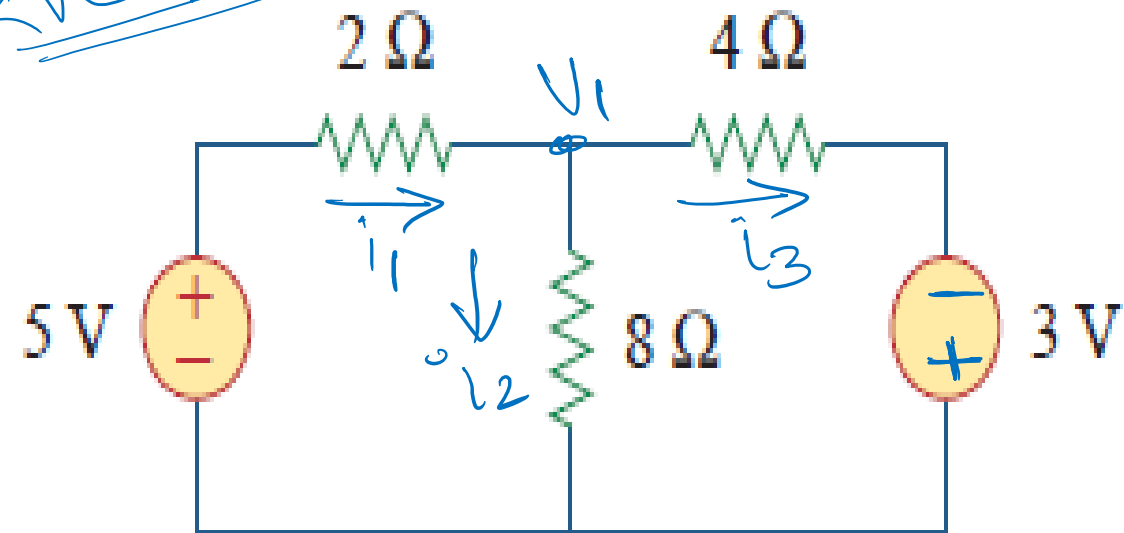

$$i_1 = i_2 + i_3$$

$$\frac{5 - V_1}{2} = \frac{V_1}{8} + \frac{V_1 - (-3)}{4}$$

$$\frac{5}{2} - \frac{3}{4} = V_1 \left( \frac{1}{2} + \frac{1}{8} + \frac{1}{4} \right)$$

$$\frac{7}{4} = V_1 \left( \frac{7}{8} \right)$$

$$\boxed{V_1 = 2V}$$

$$i_1 = \frac{5 - V_1}{2} = \frac{5 - 2}{2} = 1.5A$$

$$i_2 = \frac{V_1}{8} = \frac{2}{8} = 0.25A$$

$$i_3 = \frac{V_1 + 3}{4} = \frac{5}{4} = 1.25A$$

To verify KCL:


$$i_1 = i_2 + i_3$$

$$1.5 = 0.25 + 1.25$$

Hence proved: Also, the currents are identical as we solve using KVL.


# Example 2:

Find the currents using node analysis.

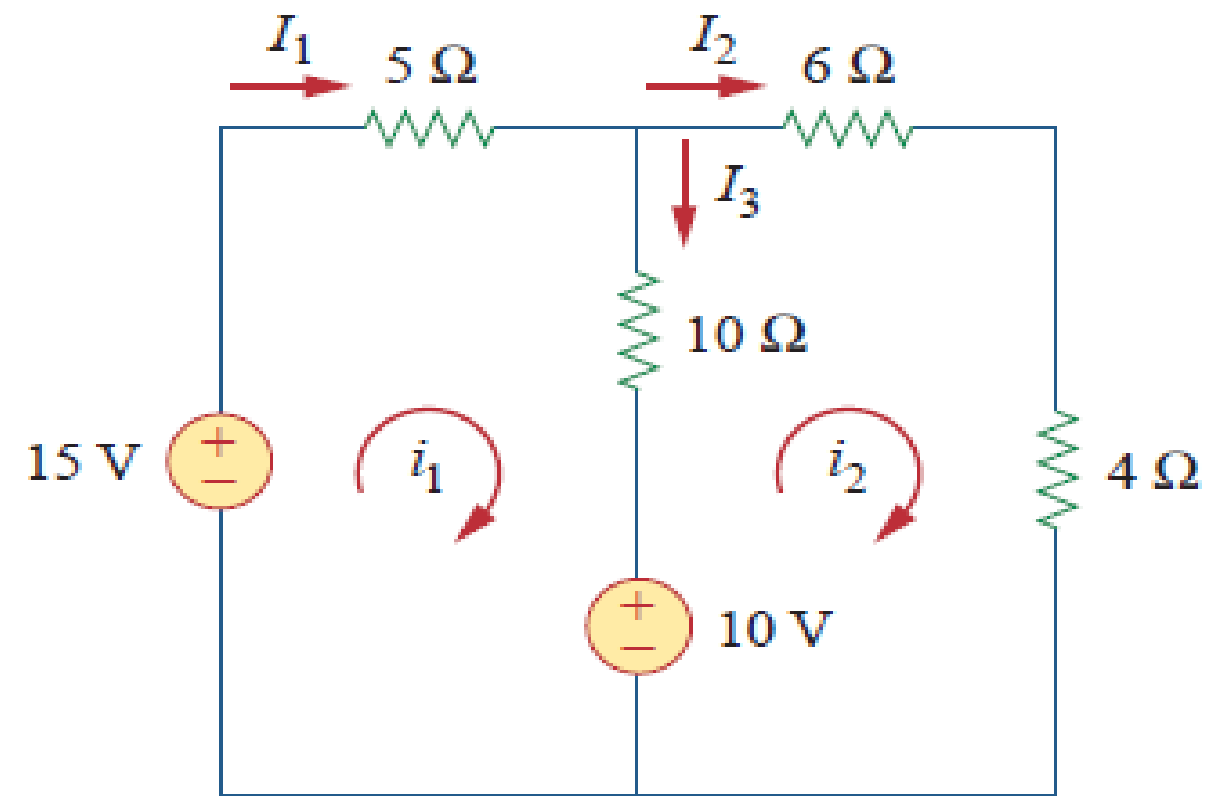

# Example 3:

Find the voltages using node analysis.

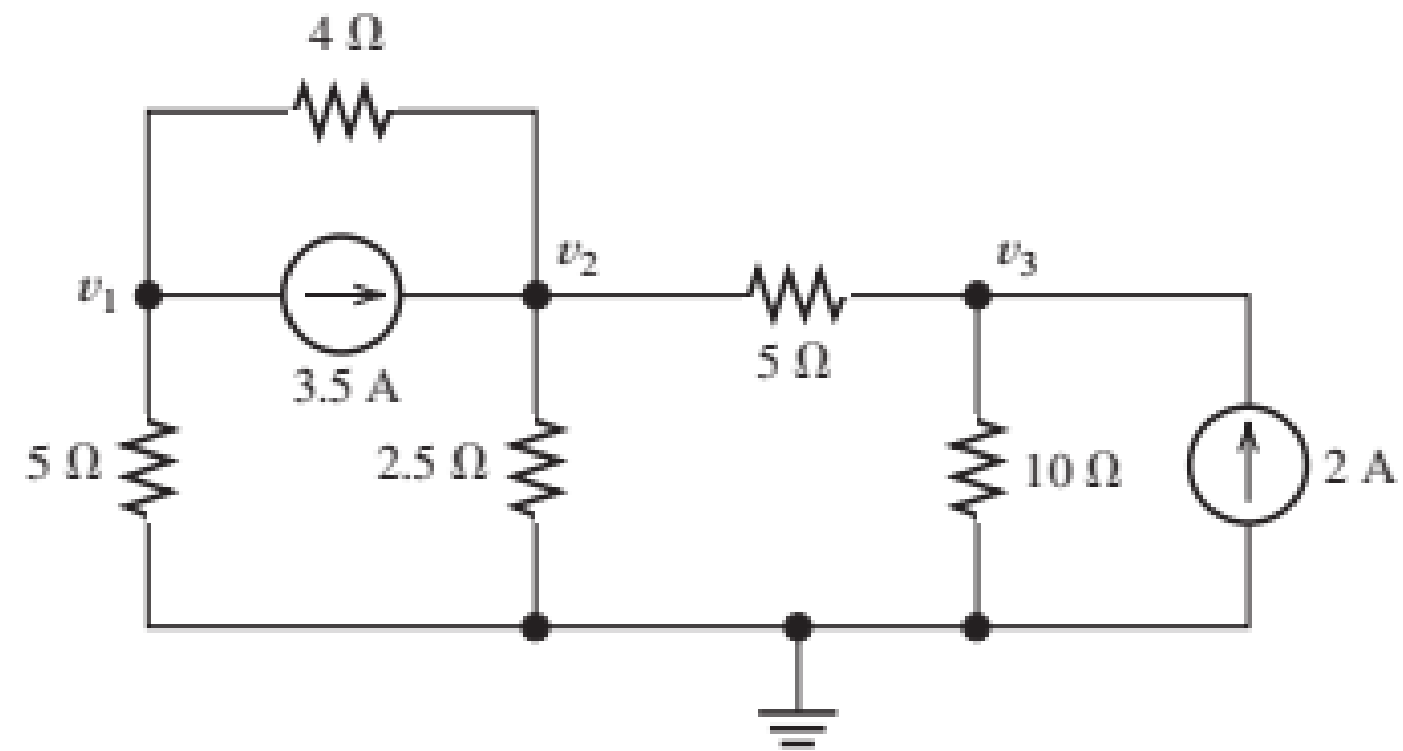

# Example 4:

Use node analysis to find  $i_x$ .

