

11/3/22

## Tutorials

1) A series RLC circuit with  $R = 100\Omega$ ;  $L = 2\text{mH}$ ; and  $C = 10\mu\text{F}$  is connected to an ac source of  $220\text{V}$ ,  $50\text{Hz}$ . Find the current in the circuit. Also find various components of power, power factor and the frequency at which reactances are equal.

Solution:

Given data:  $R = 100\Omega$ ;  $L = 2 \times 10^{-3}\text{H}$ ;  $C = 10 \times 10^{-6}\text{F}$ ;  $V = 220\text{V}$ ;  $f = 50\text{Hz}$ .

Formulae:

$$I = \frac{V}{Z} \quad ; \quad Z = R + j(X_L - X_C) \quad ; \quad X_L = 2\pi fL \quad ; \quad X_C = \frac{1}{2\pi fC} \quad ; \quad |Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi_Z = \tan^{-1} \left[ \frac{X_L - X_C}{R} \right]$$

$$P = VI \cos \phi \text{ W} \quad ; \quad \text{Power factor} = \cos \phi$$

$$Q = VI \sin \phi \text{ VAR}$$

$$S = VI \text{ VA}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 2 \times 10^{-3} = 0.628 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 10 \times 10^{-6}} = 318.30 \Omega$$

$$Z = R + j(X_L - X_C) = 100 + j(0.628 - 318.30) \Omega = 100 - j317.67 \Omega$$

$$|Z| = \sqrt{100^2 + 317.67^2} = 333.2 \Omega$$

$$\phi = \tan^{-1}\left(\frac{-317.67}{100}\right) = -72.54^\circ$$

$$I = \frac{V}{Z} = \frac{220 \angle 0}{333.2 \angle -72.54^\circ} = \frac{220}{333.2} \angle 0 - (-72.54^\circ) = 0.66 \angle 72.54^\circ \text{ A}$$

$$\text{Real power } P = VI \cos \phi = 220 \times 0.66 \cos(72.54) = 43.56 \text{ W}$$

$$\text{Reactive Power } Q = VI \sin \phi = 220 \times 0.66 \sin(-72.54) = -138.52 \text{ VAR}$$

$$\text{Apparent Power } S = VI = 220 \times 0.66 = 145.2 \text{ VA}$$

$$\text{Power factor} = \cos(-72.54) = 0.3 [\text{leading}]$$

To find the frequency at which reactances are equal:

$$\underline{f @ X_L = X_C}$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{(2\pi)^2 LC}$$

$$f = \frac{1}{2\pi \sqrt{LC}}$$

$$= \frac{1}{2\pi \sqrt{2 \times 10^{-3} \times 10 \times 10^{-6}}}$$

$$f = 1125.40 \text{ Hz}$$

$$R = 20\Omega \quad L = 10\text{mH} \quad C = 1000\mu\text{F} \quad V = 220\text{V}, \quad f = 50\text{Hz}.$$

$$X_L = 2\pi fL = 3.141\Omega$$

$$X_C = \frac{1}{2\pi fC} = 3.183$$

$$Z = R + j(X_L - X_C) = 20 - j0.042$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2} = 20\Omega$$

$$\phi = -0.120$$

$$I = \frac{V}{Z} = \frac{220}{20 \angle -0.120} = 11 \angle 0.120$$

$$P = VI \cos \phi = 2417.58 \text{ W}$$

$$Q = VI \sin \phi = -5.082 \text{ VAR}$$

$$S = VI = 2420 \text{ VA}$$

$$\cos \phi = 0.99 \text{ leading}$$

$$f_r = 1/(2\pi\sqrt{LC}) = 5 \text{ Hz}.$$

Find the circuit parameters of a series three element circuit excited from an ac source of 115V, 60Hz. The circuit consumes 1000W at 0.77 lagging power factor, and resonates at 550 Hz.

Solution:

To find: R, L, C

Data given:  $V = 115V$  ;  $f = 60Hz$  ;  $P = 1000W$   $\cos\phi = 0.77$  lag  $\rightarrow [X_L > X_C]$

$$Z = R + jX$$

$$P = VI \cos\phi \Rightarrow I = \frac{P}{V \cos\phi} ; P = I^2 R \Rightarrow R = \frac{P}{I^2}$$

$$|Z| = \frac{|V|}{|I|}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$I = 11.3A$$

$$R = 7.84$$



