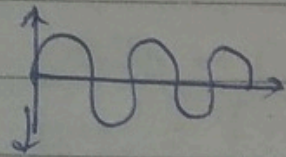


## Three phase circuits

\* ~~1~~  $1\phi$  generator — by electromagnetic induction

— by faraday's law :  $\Delta \phi_B$  induces  $\mathcal{E}$



\* frequency :  $f = \frac{NP}{120^\circ}$


$N$  = speed,  $P$  = No. of poles

generator : coil — rotated : magnetics — fixed



Alternator : coil — fixed : magnets — rotated

\* clockwise — leading  $30^\circ$

anticlockwise — lagging

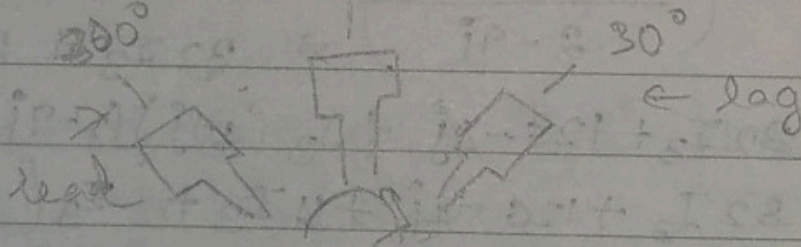


3 $\phi$  a

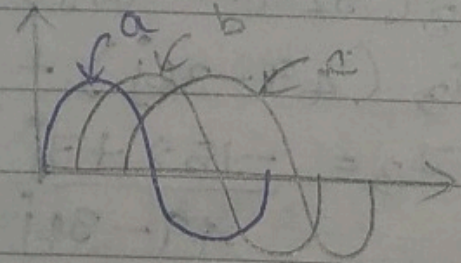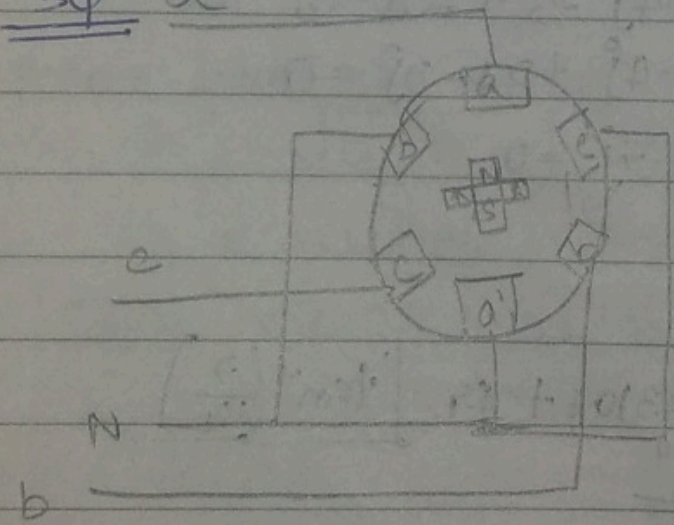




## Star connection

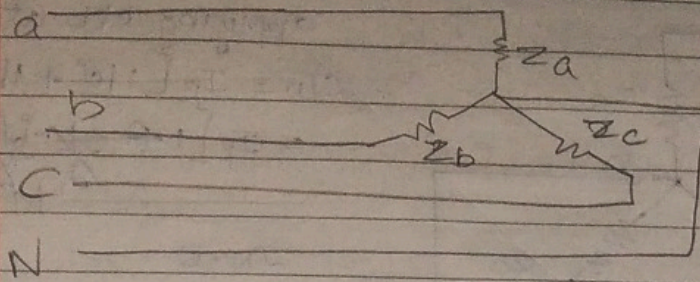

## Star connection

## Delta connection

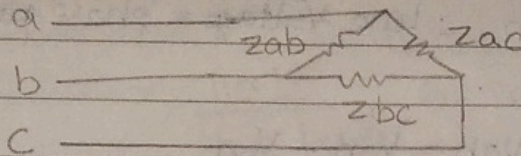

## \* Phase voltage

$V_p$  - voltage b/w  
a & N

## \* Line voltage

- voltage b/w  
a-b / b-c / c-a

\* Phase sequence in clockwise  $\Rightarrow$  abc  
'+' sequence

a reaches 1st  
b reaches 2nd  
c reaches 3rd

\* Phase sequence in anticlockwise  $\Rightarrow$  acb  
'-' sequence.

For abc sequence,  
 $V_{an} = V_p \angle 0^\circ$   
 $V_{bn} = V_p \angle -120^\circ$   
 $V_{cn} = V_p \angle -240^\circ$

## Problem (1)

$$V_{an} = 200 \angle \cos(\omega t + 10^\circ)$$

find  $V_{bn}$  &  $V_{cn}$  for abc sequence,

solution:-

$$V_{an} = 200 \angle 10^\circ ; V_{bn} = 200 \angle -110^\circ ; V_{cn} = 200 \angle -230^\circ$$

\* Current flowing through the line  $= I_a = I_b = I_c = I_L$   
 $\Rightarrow$  line current

$$I_{ab} = I_{bc} = I_{ca} = I_{\text{phase}} \Rightarrow \text{Phase current}$$

\* balanced circuit  $\Rightarrow Z_{ab} = Z_{bc} = Z_{ac} = Z_p$

$$Z_D = 3 \times Z_Y \Rightarrow$$

$\nearrow$  impedance of delta connection  
 $\nwarrow$  impedance in star connection.




Three pin plug

⊙ large radius, ↑ A - ↓ Resistance, all  $\Sigma$  goes into the earth due in case of short circuit

○ ○

In star connection (balanced circuit)

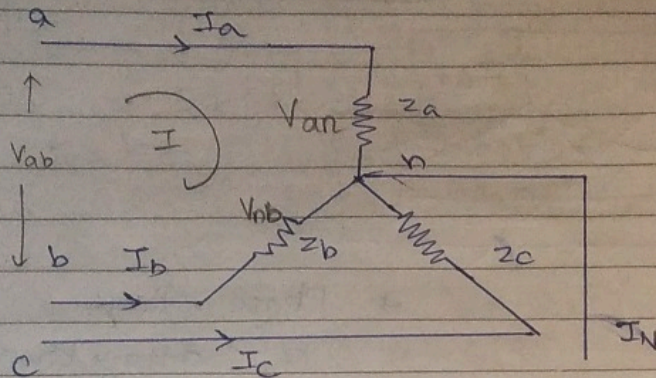

applying KCL at node 1

$$I_n = I_p [1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle -240^\circ]$$

$$= I_p \left[ 1 + \frac{-1 - j\sqrt{3}}{2} - \frac{0.5 + j\sqrt{3}}{2} \right]$$

$$I_n = 0$$

$I_L = I_{ph}$  : Line <sup>current</sup> Voltage = phase ~~current~~ Current

Applying KVL at loop 1.

$$V_{ab} = V_{an} + V_{nb} \Rightarrow V_{ab} = V_{an} - V_{bn}$$

$$V_{ab} = V_p [1 \angle 0^\circ - 1 \angle -120^\circ] = V_p (1.5 + j0.866)$$

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{ab} = \sqrt{3} V_p \angle 0^\circ \angle 30^\circ$$

$$[\because V_{an} = V_p \angle 0^\circ]$$

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ \Rightarrow V_L = \sqrt{3} V_{ph} \angle 30^\circ$$

$$I_L = I_{ph}$$


$$\star \quad I_{an} + I_{bn} + I_{cn} = I_n = 0$$

$$V_{an} + V_{bn} + V_{cn} = 0 \quad \leftarrow \text{since } \phi \text{ same impedance.}$$

$$\star \quad I_{\text{phase}} = \frac{V_{\text{phase}}}{Z_{\text{phase}}}$$

$$I_L \neq \frac{V_L}{Z_{\text{phase}}}$$

Problem 1

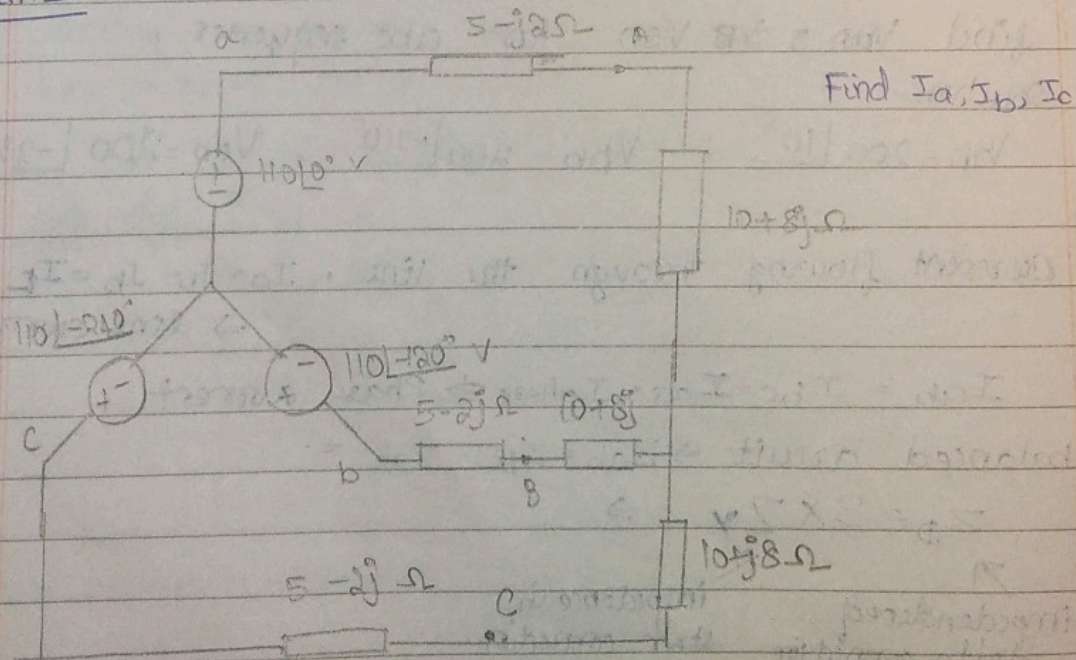



Given:-

$$Z_Y = Z_a = (10 + j8) \Omega, \quad Z_L = 5 - j2 \Omega$$

$$V_{an} = 110 \angle 0^\circ, \quad V_{bn} = 110 \angle -120^\circ$$

$$V_{cn} = 110 \angle 40^\circ$$

} abc sequence

To find:-  $I_a = ?$  ;  $I_b = ?$  ;  $I_c = ?$

Solution:-

$$I_a = I_{ab} = \frac{110 \angle 0^\circ}{5 - j2 + 10 + j8} = \frac{110 \angle 0^\circ}{15 + 6j}$$


Polar form of  $15 + 6j = \sqrt{6^2 + 15^2} \angle \tan^{-1} \frac{6}{15}$   
 $= 16.15 \angle 21.8^\circ$

$$I_a = \frac{110 \angle 0^\circ}{16.15 \angle 21.8^\circ} \Rightarrow I_a = 6.81 \angle -21.8^\circ$$

$$I_b = 6.81 \angle -141.8^\circ$$

$$I_c = 6.81 \angle -261.8^\circ$$

H.W

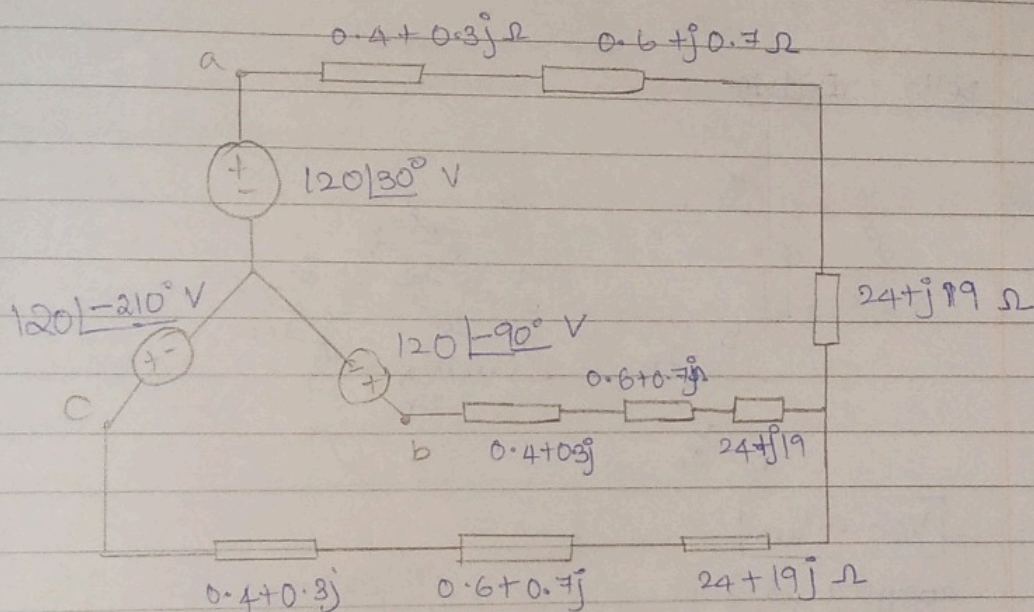

To find: line voltages:  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ac} = ?$   
 $I_a$ ,  $I_b$ ,  $I_c$

Solution:-

$$I_a = I_{ab} = \frac{120 \angle 30^\circ}{0.4 + j0.3 + 0.6 + j0.7 + 24 + j19}$$

$$= \frac{120 \angle 30^\circ}{25 + j20} = \frac{120 \angle 30^\circ}{32.015 \angle 38.66^\circ}$$

$$I_a = 3.748 \angle -8.66^\circ$$

$$I_b = 3.748 \angle -128.66^\circ ; \quad I_c = 3.748 \angle -248.66^\circ$$



$$V_L = \sqrt{3} V_{ph} \angle 30^\circ$$

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ \Rightarrow V_{ab} = \sqrt{3} \times 120 \angle 30^\circ \times \angle 30^\circ$$


$$V_{ab} = 207.85 \angle 60^\circ \text{ V}$$

$$V_{bc} = \sqrt{3} V_{bn} \angle 30^\circ \Rightarrow V_{bc} = \sqrt{3} \times 120 \angle -120^\circ \times \angle 30^\circ$$

$$V_{bc} = 207.85 \angle -90^\circ \text{ V}$$


$$V_{ca} = \sqrt{3} V_{cn} \angle 30^\circ \Rightarrow V_{ca} = \sqrt{3} \times 120 \angle -240^\circ \times \angle 30^\circ$$
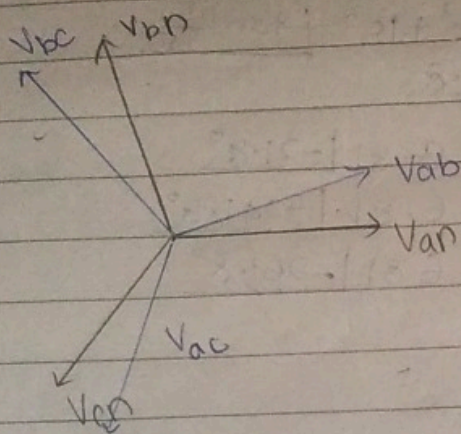
$$V_{ca} = 207.85 \angle -180^\circ \text{ V}$$



Phasor diagram.

Delta connection

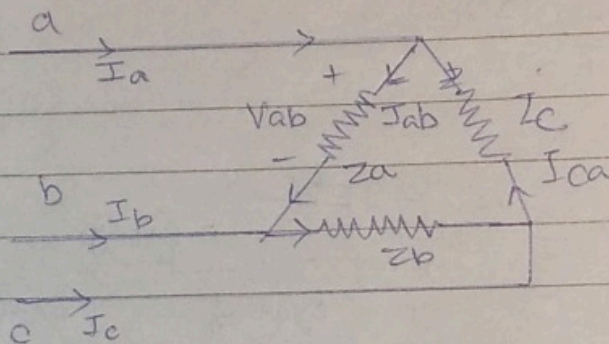

$$V_{ab} = V_{an}$$

applying kcl

$$I_a + I_{ca} = I_{ab} \Rightarrow I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ac} - I_{bc}$$

assumption:

$$I_{ab} = I_p \angle 0^\circ$$

$$I_{bc} = I_p \angle -120^\circ$$

$$I_{ca} = I_p \angle -240^\circ$$


$$I_a = I_p \angle 0^\circ - I_p \angle -240^\circ$$

$$I_a = I_p \sqrt{3} \angle -30^\circ$$

$$I_a =$$



Problem:

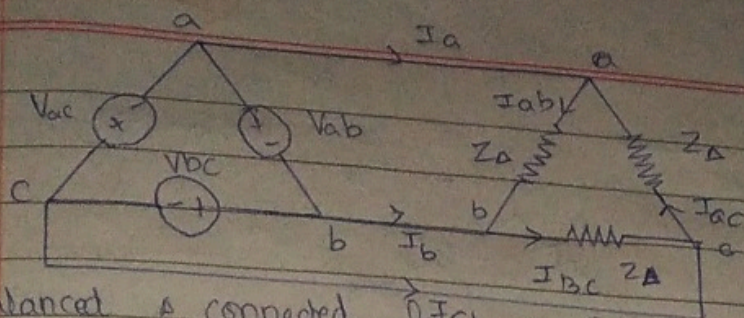

A balanced  $\Delta$  connected load having an impedance  $20 - j15 \Omega$  is connected to a  $\Delta$  connected positive sequence generator having  $V_{ab} = 330 \angle 0^\circ$  V. Calculate the phase currents of the load & the line currents.

Solution: - Given -

$$Z_p = 20 - j15 \Omega \quad V_{ab} = 330 \angle 0^\circ ; V_{bc} = 330 \angle -120^\circ ; V_{ca} = 330 \angle -240^\circ$$

To find:

$$I_{ab} = ? ; I_{bc} = ? ; I_{ca} = ?$$

$$I_a = ? ; I_b = ? ; I_c = ?$$

Solution:-

$$I_{ab} = \frac{V_{ab}}{Z_p} = \frac{330 \angle 0^\circ}{20 - j15}$$

$$\text{polar form of } 20 - j15 = 25 \angle -36.8^\circ$$

$$I_{ab} = 13.2 \angle 36.8^\circ$$

$$I_a = \sqrt{3} I_{ph} \angle -30^\circ \Rightarrow I_a = 22.86 \angle -3.2^\circ$$


$$I_{bc} = 13.2 \angle -83.2^\circ$$

$$I_b = 22.86 \angle -113.2^\circ$$

$$I_{ca} = 13.2 \angle -203.2^\circ$$

$$I_c = 22.86 \angle -233.2^\circ$$


How  
Problem 2

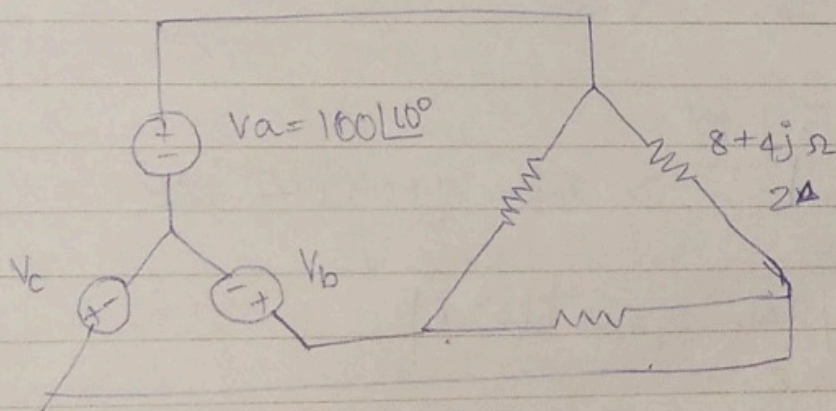

A balanced abc-sequence  $\Delta$  connected source with  $V_{an} = 100 \angle 10^\circ$  V is connected to a  $\Delta$  connected load  $8 + j4 \Omega$  per phase. Calculate phase & line currents.



Solution:-

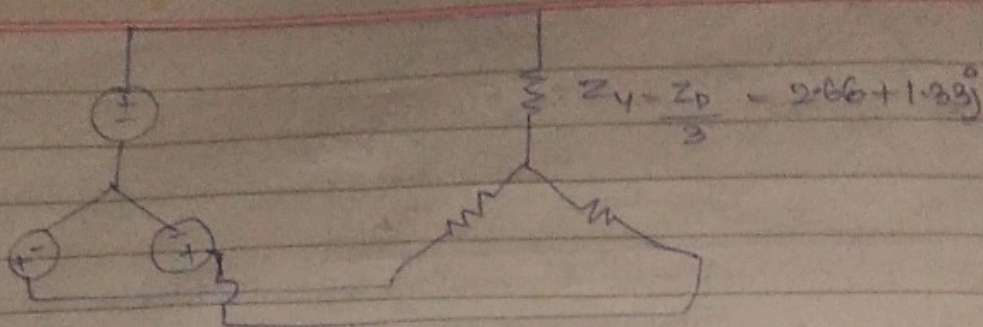

$$I_{ab} = \frac{V_{ab}}{Z_y} = \frac{100 \angle 10^\circ}{2.66 + j1.93} = \frac{100 \angle 10^\circ}{2.981 \angle 26.57^\circ}$$

$$I_{ab} = 33.5 \angle -16.57^\circ = I_a$$


$$I_{bc} = 33.5 \angle -136.57^\circ = I_{bc}$$

$$I_{ca} = 33.5 \angle -256.57^\circ = I_{ca}$$

H.W

A positive sequenced balanced  $\Delta$  connected source supplies a balanced  $\Delta$  connected load. If the impedance per phase of the load is  $18 + j12 \Omega$  and  $I_a = 9.609 \angle 35^\circ$ . Find  $I_{AB}$  &  $V_{AB}$

Solution:-

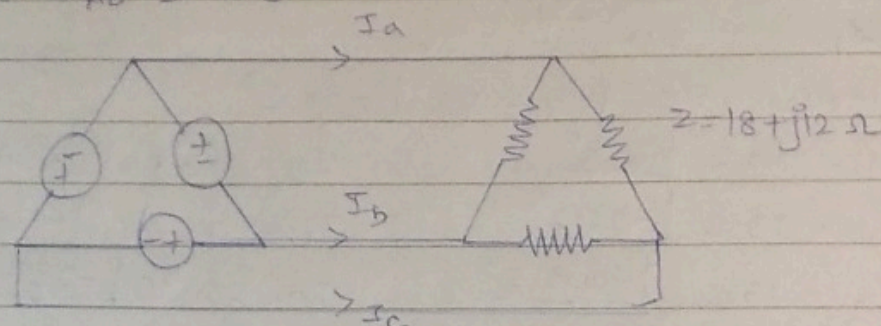

Given:-

$$I_a = 9.609 \angle 35^\circ \therefore Z = 18 + j12 \Omega$$

To find:  $I_{ab} = ?$   $V_{ab} = ?$

Solution:-

$$I_a = I_{ab} \sqrt{3} \angle -30^\circ$$

$$I_{ab} = \frac{I_a \angle 30^\circ}{\sqrt{3}} \Rightarrow I_{ab} = \frac{9.609 \angle 35^\circ \angle 30^\circ}{\sqrt{3}}$$

$$I_{ab} = 5.548 \angle 65^\circ \text{ A}$$

$$V_{ab} = I_{ab} \times Z_y$$

$$\text{Polar form of } 18 + j12 \Omega = 21.63 \angle 33.69^\circ$$

$$V_{ab} = 5.548 \angle 65^\circ \times 21.63 \angle 33.69^\circ$$

$$V_{ab} = 120 \angle 98.69^\circ \text{ V}$$



## 3 Phase power

Power in single phase:-

Real power:  $\bar{P} = V_{ph} I_{ph} \cos \phi$

Complex power:  $Q = V_{ph} I_{ph} \sin \phi$

apparent power =  $|S| = \sqrt{P^2 + Q^2} = V_{ph} I_{ph}$

$$S = P + jQ$$

Power in 3 phases:-

real power =  $3 V_{ph} I_{ph} \cos \phi = P$

complex power =  $3 V_{ph} I_{ph} \sin \phi = Q = \text{reactive power}$

apparent power =  $3 V_{ph} I_{ph}$

$S = 3P + j3Q$  ← complex power

In Y connection (In terms of  $V_L, I_L$ ) :-  $V_L = V_{ph} \sqrt{3}$

real power =  $P_{3\phi} = 3 \times \frac{V_L}{\sqrt{3}} \cdot I_L \cos \phi = \sqrt{3} V_L I_L \cos \phi$

$Q_{3\phi} = \sqrt{3} V_L I_L \sin \phi$

apparent power =  $\frac{V_L I_L}{3}$

In  $\Delta$  connection :-  $I_L = I_{ph} \sqrt{3}$

$P_{3\phi} = 3 \times V_L \times \frac{I_L}{\sqrt{3}} \cos \phi = \sqrt{3} \times V_L \times I_L \cos \phi$


$Q_{3\phi} = \sqrt{3} V_L I_L \sin \phi$

apparent power =  $\frac{V_L I_L}{3}$

power factor =  $\cos \phi$



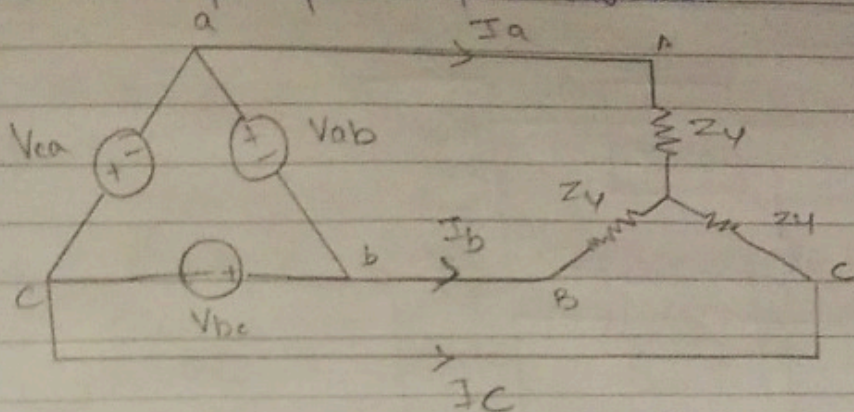Problem 1: A balanced Y-connected load with a phase impedance of  $40 + j25$  is supplied by a balanced, positive sequence  $\Delta$ -connected source with a line voltage of 210 V. Calculate real power, reactive power, complex power, phase currents.



Given:-  $V_{ab} = 210V$ ;  $Z_Y = 40 + j25$

To find:  $P = ?$ ;  $Q = ?$ ;  $S = ?$

Solution:-

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ \Rightarrow V_{an} = \frac{210}{\sqrt{3}} \angle 30^\circ$$

$$V_{ph} = \frac{210}{\sqrt{3}} \angle 30^\circ V \quad V_{ph} = 121.24 \angle -30^\circ$$

$$|V_{ph}| = 121.24 V \quad |V_{ph}| = 121.24$$

$$Z_Y = 40 + j25 = 47.17 \angle 32^\circ$$

Ref:  $I_{ab} = I_{an} = \frac{V_{an}}{Z_Y} = \frac{121.24 \angle -30^\circ}{47.17 \angle 32^\circ} = 2.57$

$$P = 3 I_{ab}^2 R = \sqrt{3} V_L I_L \cos \phi$$

$$P_{3\phi} = \sqrt{3} (210) (2.57) \cos 32^\circ = 792.74 W$$

$$Q_{3\phi} = \sqrt{3} (210) (2.57) \sin 32^\circ = 495.36$$

$$S = 792.74 + j495.36$$

Problem 2

A 3 phase motor can be regarded as a balanced Y-load. A three phase motor draws 5.6 kW when the line voltage is 220 V & the line current is 18.2 A. Determine power factor of the motor.

Solution:

Given: Power = 5600 W;  $V_L = 220V$ ;  $I_L = 18.2A$ ;

$\cos \phi = ?$




$$\text{Power} = \sqrt{3} V_L I_L \cos \phi \Rightarrow \cos \phi = \frac{5600}{\sqrt{3} \times 220 \times 18.2}$$

$$\boxed{\cos \phi = 0.807}$$



### 3 Phase measurement

\* wattmeter - to measure power.

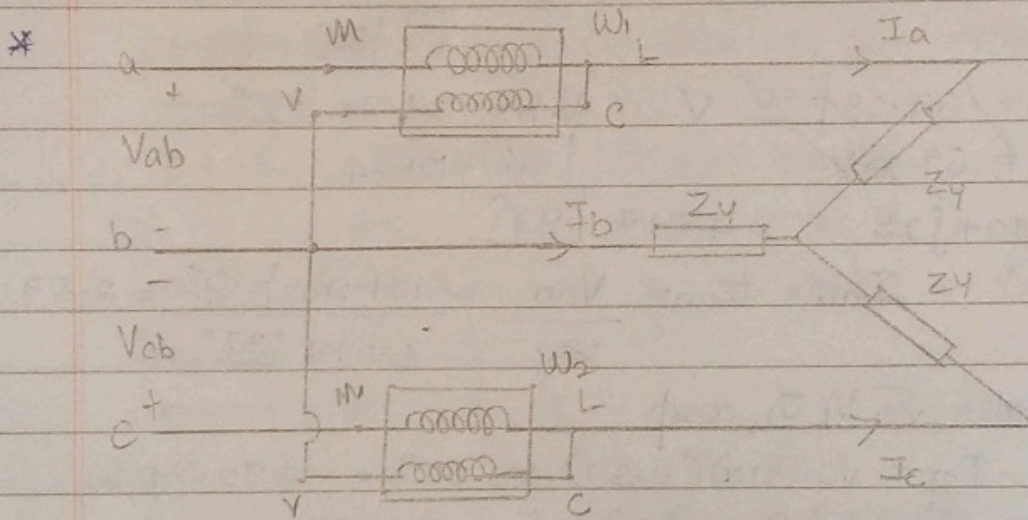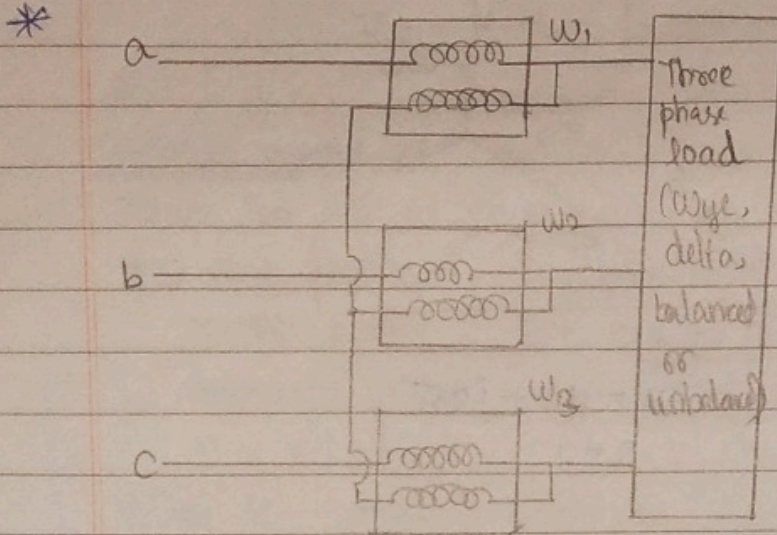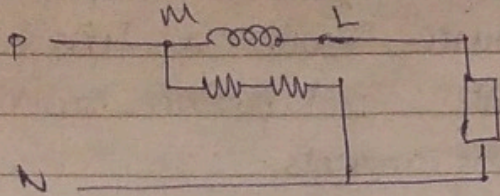

Wattmeter 1 : - Voltage measured =  $V_{ab}$

current measured =  $I_a$

angle between  $I_a$  &  $V_{ab} = 30^\circ + \phi$

$$P_1 = V_{ab} I_a \cos(30^\circ + \phi)$$


wattmeter 2 :

Voltage measure =  $V_{cb}$

current measured =  $I_c$

angle between  $I_c$  &  $V_{cb} = 30^\circ - \phi$
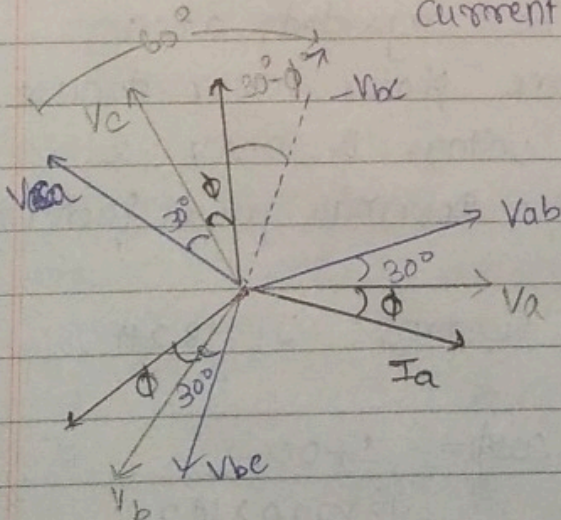
$$P_2 = V_{cb} \times I_c \times \cos(30^\circ - \phi)$$





$$P_T = P_1 + P_2 = V_L I_L [\cos(30+\phi) + \cos(30-\phi)]$$

$$= 2 \cos 30^\circ V_L I_L \cos \phi$$

$$P_T = \sqrt{3} V_L I_L \cos \phi = P_{3\phi} \leftarrow \text{3 phase real power}$$

$$\text{reactive power} \rightarrow Q_{3\phi} = \sqrt{3} V_L I_L \sin \phi$$

$$P_2 - P_1 = V_L I_L [\cos(30-\phi) - \cos(30+\phi)]$$

$$= 2 V_L I_L \sin 30^\circ \sin \phi \Rightarrow V_L I_L \sin \phi$$

$$Q_{3\phi} = \sqrt{3} (P_2 - P_1)$$

$$\phi = \tan^{-1} \left( \frac{\sqrt{3} (P_2 - P_1)}{P_1 + P_2} \right)$$

(i) if  $\phi = 0 \Rightarrow P_1 = P_2 \leftarrow \text{resistive load}$

(ii) Power factor  $\phi > 0 : P_2 > P_1 \leftarrow \text{Inductive load, } I \text{ lagging } V$

(iii) Power factor  $\phi < 0 : P_2 < P_1 \leftarrow \text{capacitive load, } I \text{ leading } V$

### Problem 1

Two wattmeter method produces wattmeter readings  $P_1 = 1560 \text{ W}$  and  $P_2 = 2100 \text{ W}$  when connected to a delta connected load, if the line voltage is  $220 \text{ V}$ . Calculate power per phase - ...?

Given:  $P_1 = 1560 \text{ W}$

$P_2 = 2100 \text{ W}$

$V_L = 220 \text{ V}$

To find: a) Per phase average power

b) per phase reactive power

c) power factor: d) phase impedance.

Solution:-

a)  $P_{3\phi} = P_1 + P_2 = 1560 + 2100 \Rightarrow P_{3\phi} = 3660 \text{ W}$

$P_{1\phi} = \frac{P_{3\phi}}{3} = \frac{3660 \text{ W}}{3} \Rightarrow P_{1\phi} = 1220 \text{ W} \leftarrow \text{real power/phase}$

b)  $Q_{3\phi} = \sqrt{3} (P_2 - P_1)$

$= \sqrt{3} (2100 - 1560) = 935.30 \text{ VAR}$

$\frac{Q_{3\phi}}{3} = Q_{1\phi} = \frac{935.30}{3} = 311.7 \text{ VAR} \leftarrow \text{reactive power/phase}$

c)  $\cos \phi = \phi = \tan^{-1} \left( \frac{Q}{P} \right) = 4.332^\circ$

$\cos \phi = 0.9688 \leftarrow \text{power factor}$



$$d) \vec{Z} = |Z| \angle \phi$$

$$|Z| = \frac{V_{ph}}{I_{ph}} = \frac{220}{I_L}$$

$$I_L = \frac{P_{3\phi}}{\sqrt{3} V_L \cos \phi} = 9.91 \text{ A}$$

$$|Z| = 220 \quad I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{9.91}{\sqrt{3}} = 5.723 \text{ A}$$

$$|Z| = \frac{220}{5.723} = 38.44$$

$$Z = 38.44 \angle 14.332^\circ \Omega$$

Problem 2 If the load ~~is~~ is delta connected with impedance per phase of  $Z_{ph} = 30 - 40j \Omega$  &  $V_L = 440 \text{ V}$ . Predict the readings of the wattmeters  $W_1$  &  $W_2$ . Calculate  $P_T$  &  $Q_T$ .

Given:-  $Z_{\Delta} = 30 - 40j$

$$V_L = 440 \text{ V}$$

To find:  $P_1 = ?$ ,  $P_2 = ?$ ,  $P_T = ?$ ;  $Q_T = ?$

Solution:-

$$\phi \quad Z = 50 \angle -53.13^\circ \Rightarrow \phi = -53.13^\circ$$

$$I_{ph} = \frac{V_{ph}}{|Z|} = \frac{440}{50} = 8.8 \text{ A}$$

$$I_L = \sqrt{3} \times 8.8$$

$$I_L = 15.24 \text{ A}$$

$$P_1 = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 15.24 \times 440 \times \cos(+53.13^\circ) = 6166.57$$

$$P_2 = \sqrt{3} V_L I_L \cos \phi (30^\circ + \phi) = \sqrt{3} \times 15.24 \times 440 \times \cos(30 - 53.13^\circ)$$

$$P_2 = 8021 \text{ W}$$

$$P_T = P_1 + P_2 = 6168.67 \text{ W}$$

$$Q_T = \sqrt{3} (P_2 - P_1) = \sqrt{3} (8021 - 6166.5)$$

$$Q_T = -9291.41 \text{ VAR}$$