

## Module I: DC Circuits

6 Hrs

Basic circuit elements and sources; Ohms law, Kirchhoff's laws; Series and parallel connection of circuit elements; Source transformation; **Node voltage analysis**; Mesh current analysis; Maximum power transfer theorem

### CO1:

Evaluate DC and AC circuit parameters using various laws and theorems

### Module 1

Evaluate DC circuit parameters using various laws and theorems


# Nodal analysis


- Node voltages as the circuit variables
- Kirchhoff's current law
- Node is a point of connection between two or more branches
- Branch represents any two terminal element

# Steps

- Select a node as the reference node
- Assign voltages  $V_1, V_2, \dots, V_n$  to the remaining  $N-1$  nodes
- Apply Kirchhoff's current law to each of the  $n-1$  non-reference nodes
- Use Ohm's law to express the branch currents in terms of node voltages
- Solve the resulting simultaneous equations


# Example 1

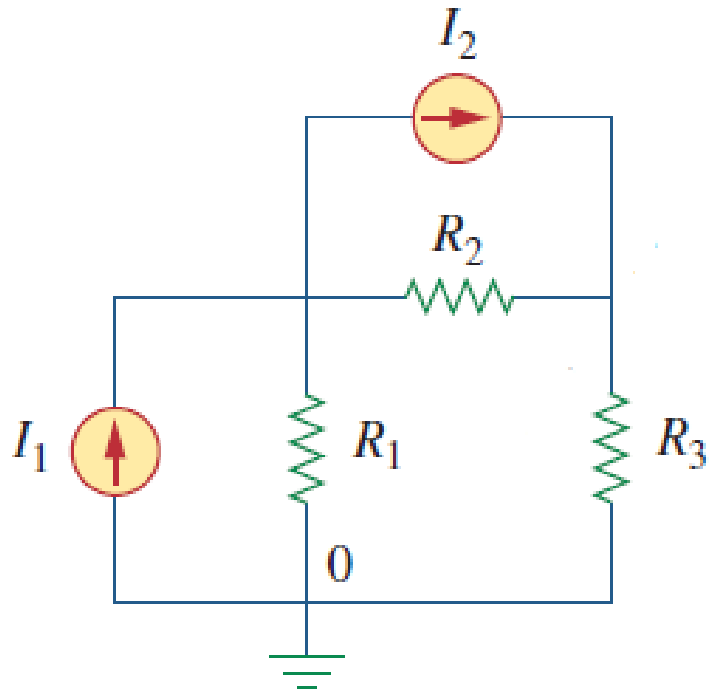


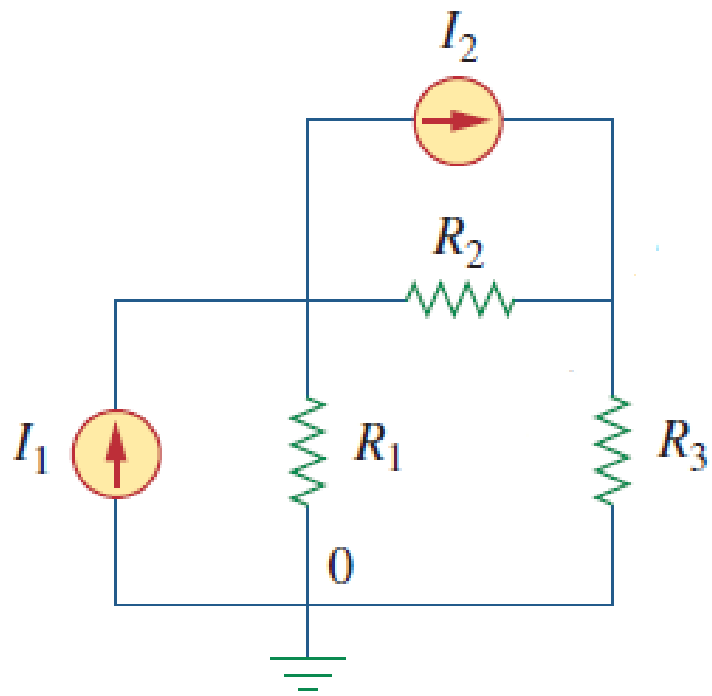

## Example 2


Obtain the nodal voltages

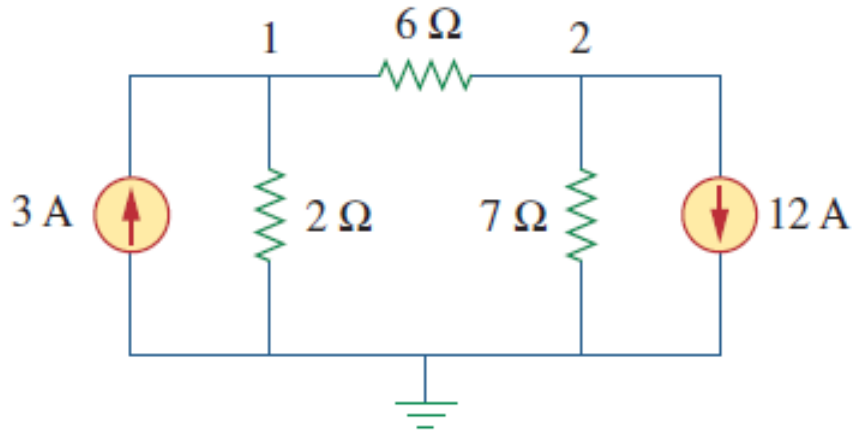

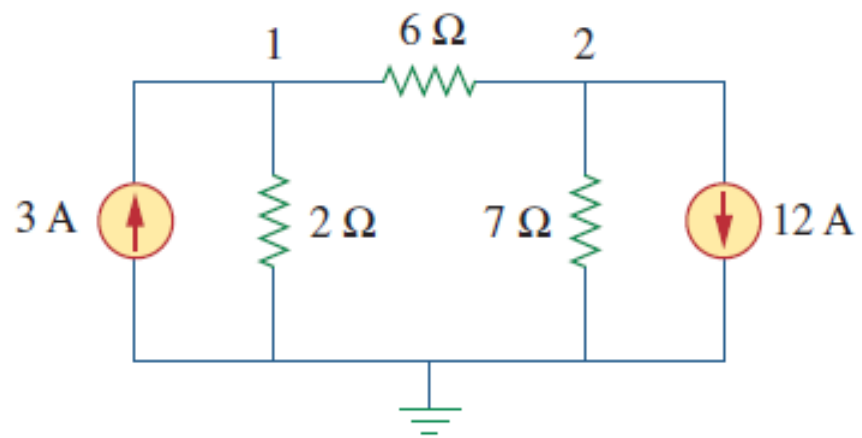

## Example 3


Determine the nodal voltages

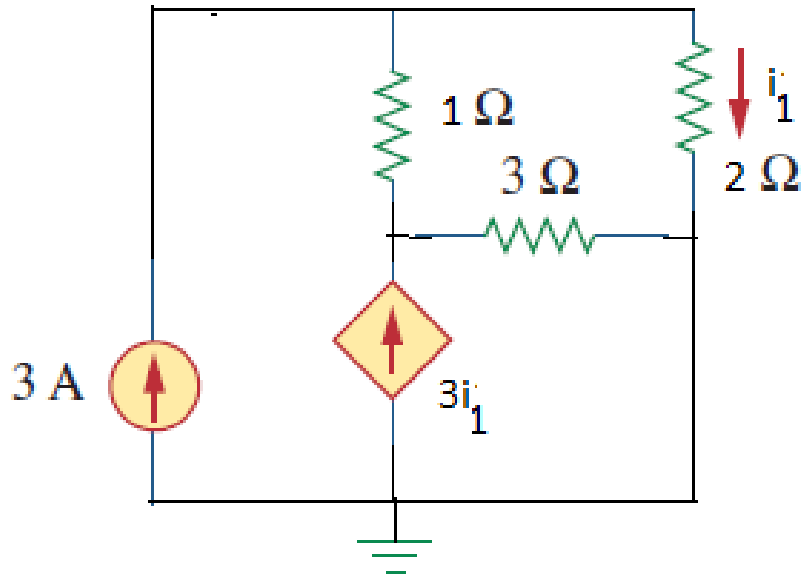



# Exercise 1

## Find the nodal voltages

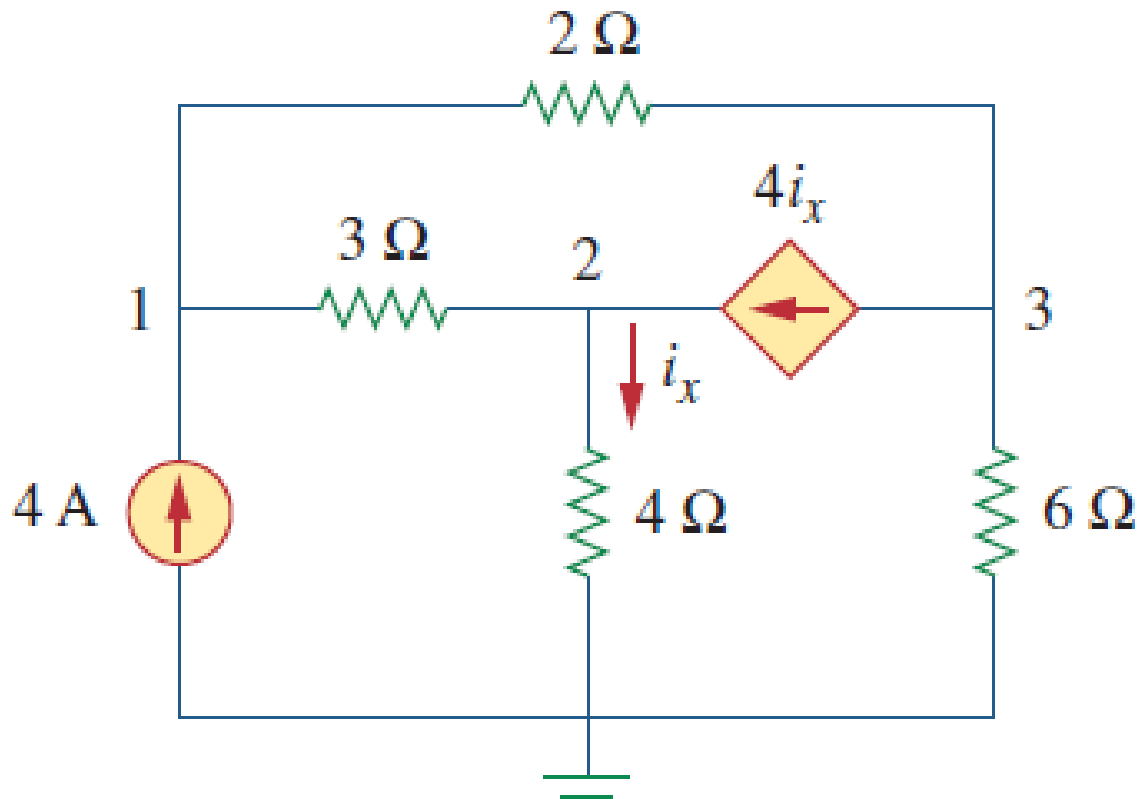

Ans:  $V_1 = 32 \text{ V}$ ;  $V_2 = -25.6 \text{ V}$ ;  $V_3 = 62.4 \text{ V}$