

## MODULE -1 : DC circuits

- \* Electrical circuits : Interconnection of electrical components
  - \* Active elements : Voltages from the sources changes/provides electric current. Battery
  - Passive elements: Values doesn't change irrespective of any voltage change. Resistors.
  - \* Analysing: Calculating I, V etc.,  
Reason for analysing: To know what's happening,  
power factors & problems in that circuit etc.  
using laws & theorems.
  - \* magnetically coupled circuits: electrical circuits not connected physically but magnetically. ej: Transformer
  - \* Maxwell eq:  $\oint \vec{H} \cdot d\vec{l} = I_{\text{elec}}$  charge-electrical property of the atomic particles of which materials consist, measured in coulombs
- DC circuits
- \* current doesn't change with time in DC
  - \* I flows from higher potential-free to lower  
→ find low resistance path

### Problem 4.

$$I = \begin{cases} 4A, & 0 < t < 1 \\ 4t^2, & 1 < t < 2 \end{cases} \quad \text{find } q \text{ from } t=0 \text{ to } t=2$$

Solution:-

$$\begin{aligned} q &= \int i dt \\ q &= \int_0^1 4 dt + \int_1^2 4t^2 dt = 4[t]_0^1 + \frac{4}{3}[t^3]_1^2 \\ &= 4(1) + \frac{4}{3}(8-1) = 4 + \frac{4}{3}(7) = 4\left(1+\frac{7}{3}\right) \end{aligned}$$

$$q = \frac{40}{3} C$$

\* Voltage - force that is required to move the charges

$$V = \frac{dw}{dq}$$


\* Power - work done per unit time

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V \cdot I$$

\* law of energy conservation: power lost = power gained


$$\sum P = 0 \quad \text{across any circuit}$$

\* +  $I$  in Passive sign convention

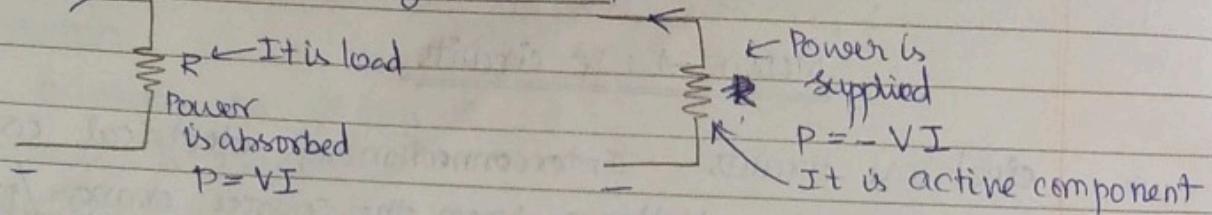

\* If power supplied is  $'+$ ve, then power is absorbed.  
If power supplied is  $'-$ ve, then power is supplied.

In active sign convention

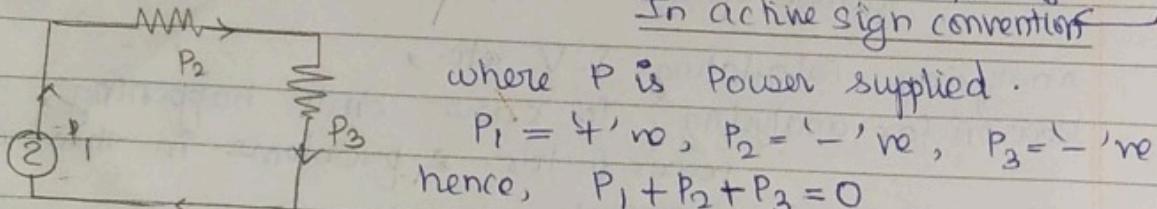

where  $P$  is Power supplied.

$$P_1 = '-' \text{ ve}, \quad P_2 = '+' \text{ ve}, \quad P_3 = '-' \text{ ve}$$

hence,  $P_1 + P_2 + P_3 = 0$

\* In Passive sign convention,  $P$  is Power absorbed,

$$P_1 = '-' \text{ ve}, \quad P_2 = '+' \text{ ve}, \quad P_3 = '+' \text{ ve}.$$

But however,  $\sum P_1 + P_2 + P_3 = 0$

↑ - dependent current source

\* Energy: Capacity to do work ( $J$ ) =


$$\text{Power} \times t = P \times t$$

$$\text{Unit} = 1 \text{ kWh} = 3600 \text{ J}$$

$$1 \text{ HP} = 746 \text{ W}$$

◇ + - dependent voltage source

Problem ②  $I = 5 \text{ A}$

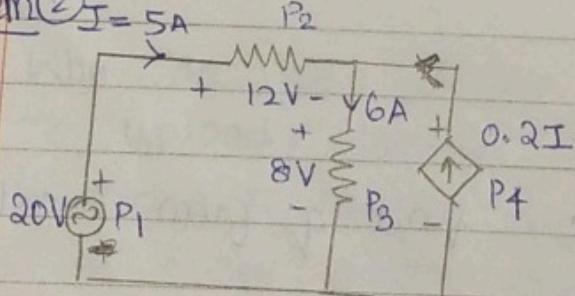

Find power absorbed in each elements.  
(Passive sign convention)

Solution:-


$$P_1 = 20(-5) = -100 \text{ W}$$

$$P_2 = 12(5) = 60 \text{ W}$$

$$P_3 = 8(6) = 48 \text{ W}$$

$$P_4 = 8(0.2)(20) = 8 \text{ W}$$

END POD

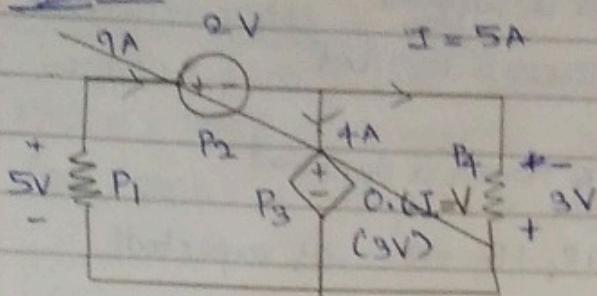

Calculate Power absorbed & power supplied by each element using both active sign convention & passive sign convention.

Solution :-

(i) using Passive sign convention :-


$$P_1 = 5(9) = +45W \quad \leftarrow \text{Power is absorbed}$$

$$P_2 = -2(9) = -18W \quad ? \quad \leftarrow \text{Power is supplied}$$

$$P_3 = -4(0.6)(5) = -12W \quad ?$$

$$P_4 = 3(5) = +15W \quad ? \quad \leftarrow \text{Power is absorbed.}$$

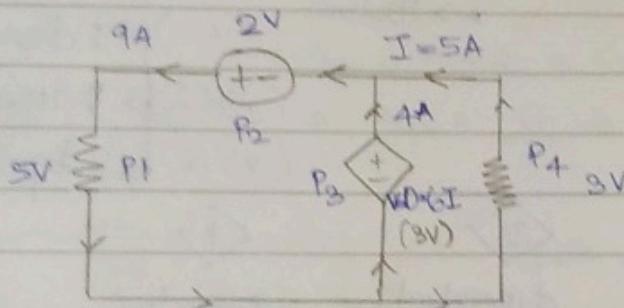[∴ we didn't get the summation of power in this circuit as zero. hence,  $P_4$  must be negative (i.e., element 4 must supply energy power)]




(ii) using Active sign convention :-

$$P_1 = -45W \quad \leftarrow \text{Power is absorbed}$$

$$P_2 = +18W \quad ? \quad \leftarrow \text{Power is supplied.}$$

$$P_3 = +12W \quad ?$$

$$P_4 = +15W \quad ?$$

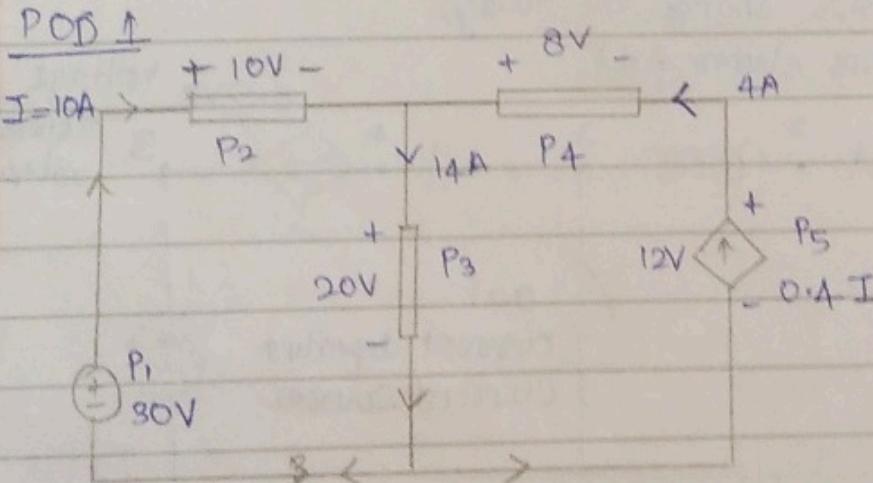

compute power supplied / absorbed by each component of the circuit

Using Passive sign convention:

$$P_1 = -30V \times 10A = -300W \leftarrow \text{Power is supplied}$$

$$P_2 = 10V \times 10A = 100W \quad ? \leftarrow \text{Power is absorbed}$$

$$P_3 = 20V \times 14A = 280W$$

$$P_4 = -8V \times 4A = -32W \quad ? \leftarrow \text{Power is supplied}$$

$$P_5 = -12V \times 4A = -48W$$

$$\text{total } P = P_1 + P_2 + P_3 + P_4 + P_5 = 0 \quad \text{as expected.}$$

Using active sign convention:



$$P_1 = 300W \leftarrow \text{Power is supplied}$$

$$P_2 = -100W \quad ? \leftarrow \text{Power is absorbed}$$

$$P_3 = -280W$$

$$P_4 = 32W \quad ? \leftarrow \text{Power is supplied}$$


$$P_5 = 48W$$

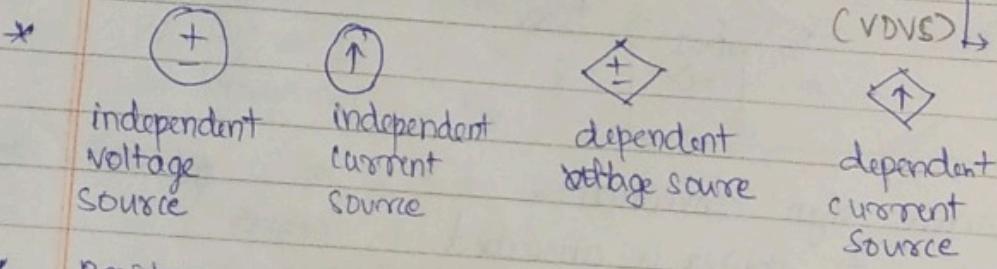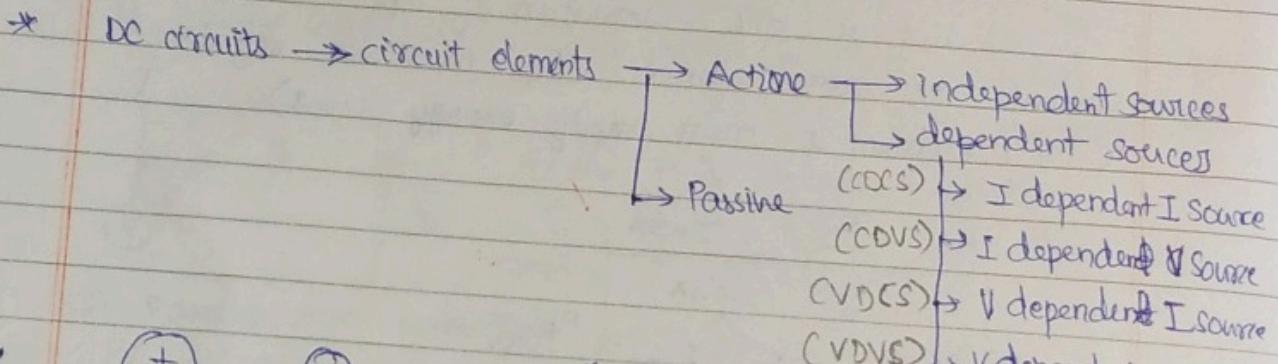

\* Resistance - Resists flow of I  
- dissipates power in the form of heat

\* Inductance - Stores magnetic field  
- resists change in I

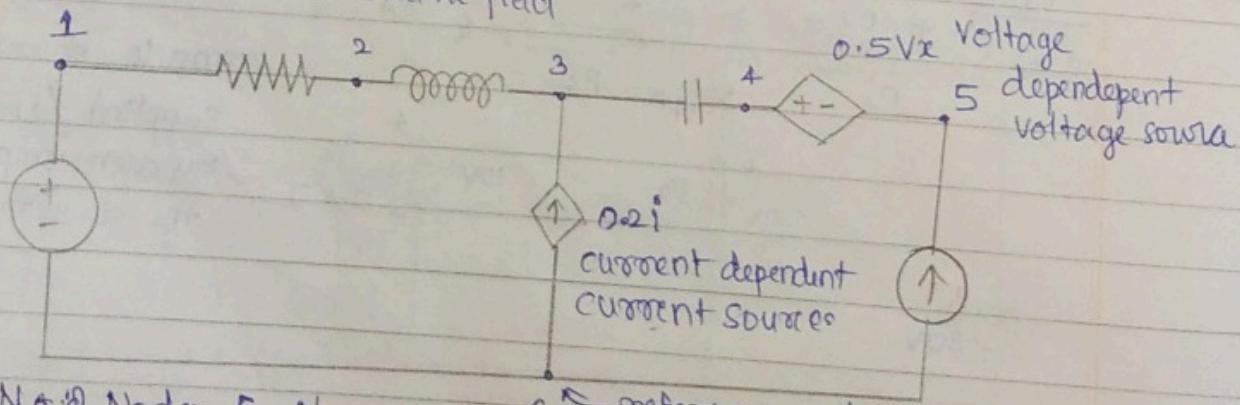\* Capacitance - resists change in voltage  
- stores electric field



No. of Nodes = G = 6

No. of branches = B = 7

## Nodes, branches & loops


- \* branch - each circuit elements represents branches (B)
  - \* Nodes : point of intersection of  $\geq 2$  branches (N)
  - \* loop/mesh : closed path in an circuit (L)
- $L = B - (N - 1)$

## Combination of resistance

Series :  $R_{eq} = R_1 + R_2 + R_3 \dots$

parallel :  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$

Problem 1:

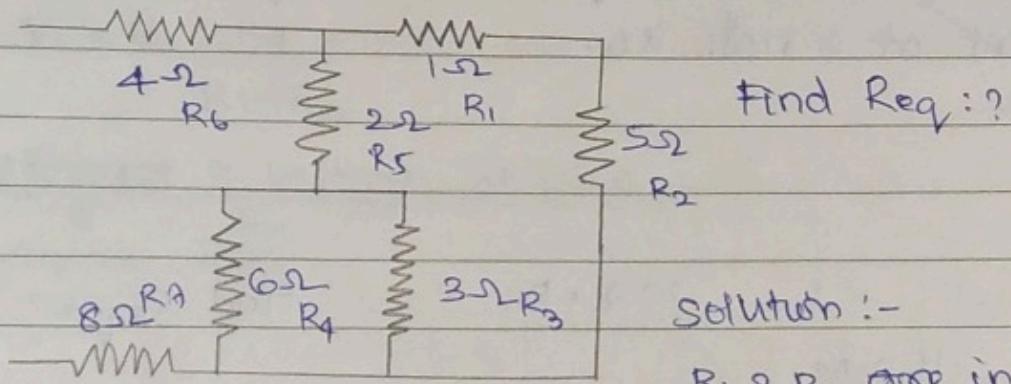


Solution :-

$R_1$  &  $R_2$  are in series

$$R_{S1} = R_1 + R_2 = 1\Omega + 5\Omega = 6\Omega$$
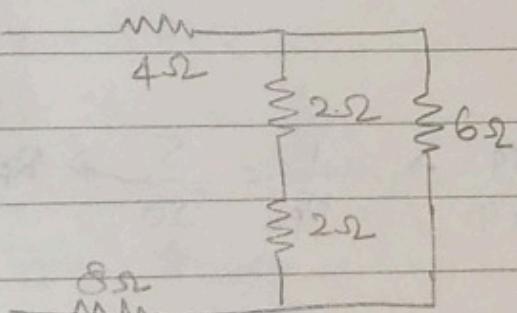
$$\frac{1}{R_{p1}} = \frac{1}{4\Omega} + \frac{1}{6\Omega} \Rightarrow R_{p1} = \frac{6}{3} \Rightarrow R_p = 2\Omega$$




$$R_{p2} = \frac{1}{R_p} = \frac{1}{6\Omega} + \frac{1}{4\Omega} = \frac{10}{24} = \frac{5}{12}\Omega$$

$$R_p = \frac{12}{5} \Rightarrow 2.4$$


$$R_{eq} = 4\Omega + 2.4\Omega + 8\Omega = 14.4\Omega$$

## Laws

\* Ohms Law :

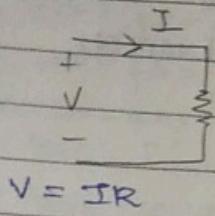

$$V = IR$$

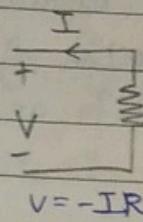


$$V = -IR$$

\* Kirchoff Voltage Law: algebraic sum of voltage drop across each element is 0.

Kirchoff Current Law: sum of current entering = sum of current leaving.  
current at a node is 0.

## H.W

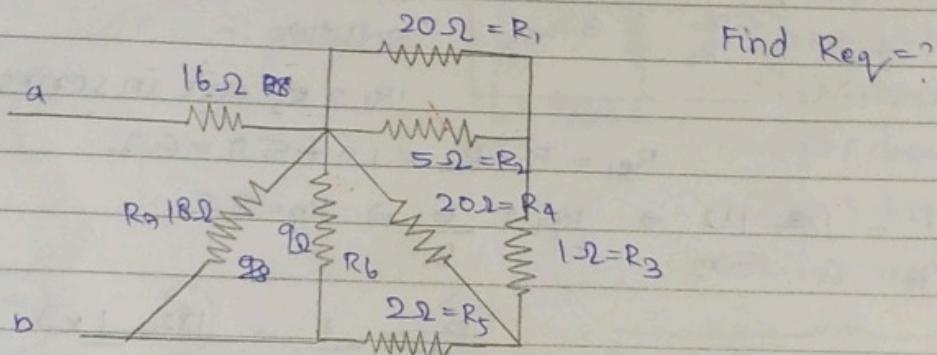


Find  $R_{eq} = ?$

Solution:

$$\frac{1}{R_{p1}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{R_{p1}} = \frac{1}{20} + \frac{1}{5 \times 4} \Rightarrow \frac{1}{R_{p1}} = \frac{5}{20} \Rightarrow R_{p1} = 4 \Omega$$

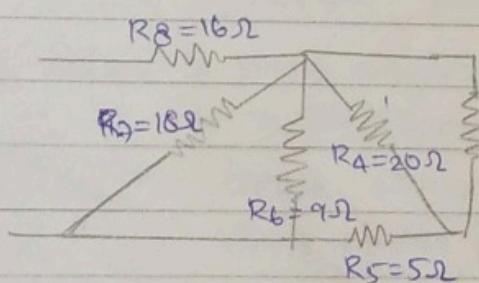
$$R_{S1} = R_{p1} + R_3 = 4 \Omega + 1 \Omega = 5 \Omega$$



$$\frac{1}{R_{p2}} = \frac{1}{R_{S1}} + \frac{1}{R_4}$$

$$\frac{1}{R_{p2}} = \frac{1}{5} + \frac{1}{20}$$
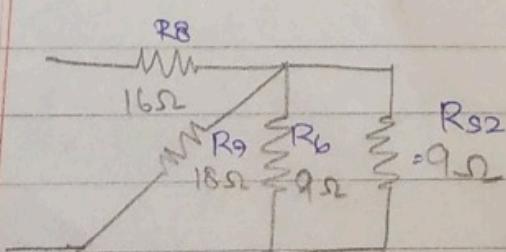
$$R_{p2} = R_{p2} + R_5 \Rightarrow R_{p2} = 4 \Omega + 5 \Omega \Rightarrow R_{p2} = 9 \Omega$$




$$\frac{1}{R_{p3}} = \frac{1}{R_{S2}} + \frac{1}{R_6} + \frac{1}{R_7}$$

$$= \frac{1}{9 \times 2} + \frac{1}{9 \times 2} + \frac{1}{18} = \frac{5}{18}$$

$$R_{p3} = \frac{18}{5} \Omega = 3.6 \Omega$$


$$R_{eq} = R_{p3} + R_8 = (16 + 3.6) \Omega = 19.6 \Omega$$

## current & voltage division

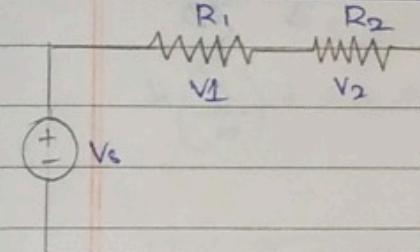

$$V_1 = R_1 \cdot V$$

$$R_1 + R_2 + R_3 \dots$$

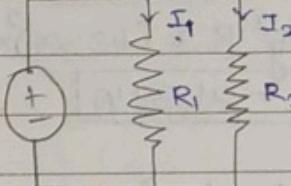

\* Voltage divides in series circuit

$$\star \cancel{I} = V_1 = IR_1$$

$$I = \frac{V_s}{R_{eq}} = \frac{V_s}{R_1 + R_2}$$

$$V_1 = \frac{V_s}{R_1 + R_2} \cdot R_1$$

$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) \cdot V_s$$

$$\text{If } V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V_s$$

\* Current divides in parallel circuits

$$\star I_1 = \frac{V}{R_1}; V = I R_{eq}$$


$$= I \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) V_s ; I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I$$

$$\text{If } I_2 = \left( \frac{R_1}{R_1 + R_2} \right) V_s$$

$$I_1 = \frac{G_1}{G_1 + G_2 + G_3 + G_4} I \quad G = \text{conductance}$$

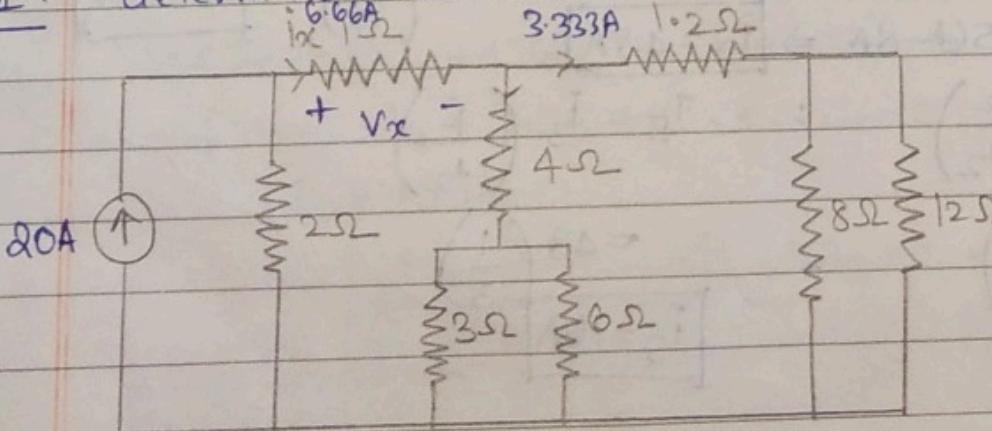
exp 1: determine  $V_x$  and Power absorbed by the  $12\Omega$  resistor



$$\therefore V_x = i_x (1)$$

to find  $i_x$

reducing the circuit to

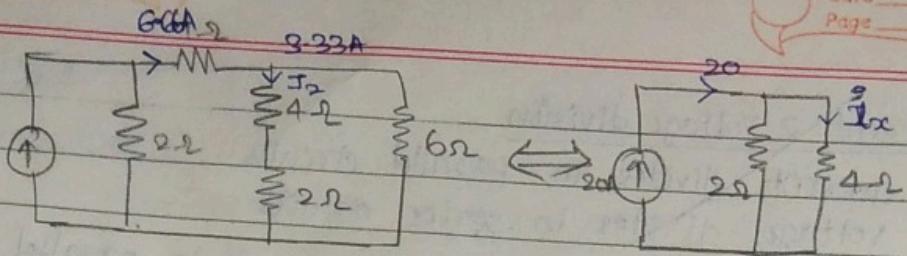

$$i_x = I \left( \frac{2}{2+4} \right) = 20 \left( \frac{2}{6} \right) = \frac{20}{3} A = 6.667 A$$

$$V_x = i_x(1\Omega) \Rightarrow V_x = 6.667 V$$

To calculate Power across  $1\Omega$  resistor, we should know the current ( $I_y$ ) flowing through it.


$$I_2 = 6.667 \left( \frac{6}{6+6} \right) = \frac{20}{3} \left( \frac{1}{2} \right) = \frac{10}{3} = 3.333 A$$

$$I_y, I_y = 3.333 \left( \frac{8}{12+8} \right) = \frac{3.333}{20} \times \frac{8}{20} = \frac{210}{3} \times \frac{84}{20} = 1.333$$


$$\text{Power} = I_y^2 R = (1.333)^2 \times 1\Omega$$

$$P = 21.33 W$$

Exp 2 determine  $i_1$  to  $i_5$

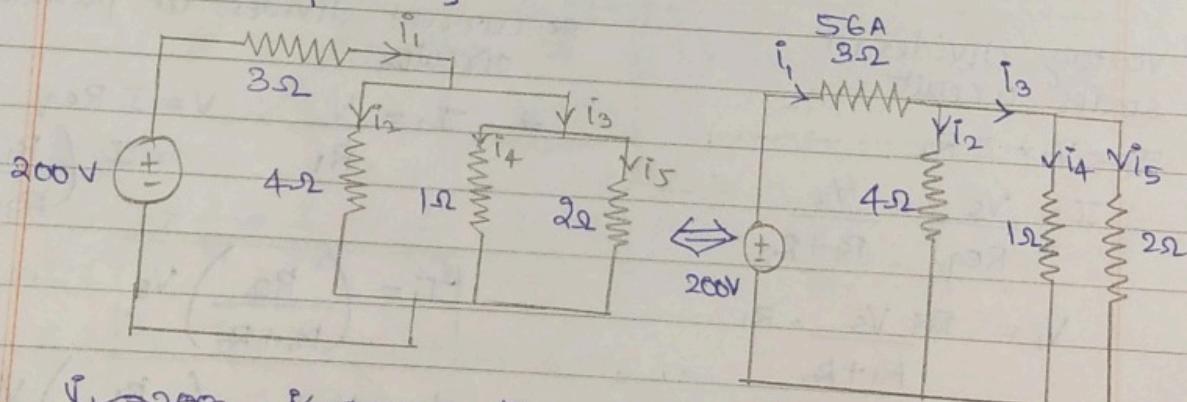
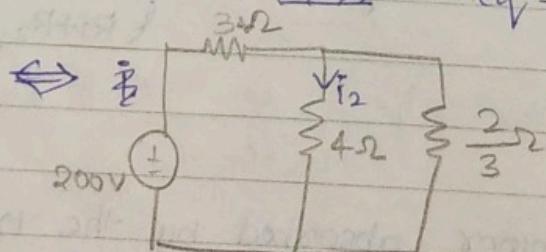
$$i_1 = 200 \text{ A} \quad V = 200 \text{ V} \quad R_{eq} = \frac{25}{7} \Omega; \quad i_1 = \frac{V}{R_{eq}} = \frac{200 \times 7}{25} \Rightarrow i_1 = 56 \text{ A}$$



$$i_2 = i_1 - i_2 = 56 - 8 \text{ A} \Rightarrow i_2 = 48 \text{ A}$$

$$i_4 = i_3 \left( \frac{2}{1+2} \right) : \quad i_5 = i_3 \left( \frac{1}{1+2} \right)$$


$$= 48 \left( \frac{2}{3} \right)$$

$$i_4 = 32 \text{ A}$$

$$= 48 \left( \frac{1}{3} \right)$$

$$i_5 = 16 \text{ A}$$

Exp 3:

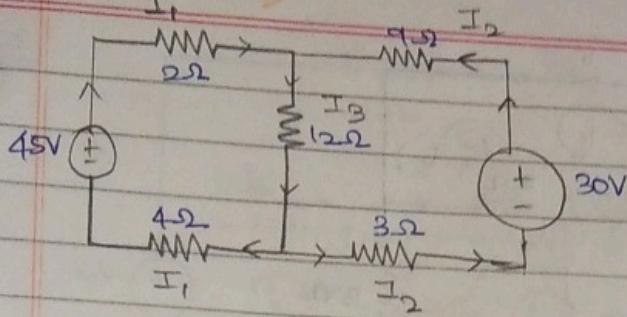

for loop 1:  $-45 + 25I_1 + 12I_3 + 4I_1 = 0$   
 $-45 + 25I_1 + 12I_1 + 12I_2 + 4I_1 = 0$   
 $41I_1 + 12I_2 = 45 \quad \text{--- (1)}$

For loop 2:  $-30 + 9I_2 + 12I_3 + 3I_2 = 0$

$$-30 + 12I_2 + 12I_1 + 12I_2 = 0$$

$$12I_1 + 24I_2 = 30 \Rightarrow 2I_1 + 4I_2 = 5 \quad \text{--- (2)}$$

~~$3I_1 + 12I_2 = 45$~~

~~$6I_1 + 12I_2 = 15$~~

$$35I_1 - 30 = 0 \Rightarrow I_1 = \frac{6}{7} A = 0.857 A$$


$$2\left(\frac{6}{7}\right) + 4I_2 = 5 \Rightarrow 4I_2 = 5 - \frac{12}{7} \Rightarrow 4I_2 = \frac{35 - 12}{7}$$

$$I_2 = \frac{23}{28} A = 0.8214$$

$$\boxed{I_3 = 1.678 A}$$

35  
12  
23

Exp 4:

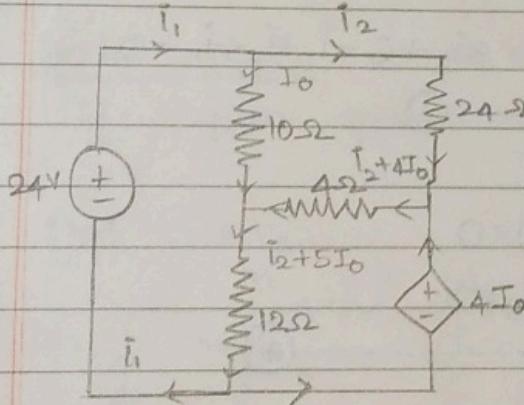

In loop 1:  $I_0 = i_1 - i_2 \Rightarrow i_1 = I_0 + i_2$

$$-24 = 10I_0 + 12(i_2 + 5I_0)$$

$$-24 = 10I_0 + 12i_2 + 60I_0$$

$$-70I_0 + 12i_2 = 0$$

$$85I_0 + 6i_2 + 12 = 0 \quad \text{--- (1)}$$

In loop 2:-

$$24i_2 + 4(i_2 + 4I_0) - 10I_0 = 0$$

$$24i_2 + 4i_2 + 4I_0 - 10I_0 = 0$$

$$28i_2 - 6I_0 = 0 \Rightarrow 14i_2 - 3I_0 = 0 \quad \text{--- (2)}$$

In loop 3:-

$$-4I_0 + 4(i_2 + 4I_0) + 12(i_2 + 5I_0) = 0$$

$$-4I_0 + 4i_2 + 16I_0 + 12i_2 + 60I_0 = 0$$


$$16i_2 + 72I_0 = 0$$

$$4i_2 + 18I_0 = 0 \Rightarrow 2i_2 + 9I_0 = 0 \quad \text{--- (3)}$$

$$2I_0 = -0.3307 A \Rightarrow I_0 = \frac{3}{12} \left( \frac{-42}{127} \right) \Rightarrow I_2 = 0.0708 A$$

$$\boxed{i_1 = -0.4015 A}$$

Q5.

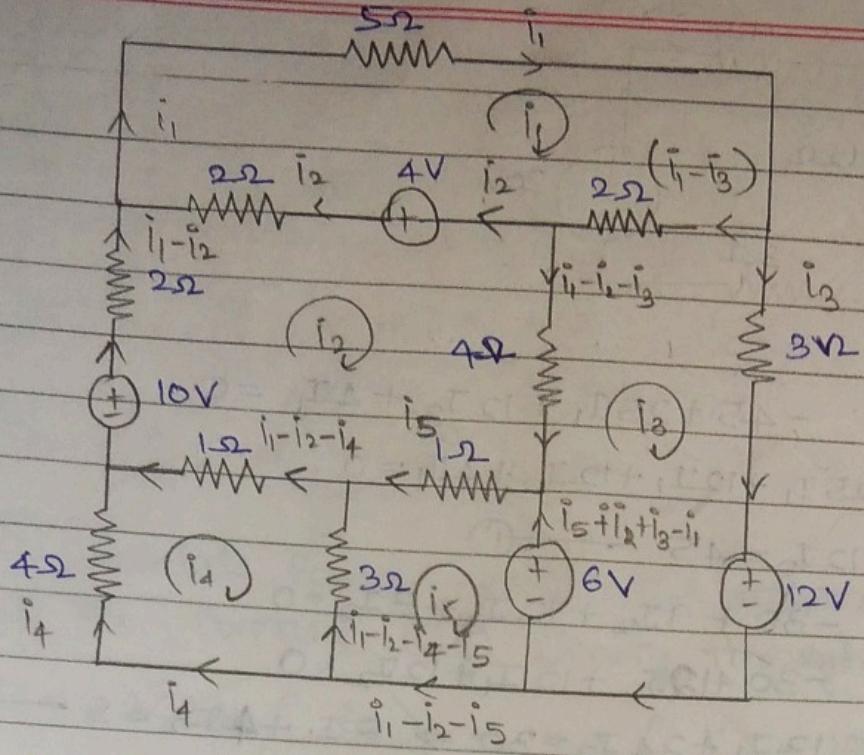

in loop 1:

$$5i_1 + 2(i_1 - i_3) - 4 + 2i_2 = 0$$

$$5i_1 + 2i_1 - 2i_3 - 4 + 2i_2 \Rightarrow 7i_1 + 2i_2 - 2i_3 - 4 = 0 \quad \text{--- (1)}$$

in loop 2:-

~~$-10 + 2(i_1 - i_2) - 2i_2 + 4 + 4(i_1 - i_2 - i_3) = 0 + i_5 + i_1 - i_2 - i_4 = 0$~~

~~$6 + 2i_1 - 2i_2 - 2i_2 + 4i_1 - 4i_2 - 4i_3 + i_5 + i_1 - i_2 - i_4 = 0$~~

$$7i_1 - 9i_2 - 4i_3 - i_4 + i_5 = 0 \quad \text{--- (2)}$$

in loop 3:-

$$3i_3 + 12 - 6 - (i_1 - i_2 - i_3) = 0 \Rightarrow 3i_3 + 6 - i_1 + i_2 + i_3 = 0$$

$$6 - i_1 + i_2 + 4i_3 = 0 \quad \text{--- (3)}$$

in loop 4:-

$$4i_4 - i_1 + i_2 + i_4 - 3i_1 + 3i_2 + 3i_4 + i_5 = 0$$

$$4i_4 - i_1 + i_2 + i_4 - 3i_1 + 3i_2 + 3i_4 + i_5 = 0$$

$$-4i_1 + 4i_2 + 8i_4 + i_5 = 0 \quad \text{--- (4)}$$

in loop 5:-

$$-6 + i_5 - 3(i_1 - i_2 - i_4 - i_5) = 0$$


$$-6 + i_5 - 3i_1 + 3i_2 + 3i_4 + 3i_5 = 0$$

$$-3i_1 + 3i_2 + 3i_4 + 4i_5 = 6 \quad \text{--- (5)}$$

$$i_1 = -0.1065A \quad ; \quad i_2 = 0.6742A \quad ; \quad i_3 = -1.695A$$

$$i_4 = -0.357A \quad ; \quad i_5 = -0.3237A$$

## POD 2

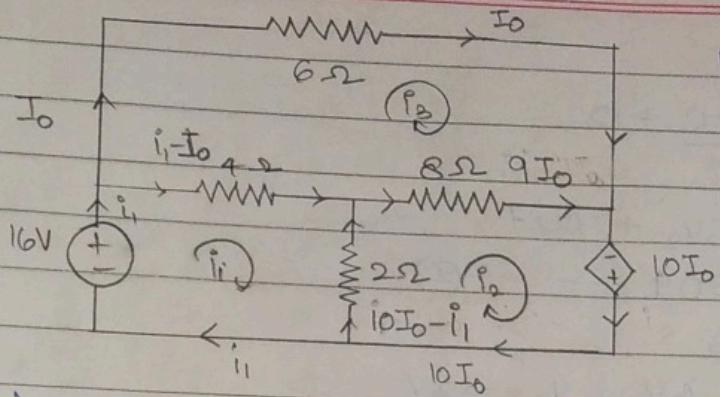

Find current through  
the circuit.

$$\text{along loop 1: } -16 + 4(i_1 - I_o) - 2(I_o I_o - i_1) = 0$$

$$-16 + 4i_1 - 4I_o - 2I_o I_o + 2i_1 = 0 \Rightarrow 6i_1 - 24I_o - 16 = 0$$

$$3i_1 - 12I_o - 8 = 0 \quad \text{---} \quad (1)$$

along loop 2 :-

$$-10I_0 + 2(10I_0 - i_1) + 8(9I_0) = 0$$

$$-10I_0 + 20I_0 - 2i_1 + 72I_0 = 0$$

$$82I_0 - 2i_1 = 0 \Rightarrow i_1 = 41I_0 \quad \text{--- (2)}$$

$$3(41I_0) - 12I_0 - 8 = 0 \Rightarrow 123I_0 - 12I_0 - 8 = 0$$


$$\Rightarrow 111I_0 - 8 = 0 \Rightarrow \boxed{\frac{I_0 - 8}{111} A} = 0.0720A$$

$$i_1 = 41 \left( \frac{8}{111} \right) \neq \boxed{i_1 = 2.954 \text{ A}}$$

Nodal analysis - use use kcl

If  $I$  flows from A to B, then  $i = \frac{V_A - V_B}{R}$

1) Find  $V_1 \otimes V_2$

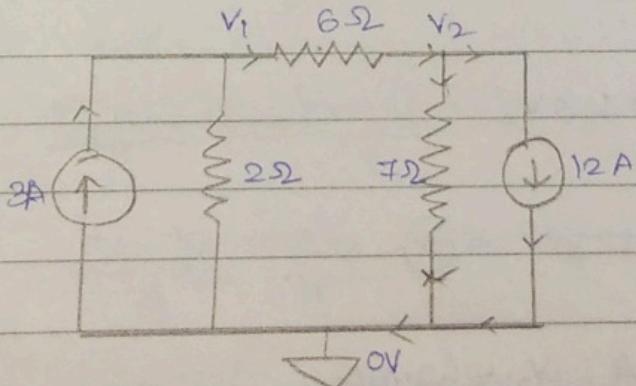

applying KCL, at node 1

$$Z = \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{6}$$

$$8V_1 - 2V_2 = 36$$

$$4V_1 - V_2 = 18 \quad \text{--- (1)}$$

at node 2:-

$$\frac{V_1 - V_2}{6} = \frac{V_2 - 0}{7} + 12$$


$$7V_1 - 7V_2 = 6V_2 + 72 \times 7$$

$$7V_1 - 13V_2 = 509 \quad \textcircled{2}$$

solving ① & ②,

$$V_1 = -6V \quad ; \quad V_2 = -42V$$

2)

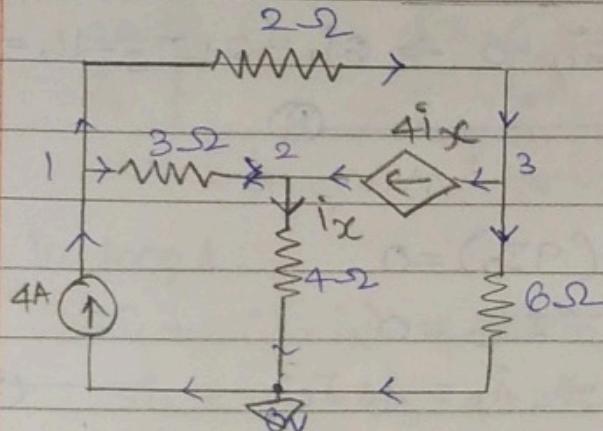

Find  $i_x = ?$

at node 2:

$$i_x = \frac{V_2 - 0}{4}$$

Applying KCL at nodes 1

$$4 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2} \Rightarrow 24 = 2V_1 - 2V_2 + 3V_1 - V_3$$
$$\Rightarrow 5V_1 - 2V_2 - 2V_3 = 24 \quad \textcircled{1}$$

At node 2:-

$$\frac{V_1 - V_2}{3} + 4i_x = i_x \Rightarrow \frac{V_1 - V_2}{3} + \frac{3V_2}{4} = 0$$

$$4V_1 + 5V_2 = 0 \quad \textcircled{2}$$

at node 3:-

$$\frac{V_1 - V_3}{2} = \frac{V_3 - 0}{6} + 4i_x$$

$$24V_1 - 24V_3 = 8V_3 + 48V_2$$

$$24V_1 - 48V_2 - 32V_3 = 0$$

$$3V_1 - 6V_2 - 4V_3 = 0 \quad \textcircled{3}$$


Solving ①, ②, ③

$$V_1 = 32V ; V_2 = -25.6V ; V_3 = 62.4V$$

$$i_x = -6.4A$$

3) H.W

write nodal equations.

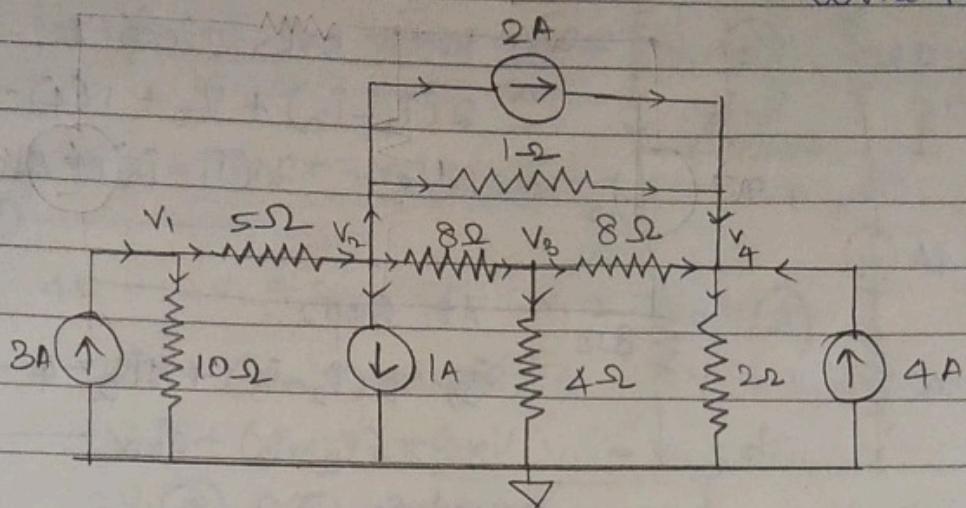

at node 1:-  $3 = \frac{v_1 - 0}{10} + \frac{(v_1 - v_2) \times 2}{5 \times 2}$

$$30 = v_1 + 2v_1 - 2v_2 \Rightarrow 3v_1 - 2v_2 = 30 \quad \text{--- (1)}$$

at node 2:-  $\frac{v_1 - v_2}{5} = 1 + \frac{v_2 - v_3}{8} + 2 + \frac{v_2 - v_4}{1}$

$$\frac{8(v_1 - v_2)}{5 \times 8} + \frac{(v_3 - v_2)5}{8 \times 5} = 3 + v_2 - v_4$$

$$8v_1 - 8v_2 + 5v_3 - 5v_2 = 40 (3 + v_2 - v_4)$$

$$8v_1 - 13v_2 + 5v_3 = 120 + 40v_2 - 40v_4$$

$$8v_1 - 53v_2 + 5v_3 + 40v_4 = 120 \quad \text{--- (2)}$$

at node 3:-

$$\frac{v_2 - v_3}{8} = \frac{v_3 - v_4}{8} + \frac{2v_3}{8} \Rightarrow v_2 - v_3 = v_3 - v_4 + 2v_3$$

$$v_2 - 4v_3 + v_4 = 0 \quad \text{--- (3)}$$


at node 4:-

$$\frac{v_3 - v_4}{8} + \frac{v_2 - v_4}{1} + 2 + 4 = \frac{v_4 \times 4}{2 \times 4}$$

$$\frac{v_3 - v_4}{8} - \frac{4v_4}{8} + v_2 - v_4 + 6 = 0$$

$$v_3 - 5v_4 + 8v_2 - 8v_4 + 48 = 0$$
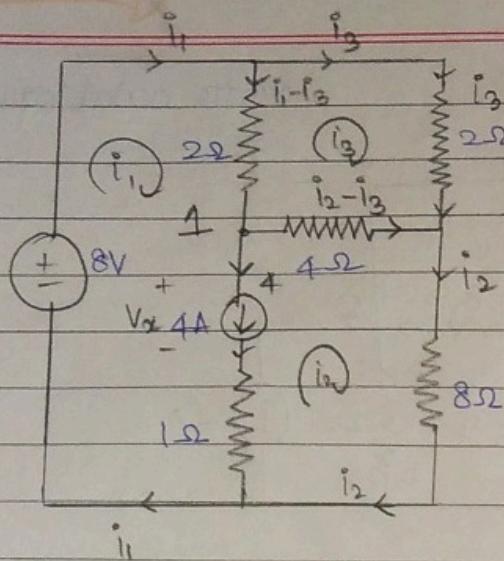
$$8v_2 + v_3 - 3v_4 + 48 = 0 \quad \text{--- (4)}$$



Find  $i_1, i_2, i_3$ :

From KVL, at loop 1 :-  
 $2(i_1 - i_3) + V_x + 1(4) - 8 = 0$   
 $V_x = -2(i_1 - i_3) + 4 \quad \text{--- (1)}$

At loop 2:-

~~2*i*<sub>2</sub>~~ + 4(*i*<sub>2</sub> - *i*<sub>3</sub>) + 8*i*<sub>2</sub> - 4 - *V*<sub>x</sub> = 0  
 $V_x = 4(i_2 - i_3) + 8i_2 \quad \text{--- (2)}$

equating (1) & (2)

$$2\frac{i}{3} - 4(i_2 + i_3) - 8(i_1 - i_3)$$

$$-2(i_1 - i_3) + 8 = 4(i_2 - i_3) + 8i_2$$

$$8 = 2i_1 - 6i_3 + 2i_2 \quad \text{--- (3)} \quad 8 =$$

At loop 3:-

$$8i_2 - 2i_3 - 4(i_2 - i_3) - 2(i_1 - i_3) = 0$$

$$i_1 - i_2 = 4 \quad 2i_3 - 4i_2 + 4i_3 - 2i_1 + 2i_3 = 0$$

$$\Rightarrow -2i_1 - 4i_2 + 8i_3 = 0 \Rightarrow -i_1 - 2i_2 + 4i_3 = 0 \quad \text{--- (4)}$$

From KCL,  $i_1 = i_2 + 4$

$$\textcircled{3} \Rightarrow 2(i_2 + 4) + 12i_2 - 6i_3 = 8 \Rightarrow 2i_2 + 8 + 12i_2 - 6i_3 = 8$$

$$\Rightarrow 14i_2 - 6i_3 = 0 \Rightarrow 7i_2 - 3i_3 = 0$$

$$\textcircled{4} \Rightarrow -(i_2 + 4) - 2i_2 + 4i_3 = 0 \Rightarrow -i_2 - 4 - 2i_2 + 4i_3 = 0$$

$$\Rightarrow 3(-3i_2 + 4i_3 = 0) \Rightarrow -9i_2 + 12i_3 = 12$$


$$\begin{array}{r} 28i_2 - 12i_3 = 0 \\ \hline 19i_2 = 12 \end{array}$$

$$i_2 = \frac{12}{19} \text{ A}$$

$$i_3 = \frac{7}{3} i_2 = \frac{7}{3} \times \frac{12}{19} \Rightarrow i_3 = \frac{28}{19} \text{ A}$$

$$i_1 = \frac{12}{19} + 4 \Rightarrow i_1 = \frac{88}{19} \text{ A}$$

A.

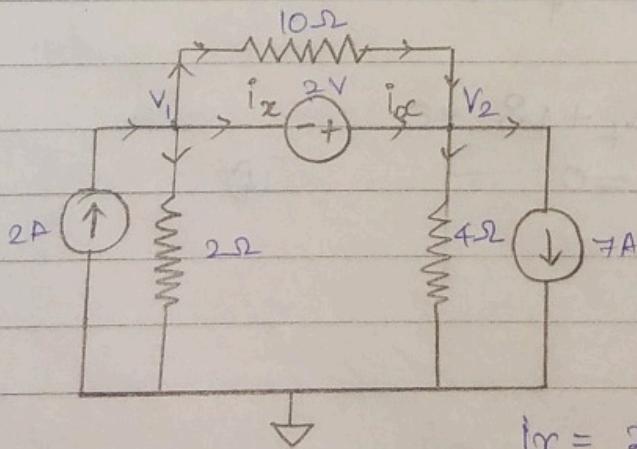

Find  $V_1, V_2$

solution:-

$$2 = \frac{V_1 \times 5 + i_x + V_1 - V_2}{2 \times 5} + \frac{V_1 - V_2}{10}$$

$$i_x = \frac{20}{20} \frac{20 - 5V_1 + V_2 - V_1}{10}$$

$$i_x = \frac{20 - 6V_1 + V_2}{10} \quad \text{--- (1)}$$

\* Linearity is a property of an element describing a linear relationship btwn input & output.  
For ex: doubling voltage across an elements <sup>Date</sup> doubles the I flowing through it. Such circuit is called linear circuit.

at node 2:-

$$i_x + 2(V_1 - V_2) = \frac{V_2}{8\Omega} + \frac{7V_2}{4\Omega} \Rightarrow i_x = \frac{5V_2 + 140 + 2V_2 - 2V_1}{20}$$

$$i_x = \frac{-2V_1 + 7V_2 + 140}{20} \quad \textcircled{2}$$

$$40 - 12V_1 + 2V_2 = -2V_1 + 7V_2 + 140$$

$$10V_1 + 5V_2 + 100 = 0 \Rightarrow 2V_1 + V_2 + 20 = 0 \quad \textcircled{3}$$

$$V_1 - V_2 = 2 \quad V_1 - V_2 = -2 \quad \textcircled{4}$$

$$3V_1 = -22 \Rightarrow V_1 = \frac{-22}{3} \quad V_1 + 22 = 22 \quad \begin{matrix} 1/2 \\ \cancel{22} \\ 16 \end{matrix}$$

$$V_2 = 2 - \frac{22}{3} \Rightarrow V_2 = \frac{6-22}{3} \Rightarrow V_2 = -\frac{16}{3}$$

### Superposition Principle


Voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or I through) that element due to each independent source acting alone.

Steps to apply Superposition principle:

1) Turn off all independent sources except one source. Find the output (voltage/current) due to that active source using the techniques covered in ch 2 & 3.

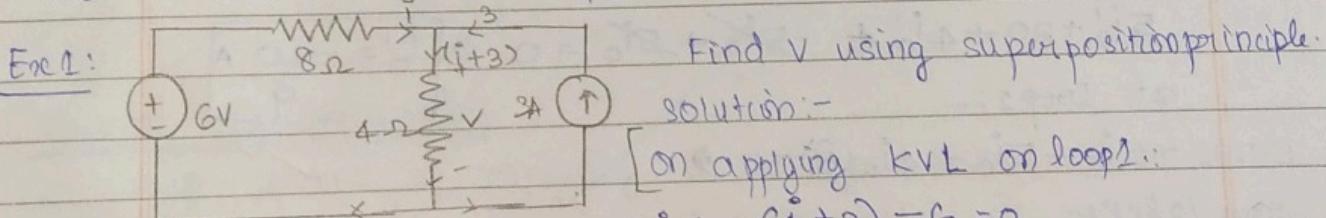2) Repeat step 1 for each of the other independent sources.

Ex 1: 3) Find the total contribution by adding algebraically all the contribution due to independent sources.



Solution:-


[On applying KVL on loop 1:

$$8i + 4(i+3) - 6 = 0$$


$$12i = -6 \Rightarrow i = -0.5$$

$$V = 4(i+3) \Rightarrow V = 4(3-0.5) \Rightarrow V = 10V$$

In absence of 3A current source:-

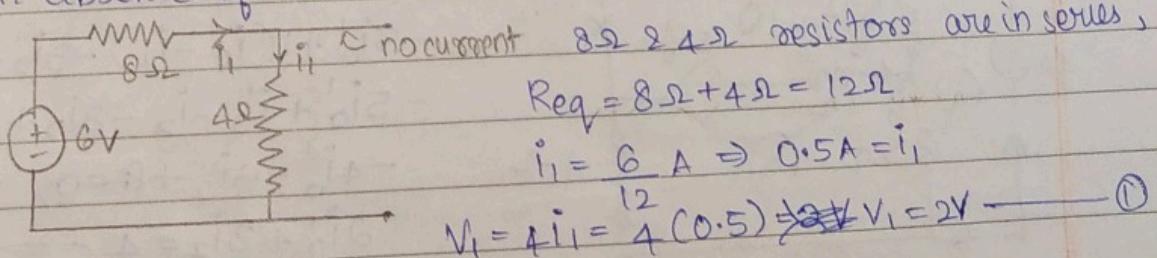

in the absence of voltage source :-

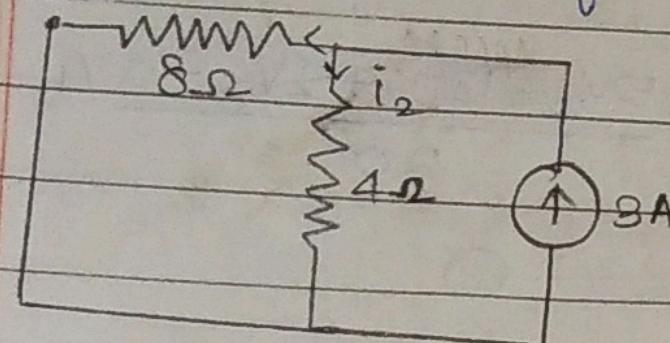

according to current division rule  
in parallel circuit,


$$i_2 = \frac{8}{4+8} (3) = \frac{2}{3} \times 3 = 2A$$

$$V_2 = 4\Omega (2A) \Rightarrow V_2 = 8V \quad \text{--- (2)}$$

$$V = V_1 + V_2 = 2V + 8V \Rightarrow V = 10V$$

H.W

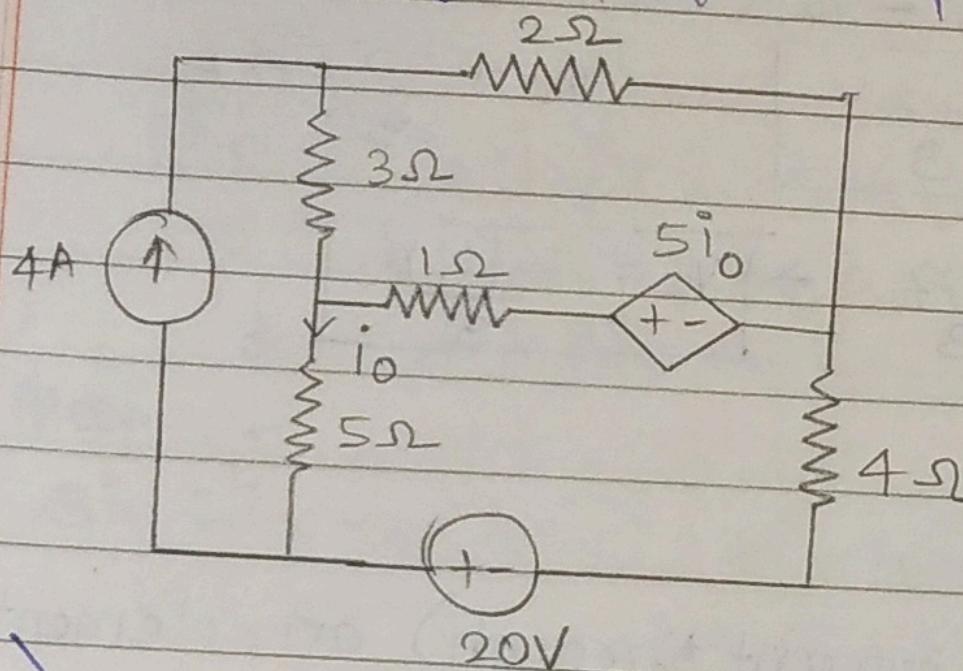Find  $i_o$  using superposition principle,



$$\text{Prove that : } i_o = i_o' + i_o''$$


where  $i_o''$  is current through  
5Ω resistor when current

source is removed &

$i_o'$  is the current through  
5Ω resistor when voltage  
source is removed.

Solution:-

when voltage source is removed:-

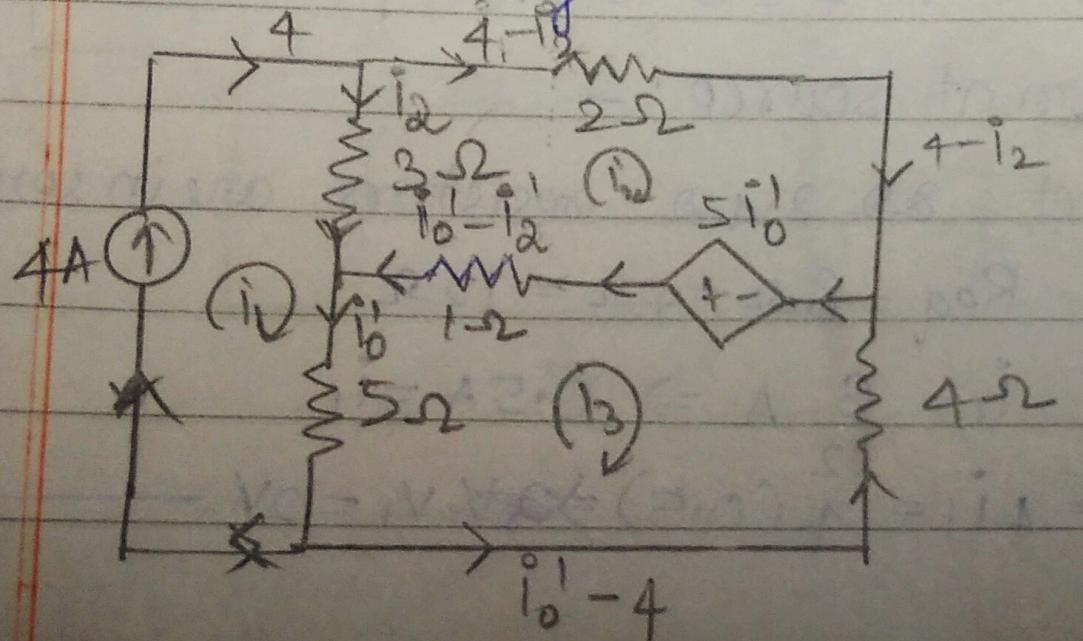

around loop 2:-

$$-5i_0' + 1(i_0' - i_2) - 3i_2 + 2(4 - i_2) = 0$$
$$-5i_0' + i_0' - i_2 - 3i_2 + 8 - 2i_2 = 0$$

$$-4i_0' - 6i_2 + 8 = 0$$

$$2i_0' + 3i_2 = 4$$

①

around loop 3:-

$$-4(i_0' - 4) - 5i_0' - 1(i_0' - i_2) + 5i_0'' = 0$$


$$-4i_0 + 16 - 5i_0' - i_0' + i_2 + 5i_0'' = 0$$

$$\rightarrow -5i_0' + i_2 + 16 = 0 \quad \text{||||||} \quad (2)$$

$$\begin{aligned} -15i_0' + 3i_2 &= -48 \\ 2i_0' + 3i_2 &= 4 \\ -17i_0' &= -52 \end{aligned}$$

$$\boxed{i_0' = \frac{-52}{17} \text{ A}}$$

when current source is removed :-

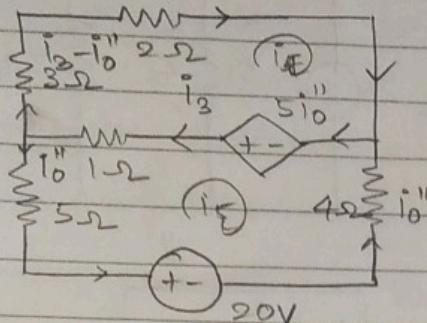

along loop 4:-

$$-5i_0'' + i_3 + 3(i_3 - i_0') + 2(i_2 - i_0') = 0$$

$$-5i_0'' + i_3 + 5i_3 - 5i_0' = 0$$

$$6i_3 - 10i_0' = 0$$

$$3i_3 - 5i_0'' = 0 \quad (3)$$

along loop 5:-

$$-i_3 + 5i_0'' - 4i_0' - 20 - 5i_0'' = 0$$

$$-i_3 + 4i_0'' = -20 \quad (4)$$

$$3i_3 - 5i_0'' = 0 \Rightarrow 3(-4i_0'' - 20) - 5i_0'' = 0$$

$$-12i_0'' - 60 - 5i_0'' = 0 \Rightarrow -17i_0'' = 60$$



$$\boxed{i_0'' = \frac{-60}{17} \text{ A}}$$


total current,  $i_0 = i_0' + i_0'' = \frac{52}{17} \text{ A} - \frac{60}{17} \text{ A}$

$$\boxed{i_0 = \frac{-8}{17} \text{ A}}$$
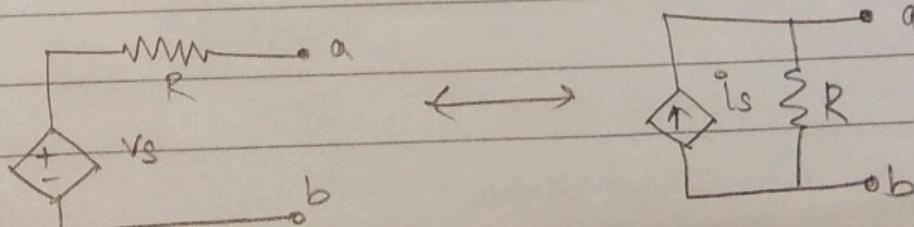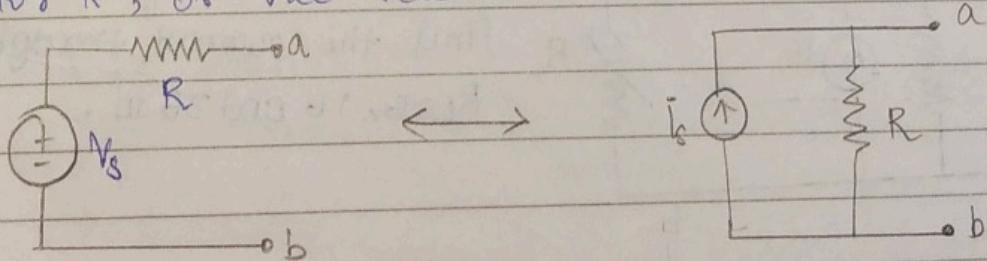
### Source transformation


is a process of replacing a voltage source  $V_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.



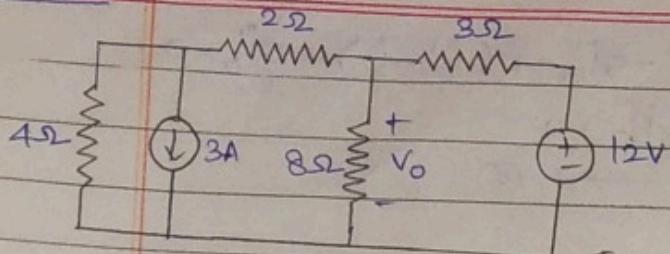Find  $V_o = ?$ 

solution:-

according to source transformation.

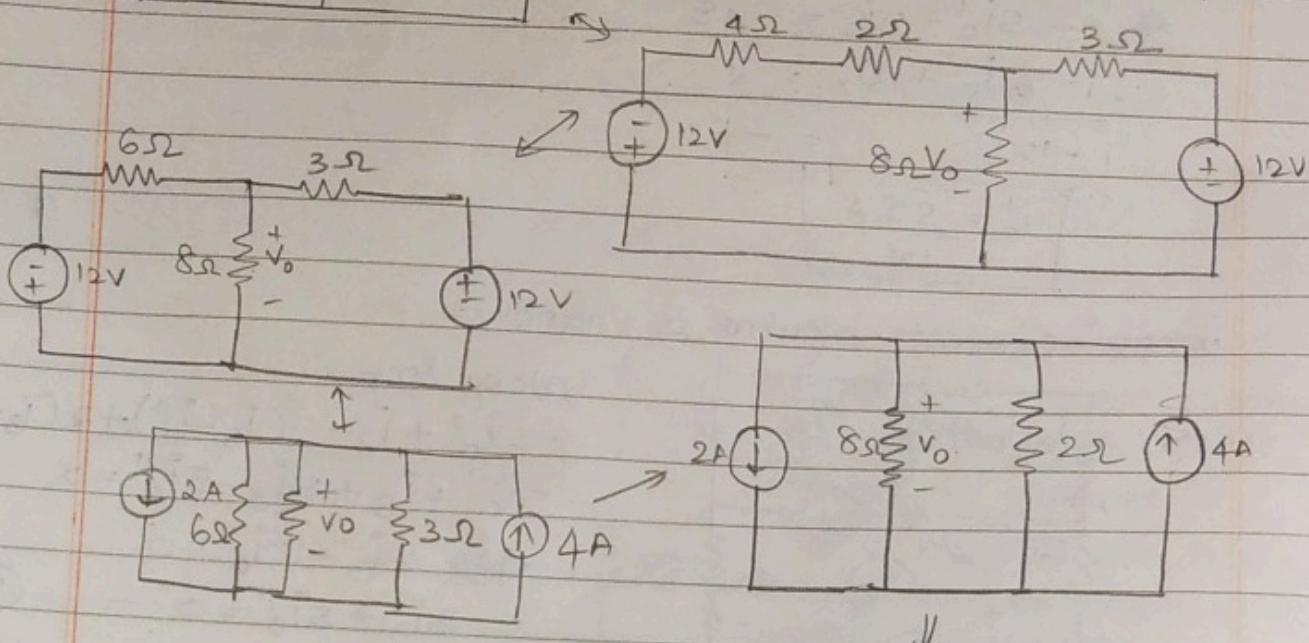


Q28

Q3

according to  
current division rule,


$$I_2 = \frac{2}{2+8} (I) \Rightarrow I_2 = \frac{1}{5} (2) A \Rightarrow V_o = IR \Rightarrow V_o = \frac{2}{5} \times 8$$

$$V_o = \frac{16}{5} N$$

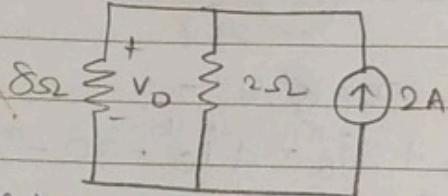Thevenin's theorem

States that a linear 2-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{TH}$  in series with a resistor  $R_{TH}$ , where  $V_{TH}$  is the open-circuit voltage at the terminals and  $R_{TH}$  is the input/equivalent resistance at the terminals when the independent sources are turned off.

Ex 1) Find

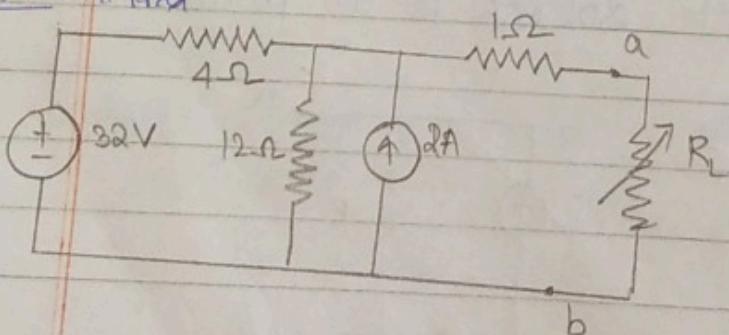


Find the Thevenin equivalent circuit of the given circuit.

Find the current through  $R_L = 6, 16$  and  $36\Omega$ .

To find  $V_{TH}$  :-

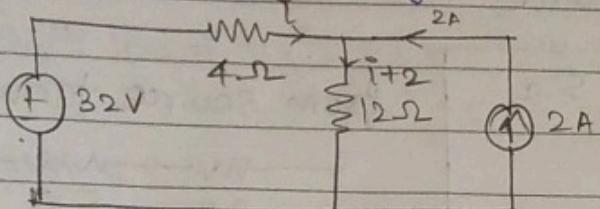use open circuit. we open circuit, we remove  $R_L$ , hence no current flows through  $1\Omega$  resistor.



$V_{TH}$  = Voltage across  $12\Omega$


resistor for which we need to find the current flowing through it.

according to KVL rule:-

$$4i + 12(i+2) = 32 \Rightarrow i = \frac{8}{16} = 0.5A$$

$$\text{Voltage across } 12\Omega = 0.5 \times 12(0.5+2) \Rightarrow V_{TH} = 30V$$

To find  $R_{TH}$  :-

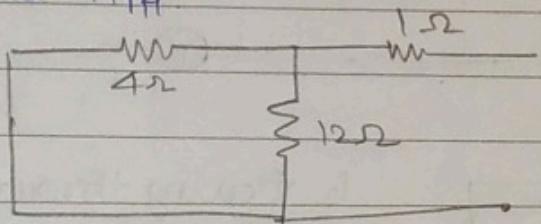


$4\Omega$  &  $12\Omega$  are in parallel

$$R_p = \frac{(4)(12)}{16} \Rightarrow R_p = 3\Omega$$

$$R_{TH} = 3\Omega + 1\Omega \Rightarrow R_{TH} = 4\Omega$$

Finding  $I$  through  $R_L$  :-

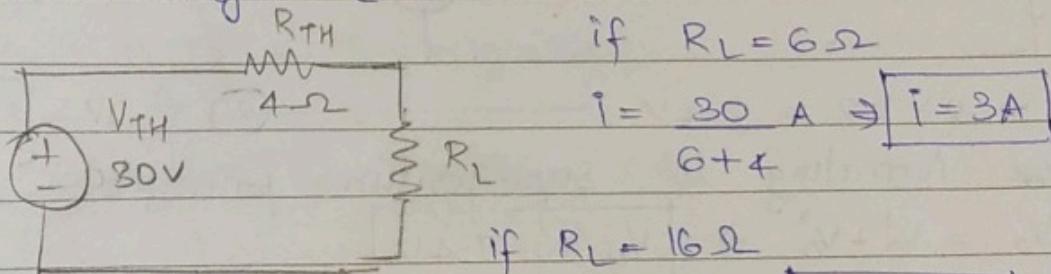

if  $R_L = 6\Omega$


$$i = \frac{30}{6+4} A \Rightarrow i = 3A$$

if  $R_L = 16\Omega$

$$i = \frac{30}{16+4} \Rightarrow i = 1.5A$$


$$\text{if } R_L = 36\Omega \Rightarrow i = \frac{30}{36+4} \Rightarrow i = 0.75A$$

Ex 2:

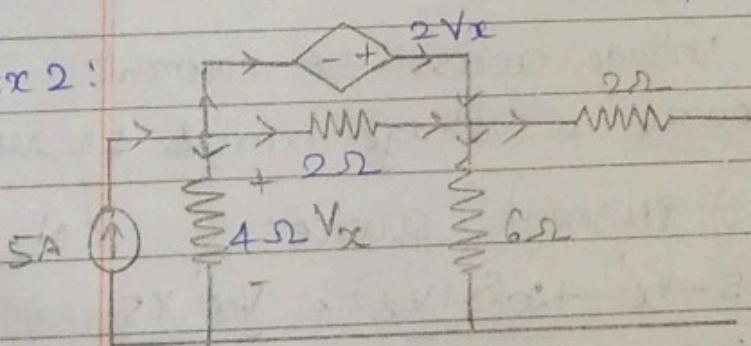

Find Thevenin equivalent of the circuit.

on calculating  $V_{Th}$ :-

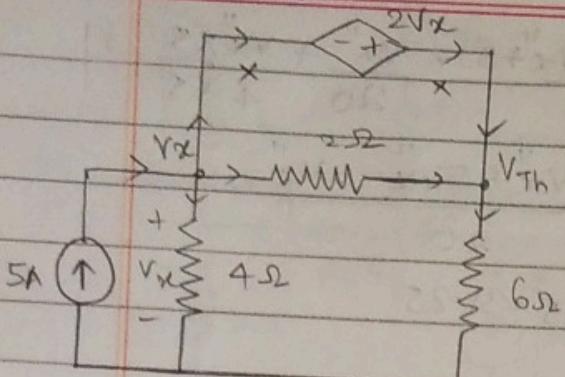

Voltage across a and b  
= Voltage across 6Ω resistor

applying KCL at nodes:-  
at node  $V_{Th}$ :-

$$5 = \frac{V_x}{4} + \frac{V_x - V_{Th}}{2} + x$$

$$x = 5 - \frac{V_x}{4} + \frac{V_{Th} - V_x}{2} \quad \text{--- (1)}$$

at  $V_{Th}$ :-

$$\frac{V_{Th}}{6} = \frac{V_x - V_{Th}}{2} + x \Rightarrow x = \frac{V_{Th}}{6} + \frac{V_{Th} - V_x}{2} = x$$

equating two x values,

$$2V_{Th} + 3V_x = 60 \quad \text{--- (1)}$$


applying KVL across loop 1,  $-2V_x + (V_{Th} - V_x) = 0 \quad \text{--- (2)}$

solving (1) & (2)

$$\therefore [V_{Th} = 20V]$$

on calculating  $R_{Th}$ :-

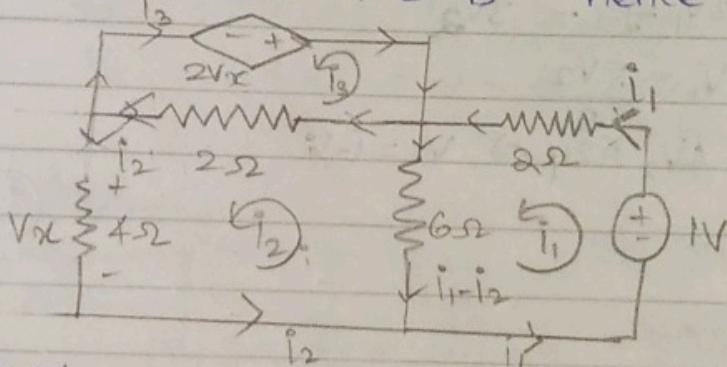Due to the presence of Dependent voltage source which cannot be short circuited, we place an ~~not~~ 1V voltage source across the a & b. hence  $R_{Th} = \frac{1}{i_1}$ .



applying KVL in loop 1:-

$$-1 + 2i_1 + 6(i_1 - i_2) = 0$$

$$8i_1 - 6i_2 = 0 \quad \text{--- (1)}$$

in loop 2:-

$$6i_2 - 3i_1 - i_3 = 0 \quad \text{--- (2)}$$

in loop 3:-

$$2(i_2 - i_3) + 2V_x = 0 \quad \therefore V_x = 4i_2$$

$$2(i_2 - i_3) + 2(4i_2) = 0 \quad \text{--- (3)}$$

solving (1), (2), (3),  $i_1 = \frac{1}{16} A$


$$R_{Th} = \frac{1}{i_1} = \frac{1}{\frac{1}{16}} \Rightarrow R_{Th} = 16\Omega$$

Norton's theorem: a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where  $I_N$  is the short circuit I through the terminals &  $R_N$  is the input or equivalent resistance at the terminals when the independent sources of the circuit are turned off.

\* Can do the previous sum using Norton's theorem connecting 1A current source in parallel to series with  $2\Omega$  resistor to calculate  $I_N$ .

$$\text{hence } \frac{V_{Th}}{I_N} = R_{Th}$$

Maximum Power transfer theorem:

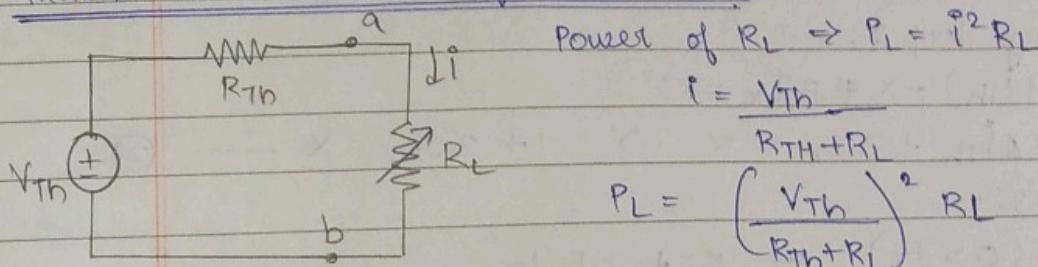


maximum current is drawn, when


$$R_{Th} = R_L$$

hence  $P_L = \left( \frac{V_{Th}}{2R_{Th}} \right)^2 R_{Th} = \frac{V_{Th}^2}{4R_{Th}} \cdot R_{Th}$

$$P_L = \frac{V_{Th}^2}{4R_{Th}}$$

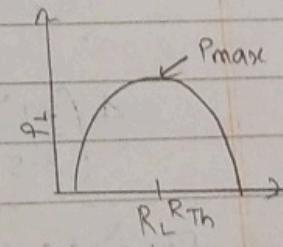

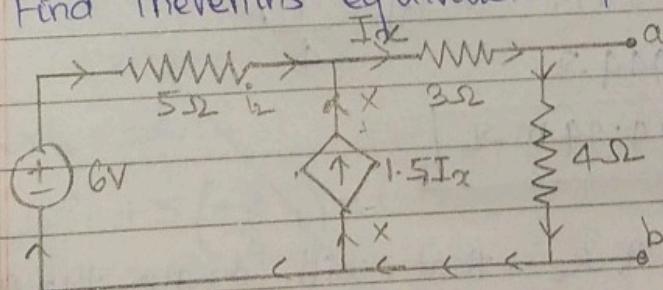H.W : Find Thévenin's equivalent of the circuit



solution: calculating  $V_{Th}$ :-

$V_{Th}$  = Voltage across  $4\Omega$  resistor.

applying KVL along loop 1:-

$$3Ix + 4Ix - x = 0 \Rightarrow x = 7Ix$$

applying KVL along loop 2:-

$$-6 + 5(-0.5Ix) + \cancel{7Ix} = 0 \Rightarrow -6 - 2.5Ix + \cancel{7Ix} = 0$$

$$x = 6 + 2.5Ix \Rightarrow 7Ix - 2.5Ix = 6 \Rightarrow 4.5Ix = 6$$

$$I_x = \frac{G}{3.5} = \frac{12}{3.5} A = 3.43 A$$

Page 35


Voltage across  $\frac{1}{3}$  resistor:

$$= \frac{12}{3.5} A \times 1\Omega = \frac{6.85}{3} V = 2.28 V$$

$V_{Th} = 5.333 V$

Finding  $R_{Th}$ :

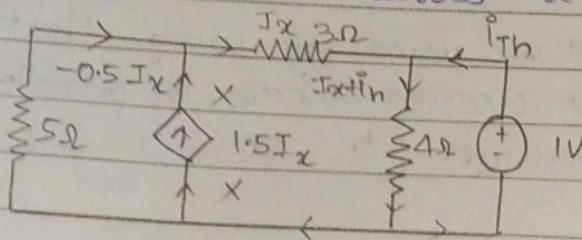removing voltage source & adding an  $1V$  voltage source across  $a$  &  $b$ , so that  $i_{Th} = 1$



applying KVL on loop 1:-

$$4(I_x + i_h) - 1 = 0 \Rightarrow 4I_x + 4i_h = 1 \quad \text{--- (1)}$$

applying along loop 2:-

$$4(I_x + i_h) - x + 3I_x = 0$$

$$4I_x + 4i_h + 3I_x = x \Rightarrow 1 + 3I_x = x \quad \text{--- (2)}$$

along loop 3:-

$$+x = 5(0.5I_x) \Rightarrow x = +2.5I_x$$

~~$$1 + 3I_x = +2.5I_x \Rightarrow +5I_x = 0.5I_x = -1$$~~

~~$$I_x = \frac{-1}{5.5} A \quad I_x = -2 A$$~~

~~$$4\left(\frac{-1}{5.5}\right) + 4i_h = 1 \Rightarrow 4i_h = 1 + \frac{40}{55} A$$~~

~~$$4i_h = \frac{19}{11} \Rightarrow i_h = \frac{19}{44} A$$~~

~~$$R_{Th} = \frac{44}{11} \Omega$$~~

11


~~$$\text{From (1)} \Rightarrow 4(-2) + 4i_h = 1$$~~

~~$$4i_h = 1 + 8 \Rightarrow i_h = \frac{9}{4} A$$~~

~~$$R_{Th} = \frac{4}{9} \Omega = 0.44444 \Omega$$~~

~~$$R_{Th} = 444.44 \Omega$$~~

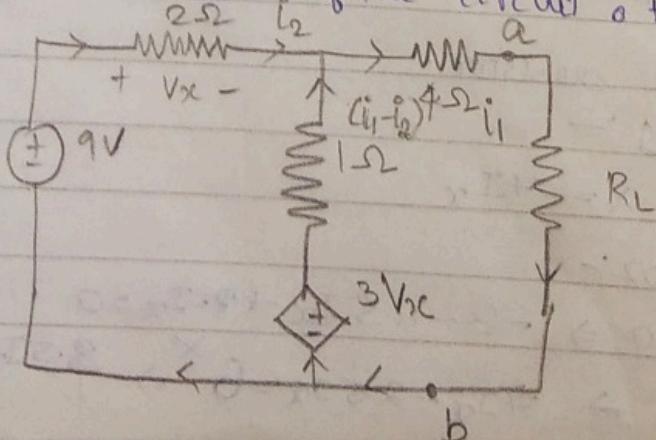
H.W.: Determine the value of  $R_L$  that will draw the max power from the rest of the circuit & calculate maximum power



Calculating  $V_{Th}$  :-

Voltage across  $R_L = V_{Th}$  (Voltage across load resistor & dependent source).

If  $R_L$  is open circuited,

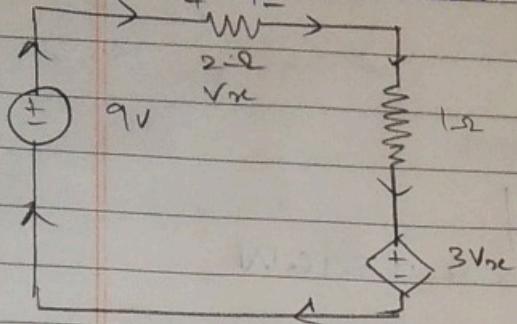

$$-9 + V_x + 1i + 3V_x = 0$$

$$i = \frac{3V_x - 9}{3}$$

$$-9 + V_x + \frac{3V_x - 9 + 3V_x}{3} = 0$$

$$4V_x - 9 = \frac{3x - 9}{3} = 0$$

$$12V_x - 27 + 3x - 9 = 0$$

$$15V_x = 36 \Rightarrow V_x = 2.4V$$


$$\frac{1}{2} \cdot \frac{9}{3} = \frac{3}{3}$$

Voltage across them  $V_{Th} = \frac{3(2.4) - 9 + 3(2.4)}{3}$

$$= 2 \cdot 2 - 0.6 + 7.2 =$$

$$V_{Th} = 6.6V$$

Calculating

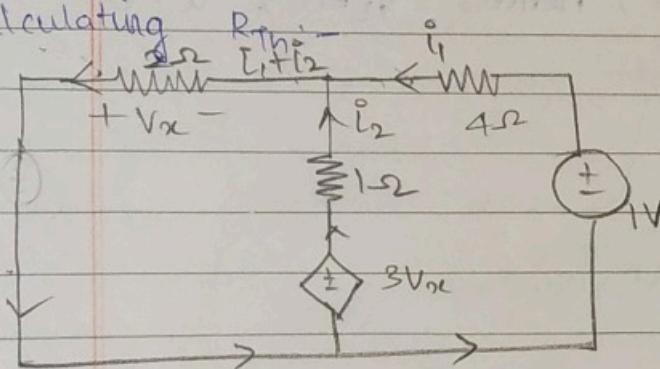

On connecting 1V voltage source across the open circuited load, we get

$$R_{Th} = \frac{1}{i}$$

on applying KVL on loop:-

$$-1 + 4i_1 - 1i_2 + 3V_x = 0 \Rightarrow 4i_1 - i_2 + 6i_1 + 6i_2 = 1$$

$$\Rightarrow 10i_1 + 5i_2 = 1$$

loop 2:-

$$-3V_x + i_2 - V_x = 0 \quad ; \quad V_x = -2(i_1 + i_2)$$

$$-4V_x - 4V_x + i_2 = 0 \Rightarrow -8i_1 - 8i_2 = i_2 \Rightarrow -8i_1 = 9i_2$$

$$\Rightarrow i_2 = \frac{-8}{9} i_1$$

$$\textcircled{1} \Rightarrow 10i_1 + 5\left(\frac{-8}{9} i_1\right) = 1 \Rightarrow 10i_1 - \frac{40}{9} i_1 = 1 \Rightarrow \frac{50}{9} i_1 = 1 \Rightarrow i_1 = \frac{9}{50} A$$

$$R_{Th} = \frac{50}{9} \Omega = 5.55$$

$$V_{Th} = -2(i_1 + i_2)$$

for loop 1:-  $-1 + 4i_1 - i_2 + 3V_x = 0 \Rightarrow -1 + 4i_1 - i_2 - 6i_1 - 6i_2 = 0$

$$-2i_1 - 7i_2 = 1 \quad \textcircled{1}$$

loop 2:-  $-3V_x + i_2 - V_x = 0 \Rightarrow -4V_x + i_2 = 0 \Rightarrow 8i_1 + 8i_2 + i_2 = 0$

$$8i_1 = -9i_2 \Rightarrow i_2 = \frac{-8}{9} i_1$$

$$\text{From } (1) \Rightarrow -2i_1 - i\left(\frac{-8}{9}\right)i = 1$$

$$-\frac{18i_1 + 56i}{9} = 1 \Rightarrow i_1 = \frac{9}{38} \text{ A}$$

$$R_{Th} = \frac{38 \Omega}{9} = 4.222 \Omega$$

$$P = V \cdot I$$

$$P = \frac{V^2}{R}$$

For max power  $\Rightarrow R_{Th} = R_L$



$$P_L = \frac{V_{Th}^2}{4R_L} = \frac{(6.6)^2}{4 \times 4.222} = 2.596 \text{ W}$$

### MODULE:2 : AC circuits

\* Use dont connect capacitor / inductor in DC circuits,

$$V_L = -L \frac{di}{dt} ; \quad i_C = C \frac{dv}{dt}$$

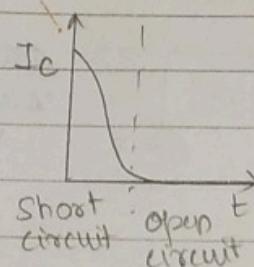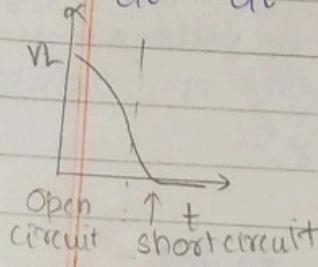$\frac{di}{dt}, \frac{dv}{dt} = 0$  in DC circuit, hence,  $V_L = 0$  &  $i_C = 0$




### Equivalent capacitance


$$\text{Series} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} ; \quad \text{Parallel} \Rightarrow C_{eq} = C_1 + C_2$$

\* AC: current & Voltage are sinusoidal

$$V_t = V_m \sin(\omega t + \phi)$$

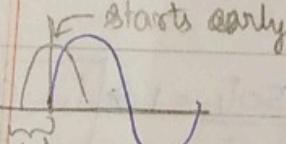

$$V_t = V_m \sin(\omega t + \phi)$$

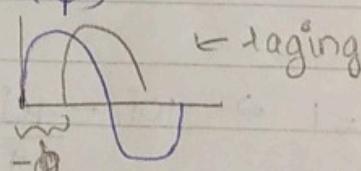

$$V_t = V_m \sin(\omega t - \phi)$$

(should see like which wave reaches peak first/ 0 first)

\*

$$V_{av} = \frac{1}{\pi} \int_0^\pi V \sin \omega t dt$$

$$= -\frac{1}{\pi} [V_m \cos \omega t]_0^\pi$$

$$\boxed{V_{av} = \frac{2V_m}{\pi}}$$

\*

$$V_{RMS} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$

