

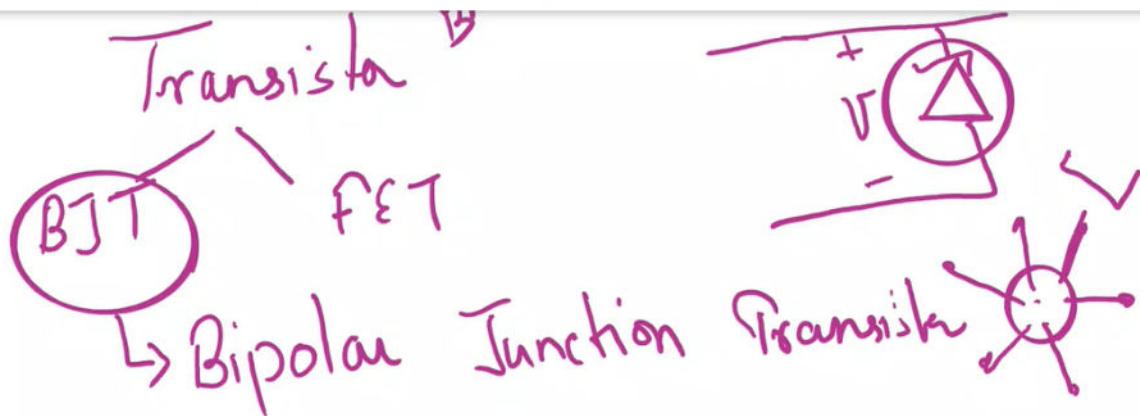
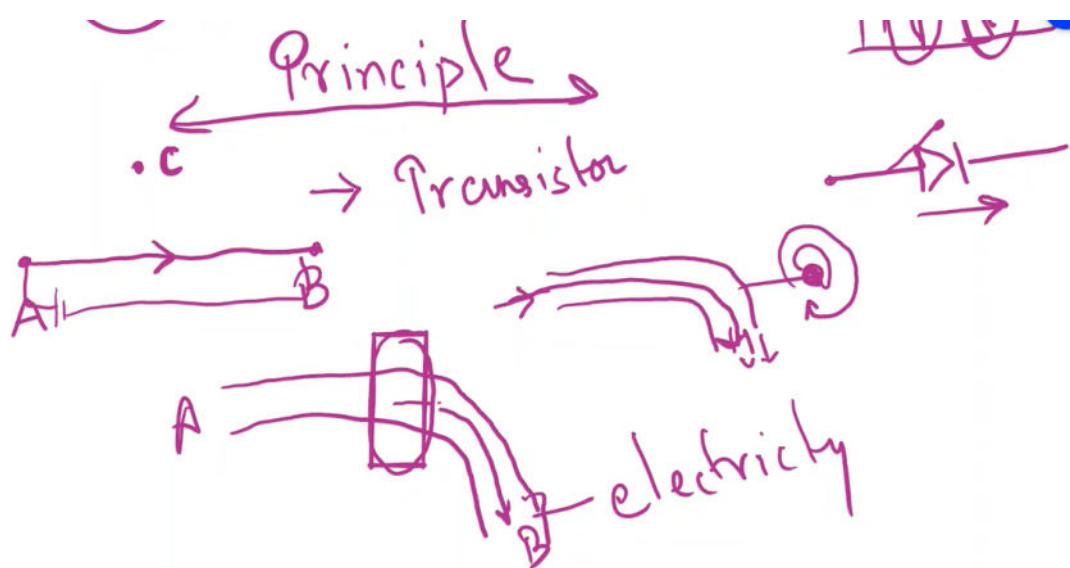
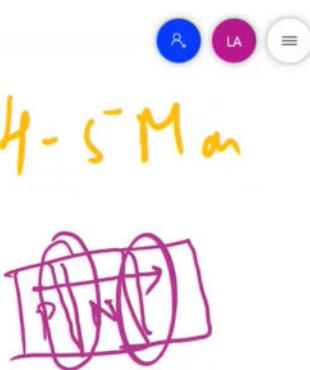


18.10.21

### Module 3: Transistors

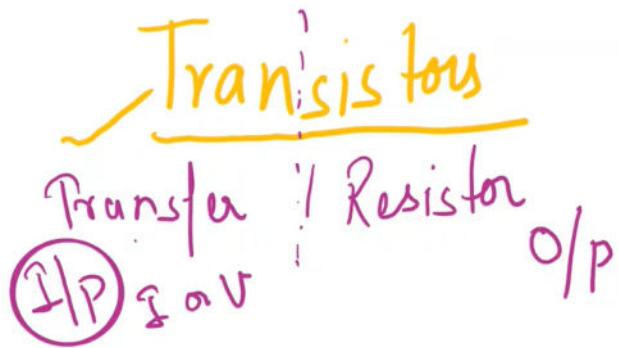



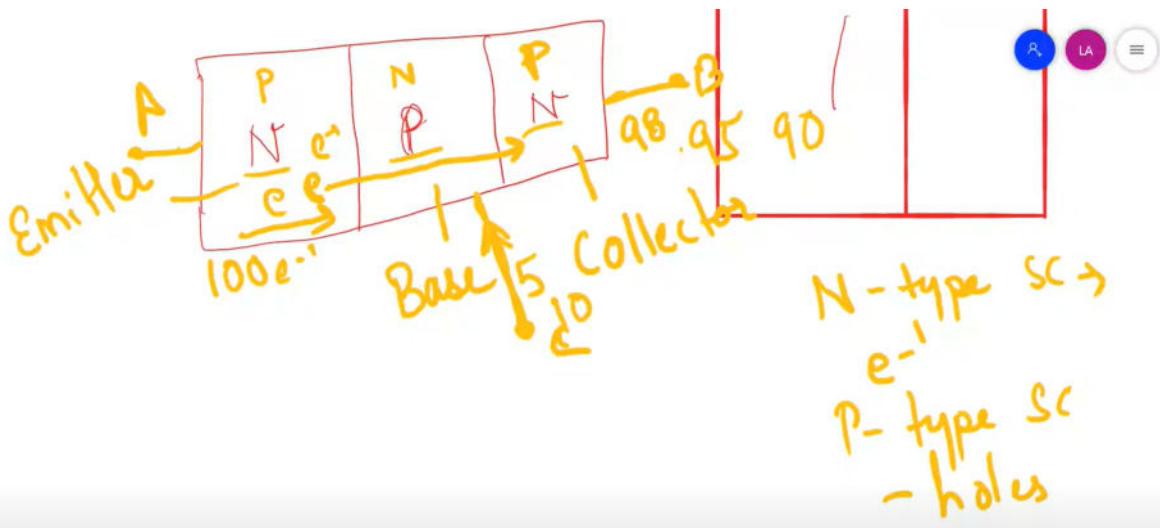





- 1) Emitter highly doped  $e^-$  p-type sc  
- holes
  - 2) Base lightly doped
  - 3) Area of base should be very small  
" collector " " high
  - 4)


$$F > C \times B \quad \frac{D_6}{\text{Area}}$$

$$C > E > B$$

~~$F = P/B$~~

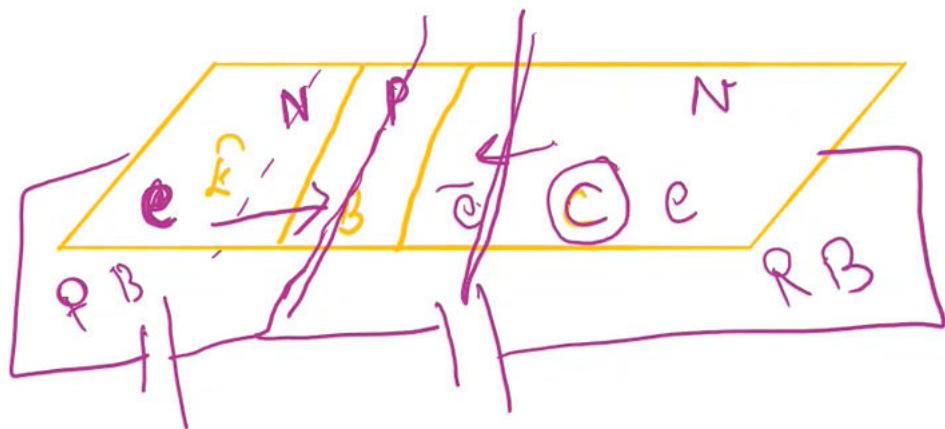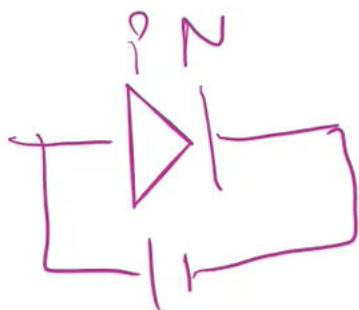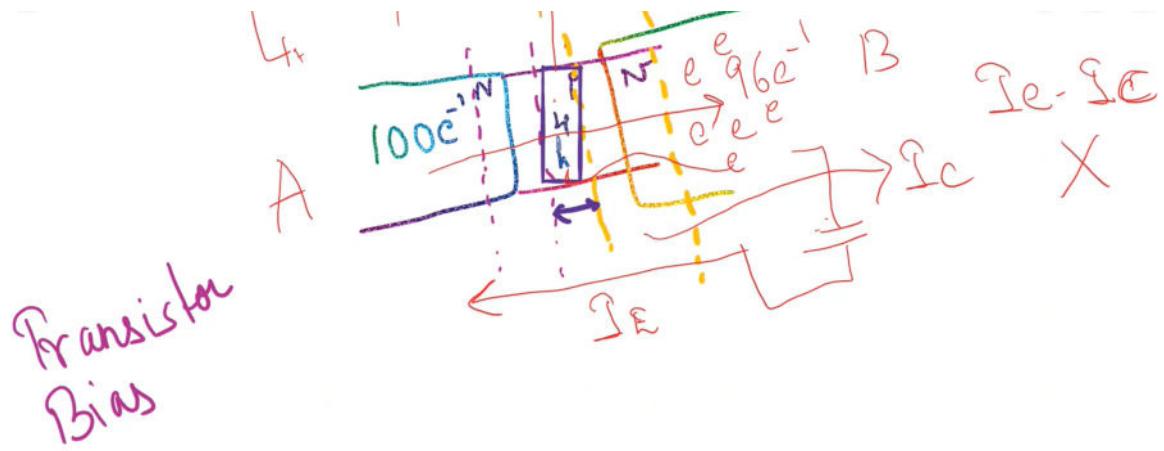

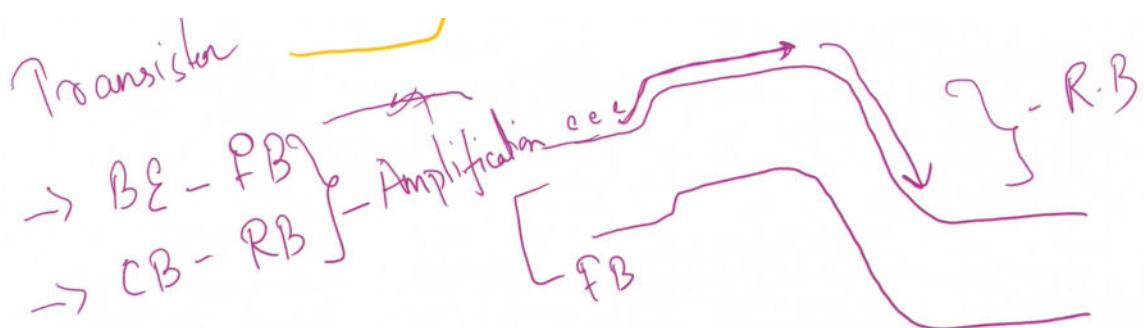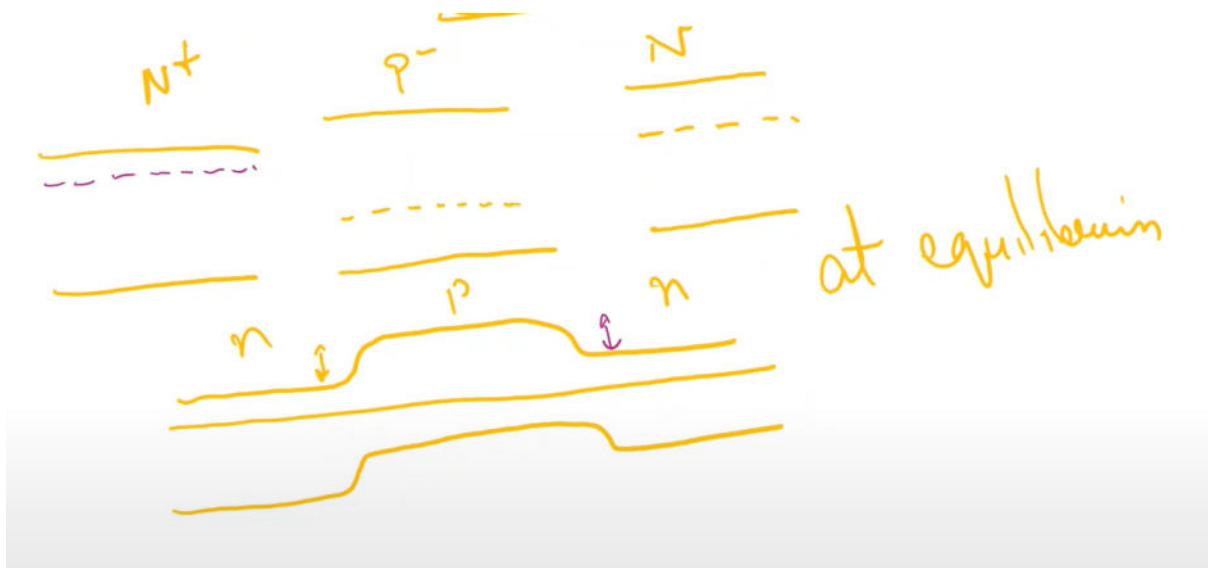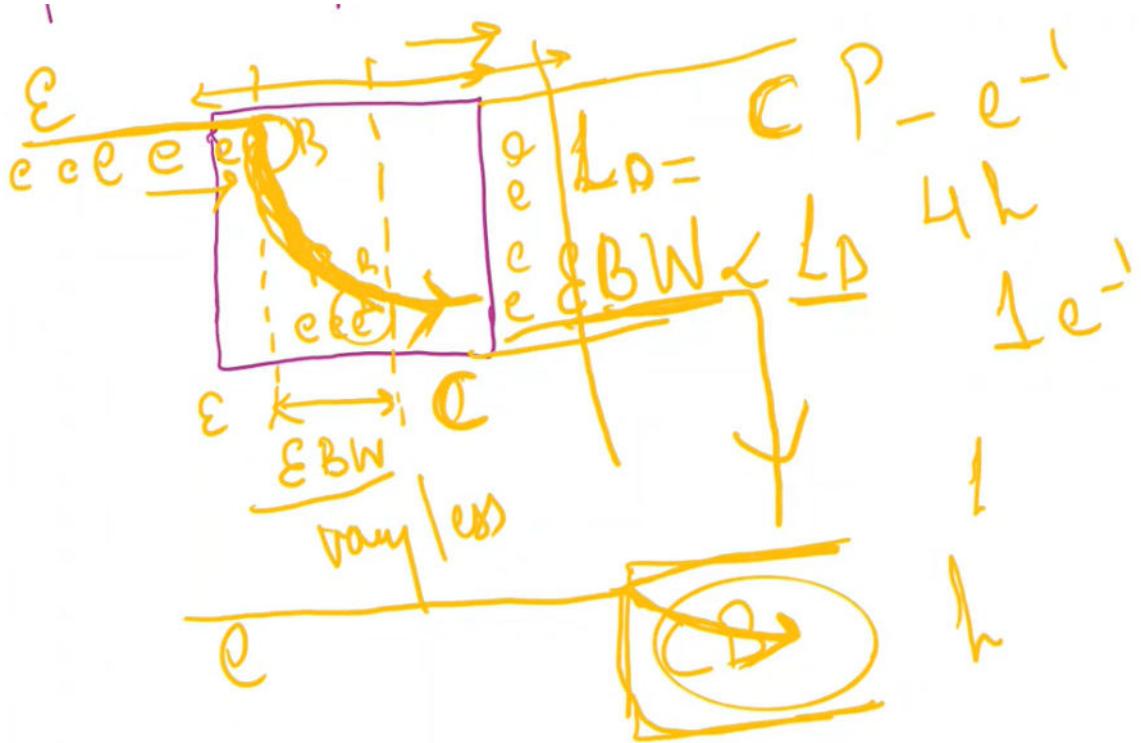

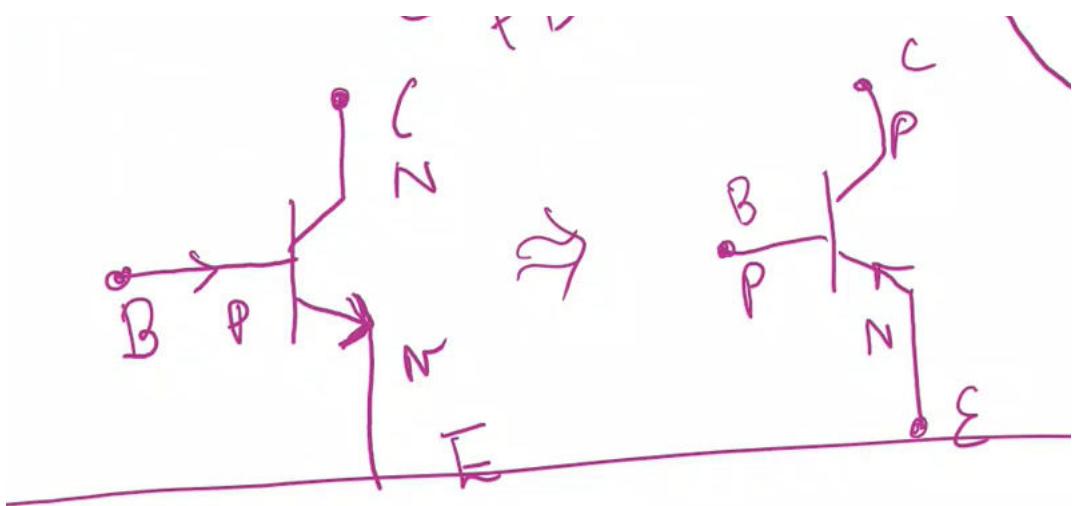



II)  $(F_B, f_B)$    
  $\hookrightarrow$  Closed switch   
  $\hookrightarrow$  Saturation Region   
  $I_{e-S}$   $R_A$   $I_A$

III)  $R_B, R_B \rightarrow$  open switch   
  $\hookrightarrow$  Cut-off Region

IV)  $R_B, f_B$    
  $\hookrightarrow$  Increase active Region

Current Component in a Transistor



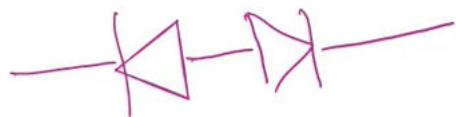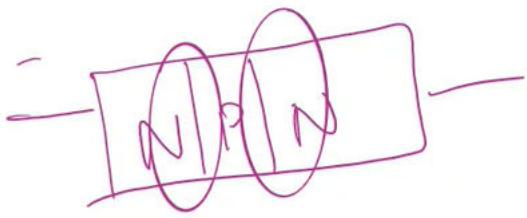

21.10.21

Current Components

$E_B - F_B$

$C_B - R_B$

$I_E = I_{ent} + I_{hn}$

$I_B = I_e$

$I_C = I_{ct} + I_{chot} + I_{ceo}$

$$= I_c + I_{ceo}$$

$$I_{CO} \propto V \cdot T$$

$$\cancel{I_{CO} = I_{CO,T_0} \left( 2 \frac{T_0 - T_1}{10} \right)}$$


$$I_{CO} = I_{CO} \left( e^{\frac{V_{CB}}{nV_T}} - 1 \right)$$

$$I_{CEO} = I_{CO} \Rightarrow I_{ch0} + I_{ce0}$$



- 1) Emitter Efficiency  $\Rightarrow \frac{I_{en}}{I_E} \uparrow \Rightarrow \frac{I_{en}}{I_{en} + I_{em}} \uparrow$
- 2) Base Transport factor  $\Rightarrow \frac{I_c}{I_{en}}$
- 3) Large Current Gain  $\alpha = \frac{I_c}{I_E}$

$I_{CO}$ -very small

$I_{CO}$ -very small

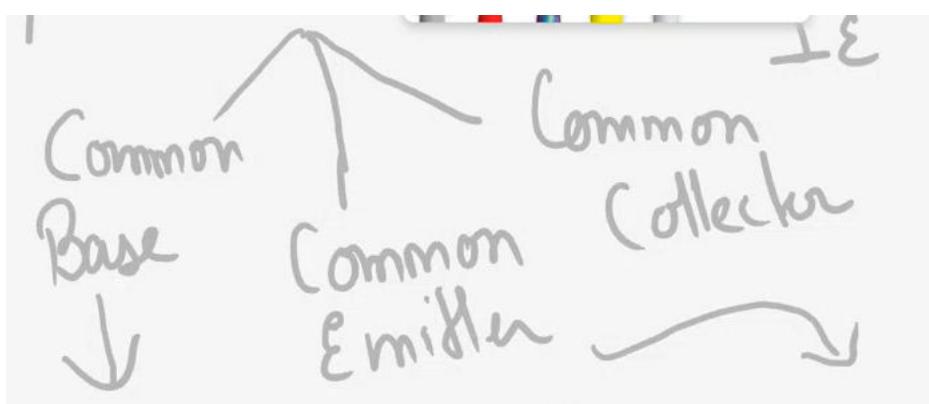

$$\alpha = \frac{I_c}{I_E}$$

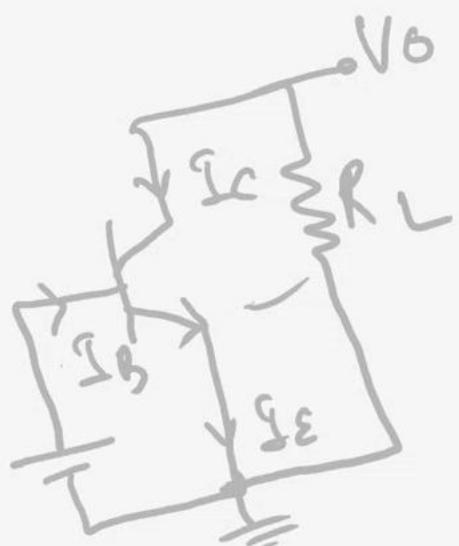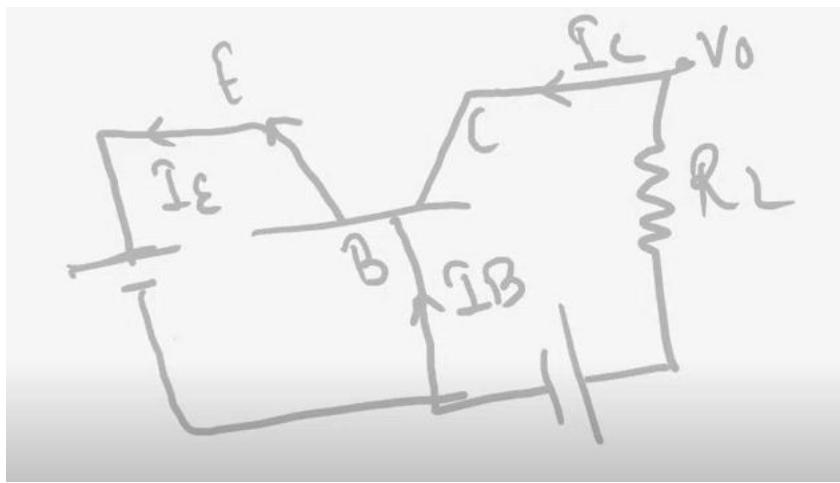

$$\beta = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C$$

$$I_C = I_C + I_{CO}$$

$$\alpha = \frac{I_C}{I_B + I_C} \Rightarrow \frac{\beta I_B}{I_B + \beta I_B}$$

$$= \frac{\beta (I_B)}{(1+\beta) I_B}$$

$$\alpha = \frac{\beta}{1+\beta}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$I_{CEO} = \frac{I_{CBO}}{1-\alpha}$$

1)  $\alpha$  (current am. factor)      Given  $I_{CO}$

$$\alpha = 0.988$$

$I_B = ?$      $I_E = 1.2 \text{ mA}$

$$\alpha = \frac{I_C}{I_E} = \hat{I}_C = \alpha \hat{I}_E$$

$$= 0.988 \times 1.2$$

$$= \underline{\underline{1.1856 \text{mA}}}$$

$$I_B = I_E - I_C$$

$$1.2 - 1.1856$$

$$= 0.0144 \text{mA}$$

Q)  $I_B = 45 \text{mA}$ ,  $I_C = 5.45 \text{mA}$

(i)  $\alpha, \beta, I_E$

(ii)  $I_B \rightarrow I_C = 10 \text{mA}$

\* For any term  $\alpha, \beta$  will be

Answer:

$$I_E = I_B + I_C$$

$$= 45 \mu + 5.45 = \underline{\underline{5.495 \text{mA}}}$$

$$\alpha = \frac{I_C}{I_E} = \frac{5.45}{5.495} = \underline{\underline{0.9918}}$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1-\alpha} = \frac{5.45 \times 10^3}{45 \times 10^{-6}} = \underline{\underline{121}}$$

$$I_B \Rightarrow I_C = 10 \text{ mA}$$

$$I_C = \beta I_B$$

$$I_B = \frac{I_C}{\beta} = \frac{10 \times 10^{-3}}{121}$$

$$= \underline{\underline{82.6 \mu A}}$$

3) In a CB,  $I_E = 1.6 \text{ mA}$   
 $I_{CEO} = 10 \text{ mA}$ ,  $I_C = ?$ ,  $\alpha = 0.98 \Rightarrow I_C = I_E + I_{CEO}$

$$I_C = 0.98 \times 1.6 + 10 \text{ mA}$$

$$= 1.57 \text{ mA}$$

4) In a CE,  $I_E = 5 \text{ mA}$ ,  $I_C = 4.95 \text{ mA}$   
 $I_{CEO} = 200 \mu \text{A}$ , find  $\beta$  &  $I_{CBO}$

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha}$$

$$\alpha, \beta \quad \beta = \frac{I_C}{I_B}, \alpha = \frac{I_C}{I_E}$$

$$I_{CBO} = (1 - \alpha) I_{CEO} \quad \beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{4.95}{5}$$

$$= (1 - 0.99) 200 \mu \text{A} \quad = \frac{0.99}{1 - 0.99} = \underline{\underline{99}} = \underline{\underline{0.99}}$$

$$= 2 \mu \text{A}$$

$$I_E = I_B + I_C$$


$$5 - 4.95 = I_B = 0.05 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = \frac{4.95}{0.05} = \underline{\underline{99}}$$


$$\alpha = \beta / (1 + \beta) = \frac{99}{1+99} = \underline{\underline{0.99}}$$

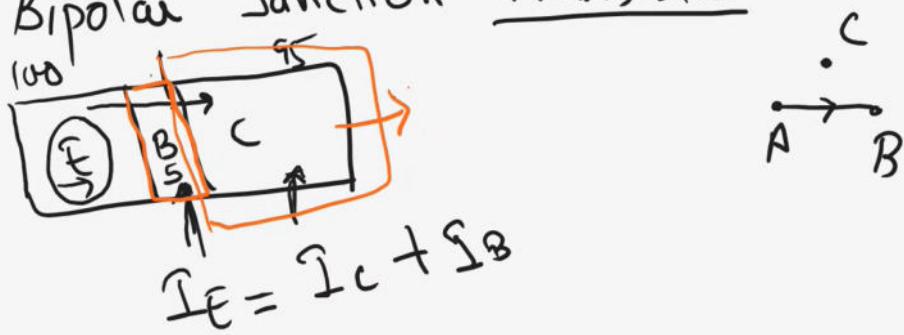18.11.21

BJT  $\rightarrow$  Bipolar Junction Transistor




Configuration of Tr:

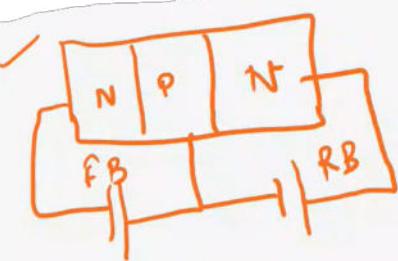

- \* Common Base
- # Common Emitter
- \*\* Common Collector

i) Common Base

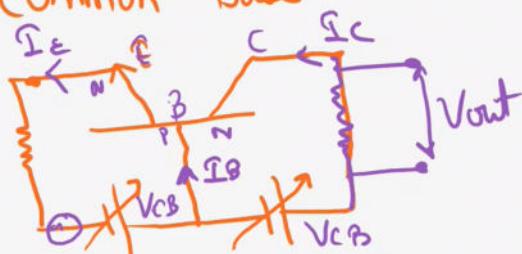

$$\frac{I_C}{I_E} = \alpha_{dc}, \alpha_{ac}$$

$$\text{Be } I_{CO} \quad \alpha_{dc} = \frac{I_C - I_{CO}}{I_E}$$

## \* Characteristic of CB Configuration

I/P      O/P  
I/P Current  $\uparrow$  wrt  
to i/p voltage


$I_{IC}$  vs  $V_{CB}$

for a given value of

$I_E$


-> o/p

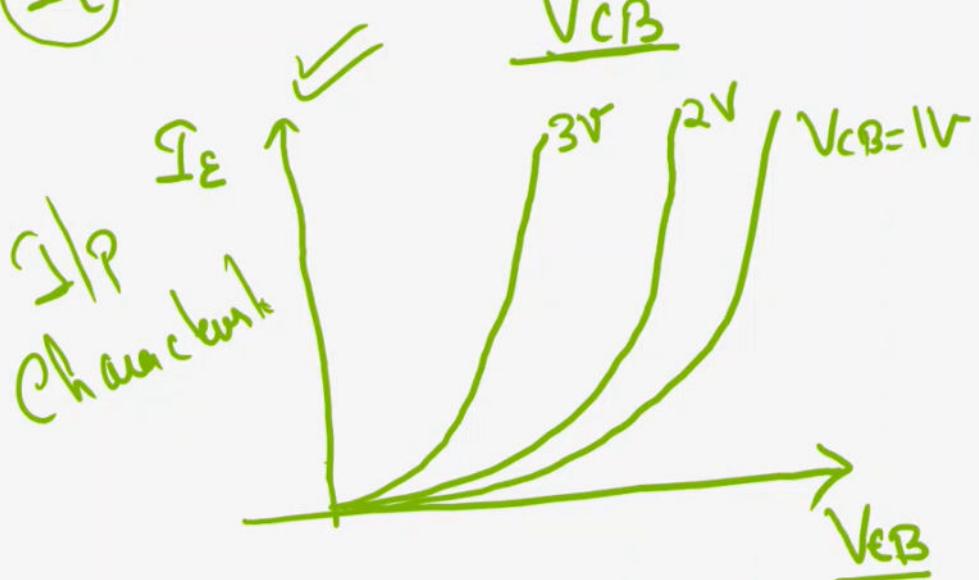①  $I_E = I_{C+I_B} \leftarrow I_E \text{ vs } V_{EB}$  for a given









resistance of B-E junction

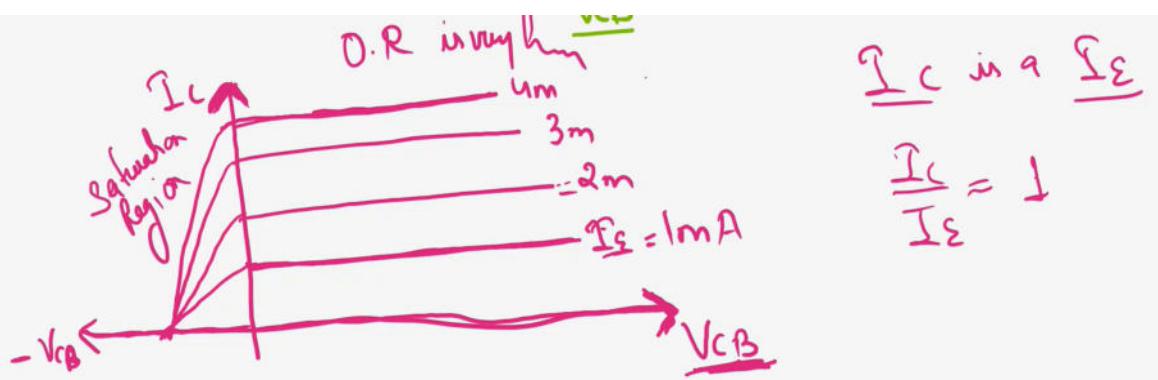

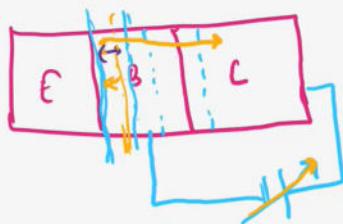i) Early effect or Base Width modulation effect



## 2) Common Emitter

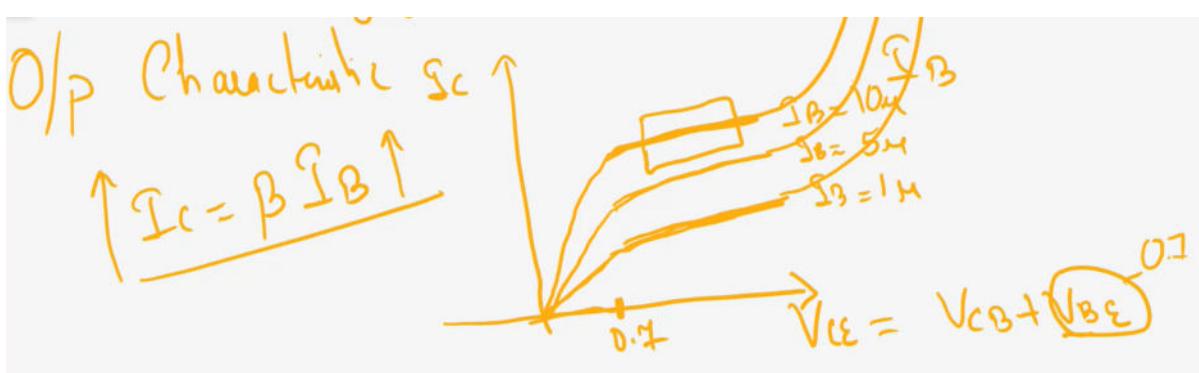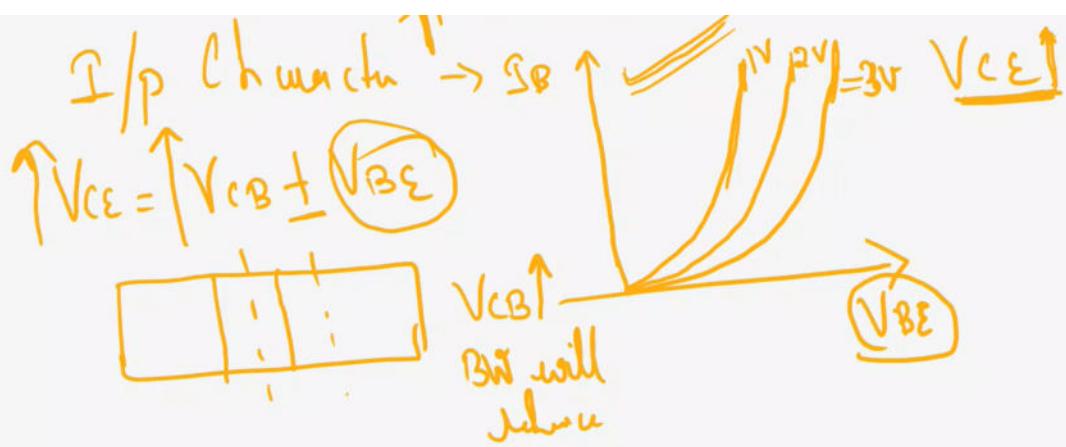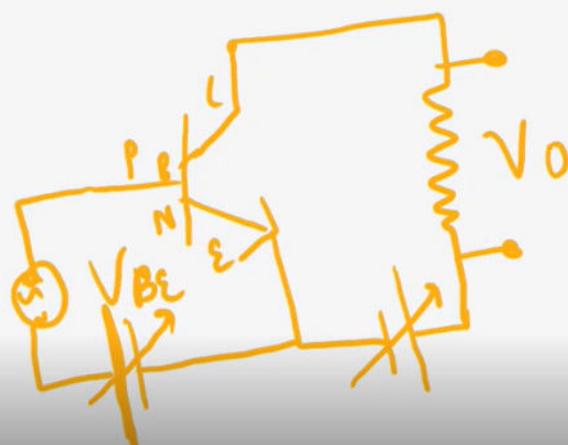

OR - high  
 $S_R$  - Medium  
 $C_G$  -  $\frac{S_C}{I_B}$  - very high  
 $V_G$  - moderation - Amplifier

$$I_C = \alpha I_B + I_{CBO}$$

$$I_C = \underbrace{\alpha I_E + I_{CBO}}_{\text{ampl. CB}} \quad E \text{ is open}$$

$$I_E = I_B + I_C$$

$$I_C = \alpha (I_B + I_C) + I_{CBO}$$

$$I_C(1-\alpha) = \alpha I_B + I_{CBO}$$

21.11.21

$$I_C = \frac{\alpha I_B}{1-\alpha} + \frac{I_{CBO}}{1-\alpha}$$

$$\therefore I_C = \beta I_B + (\beta+1) I_{CBO}$$

$$I_C = \beta I_B + I_{CEO}$$

$$\frac{\alpha}{1-\alpha} = \beta \Rightarrow \frac{1}{1-\alpha} = 1+\beta$$

2) Fin a nela  $\alpha, \beta$

$$I_{CBO}, I_{CEO}$$

$$I_C, I_{CEO}$$

$$1) V_{CC} = 10V \quad R_C = 1k \quad , V_{B-E} = 0.5V \quad \alpha = 0.98$$


$$V_{CE} \quad \& \quad I_B$$

$$V_{CE} = V_{CC} - I_C R_C \\ = 10 - 0.5V = \underline{\underline{9.5V}}$$

$$\beta I_B = I_C$$

$$I_C R_C = 0.5$$

$$I_C = 0.5 / 1k = 0.5 \text{ mA}$$

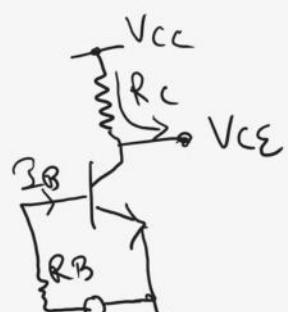

$$\alpha = 0.98 \quad \beta = \frac{0.98}{1-0.98} = 49$$

$$I_B = \frac{0.5}{49} \approx \underline{\underline{10.2 \mu A}}$$

- 2) 
- $I_C = 5mA$ ,  $I_B = 50\mu A$ ,  $I_{CBO} = 1\mu A$
- 1)  $\alpha, \beta, I_E$
  - 2) find  $I_B$  corresponding to  $I_C = 10mA$

$$\begin{aligned} \beta &= \frac{I_C - I_{CBO}}{I_B + I_{CBO}} = \frac{5 \times 10^{-3} - 1 \times 10^{-6}}{50 \times 10^{-6} + 1 \times 10^{-6}} \\ &\Rightarrow \frac{10^{-3}}{10^{-6}} \left[ \frac{1 - 10^{-3}}{51} \right] \\ &= 10^3 \left[ \frac{1}{51} \right] = 0.098 \\ &= 98\% \end{aligned}$$

$$\alpha = \frac{\beta}{\beta+1} = \frac{98}{99} = 0.99 \approx 1.0$$

$$I_E = I_B + I_C = (5 + 5 \times 10^{-3}) \text{ mA}$$

5.05 mA

$$I_C = (\beta I_B + (1+\beta) I_{CBO})$$




$$I_B = \frac{I_C - (1+\beta) I_{CBO}}{\beta}$$


$$= 101 \text{ mA}$$

BJT



- ↳ noisy ✓
- ↳ large area
- low gain
- high Power dissipation
- high leakage current
- switching activity
- low

FET- field effect transistor

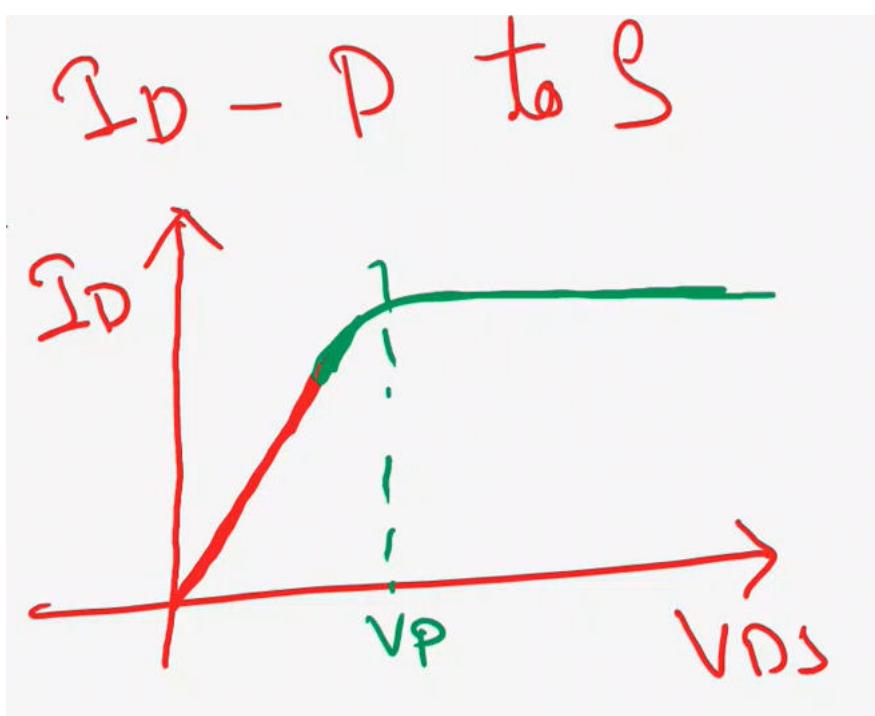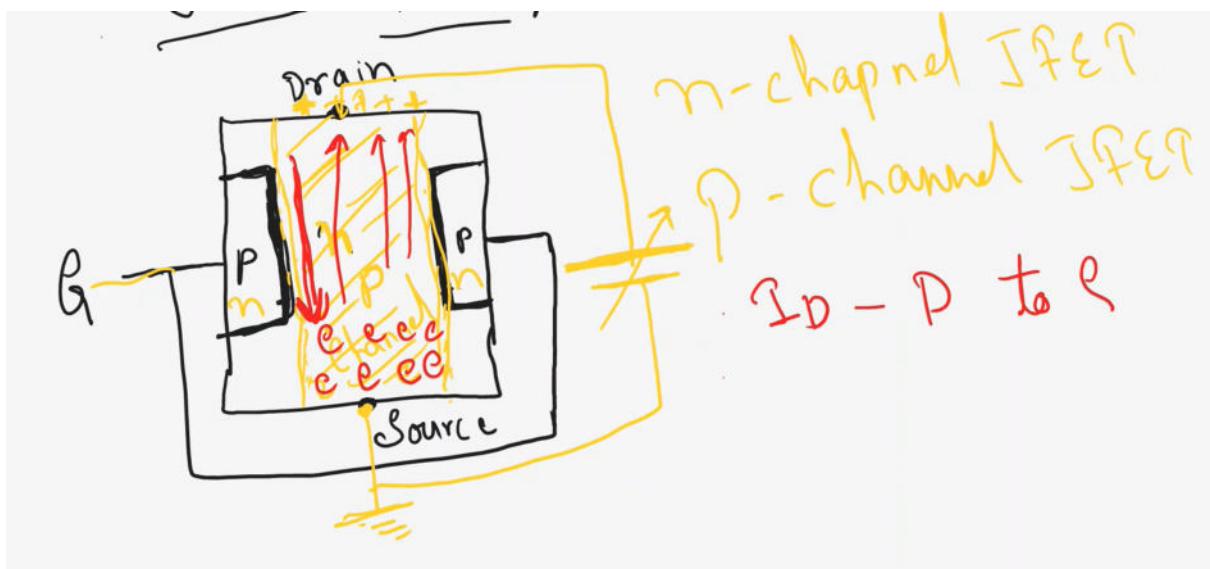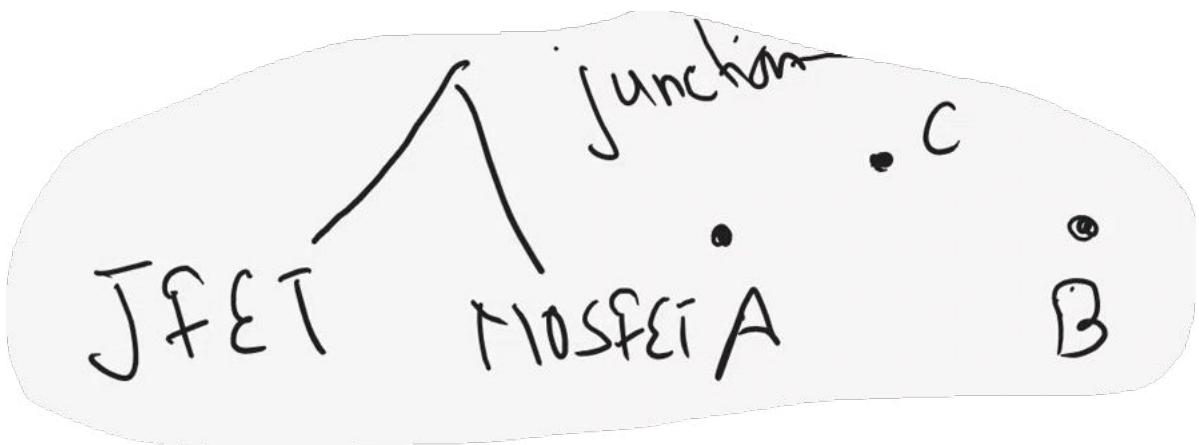

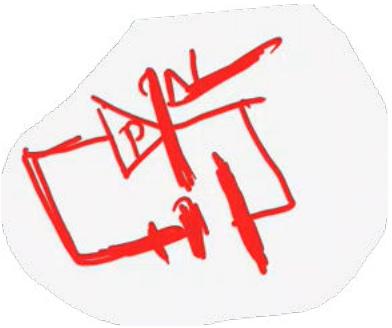


22.11.21

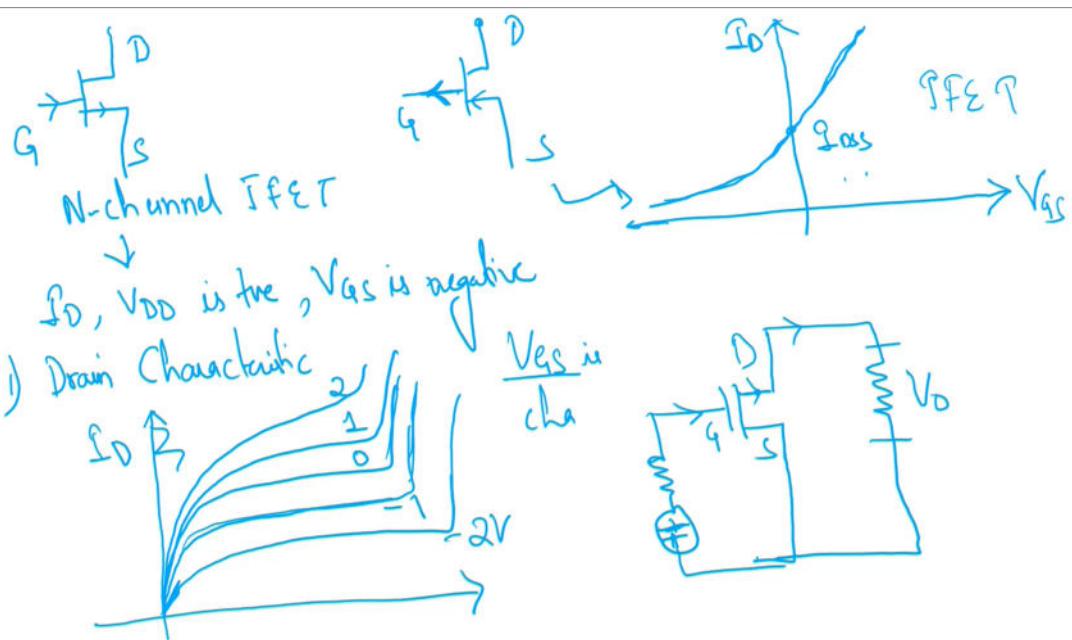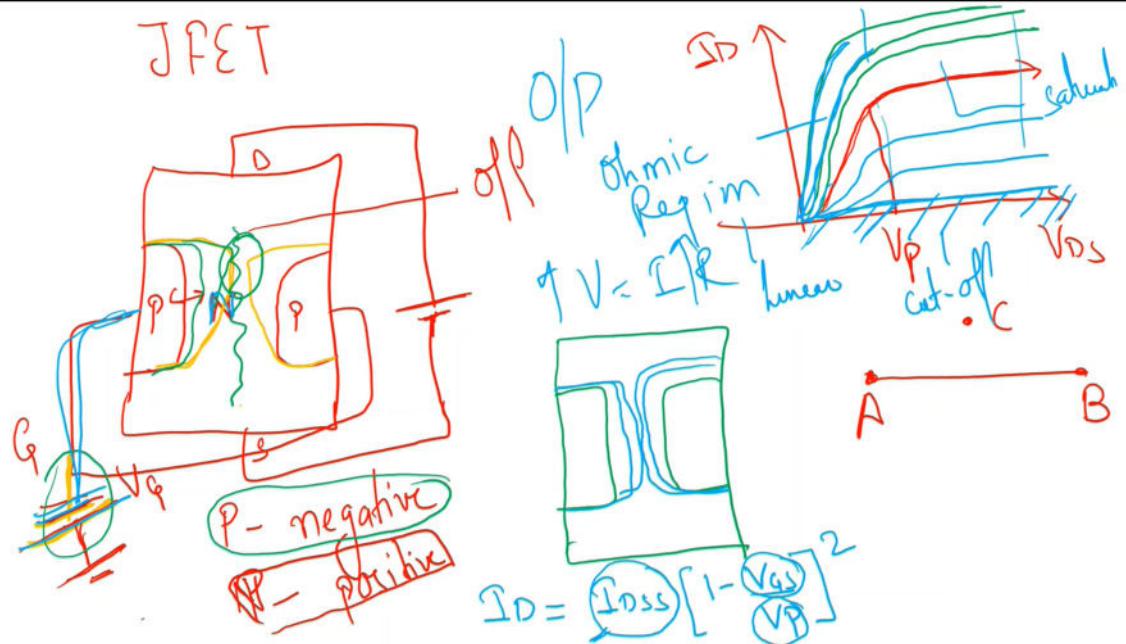

$V_{DS}$  NFEF to pinch off condition
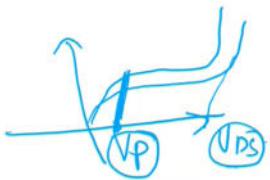
$$\beta = \frac{I_D}{I_S} \quad V_{GS} = 1V, \quad V_P = -2V, \quad I_{DSS} = 10mA, \quad I_D$$



$$V_P = V_{DS} = -2V \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$V_{GS} \rightarrow I_D$  Transconductance  $\frac{\partial I_D}{\partial V_{GS}}$

$$\frac{\partial I_D}{\partial V_{GS}} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{\partial I_D}{\partial V_{GS}} = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P}\right) \quad g_{m0} = \frac{2I_{DSS}}{V_P}$$

$$= 10 \left(1 + \frac{1}{2}\right)^2$$

$$10 \times \frac{3}{2} \times \frac{3}{2} = \frac{45}{2} = \underline{22.5mA}$$

Amplification factor

$$M = \frac{\Delta V_{DS}}{\Delta V_{GS}} = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{\Delta V_{DS}}{\Delta V_{GS}} \Rightarrow g_m \times r_a$$

$V_P = -4.5V, \quad I_{DSS} = 9mA, \quad I_{DS} = 3mA, \quad (g_m) \text{ at } I_{DS} = 3mA$

$V_{GS} = ?$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \Rightarrow V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$= -1.902V$$

$$g_m = -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \underline{2.31mA/V \text{ or } mS}$$

I ab Mosfet C/E amp (4) MOSFET JFET

25.11.21

←





P N



MOSFET



Metal

Oxide

Semiconductor

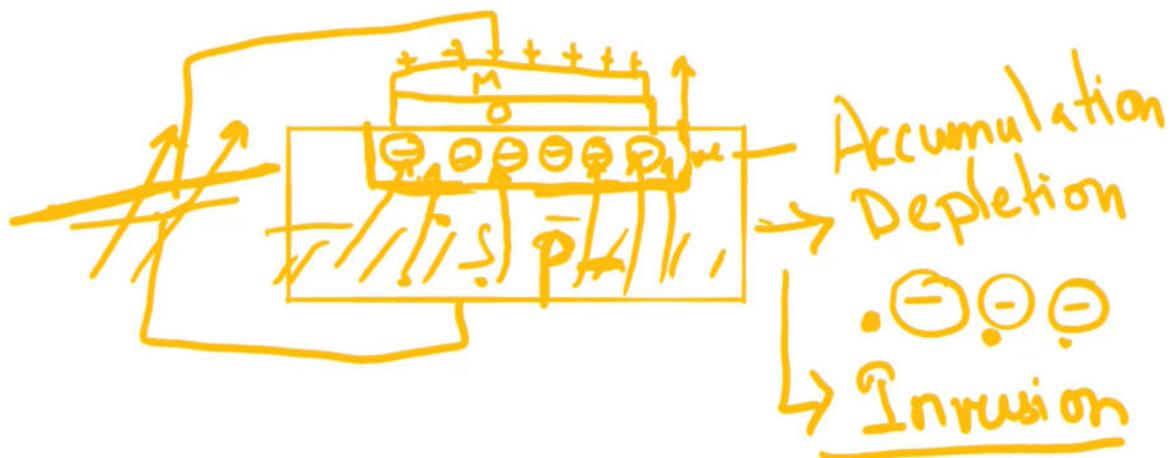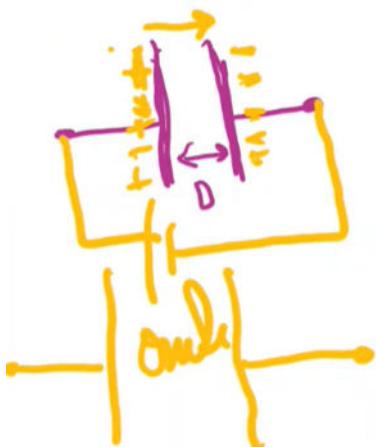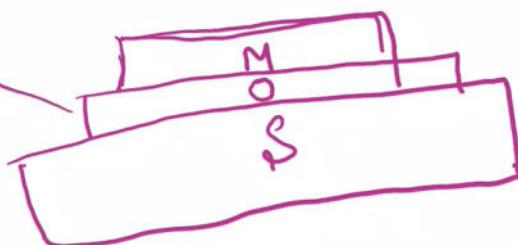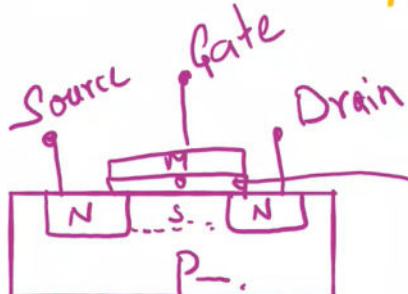

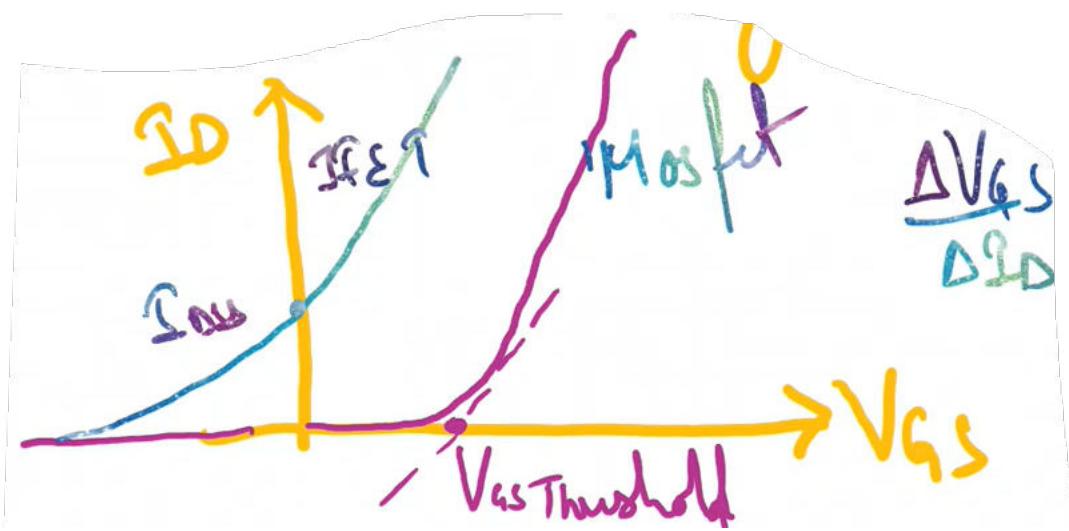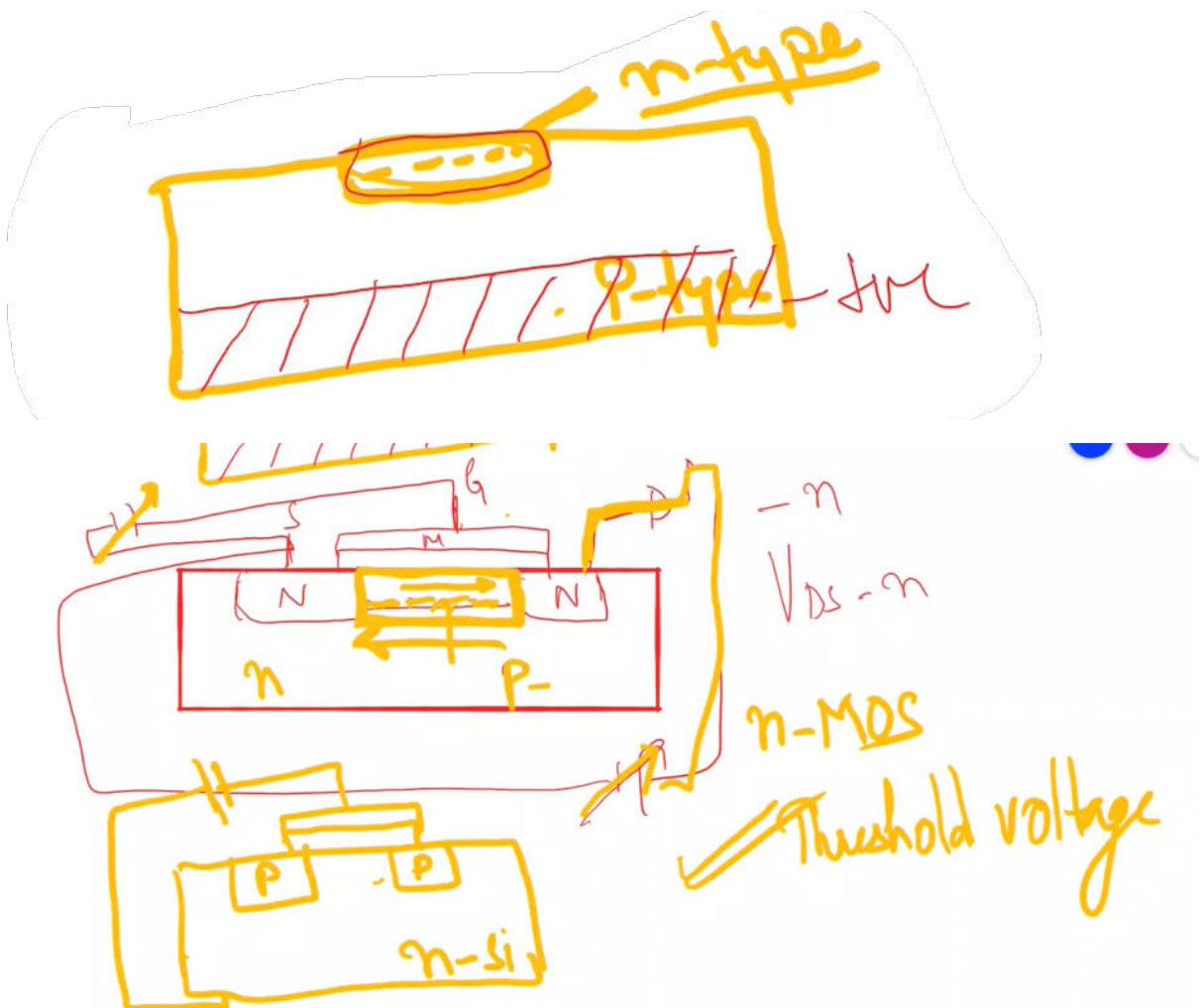

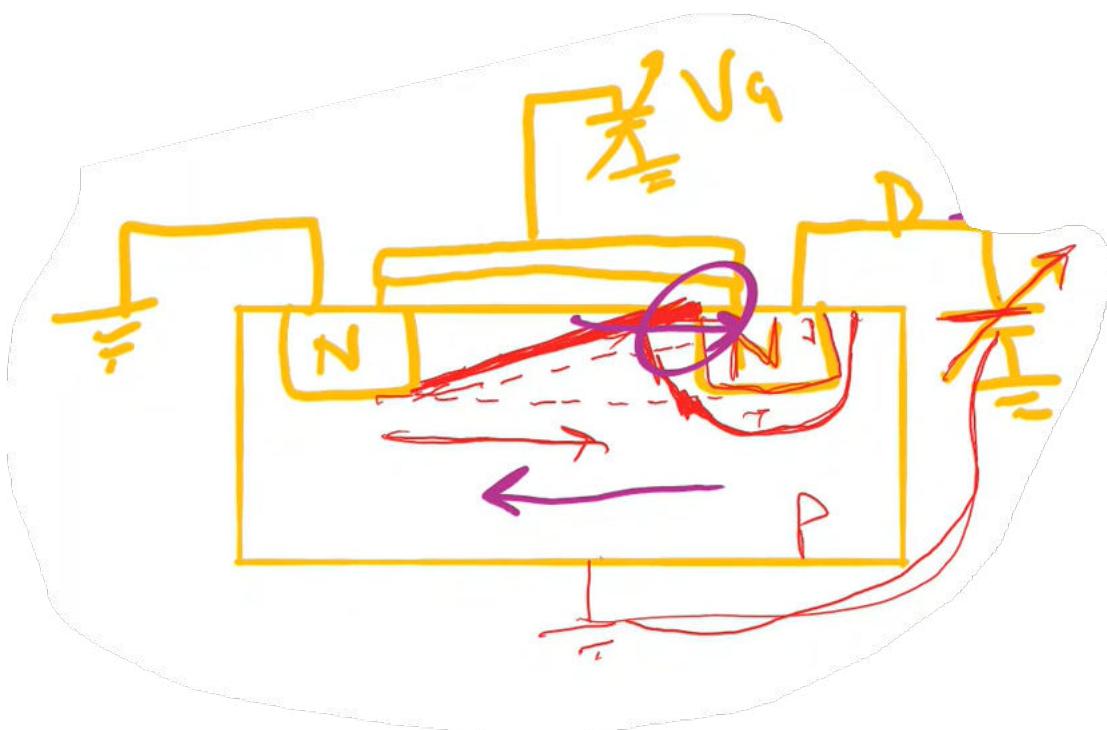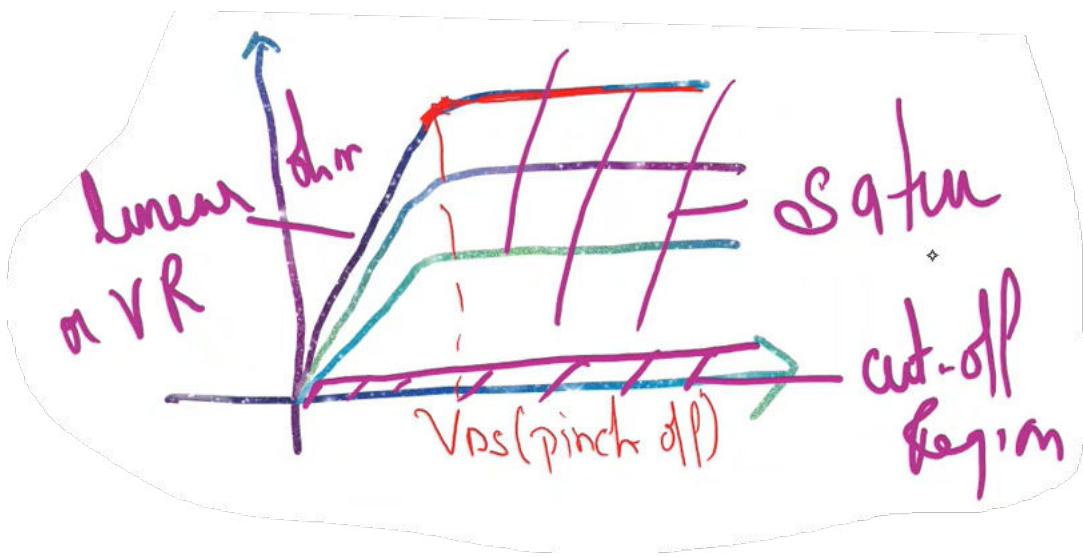

$$I_D = K'n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


- linear Region  
- ohmic Region

$$I_D = K'n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 \rightarrow \text{Saturation Region}$$

$$\boxed{V_{DS} \geq V_{GS} - V_{th}} \rightarrow \text{Saturation Region}$$

Enhancement type Mosfet

Depletion type Mosfet

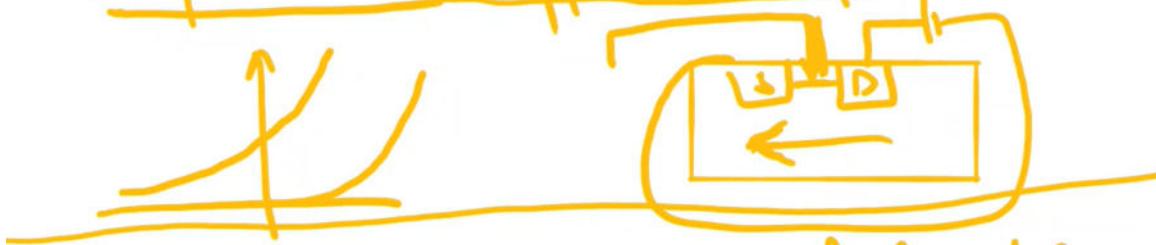


Voltage Controlled Current Source



$\alpha$  or  $\beta$



$$g_m = \text{transconductance} = \frac{\partial I_D}{\partial V_{GS}}$$


29.11.21

Module 4: Transistor as an amplifier

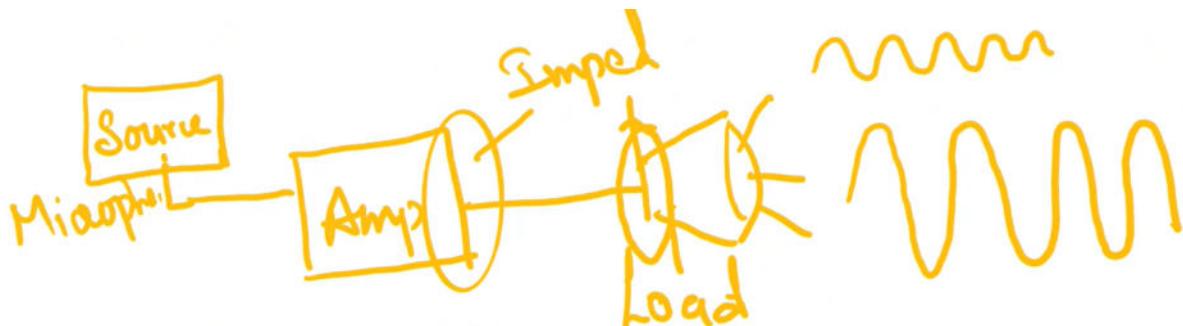

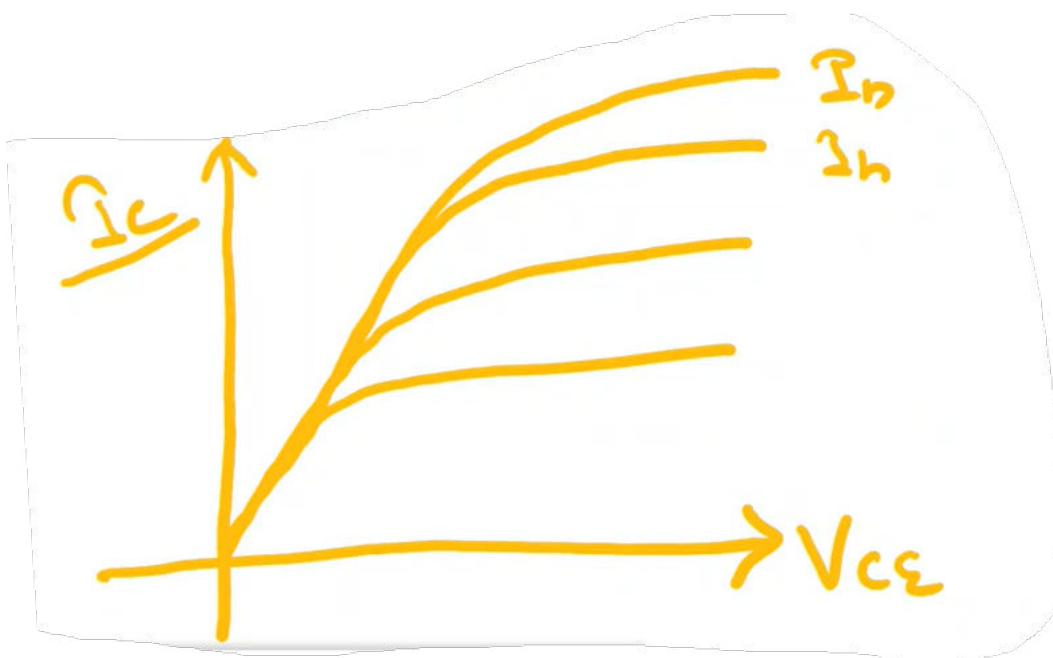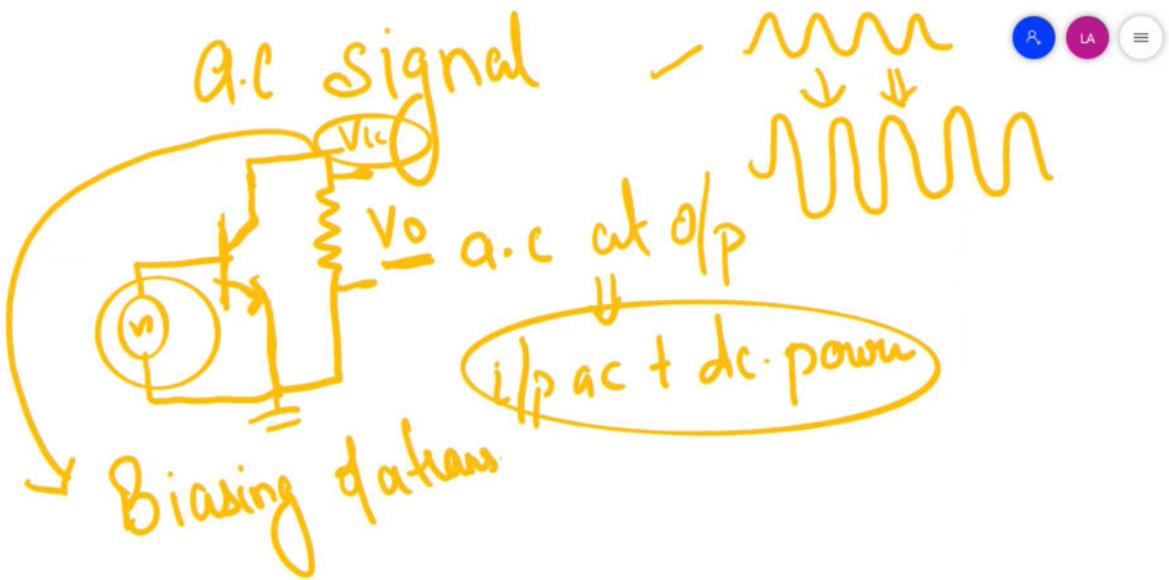

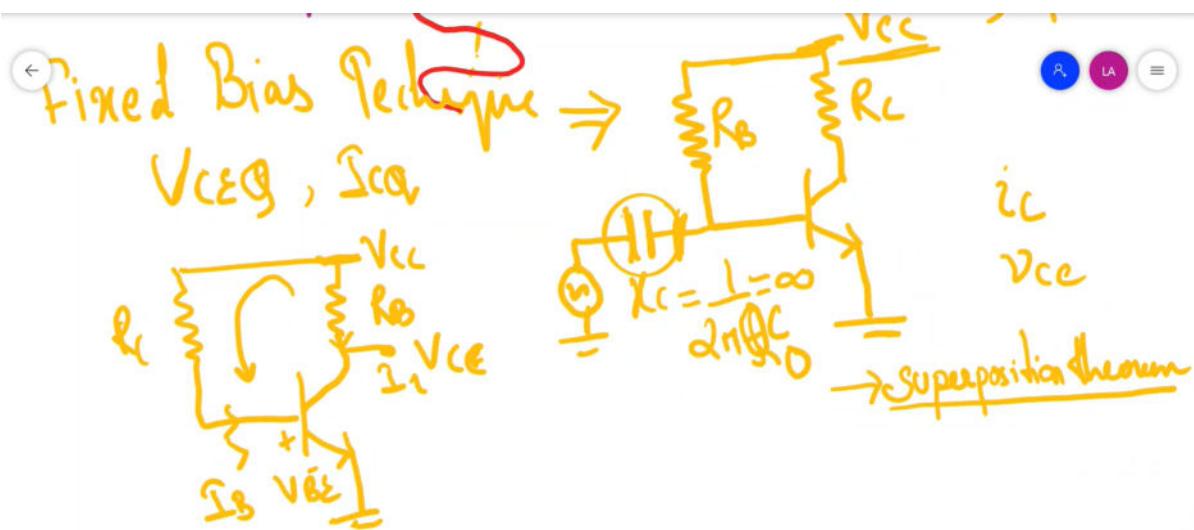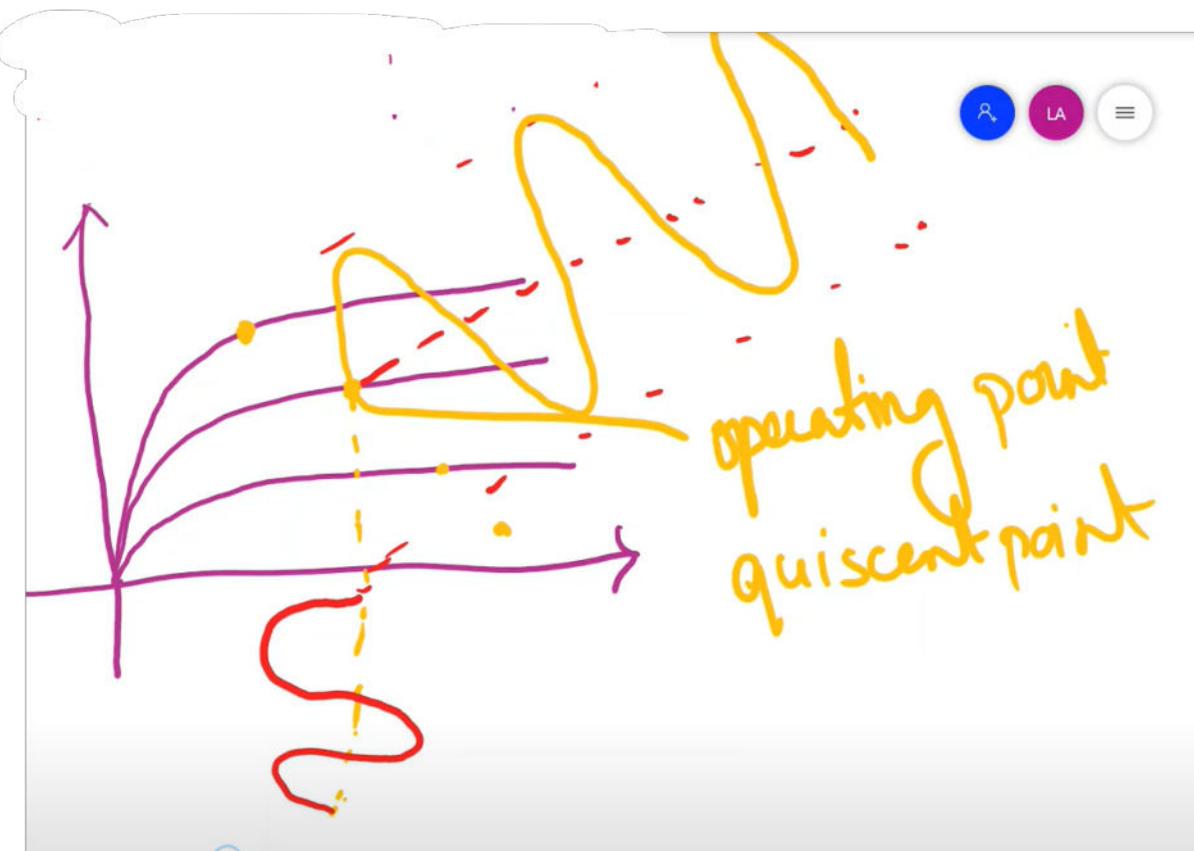

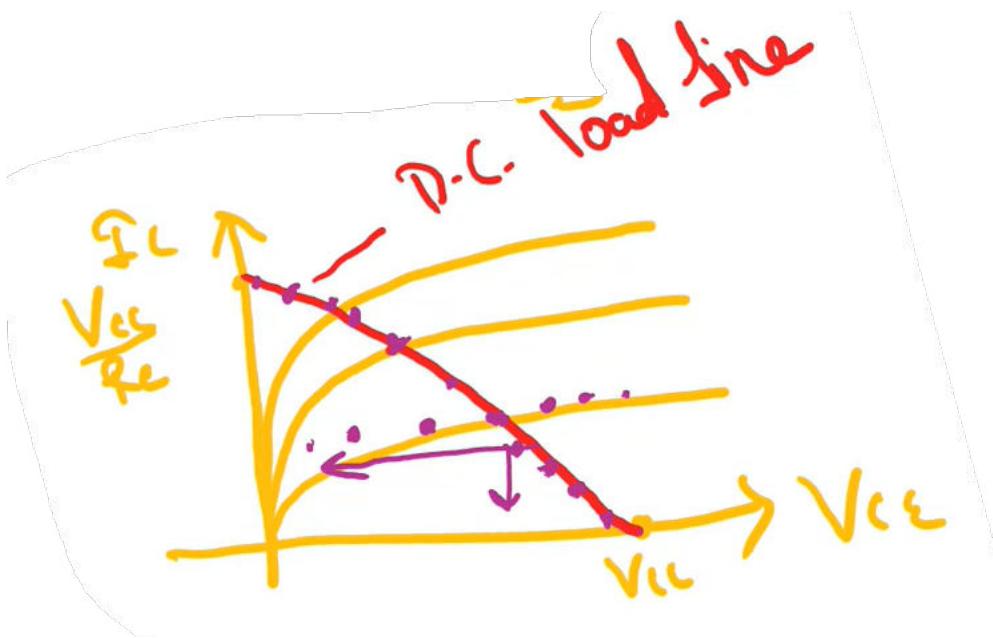

$$V_{CE} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


$$I_C = \beta I_B$$

$$V_{CE} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = \left( \frac{V_{CC}}{2} \right)$$

Stability:

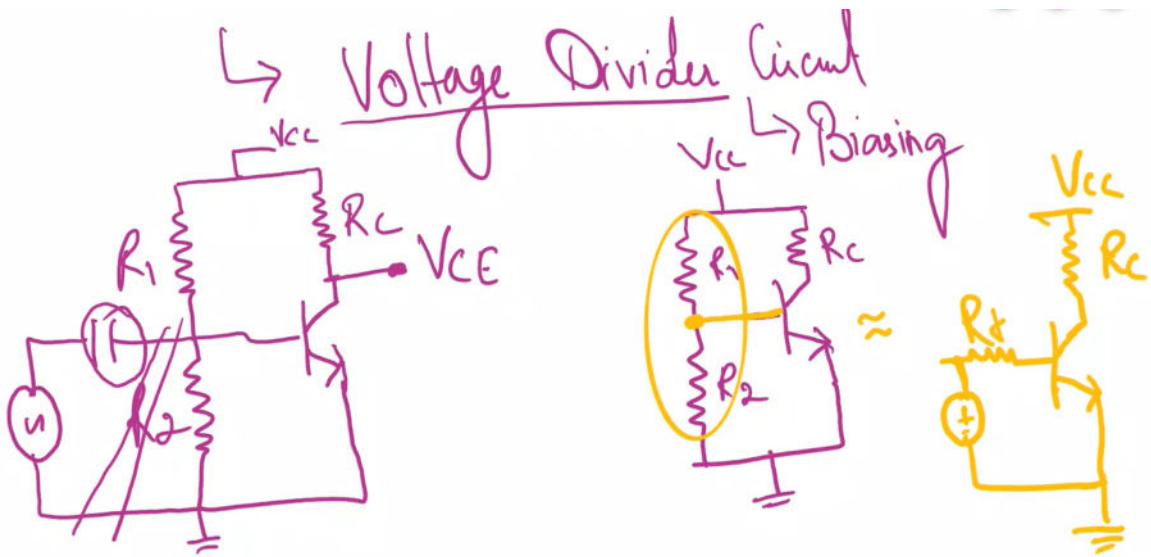

$$R_{th} = R_1 \parallel R_2$$

$$V_{th} = \frac{V_B \times R_2}{R_1 + R_2}$$

Q-point  
 $V_{CE}, I_C$

~~$$V_{th} = I_B R_{th} + V_{BE}$$~~

$$\frac{V_{th} - V_{BE}}{R_{th}} = I_B$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{th} = I_B R_h + V_{BE} + \underline{I_E R_E}$$

$$V_{th} - V_{BE} = I_B R_h + (I_B + I_C) \underbrace{R_E}_{\beta I_B}$$

$$V_{th} - V_{BE} = I_B R_h + I_B (\beta + 1) R_E$$

$$I_B = \frac{V_{th} - V_{BE}}{R_h + (\beta + 1) R_E}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} + I_C R_C + I_E R_E$$


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

~~Voltage Divider with emitter resistance~~

2.12.21 - class cancelled due to internet problems


3.12.21

a.c. analysis of transistor

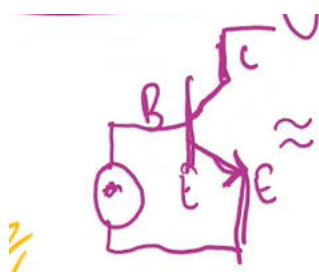

Operating

$$V_{CE} \approx \frac{V_{CC}}{2}$$

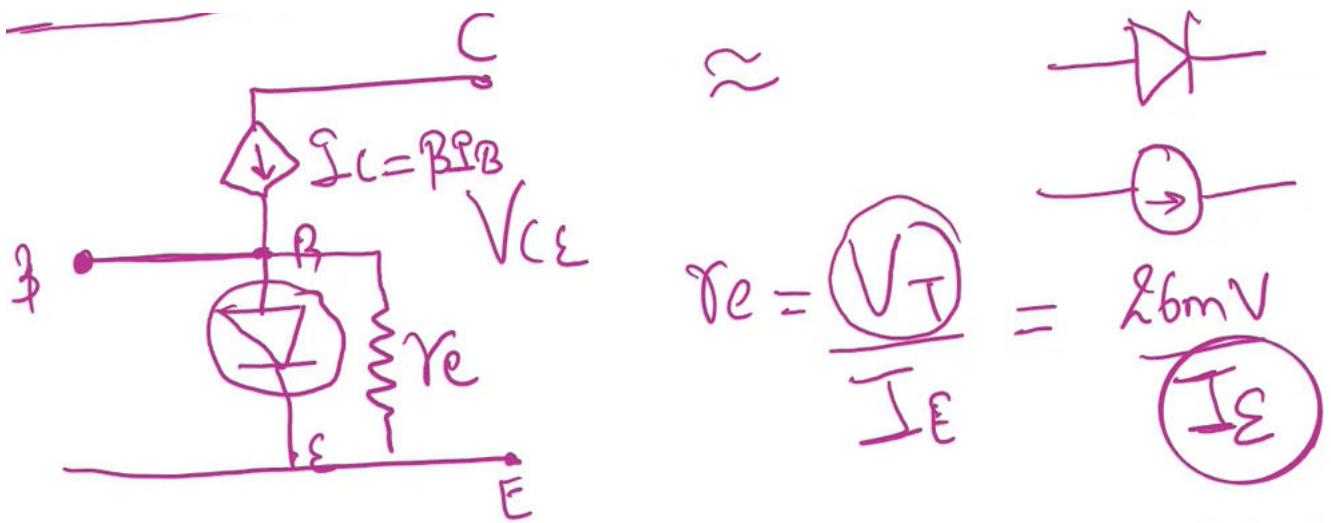



$$Z_i = \frac{V_i}{I_i} = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I}$$

$$I_c = I_c + I_b \Rightarrow \beta I_b + I_b = I_b (\beta + 1)$$

$$(Z_i = (\beta + 1) r_e)$$
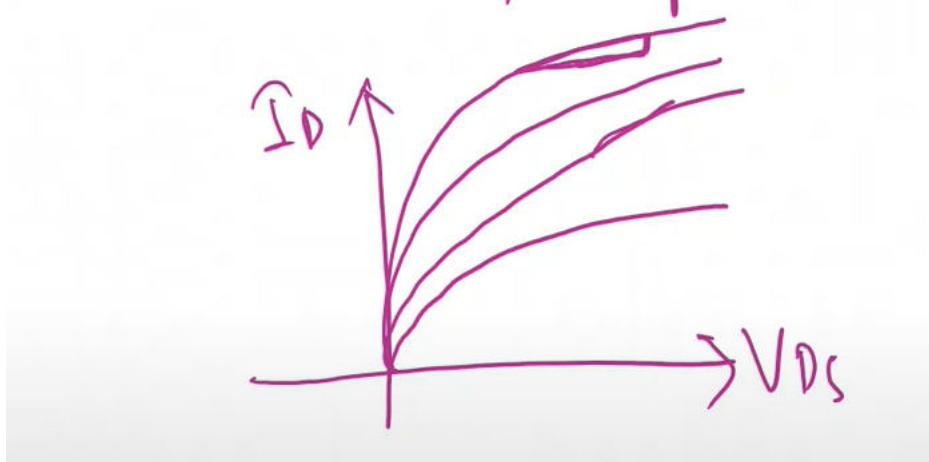
$$Z_o \approx r_o \Rightarrow \text{slope}$$




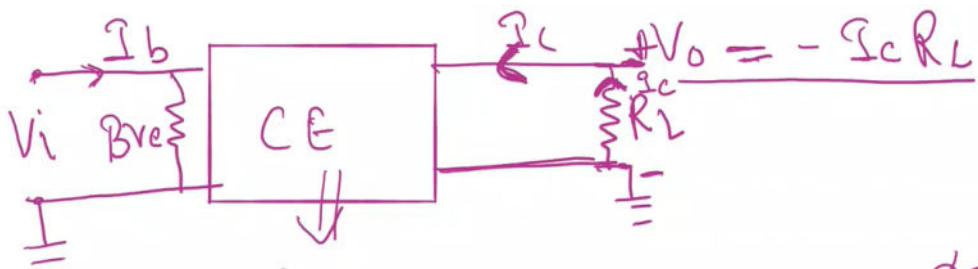

$$A \Rightarrow \frac{V_0}{V_i} = -\frac{I_c R_L}{I_i Z_i} = -\frac{\beta R_L}{\beta_b \beta_{re}}$$

$$A = -\frac{R_L}{r_e}$$
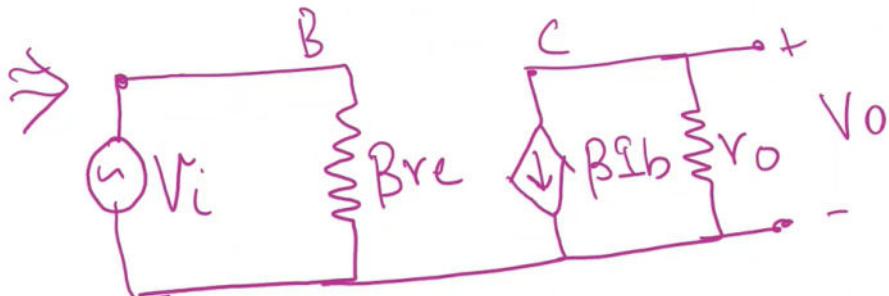
$$A = -\frac{R_L}{r_e} = -\frac{h_{ie} r_e}{V_T} = \frac{V_T}{I_e}$$



A0-equivalent re model of CE amp

$$\textcircled{1} \quad \beta = 120, \quad I_e = 3.2 \text{ mA} \quad r_o = \infty$$

$$1) \quad Z_i$$

$$2) \quad \underline{A_V} \text{ if a load of } 2k\Omega \text{ is applied}$$

$$3) \quad \underline{G_a} \text{ or } A_i$$

$$r_e = \frac{V_T}{I_E} = \frac{26mV}{3.2\mu A} = \underline{\underline{8 \cdot 125 \Omega}}$$

1.2)


$$A_V = -\frac{R_L}{r_e} = -\frac{2000}{8.125} =$$

$$A_V = -246.15$$

1.3)

$$A_i = \frac{I_O}{I_i} = \boxed{\frac{I_C}{I_B} \approx \beta} \approx \underline{\underline{120}}$$

2) R-C coupled CE amplifier

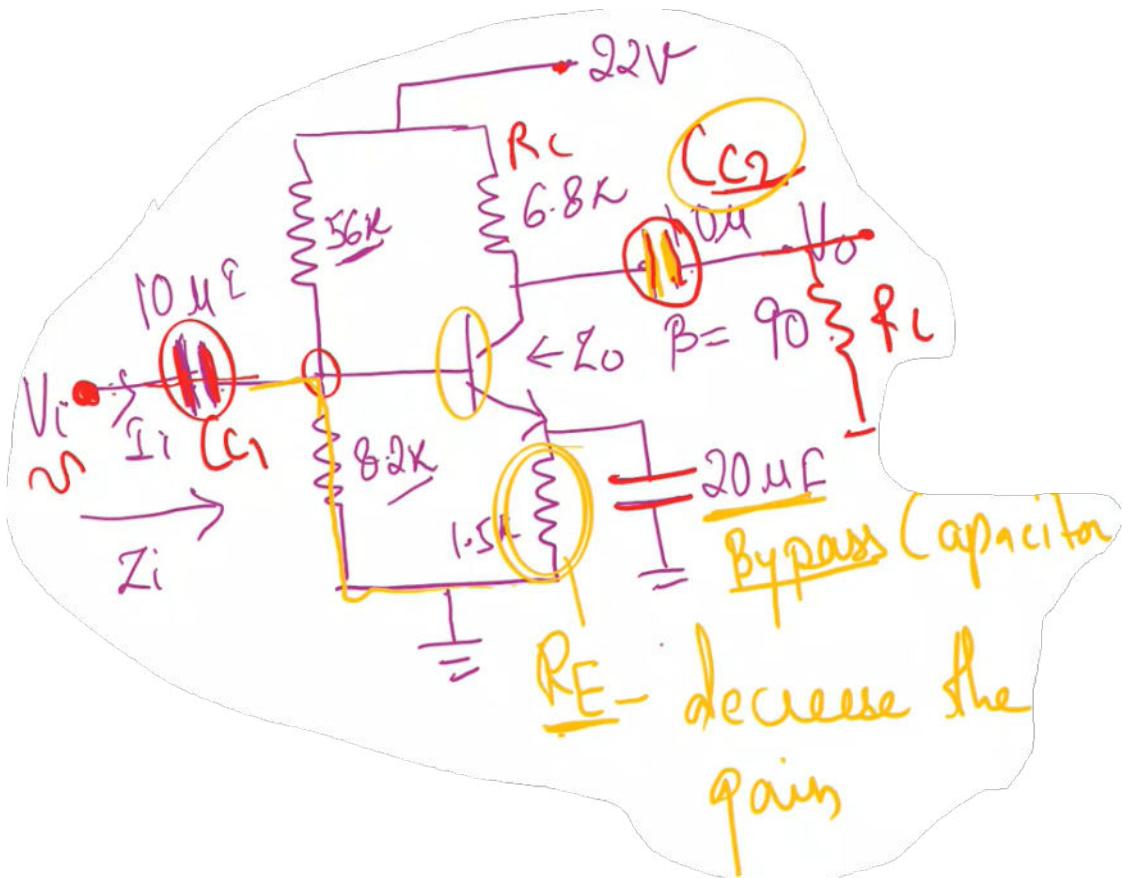


$$A_V = -\frac{R_L}{r_e}$$

$$= -\frac{R_L R_C}{r_{e\parallel} + R_E}$$

C - DC - Open circuit  
 $X_{L\parallel} = \frac{1}{2\pi f C} \approx 0$   
 $X_C = \frac{1}{2\pi f C} \approx 0$

- 1)  $r_e$
- 2)  $Z_i$
- 3)  $Z_0 \quad (r_o = \infty)$
- 4)  $A_v \quad (r_o = \infty)$

$$r_e = \frac{V_T}{I_E}$$

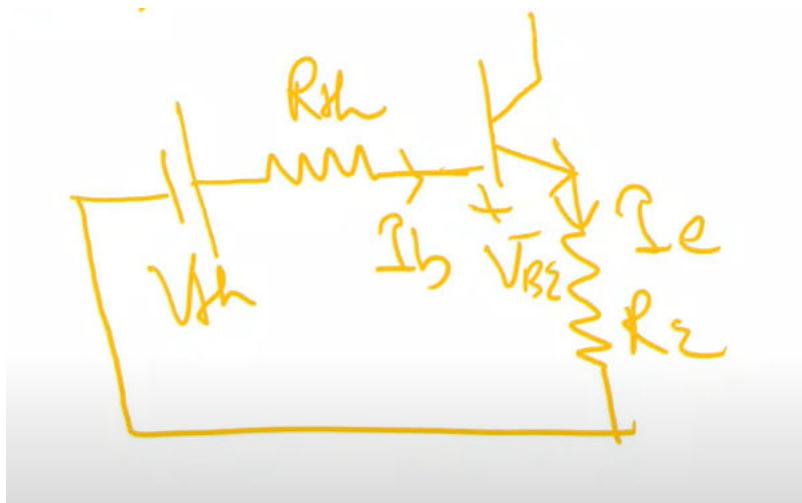

$$V_{th} = I_b R_h + V_{be} + q_e r_e$$

$$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2}$$

$$R_{th} = R_1 \parallel R_2$$

$R_{th} = R_1 \parallel R_2 =$

$$V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE}$$

$$V_E = 2.8 - 0.7 = 2.1 \text{ V}$$

$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2}$

$R_{th} = R_1 \parallel R_2$

$I_b$

$$V_E = I_E R_E = \frac{2.1}{1.5} = 1.41 \text{ mA}$$

$$I_C = \frac{V_T}{1.41} = \frac{26}{1.41} = 18.44$$

$$Z_i = R_1 \parallel R_2 \parallel \beta R_E$$

$$= 56 \parallel 8.2 \parallel 90 \times 18.44$$

$$Z_i = \frac{R_1 R_2 R_E}{R_1 + R_2 + R_E}$$

$$Z_o = R_C = 6.8 \text{ k}\Omega$$

$$R_C \parallel R_L$$

$$A_v = - \frac{R_f}{r_e} \approx - \frac{6.8K}{18.44} = - \underline{\underline{368.96}}$$


## OSCILLATOR

### INTRODUCTION

- convert dc energy to ac energy at a very high frequency.
- If the feedback signal is **large enough and has correct phase**, there will be an output signal even though there is **no external input signal**.
- The criterion is that the **signal fed back to the input of the amplifier** must be **In phase**. In-phase feedback is also called **positive feedback**, or regenerative feedback.
- It is an **unstable amplifier**.
  
- Electronic oscillators are divided into:
  - **Sinusoidal** (or **harmonic**) oscillators-which produce an output having sine waveform
  - **Non-sinusoidal** (or **relaxation**) oscillator-the output is square, rectangular or saw-tooth or pulse shape.
- Oscillators are widely applied in many digital devices, Signal generator, Touch-tone telephone, musical instrument and radio/television transmitter and etc.
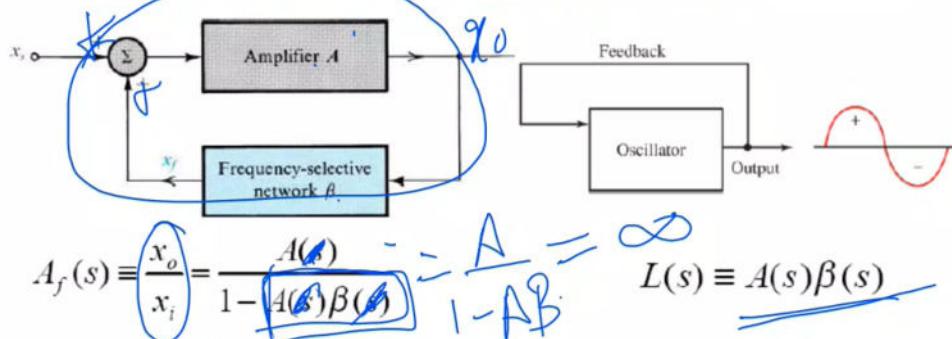
## The Oscillator Feedback Loop

A basic structure of a sinusoidal oscillator consists of an amplifier and a frequency-selective network connected in a positive-feedback loop.



The condition for the feedback loop to provide sinusoidal oscillations of frequency  $\omega_0$  is

$$L(j\omega_0) \equiv A(j\omega_0)\beta(j\omega_0) = 1 \quad AB = 1$$

*Barkhausen Criterion:*

- ① At  $\omega_0$  the phase of the loop gain should be zero.
- ② At  $\omega_0$  the magnitude of the loop gain should be unity.

**Barkhausen criterion :**

for oscillation

$$AB > 1$$

- The feedback factor or loop gain . The gain is infinite, this represent the condition for oscillation.
- The net phase shift around the loop  $0^\circ$  (or an integral multiple of  $360^\circ$ ). In other word, feedback should be positive.
- The amplifier gain must be greater than the loss in the feedback path.

## OSCILLATOR CONDITION

1)  $A\beta > 1$   
2)  $P_{BS} > 0.95\%$

- $A\beta$  less than 1

$A\beta V_{in}$  is less than  $V_{in}$  the output signal will die out  
**(Damped Oscillation).**

- $A\beta$  greater than 1

$A\beta V_{in}$  is greater than  $V_{in}$  the output signal will build up.

- $A\beta$  equal to 1

$A\beta V_{in}$  is equal to  $V_{in}$  the output signal will steady,  
**Undamped Oscillations (Stable oscillator).**

## HARTLEY OSCILLATOR



- The configuration of the transistor amplifier is of a Common emitter amplifier with the output signal 180° out of phase with regards to the input signal
- These two inductances form an autotransformer action and gives the feedback with a phase reversal of 180°, thus the total phase shift becomes 360° to give the feedback positive or regenerative feedback.
- A Hartley oscillator uses an inductive (single tapped-coil) of L<sub>1</sub> and L<sub>2</sub>. Voltage divider to determine the feedback ratio.  
$$\beta = \frac{L_2}{L_T}$$
- If ignore Mutual inductance,  $\beta = \frac{L_2}{L_1}$

- When the LC tank is resonant, the circulating current flows through L<sub>1</sub> in series with L<sub>2</sub>. The equivalent L to use in equation is:
- $L_T = L_1 + L_2 + 2M$  or  $L_T \approx L_1 + L_2$
- L<sub>1</sub> is a primary
- L<sub>2</sub> is the secondary
- M, Mutual inductance between the coils.
- The tuning capacitor C<sub>T</sub> allows the Hartley oscillator to be tuned over a wide range of frequency

- The lowest frequency is determined by the maximum capacitance of CT or otherwise.
- The frequency is determined by the tank's **resonant frequency**:


$$f = \frac{1}{2\pi\sqrt{L_T C_T}}$$

- To start Oscillating, the circuit needs a minimum voltage gain or must be greater than  $1/\beta$

$$A_{\min} = \frac{L_T}{L_2}$$

- If ignore Mutual inductance

$$A_{\min} = \frac{L_1}{L_2}$$

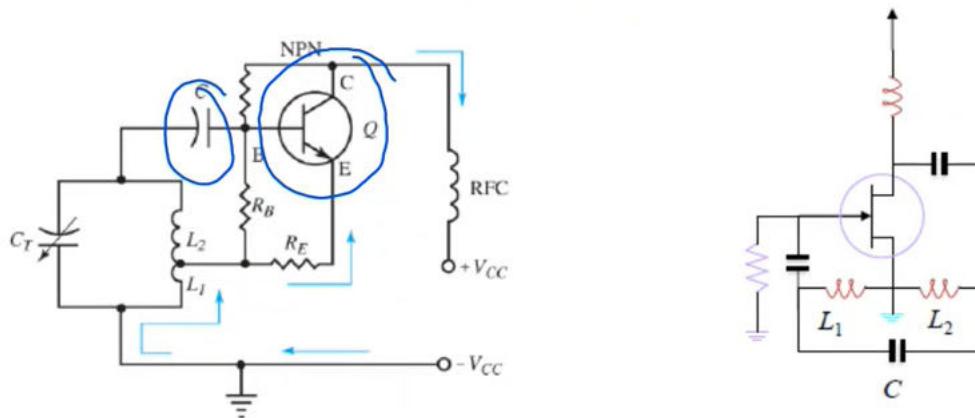


$$f_0 = \frac{1}{2\pi\sqrt{L_{eq}C}} \quad \text{where } L_{eq} = L_1 + L_2 + 2M$$

$M$  = Mutual coupling between  $L_1$  &  $L_2$

## Colpitts Oscillators


BJT; FET; and IC Based

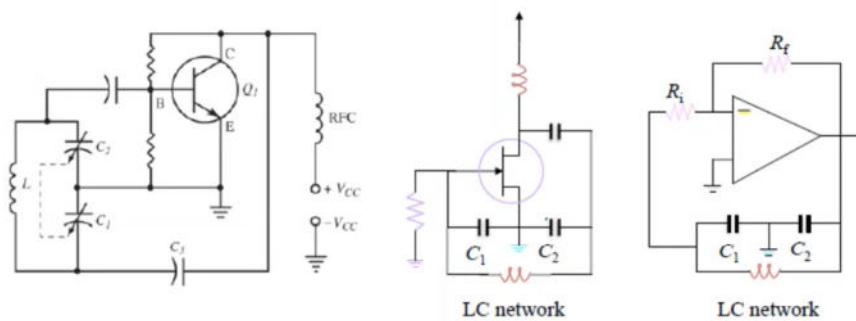


$$f_0 = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad \text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

RFC is an impedance which is high (open) at high RF frequencies and low (short) to dc voltages
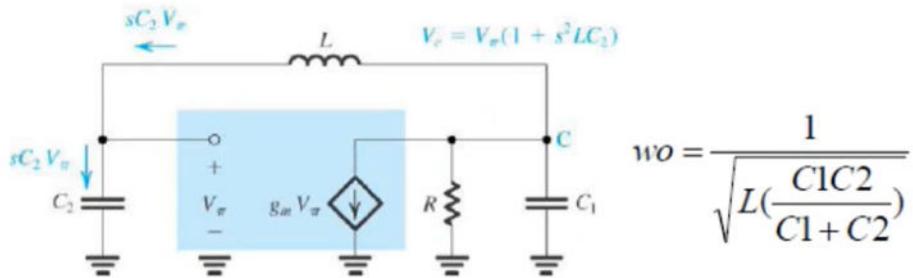
## Equivalent Circuit of the Colpitts Oscillator



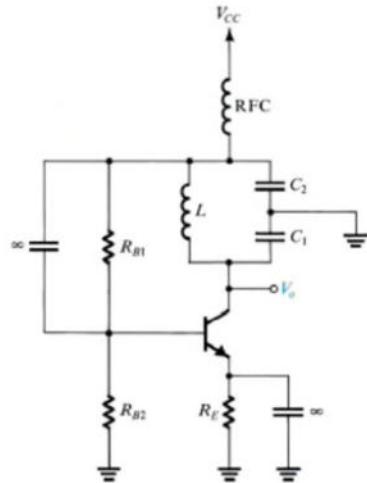Complete Circuit for a Colpitts Oscillator




## The Phase Shifter Oscillator



R-C phase

The phase-shifter consists of a negative gain amplifier ( $-K$ ) with a third order RC ladder network in the feedback.

The circuit will oscillate at the frequency for which the phase shift of the RC network is  $180^\circ$ . Only at the frequency will the total phase shift around the loop be  $0^\circ$  or  $360^\circ$ .

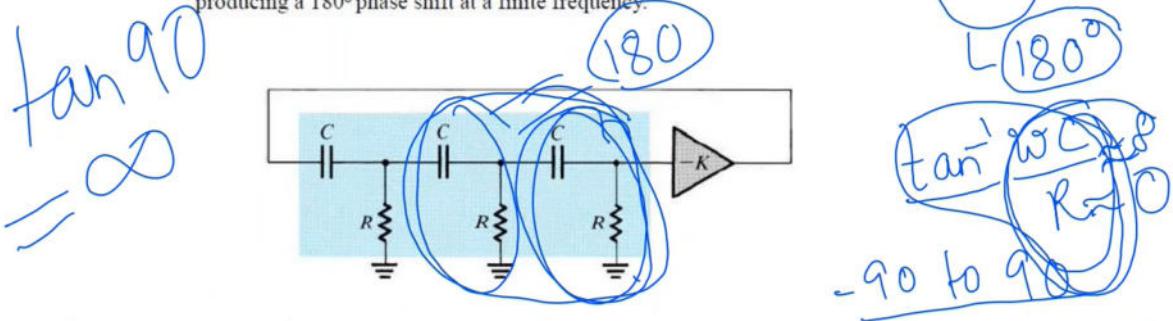The minimum number of RC sections is 3 because it is capable of producing a  $180^\circ$  phase shift at a finite frequency.



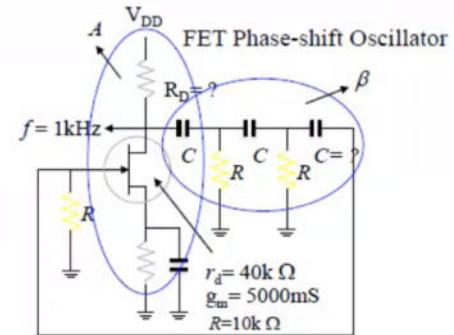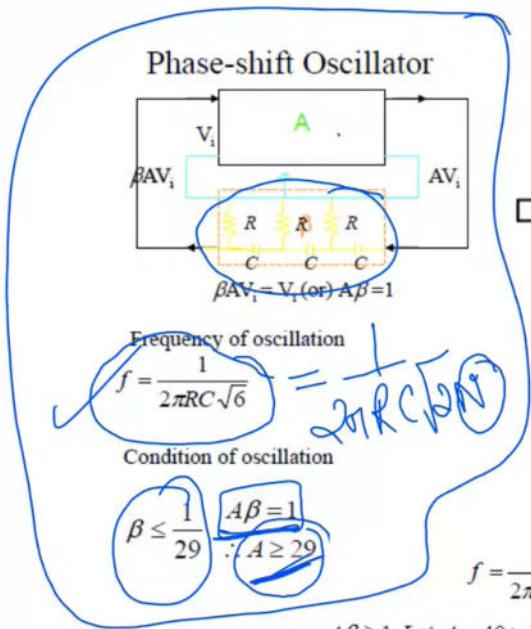

**Example:**

Determine the value of capacitance  $C$  and the value of  $R_D$  of the Phase-shift oscillator shown, if the output frequency is 1 kHz. Take  $r_d = 40k$  and  $g_m = 5000mS$ , for the FET and  $R = 10k\Omega$ .

$$f = \frac{1}{2\pi RC\sqrt{6}} \Rightarrow C = \frac{1}{2\pi R f \sqrt{6}} = \frac{1}{2\pi 10k \times 1k \sqrt{6}} = 6.5nF$$

$$A\beta > 1. \text{ Let } A = 40 > 29 \cdot |A| = \sigma. R = 40 \Rightarrow R = \frac{40}{40} = 8k\Omega$$


---