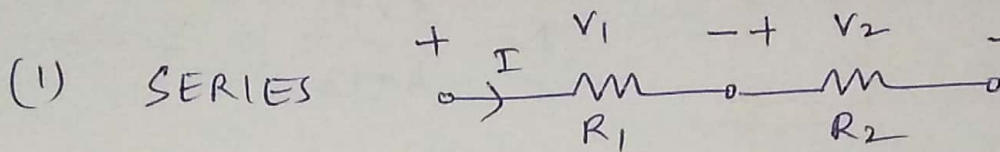


LECTURE # 7

SERIES / PARALLEL RESISTANCES




$$R_{eq} = (R_1 + R_2) \Omega$$

$$V = V_1 + V_2$$

$$I = \frac{V}{R}$$

(2) PARALLEL

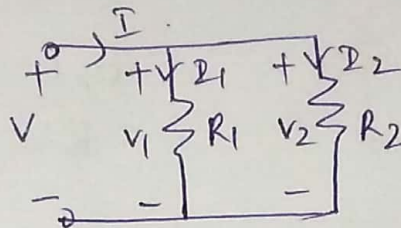

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R = \frac{R_1 R_2}{R_1 + R_2}$$

$$V = V_1 = V_2$$


$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$I = I_1 + I_2$$

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$


Problems

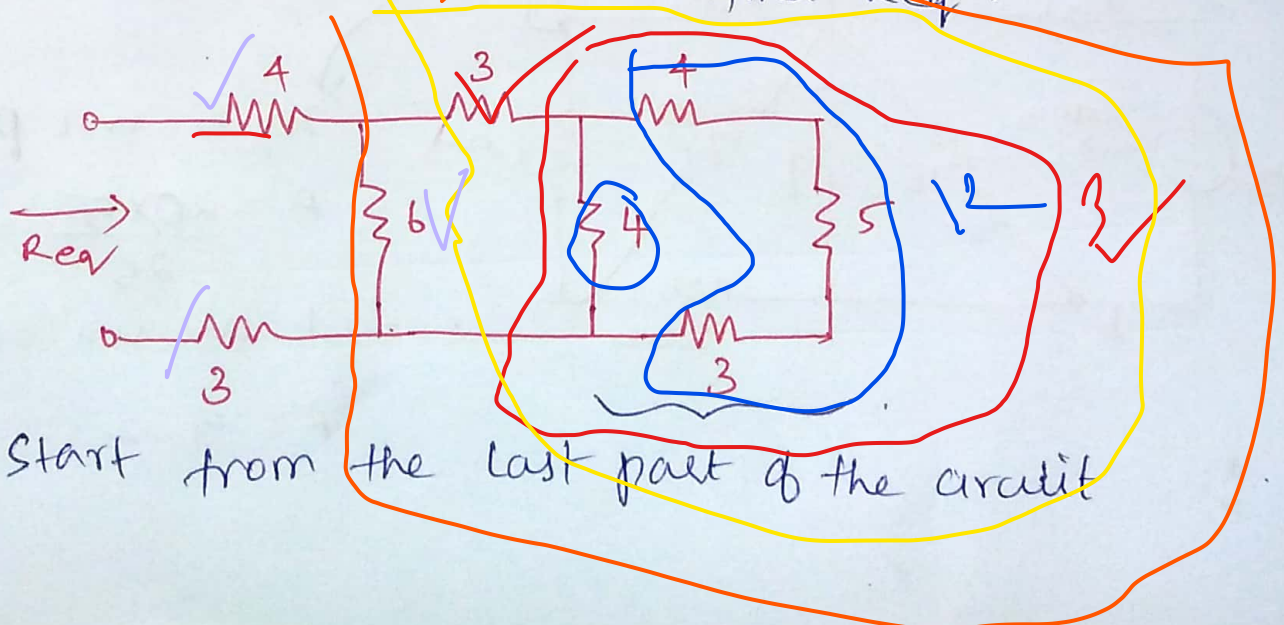(1) Combine the resistors and find R_{eq} .




②

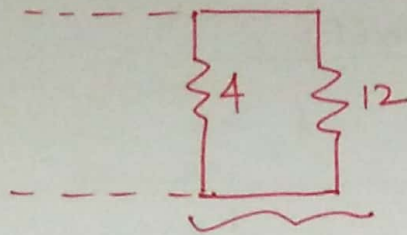4, 5, 3 are in series $R = 4 + 5 + 3 = 12 \Omega$



4, 12 in parallel
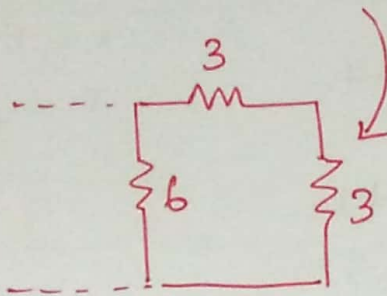
$$R = \frac{4 \times 12}{4 + 12} = 3 \Omega$$




3 + 3 series $R = 6 \Omega$

6, 6 parallel

$$R = 3 \Omega$$


Finally,

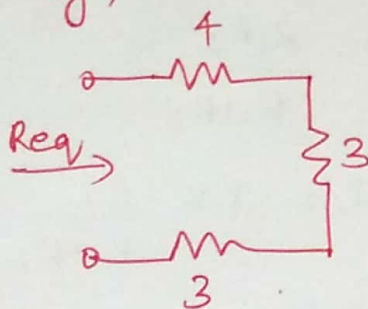

$$R_{eq} = 4 + 3 + 3 = 10$$

$$R_{eq} = 10 \Omega$$

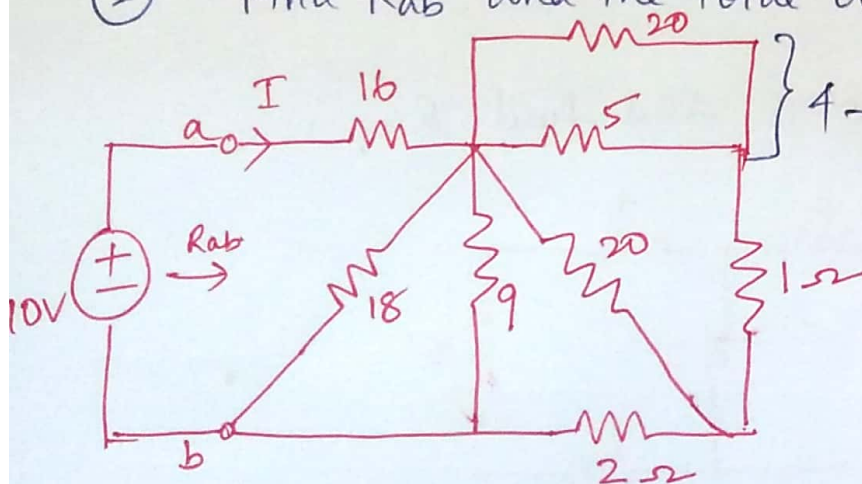② Find R_{ab} and the total current I in the circuit.




20, 5 in parallel.

$$R = \frac{20 \times 5}{20 + 5} = 4$$

4, 1 are in series.

$$R = 5 \Omega$$

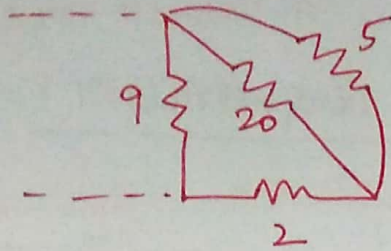

again 20, 5 in parallel


$$R = 4 \Omega$$

4, 2 in series

$$R = 6 \Omega$$


9, 6 in parallel.
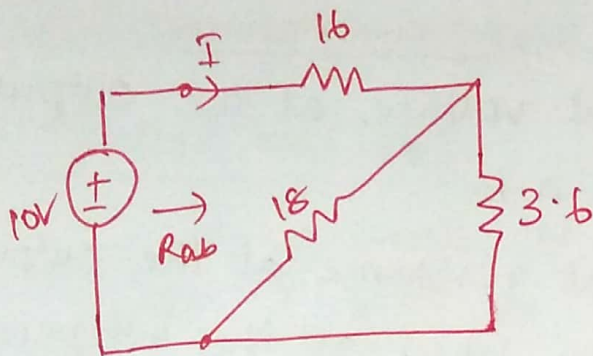
$$R = \frac{9 \times 6}{9 + 6} = 3.6 \Omega$$



Here 18, 3.6 in parallel.
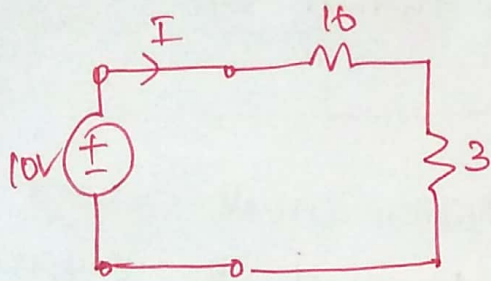
$$R = \frac{18 \times 3.6}{18 + 3.6} = 3$$



$$R_{ab} = 16 + 3 = 19 \Omega$$

$$I = \frac{V}{R_{ab}} = \frac{10}{19}$$


$$I = 0.526 \text{ A}, R_{ab} = 19 \Omega$$

④

NETWORK REDUCTION

M. LEON THEVENIS (1857-1926)
A FRENCH TELEGRAPH ENGINEER


THEVENIN & NORTON EQUIVALENT

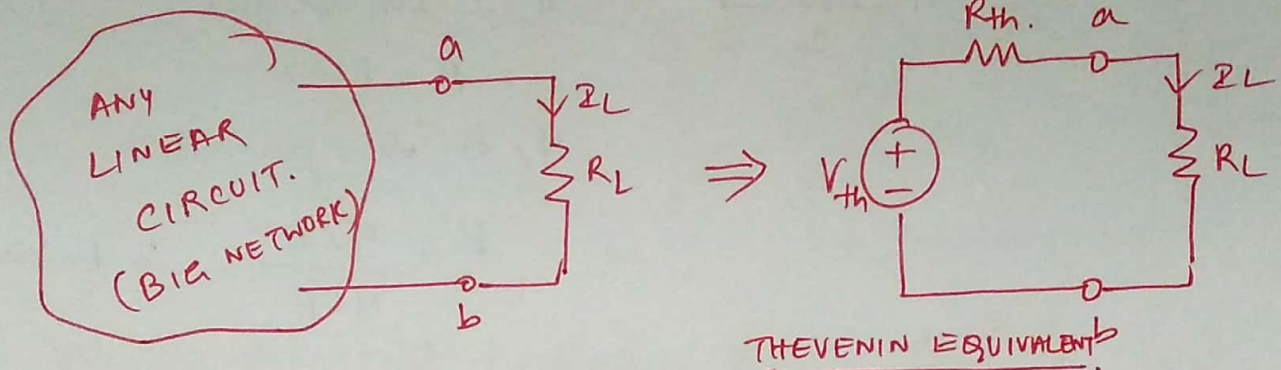

Where, V_{th} = open-circuit voltage at the output terminals a-b.

R_{th} = equivalent resistance at the output terminals when all the independent sources are turned off.

NORTON EQUIVALENT.

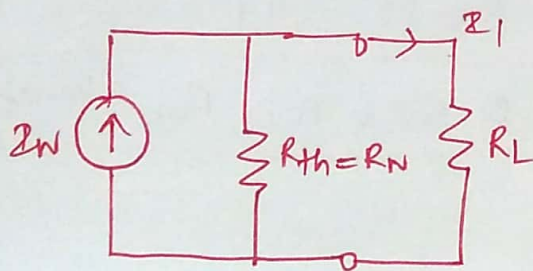

Where,

I_N = short circuit current through the output terminals a-b

We will see that.

$$V_{th} = I_N R_{th}.$$

(or)

$$V_{oc} = I_{sc} R_{th}.$$


$$R_{th} = \frac{V_{oc}}{I_{sc}} = R_N.$$

E. L. NORTON (1926)

AN AMERICAN
ENGINEER AT BELL
TELEPHONE LABORATORIES.

Problem

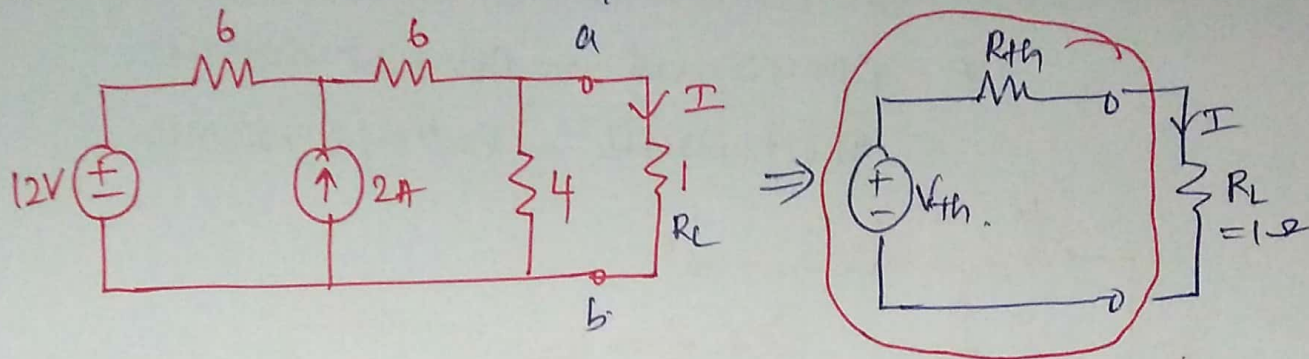(1) Find the thevenin equivalent, then find I .




Find.

Consider the circuit, (excluding R_L)

To find $V_{th}(V_{oc})$

open circuit the output terminals, a-b

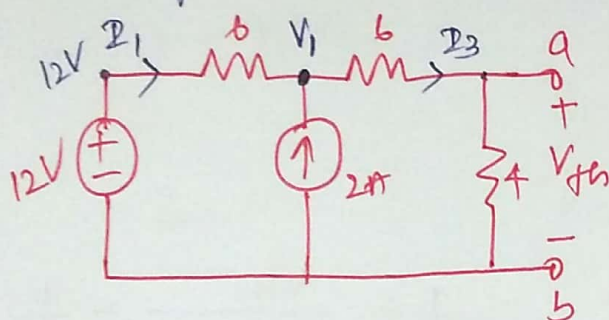

6, 4 series.

Combine $R = 10\Omega$.


Apply KCL at node (V_1), $I_1 + 2 = I_3$.

$$\frac{12 - V_1}{6} + 2 = \frac{V_1 - 0}{10}$$

$$2 + 2 = \frac{V_1}{10} + \frac{V_1}{6} = \frac{16V_1}{60}$$

$$V_1 = \frac{4 \times 60}{16} = 15V$$

$$V_1 = 15V$$

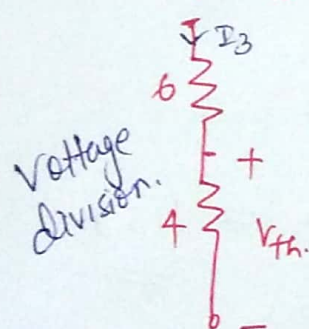

$$V_{th} = V_1 \times \frac{4}{4+6} = 6V$$

$$V_{th} = 6V$$

$$(or) I_3 = \frac{V_1}{10} = 1.5A \therefore V_{th} = 1.5 \times 4 = 6V$$


⑥

To find R_{th}

turn off all independent sources

i.e. open circuit — current sources.

Short circuit — voltage sources.

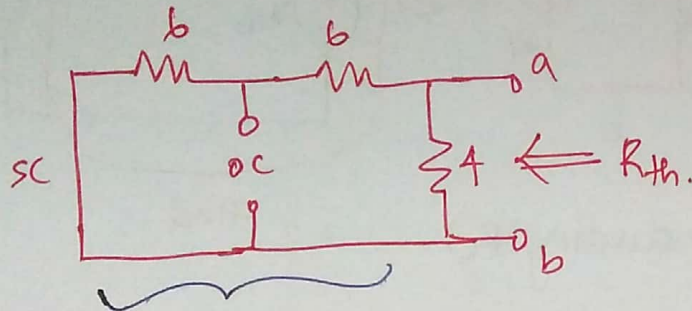


6, 6 series. $R = 12 \Omega$.

$$12 \text{ and } 4 \text{ parallel } R_{th} = \frac{12 \times 4}{12 + 4} = 3 \Omega$$

$$R_{th} = 3 \Omega$$


Thevenin Equivalent

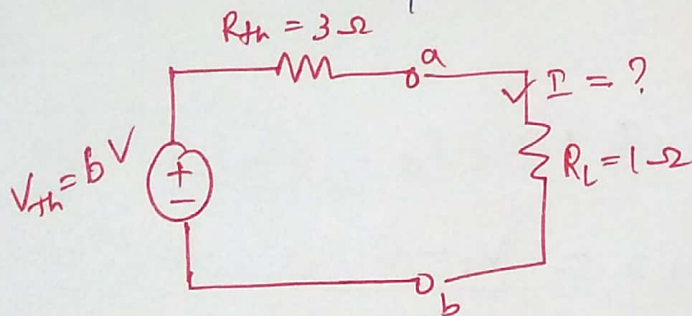

$$I = \frac{V_{th}}{R_L + R_{th}} = \frac{6}{3 + 1}$$

$$I = 1.5 \text{ A}$$

Norton Equivalent

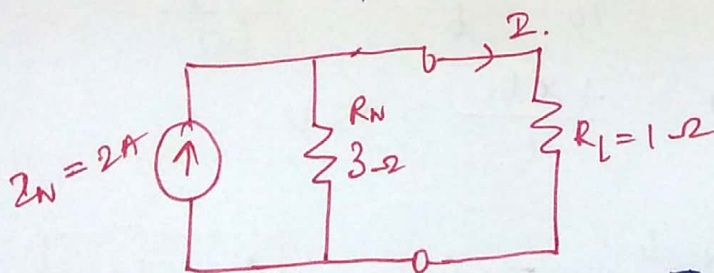

$$I_N = \frac{V_{th}}{R_{th}} = \frac{6}{3} = 2 \text{ A}$$

$$R_N = R_{th} = 3 \Omega$$

current division $\rightarrow I = 2 \times \frac{3}{3 + 1} = 1.5 \text{ A}$