
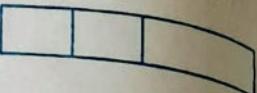


Module 2:

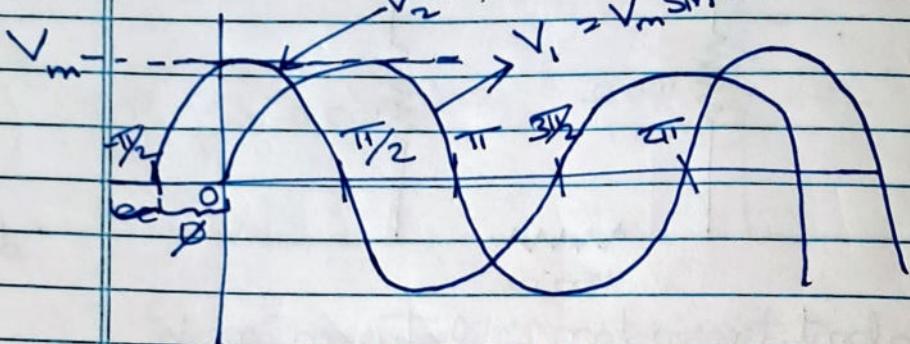

Ac Circuits: $V_2 = V_m \sin(\omega t + \phi)$



We can find

1. Amplitude, $V_m \rightarrow$ Volts
2. Phase angle, $\phi \rightarrow$ deg
3. Angular frequency $\omega = 2\pi f \rightarrow$ rad/sec
4. Time period $T = \frac{2\pi}{\omega} \rightarrow$ sec
5. Frequency $f = \frac{1}{T} \rightarrow$ Hz or cycles/sec

Eg: $V(t) = 10 \sin(50\pi t + 60^\circ)$

Sol: $V_m = 10 \text{ Volts}$

$$\phi = 60^\circ$$

$$\omega = 50\pi \text{ rad/sec}$$

$$T = \frac{2\pi}{\omega} = \frac{1}{25} \text{ sec}$$

$$f = \frac{1}{T} = 25 \text{ Hz}$$

Phasor: (a rotating vector)

→ A scaled line where length of the line represents the magnitude and direction of the line represents the phase at a particular instant of time.

Complex → (i) $z = x + jy$ [rectangular coordinate]

(ii) $z = r \angle \phi$ [polar coordinates]

where $r = \sqrt{x^2 + y^2}$

$\phi = \tan^{-1} \left(\frac{y}{x} \right)$

also can be written

(iii) $z = r e^{j\phi}$

$z = r \cos \phi + j r \sin \phi$ [exponential form]
Real Imaginary

Suppose,

$$V(t) = V_m \cos(\omega t + \phi)$$

In exponential form:

$$V(t) = V_m e^{j(\omega t + \phi)}$$

$$\Rightarrow V_m \cos(\omega t + \phi) + j V_m \sin(\omega t + \phi).$$

So,

$$V(t) = V_m \cos(\omega t + \phi)$$

$$= \text{Real} \{ V_m e^{j(\omega t + \phi)} \}$$

$$= \text{Real} \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$V(t) = \text{Real} \{ V_m e^{j\phi} \} \quad [e^{j\omega t} \text{ negligible}]$$

$$V(t) = V_m \angle \phi$$

So overall,
 $V(t) \approx V_m \cos(\omega t + \phi) = V_m \angle \phi$

Eg: ① $V(t) = 10 \cos[50t + 10^\circ]$

$$V = 10/10$$

$$\omega = 50 \text{ rad/s}$$

② $V(t) = 20 \cos(100\pi t - 20^\circ)$

$$V = 20 \angle 20^\circ$$

$$\omega = 100\pi \text{ rad/s}$$


Note:

- $V_m \cos(\omega t + \phi) = V_m \angle \phi$




- $V_m \cos(\omega t - \phi) = V_m \angle -\phi$


Plotting:

(i) $\vec{V}(t)$

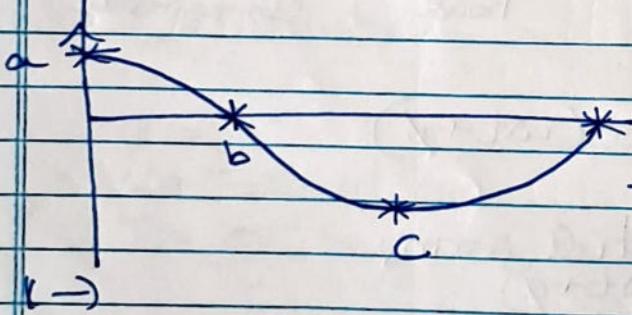

(iv)

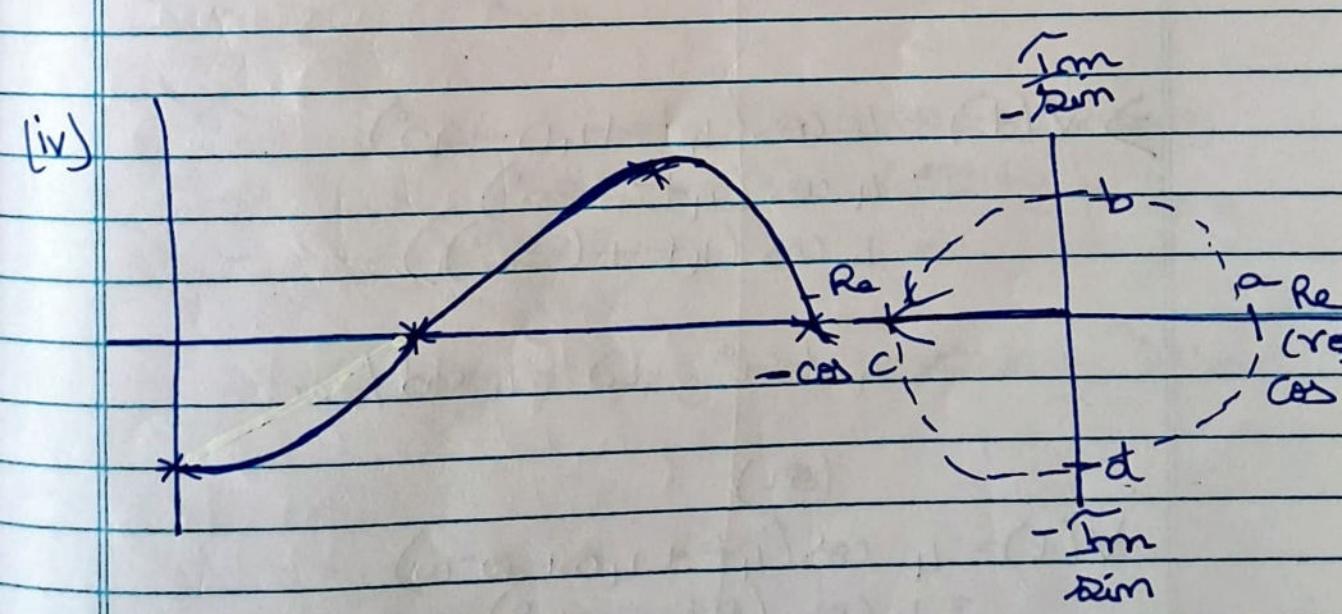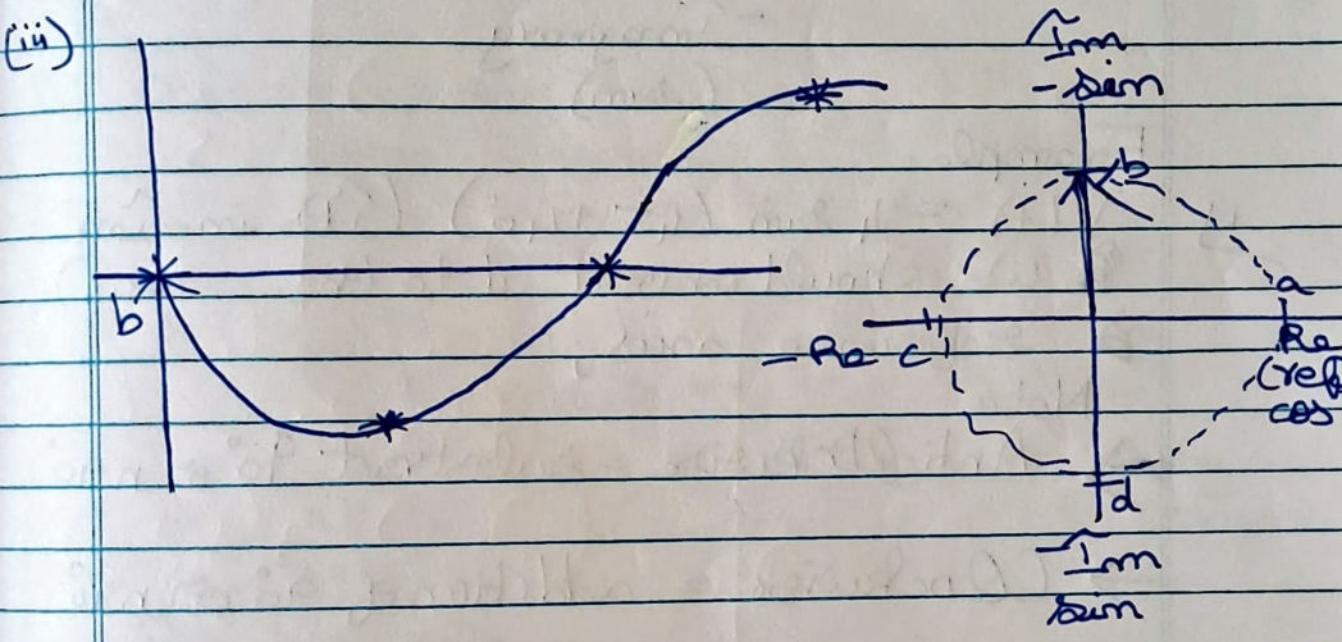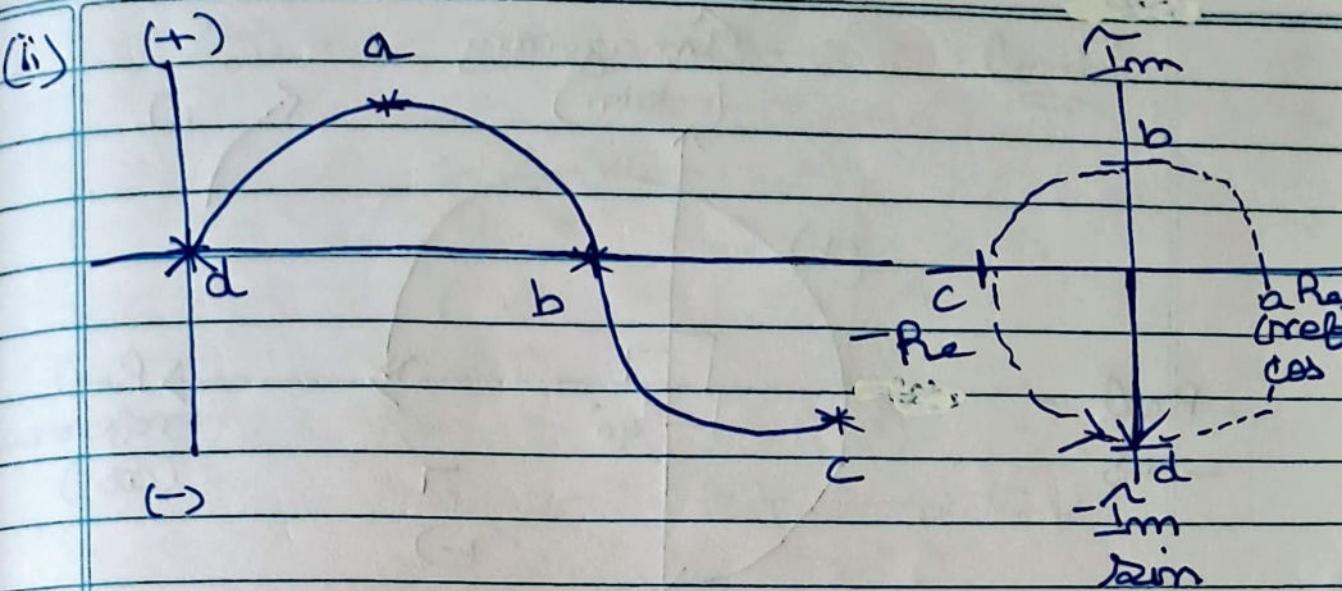

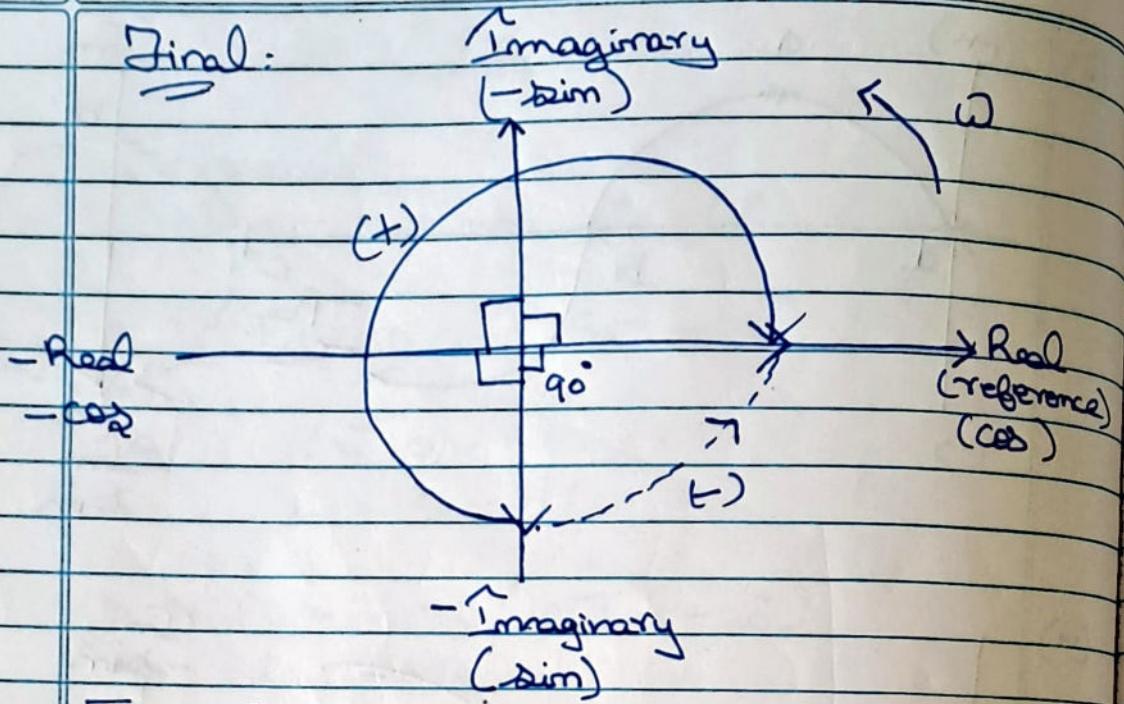

Example:

$\rightarrow V(t) = 4 \sin(4t + 140^\circ)$ (\hat{i} is im- \hat{j} om)
 We should convert it to the reference axis;

Note

\rightarrow Anticlockwise = subtract 90° or $+90^\circ$

\rightarrow Clockwise = addition of 90° or $+90^\circ$

$$\begin{aligned} \Rightarrow V(t) &= 4 \cos(4t + 140 - 90^\circ) \\ &= 4 \cos(4t - 50^\circ) \\ &= 4 \cos(4t + (-50^\circ)) \end{aligned}$$

$$= 4 \text{ } /-50^\circ; \omega = 4 \text{ rad/sec}$$

(or)

$$\begin{aligned} V(t) &= 4 \cos(4t + 140 + 270^\circ) \\ &= 4 \cos(4t + 310^\circ) \\ &= 4 \text{ } /310^\circ; \omega = 4 \text{ rad/sec} \end{aligned}$$

--	--	--

2)

$$\begin{aligned}V(t) &= -4 \sin(\omega t + 45^\circ) \\&= 4 \cos(\omega t + 45^\circ + 90^\circ) \\&= 4 \cos(\omega t + 135^\circ) \\&= 4 \angle 135^\circ ; \quad \omega = \omega.\end{aligned}$$

(or)

$$\begin{aligned}V(t) &= -4 \sin(\omega t + 45^\circ) \\&= 4 \cos(\omega t + 45^\circ - 270^\circ) \\&= 4 \cos(\omega t - 225^\circ) \\&= 4 \angle -225^\circ ; \quad \omega = \omega.\end{aligned}$$

So steps simplified;

- Given Sinusoid



Check



$$V_m \cos(\omega t + \phi) - \checkmark \Rightarrow V_m \angle \phi$$

$\hookrightarrow \times \rightarrow$ convert using phasor.

Sum of phasors:

- To add sinusoids in time domain;
→ use $\cos(A+B)$ identity } long
→ simplify }
(81)
→ Change to phasor and solve } short

Example:

$$\begin{aligned}\downarrow \quad V_1(t) &= -10 \cos(\omega t - 30^\circ) \\V_2(t) &= 20 \cos(\omega t + 50^\circ)\end{aligned}$$

Find $V_1(t) + V_2(t)$;

Ques:

First convert $V_1(t)$ to reference axis,

$$\begin{aligned}V_1(t) &= -10 \cos(\omega t - 30^\circ) \\&= 10 \cos(\omega t - 30^\circ + 180^\circ) \\&= 10 \cos(\omega t + 150^\circ)\end{aligned}$$

$$\Rightarrow V_1(t) = 10 \angle 150^\circ$$

$$V_2(t) = 20 \angle 50^\circ$$

$$V_1 + V_2 = 10 \angle 150^\circ + 20 \angle 50^\circ$$

$$\Rightarrow (-8.67 + j5) + (12.85 + j5.32)$$

$$\Rightarrow 4.18 + j20.32$$

\downarrow \uparrow polar

$$\Rightarrow 20.71 \angle 18.31$$

$$\Rightarrow V_1(t) + V_2(t)$$

$$= 20.71 \cos(\omega t + 18.31)$$

Addition / Subtraction
 $(x_1 \pm jy_1) \pm (x_2 \pm jy_2)$

$$\Rightarrow (x_1 + x_2) + j(y_1 + y_2)$$

$$\text{Eg: } (2 + j4) + (3 + j5)$$

$$\Rightarrow (2+3) + j(4+5)$$

$$= \cancel{5+5} \cdot 5 + j9.$$

$$\text{Eg: } (2 + j4) - (3 + j5)$$

$$\Rightarrow (2-3) + j(4-5)$$

$$\Rightarrow -1 - j1$$

Eg:

-cos


(i)

v

Multiplication / Division

$$\frac{r_1 \angle \phi_1}{r_2 \angle \phi_2} \times \frac{r_2 \angle \phi_2}{r_3 \angle \phi_3} = (r_1 \times r_2) \angle (\phi_1 + \phi_2 + \phi_3)$$

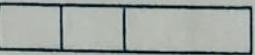
$$\frac{r_1 \angle \phi_1}{r_2 \angle \phi_2} = \left[\frac{r_1}{r_2} \right] \angle (\phi_1 - \phi_2)$$



Angle between the phasors:

$$\text{Eq: } V_1(t) = -10 \sin(\omega t - 30^\circ) = 10 \cos(\omega t + 60^\circ)$$
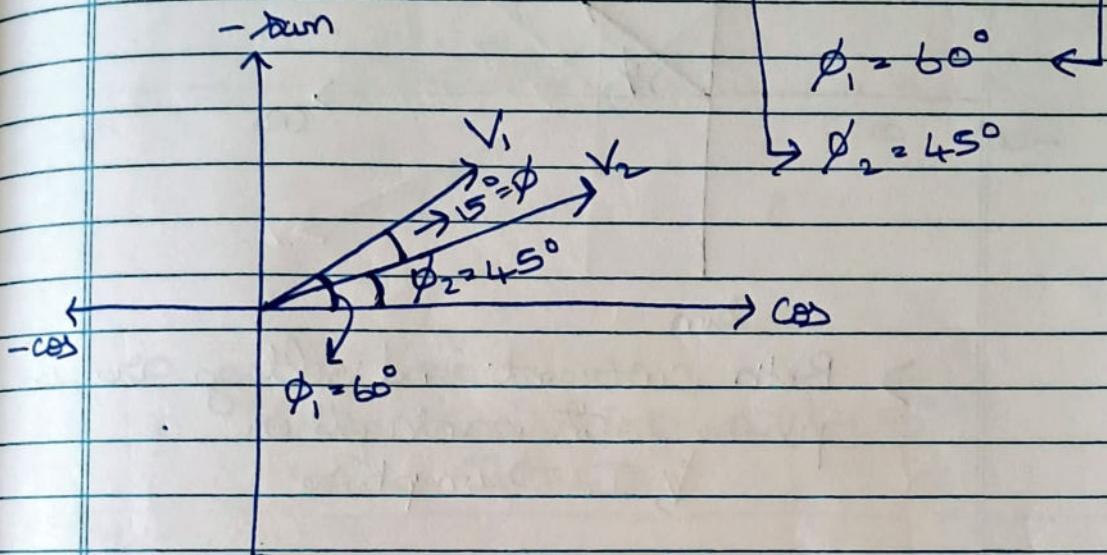
$$V_2(t) = 20 \cos(\omega t + 45^\circ)$$




$$\Rightarrow \phi = \phi_1 \sim \phi_2 = 15^\circ$$

$$\Rightarrow V_1 \text{ leads } V_2 \text{ by } 15^\circ$$

$$V_2 \text{ lags } V_1 \text{ by } 15^\circ$$

Phasor Relationships of R: (RESISTOR).

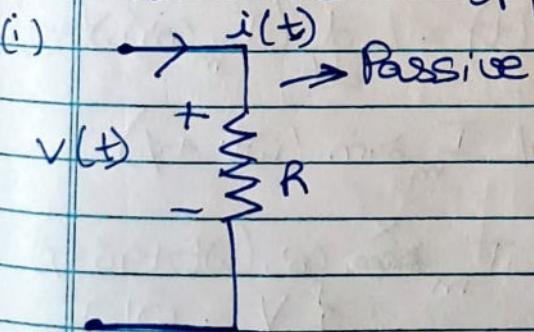

$$V(t) = R \times i(t)$$


$$\text{if } i(t) = I_m \cos(\omega t + \phi) \rightarrow \textcircled{1} \left\{ I_m \neq 0 \right.$$

$$\rightarrow V(t) = \underbrace{I_m}_m R \cos(\omega t + \phi)$$

$$V_m = I_m R \Rightarrow V(t) = V_m \cos(\omega t + \phi) \rightarrow \textcircled{2}$$


$$\Downarrow V_m \neq 0$$

Graphical Representation:

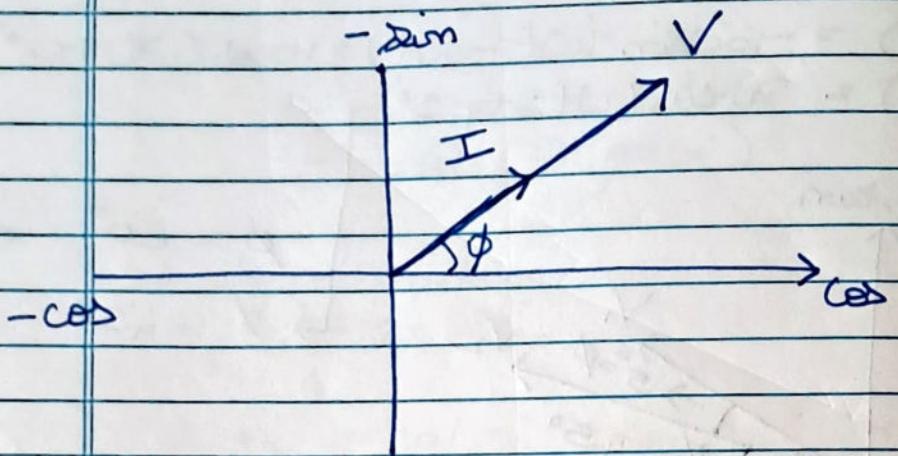

\Rightarrow Both current and voltage are in phase with each other.
 $V, I \rightarrow$ in phase

Phasor Relationship of L:

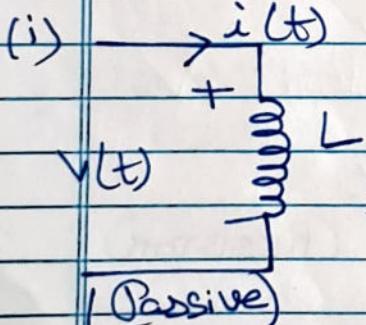

$$V(t) = L \frac{di(t)}{dt}$$

$$\text{If } i(t) = I_m \cos(\omega t + \phi) \rightarrow 0$$

$$(\text{Passive}) \quad V(t) = L \frac{d}{dt} (I_m \cos(\omega t + \phi))$$

$$\Rightarrow V(t) = -\omega L I_m \sin(\omega t + \phi).$$

$$V(t) = \omega L I_m \cos(\omega t + 90^\circ + \phi) \quad \left\{ V_m = \omega L I_m \right.$$

$$V(t) = V_m \cos(\omega t + \phi + 90^\circ) \rightarrow (2) \quad \left\{ V_m \right.$$


$$L \phi + 90^\circ$$

$$\omega L = \frac{V_m}{I_m}$$

$$= |X_L|$$

= inductive reactance
Page: 2


Graphical Representation:

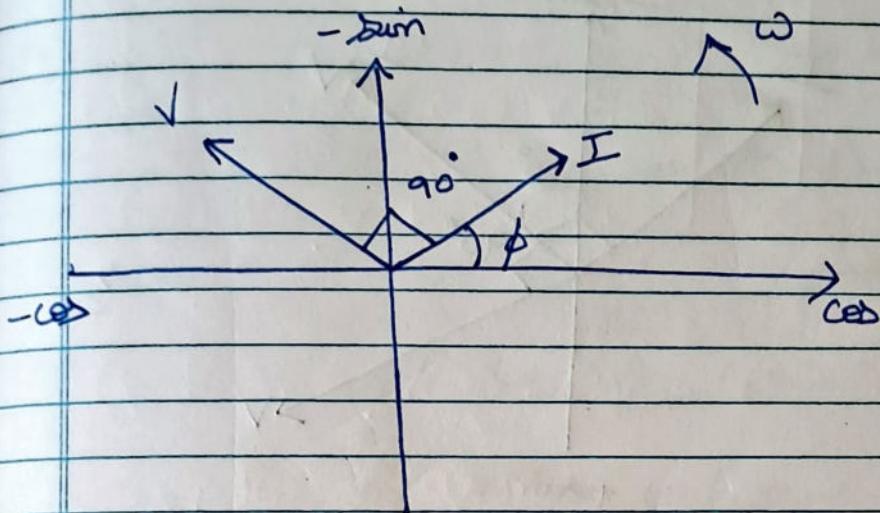

⇒ Voltage leads current by 90° .

V leads $I \rightarrow$ by 90°

H.W

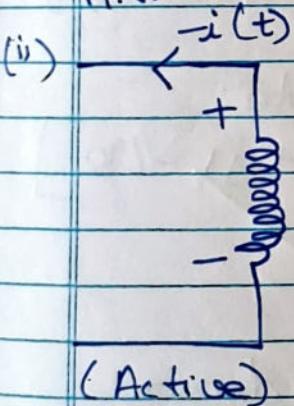

$$V(t) = -L \frac{di}{dt}$$

$$i(t) = I_m \cos(\omega t + \phi) \rightarrow 0$$

$$V(t) = -L \frac{d}{dt} (I_m \cos(\omega t + \phi))$$


$$V(t) = +L \omega I_m \sin(\omega t + \phi).$$

$$V(t) = \omega L I_m \cos(\omega t + \phi - 90^\circ)$$

$$\Rightarrow V(t) = V_m \cos(\omega t + \phi - 90^\circ)$$

$$= V_m \underbrace{\cos}_{\phi - 90^\circ}$$

Graphical Representation.

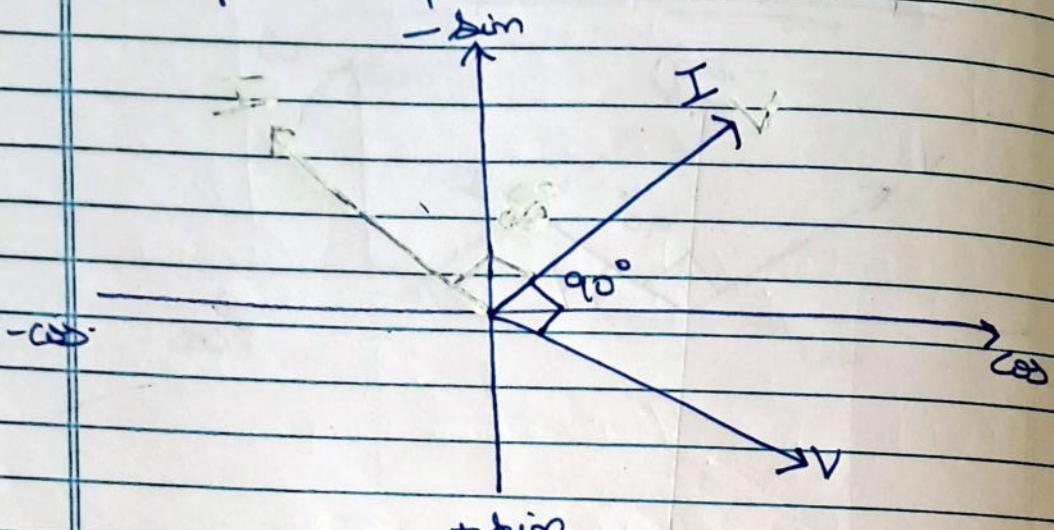

V lags behind I by 90° .

$$V = \text{phasor } V_m \angle \phi + 90^\circ \quad (\text{Cond for passive convention})$$

$$= \omega L T_m \angle \phi / 90^\circ$$

$$V = j\omega L I$$

Note:
 $0 + j1 = 1/90$

$$j\omega L = \frac{V}{I}$$

Time domain
 $V(t) = L \frac{di}{dt} \Rightarrow$

Phaser domain
 $V = j\omega L I$

$$\boxed{\frac{d}{dt} \rightarrow j\omega}$$

Note:

$$S = P + jQ$$

$$S = VI^*$$

$$[I = T_m \angle \phi]$$

$$= V_m L \angle \phi + 90^\circ \times T_m \angle \phi \quad I^* = I_m \angle -\phi$$


$$= V_m I_m \angle \phi + 90^\circ$$

$P + jQ \leftarrow \boxed{S = V_m I_m \angle 90^\circ} \rightarrow \text{for an inductor}$

$\text{Let } V_m I_m = 1 \Rightarrow \begin{array}{l} \text{Page } 1/90 \\ \text{or } 1/j^3 P_{90^\circ Q} \end{array}$

$\therefore \text{Real Power} = 0W$

Phasor Relationships of C:

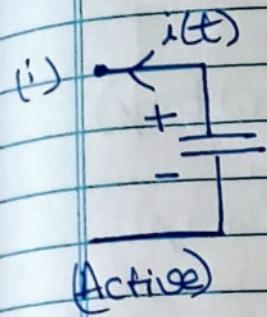

$$i(t) = C \frac{dv}{dt}$$

$$\text{Let } V(t) = V_m \cos(\omega t + \phi) \rightarrow ①$$


$$\Rightarrow i(t) = -C \frac{d}{dt} [V_m \cos(\omega t + \phi)]$$

$$i(t) = \underline{\omega V_m} \sin(\omega t + \phi).$$

$$= \underline{I_m} \cos(\omega t + \phi - 90^\circ)$$

As a phasor; $V = V_m / \phi$; $I = I_m / \phi - 90^\circ$

Graphical Representation:

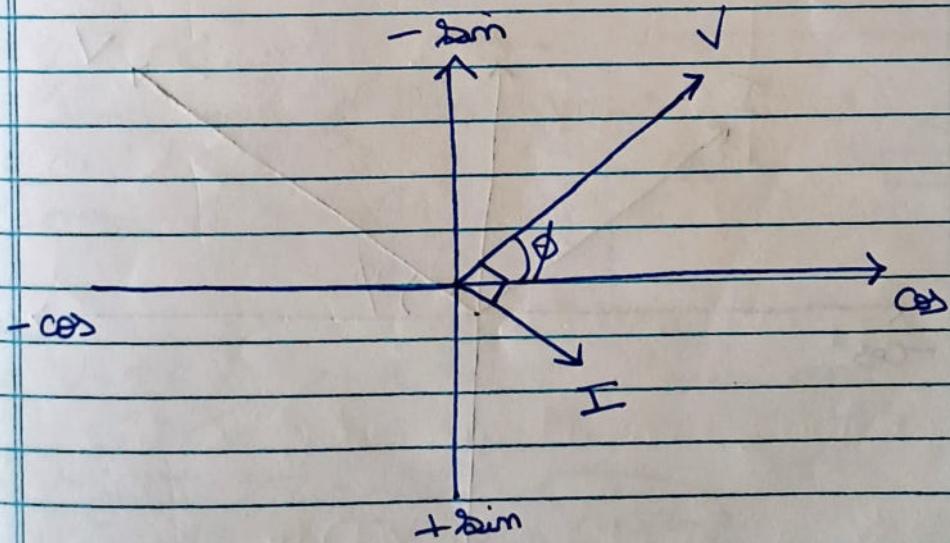


I lags V by 90°
(or)

V leads I by 90° .

H.W

(ii)

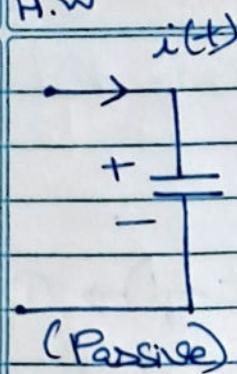

$$i(t) = C \frac{dv}{dt}$$

$$\text{Let } V(t) = V_m \cos(\omega t + \phi)$$


$$\rightarrow i(t) = C \frac{d}{dt} (V_m \cos(\omega t + \phi))$$

$$i(t) = -C\omega V_m \sin(\omega t + \phi)$$

$$= \underline{\underline{C\omega V_m}} \sin(\omega t + \phi + 90^\circ)$$

$$\text{As a phasor; } V = V_m \angle \phi, I = I_m \angle \phi + 90^\circ$$

Graphical Representation:

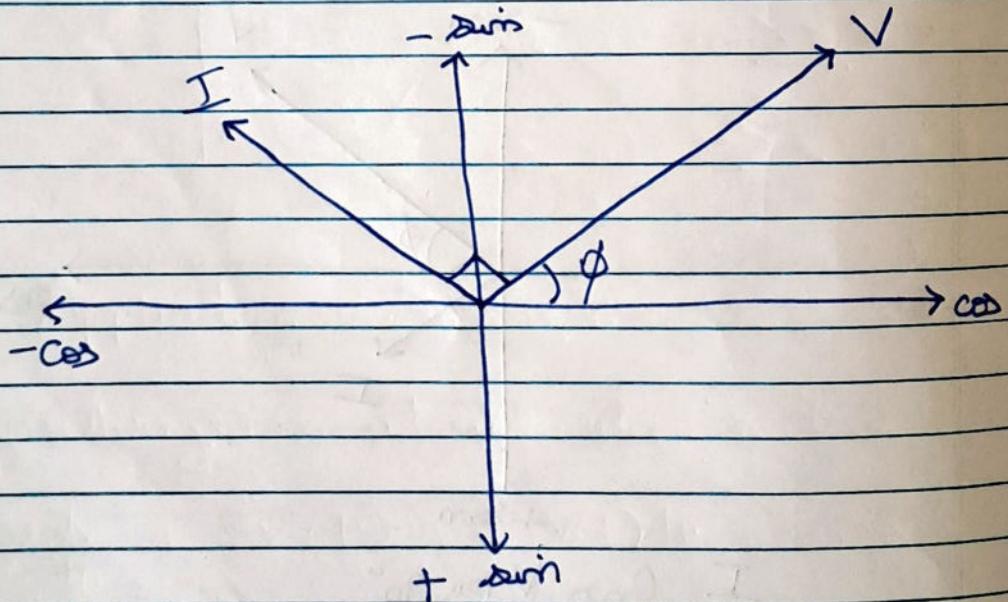

Current leads Voltage by 90°
I leads V by 90°

Contd for active;

$$I = I_m \angle \phi - 90^\circ$$

$$= C\omega V_m \angle \phi - 90^\circ$$

$$= C\omega V_m \frac{\phi}{90^\circ}$$

$$\frac{1}{90^\circ} \rightarrow -jz \left[\frac{1}{j} \right]$$

$$= -jC\omega V_m \angle \phi$$

$$\left[90^\circ = j \right]$$


$$I = -jC\omega V$$

~~Time domain~~
(Time domain)


Note:	
Time	Phasor
\int	$\frac{1}{j\omega}$
C	$\frac{1}{j\omega C}$

Impedance & Admittance:
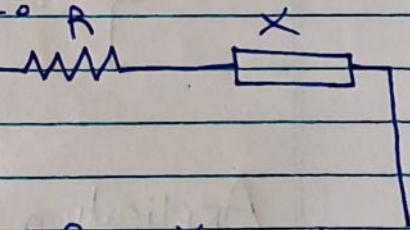
$$\text{Impedance } Z = R + jx \\ = R + j(x_L - x_C)$$


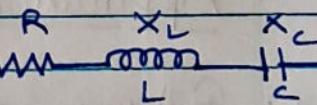
$$\text{Resistor: } V = IR \Rightarrow Z = R$$



$$\text{Inductor } V = j\omega LI \Rightarrow Z = j\omega L$$


$$V = IZ$$

$$\text{Capacitor } V = \frac{1}{j\omega C} I \Rightarrow Z = \frac{1}{j\omega C}$$

$$\text{Admittance } = \frac{1}{Z} = Y$$

Behaviour of Inductor and Capacitor at different frequency (ω):

$$\omega = 2\pi f$$

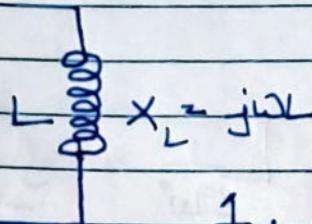

S-frequency

1. At low frequency ($\omega=0$)


$$X_L = 0$$

Inductor \rightarrow Short circuited

2. At high frequency ($\omega=\infty$)

$$X_L = \infty$$

Inductor \rightarrow Open circuited

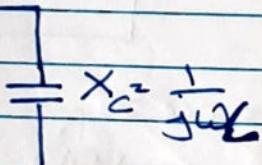

1. $\omega = 0 \Rightarrow X_C = \infty$ (open circuited)

2. $\omega = \infty \Rightarrow X_C = 0$ (short circuited)

Application of Phasors:

1. Solving an integro-differential equation

$$\text{Eq: } 2\frac{dv}{dt} + 5v(t) + 10\int v(t) dt = 5\cos(5t - 30^\circ)$$

Note:

$$\therefore \left| \frac{d}{dt} \rightarrow j\omega ; \int dt \rightarrow \frac{1}{j\omega} \right| \quad \therefore e^{\frac{1}{j\omega}} = -j$$

Transforming for phasor domain,

$$2j\omega V + 5V + 10 \cdot \frac{V}{j\omega} = 50 \angle 30^\circ$$

Given $\omega = 5$,

$$10jV + 5V + \frac{2V}{j} = 50 \angle 30^\circ$$

$$V[10 + 5 + \frac{2}{j}] = 50 \angle 30^\circ$$

$$V[j10 + 5 - j2] = 50 \angle 30^\circ$$

$$V[j8 + 5] = 50 \angle 30^\circ$$

$$V = \frac{50 \angle 30^\circ}{5 + j8} \Rightarrow V = \frac{50 \angle 30^\circ}{9.43 / 57.99}$$

$$V = \frac{50 \angle 30^\circ - 57.99}{9.43} = 5.3 \angle -81.99^\circ$$

$$\Rightarrow V = 5.3 \cos(5t - 81.99^\circ)$$

Practice H.W.:

$$1. \frac{d^2i}{dt^2} + 3i(t) = 4 \cos(\omega t - 74.5^\circ)$$

$$2j\omega i + 3i = 4 \angle -45^\circ$$

$$i(3 + j\omega 2) = 4 \angle -45^\circ$$

Given $\omega = 2$;

$$\Rightarrow i(3 + j4) = 4 \angle -45^\circ$$

$$i = \frac{4/-45^\circ}{5/53.13^\circ}$$

$$i = 0.8 \angle -98.13^\circ$$

$$i = 0.8 \cos(\omega t - 98.13^\circ)$$

$$2. \quad 10(i(t))dt + \frac{di}{dt} + 6i(t) = 5\cos(5t + 22^\circ)A$$

$$\frac{10}{j\omega} i + j\omega i + 6i = 5/22^\circ$$

$$\text{Given } \omega = 5;$$

$$2 - 2j i + 5ji + 6i = 5/22^\circ$$

$$i(-j2 + j5 + 6) = 5/22^\circ$$

$$i(6 + j3) = 5/22^\circ$$

$$i = \frac{5/22^\circ}{6.708/26.565}$$

$$i = 0.7453 \angle -4.565^\circ$$

$$i(t) = 0.7453 \cos(5t - 4.565^\circ)$$


2.

Solving circuits with ac sources in phasor domain.

Ex:

If $V = 10 \cos(100t + 30^\circ)$ is applied to a $50 \mu F$ capacitor, calculate the current through the capacitor.

Sol:

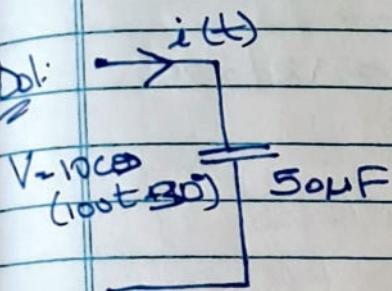

$$X_C = \frac{1}{j\omega C}$$

$$\omega = 100 \text{ rad/s}$$

$$X_C = \frac{1}{j \times 100 \times 50 \times 10^{-6}}$$

$$X_C = j200 \Omega$$

$$X_C = 200/-90^\circ \Omega$$

W.K.T,

$$V = IZ$$

$$I = \frac{V}{Z} = \frac{V}{R + jX_C}$$

$$\boxed{I = \frac{V}{jX_C}}$$

As a phasor, $V = 10/30^\circ V$.

$$\Rightarrow I = \frac{V}{Z}$$

$$= \frac{10/30^\circ}{200/-90^\circ}$$

$$I = 0.05/120^\circ \Rightarrow I(t) = 0.05 \cos(\omega t + 120^\circ) A$$

$$I(t) = 0.05 \cos(100t + 120^\circ) A$$

Practice H.W:

The voltage $V(t) = 12\cos(600t + 45^\circ)$ is applied to a 1H inductor. Find the steady state current through the inductor.

$$V(t) = 12\cos(600t + 225^\circ) = 12 \angle 225^\circ$$

$$X_L = j\omega L$$

$$\omega = 600 \text{ rad/s.}$$

$$X_L = j60$$

$$Z = X_L = j60 \Omega$$

$$Z = X_L = 60 \angle 90^\circ$$

$$I = \frac{V}{Z}$$

$$= \frac{12 \angle 225^\circ}{60 \angle 90^\circ}$$

$$I = 0.2 \angle 135^\circ$$

$$\Rightarrow I = 0.2 \cos(600t + 135^\circ).$$

Instantaneous Power:

$$\text{If } V(t) = V_m \cos(\omega t + \phi_v) \Rightarrow V_m / \phi_v$$

$$i(t) = I_m \cos(\omega t + \phi_i) \Rightarrow I_m / \phi_i$$

$$P(t) = V(t) \cdot i(t)$$

$$= \underbrace{V_m \cos(\omega t + \phi_v)}_{A} \cdot \underbrace{I_m \cos(\omega t + \phi_i)}$$

W.K.T.

$$\cos A \cdot \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$\Rightarrow P(t) = \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i) +$$

$$\frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

1. Constant
2. Independent
of ω, t

3 depends upon
 $(\phi_v - \phi_i)$

1. Sinusoidal

2. dependent on twice
the frequency of
 $V(t) \notin i(t)$

Average Power: (P)

$P(t)$

→ Average of the instantaneous power
over one period.

→ Measure using Wattmeter (Watt).

$$P = \frac{1}{T} \int_0^T P(t) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

As a phasor;

$$V = V_m / \phi_v \quad \& \quad I = I_m / \phi_i$$

$$P + jQ \quad \boxed{S = \frac{1}{2} VI^*} \quad \rightarrow \text{Complex power.}$$

$$\boxed{S = \frac{1}{2} V_m I_m / \phi_v - \phi_i}$$

Power in AC Circuits

P → Real power (True / Active) → Watts 'W'

Q → Reactive power → VAr (Volt Amperes reactive)

$$S = P + jQ \rightarrow \text{Complex Power} / \text{Total VA}$$

(Contd) Average Power:

Using Average power we can rewrite S as,

$$P + jQ = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

$(\theta_v - \theta_i)$ — angle b/w $V \& I$

① Circuit → Resistive; $\theta_v - \theta_i = 0$.

$$P = \frac{1}{2} V_m I_m ; Q = 0.$$

② circuit → reactive (inductive or capacitive)

$$(\theta_v - \theta_i) = \pm 90^\circ$$

$$P = 0 ; Q = \pm \frac{1}{2} V_m I_m$$

Eg 1: $V(t) = 330 \cos(\omega t + 20^\circ)$ V and $i(t) = 33 \sin(\omega t + 60^\circ)$ A. Calculate instantaneous and average power.

Sol: $i(t) = 33 \cos(\omega t + 60^\circ - 90^\circ)$
 $i(t) = 33 \cos(\omega t - 30^\circ)$

$$P(t) = V(t) \cdot i(t)$$

$$= \frac{1}{2} V_m I_m \cos(\omega_0 t + \theta_v + \theta_i)$$

$$+ \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\Rightarrow P(t) = 544.5 \cos(\omega_0 t + 10^\circ) + \underbrace{3499.97854}_{\text{Avg. Power}}$$

$$\text{Average Power (P)} = 3499.97854 \text{ Watt}$$

Eg 2: A current $I = 33/30^\circ$ A flows through an impedance of $Z = 40/22^\circ$ Ω. Find the average power delivered to the load.

Sol: Average power $= \frac{1}{2} I_m^2 R (\theta_i) \frac{V_m^2}{2R}$
 \downarrow Use this
 for now


$$Z = 40/22 \Omega$$

$$\Rightarrow R + jX \Rightarrow Z = \underbrace{37.08}_{\sqrt{R}} - j14.98$$

$$\Rightarrow P = \frac{1}{2} \times 33^2 \times 37.08 = 20190.06 \text{ W}$$

P = 20.19 kW

Eg:3

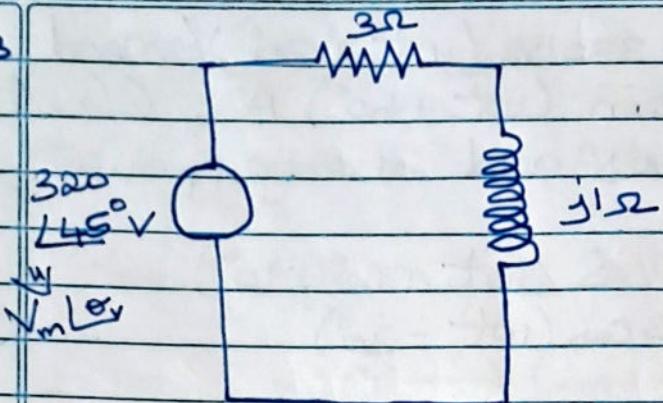

Calculate power supplied by voltage source, power absorbed by resistor and inductor.

Sol:

$$P = \frac{1}{2} \times \frac{320}{Z} \times 101.26 \cos(45^\circ - 26.57^\circ)$$

~~26.57~~

Power supplied by source

Power absorbed by resistance

$$I = \frac{V}{Z} = \frac{320 \angle 45^\circ}{13 + j1}$$

$(\because Z = R + jX)$

$$= \frac{320 \angle 45^\circ}{3.16 \angle 18.43} = 101.26 \angle 26.57 \text{ A.}$$


$$\rightarrow P = \frac{1}{2} \times 320 \times 101.26 \cos(45 - 26.57)$$
$$= 15.35 \text{ kW}$$

$$\text{Power absorbed by Resistor} = \frac{1}{2} I_m^2 R$$
$$= \frac{1}{2} \times (101.26)^2 \times 3$$
$$= 15.35 \text{ kW}$$

Power absorbed by inductor = 0W.

\therefore No REAL POWER ABSORBED BY
INDUCTOR \therefore

Circuit with Resistance & Inductance in

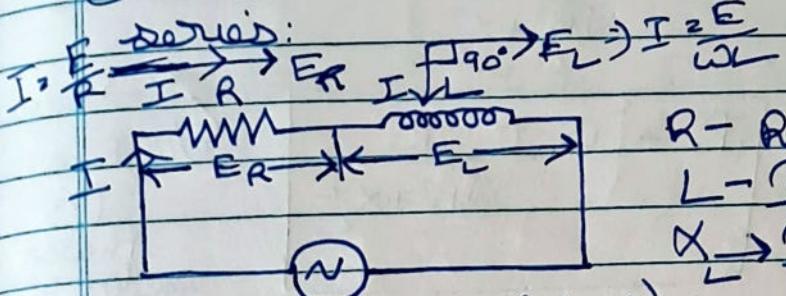

R - Resistance $\rightarrow \Omega$
L - Inductance $\rightarrow H$
 X_L \rightarrow Inductive reactance $\rightarrow \Omega$

$$e = E_m \sin(\omega t + \phi)$$

Voltage drops across
resistance,

$$E_R = IR$$

Voltage drop across
reactance,

$$E_L = I \cdot \omega L = IX_L$$

$$X_L = \omega L = 2\pi f L$$

E \rightarrow Effective value
of applied voltage

I \rightarrow Effective value
of current in
circuit

$$Z = R + jX_L = \sqrt{R^2 + X_L^2}$$

From $\frac{X_L}{R}$

$$Z = |Z| \angle \phi$$

$$I = \frac{E}{Z} = \frac{E \angle \phi}{|Z| \angle \phi} = \frac{E \angle \phi}{Z} = I_m \angle \phi$$


$$i = I_m \sin(\omega t - \phi)$$

$$\text{I lags by } \phi = \tan^{-1} \frac{X_L}{R}$$

$$E = \sqrt{E_R^2 + E_L^2}$$

$$= \sqrt{(IR)^2 + (IX_L)^2} = I \sqrt{R^2 + X_L^2}$$
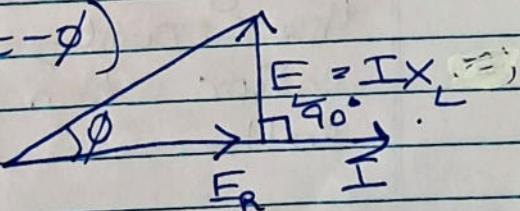
$$\Rightarrow E = IZ \Rightarrow I = \frac{E}{Z} = \frac{E}{\sqrt{R^2 + X_L^2}}$$



Power → Consumed by 'R' only

$$P = I^2 R = I \cdot IR \\ = \frac{E}{\sqrt{R^2 + X_L^2}} \cdot IR$$

$$P = E \cdot I \frac{R}{\sqrt{R^2 + X_L^2}}$$

ϕ → angle
b/w E and I
(or)
Power factor angle

$$\text{Power factor} (\cos\phi) = \frac{E_R}{E} = \frac{IR}{I\sqrt{R^2 + X_L^2}}$$

$$\Rightarrow \cos\phi = \frac{R}{\sqrt{R^2 + X_L^2}} = \frac{R}{Z}$$

$$P = E \cdot I \cos\phi$$

$$i = I_m \sin(\omega t - \phi)$$

Eg: (i) Voltage across a coil is 4.5V when it carries direct current of 9A. If the same coil carries an alternating current of 9A at 25Hz, then the voltage across the coil is 24V. Find the current, active power, and power factor when it is supplied by 50V at 50Hz.

Sol: ① Coil → inductor and small resistance in series.
 $Z = (R + jX_L)$.

$$\textcircled{2} \text{ DC } \Rightarrow R = \frac{V}{I}$$

$$\text{i) } V_{\text{coil}} = 4.5V ; I_{\text{coil}} = 9A ; R_{\text{coil}} = 0.5\Omega$$

$$\text{ii) } V_{\text{coil}} = 24V \text{ at } 25\text{Hz} ; I_{\text{coil}} = 9A$$

$\therefore V = \frac{4.5}{9} \times 24$

$$Z_{\text{coil}} = \frac{V_{\text{coil}}}{I_{\text{coil}}} = \frac{24}{9} = 2.66\Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$\downarrow \quad \downarrow$

$2.66\Omega \quad 0.5\Omega$

$$\Rightarrow Z_{\text{coil}} = \sqrt{R^2 + X_{\text{coil}}^2}$$

$$X_{\text{coil}} = \sqrt{(2.66)^2 - (0.5)^2}$$

$f = 25\text{Hz}$

$$X_L = 2.62\Omega \Rightarrow 2\pi f L = 2.6 \Rightarrow L = \frac{2.6}{2\pi \times 25}$$

$$\text{iii) New AC circuit: } \Rightarrow L = 0.0167\text{H}$$

$$f = 50\text{Hz}, X_{\text{coil new}} = \sqrt{R_{\text{coil}}^2 + (X_{\text{coil new}})^2}$$

$$= \sqrt{0.5^2 + (5.24)^2}$$

$$= 5.26\Omega$$

$$Z_{\text{coil new}} = \sqrt{(R_{\text{coil}})^2 + (X_{\text{coil new}})^2}$$

$$= \sqrt{(0.5)^2 + (5.24)^2}$$


$$Z_{\text{coil new}} = 5.26\Omega$$

$$(a) I_{\text{new}} = \frac{V}{Z_{\text{coil, new}}} = \frac{50}{5.26} = 9.50 \text{ A.}$$

$$I_{\text{new}} = 9.5 \text{ A}$$

$$(b) P = I^2 R_{\text{coil}} = (9.5)^2 \times (0.5) = 45.1 \text{ W}$$

$$(c) \cos \phi = P_f =$$

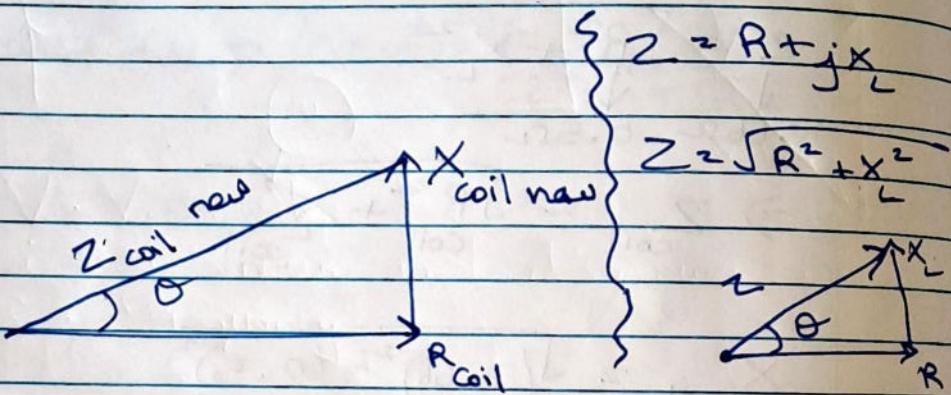

$$\cos \theta = \frac{R_{\text{coil}}}{Z_{\text{coil, new}}} = \frac{0.5}{5.26} = 0.095 \text{ (lagging)}$$

$$\theta = \cos^{-1}(0.095) = 84.54^\circ$$

Till CAT-1

Eg2: In a series R-L circuit, the instantaneous voltage $V = 141.4 \sin(\omega t)$ and instantaneous current $i = 0.707 \sin(\omega t)$, where $\omega = 314 \text{ rad/sec}$.


$$(a) Z = ?$$

$$(b) \text{Active Power \& Power factor (cos)}$$

$$(c) \text{Draw the phasor diagram b/w } V \text{ \& } I.$$

$$\textcircled{a} \quad Z = \frac{V_{\text{rms}}}{I_{\text{rms}}}$$

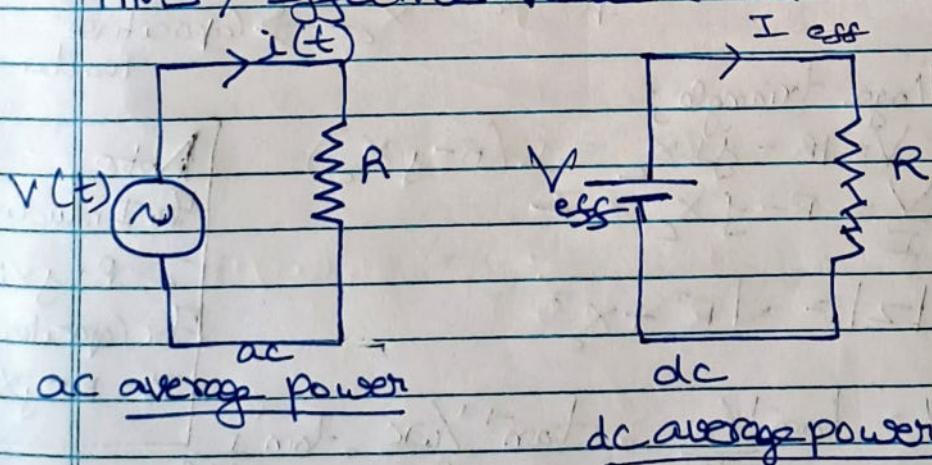RMS / Effective Value (Root Mean Square):



$$P = \frac{1}{T} \int_0^T i^2 R dt \rightarrow \textcircled{1}$$

$$P = \frac{T}{\text{eff}}^2 R \rightarrow \textcircled{2}$$


$$I_{\text{eff}}^2 = \frac{1}{T} \int_0^T i^2 dt \rightarrow$$

$$\boxed{\frac{1}{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{\text{rms}}}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int^T V^2 dt} = \sqrt{\frac{V_{\text{rms}}^2}{T} T} = V_{\text{rms}}$$

$$\Rightarrow V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \quad \text{and} \quad I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

RC series circuit:

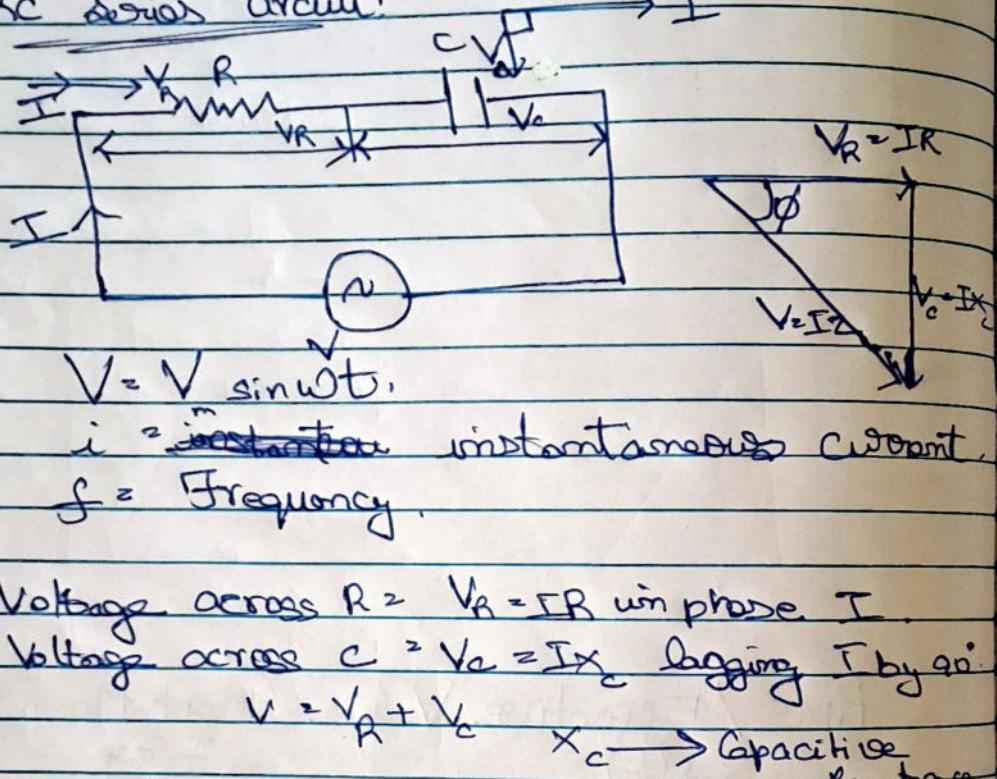

$$V = V \sin \omega t,$$

i = instantaneous instantaneous current.

f = Frequency.

Voltage across $R = V_R = IR$ in phase I .

Voltage across $C = V_C = I X_C$ lagging I by 90° .

$$V = \sqrt{V_R^2 + V_C^2} \quad X_C \rightarrow \text{Capacitive Reactance}$$

Voltage triangle:

$$V = IR - jIX_C = I(R - jX_C)$$

$$\frac{V}{I} = R - jX_C = Z$$

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{1/X_C}{R} = \tan^{-1} \frac{1}{\omega C}$$

$$X_C = \frac{1}{\omega C}$$

$$\phi = \text{phase angle}, z = R - jX_C = |Z| / \angle \phi$$

$$\cos \phi (\text{P.f.}) = R/z \quad \text{Active power (True Power) } P = V_{\text{rms}} I_{\text{rms}} \quad (\text{Watt})$$


$$\text{Reactive power } Q = V_{\text{rms}} I_{\text{rms}} \sin \phi \quad (\text{VAR})$$

--	--	--

POWER FACTOR:

Load → Real → Useful work.
 Load → Reactive → flux (rotating machine)

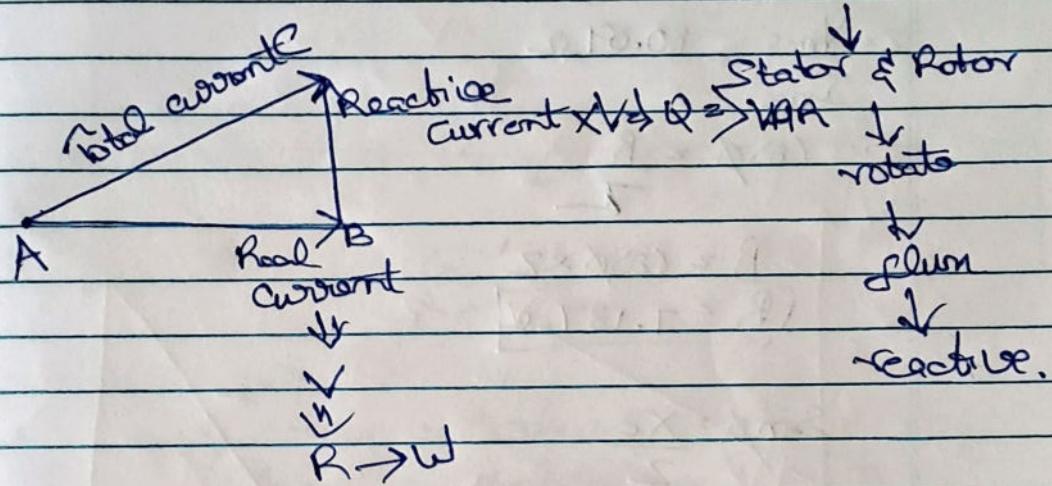Total current $\rightarrow \sqrt{(Real\ current)^2 + (Reactive\ current)^2}$



Power factor = $\frac{AB}{AC} = \frac{RW}{kVA} = \frac{P}{S}$

e.g.: Find the circuit constants of a star connected series circuits which consumed 700W with 0.707 loading P.f. The applied voltage is $V = 141.4 \sin 314t$. Find R & Z.

Soln: $V_m = 141.4 V$

$$V_{rms} = \frac{141.4}{\sqrt{2}} = 99.98 V$$

$$\cos \phi = 0.707 \text{ Reading}$$

$$\phi = 45^\circ$$

$$\text{Power} = VI \cos \phi$$

$$700 = 0.707 \times 99.98 \times I$$

$$I_{\text{rms}} = 9.902 \text{ A}$$

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = 10.09 \Omega$$

I_{rms}

$$\cos \phi = \frac{R}{Z}$$

$$\boxed{R = \cos \phi \times Z}$$

$$\boxed{R = 7.137 \Omega}$$

$$\sin \phi = \frac{X_C}{Z}$$

$$\sin 45^\circ = \frac{X_C}{10.09}$$


$$\boxed{X_C = 7.134 \Omega}$$

$$X_C = \frac{1}{wC}$$

$$C = \frac{1}{314 \times 7.134} = 446.6 \mu\text{F}$$

RLC series circuits:

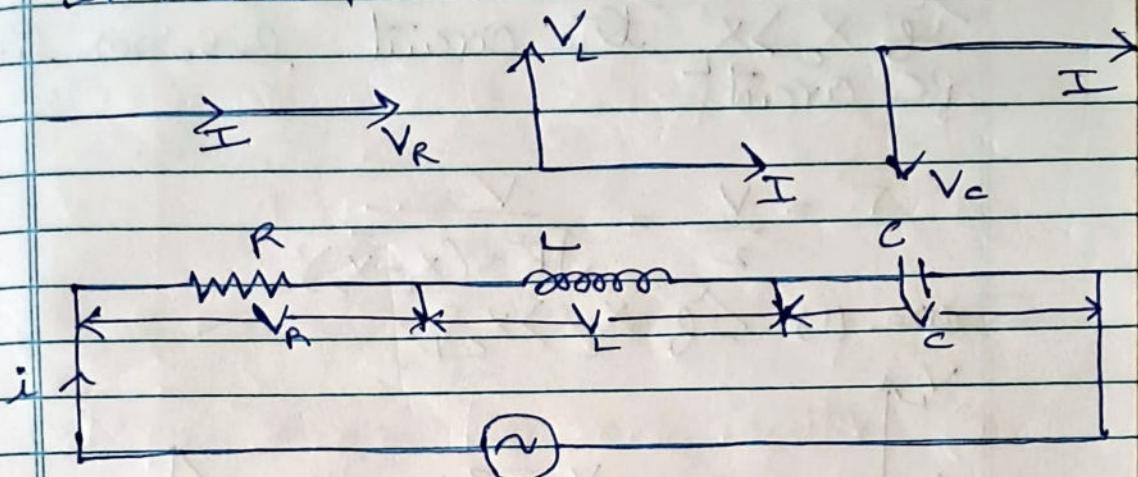Resistance R, inductance L & capacitors C all are connected in series.



$$V = V_m \sin(\omega t)$$

i = instantaneous current

I is taken as reference vector

Voltage across $R = V_R = IR$ in phase with I

Voltage across $L = V_L = IX_L 190^\circ$ V leads I by 90°

Voltage across $C = V_C = IX_C - 190^\circ$ V lags I by 90°

$$\text{Applied Voltage } V = V_R + V_L + V_C$$

$$= IR + jIX_L - jIX_C$$

$$\frac{V}{I} = R + j(X_L - X_C)$$

$$Z = R + j(X_L - X_C)$$

$$= Z \angle 0^\circ$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$(X_L - X_C) \rightarrow$ not reactance.

If $X_L > X_C$, the circuit behaves like RL circuit.

If $X_C > X_L$ the circuit behaves like RC circuit.

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

case (i) If $X_L > X_C$,

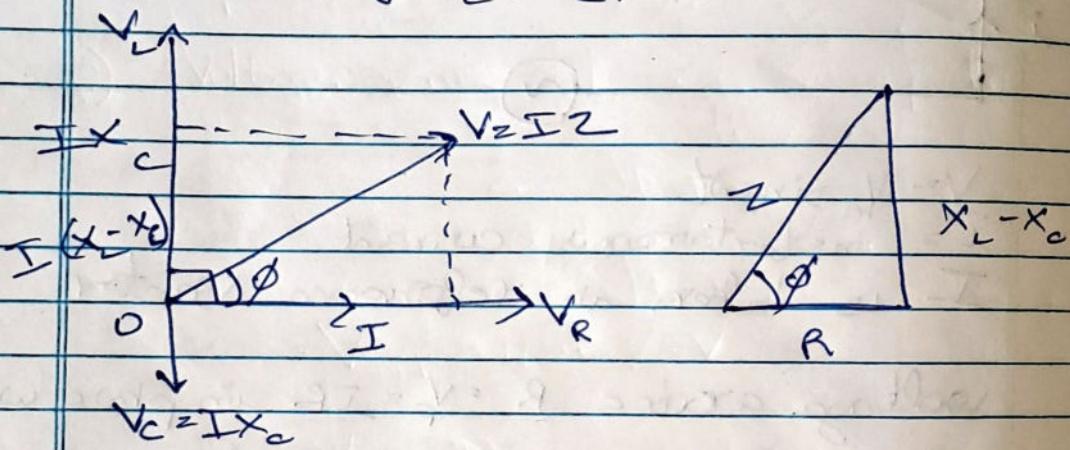


$$\begin{aligned}\tan \phi &= \frac{X_L - X_C}{R} \\ &= (\omega L - \frac{1}{\omega C})\end{aligned}$$

$$\phi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$P.dg = \cos \phi = \frac{R}{Z} \text{ lagging (R-L).}$$

case (ii) If $X_C > X_L$ RC circuit.

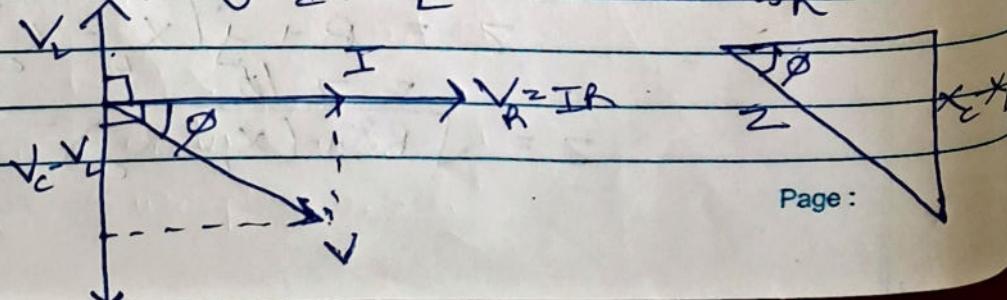

Here I leads V by ϕ \therefore capacitive

$$V = IX_c$$

$$\tan \phi = \frac{X_c - X}{R} \rightarrow \frac{1/X_c - \omega L}{R}$$

$$\phi = \tan^{-1} \left(\frac{1/X_c - \omega L}{R} \right)$$


$$P.F = \cos \phi = \frac{R}{Z} \text{ looking (RC circuits)}$$

$$\text{Actual power} = VI \cos \phi \text{ (Watt)}$$


$$\text{Reactive power} = VI \sin \phi \text{ (VAR)}$$

eg: A coil of resistance 10Ω and $L = 0.1\text{H}$ is connected in series with a $150\mu\text{F}$ capacitor across 200V , 50Hz supply. calculate (a) inductive reactance (b) capacitive reactance (c) impedance (d) current (e) P.F (f) voltage across coil and capacitor.

Sol: General:

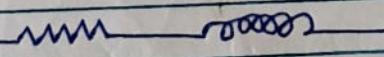Coil \rightarrow 

Non-inductive coil \rightarrow 

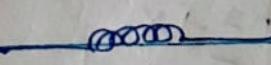Non resistive coil \rightarrow 

$$a) X_L = \omega L = 2\pi f L = 31.4 \Omega$$

$$b) X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 21.23 \Omega$$

Here $X_L > X_C \Rightarrow$ Inductive circuit.

$$c) Z = \sqrt{R^2 + (X_L - X_C)^2} = 41.28 \Omega$$

$$d) I = \frac{V}{Z} = \frac{220}{41.28} = 5.33 A$$

$$e) p.f = \cos \phi = R/Z = 0.7 \text{ lagging}$$

f) Voltage across coil $= I \times$ ~~impedance~~ ^{*} of the coil.

$$= \sqrt{R^2 + X_L^2}$$

$$= \sqrt{10^2 + 31.42^2} = 32.97 \Omega$$

$$V_{coil} = 161.62 V$$

$$V_C = IX_C = 29.7 \Omega$$

$$V_L = IX_L = 439.82 V$$

Admittance (Y) : Inverse of impedance, expressed in Ω^{-1} mho (Ω).

$$Y = \frac{1}{Z}$$

$$Z = R + jX$$

$$Y = \frac{1}{R + jX} = G + jB$$


$$G = \text{Conductance} = \frac{1}{R}$$

$$B = \text{Susceptance} = \frac{1}{X}$$

eg:

An impedance of $(7 + j5) \Omega$ is connected in Π cl with another circuit having an impedance of $(10 - j8) \Omega$. The Supply voltage is $230V, 50Hz$. Calculate (i) the admittance (Y), the conductance (G) and susceptance (B) of the combined circuit (ii) the total current (I) taken from mains and its p.f.

Sol:

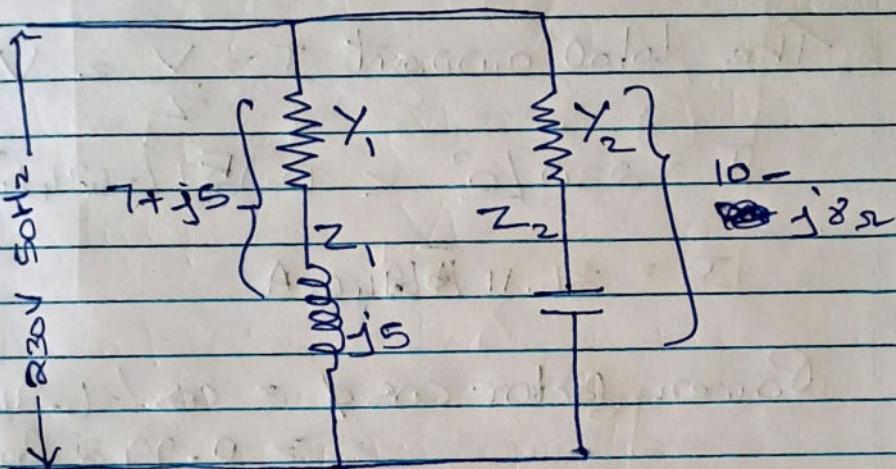

$$Z \text{ in series} = Z_1 + Z_2$$

$$Z \text{ in parallel} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Y \text{ in } \Pi \text{ cl} = Y_1 + Y_2$$

$$Y \text{ in series} = \frac{Y_1 Y_2}{Y_1 + Y_2}$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{7 + j5} = \frac{1}{8.6 / 35.53}$$

$$= 0.11627901 / -35.53 = 0.095 - j0.0680$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{10-j8} = \frac{1}{12.806 - j28.660} \\ = 0.061 + j0.01975$$

The net admittance in $\text{H.b.} = Y_1 + Y_2$

$$= 0.156 - j0.01975$$

$$Y = G - jB$$

$$\therefore G = 0.156 \text{ S}, B = 0.01975$$

\checkmark conductance

\checkmark Susceptance

The total current $I = \frac{V}{Z} = \frac{V}{Y}$

$$I = 230 / 0^\circ \times 0.157 L - j0.944$$



$$I = 36.11 \angle 6.94^\circ \text{ A.}$$

$$\begin{aligned} \text{Power factor } \cos \phi &= \cos (-6.94) \\ &= 0.992 \text{ lagging.} \\ &\quad \downarrow \\ &\quad \text{Since L >} \end{aligned}$$



Poly Phase System (Same frequency but different phases)

- (i) Single phase - two wire system

Phase (P) Neutral (N)

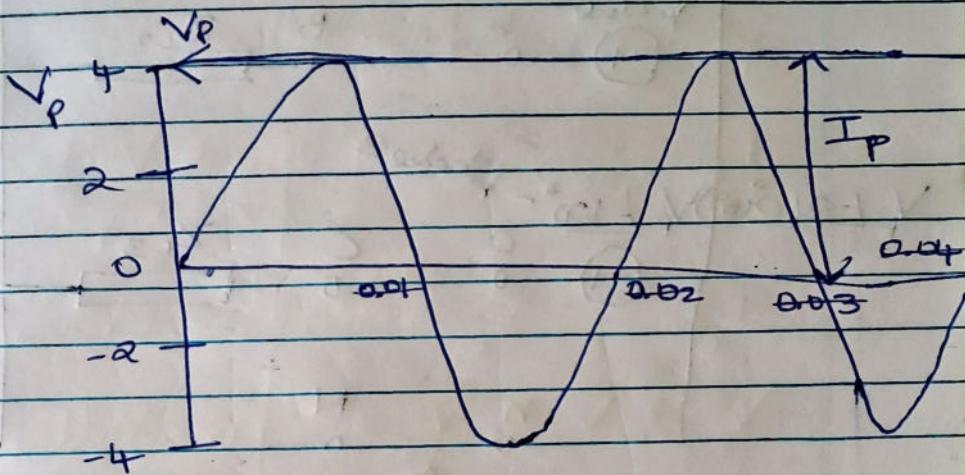
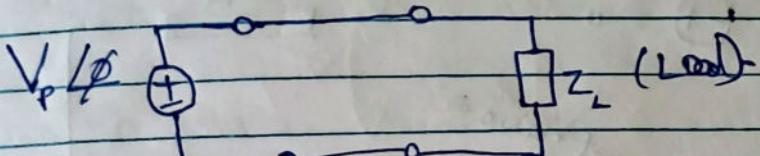


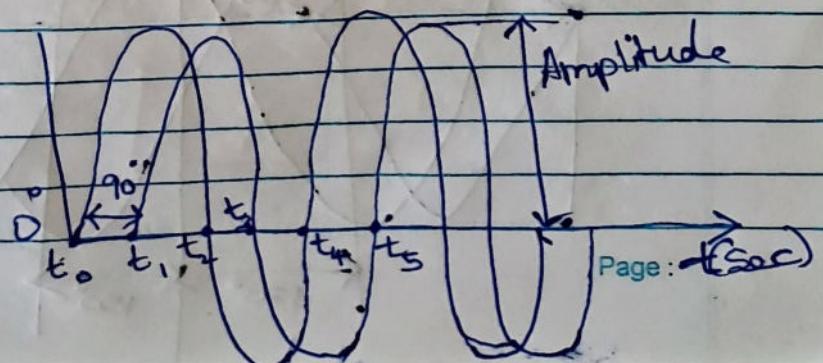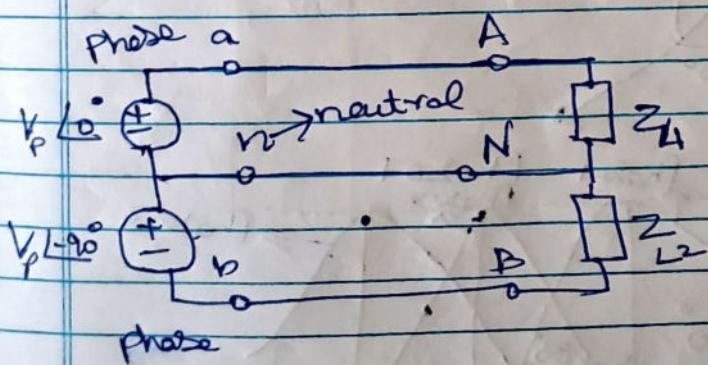- (ii) Two phase - Same frequency and the phase angle difference between the phases are 90° .



(iii)

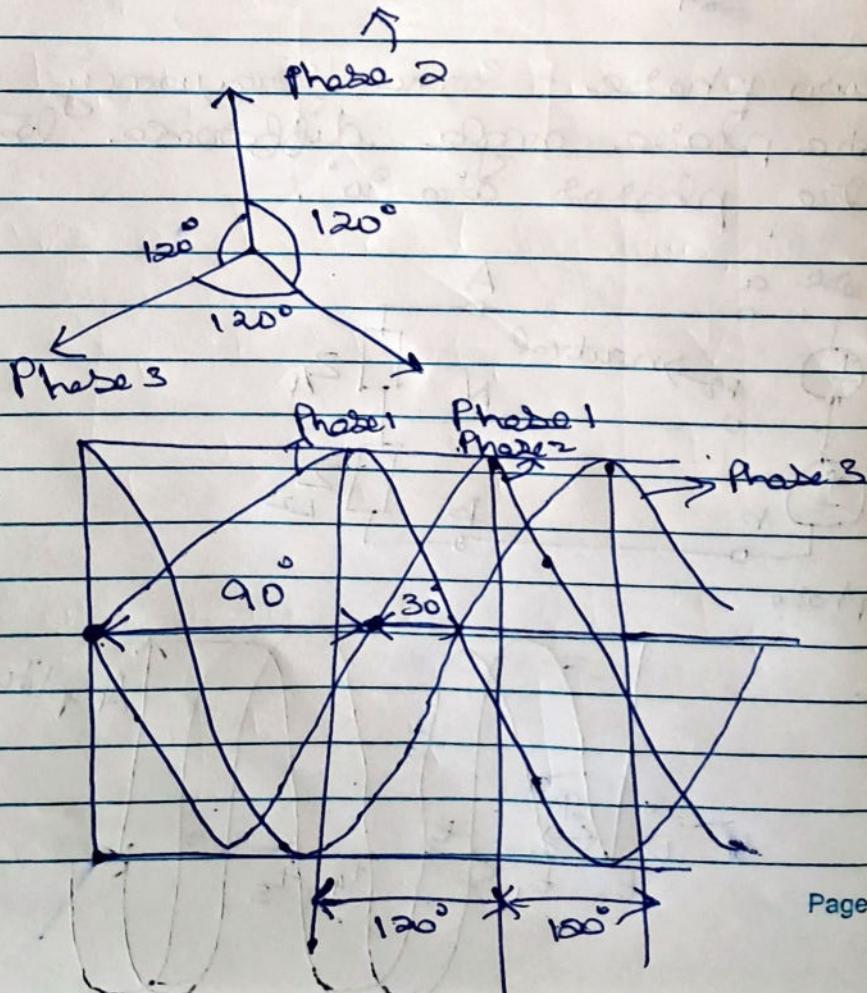
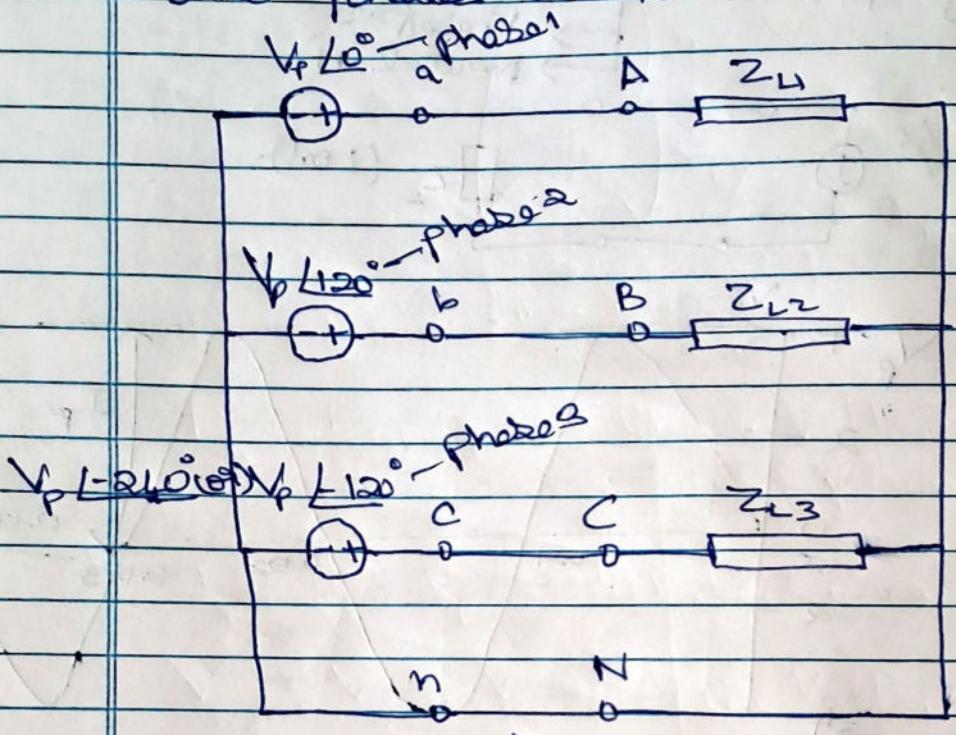
Three phase - same frequency and the phase angle difference between the phases are 120° .



Balanced three phase Systems.


Star (wye) connection (Δ)

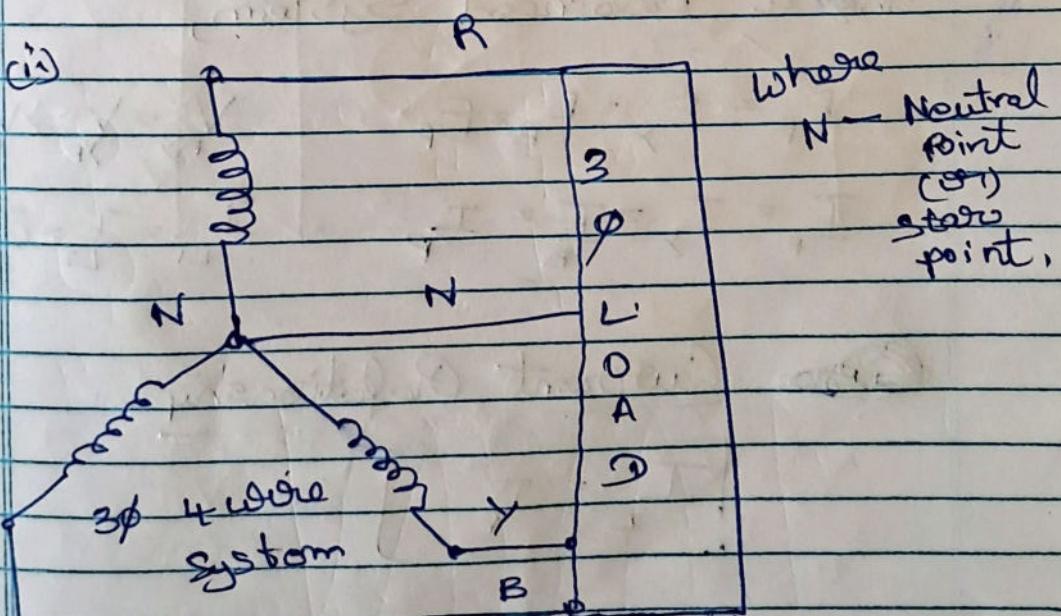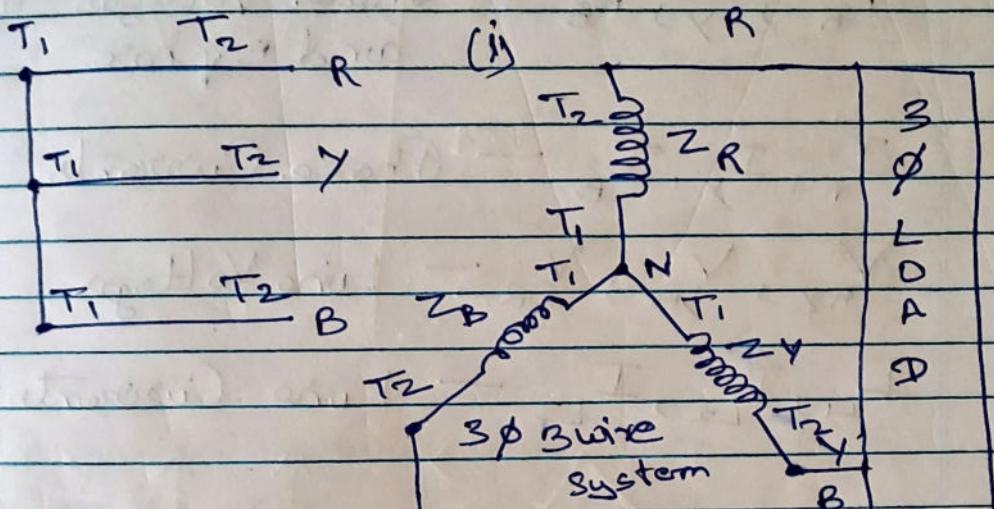- Three wire system.
- Four wire system.
- The phase angle difference b/w each phase is 120° .
- All the three phase voltages have the same amplitude, same period and frequency.



Voltage & Current relationships

(i) Y - 3 phase system

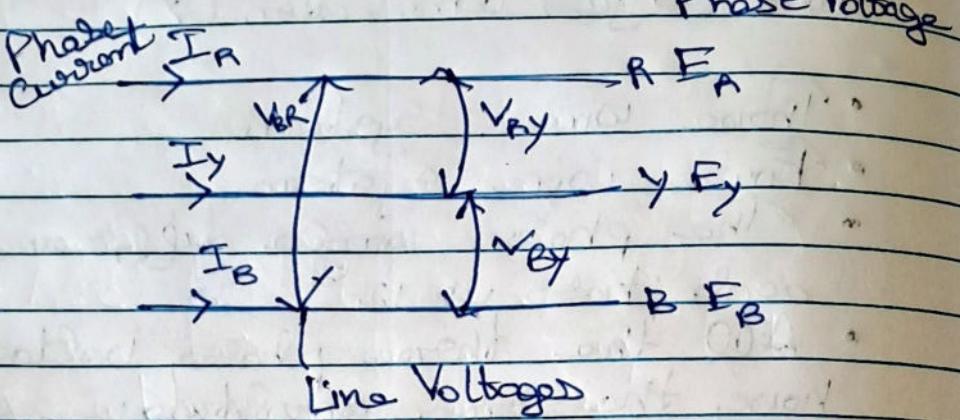

E_R , E_Y , E_B — Phase Voltages of R, Y and B phase.

I_R , I_Y , I_B — Phase Currents.

V_{RY} , V_{YB} , V_{BR} — Line Voltages.

I_{L1} , I_{L2} , I_{L3} — Line Currents (load)

Taking a balanced System,

$$E_R = E_Y = E_B = E_p$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$


$$I_R = I_Y = I_B = I_p$$

$$I_{L1} = I_{L2} = I_{L3} = I_L$$



Current Relationship:

$$I_L = I_p$$

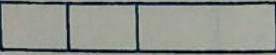

Voltage Relationship:

$$V_L = \sqrt{3} E_p$$

Power Relationship:

Let $\cos\phi$ be the power factor.

Power consumed in 1 phase = $E_p I_p \cos\phi$

(line
real/active)

Power consumed in 3 phases = $3E_p I_p \cos\phi$
 $= \sqrt{3} V_L I_L \cos\phi$ (total)

Reactive power in 1 phase = $E_p I_p \sin\phi$

Total reactive power = $3E_p I_p \sin\phi$
 $= \sqrt{3} V_L I_L \sin\phi$ (VAR)

(complex)
Total Apparent power per phase = $E_p I_p$



Total apparent power = $3E_p I_p$

(VA)

$$\sqrt{3} V_L I_L$$
 (Volt Amp)

Balanced three phase Systems. Delta (mesh) connection (Δ)

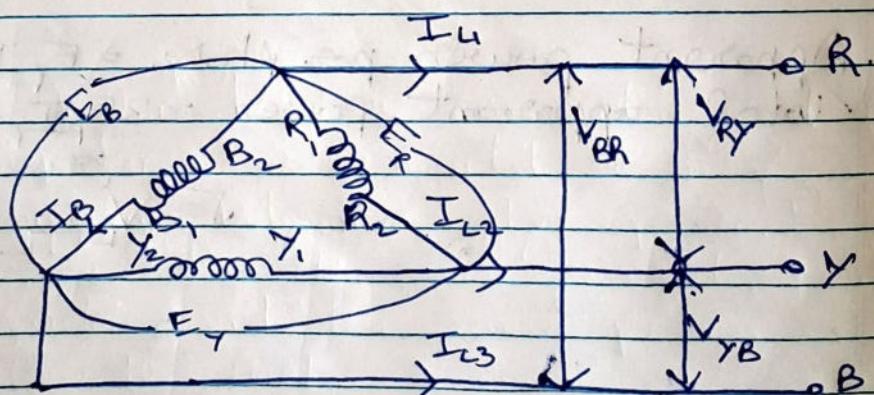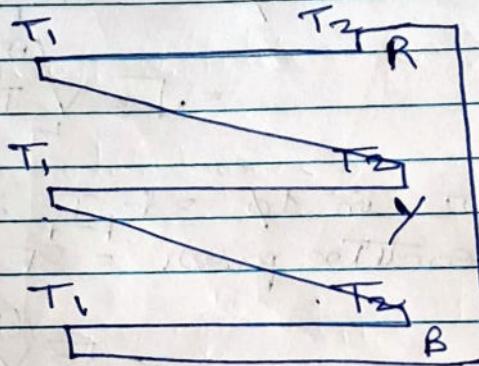- Three wire System
- The phase angle difference b/w each phase is 120° .
- All the three phases voltages have the same amplitude, same period and frequency.



Here;

$$E_R = E_Y = E_B = E_p; \text{ phase voltage}$$

$$I_R = I_Y = I_B = I_p; \text{ phase current.}$$

$$V_{RY} = V_{YB} = V_{BR} = V_p; \text{ line Voltage}$$

$$I_U = I_V = I_W = I_L = I; \text{ line Current}$$

Voltage Relationship:

$$E_p = V_L$$

Current Relationship:

$$I_L = \sqrt{3} I_p$$

Power Relationship:

Let $\cos\phi$ be the power factor;

$$\text{Power for } 1\phi = E_p I_p \cos\phi$$

$$\text{Total power for } 3\phi = 3E_p I_p \cos\phi$$

(Q3)

$$\sqrt{3} V_L I_L \cos\phi \text{ (Watts)}$$

$$\text{Reactive power in } 1\phi = E_p I_p \sin\phi$$

$$\text{Total reactive power for } 3\phi = 3E_p I_p \sin\phi$$

$$\sqrt{3} V_L I_L \sin\phi \text{ (VAR)}$$

$$\text{Apparent power for } 1\phi = E_p I_p$$

$$\text{Total apparent power} = 3E_p I_p$$

$$\sqrt{3} V_L I_L \text{ (Volt Amp)}$$

Star

Y

Current $I_L = I_p$

Voltage $V_L = \sqrt{3} \times E_p$

Delta (Mesh)

$$I_L = \sqrt{3} \times I_p$$

$$V_L = E_p$$

Similarities are:

3) True/Real/Active Power $\Rightarrow 3E_p I_p \cos(\theta) \sqrt{3} V_L I_{\text{avg}}$ (Watts)

4) Reactive Power $\Rightarrow 3E_p I_p \sin(\theta) \sqrt{3} V_L I_{\text{avg}}$ (VAR)

5) Total/Complex Apparent Power $\Rightarrow E_p \times I_p$ (VA)

Ex: A balanced star connected load of $3 + j4$ impedance is connected to $400\sqrt{3}$ 3-phase supply. Determine the phase voltage, phase current, line current, power factor and the real power consumed by the load.

Sol: Y-connected system;

$$V_L = \sqrt{3} \times E_p \Rightarrow 400 = \sqrt{3} \times E_p \Rightarrow E_p = 230.9 \text{ V}$$

$$I_p = \frac{E_p}{Z}; Z = 3 + j4 \Rightarrow Z = 5 \angle 53.1^\circ$$

$$T_p = \frac{230.9 / 0}{5 / 53.1^\circ} = \underline{\underline{46.18 / -53.1^\circ A}}$$

$$\cos \phi = \cos 53.1^\circ = 0.6 \text{ lagging}$$

$$I_L = I_p = 46.18 / -53.1^\circ A$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos \phi = \sqrt{3} \times 400 \times 46.18 \times 0.6 = 19196.66 W$$

Ex 2) A 3-phase balanced wye connected load has 400V line to line voltage and 10A line current. Determine the line to neutral voltage and phase current. ($N = \text{Neutral}$)

Sol:

$V_L = 400V$	$(V_{RN} = V_{YN} = V_{BN} = \text{Phase Voltage})$
$E_p = 230.9V$	$(E_p \text{ is also known as line to Neutral voltage})$
$I_L = 10A$	
$I_p = 10A$	

Ex 3) A balanced delta connected load of $(4 + j6)\Omega$ impedance is connected to 415V, 50Hz, 3-phase supply. Determine the phase voltage (E_p), phase current (I_p), line current (I_L), power factor and the real power consumed by the load.

Sol:

$$E_p = V_L = 415V$$

$$I_p = \frac{I_L}{\sqrt{3}} \Rightarrow T_p = \frac{E_p}{Z} = \frac{415}{4 + j6} = 57.5 / 56.3^\circ A$$

$$I_L = \sqrt{3} \times I_p = \sqrt{3} \times 57.5 = 99.6A$$

$$\cos \phi = \cos 56.3^\circ = 0.5$$

$$P = \sqrt{3} \times 120 \text{ V} \times I_L \cos \phi = 35.7 \text{ kW}$$

Ex: When 3 balanced impedances are connected in delta across a 3 phase, 400V, 50Hz supply, the line current drawn is 20A at a lagging power factor of 0.3. Determine the impedance connected in each phase.

$$\text{Sol: } Z = \frac{E_p / 0^\circ}{I_p L \phi}$$

$$\phi = \cos^{-1} 0.3 = -72.542^\circ$$

$$Z = \frac{400 / 0^\circ}{11.547 / -72.542^\circ}$$

$$Z = 34.641 / 72.542^\circ$$

$$Z = 10.393 + j 33.045$$