

## Module 2 : AC Circuits

6 Hrs

Alternating voltages and currents, RMS, average, form factor, peak factor; Single phase RL, RC, RLC series and **parallel circuits**; Power and power factor; **Balanced three phase systems**

### Course Outcome

- Evaluate AC circuit parameters using laws

## Simple problems

A balanced star connected load of  $3+j4$  impedance is connected to 400 V, 3-phase supply. Determine the phase voltage, phase current, line current, power factor and the real power consumed by the load



## Simple problems

A 3-phase balanced wye connected load has 400 V line to line voltage and 10 A line current. Determine the line to neutral voltage and phase current.

## Simple problems

A balanced delta connected load of  $(4+j6)\Omega$  impedance is connected to 415 V, 50 Hz, 3-phase supply. Determine the phase voltage, phase current, line current, power factor and the real power consumed by the load.



## Simple problems


When 3 balanced impedances are connected in delta across a 3-phase, 400 V, 50 Hz supply, the line current drawn is 20 A at a lagging power factor of 0.3. Determine the impedance connected in each phase.





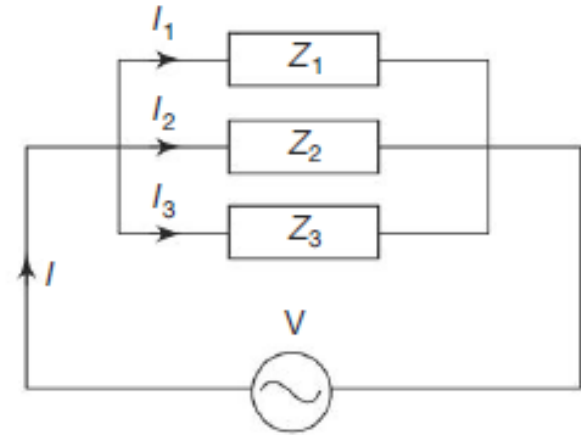
# Admittance and its components


- Admittance of a circuit is defined as reciprocal of impedance.
- $Z = R + jX_L$
- $Y = 1/Z$



# Admittance and its components

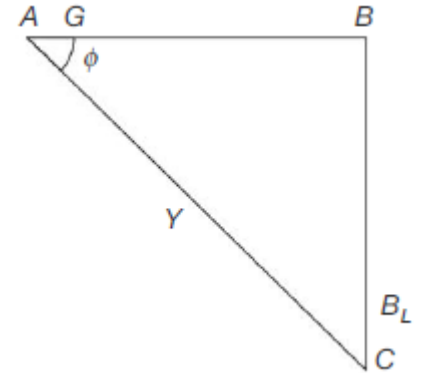

# Simple parallel circuits

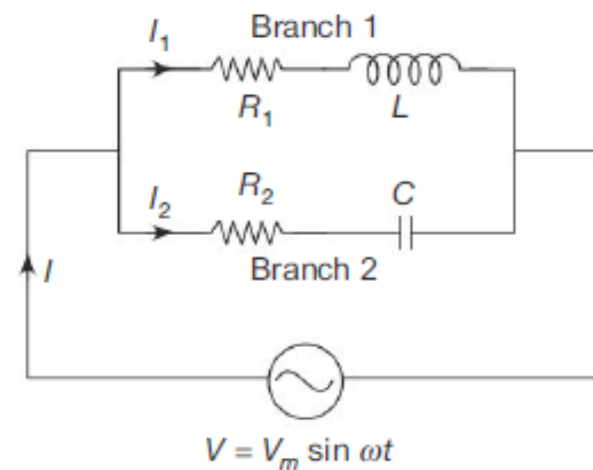

# Simple parallel circuits

