

POWER IN AC CIRCUITS

1. Instantaneous Power.

$$\text{If } v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$\text{then } p(t) = v(t) \cdot i(t).$$

$$= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\text{using } \cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$p(t) = \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


$$+ \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

sinusoidal.

twice the frequency
of $v(t)$, $i(t)$

Constant - independent of ω , t .
depends of $(\theta_v - \theta_i)$

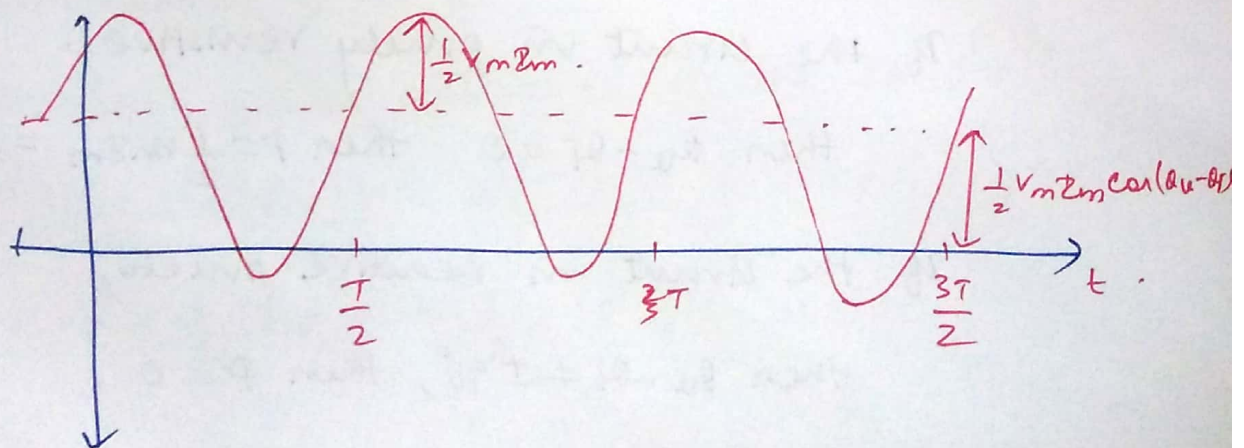Instantaneous power is different to mean.



②

2. Average Power.

- Average of the instantaneous power over one period.
- measured in wattmeter. unit is WATTS.

$$\text{average power } P = \frac{1}{T} \int_0^T p(t) dt.$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i).$$

If P is calculated using phasors -

$$V = V_m \angle \theta_v \quad I = I_m \angle \theta_i.$$

$$\frac{1}{2} V I^* = \frac{1}{2} V_m I_m \angle \theta_v - \theta_i$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

$$P = \frac{1}{2} \text{Real}\{V I^*\}.$$

As $\theta_v - \theta_i$ is the angle between voltage and current,

If the circuit is purely resistive,

$$\text{then } \theta_v - \theta_i = 0 \quad \text{then } P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R.$$

If the circuit is reactive purely,

$$\text{then } \theta_v - \theta_i = \pm 90^\circ, \text{ then } P = 0.$$

Resistive - absorbs real power.

Reactive circuit - absorbs zero real power.

Example.

$$\textcircled{1} \quad u(t) = 330 \cos(10t + 20^\circ) \text{ V}$$

$$\begin{array}{c} \text{cos} \\ \swarrow \\ \text{sin} \searrow -90^\circ \end{array}$$

$$i(t) = 33 \sin(10t + 60^\circ) \text{ A} = 33 \cos(10t - 30^\circ)$$

Instantaneous power.

$$p(t) = u(t)i(t).$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{1}{2} \times 330 \times 33 \times \cos(20 - 30^\circ)$$

$$+ \frac{1}{2} 330 \times 33 \times \cos(20t + 20 - 30^\circ)$$

$$= 5445 \cos(-10^\circ) + 5445 \cos(20t - 10^\circ)$$

$$p(t) = \underline{\underline{5362}} + 5445 \cos(2t - 10^\circ).$$

$$\text{Average power} = 5362 \text{ W}.$$

$\textcircled{2}$ A current $I = 33 \angle 30^\circ \text{ A}$ flows through an impedance of $Z = 40 \angle -22^\circ \Omega$.

Average power delivered to the load = ?


$$Z = R + jX = 40 \angle -22^\circ = 3.7087 - 1.498j$$

$$P = \frac{1}{2} |I_m|^2 R = \frac{1}{2} \times 33^2 \times 3.7087$$

$$P = 2019.387 \text{ W}$$

$$P = 2.019 \text{ kW}.$$

④

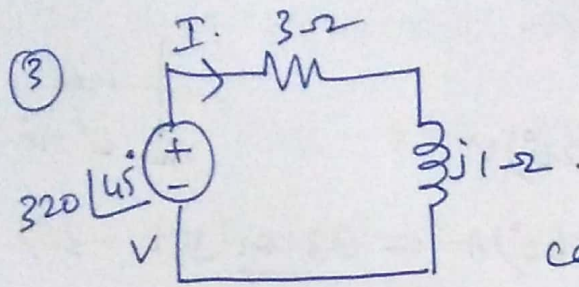

calculate power supplied by vt-source.

power absorbed by resistor & inductor = ?

$$I = \frac{V}{Z} = \frac{320 \angle 45^\circ}{3 + j1} = 101.19 \angle 26.56^\circ$$

$$V = 320 \angle 45^\circ \quad I = 101.19 \angle 26.56^\circ$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \times 320 \times 101.19 \cos(45 - 26.56^\circ)$$

power supplied by source $\Rightarrow P = 15359.11 \text{ W}$

power absorbed by resistor = $\frac{1}{2} |I|^2 R$

$$= \frac{1}{2} \times 101.19^2 \times 3$$

$$= \frac{1}{2} \times 15359.12 \text{ W}$$

power absorbed by inductor = 0 W.


power supplied by the vt-source = power absorbed by the resistor.

No real power absorbed by inductor.

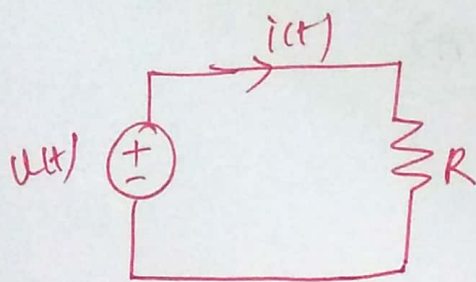3. RMS / EFFECTIVE VALUE.


RMS - Root Mean Square Value

It is the dc current that delivers the same average power to the resistor as the periodic current.



ac

$$P = \frac{1}{T} \int_0^T i^2 R dt$$

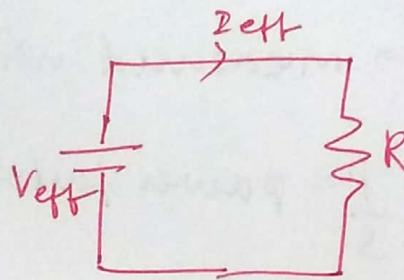

dc.

$$P = I_{eff}^2 R$$

Equating both we get.

$$I_{eff}^2 = \frac{1}{T} \int_0^T i^2 dt$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

Similarly

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2 dt} = V_{rms}$$

For a Sine wave,

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1 + \cos 2\omega t}{2} dt} = \frac{I_m}{\sqrt{2}}$$

$$\text{and } V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

⑥

$$P = V_{rms} I_{rms} \cos(\theta_u - \theta_i).$$

4. Apparent power & POWER FACTOR

defined as $S = V_{rms} I_{rms}$.

angle $\cos(\theta_u - \theta_i) = \text{power factor}$.

$$P = S \times \text{power factor} = V_{rms} I_{rms} \cos(\theta_u - \theta_i).$$

$S \rightarrow$ measured in (VA)

$$\frac{P}{S} = \text{power factor}.$$

$$\text{Impedance } Z = \frac{V}{I} = \frac{V_m}{I_m} \angle \theta_u - \theta_i.$$

\therefore load angle = power factor angle.

5. Complex Power

$$S = V_{rms} I_{rms}^* \quad (\text{defined quantity})$$

$$\text{where, } V_{rms} = \frac{V_m}{\sqrt{2}}, \text{ and } I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_u - \theta_i)} + j V_{rms} I_{rms} \sin(\theta_u - \theta_i)$$

\downarrow
apparent power (magnitude of S).

$$S = P + jQ.$$

$$P = V_{rms} I_{rms} \cos(\theta_u - \theta_i) \Rightarrow \text{Real power (W)}$$

$$Q = V_{rms} I_{rms} \sin(\theta_u - \theta_i) \Rightarrow \text{Reactive power (VAR)}$$

Intenn of Impedance

$$Z = R + jX$$


$$S = I_{rms}^2 Z = I_{rms}^2 R + j I_{rms}^2 X$$

$$P = I_{rms}^2 R \quad Q = I_{rms}^2 X$$


Note:

$P=0$ for reactive loads. $V_{rms} I_{rms} \sin(\theta_u - \theta_i)$
 $Q=0$ for resistive loads. $V_{rms} I_{rms} \cos(\theta_u - \theta_i)$

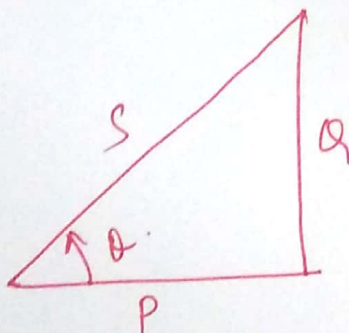All these quantities can be related in a power/impedance triangle.



$$\cos \theta = \frac{P}{S}$$

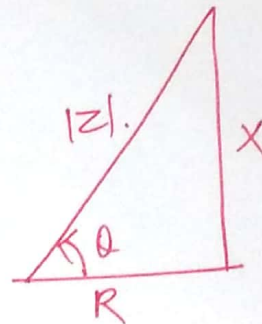

$$\cos \theta = \frac{R}{|Z|}$$