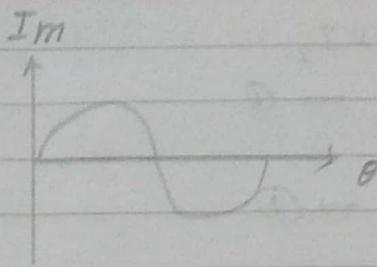



Module 2

classmate
Date _____
Page _____




$$\rightarrow \frac{E}{V} = E_m \sin \omega t \\ i = I_m \sin \omega t \\ \text{phase angle} = 0$$
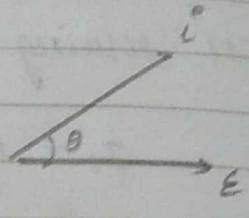
$$\rightarrow E = E_m \sin \omega t \\ i = I_m \sin(\omega t + \theta) \\ \downarrow$$




current leads voltage by an angle θ .
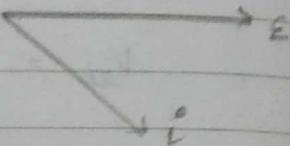
$$\rightarrow E = E_m \sin \omega t \\ i = I_m \sin(\omega t - \theta) \\ \downarrow$$



current lags voltage by an angle θ .

pure resistive

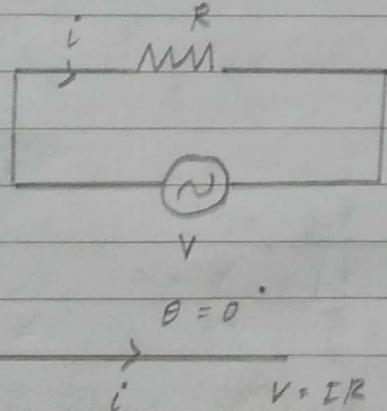

$$V = V_m \sin \omega t$$

$$i = \frac{V}{R}$$

$$= \frac{V_m \sin \omega t}{R}$$

$$i = I_m \sin \omega t$$

$$Z = \frac{V}{i} = \frac{V_m \sin \omega t}{I_m \sin \omega t} = \frac{V_m}{I_m / R} = R$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$


In polar form,

$$V = |V| \angle 0^\circ$$

$$I = |I| \angle 0^\circ$$

$$Z = R \angle 0^\circ = Z \angle 0^\circ$$


pure
inductive

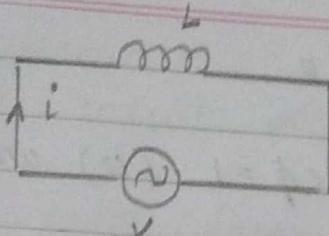

$$V = V_m \sin \omega t$$

$$V = L di/dt$$
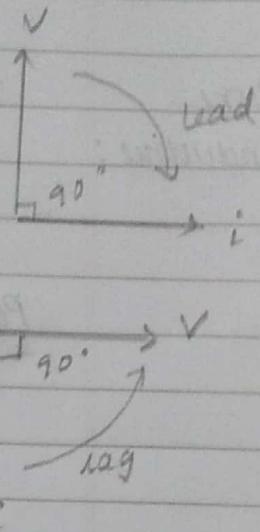
$$\begin{aligned} i &= \frac{1}{L} \int V dt \\ &= \frac{1}{L} \int V_m \sin \omega t dt \\ &= \frac{V_m}{L} \left(-\frac{\cos \omega t}{\omega} \right) \\ i &= I_m \sin(\omega t - \pi/2) \end{aligned}$$



current lags voltage by $\pi/2$.

$$\begin{aligned} \text{pure resistive: Instantaneous power} &= V \times i \\ &= V_m \sin \omega t \cdot I_m \sin \omega t \\ &= V_m I_m \sin^2 \omega t \\ &= V_m I_m \left(\frac{1 - \cos 2\omega t}{2} \right) \end{aligned}$$

when $\theta = \omega t = \pi/2$ we get max. power

$$\begin{aligned} &= V_m I_m \left(\frac{1 - (-1)}{2} \right) \\ &= V_m I_m \end{aligned}$$

$$\begin{aligned} \text{Average power } P &= \frac{1}{\pi} \int_0^\pi V \cdot i d\omega \\ &= \frac{1}{\pi} \int_0^\pi V_m I_m \left(\frac{1 - \cos 2\omega}{2} \right) d\omega \\ &= \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} I_{rms} \end{aligned}$$

phase angle $\phi = 0$

power factor $\cos \phi = 1$ (ie) unity

Pure inductive:

$$Z = \frac{V_m}{I_m} = \frac{V_m}{V_m / \omega L} = \omega L = X_L$$

↓
inductive reactance

Polar representation,

$$V = |V| \angle 0^\circ$$

$$I = |I| \angle -\pi/2$$

$$Z = |Z| \angle \pi/2$$

$$= X_L \angle \pi/2 = j X_L$$

$$Z_1 = a + jb \quad Z_1 = V_1 \angle \theta_1$$

$$Z_2 = c + jd \quad Z_2 = V_2 \angle \theta_2$$

rectangular

polar

can be + (or) -

can be x (or) +

$$\frac{Z_1}{Z_2} = \frac{V_1}{V_2} \angle \theta_1 - \theta_2$$

$$Z_1 Z_2 = V_1 V_2 \angle \theta_1 + \theta_2$$

Avg. power = 0

phase angle $\phi = 90^\circ$

Lagging power factor $\cos \phi = 0$

$$v = V_m \sin \omega t$$

$$i = I_m \cos \omega t$$

pure
capacitive

current leads voltage by 90°

polar form,

$$v = |V| \angle 0^\circ$$

$$I = |I| \angle \frac{\pi}{2}$$

$$Z = |Z| \angle -\frac{\pi}{2}$$

$$Z = -j X_c$$

$$\text{Instantaneous power} = \frac{V_m I_m \sin \omega t}{2}$$

$$\text{Average power} = 0$$

$$\phi = \frac{\pi}{2} \quad \begin{matrix} \text{leading} \\ \text{power factor} = 0 \end{matrix}$$

polar form (\times and \div)

$$A \angle \theta \times B \angle \phi = AB \angle \theta + \phi$$

$$A \angle \theta \div B \angle \phi = \frac{A}{B} \angle \theta - \phi$$

rectangular form (+ and -)

$$(A + jB) + (C + jD) = (A + C) + j(B + D)$$

$$(A + jB) - (C + jD) = (A - C) + j(B - D)$$

Phasor algebra:

R , X_L , X_C in rectangular form

$$Z_R = R + j0$$

$$Z_L = 0 + jX_L$$

$$Z_C = 0 - jX_C$$

R , X_L , X_C in polar form

$$Z_R = R \angle 0^\circ$$

$$Z_L = X_L \angle 90^\circ$$

$$Z_C = X_C \angle -90^\circ$$

polar form: shift + pol(10, 16) = r value $\rightarrow 18.027$
θ value $\rightarrow 56.31$

rectangular form: shift - rec(18.02, 56.31) = $x = 10$
 $y = 16$

Write result in polar form:

$$10 \angle 60^\circ + 8 \angle 45^\circ$$

Polar forms cannot be added. so first convert each into rectangular form, add it and convert the final answer to polar form.

$$\therefore \underline{\text{Ans.}}: 11.07 \angle 15.72^\circ$$

1. $Z_1 = 10 + j10$ and $Z_2 = 20 - j30$ are in series
Find Z_T in polar form.

$$\begin{aligned} Z_T &= Z_1 + Z_2 \\ &= 30 - j20 \\ &= 36.1 \angle -33.7^\circ \end{aligned}$$

2. The total impedance of a circuit in which Z_1 , Z_2 are in series is equal $(30 + j40)$ Ω .
 $Z_1 = (20 + j60)$ Ω . Find Z_2 .

$$\begin{aligned} Z_T &= Z_1 + Z_2 \\ Z_2 &= Z_T - Z_1 \\ &= 10 - j20 \text{ (rectangular form)} \\ &= 22.36 \angle -63.43^\circ \text{ (polar form)} \end{aligned}$$

3. In a given circuit $I = 10 \angle 60^\circ$, $Z = 20 \angle 30^\circ$.
Find V .

$$\begin{aligned} V &= IZ \\ &= (10 \times 20) \angle 60 + 30^\circ \\ &= 200 \angle 90^\circ \end{aligned}$$



~~W.K.T. $Z_L = 0 + jX_L$~~

$$X_L = 0 \quad Y = 200 \quad \therefore Z_L = 0 + j200$$

If we have $V = 200 \angle -90^\circ$,

$$Z_L = 0 - j200$$


4. In a circuit $V = 200V$ $I = 10 \angle 30^\circ$.
 Find Z both in polar and rectangular form.

$$I = \frac{V}{Z}$$

$$Z = \frac{V}{I} = \frac{200 \angle 0^\circ}{10 \angle 30^\circ} = 20 \angle -30^\circ$$

$$= 17.32 - 10j$$

RL series circuit

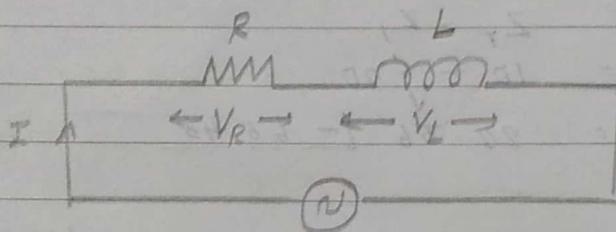

$V = V_m \sin \omega t$ - applied voltage

i = instantaneous current


f = frequency

Voltage across resistor $R = V_R = IR$

Voltage across inductor $L = jIX_L = V_L$


$$\begin{aligned} V &= V_R + V_L \\ &= TR + jIX_L \\ &= I(R + jX_L) \end{aligned}$$

$$\frac{V}{I} = R + jX_L = Z$$

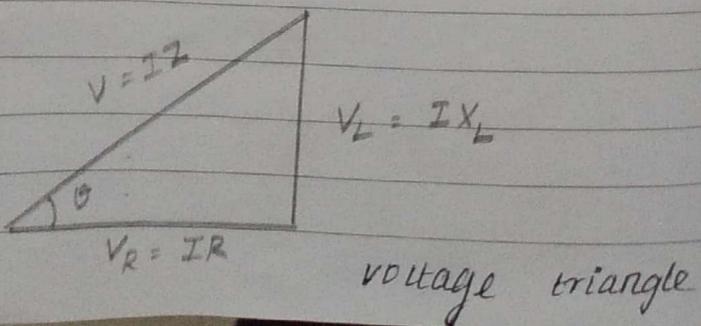

$$Z = R + jX_L \quad |Z| = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$

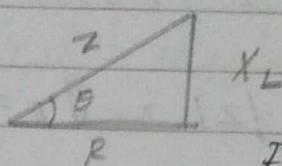

Impedance
Δz

$$\text{power factor} = \cos \phi = \frac{R}{Z}$$

From the impedance Δz,

$$\cos \phi = \frac{R}{Z} \quad (\text{or}) \quad \cos \left[\tan^{-1} \left(\frac{X_L}{R} \right) \right]$$

Hence I lags the voltage, power factor is also lagging.

$$\begin{aligned} \text{Active power (or) real power} &= VI \cos \phi \\ &= VI \cdot \left(\frac{R}{Z} \right) \\ &= \frac{V}{Z} IR = I^2 R \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= VI \sin \phi \\ &= VI \cdot \frac{X_L}{Z} = I^2 X_L \end{aligned}$$

1. A coil having a resistance of 10Ω and an inductance of 0.01H is connected across a 220V, 50Hz supply. calculate
 - a) current
 - b) phase angle b/w current and voltage
 - c) P.F
 - d) Power

$$V = 220 \text{ V} \quad R = 10 \Omega \quad f = 50 \text{ Hz}$$

$$L = 0.01 \text{ H} \quad X_L = 2\pi f L = 3.141 \Omega$$

$$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 3.14^2} \\ = 10.48 \Omega$$


a) current $I = \frac{V}{Z} = \frac{220}{10.48} = 20.99 \text{ A}$

b) $\phi = \tan^{-1} \frac{X_L}{R} = \frac{3.141}{10} = 17.43^\circ (\text{lag})$

c) PF = $\cos \phi = 0.954 (\text{lag})$

d) power = $V I \cos \phi$
 $= 220 \times 20.99 \times 0.954$
 $= 4406.2 \text{ W}$

RC Series circuit

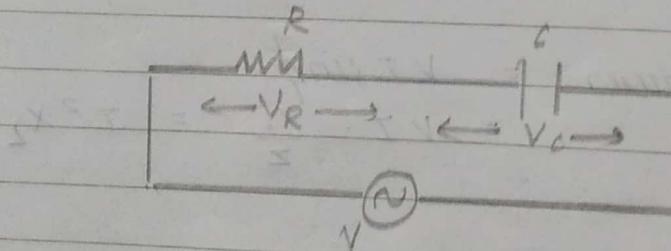


$$V = V_m \sin \omega t$$

i = instantaneous current

f = frequency

$$V_R = IR$$

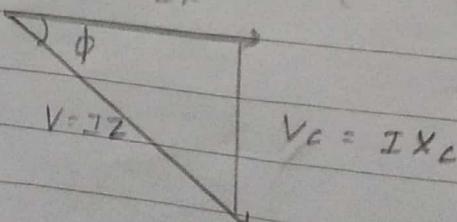

Voltage across $R = V_R = IR$ in phase with I

Voltage across $C = V_C = IX_C$ lagging I by 90°

$$V = V_R + V_C$$

voltage triangle,


$$V = IR - jIX_C = I(R - jX_C)$$

$$\frac{V}{I} = R - jX_C = z$$

$$|z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{1/C\omega C}{R} = \tan^{-1} \frac{1}{\omega CR}$$

ϕ = phase angle

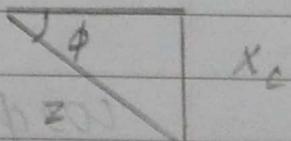

$$z = R - jX_C = |z| \angle -\phi$$

$$PF = \cos \phi = R/z$$

Active power = $VI \cos \phi$ (Watt)

Reactive power = $VI \sin \phi$ (volt Amp.)

R, C

Find the circuit constants of a two element series circuit which consumes 700 W with 0.707 leading PF. The applied voltage is $V = 141.4 \sin 314t$

$$V_m = 141.4$$

$$V_{rms} = \frac{141.4}{\sqrt{2}} = 99.98 \text{ V}$$

$$\cos \phi = 0.707 \text{ (leading)}$$

$$\text{power} = VI \cos \phi$$

$$700 = 99.98 \times I \times 0.707$$

$$I = 9.9 \text{ A}$$

$$Z = \frac{V}{I} = \frac{99.98}{9.9} = 10.09 \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$\begin{aligned} R &= Z \cos \phi \\ &= 10.09 \times 0.707 \\ R &= 7.13 \Omega \end{aligned}$$

$$\phi = \cos^{-1} 0.707 = 45^\circ$$

$$\sin \phi = \frac{X_C}{Z} \Rightarrow X_C = Z \sin \phi$$

$$\begin{aligned} X_C &= 10.09 \times \sin 45^\circ \\ &= 10.09 \times 0.707 \end{aligned}$$


$$X_C = 7.13 \Omega$$

$$X_C = 1/2\pi f C$$

$$C = \frac{1}{2\pi X_C} = 446.64 \mu F$$

RLC circuit

CLASSMATE
Date _____
Page _____

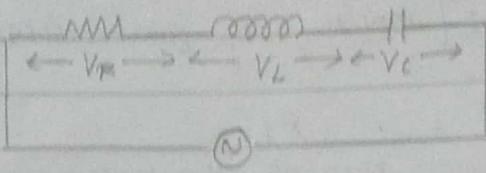

$$V = V_m \sin \omega t$$

$$V_R = IR$$

$$V_L = jIX_L = IX_L \angle 90^\circ$$

$$V_C = -jIX_C = IX_C \angle -90^\circ$$

$$V = V_R + V_L + V_C$$

$$= IR + IjX_L - IjX_C$$

$$= I(R + j(X_L - X_C))$$

$$\frac{V}{I} = Z = R + j(X_L - X_C)$$

$$= |Z| \angle \phi$$


$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

2 cases: If $X_L > X_C \rightarrow$ inductive circuit
 (R_L)

If $X_C > X_L \rightarrow$ capacitive circuit
 (R_C)


$$X_L > X_C$$

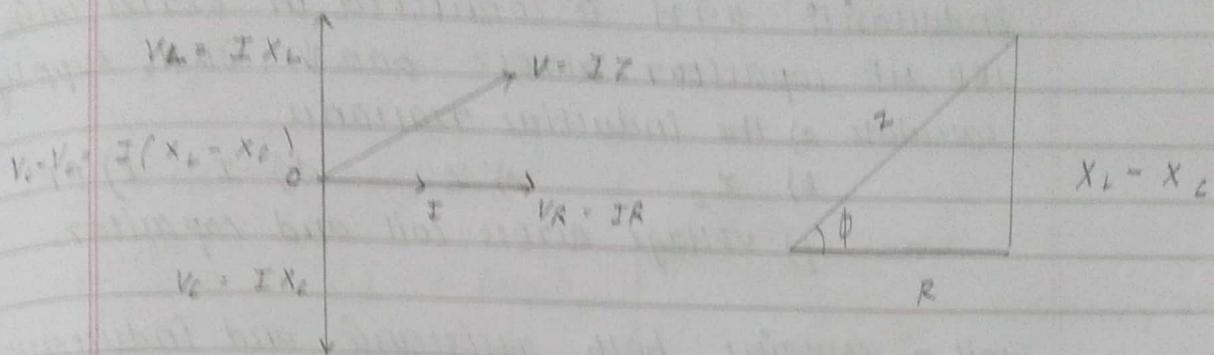

$$\tan \phi = \frac{X_L - X_C}{R} = \frac{V_{LC} - V_{RC}}{R}$$

$$\cos \phi = \text{Power factor} = \frac{R}{Z}$$

$$X_C > X_L$$

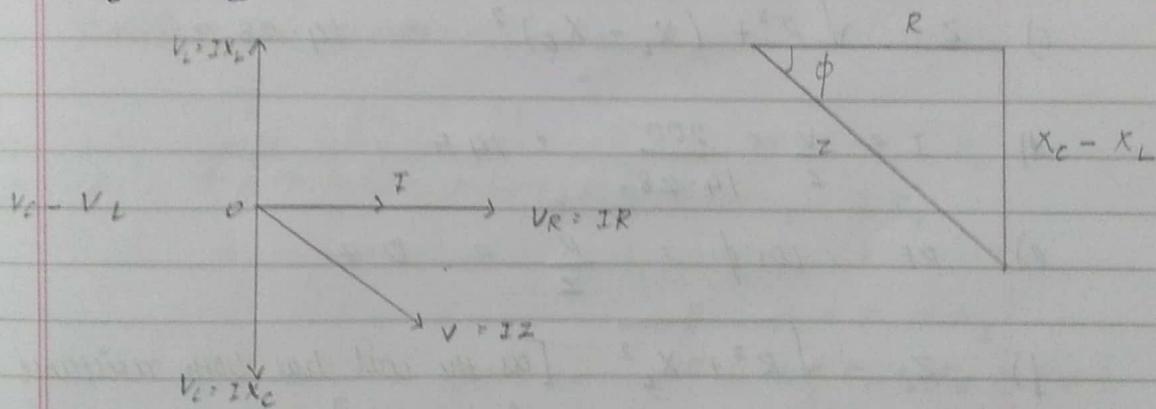

$$\tan \phi = \frac{X_C - X_L}{R} = \frac{V_{RC} - V_{LC}}{R}$$

$$P_f = \cos \phi = \frac{R}{Z}$$

$$\text{Actual power} = VI \cos \phi$$

$$\text{Reactive power} = VI \sin \phi$$

1. A coil of resistance 10 ohm and an inductor of inductance 0.1 H is connected in series with 150 μF capacitor across 200 V, 50 Hz supply calculate
 a) the inductive reactance
 b) X_L c) Z d) I e) PF
 f) voltage across coil and capacitor.

coil - contains both resistance and inductance

$$a) X_L = 2\pi f L = 314 \times 0.1 = 31.4 \Omega$$

$$b) X_C = \frac{1}{2\pi f C} = \frac{10^6}{314 \times 150} = \frac{10^6}{47100} = \frac{10^4}{471} = 21.23 \Omega$$


$$c) Z = \sqrt{R^2 + (X_L - X_C)^2} = 14.28 \Omega$$

$$d) I = \frac{V}{Z} = \frac{200}{14.28} = 14 A$$

$$e) PF = \cos \phi = \frac{R}{Z} = 0.7$$

$$f) Z_L = \sqrt{R^2 + X_L^2} \quad [\text{as the coil has both resistance and inductance}]$$


$$Z_L = 32.97$$

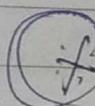 $V_{\text{coil}} = IZ_L = I\sqrt{R^2 + X_L^2} = 461.6 V$

$$V_{\text{capa.}} = IX_C = 297.08 V$$

RMS, Average, Peak:


$V(0t) i$

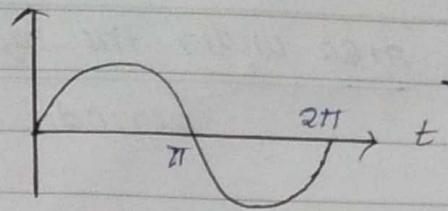


sinusoidal /
Alternating /
periodic wave form

Amplitude: Max. value of the graph.

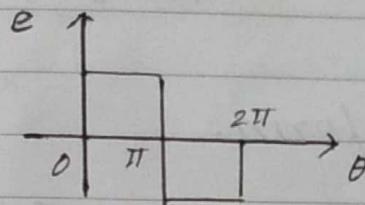
Frequency: NO. of cycles per second ($\frac{1}{T}$)
(Hertz)




rectangular

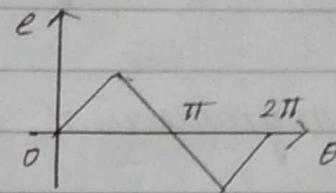


triangular

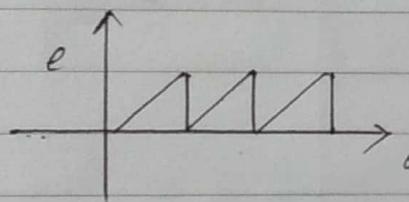

saw tooth

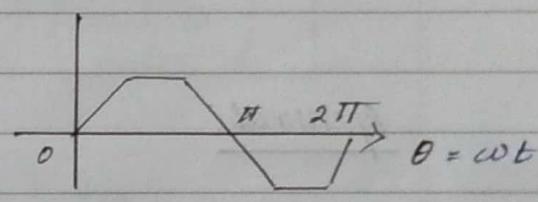

trapezoidal

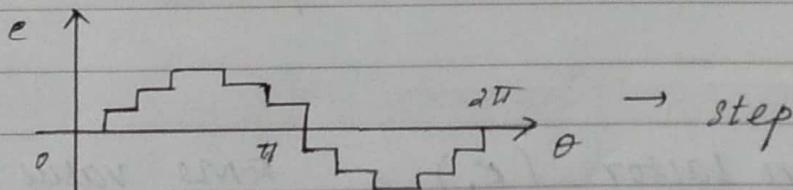

step

RMS:

Symmetrical wave form: (we consider only half cycle)

$$I_{RMS} = \sqrt{\frac{1}{T/2} \int_0^{T/2} i^2 dt} = \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 d\theta}$$

Unsymmetrical wave form: (we consider full cycle)

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 d\theta}$$

General:

$$\text{RMS value} = \sqrt{\frac{\text{Area under the square wave for one cycle}}{\text{period}}}$$

Average:

Symmetrical wave form:

$$I_{av} = \frac{1}{\pi} \int_0^{\pi} i d\theta = \frac{1}{T/2} \int_0^{T/2} i d\theta$$

Unsymmetrical wave form:

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} i d\theta = \frac{1}{T} \int_0^T i dt$$

General:

Ave value = Area under the curve for one cycle
period.


$$\rightarrow \text{Form factor } (K_f) = \frac{\text{RMS value}}{\text{Average value}}$$

$$\rightarrow \text{Peak factor } (K_p) = \frac{\text{Peak value}}{\text{RMS value}}$$

Conductance:

$$G = \frac{1}{R} = \frac{1}{V/I} = \frac{I}{V} \text{ or } (\text{mho/siemens})$$

$$G = \frac{I}{V} \Rightarrow V = \frac{I}{G}$$

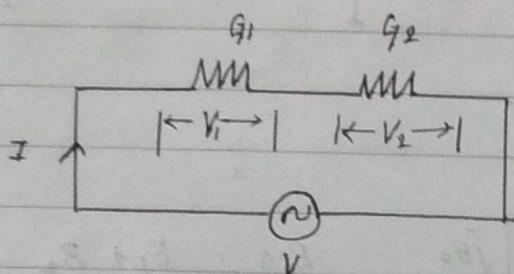series:

$$V_1 = I/G_1$$


$$V_2 = I/G_2$$

$$V_{\text{net}} = V_1 + V_2 = I \left(\frac{1}{G_1} + \frac{1}{G_2} \right)$$

$$V = I \left(\frac{G_1 + G_2}{G_1 G_2} \right)$$

$$I = \frac{V}{\left(\frac{G_1 + G_2}{G_1 G_2} \right)} = V G_{\text{eq}}$$

$$\frac{1}{G_{\text{eq}}} = \frac{1}{G_1} + \frac{1}{G_2}$$

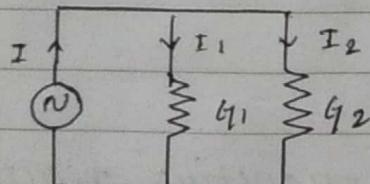Parallel:

$$I_1 = V G_1$$

$$I_2 = V G_2$$

$$I = I_1 + I_2$$

$$I = V G_1 + V G_2$$


$$G_{\text{eq}} = G_1 + G_2$$

Susceptance: (B)




→ Reciprocal of reactance (X) is susceptance

Series:

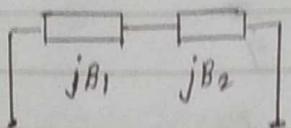

$$B_{eq} = \frac{B_1 B_2}{B_1 + B_2}$$

Parallel:

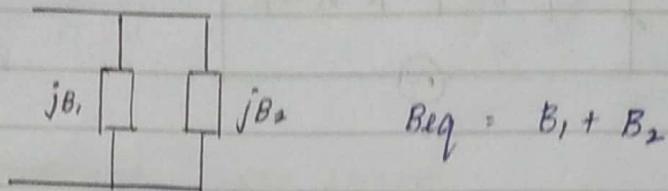

$$B_{eq} = B_1 + B_2$$

Impedance: (Z)

Series: $Z_{eq} = Z_1 + Z_2$

combination of resistance and reactance

Parallel: $Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$

$$Z = R + j X$$

$$Z = \sqrt{R^2 + X^2} \tan^{-1}(X/R)$$

Admittance: (Y or) \bar{y})

→ Reciprocal of impedance ($y = \frac{1}{Z}$)

$$y = g + j B$$

Inductive susceptance

$$\downarrow$$

$$B_L = \frac{1}{\omega L} = \frac{1}{j X_L}$$

Capacitive susceptance

$$\downarrow$$

$$B_C = c \omega$$

Inductive reactance

$$\downarrow$$

$$X_L = L \omega$$

Capacitive reactance

$$\downarrow$$

$$X_C = \frac{1}{c \omega}$$

series: $Y_{eq} = \frac{Y_1 Y_2}{Y_1 + Y_2}$

parallel: $Y_{eq} = Y_1 + Y_2$


 If circuit is pure L, $B = -B_L$

If circuit is pure C, $B = B_C$


Combination of L and C, $B = B_C - B_L$

$$y = G + jB = \sqrt{G^2 + B^2} \quad [\tan^{-1} B/G] \\ = |y| \angle$$

Graph:

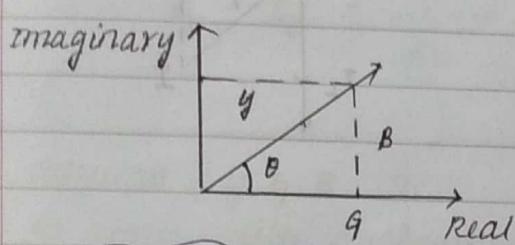


Admittance

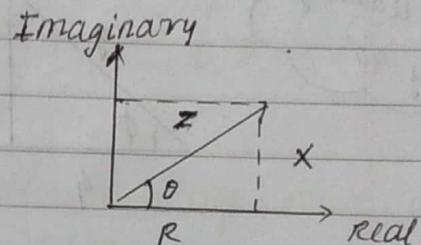

Impedance

RL Parallel circuit:

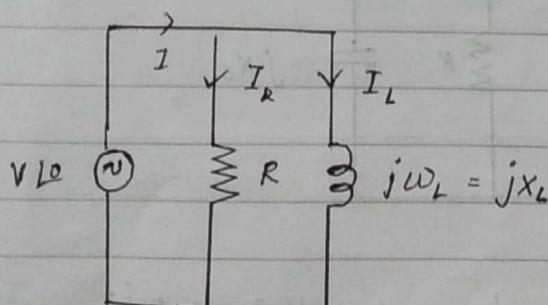

circuit
parallel series
↓ admittance impedance

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jwL} \Rightarrow y = G - jB_L \\ = \sqrt{G^2 + B_L^2} \quad [\tan^{-1} B_L/G] \\ = |y| \angle -\phi$$

$$\tau = \frac{V}{Z} = Vy = V \angle \times y \angle -\phi = I \angle -\phi$$

$$I_R = \frac{V}{Z} = \frac{V}{R} = V G = I_R 10^\circ$$



$$I_L = \frac{V}{jX_L} = -jVB_L = VB_L 1-90^\circ = I_L 1-90^\circ$$

$$V = V_R = V_L = I_R \cdot R = I_L jX_L$$


$$I = I_R + I_L = \frac{V}{R} + \frac{V}{jX_L} = Vy$$

$$\text{where } y = \frac{1}{R} + \frac{1}{jX_L}$$

I_L leading by 90°

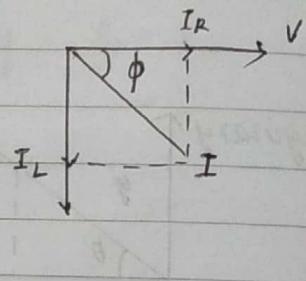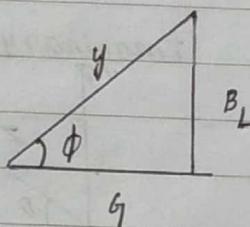

RC parallel circuit:

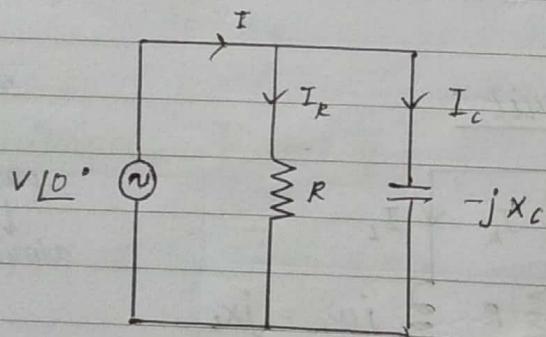

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{-jX_C} \Rightarrow y = G + jB_C$$



$$y = \sqrt{G^2 + B_C^2} \left[\tan^{-1} B_C/G \right]$$

$$y = |y| 1\Phi$$

$$I = \frac{V}{Z} = V 10^\circ y 1\Phi = I 1\Phi$$

$$I_R = \frac{V}{Z} = \frac{V}{R} = Vg = V 10^{\circ} g 10^{\circ} = I_R 10^{\circ}$$
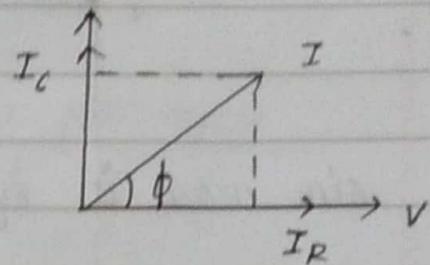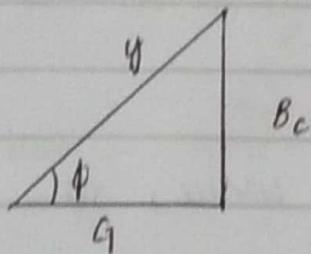
$$I_C = \frac{V}{-jX_C} = jVB_C = V 10^{\circ} B_C 190^{\circ} = I_C 190^{\circ}$$



$$V = V_R = V_C = I_R R = I_C j X_C$$

$$I = I_R + I_C = \frac{V}{R} + V j B_C = V \left[\frac{1}{R} + j B_C \right]$$

1. calculate y, g, B in a circuit consisting 10Ω connected in series with an inductance $0.1H$ and frequency $= 50Hz$

$$R = 10\Omega \quad L = 0.1H \quad f = 50Hz$$

In a RL series circuit, $Z = R + j X_L$

$$\therefore X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 0.1 = 31.4$$

$$Z = 10 + j 31.4$$


$$y = \frac{1}{Z} = \frac{1}{10 + j 31.4}$$

convert this to polar form below.
only in that form we can \times and \div .

θ-axis

2. Find RMS value, Average value, form factor, peak factor.

a)

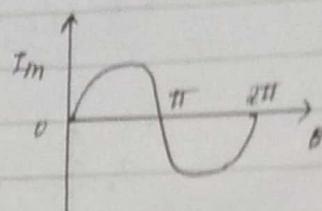

Sine wave is symmetrical wave, so

$$\text{Avg. value: } i = I_m \sin \theta$$

$$I_{\text{ave}} = \frac{\text{Area under one half cycle}}{\text{Period}}$$

$$= \frac{1}{\pi} \int_0^{\pi} i d\theta$$

$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta d\theta$$


$$= \frac{2I_m}{\pi} = 0.637 I_m$$

$$\begin{aligned} \text{RMS value: } I_{\text{rms}} &= \sqrt{\frac{\text{Area under the squared curve of 1 half cycle}}{\text{Period}}} \\ &= \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 d\theta} \\ &= \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta d\theta} \\ &= \frac{I_m}{\sqrt{2}} \end{aligned}$$

$$\text{Form factor: } FF = \frac{\text{RMS}}{\text{Average}} = \frac{0.707 I_m}{0.637 I_m} = 1.11$$

$$\text{Peak factor: } PF = \frac{\text{Peak value}}{\text{RMS value}} = \frac{I_m}{0.707 I_m} = 1.414$$

b)

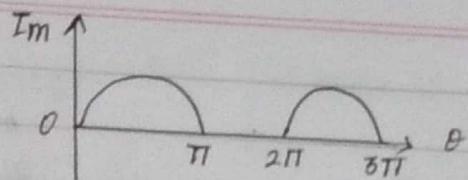

This is an unsymmetrical wave, so

Avg. value: $I_{\text{ave}} = \frac{\text{Area under one full cycle}}{\text{period}}$

$$\begin{aligned}
 &= \frac{1}{2\pi} \int_0^{2\pi} i \, d\theta \\
 &= \frac{1}{2\pi} \left[\int_0^{\pi} i \, d\theta + \int_{\pi}^{2\pi} i \, d\theta \right] \\
 &= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \theta \, d\theta \\
 &= \frac{I_m}{\pi}
 \end{aligned}$$

RMS value: $I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 \, d\theta}$

$$\begin{aligned}
 &= \frac{I_m}{\sqrt{2}}
 \end{aligned}$$

Form factor: $FF = \frac{\text{RMS}}{\text{Average}} = \frac{I_m/\sqrt{2}}{I_m/\pi} = \frac{\pi}{2} =$


Peak Factor: $PF = \frac{\text{Peak value}}{\text{RMS value}} = \frac{I_m}{I_m/\sqrt{2}} = 2$

t-x axis


classmate

Date _____

Page _____

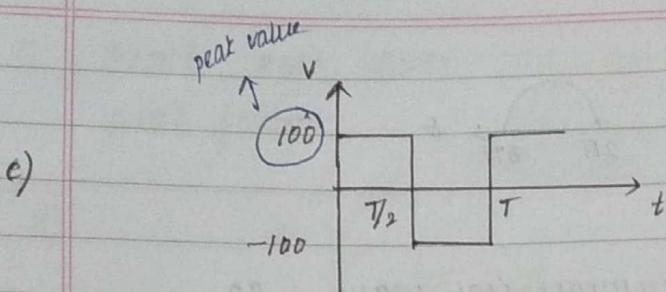

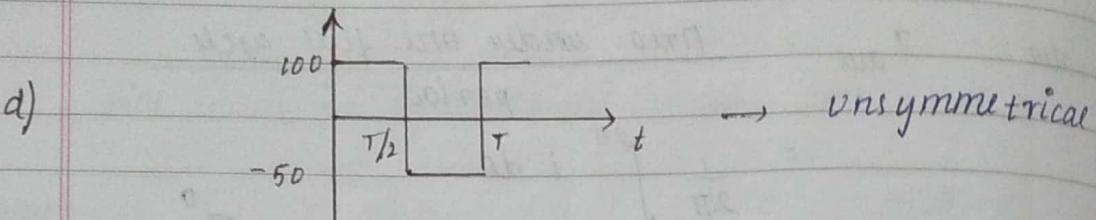→ magnitude of
as amplitude is
same (100), it is
symmetrical.



C. Ans: Area of rectangle = $100 \times T/2$

Period = $T/2$ [as we consider only the half cycle due to symmetry]

$$I_{av} = \frac{100 \times T/2}{T/2} = 100$$

$$I_{rms} = \sqrt{\frac{\text{Area under squared curve}}{\text{period}}} \\ = \sqrt{\frac{100^2 \times T/2}{T/2}} \\ = 100$$

$$FF = 1 \quad \text{and} \quad PF = 1$$

d. Ans: Area of rectangle = $100 \times T/2 + (-50) \times T/2$
= $25T$

Period = T [as we consider full cycle due to unsymmetry]

$$I_{av} = \frac{25T}{T} = 25$$

$I_{RMS} = \sqrt{\frac{\text{Area under squared curve}}{\text{period}}}$


$$= \sqrt{\frac{(100)^2 \times T/2 + (-50)^2 \times T/2}{T}}$$

$$= \sqrt{5000 + 1250} = 79.057$$

$$FF = \frac{\text{RMS}}{\text{average}} = \frac{79.057}{25} = 3.16$$

$$\text{Peak } F = \frac{\text{Peak}}{\text{RMS}} = \frac{100}{79.057} = 1.26$$

RLC parallel circuit:

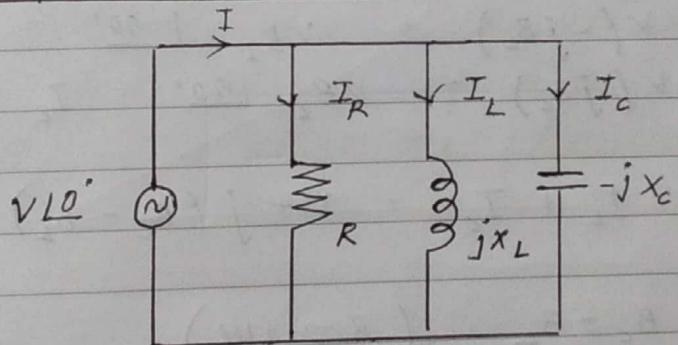

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jx_L} + \frac{1}{-jx_C}$$

$$Y = G - jB_L + jB_C = G + j(B_C - B_L)$$

$$Y = G \pm jB$$

$B = +\omega C$ (capacitive)

$B = -\omega L$ (inductive)

$B = 0$ (resistive)

$$I = VY$$

$$I_R = VG$$

$$I_L = V(-jB_L) \quad I_c = V(jB_c)$$

$$V = I_R R = I_L j\omega_L = I_c j\omega_c$$

$$I_T = I_R + I_L + I_c = \frac{V}{R} + \frac{V}{jX_L} + \frac{V}{jX_C}$$

$$I_T = V \left[\frac{1}{R} + \frac{1}{j\omega_L} - \frac{1}{j\omega_c} \right]$$

$$y = y L\phi \Rightarrow I = VY = V 10 \times y L\phi \\ = I L\phi$$


$$I_R = VG = I_R 10^\circ$$

$$I_L = V(-jB_L) = VB_L -90^\circ = I_L -90^\circ$$

$$I_c = V(jB_c) = VB_c 90^\circ = I_c 90^\circ$$


$$I_B = I_L + I_c = V + j(B_c - B_L) = I_B 190^\circ$$

Case 1: $B = B_c - B_L$ ($B \rightarrow +ve$)

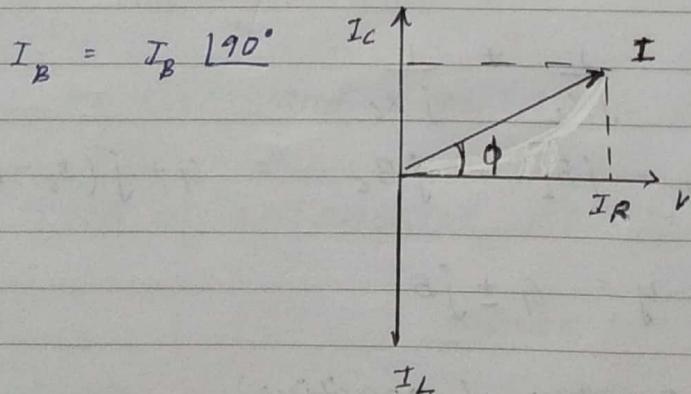


Case 2: $B = B_L - B_c$ ($B \rightarrow -ve$)

$$I_B = I_B -90^\circ$$

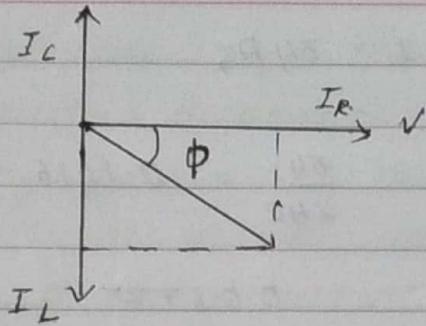

case 3: $B = 0$ $I_B = 0$

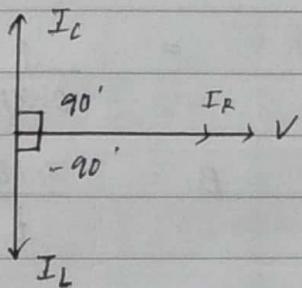

- When a 240V, 50Hz supply is applied to a resistor of 15Ω is connected in parallel with an inductor of total current 22.1A. What value must the frequency have for the total current to be 34A.

$$G = \frac{1}{R} = \frac{1}{15} = 0.067$$

$$B = \frac{1}{X_L} = \frac{1}{C\omega L} = \frac{1}{2\pi f L} = \frac{0.00318}{L}$$

$$\gamma = G - jB$$

$$\gamma = 0.067 - \frac{0.00318}{L}$$

$$\gamma = \frac{I}{V} = \frac{22.1}{240} = 0.09 \rightarrow \text{this method always won't give correct answer}$$

$$\therefore 0.09 = 0.067 - \frac{0.00318}{L}$$


$$L = 0.055$$

university method.

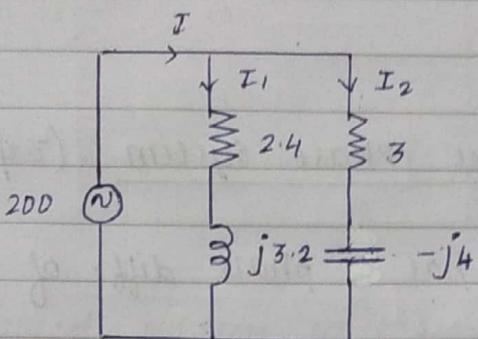2. An inductance $z_1 = (2.4 + j3.2)\Omega$ is in parallel with another inductance

$$z_2 = (3 - j4)\Omega \quad V = 200V$$

Calculate current in each branch, impedance, reactive power, total current, apparent power and power factor.



$$I_1 = \frac{V}{z_1} = \frac{200 \angle 0^\circ}{(2.4 + j3.2)} = \frac{200 \angle 0^\circ}{4 \angle 53.13^\circ} = 50 \angle -53.13^\circ$$

$$I_2 = \frac{V}{z_2} = \frac{200 \angle 0^\circ}{(3 - j4)} = \frac{200 \angle 0^\circ}{5 \angle -53.13^\circ} = 40 \angle 53.13^\circ$$

$$\begin{aligned} I &= I_1 + I_2 = 50 \angle -53.13^\circ + 40 \angle 53.13^\circ \\ &= 30 - j40 + 24 + j32 \\ &= 54 - j8 \\ I &= 54.59 \angle -8.43^\circ \end{aligned}$$

$$Z = \frac{V}{I} = \frac{200 \angle 0^\circ}{54.59 \angle -8.43^\circ} = 3.66 \angle 8.43^\circ = 3.62 + j0.54$$

 When we compare voltage and current sign,

$$\phi = 8.43^\circ \text{ (lagging)}$$


$$\text{Power factor} = \cos \phi = \cos 8.43^\circ = 0.99$$

10.98 X 0.99

$$\begin{aligned}
 \text{True / Real power} &= VI \cos \phi = 10.761 \text{ kW} \\
 \text{Reactive power} &= VI \sin \phi = 10.98 \times 0.99 \quad 1.63 \text{ KVAR} \\
 \text{Total power / Apparent power} &= VI \\
 &= 10980 \quad [-8.43^\circ] \\
 &= (10861.37)^2 + (1609.7)^2 \\
 &= 10.98 \text{ kW}
 \end{aligned}$$

Three Phase system (3ϕ)

Each phase has a phase diff. of 120°

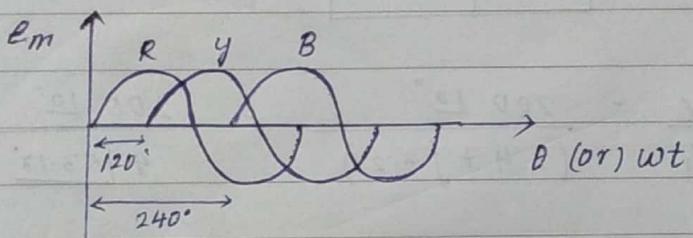


These 3 phases are interconnected to
 → reduce the no. of conductors and spaces.
 → reduce the complexity of circuit.

connections:
 1. star (or) γ -connection
 2. delta (or) Mesh connection

Star (or) γ

Each coil is known as phase winding

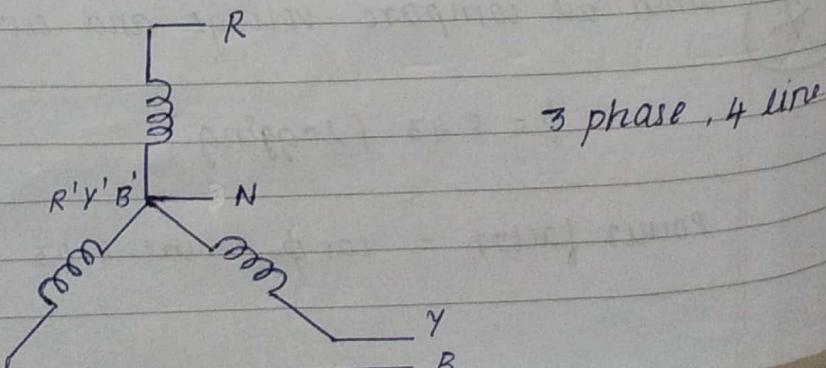

Phase voltage across each coil, is called phase voltage (or) line voltage: Voltage b/w a line and neutral.

E_ϕ (or) $E_\phi \leftarrow$ symbol

E_{RN} , E_{YN} , E_{BN} are the three phase voltages.

Balanced system: 3 loads are same, $-z, z, z$

$$z = a \pm jb$$

Unbalanced system: 3 loads are unequal $\rightarrow z_1, z_2, z_3$

In balanced system, voltages are equal, and displaced by 120° in magnitude

$$|E_{RN}| = |E_{YN}| = |E_{BN}| = E_\phi \rightarrow \text{①}$$

Take E_{RN} as reference voltage

$$\text{For RYB, } E_{RN} = E_\phi L^0$$

$$E_{YN} = E_\phi L^{-120^\circ}$$

$$E_{BN} = E_\phi L^{120^\circ} \text{ (or) } E_\phi L^{-240^\circ}$$

$$\text{For RBY, } E_{RN} = E_\phi L^0$$


$$E_{BN} = E_\phi L^{-120^\circ}$$

$$E_{YN} = E_\phi L^{-240^\circ}$$



Line voltage: Voltage between 2 lines.

(E_L)

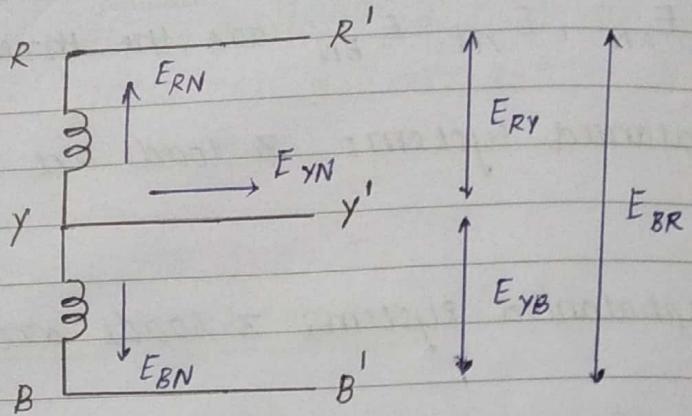$E_{RY}, E_{YB}, E_{BR} \rightarrow$ three line voltages



$$(120^\circ) / (-240^\circ)$$

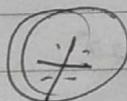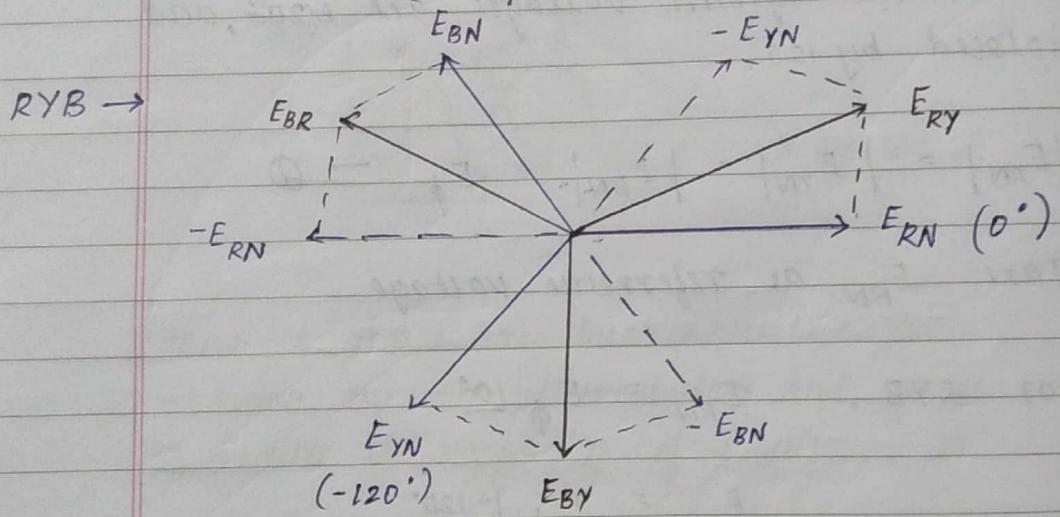

In star connection, $E_\phi \neq E_L$

From diag, $E_{RY} = E_{RN} - E_{YN}$

$$= E_\phi [0^\circ] - E_\phi [-120^\circ]$$

$$= E_\phi (1 [0^\circ]) - E_\phi (1 [-120^\circ])$$

$$= E_\phi (1 + j0) - E_\phi (-0.5 - j0.866)$$

$$= E_\phi (1.55 + j0.866) = 1.753 E_\phi [30^\circ]$$

$$= \sqrt{3} E_\phi [30^\circ]$$

$$\begin{aligned}
 E_{YB} &= E_{YN} - E_{BN} \\
 &= E_\phi \underline{120^\circ} - E_\phi \underline{240^\circ} \\
 &= E_\phi (-0.5 - j0.866) - E_\phi (-0.5 + j0.866) \\
 &= \sqrt{3} E_\phi \underline{-90^\circ}
 \end{aligned}$$

$$\begin{aligned}
 E_{BR} &= E_{BN} - E_{RN} \\
 &= E_\phi \underline{120^\circ} - E_\phi \underline{120^\circ} \\
 &= \sqrt{3} E_\phi \underline{150^\circ}
 \end{aligned}$$

$$E_L = |E_{RY}| = |E_{YB}| = |E_{BR}| = \sqrt{3} E_\phi$$


$$\begin{cases} E_{RY} + E_{YB} + E_{BR} = 0 \\ E_{RN} + E_{YN} + E_{BN} = 0 \end{cases}$$

(*) The phasor sum of line and phase voltages are zero.

Relation b/w E_L and E_ϕ : $E_L = \sqrt{3} E_\phi$


(*) Relation b/w line current (I_L) and phase current (I_ϕ):

$$I_L = I_\phi$$

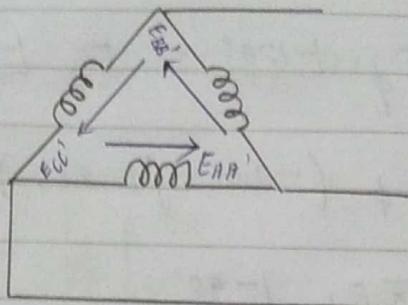Delta connection


120° phase shift

3 phase, 3 wire system

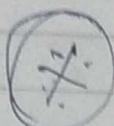

$$E_L = E_\phi$$

$$I_L = \sqrt{3} I_\phi$$

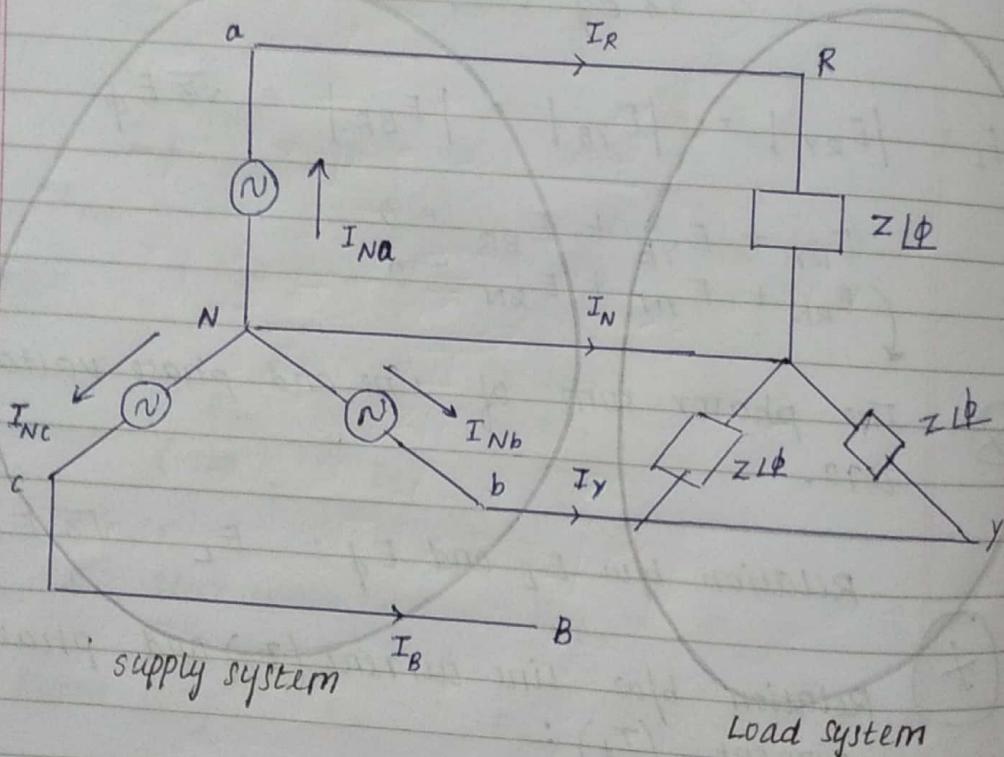Balanced 3 phase star connected system

$$I_{Na} = I_R = I_{R_S}$$

$$I_{Nb} = I_y = I_{y_S}$$

$$I_{Nc} = I_B = I_{B_S}$$

$$I_R = \frac{E_{AN}}{Z} = \frac{E_\phi \angle 0^\circ}{Z \angle \phi^\circ} = I_\phi \angle -\phi$$

$$I_Y = \frac{E_{BN}}{Z} = \frac{E_\phi \angle 120^\circ}{Z \angle \phi^\circ} = I_\phi \angle -120^\circ - \phi$$

$$I_B = \frac{E_{CN}}{Z} = \frac{E_\phi \angle -240^\circ}{Z \angle \phi^\circ} = I_\phi \angle -240^\circ - \phi$$

By applying KCL at neutral point,

$$I_N = I_R + I_Y + I_B$$

1. A balanced star connected load of $(8+j6)$ Ω /phase, is connected to a 3 phase, 230V, 50Hz supply. Find the line current, power factor, reactive volt ampere and total volt ampere.

line voltage $E_L = 230V$

$$Z_\phi = 8 + j6 \Omega = 10 \angle 36.86^\circ V$$

W.K.T in star connection, $E_L = \sqrt{3} E_\phi$

$$E_\phi = \frac{E_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 133 V$$

$$I_L = I_\phi = \frac{|E_\phi|}{|Z_\phi|} = \frac{133}{10} = 13.3 A$$

$$PF = \cos(36.86) = 0.8 \text{ lag}$$

how we decided lag?

NOTE: $z = a + jb \rightarrow$ inductive load \rightarrow lag
 $z = a - jb \rightarrow$ capacitive load \rightarrow lead
 $+ \rightarrow$ lag
 $- \rightarrow$ lead

Total volt ampere (total power) = $\sqrt{3} |V_L| |I_L|$

(*) Real volt ampere / power = $\sqrt{3} |V_L| |I_L| \cos \phi$

Reactive volt ampere / power = $\sqrt{3} |V_L| |I_L| \sin \phi$

Total VA = $\sqrt{3} \times 230 \times 18.3 = 5298$

Real VA = 4289

Reactive VA = 3181

2. A balanced star connected load of $3-j4$ impedance with a 400 V supply. Calculate Real power.

$E_L = 400 \text{ V}$

$Z_\phi = 3-j4 = 5 \angle -53.13^\circ$

$$E_\phi = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = \frac{400}{1.732} = 231 \text{ V}$$

$$I_L = I_\phi = \frac{|E_\phi|}{|Z_\phi|} = \frac{231}{5} = 46.2$$

Real power = $\sqrt{3} |V_L| |I_L| \cos \phi$

$$= \sqrt{3} \times 400 \times 46.2 \times 0.6$$

$$= 19204$$

3. Three impedances each of 10 Ω resistance and 5 Ω inductive reactance are connected in delta to a 400 V, 50 Hz, 3 phase supply. Determine the current in each phase and each line. calculate the total power drawn from the supply and power factor of load.

Given: $R_\phi = 10 \Omega$ $X_\phi = 5 \Omega$

$$|E_L| = |E_\phi| = 400V$$

$$Z_\phi = 10 + j5 = 11.2 \angle 26.6^\circ$$

$$I_\phi = \frac{|E_\phi|}{|Z_\phi|} = \frac{400}{11.2} = 35.7 = 36 A$$

$$I_L = \sqrt{3} I_\phi = 1.732 \times 36 = 62.35 A$$

$$\text{Total power} = \sqrt{3} |V_L| |I_L| = 1.732 \times 400 \times 62.35 \\ = 43,197.5$$

$$\text{power factor} = \cos \phi = \cos 26.6 = 0.9 \text{ lag}$$

