

SCHOOL OF COMPUTING SCIENCE ENGINEERING  
**Basic Electrical Engineering – EEE101L**  
 DIGITAL ASSIGNMENT -2  
**Submit DA2 on or before 10th May 2022**

1. If  $M=0.2$  H and  $v_s = 12 \cos 10t$  in the circuit of Fig.1, find and calculate the currents  $i_1$  and  $i_2$ .

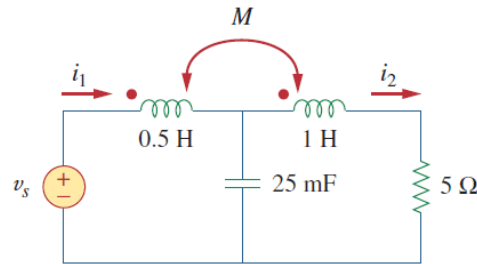


Fig. 1

2. Obtain the Thevenin equivalent circuit for the circuit in Fig. 2 at terminals a-b.

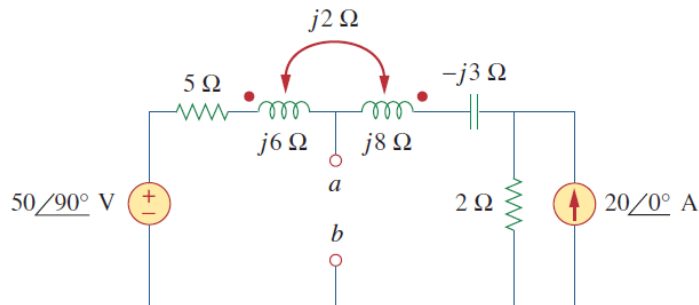


Fig. 2

3. Find current  $I_o$  for the circuit shown in Fig. 3



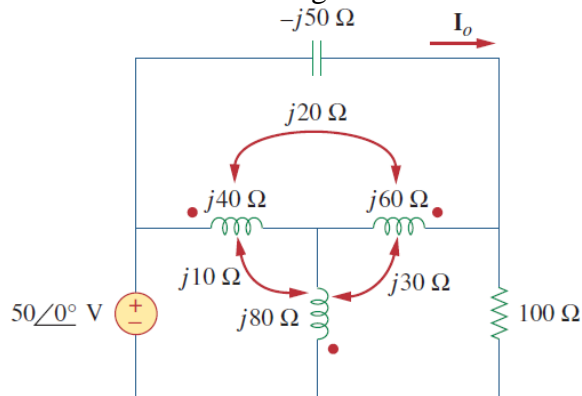


Fig. 3

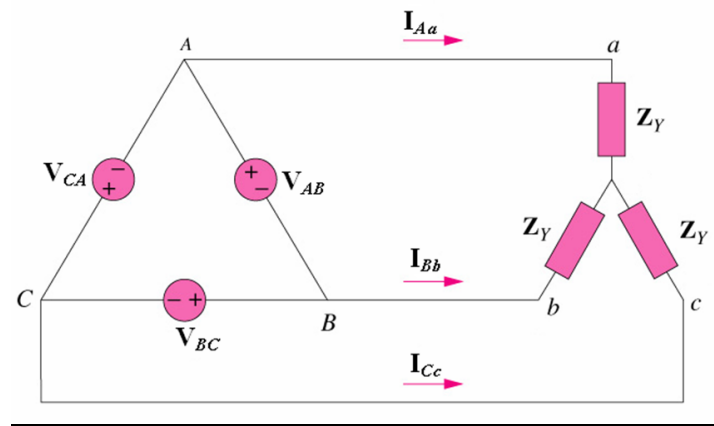
4. A balanced Y - connected load with a phase impedance  $40 + j25 \Omega$  is supplied by a balanced, positive-sequence  $\Delta$ -connected source with a line voltage of 210V. Calculate the phase currents. Use  $V_{AB}$  as reference. Draw the phasor diagram.



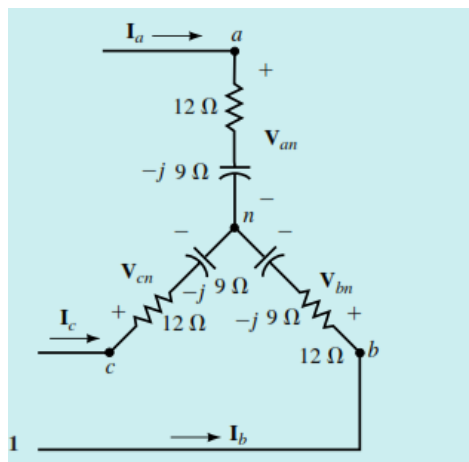5. For Figure, suppose  $V_{an} = 120 \text{ V} \angle 0^\circ$ . A) Compute  $I_a$ , then determine  $I_b$  and  $I_c$  by inspection. b) Draw the phasor diagram



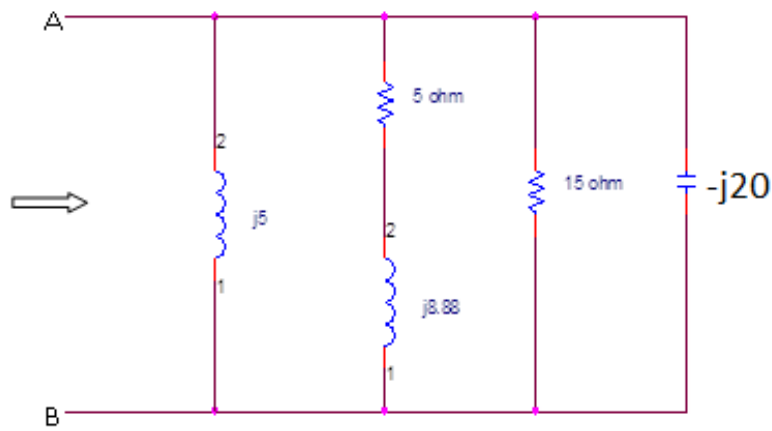6. Find the  $Z_{eq}$  for the circuit shown in below Fig.



7. Consider the circuit of below Fig.

- i) Find  $Z_T$ .
- ii) Determine the current  $I_1$ ,  $I_2$  and  $I_3$ .
- iii) Calculate the total power provided by the voltage source.

