

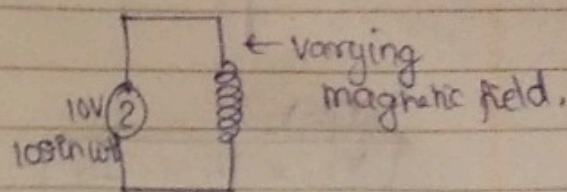


MODULE 3: MAGNETIC CIRCUITS

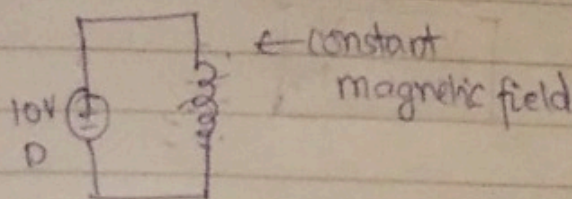* $\mathcal{E} = -N \frac{d\phi_B}{dt}$ [Faraday's law]



Transformer

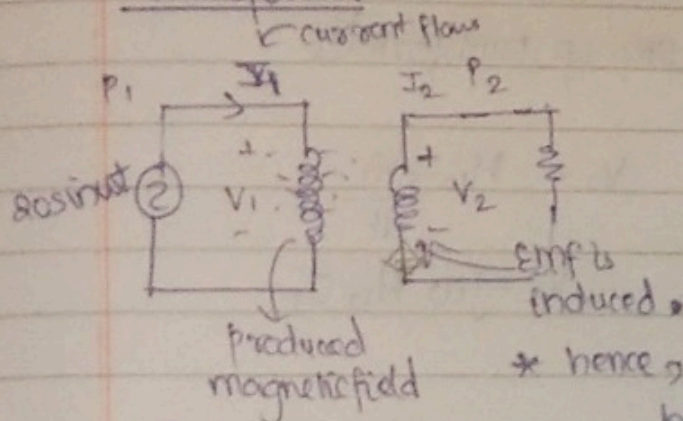


we use $\frac{V^2}{R}$ formula
but not $I^2 R$ formula

* hence, $V_2 \propto I_1$

hence can be thought of as
current dependant voltage source.

* similarly, due to inductor I_2 , current V_1 is induced
in inductor L_1 .

~~$V_1 \propto I_2$~~ $V_1 \propto I_2$

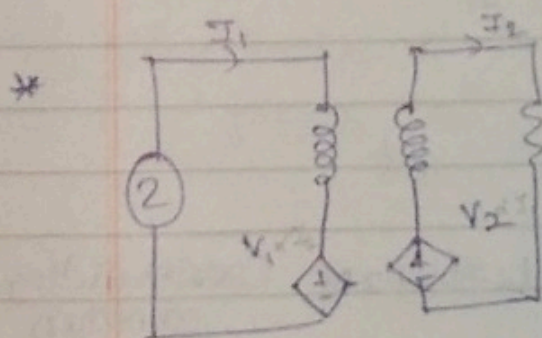

$\phi_1, \phi_2 \leftarrow$ magnetic field produced
in coil 1 & 2.

$\phi_{21} \leftarrow \vec{B}$ induced in coil 1 due to
coil 2.

* $V_1 = N_1 \frac{d\phi_1}{dt} \Rightarrow V_1 = N_1 \cdot \frac{d\phi_1}{di_1} \cdot \frac{di_1}{dt}$

hence, $L_1 = N_1 \frac{d\phi_1}{di_1} = \text{self inductance} \left[\because \mathcal{E} = L \frac{di}{dt} \right]$

Voltage across

L_2 due to I_1 $V_{12} = N_2 \frac{d\phi_{12}}{dt} \Rightarrow V_{12} = N_2 \cdot \frac{d\phi_{12}}{di_1} \cdot \frac{di_1}{dt}$

hence $M = \text{mutual inductance}$

$M = N_2 \frac{d\phi_{12}}{di_1}$

* $M_{12} = M_{21}$
 $\Phi_{12} = \Phi_{21}$

* $e_1 = e_2 \in \text{No. of turns/length.}$
 * $V_1 = N_1 \times e_1$
 $V_2 = N_2 \times e_2$


hence dividing above 2 eq.

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$V_1 I_1 = V_2 I_2$$


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

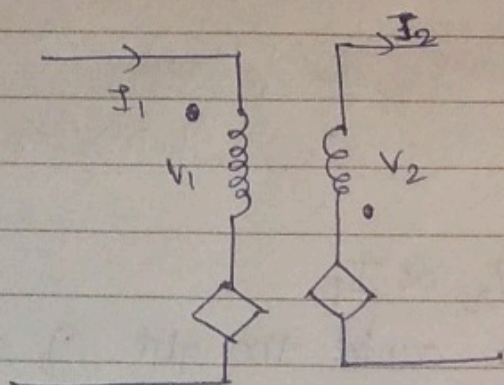if $N_1 > N_2 \Rightarrow V_1 > V_2 \in \text{step down transform}$
 $N_1 < N_2 \Rightarrow V_1 < V_2 \in \text{step up transformer}$




$$V_2 = M_{12} \frac{di_1}{dt}$$


$$V_2 = j\omega M_{12} I_1$$

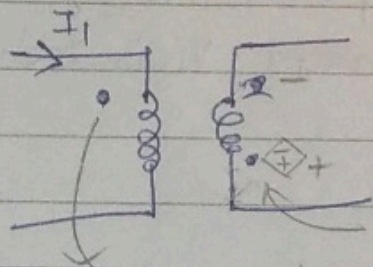

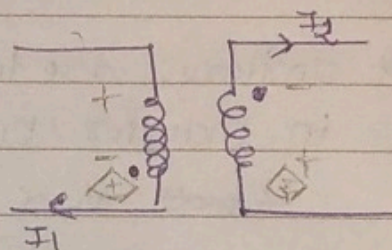
I_1 is entering the dot, hence '+' polarity is in the dot of opposite inductor



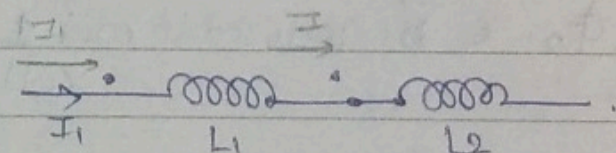I_1 is leaving dot, hence '-' polarity in the opposite dot


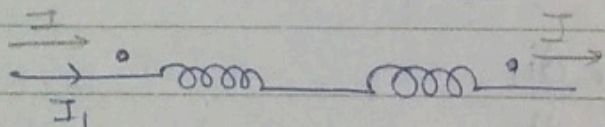
$$L = L_1 + L_2 + 2M \quad (\text{series aiding connection})$$




$$L = L_1 + L_2 - 2M$$

(series opposing connection)

Dot represents that the Inductors are mutually coupled.

H.W Determine the voltage V_o .

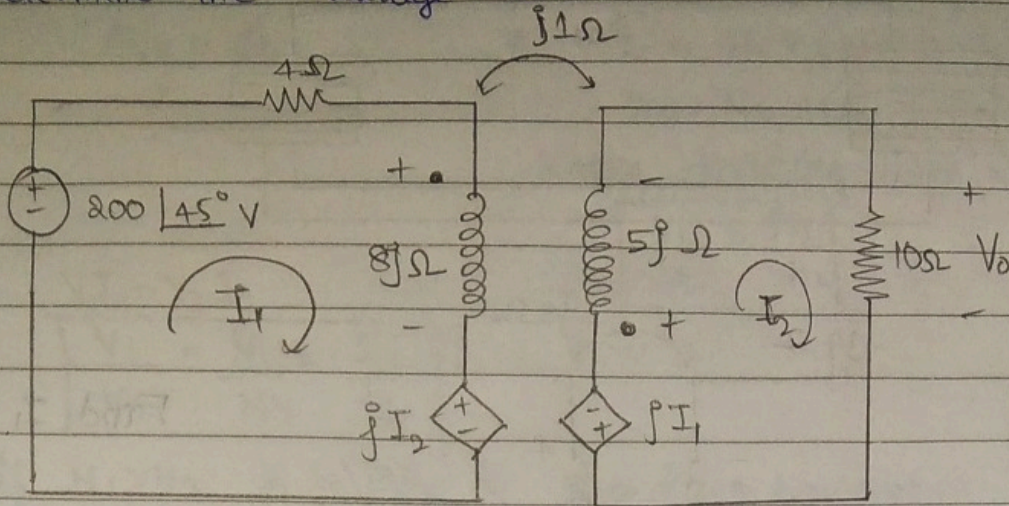

solution: applying KVL along loop 1:-

$$-200\angle 45^\circ + 4I_1 + 8jI_1 + 1jI_2 = 0$$

$$I_1(4 + 8j) + 1jI_2 = 200\angle 45^\circ \quad \text{--- (1)}$$

applying KVL along loop 2:-

$$10I_2 + jI_1 + 5jI_2 = 0$$

$$jI_1 + (10 + 5j)I_2 = 0 \Rightarrow I_1 = -\frac{(10 + 5j)I_2}{j}$$

From (1) $\Rightarrow -\frac{I_2(10 + 5j)(4 + 8j)}{j} + jI_2 = 200\angle 45^\circ$


$$-I_2 100 + jI_2 = 200\angle 45^\circ$$

$$I_2(-100 + j) = 200\angle 45^\circ \Rightarrow I_2 = \frac{200\angle 45^\circ}{100\angle 180^\circ}$$


$$I_2 = 2\angle -135^\circ \text{ A}$$

$$V_o = 10 I_2 = 20\angle -135^\circ \text{ V}$$

example 1 calculate mesh currents:

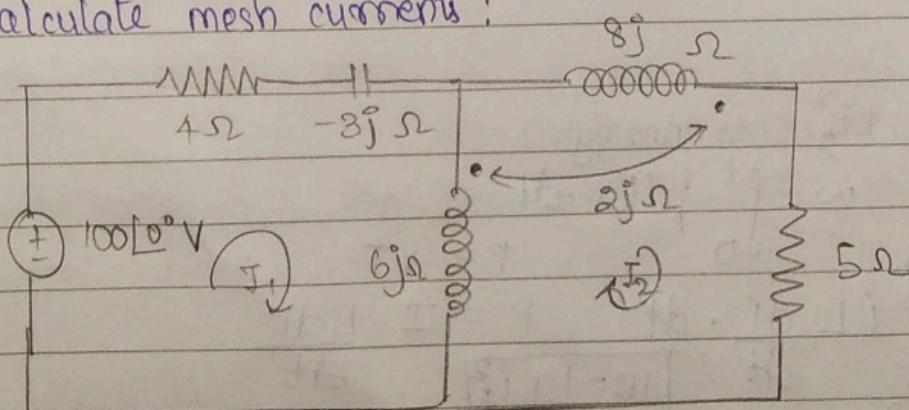

redrawing the circuit.

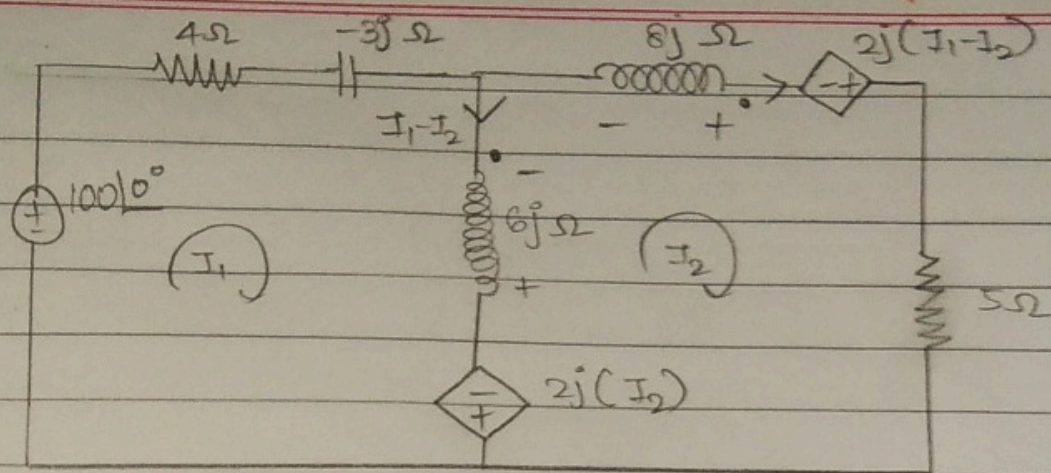

solution

applying KVL across loop 1 :-

$$\begin{aligned}
 -100 \angle 0^\circ + 4I_1 - 3jI_1 + 6j(I_1 - I_2) - 2jI_2 &= 0 \\
 -100 + 4I_1 - 3jI_1 - 6jI_1 + 6jI_2 - 2jI_2 &= 0 \\
 -100 + I_1(4 - 9j) + I_2(4j) &= 0 \quad \text{--- ①}
 \end{aligned}$$

applying KV across loop 2 :-

$$\begin{aligned}
 2jI_2 + 6j(I_1 - I_2) - 8jI_2 - 2j(I_1 - I_2) + 5I_2 &= 0 \\
 2jI_2 + 6jI_1 - 6jI_2 - 8jI_2 - 2jI_1 + 2jI_2 + 5I_2 &= 0 \\
 I_2(2j - 6j - 8j + 2j + 5) + I_1(6j - 2j) &= 0 \\
 I_2(-10j + 5) + I_1(4j) &= 0 \\
 I_1 &= \frac{(5 + 10j)I_2}{4j}
 \end{aligned}$$

$$\text{From ①} \Rightarrow \frac{-(5 - 10j)(4 - 9j)I_2 + I_2(4j)}{4j} = 100$$

$$\begin{aligned}
 (70 + 85j - 16)I_2 &= 100 \Rightarrow I_2 = \frac{100 \angle 0^\circ}{54 + 85j} \\
 I_2 &= \frac{100 \angle 0^\circ}{100 \angle 57.572^\circ} \Rightarrow \boxed{I_2 = 1 \angle -57.572^\circ \text{ A}}
 \end{aligned}$$

$$\begin{aligned}
 I_1 &= \frac{11.18 \angle 116.56^\circ \times 1 \angle -57.572^\circ}{4 \angle 90^\circ} \\
 \boxed{I_1 &= 2.795 \angle -31.012^\circ \text{ A}}
 \end{aligned}$$

* $W = \frac{1}{2} L i^2$ € energy

$$W = \int_0^t p(t) dt$$

$$P = VI$$

$$W = \int_0^t i L \frac{di}{dt} \cdot dt$$

$$P = I \frac{L di}{dt}$$

$$W = \frac{1}{2} L i^2$$

* $W = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2$

* Coupling coefficient = k ; $M = k \sqrt{L_1 L_2}$
 * if $k=1$: 100% efficiency.