

# Lecture 1: Basic Circuit Elements and Sources

Tuesday, February 15, 2022

## Charge

- Electric charge is the physical property of matter that causes it to experience a force when placed in an electromagnetic field.

## Current

- Flow of electrons.
- Unit: ampere (A)

## Potential Difference

- The difference of electrical potential between two points.
- Unit: volt (V)

## Resistance

- Measure of the opposition to current flow in an electrical circuit.
- Unit: Ohm ( $\Omega$ )

## Resistivity

- Resistance of a conducting material per unit length with unit area of cross section.
- Formula:  $\rho = \frac{RL}{A}$
- Unit:  $\Omega \text{ m}^{-1}$

## Conductivity

- Measure of electrical conduction and it shows the ability of a material to pass a current.
- Formula:  $\sigma = \frac{1}{\rho}$
- Unit:  $\text{S m}^{-1}$


## Basic Components

- Resistor: Used to reduce current flow.
- Inductor: Used to store energy in a magnetic field when electric current flows through it.
- Capacitor: Used to store energy when it is connected to a battery.

# Lecture 2: Ohm's Law

Thursday, February 17, 2022

## Basic Terms in a circuit:

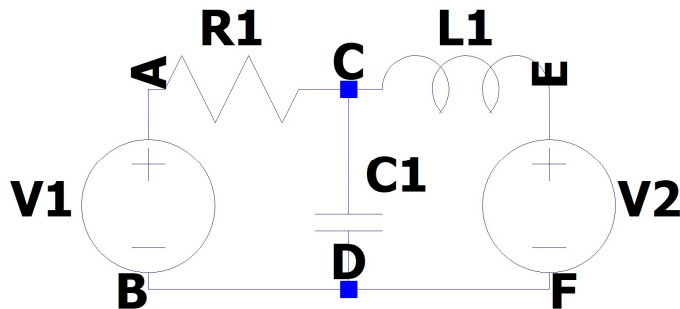

### Active Circuit Elements

Voltage and Current Source

### Passive Circuit Elements

Resistor, Inductor and Capacitor

### Branch

- It is the part of the network which connects the various points of the network with one another.
- Example: AC, CE, EF, etc.

### Junction Point

- The point where two or more branches are connected.
- Example: A, B, C, D, E, F.

### Node

- The point where two or more elements (Passive circuit Element) are joined.
- Example: C

### Mesh or Loop


- It is the closed path that forms a mesh or loop.
- Example: ACDBA, CEFDC, ACEFDBA.

## Ohm's Law

Here, the temperature is constant.

$$V \propto I$$

$$V = IR$$

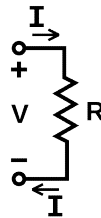

## Power

$$P = VI = I^2 R = \frac{V^2}{R}$$

## Energy

$$W = Pt$$

## Resistors in series and parallel:

When two or more resistors are connected in series,

$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$

$$IR = I(R_1 + R_2 + R_3)$$

$$\boxed{R = R_1 + R_2 + R_3}$$

**R1**

**R2**

**R3**

$$R = R_1 + R_2 + R_3$$

Don't consider  $R_3$  below,


$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$I = \frac{V}{R_1 + R_2}$$

$$V_1 = \frac{VR_1}{R_1 + R_2}$$

$$V_2 = \frac{VR_2}{R_1 + R_2}$$

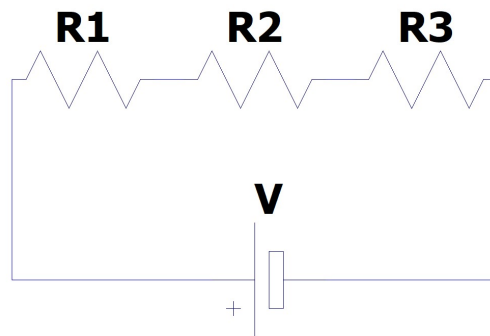

This is called as voltage divider rule in series circuit.

When two or more resistors are connected in parallel,

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Don't consider  $R_3$  below,

$$I = I_1 + I_2$$


$$V = I_1 R_1 = I_2 R_2$$

$$I_2 = \frac{I_1 R_1}{R_2}$$

$$I = I_1 + \frac{I_1 R_1}{R_2}$$

$$I_1 = I \left( \frac{R_2}{R_1 + R_2} \right)$$

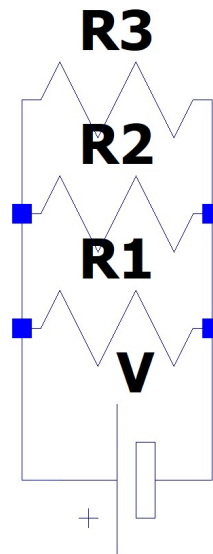
$$I_2 = I \left( \frac{R_1}{R_1 + R_2} \right)$$




This is called as current divider rule in parallel circuit.

### Example Problems:

1.

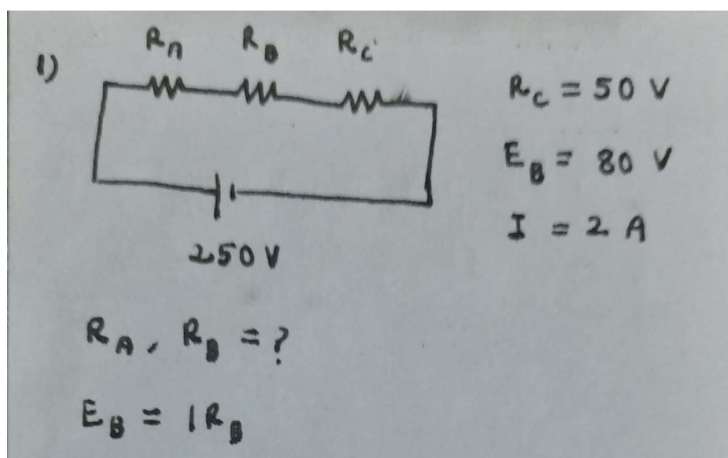

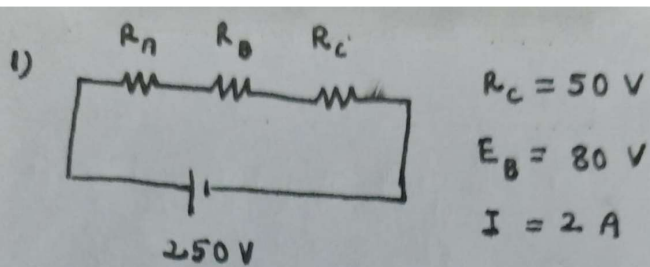

$$R_A, R_B = ?$$

$$E_B = IR_B$$

$$R_B = \frac{E_B}{I} = \frac{80}{2} = \boxed{40 \Omega}$$

$$E_B = \frac{E R_B}{R_A + R_B + R_C}$$

$$R_A + R_B + R_C = \frac{E R_B}{E_B}$$

$$\begin{aligned}
 R_A &= \frac{E R_B}{E_B} - (R_B + R_C) \\
 &= \frac{250 (40)}{80} - (40 + 50) \\
 &= 125 - 90
 \end{aligned}$$

$$R_A = 35 \Omega$$

2. Two resistors connected in parallel across 200 V supply, 10 A current. If the power dissipated in one resistor is 800 W, find the value of other resistor.

Given,

$$V = 200 \text{ V} ; I = 10 \text{ A} ; P = 800 \text{ W}$$

Soln,

$$P = VI = \frac{V^2}{R}$$

$$P = 200(10)$$

$$P_t = 2000 \text{ W}$$

$$P_2 = P_t - P_1$$

$$P_2 = 2000 - 800$$

$$P_2 = 1200 \text{ W}$$

$$P_2 = \frac{V^2}{R_2}$$

$$R_2 = \frac{V^2}{P_2}$$

$$R_2 = \frac{200 \times 200}{1200}$$

$$R_2 = 33.33 \Omega$$